


ENEE236 & 241


Analog Electronics


L5 Diode Applications 3
Instructor: Nasser Ismail


Dc Power Supply

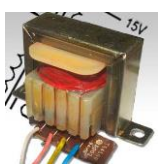
- All electronic circuits and systems require a stable source of dc voltage and current (or dc power) to operate correctly.



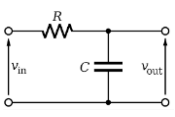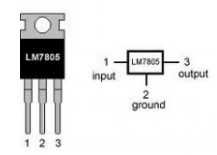
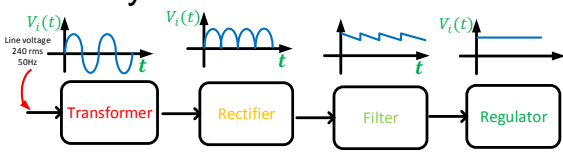














Block diagram of a dc power supply.

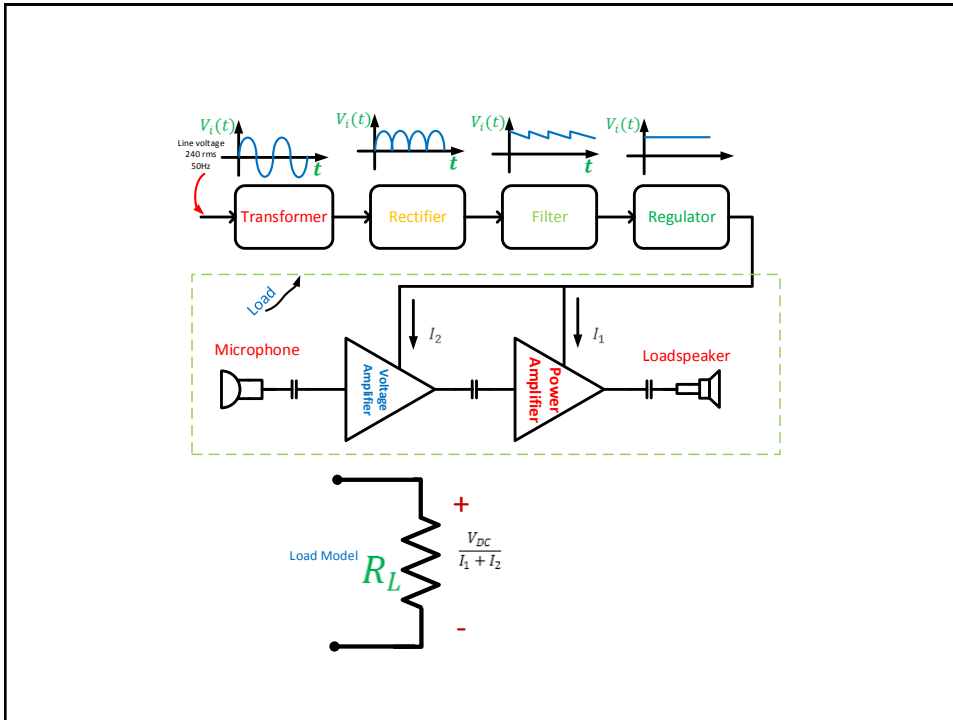

Designing a power supply

1) Transformer

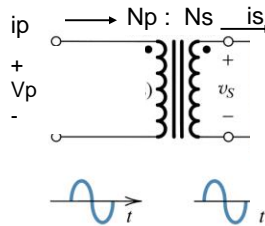

Usually steps down type to decrease the amplitude of the ac line voltage

$$\frac{V_p}{V_s} = \frac{N_p}{N_s}$$


$$\frac{i_s}{i_p} = \frac{N_p}{N_s}$$

$$n = \frac{N_s}{N_p} \text{ transformer turns ratio}$$

$$\Rightarrow V_s = nV_p$$

Designing a power supply


2) Rectifier

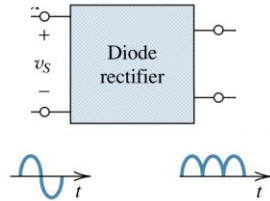


- Used to convert ac voltage (with zero average value) to pulsating dc voltage (non zero average)
- Rectifiers are two types:
 - a) Half Wave Rectifier
 - b) Full Wave Rectifier
 - Bridge Full Wave Rectifier
 - Center Tapped Transformer Full Wave Rectifier

Half Wave Rectifier

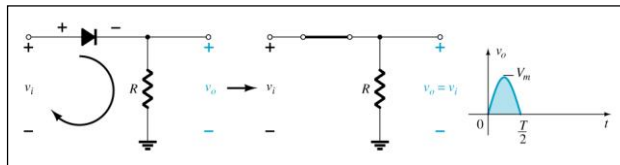1) When $V_i(t) > 0$,
Diode is ON
 $V_o = V_i$



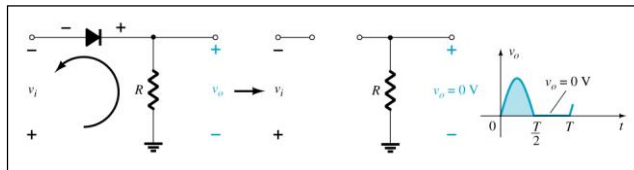2) When $V_i(t) < 0$,
Diode is OFF
 $V_o = 0$



The diode conducts only when it is forward biased, therefore only half of the AC cycle passes through the diode to the output.

$$V_{AVG} = \frac{1}{T} \int_0^T V_m \sin(\omega t) dt$$

Half Wave Rectifier

$$\begin{aligned}
 V_{AVG} &= \frac{1}{T} \int_0^T V_m \sin(\omega t) dt \\
 &= \frac{1}{2\pi} \int_0^\pi V_m \sin(\theta) d\theta \\
 &= \frac{1}{2\pi} [-V_m \cos(\theta)]_0^\pi = \frac{V_m}{2\pi} [-\cos(\pi) - (-\cos(0))]
 \end{aligned}$$


$$\begin{aligned}
 V_{AVG} &= \frac{V_m}{2\pi} [-(-1) - (-1)] \\
 &= \frac{2V_m}{2\pi} = \frac{V_m}{\pi} \cong 0.318V_m
 \end{aligned}$$

$$T = T_o \text{ and } f = f_o$$

(period and frequency of the rectified waveform is the same as ac input)

Important Electrical Ratings

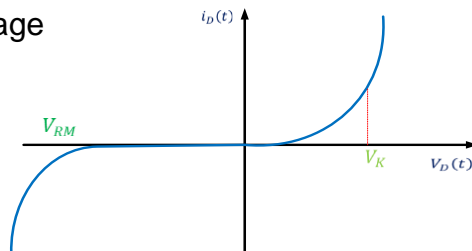- I_{FM} = maximum forward current
- I_{FM} = maximum average current that can safely be sustained by the diode when it is forward biased
- V_{RM} = maximum reverse voltage
- V_{RM} = maximum voltage that can be applied to the diode in the reverse bias polarity before voltage break down occur
- PIV \equiv Peak Inverse Voltage
- PIV = V_{RM}



PIV (For Half Wave Rectifier)

Because the diode is only forward biased for one-half of the AC cycle, it is also reverse biased for one-half cycle.

It is important that the reverse breakdown voltage rating of the diode be high enough to withstand the peak, reverse-biasing AC voltage.


$$V_D(t) = V_i(t)$$

$$V_D(t)_{\max} = -V_m$$

$$\text{PIV} = -V_m$$

$$I_{FM} = \frac{V_{AVG}}{R_L}$$

$$I_{FM} = \frac{V_m}{\pi R_L}$$

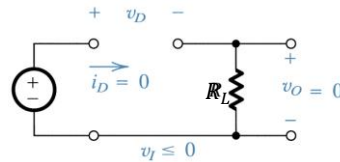


Full-Wave Rectification

The rectification process can be improved by using a full-wave rectifier circuit.

Full-wave rectification produces a greater DC output:

$$\text{Half-wave: } V_{dc} = 0.318V_m$$

$$\text{Full-wave: } V_{dc} = 0.636V_m$$

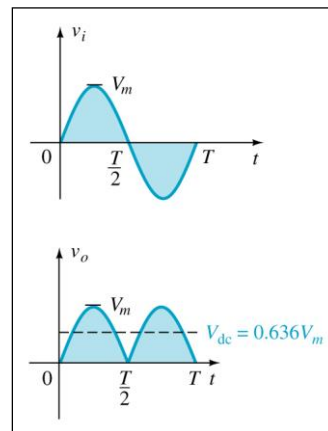

Bridge Full-Wave Rectifier



A full-wave rectifier with four diodes that are connected in a bridge configuration

1) When $V_i(t) > 0$,
D2, D3 are ON
D1, D4 are OFF

$$\Rightarrow V_o(t) = V_i(t)$$

2) When $V_i(t) < 0$,
D2, D3 are OFF
D1, D4 are ON


$$\Rightarrow V_o(t) = -V_i(t)$$

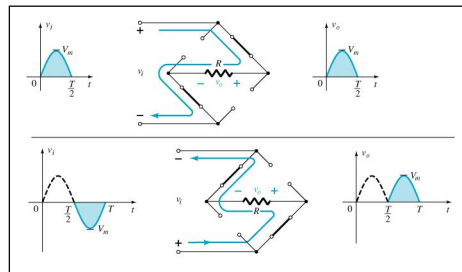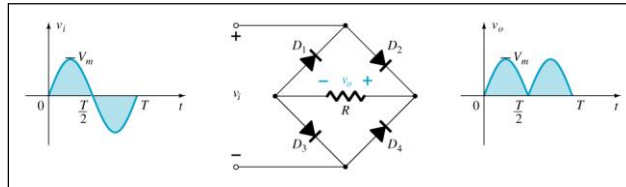

Bridge Full-Wave Rectifier

$$V_{AVG} = \frac{1}{T} \int_0^T V_m \sin(\omega t) dt$$
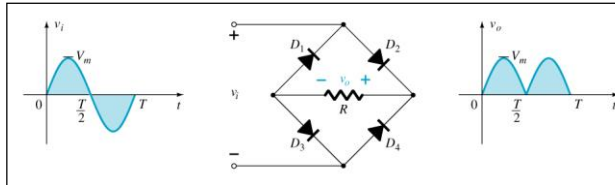
$$= \frac{1}{\pi} \int_0^{\pi} V_m \sin(\theta) d\theta$$



$$V_{AVG} = \frac{2V_m}{\pi} \cong 0.636V_m$$

$$T = \frac{T_o}{2} \text{ and } f = 2f_o$$

(period and frequency of the rectified waveform is not the same as ac input)


PIV for each of the 4 diodes

For ideal diode


$$V_{D1}(t) = -V_i(t)$$

$$V_{D1}(t)_{\max} = -V_m$$


$$\text{PIV} = -V_m$$

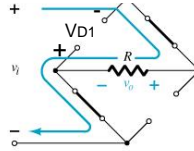

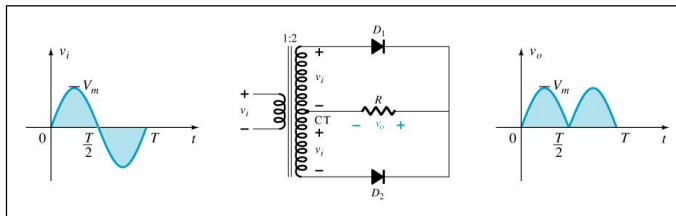Center Tapped Transformer Full-Wave Rectifier



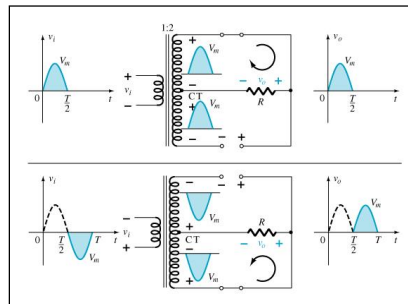Requires two diodes and a center-tapped transformer



CT Transformer Full-Wave Rectifier

1) When $V_i(t) > 0$,

D1 is ON

D2 is OFF

$$\Rightarrow V_o(t) = V_i(t)$$

2) When $V_i(t) < 0$,


D1 is OFF

D2 is ON


$$\Rightarrow V_o(t) = -V_i(t)$$

$$V_{AVG} = \frac{2V_m}{\pi} \cong 0.636V_m$$
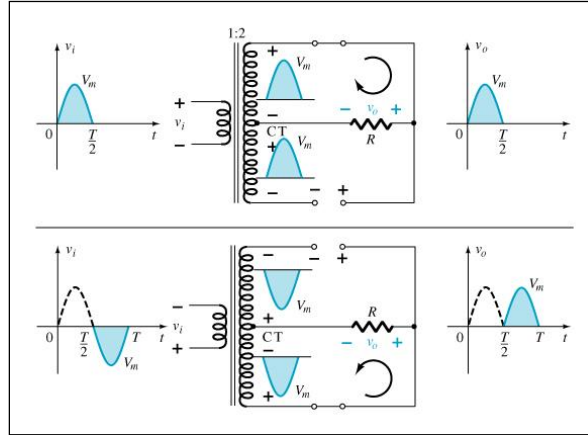
$$T = \frac{T_o}{2} \text{ and } f = 2f_o$$





3) Filter

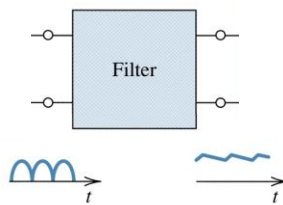

- One of dc power supply components
- Used to smooth out (remove) the pulsating DC produced by the rectifiers and to pass only the DC component (average value; mean value)

Simplified Circuit


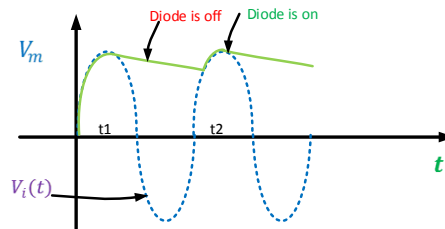
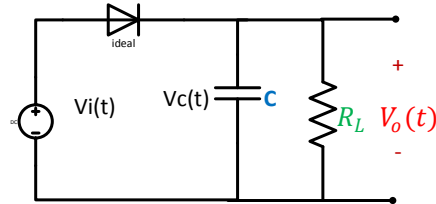
- A) when $V_i(t) > V_c(t)$;
Diode is on and $V_o(t) = V_c(t) = V_i(t)$
- B) when $V_i(t) < V_c(t)$;
Diode is off and the capacitor starts discharging



- Ripple factor is an indicator for the effectiveness of the filter


$$r = \frac{RMS(ripple\ voltage)}{Average\ value\ of\ the\ output\ signal} \times 100\%$$

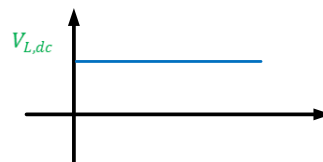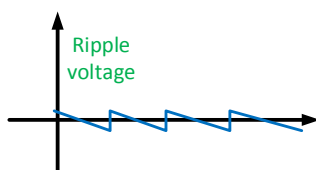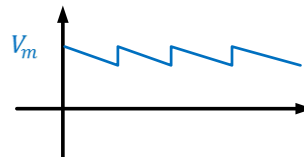- The output signal can be approximated as shown



Example

Find average output voltage?

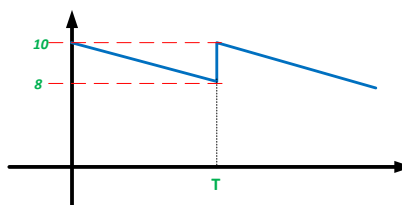

$$V_{O,DC} = V_{O,AVG} = \frac{1}{T} \int_0^T V_O(t) dt$$

$$= \frac{1}{T} (\text{Area})$$

$$= \frac{1}{T} \left(8T + \frac{2T}{2} \right) = 9 \text{ V}$$

OR

$$V_{O,DC} = V_m - \frac{1}{2} V_{Lr,p-p}$$

where $V_m = 10$
 $V_{Lr,p-p} = 2$

$$V_{O,DC} = 10 - \frac{1}{2} \cdot 2 = 9 \text{ V}$$

- Also for a triangular signal,

$$\text{RMS Value} = \frac{\text{Peak Value}}{\sqrt{3}}$$

OR

$$\text{RMS Value} = \frac{\text{Peak to peak Value}}{2\sqrt{3}} = \frac{V_{Lr,p-p}}{2\sqrt{3}}$$

$$\therefore r \% = \frac{\frac{V_{Lr,p-p}}{2\sqrt{3}}}{V_m - \frac{1}{2} V_{Lr,p-p}} \cdot 100\%$$

⇒ To Determine the ripple factor we need to find the peak to peak ripple $V_{Lr,p-p}$

Ripple Factor

For $t_2 > t > t_1$

$$V_L(t) = V_m e^{\frac{-(t-t_1)}{RC}}$$

$$V_{Lr,p-p} = V_L(t_1) - V_L(t_2)$$

$$V_{Lr,p-p} = V_m - V_m e^{\frac{-(t_2-t_1)}{RC}}$$

$$V_{Lr,p-p} = V_m \left[1 - e^{\frac{-(t_2-t_1)}{RC}} \right]$$

using $e^{-x} \cong 1 - x$

ENEE236 – Analog Electronics

using $e^{-x} \cong 1 - x$

$$V_{Lr,p-p} = V_m \left[1 - e^{\frac{-(t_2-t_1)}{RC}} \right] \Rightarrow V_{Lr,p-p} = V_m \left(\frac{(t_2-t_1)}{RC} \right)$$

$$V_{L,dc} = V_m - \frac{1}{2} V_{Lr,p-p}$$

ENEE236 – Analog Electronics

a) For Half Wave Rectifier

$$t_2 - t_1 \cong T_o = \frac{1}{f_o}$$

$$V_{Lr,p-p} = V_m \left(\frac{T_o}{RC} \right) = V_m \left(\frac{1}{f_o RC} \right)$$

$$V_{L,dc} = V_m \left(1 - \frac{1}{2f_o RC} \right)$$

$$(V_{L,r})_{RMS} = \frac{V_{Lr,p-p}}{2\sqrt{3}}$$

$$(V_{L,r})_{RMS} = \frac{V_m}{2\sqrt{3}f_o RC}$$

$$\therefore r \% = \frac{(V_{L,r})_{RMS}}{V_{L,dc}} 100\%$$

$$\therefore r \% = \frac{1}{\sqrt{3}[2f_o RC - 1]} 100\%$$

ENEE236 – Analog Electronics

b) For Full Wave Rectifier

$$t_2 - t_1 \cong \frac{1}{2} T_o = \frac{1}{2f_o}$$

$$V_{Lr,p-p} = V_m \left(\frac{T_o}{2RC} \right) = V_m \left(\frac{1}{2f_o RC} \right)$$

$$V_{L,dc} = V_m \left(1 - \frac{1}{4f_o RC} \right)$$


$$(V_{L,r})_{RMS} = \frac{V_{Lr,p-p}}{2\sqrt{3}}$$

$$(V_{L,r})_{RMS} = \frac{V_m}{4\sqrt{3}f_o RC}$$

$$\therefore r \% = \frac{1}{\sqrt{3}[4f_o RC - 1]} 100\%$$

Example

► Find the ripple factor r

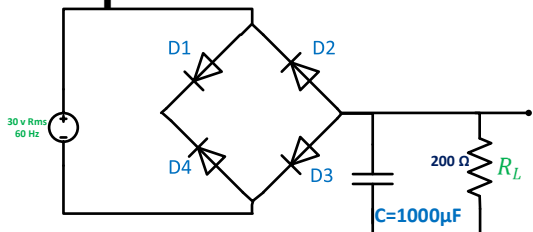

- $V_{L,dc} = V_m - \frac{1}{2} \frac{V_m}{2f_o R_{LC}} = 41.54 \text{ v}$
- $V_{Lr,p-p} = \frac{V_m}{2f_o R_{LC}} = 1.7677 \text{ v}$
- RMS (ripple voltage) = $\frac{V_{Lr,p-p}}{2\sqrt{3}} = 0.51 \text{ v rms}$

$\therefore r = \frac{0.51}{41.54} \times 100\%$

$r = 1.2277 \%$