

ENEE236

Analog Electronics

L6 Diode Applications 4
Instructor: Nasser Ismail

ENEE236 – Analog Electronics

Zener Diode Simple Voltage Regulator

- *The Zener is used as a voltage regulator to maintain a constant dc output under variations in load current and ac line voltage*
- *It can also be used as protection device against overvoltage*
- *Analysis starts by defining state of diode followed by using appropriate model, then find unknown quantities*

ENEE236 – Analog Electronics

Voltage Regulator

A voltage regulator supplies constant voltage to a load.

ENEE236 – Analog Electronics

Zener Diode V-I Curve

- In data sheet , we have I_{ZT} , V_{ZT}
- Zener currents will be assumed positive if passing from cathode to Anode
- If $I_Z < I_{ZK}$ zener will act as an open circuit
- If $I_Z > I_{Zmax}$ zener will be damaged

• If $I_{ZK} < I_Z < I_{Zmax}$ zener will be in voltage regulation (zener) region

EENE236 – Analog Electronics

Zener Diode Operation Regions

Region (1)
 > When $V_{AK} > 0$, zener acts as regular diode ON
 > Region (2)
 When $V_{ZK} < V_{AK} < 0$, zener acts as regular diode OFF
 > Region (3)
 When $V_{ZK} > V_{AK}$, This is the intended operating region, and the zener acts as a voltage regulator
 > And $V_Z = V_{KA}$, it can be replaced by either a battery or a battery in series with resistor r_Z

EENE236 – Analog Electronics

Zener Diode Operation & Models

The Zener is a diode that is operated in reverse bias at the Zener Voltage (V_Z).

Conditions for zener diode to operate in the breakdown (Zener/ON) region When

1. Cathode is more positive than anode
2. $V_{th} \geq V_Z$
3. $I_Z > I_Z(\min)$
4. $I_Z < I_Z(\max)$

==> Voltage across the Zener is V_Z

- Zener current: $I_Z = I_S - I_L$
- The Zener Power: $P_Z = V_Z I_Z$

ENEE236 – Analog Electronics

Zener Diode Models

1. *Ideal Model*

2. *Simplified Model*

ENEE236 – Analog Electronics

Fixed V_{in} , Variable R_L

- Due to the value of V_Z , there is specific values of R_L (I_L) that ensure the zener is in the ON (regulation) state
- Too small values of R_L can result in zener being OFF

$$V_L = V_Z = \frac{R_L}{R_L + R_S} V_{in}$$

$$R_{L(\min)} = \frac{R_S \cdot V_Z}{V_{in} - V_Z}$$

$$R_L \geq R_{L(\min)} \Rightarrow I_{L(\max)} = \frac{V_L}{R_L} = \frac{V_L}{R_{L(\min)}}$$

Also, values of $R_L \geq R_{L(\max)}$ can result in $\Rightarrow I_Z > I_{Z(\max)}$

$$I_{L(\min)} = I_S - I_{Z(\max)}$$

$$\Downarrow$$


$$R_{L(\max)} = \frac{V_Z}{I_{L(\min)}}$$

ENEE236 – Analog Electronics

Example

Given the following values of R_L , find the mode of operation of the zener and the voltage V_L , assume $R_s = 1\text{ k}\Omega$

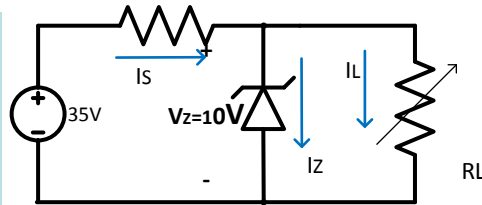- a) $R_L = 0.1\text{ k}\Omega$
- b) $R_L = 0.5\text{ k}\Omega$
- c) $R_L = 5\text{ k}\Omega$
- d) $R_L = \infty$



SOLUTION

a) $R_L = 0.1\text{ k}\Omega$
using ideal model


$$V_{th} = \frac{R_L}{R_L + R_s} V_{in} = \frac{0.1}{0.1 + 1} 35\text{ V} = 3.18\text{ V}$$

Zener works in region 2, it acts as open circuit

$$V_L = 3.18\text{ V (it is not regulated)}$$

ENEE236 – Analog Electronics

Example

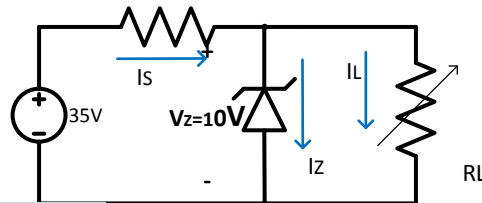

b) $R_L = 0.5\text{ k}\Omega$
using ideal model

$$V_{th} = \frac{R_L}{R_L + R_s} V_{in} = \frac{0.5}{0.5 + 1} 35\text{ V} = 11.67\text{ V}$$

$$V_{th} > V_z$$

Zener works in region 3, it works as voltage regulator


$$V_L = V_z = 10\text{ V}$$

$$I_s = \frac{35\text{ V} - 10\text{ V}}{1\text{ k}\Omega} = 25\text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{0.5\text{ k}\Omega} = 20\text{ mA}$$

$$I_z = I_s - I_L = 5\text{ mA}$$

Example

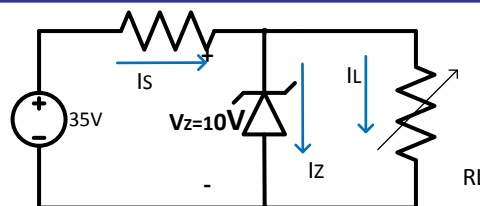

c) $R_L = 5\text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_s} V_{in} = \frac{5}{5+1} 35\text{ V} = 29.17\text{ V}$$

$$V_{th} > V_Z$$

Zener works in region 3, it works as voltage regulator


$$V_L = V_Z = 10\text{ V}$$

$$I_S = \frac{35\text{ V} - 10\text{ V}}{1\text{ k}\Omega} = 25\text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{5\text{ k}\Omega} = 2\text{ mA}$$

$$I_Z = I_S - I_L = 23\text{ mA}$$

Example

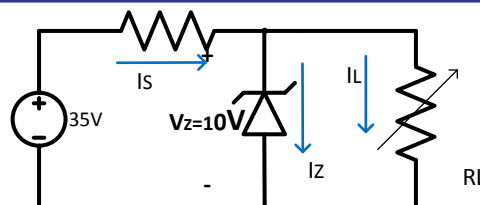

d) $R_L = \infty$

using ideal model

$$V_{th} = \frac{\infty}{\infty + R_s} V_{in} = 35\text{ V}$$

$$V_{th} > V_Z$$

Zener works in region 3, it works as voltage regulator

$$V_L = V_Z = 10\text{ V}$$


$$I_S = \frac{35\text{ V} - 10\text{ V}}{1\text{ k}\Omega} = 25\text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{\infty} = 0$$

ENEE236 – Analog Electronics

Example

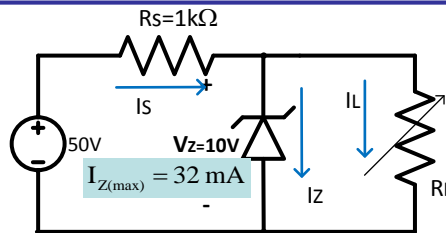- 1) Determine Range of R_L & I_L that will result in V_L be maintained at 10V
- 2) Determine the power rating of the zener diode



SOLUTION

- 1) To find $R_{L(min)}$ that will turn the zener diode ON :

$$V_L = V_Z = \frac{R_L}{R_L + R_S} V_i \Rightarrow$$

$$R_L = \frac{R_S}{V_i - V_Z} V_Z$$

$$R_{L(min)} = \frac{1 \text{ k}\Omega}{50 - 10} \cdot 10 = 250 \Omega$$

$$250 \Omega \leq R_L \leq 1.25 \text{ k}\Omega$$

- 2) To find $R_{L(max)}$ \Rightarrow we need $I_{L(min)}$

$$I_{L(min)} = I_S - I_{Z(max)}$$

$$I_S = \frac{V_i - V_Z}{R_S} = \frac{50 - 10}{1 \text{ k}\Omega} = 40 \text{ mA}$$

$$I_{L(min)} = 40 - 32 = 8 \text{ mA}$$

\Downarrow

$$R_{L(max)} = \frac{V_L}{I_{L(min)}} = \frac{10 \text{ V}}{8 \text{ mA}} = 1.25 \text{ k}\Omega$$

- 3) $P_{Z(max)} = V_Z \cdot I_{Z(max)} = 10 \text{ V} \cdot 32 \text{ mA} = 320 \text{ mW}$

The zener diode is chosen with power rating $\geq P_{Z(max)}$

ENEE236 – Analog Electronics

Fixed R_L , Variable V_{in}

For Fixed R_L , the voltage V_{in} must be large enough to turn the zener diode on (regulation region (3))

$$V_{in} = V_{in(min)} = \frac{R_L + R_S}{R_L} V_Z$$

$V_{in(max)}$ is limited by maximum zener current $I_{Z(max)}$


$$I_S = I_Z + I_L$$

$$I_{S(max)} = I_{Z(max)} + I_L$$

$$V_{i(max)} = I_{S(max)} \cdot R_S + V_Z$$

\Downarrow
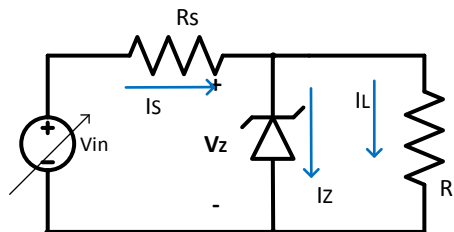
$$V_{in(min)} \leq V_{in} \leq V_{in(max)}$$



Example

Find the range of values of V_i that will maintain the zener in the ON (regulation) State

$$V_{in(min)} = \frac{R_L + R_S}{R_L} V_Z$$

$$= \frac{1200 + 220}{1200} 20 = 23.07 \text{ V}$$


$$I_S = I_Z + I_L$$

$$I_{S(max)} = I_{Z(max)} + I_L$$

$$I_L = \frac{V_L}{R_L} = \frac{20 \text{ V}}{1200 \Omega} = 16.67 \text{ mA}$$

$$I_{S(max)} = 60 \text{ mA} + 16.67 \text{ mA} = 76.67 \text{ mA}$$
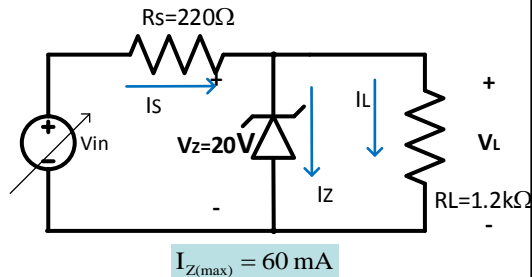
$$V_{i(max)} = (76.67 \text{ mA}) \cdot (220 \Omega) + 20 \text{ V} = 36.87 \text{ V}$$



$$\therefore 23.07 \text{ V} \leq V_{in} \leq 36.87 \text{ V}$$

Design of R_s (Current limiting Resistor)

Given : $V_Z, I_{Z(min)}, I_{Z(max)}, V_{in(min)}, V_{in(max)}, R_{L(min)}, R_{L(max)}$

Find range of acceptable R_s in the voltage regulator


$$1) I_Z = I_S - I_L \geq I_{Z(min)}$$

Worst Case : the smallest value of

$$(I_S - I_L)$$

must be always higher than $> I_{Z(min)}$
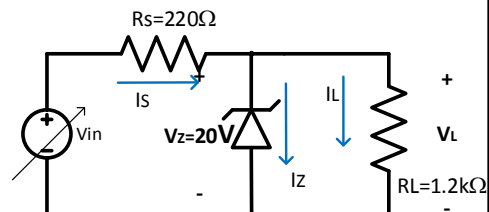
$$I_{S(min)} - I_{L(max)} \geq I_{Z(min)}$$



$$\frac{V_{S(min)} - V_Z}{R_S} - I_{L(max)} \geq I_{Z(min)}$$

$$I_{Z(min)} + I_{L(max)} \leq \frac{V_{S(min)} - V_Z}{R_S}$$

$$R_S \leq \frac{V_{S(min)} - V_Z}{I_{Z(min)} + I_{L(max)}}$$

Design of Rs (Current limiting Resistor)

Given : $V_Z, I_{Z(\min)}, I_{Z(\max)}, V_{in(\min)}, V_{in(\max)}, R_{L(\min)}, R_{L(\max)}$

Find range of acceptable Rs in the voltage regulator

$$2) I_Z \leq I_{Z(\max)}$$

Worst Case : the largest value of $(I_S - I_L)$
 must be always smaller than $I_{Z(\max)}$

$$I_{S(\max)} - I_{L(\min)} \leq I_{Z(\max)}$$

$$\frac{V_{S(\max)} - V_Z}{R_S} - I_{L(\min)} \leq I_{Z(\max)}$$

$$I_{Z(\max)} + I_{L(\min)} \geq \frac{V_{S(\max)} - V_Z}{R_S}$$

$$R_S \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Note That

$$I_{L(\min)} = \frac{V_Z}{R_{L(\max)}}$$

$$I_{L(\max)} = \frac{V_Z}{R_{L(\min)}}$$

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_S \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Design of Rs (Current limiting Resistor)

Given :

$$V_Z = 10 \text{ V,}$$

$$I_{Z(\min)} = 5 \text{ mA, } I_{Z(\max)} = 200 \text{ mA,}$$

$$V_{in(\min)} = 15 \text{ V, } V_{in(\max)} = 20 \text{ V,}$$

$$R_{L(\min)} = 500, R_{L(\max)} = \infty$$

Find R_s ?

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_S \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Solution

$$I_{L(\min)} = \frac{V_Z}{R_{L(\max)}} = \frac{10 \text{ V}}{500 \Omega} = 20 \text{ mA}$$

$$I_{L(\max)} = \frac{V_Z}{R_{L(\min)}} = \frac{10 \text{ V}}{\infty} = 0$$

$$200 \Omega \geq R_s \geq 50 \Omega$$

$$\text{let } R_s = 100 \Omega$$

Variation of V_Z (using simplified model)

$$r_Z = \frac{\Delta V_Z}{\Delta I_Z}$$


If V_{ZT} , I_{ZT} & r_Z are known

$$V_{Z(max)} = V_{ZM} = V_{ZT} + \Delta I_Z \cdot r_Z$$

$$= V_{ZT} + (I_{Z(max)} - I_{ZT}) \cdot r_Z$$

$$V_{Z(min)} = V_{ZK} = V_{ZT} - \Delta I_Z \cdot r_Z$$
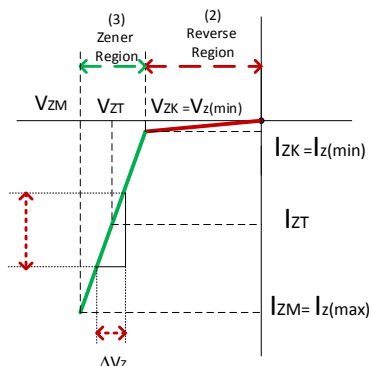
$$= V_{ZT} - (I_{ZT} - I_{Z(min)}) \cdot r_Z$$



Example

If $V_{ZT} = 15V$ at $I_{ZT} = 17mA$

& $r_{ZT} = 14 \Omega$

$I_{ZK} = 0.25 mA$

$P_{Zmax} = 1 Watt$

Find:

1) Minimum and Maximum Values of V_Z



2) Value of R_S

3) Value of $R_{L(min)}$

$$1) I_{Z(max)} \cong \frac{P_{Z(max)}}{V_Z} = \frac{1 \text{ Watt}}{15} = 66.7 \text{ mA}$$

$$\begin{aligned} V_{Z(max)} = V_{ZM} &= V_{ZT} + \Delta I_Z \cdot r_Z \\ &= V_{ZT} + (I_{Z(max)} - I_{ZT}) \cdot r_Z \\ &= 15 + (66.7 - 17) \text{ mA} (14 \Omega) = 15.7 \text{ V} \end{aligned}$$


$$\begin{aligned} V_{Z(min)} = V_{ZK} &= V_{ZT} - \Delta I_Z \cdot r_Z \\ &= V_{ZT} - (I_{ZT} - I_{Z(min)}) \cdot r_Z \end{aligned}$$

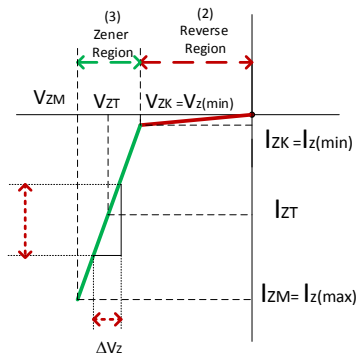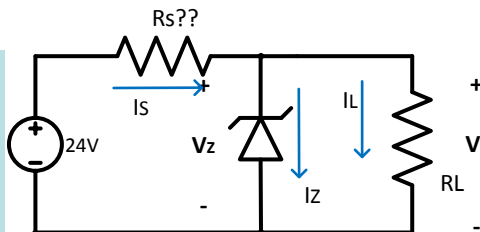

ENEE236 – Analog Electronics

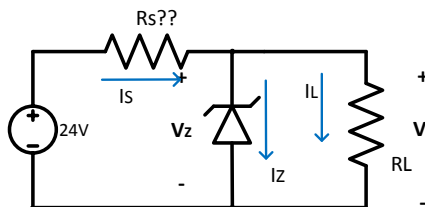Example

$$\begin{aligned} V_{Z(\min)} &= V_{ZK} = V_{ZT} - \Delta I_Z \cdot r_z \\ &= V_{ZT} - (I_{ZT} - I_{Z(\min)}) \cdot r_z \\ &= 15 - (17 - 0.25) \text{ mA} (14 \Omega) = 14.76 \text{ V} \end{aligned}$$



2) R_s


$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_s \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Here $V_{IN} = V_S$ is fixed \Rightarrow

$$R_s \geq \frac{V_S - V_{Z(\max)}}{I_{Z(\max)} + I_{L(\min)}} = \frac{24 - 15.7}{66.7 \text{ mA} + 0} = 124 \Omega$$


$$R_s \leq \frac{V_S - V_{Z(\min)}}{I_{Z(\min)} + I_{L(\max)}} = \frac{24 - 14.76}{0.25 \text{ mA} + ???}$$

we choose $R_s = 124 \Omega$

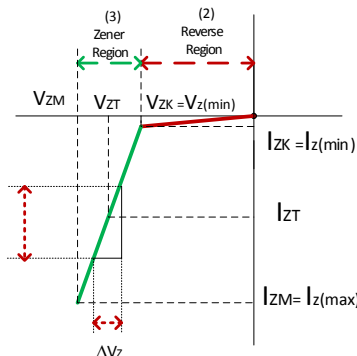

ENEE236 – Analog Electronics


Example

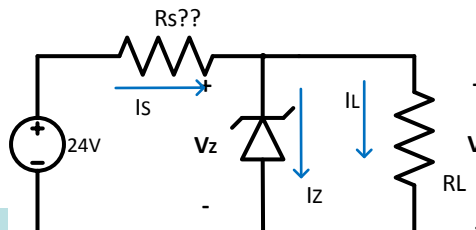

3) $R_{L(\min)} \Rightarrow I_{L(\max)}$

$$\begin{aligned} I_{L(\max)} &= I_S - I_{L(\min)} \\ &= 66.7 \text{ mA} - 0.25 \text{ mA} = 66.45 \text{ mA} \end{aligned}$$

$$\therefore R_{L(\min)} = \frac{V_{Z(\min)}}{I_{L(\max)}} = \frac{14.76 \text{ V}}{66.45 \text{ mA}} \cong 222 \Omega$$

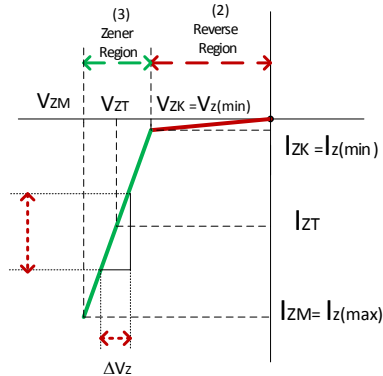

ENEE236 – Analog Electronics

Clipper circuits using Zeners

a) When $V_i(t) < -0.7 \text{ V}$, Zener works in region (1) as regular diode ON

$$0.7 + i_D(t) \cdot R + V_i(t) = 0$$




$$i_D(t) = \frac{-V_i(t) - 0.7}{R} > 0$$

$$V_i(t) < -0.7$$

$$\therefore V_o(t) = -0.7$$

b) When $V_z > V_i(t) > -0.7 \text{ V}$, Zener works in region (2) as regular diode OFF $\therefore V_o(t) = V_i(t)$


c) When $V_i(t) > V_z$, Zener works in region (3) as voltage regulator $\therefore V_o(t) = V_z$

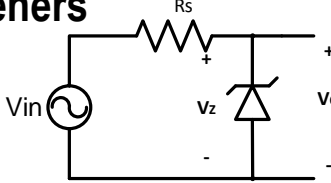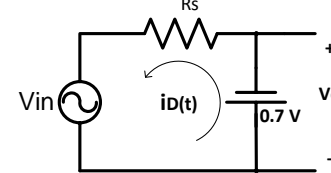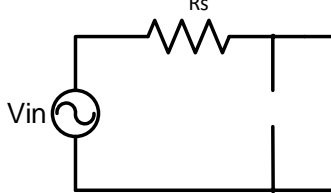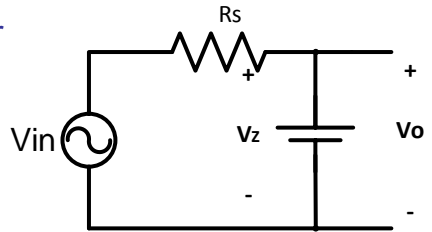




ENEE236 – Analog Electronics

Clipper circuits using Zeners

c) When $V_i(t) > V_z$, Zener works in region (3) as voltage regulator $\therefore V_o(t) = V_z$

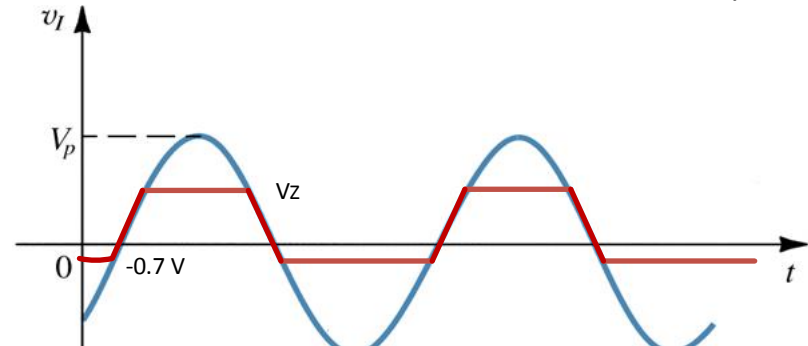



ENEE236 – Analog Electronics

Clipper circuits using Zeners

Find and sketch $V_o(t)$

a) When $0.7V < V_i(t) < V_{z2}$,
 D1- regular diode ON
 D2- regular diode OFF

$\therefore V_o(t) = V_i(t)$

b) When $V_i(t) > V_{z2}$
 D1 – ON (region 1)
 D2- Zener ON (region 3)

$\therefore V_o(t) = V_{z2} + 0.7$

ENEE236 – Analog Electronics

Clipper circuits using Zeners


c) When $-0.7V > V_i(t) > -V_{z1}$,
 D1- regular diode OFF
 D2- regular diode ON

$\therefore V_o(t) = V_i(t)$

d) When $V_i(t) < -V_{z1}$
 D2 – ON (region 1)
 D1- Zener ON (region 3)

$\therefore V_o(t) = -V_{z1} - 0.7$

Clipper circuits using zeners

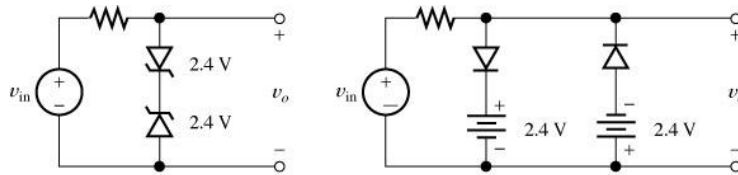

(c) Circuits for the characteristic of part (a)

Voltage-Multiplier Circuits


Voltage multiplier circuits use a combination of diodes and capacitors to step up the output voltage of rectifier circuits. Three common voltage multipliers are the:

Voltage Doubler

Voltage Tripler

Voltage Quadrupler

Voltage Doubler

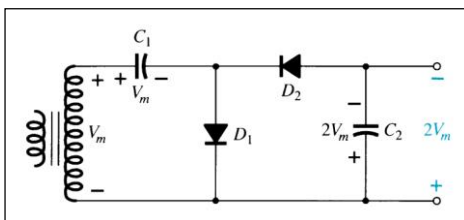

This half-wave voltage doubler's output can be calculated using:

$$V_{out} = V_{C2} = 2V_m$$

where V_m = peak secondary voltage of the transformer

Voltage Doubler

Positive Half-Cycle

D_1 conducts
 D_2 is switched off
 Capacitor C_1 charges to V_m

Negative Half-Cycle

D_1 is switched off
 D_2 conducts
 Capacitor C_2 charges to V_m

$$V_{out} = V_{C2} = 2V_m$$

