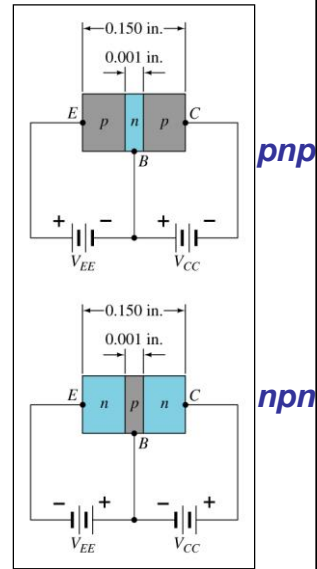


Construction

- 3-Layer Semiconductor device
- 2 p- layers and one n-layer or vice versa
- pnp or npn types
- Two pn junctions , each of them can be either forward or reverse biased
- This results in 4 possible modes of operation




ENEE236 Analog Electronics

3

Bipolar junction Transistor _ (BJT):

BJT:

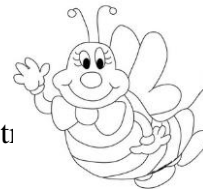
1. It's a semiconductor device that can amplify electrical signals such as radio or television signals.
2. Its essential ingredient of every electronic circuits; from the simplest amplifier or oscillator to the most elaborate digital computer.
3. It's a three terminal device;
Base, Emitter, and Collector.



There are two type of BJT:

➤ **npn** type


➤ **pn**p type

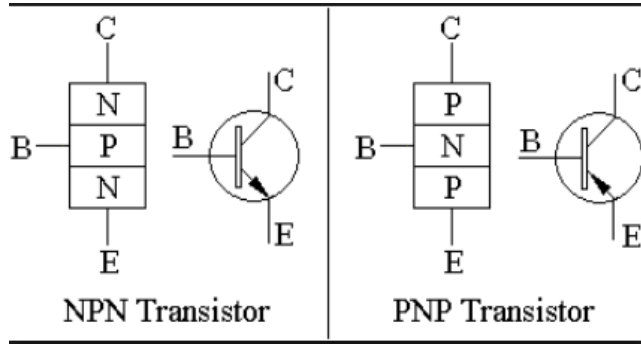

Transistor structure:

➤ **npn** type

➤ **pn**p type

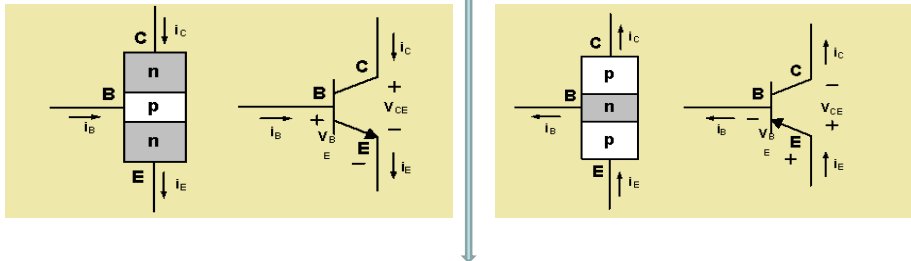


Transistor biasing:

- ✓ In order to operate properly as an amplifier, it's necessary to correctly bias the two pn-junctions with external voltages.
- ✓ Depending upon external bias voltage polarities used; the transistor works in one of **four regions** (modes). npn transistor modes of operation
- ✓ For transistor to be used as an Active device (**Amplifier**); the **emitter-base** junction must be **forward** bias, while the **collector-base** junction must be **reverse** biased.

| Junction/ Mode | BE | BC | Remarks |
|-----------------------------|---------|---------|---|
| Saturation Mode | Forward | Forward | Equivalent to short circuit $I_c = I_c(\text{sat})$ $V_{ce} = V_{ce}(\text{sat}) \approx -0.2V$ |
| Active Mode (Linear Region) | Forward | Reverse | I_c proportional to I_b V_{ce} defined by circuit |
| Cut-off Mode | Reverse | Reverse | Equivalent to open circuit $I_c = I_b = 0$ V_{ce} defined by circuit |
| Inverse Mode | Reverse | Forward | Rarely used and will not be discussed in this course |

In active region

- ✓ The base region is thin and lightly doped
- ✓ The **emitter-base** junction is **forward biased**, thus the depletion region at this junction **is reduced**.
- ✓ The **base-collector** junction is **reverse** biased, thus the depletion region at this junction **is increased**.
- ✓ The **forward** biased **BE-junction** causes the electrons in the **n-type** emitter to flow **toward the base**; this constitutes the emitter current I_E .
- ✓ As these electrons flow through the **P-type** base; they tend to recombine with holes in **p-type** base.

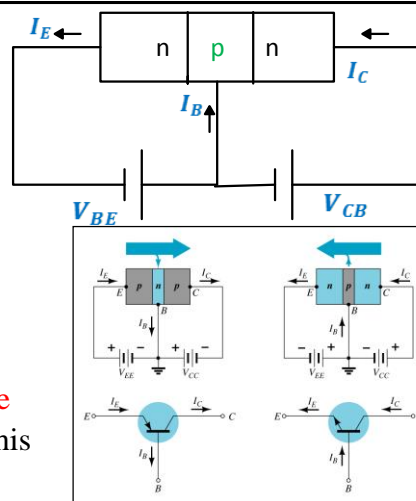

✓ Since the **base** region is **lightly doped**; very few of the electrons injected into the base from the emitter recombine with holes to constitute base current I_B and the remaining large number of electrons cross the base and move through the collector region to the positive terminal of the external DC source; this constitute collector current I_C

✓ There is another component for I_C due to the minority carrier; I_{CBO}

$$\checkmark I_C = \alpha I_E + I_{CBO}$$

Majority
Minority

$0.998 > \alpha > 0.9$

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_C + I_B$$

$$I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$\diamond I_C = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

Let Beta, $\beta = \frac{\alpha}{1-\alpha}$

$$\diamond I_C = \beta I_B + (\beta + 1) I_{CBO}$$

$$I_C = \beta I_B + I_{CEO}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

If $\alpha = 0.99$ \longrightarrow $\beta = 99$

If $\alpha = 0.995$ \longrightarrow $\beta = 199$



In active region:

$$I_C = \alpha I_E + I_{CBo}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$I_C = \beta I_B + (\beta + 1)I_{CBo}$$

$$I_C = \beta I_B + I_{CEo}$$

$$I_E = I_C + I_B$$

Approximate relationships:

$$I_C \cong \alpha I_E \cong I_E$$

$$I_C \cong \beta I_B$$

$$I_E \cong (\beta + 1)I_B$$



Basic BJT Amplifiers Circuits


$$\alpha \approx \frac{I_C}{I_E}$$

$$\beta \approx \frac{I_C}{I_B} \quad \text{---common-emitter current gain}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

BJT in Active Mode

$$I_E = I_B + I_C$$

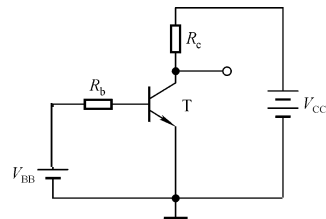

BJT DC Analysis

- Make sure the BJT current equations and region of operation match

$$V_{BE} > 0, \quad V_{BC} < 0, \quad \rightarrow V_E < V_B < V_C$$

- Utilize the relationships (β and α) between collector, base, and emitter currents to solve for all currents


$$\begin{cases} I_E = I_C + I_B = (1 + \beta)I_B \\ I_C = \beta I_B \\ I_C = \alpha I_E \end{cases}$$

Basic BJT Amplifiers Circuits



C-E Circuits I-V Characteristics

Base-emitter Characteristic (Input characteristic)

$$i_B = f(v_{BE}) \Big|_{v_{CE}=C}$$

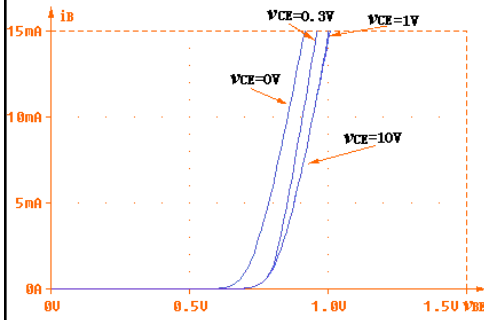
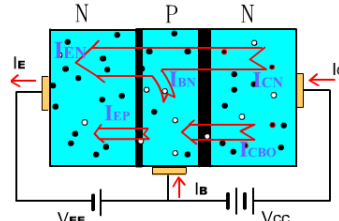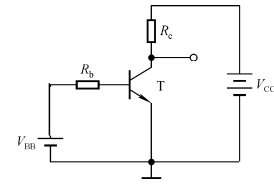
$$i_C(t) \cong I_S \left(e^{\frac{V_{BE}(t)}{\eta V_T}} \right)$$



$$i_B(t) = I_{B0} \left(e^{\frac{V_{BE}(t)}{\eta V_T}} - 1 \right)$$




$$i_B(t) \cong I_{B0} \left(e^{\frac{V_{BE}(t)}{\eta V_T}} \right)$$

Basic BJT Amplifiers Circuits

C-E Circuits I-V Characteristics

Collector characteristic (output characteristic)


$$i_C = f(v_{CE}) \Big|_{i_B=C}$$

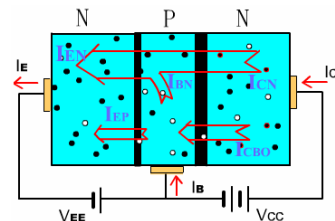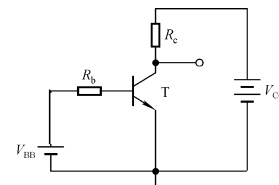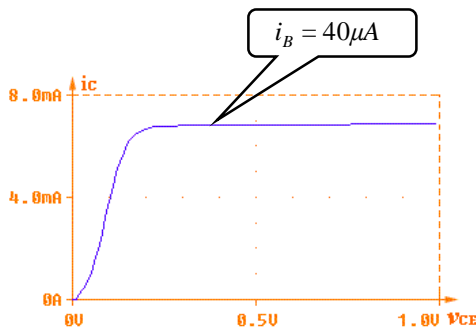

Basic BJT Amplifiers Circuits

C-E Circuits I-V Characteristics



Collector characteristic (output characteristic) $i_C = f(V_{CE})|_{i_B=C}$

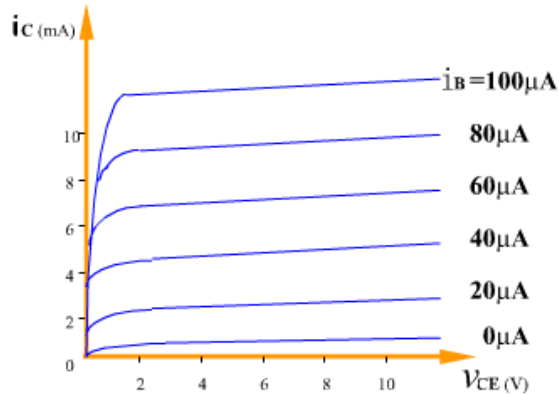

Basic BJT Amplifiers Circuits

C-E Circuits I-V Characteristics

Collector characteristic

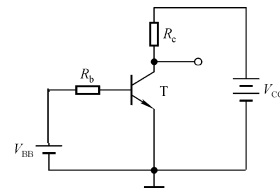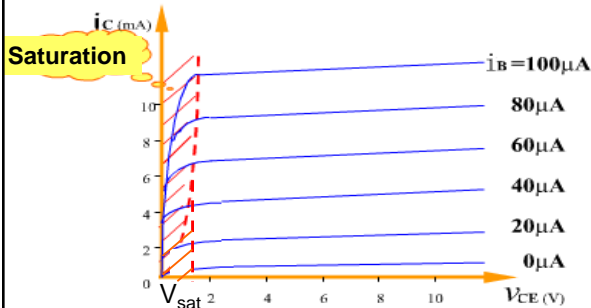

Saturation occurs when the supply voltage, V_{CC} , is across the total resistance of the collector circuit, R_C .



$$I_{C(sat)} = V_{CC}/R_C$$

Once the base current is high enough to produce saturation, further increases in base current have no effect on the collector current and the relationship $I_C = \beta I_B$ is no longer valid. When V_{CE} reaches its saturation value, $V_{CE(sat)}$, the base-collector junction becomes forward-biased.

Basic BJT Amplifiers Circuits

C-E Circuits I-V Characteristics

Collector characteristic

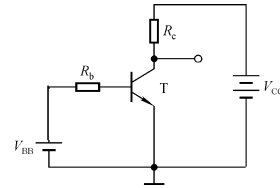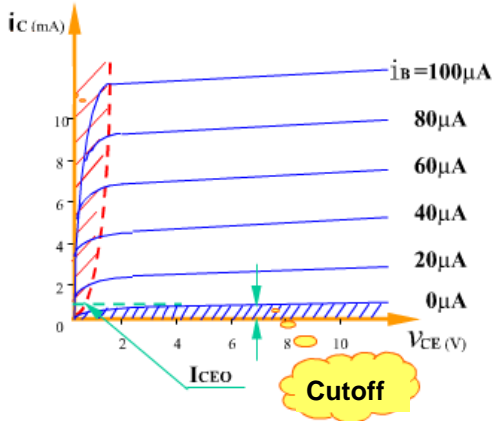



When $I_B = 0$, the transistor is in cutoff and there is essentially no collector current except for a very tiny amount of collector leakage current, I_{CEO} , which can usually be neglected. $I_C \approx 0$.

In cutoff both the base-emitter and the base-collector junctions are reverse-biased.

Basic BJT Amplifiers Circuits

C-E Circuits I-V Characteristics

Collector characteristic

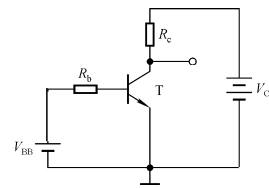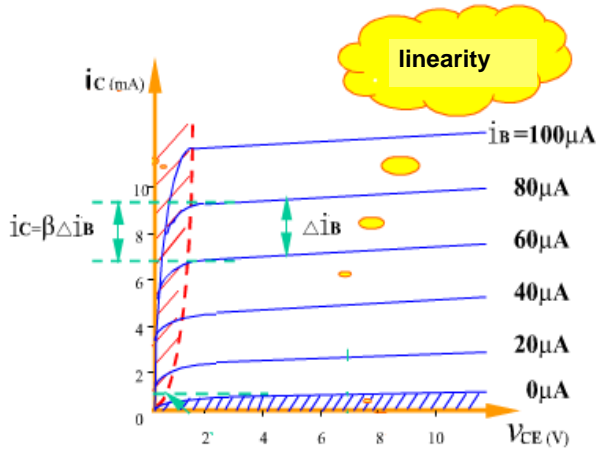

1. In the **cutoff** region :

$$I_B = I_C = I_E = 0$$

2. In the **active** region :

$$I_C = \alpha I_E$$

$$I_C = \beta I_B$$

$$I_E = (\beta + 1) I_B$$

3. In the **saturation** region :

$$V_{CE} = V_{CE,sat}$$

$$V_{BE} = 0.8 \text{ v} \quad , \text{ Si} \quad , \text{ npn}$$

$$V_{BE} = -0.8 \text{ v} \quad , \text{ Si} \quad , \text{ pnp}$$

$$V_{BE} = 0.7 \text{ v} \quad , \text{ Si} \quad , \text{ npn}$$

$$V_{BE} = -0.7 \text{ v} \quad , \text{ Si} \quad , \text{ pnp}$$

$$V_{CE} > V_{CE,sat} = 0.2 \text{ v} \quad , \text{ Si} \quad , \text{ npn}$$

$$V_{CE} < V_{CE,sat} = -0.2 \text{ v} \quad , \text{ Si} \quad , \text{ pnp}$$

Example:

Find mode of operation and the Q point V_{CEQ} , I_{CQ}

Since the base emitter junction is **forward bias**; the transistor could be either in the **active** or the **saturation** region

In General


1) In the active region:

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - R_C I_C$$

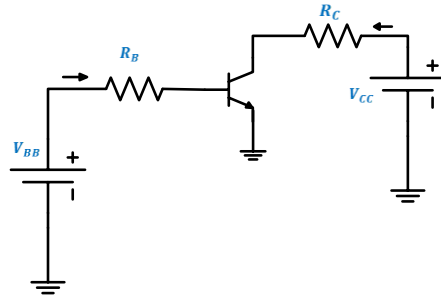As : $R_B \downarrow$, $I_B \uparrow$, $I_C \uparrow$, $V_{CE} \downarrow$



2) In the saturation region:

$$V_{CE} = V_{CE,sat} = 0.2 \text{ v} \quad , \quad \text{Si} \quad , \quad \text{npn}$$

$$I_C = I_{C,sat} = \frac{V_{CC} - V_{CE,sat}}{R_C}$$

➤ Assume that the transistor in the **active** region:



KVL: $5 = 200k I_B + V_{BE}$

$$I_B = \frac{5 - 0.7}{200k} = 0.0215 \text{ mA}$$

$$I_C = \beta I_B = 100 * 0.0215 = 2.15 \text{ mA}$$

KVL: $10 = R_C I_C + V_{CE}$

$$V_{CE} = 10 - R_C I_C$$


$$\diamond V_{CE} = 10 - 3k * 2.15\text{mA} = 3.55 \text{ Volt}$$

Since


$V_{CE} > V_{CE,sat} \gg \gg$ The transistor is in the **active** region

➤ $V_{CEQ} = 3.55 \text{ Volt}$

➤ $I_{CQ} = 2.15 \text{ mA}$

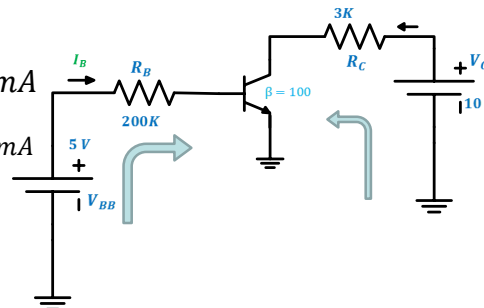

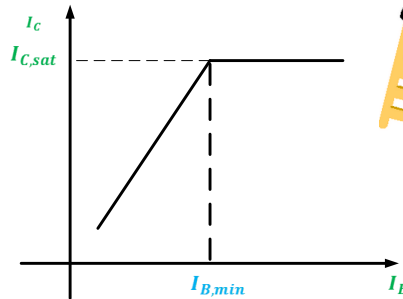Let define: $I_B(min) = \frac{I_{C,sat}}{\beta}$



$$I_B(min) = \frac{I_{C,sat}}{\beta}$$

- ✚ If $I_B > I_B(min)$ the transistor is in the **saturation** region.
- ✚ If $I_B < I_B(min)$ the transistor is in the **Active** region.

Determine Mode of Operation of BJT?

- Solution 1:
- 1) Since BE junction is forward biased ==> Q1 can be either in Active (Linear) or Saturation mode
- Assume it is in Active Mode


$$5 = 200 \text{ k}\Omega \cdot I_B + V_{BE} + 2 \text{ k}\Omega \cdot I_E$$

But, $I_E = (1 + \beta)I_B$

$$\text{Solve for } I_B = \frac{5 - V_{BE}}{200 \text{ k}\Omega + (1 + \beta) \cdot 2 \text{ k}\Omega}$$

$$I_B = \frac{5 - 0.7}{200 \text{ k}\Omega + (1 + 100) \cdot 2 \text{ k}\Omega}$$
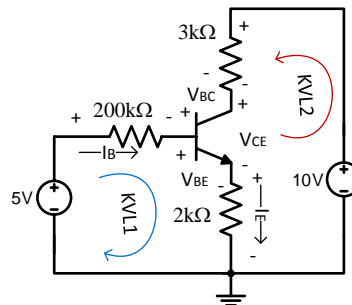
$$= \frac{4.3 \text{ V}}{402 \text{ k}\Omega} = 10.7 \text{ }\mu\text{A}$$



$$I_C = \beta I_B$$

$$= (100) \cdot (10.7 \mu\text{A})$$

$$= 1.07 \text{ mA}$$


$$I_E = (\beta + 1) I_B$$

$$= 1.0807 \text{ mA}$$

Now we find V_{CE} from output circuit

$$10 - I_C \cdot 3 \text{ k}\Omega - I_E \cdot 2 \text{ k}\Omega = V_{CE}$$
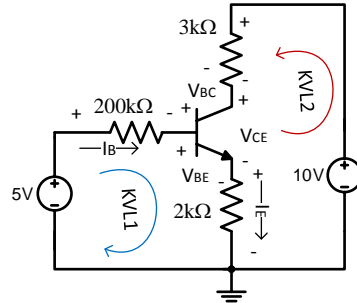
$$\Rightarrow V_{CE} = 4.63 \text{ V} > V_{CE(\text{sat})}$$



\therefore Q1 is in active mode and the assumption is true
we can also verify that the BC junction is reverse
biased which is required so that the BJT operates
in active mode


$$10 - I_C \cdot 3 \text{ k}\Omega - I_E \cdot 2 \text{ k}\Omega = V_{CE}$$

$$\Rightarrow V_{CE} = V_{CB} - V_{EB}$$

$$\Rightarrow V_{CB} = V_{CE} - V_{BE} = 4.63 - 0.7 = 3.93 \text{ V}$$

$$\therefore V_{BC} = -V_{CB} = -3.33 \text{ V}$$

BC junction is reverse biased

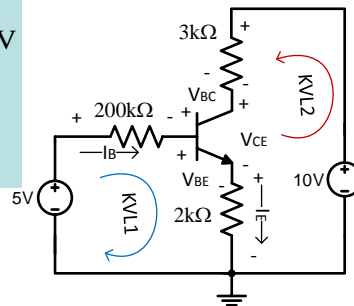

OR Second method: Assume Saturation

- 1) Since BE junction is forward biased ==> Q1 can be either in Active (Linear) or Saturation mode
- Assume it is in **saturation mode**:

$$10 - I_{C(sat)} \cdot 3k\Omega - I_{E(sat)} \cdot 2k\Omega = V_{CE(Sat)}$$

assume $I_{E(sat)} = I_{C(sat)}$

$$\therefore I_{C(sat)} = \frac{10 - 0.2}{5k\Omega} = 1.96 \text{ mA}$$



$$I_{B(min)} = \frac{I_{C(sat)}}{\beta} = 19.6 \text{ }\mu\text{A}$$

Now we find the actual value of IB

$$I_{B(actual)} = 10.7 \text{ }\mu\text{A (it was found previously)}$$

since

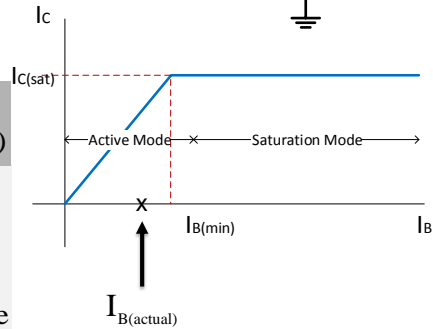
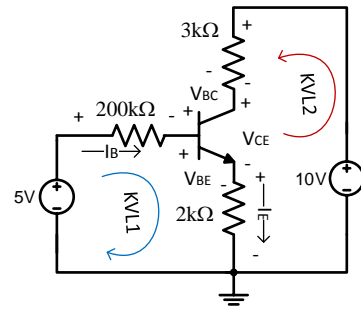
$I_{B(actual)} < I_{B(sat)} = I_{B(min)} \Rightarrow$ the assumption made earlier that BJT in saturation mode is wrong, and actually it is in active mode



BJT as switch:

Example:



Find $V_o(t)$ for the input given below:

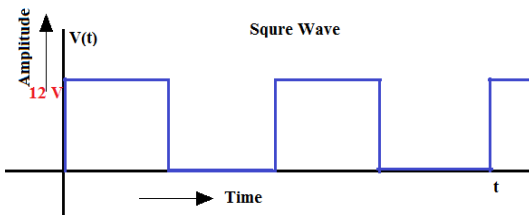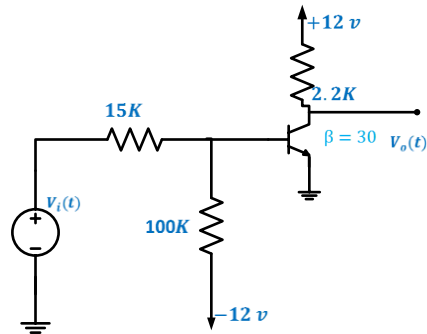

Solution:

❖ Let $V_i(t) = +12 \text{ volt}$

Calculate V_{th} & R_{th}

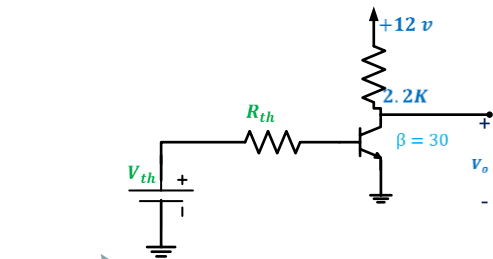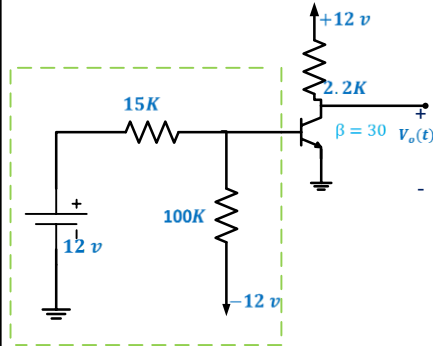

$$R_{th} = 15k // 100k = \frac{100k \cdot 15k}{15k + 100k} = 13k$$

$$V_{th} = 8.9 \text{ volt} \quad \text{Proof!!}$$



Since the base emitter junction is forward bias; the transistor could be either in the active or the saturation region

➤ Assume that the transistor in the saturation region

$$I_C = I_{C,sat} = \frac{V_{CC} - V_{CE,sat}}{R_C} = \frac{12 - 0.2}{2.2k} = 5.36 \text{ mA}$$

$$I_B(\text{min}) = \frac{I_{C,sat}}{\beta} = \frac{5.36 \text{ mA}}{30} = 0.18 \text{ mA}$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{TH}} = \frac{8.9 - 0.8}{13k} = 0.62 \text{ mA}$$

✚ Since $I_B > I_B(\text{min})$ the transistor is in the saturation region.

$$\checkmark V_o = V_{CE,sat} = 0.2 \text{ volt}$$


$$\checkmark I_C = 5.36 \text{ mA}$$

❖ Let $V_i(t) = 0 \text{ volt}$

Since $V_{th} = -1.56 \text{ volt}$
 Base emitter junction is revers biased the transistor in cutoff region
 $\checkmark V_o = V_{CE} = 12 \text{ volt}$
 $\checkmark I_C = 0 \text{ mA}$

The circuit acts as inverter or not gate

NOT gate truth table

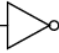Input  Output

| Input | Output |
|-------|--------|
| 0 | 1 |
| 1 | 0 |