



ANSWER BOOKLET

For Instructor's Use

Question	Grade
1	12
2	9
3	7.5
4	13.5
5	
6	
7	
8	
9	
10	
11	
12	
Total	42 + 2

Student: <u>Alham Suwan</u> Number: <u>1091696</u>
Course: Department: _____ Number: _____ Division: _____ Instructor: _____
Date: _____ Day Month Year


Q1)  $V_z = 10\text{V}$  @  $I_z = 25\text{mA}$

$P_z(\text{max}) = 0.5\text{W} = V_z * I_z(\text{max})$

12/12

$\Rightarrow I_z(\text{max}) = \frac{0.5}{10} = 0.05\text{A} = \boxed{50\text{mA}}$

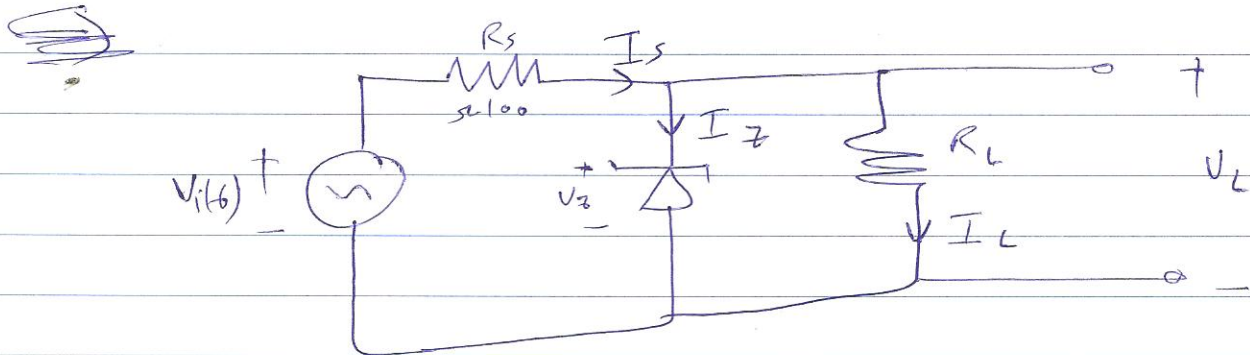$V_L = 10 \Rightarrow I_L = \frac{V_L}{R_L} = \frac{10}{250} = 40\text{mA}$



$I_s(\text{max}) = I_z(\text{max}) + I_L$

$= 50 + 40 = 90\text{mA}$


$\Rightarrow V_i(t) (\text{max})$  @  $I_s(\text{max})$

KVL  $- V_i(t)_{\text{max}} + I_s R_s + V_z = 0$

$\Rightarrow V_i(t)_{\text{max}} = 90\text{mA} * 100\ \Omega + 10$   
 $= 19\text{V}$

Also  $V_{bh} \geq V_z$

~~KVL~~

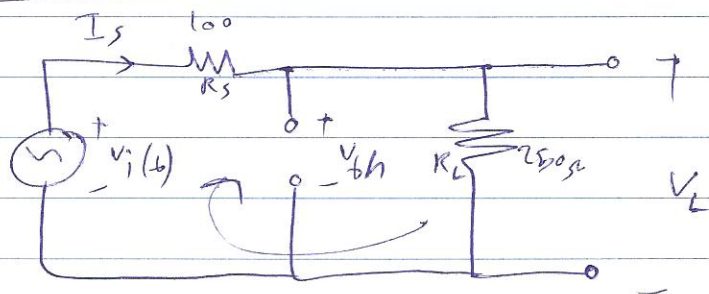

$- V_{bh} - I_s R_s + V_i(t) = 0$

$\Rightarrow V_{bh} = V_i(t) - I_s R_s \geq V_z = 10$

$\Rightarrow V_i(t) - 90\text{mA} * 100\ \Omega \geq 10$

$$V_{th} = \frac{250\Omega}{250\Omega + 100\Omega} V_i(t)$$

~~$$\Rightarrow V_{th} = 0.71 V_i(t) \geq V_Z = 10$$~~


~~$$\Rightarrow 0.71 V_i(t) \geq 10$$~~

$$V_{th} = 0.71 V_i(t) = V_Z = 10 \quad (\text{at least})$$

$$\Rightarrow \boxed{V_i(t)_{\min} = \frac{10}{0.71} = 14.08 \text{ V} \approx 14 \text{ V}}$$

$$\Rightarrow 19 \text{ mA} > V_i(t) > 14 \text{ V}$$

2)

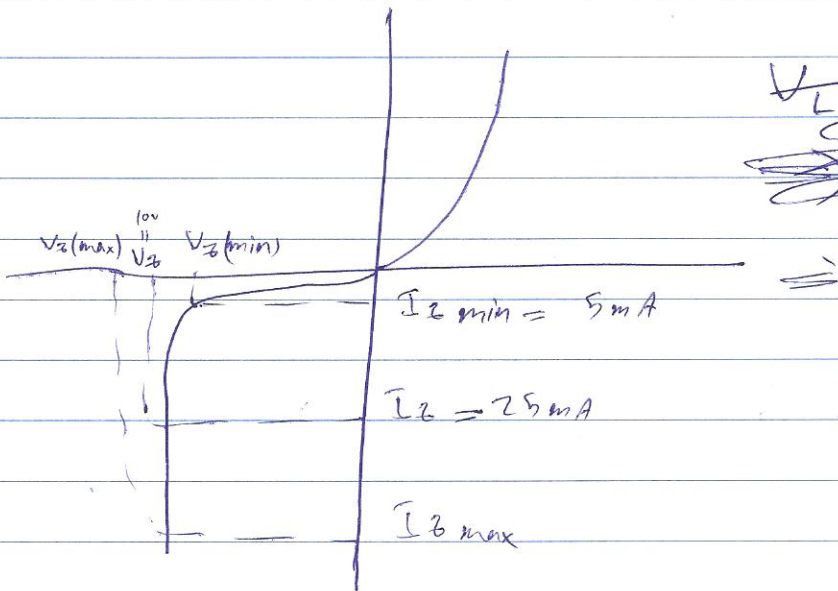

$$V_L = V_Z \Rightarrow V_L(\max) = V_Z(\max)$$

$$V_L(\min) = V_Z(\min)$$

Sind  $\Rightarrow V_Z(\min) \& V_Z(\max)$

~~$V_z(\max)$~~

$$V_z(\min) = V_z - \Delta V_z$$

$$\text{~~For~~ } r_z = \frac{\Delta V_z}{\Delta I_z} \Rightarrow \Delta V_z = r_z \times \Delta I_z$$

$$\Rightarrow \Delta I_z = \frac{V_z - V_z(\min)}{r_z} = I_z - I_z(\min)$$

$$\Rightarrow 25 - 5 = 20 \text{ mA}$$

$$\text{~~For~~ } \Rightarrow \Delta V_z = 10 \Omega \times 20 \text{ mA} = 200 \text{ mV}$$

$$\Rightarrow V_z(\min) = 10 \text{ V} - 200 \text{ mV} = 9.8 \text{ V} \\ = V_L(\min)$$

$$\text{For } V_z(\max) = V_z + \Delta V_z$$

$$\Rightarrow \Delta V_z = r_z \times \Delta I_z$$


$$\Rightarrow \Delta I_z = \frac{I_z(\max) - I_z}{r_z}$$

$$= 50 \text{ mA} - 25 \text{ mA} = 25 \text{ mA}$$


$$\Rightarrow \Delta V_z = 10 \Omega \times 25 \text{ mA} = 250 \text{ mV}$$

$$\Rightarrow V_z(\max) = 10 \text{ V} + 250 \text{ mV} = 10.25 \text{ V}$$

Q2)

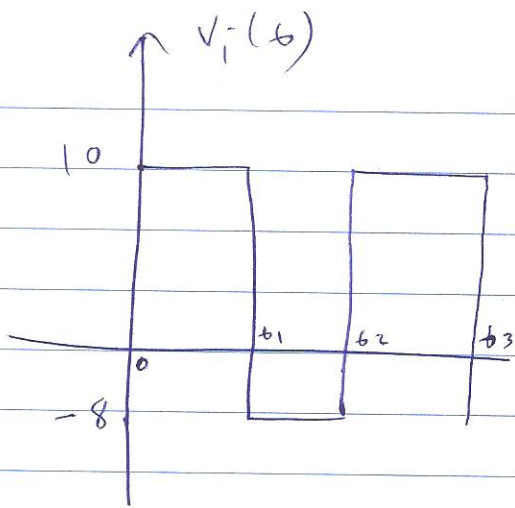


(9/10)

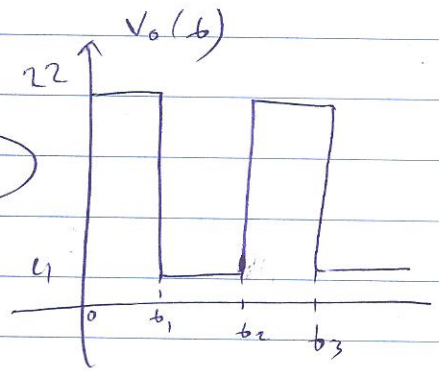

⇒ shifts up by 12V


⇒ Design =

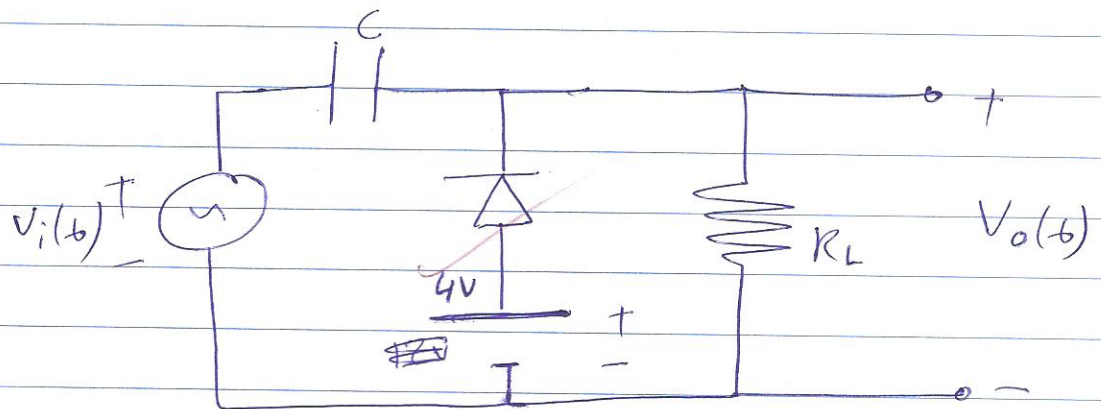

⇒ Analysis =  $2 < t < 4$


when  $V_i(t) \Rightarrow$  from  $t_1 \rightarrow t_2$

⇒  $V_o = 4$

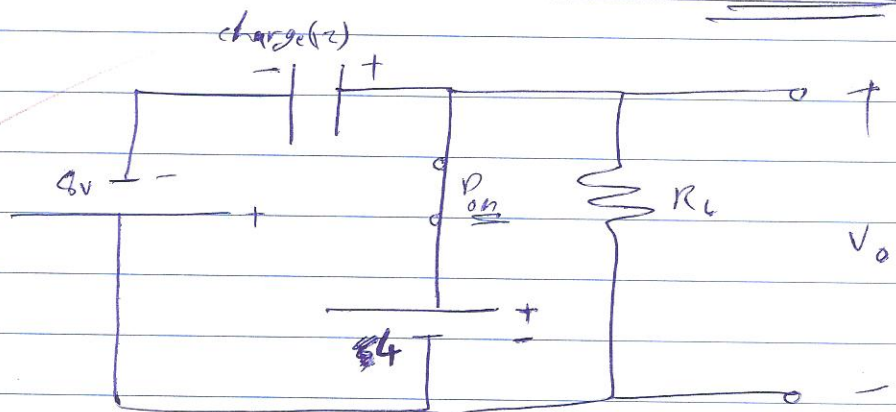

~~who when  $b_1 < b < b_2$~~

@  $4 < b < 6$

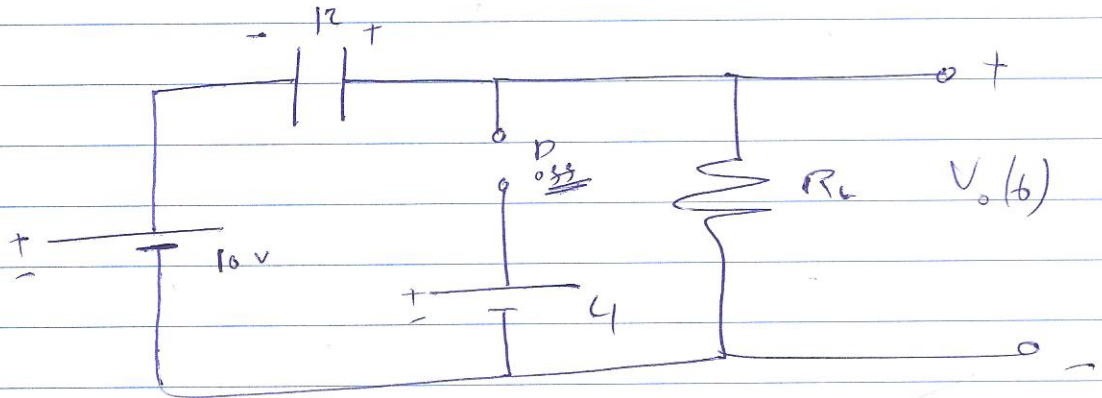

$$\Rightarrow -V_o + 12 + 10 = 0$$

$$\Rightarrow V_o = 22$$

$$R = 2$$



0


Q3) 1) DC analysis  $\Rightarrow h_{ib} = \frac{V_T}{I_{EQ}}$

- Caps open

- ACs = 0

PnP

~~2.0/k~~

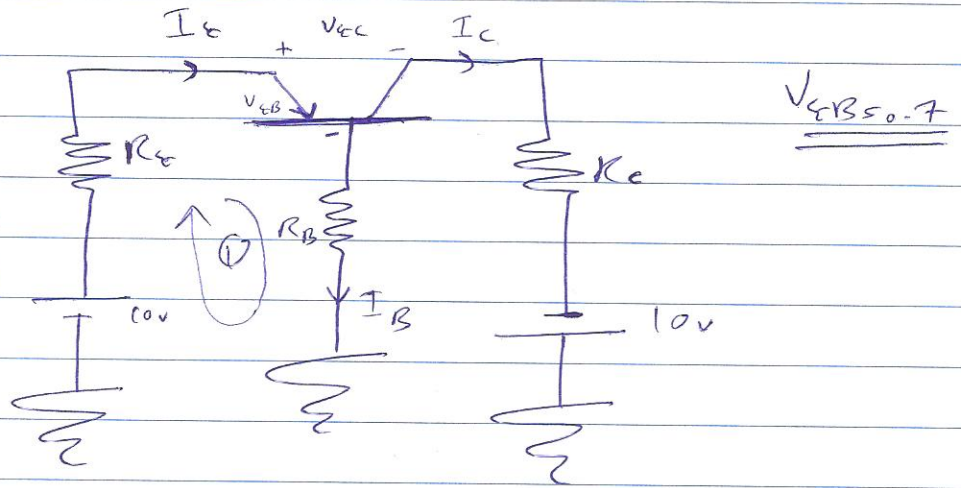

$$\text{KVL } \odot_2 \quad -10 + R_E I_E + V_{EB} + R_B I_B = 0$$

~~$$\Rightarrow -10 + R_E I_E + V_{EB} + \frac{R_B I_E}{\beta + 1}$$~~

~~$$I_E = (\beta + 1) I_B \Rightarrow I_B = \frac{I_E}{\beta + 1}$$~~

~~$$I_B = I_C$$~~

~~$$\Rightarrow -10 + 1k \times I_B$$~~

~~$$\Rightarrow -10 + 1k \times I_E + 0.7 + 10k$$~~

~~$$\alpha = \frac{I_C}{I_E} \Rightarrow I_C = \alpha I_E$$~~

~~$$\alpha I_E = (I_C + I_B) \Rightarrow I_C = I_C + I_B$$~~

$$\Rightarrow I_C = I_E - I_B \Rightarrow I_E - I_B = \alpha I_E$$

$$\Rightarrow -I_B = \alpha I_E - I_E \Rightarrow I_B = (I_E - I_E \alpha)$$

$$\Rightarrow \boxed{I_B = I_E (1 - \alpha)} \Rightarrow \text{KVL } \odot_1 \text{ في الـ } \alpha$$

$$\Rightarrow -10 + 1k \times I_c + 0.7 + 10k(1-\alpha)I_c = 0$$


$$\Rightarrow -9.3 + 1k \times I_c + 10k \times 0.01 \times I_c = 0$$

$$\Rightarrow 1100 I_c = 9.3$$

$$\Rightarrow I_c = \frac{9.3}{1100} = 8.45 \text{ mA}$$

$$\Rightarrow h_{ib} = \frac{26 \text{ mV}}{8.45 \text{ mA}} = 3.08 \approx 3$$

2) Common Base PNP  
AC analysis

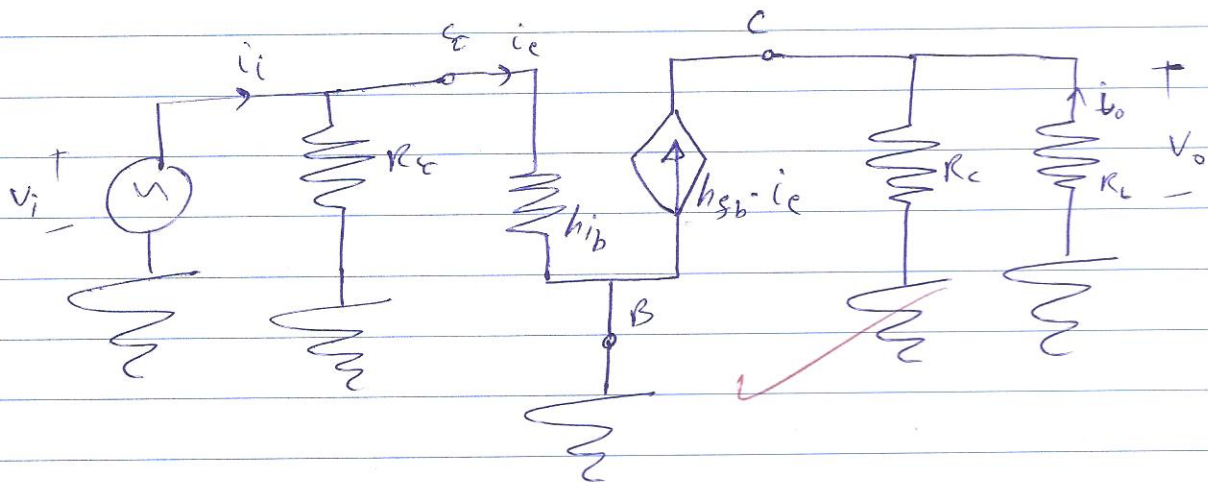

$$A_v = \frac{V_o}{v_i}$$

$$\Rightarrow V_o = -i_o \times R_L \Rightarrow \frac{V_o}{i_o} = -R_L$$

$$\Rightarrow i_o = \frac{R_C}{R_C + R_L} (-h_{sb} \cdot i_e)$$

$$\Rightarrow \frac{i_o}{i_e} = \frac{-h_{sb} R_C}{R_C + R_L}$$



$$i_e = \frac{v_i}{h_{ib}} \Rightarrow \frac{i_e}{v_i} = \frac{1}{h_{ib}}$$

$$\Rightarrow A_v = \frac{v_o}{v_i} = \frac{v_o}{i_o} \times \frac{i_o}{i_e} \times \frac{i_e}{v_i}$$


$$= R_L \times \frac{\cancel{h_{ib}} \times R_c}{R_c + R_L} \times \frac{1}{h_{ib}}$$

$$= ?$$

-0.5

Q4) a)  $h_{ie} = \frac{V_T}{I_B}$

DC analysis

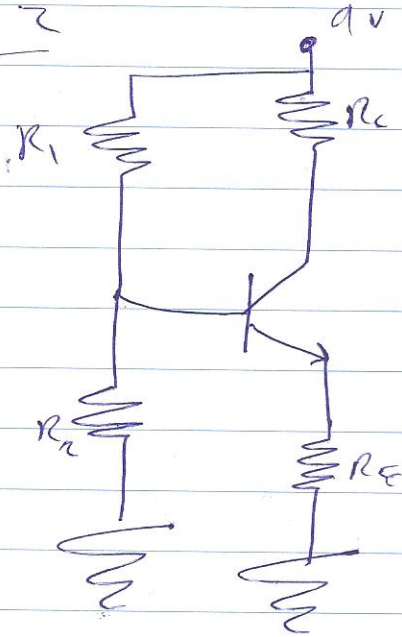

13.5/20

$$R_{dc} = R_c + R_e$$

$$= 220 + 100$$

$$= 320$$


⇒ find  $I_B$

3/4

1

$$V_{oh} = \frac{R_2}{R_2 + R_1} V_{cc}$$
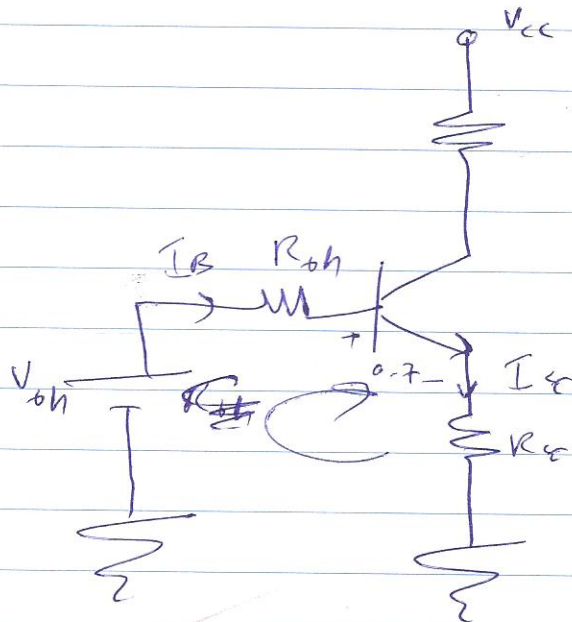
$$R_{oh} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$




$V_{BE} = 0.7$

$$KVL \Rightarrow -V_{oh} + I_B R_{oh} + V_{BE} + I_E R_e = 0$$

$$\Rightarrow -V_{oh} + I_B R_{oh} + V_{BE} + (1 + \beta) I_B R_e = 0$$

⇒ find  $I_B$

From AC domain  $\rightarrow$

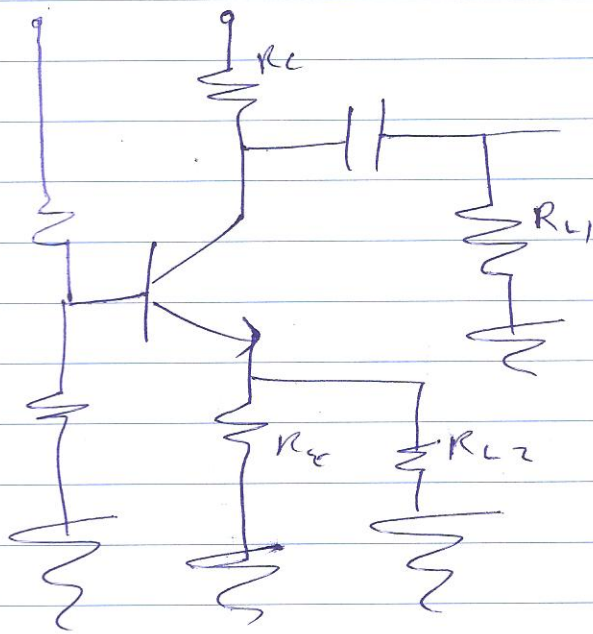


$$\Rightarrow R_{ac} = (R_E \parallel R_{L2}) + (R_C \parallel R_{L1})$$

$$\Rightarrow I_{CQ} = \frac{V_{CC}}{R_{ac} + R_{dc}}$$

$$V_{CEQ} = \frac{V_{CC}}{1 + \frac{R_{dc}}{R_{ac}}}$$


$$\Rightarrow V_{CE(t) \max} \approx 2 V_{CEQ}$$
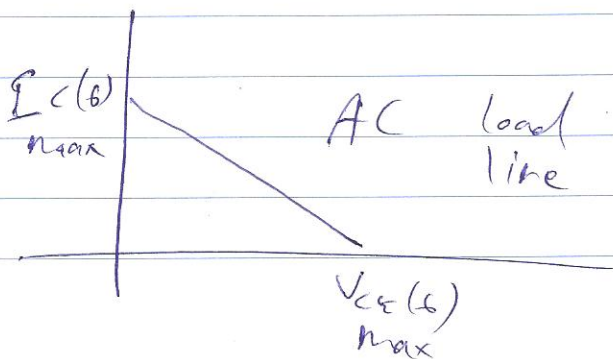
$$\Rightarrow I_{C(t) \max} \approx 2 I_{CQ}$$



$\frac{+2}{4}$   
 $-2$   
 true for design  
 for max swing  
 but we have  
 find actual values  
 may be different  
 for max

# AC analysis 2

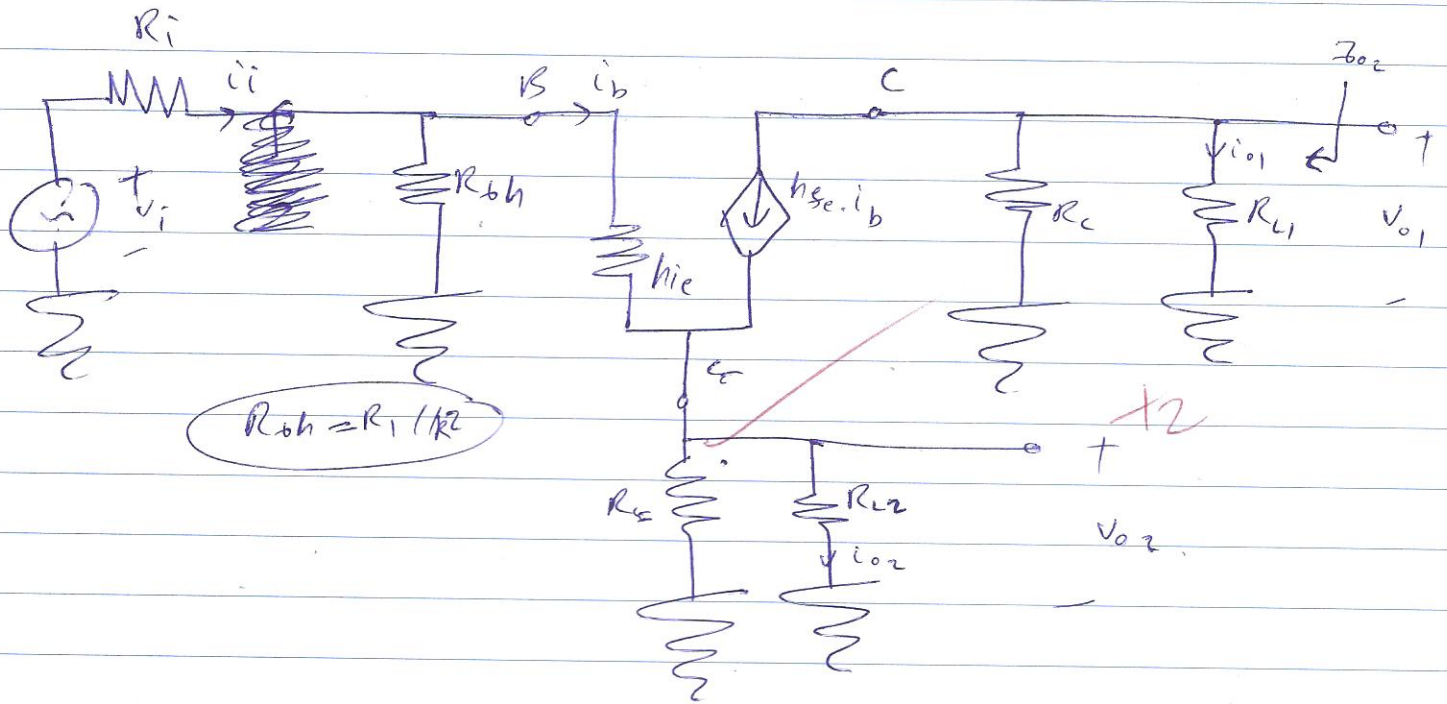


$$A_{v1} = \frac{v_{o1}}{v_i} = \frac{v_{o1}}{i_{o1}} \times \frac{i_{o1}}{i_b} \times \frac{i_b}{i_i} \times \frac{v_i}{v_i}$$

$$v_{o1} = i_{o1} R_L \Rightarrow \frac{v_{o1}}{i_{o1}} = R_L$$

$$i_{o1} = \frac{R_c}{R_c + R_L} (-h_{fe} \cdot i_b) \Rightarrow \frac{i_{o1}}{i_b} = \frac{-h_{fe} R_c}{R_c + R_L}$$

(42.5)

to find  $i_b \Rightarrow$  reflection

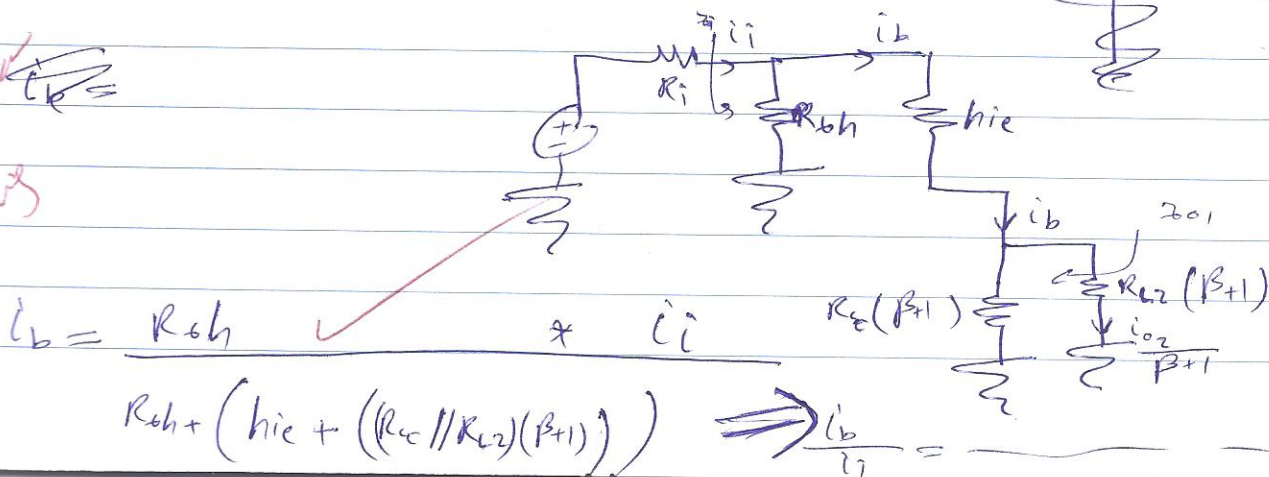

$$i_b = \frac{R_{bh}}{R_{bh} + (h_{ie} + (R_c // R_{f2})(\beta+1))} i_i$$

$$\Rightarrow \frac{i_b}{i_i} = \dots$$

$$\Rightarrow \frac{i_b}{i_i} = \frac{R_{oh}}{R_{oh}(h_i)}$$

$$i_i = \frac{V_i}{Z_i + R_i}$$

$$i_i = \frac{V_i}{\left( (h_{ie} + (R_e \parallel R_{L2})(\beta + 1)) \parallel R_{oh} \right) + R_i}$$

$\times 2$

Part (E)

$$\Rightarrow \frac{i_i}{V_i} =$$

$$D) A_{iz} = \frac{i_{o2}}{i_i} \Rightarrow \frac{i_{o2}}{\beta + 1} = \frac{R_e(\beta + 1)}{(R_e + R_{L2})(\beta + 1)} i_b$$

$$\frac{i_b}{i_i} = \frac{R_{oh}}{R_{oh} + (R_e \parallel R_{L2})(\beta + 1) + h_{ie}}$$

$\approx (C) - \text{فرجة}$

$$\Rightarrow A_{iz} = \frac{i_{o2}}{i_b} \cdot \frac{i_b}{i_i}$$

$$i_{o2} = i_e \frac{R_e}{R_e + R_{L2}} = \frac{1}{2} i_e = (1 + h_{fe}) i_b$$

$$\frac{R_e(\beta + 1)(\beta + 1)}{(R_e + R_{L2})(\beta + 1)}$$

$\frac{0.5}{2.5}$

$i_i \& i_b$  known from previous step


$$E) Z_i = h_{ie} + R$$

$\times 2$

~~$$Z_{o1} = (R_{L2} // R_c) (\beta + 1)$$~~

$$Z_{o2} = R_{L1} // R_c \quad \checkmark \quad \times 1$$

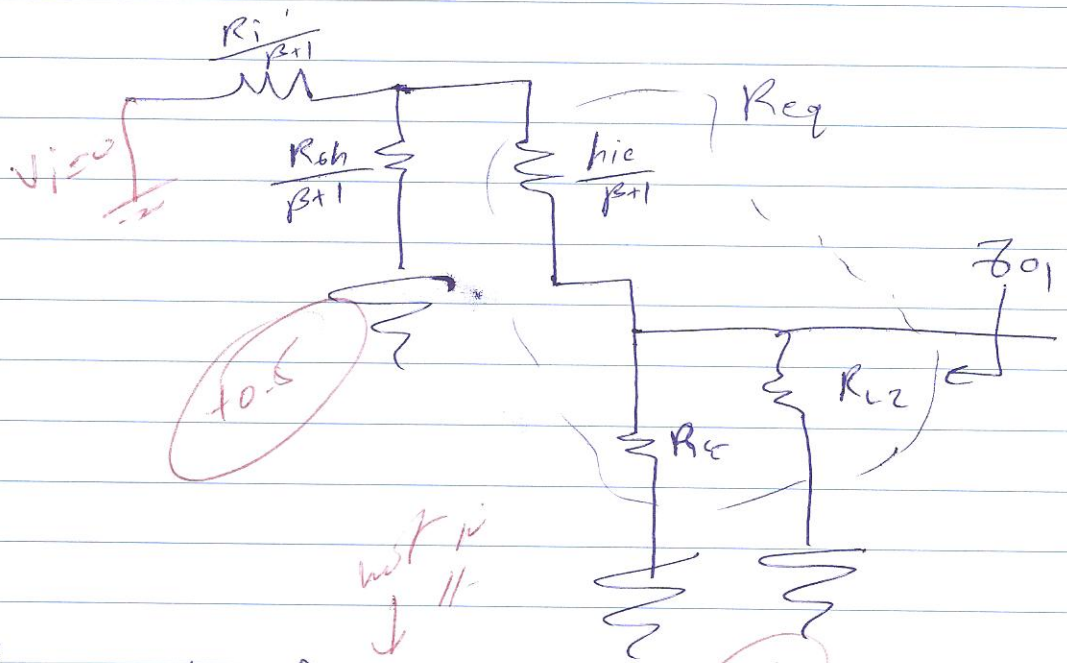to find  $Z_{o2} \Rightarrow$  reflect from Base to emitter



$$R_{eq} // Z_{o1} = (R_{L2} // R_c) // \frac{h_{ie}}{\beta + 1}$$

$$\Rightarrow Z_{o2} = \left( R_{eq} // \frac{R_{bh}}{\beta + 1} \right) + \frac{R_i}{\beta + 1}$$

$$Z_{o2} = \left( \frac{R_i}{\beta + 1} // \frac{R_{bh}}{\beta + 1} + \frac{h_{ie}}{\beta + 1} \right) // R_{L2} // R_c$$