

E<sub>NEE</sub>236  
 Questions on BJT AC Analysis (2014)

22. For the network of Fig. 8.81:  
 (a) Determine  $Z_i$  and  $Z_o$ .  
 (b) Calculate  $A_v$  and  $A_i$ .


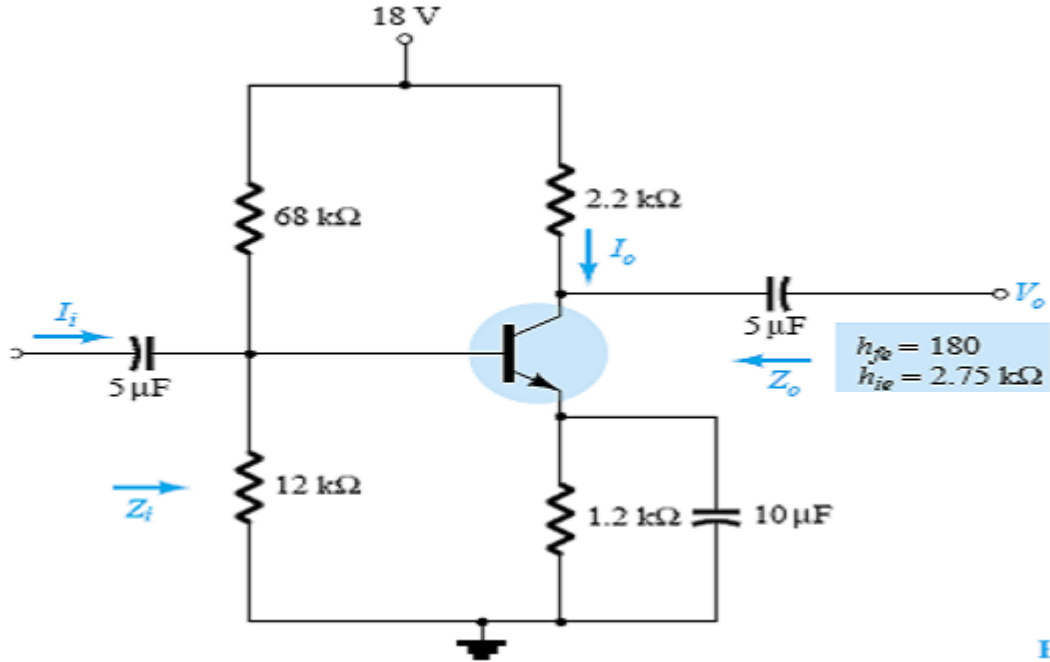



Fig. 8.81

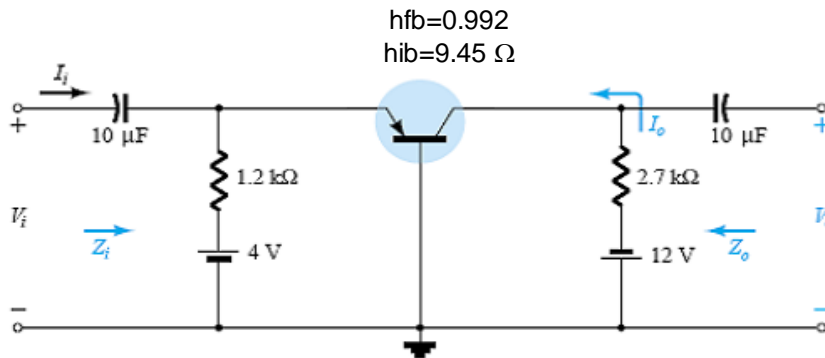- \* 23. For the common-base network of Fig. 8.82:  
 (a) Determine  $Z_i$  and  $Z_o$ .  
 (b) Calculate  $A_v$  and  $A_i$ .




\* 25. For the network of Fig. 8.83, determine:

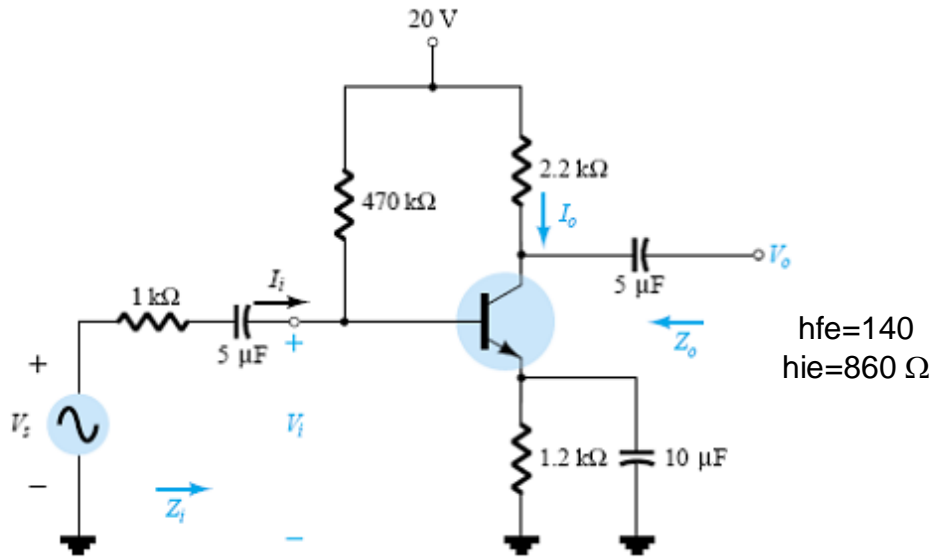- (a)  $Z_i$ .
- (b)  $A_v$ .
- (c)  $A_i = I_o/I_i$ .
- (d)  $Z_o$ .




\* 26. For the common-base amplifier of Fig. 8.84, determine:

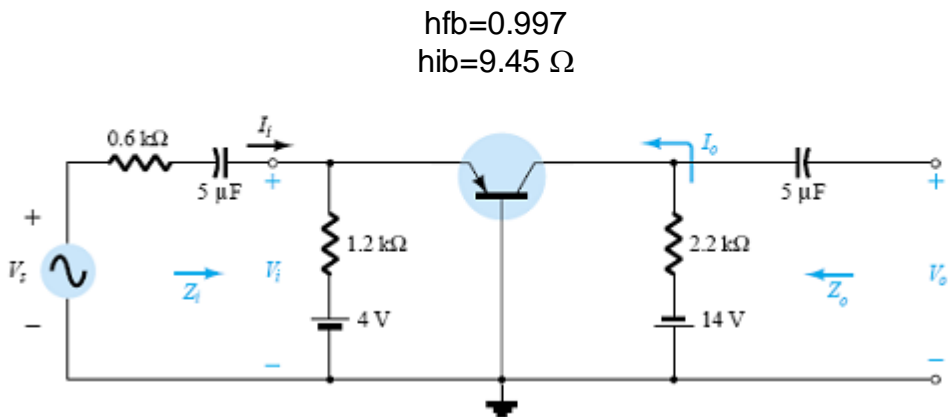- (a)  $Z_i$ .
- (b)  $A_i$ .
- (c)  $A_v$ .
- (d)  $Z_o$ .



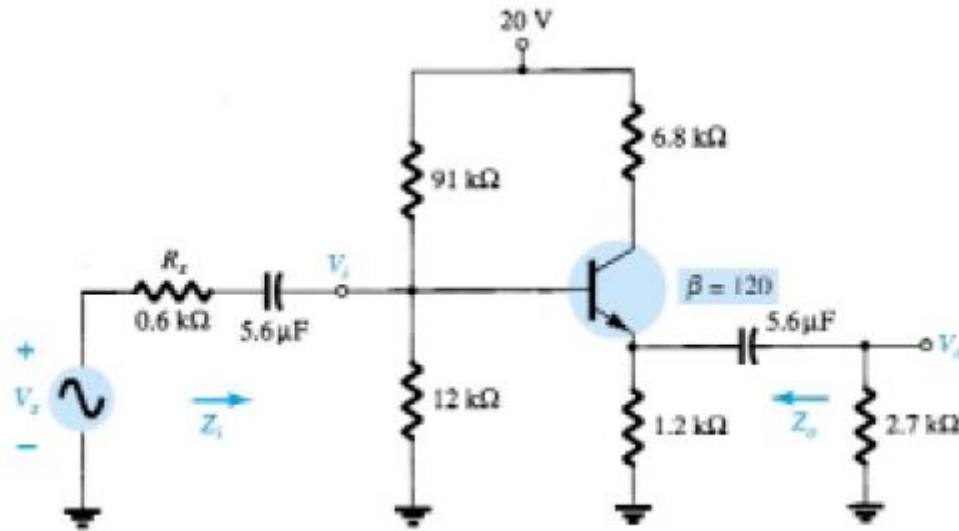Q10. Find the following parameters for the given circuit of the common collector amplifier


- DC analysis to find value of  $h_{ie}$
- AC analysis to find  $A_v$ ,  $Z_i$  and  $Z_o$



From Floyd

14. The amplifier in Figure 6–53 has a variable gain control, using a  $100\ \Omega$  potentiometer for  $R_E$  with the wiper ac-grounded. As the potentiometer is adjusted, more or less of  $R_E$  is bypassed to ground, thus varying the gain. The total  $R_E$  remains constant to dc, keeping the bias fixed. Determine the maximum and minimum gains for this unloaded amplifier.

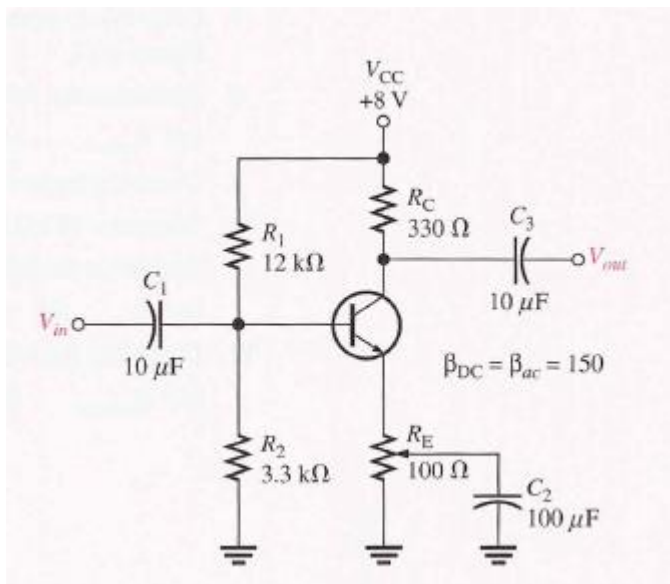**Note that  $R_E$  can vary from 0 to 100 ohms**



► FIGURE 6–53

30. If the multistage amplifier in Figure 6-57 is driven by a  $75\ \Omega$ ,  $50\ \mu\text{V}$  source and the second stage is loaded with an  $R_L = 18\ \text{k}\Omega$ , determine
- voltage gain of each stage
  - overall voltage gain

