

Homework on BJT DC
Analysis

From Boylestad

Q5. a) $I_C = \frac{V_{CC}}{R_C} = \frac{21V}{3k\Omega} = 7mA$

b) $I_B = 25\mu A$ $R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{21 - 0.7}{25\mu A} = 812k\Omega$

c) $I_{CQ} \approx 3.4mA$
 $V_{CEQ} \approx 10.75V$

d) $\beta = \frac{I_C}{I_B} = \frac{3.4 \cdot 10^{-3}}{25 \cdot 10^{-6}} = 136$


e) $\alpha = \frac{\beta}{\beta + 1} = \frac{136}{136 + 1} = 0.992$

f) $I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{21V}{3k\Omega} = 7mA$

h) $P_D = V_{CEQ} \cdot I_{CQ} = (10.75V) \times (3.4mA) = 36.55mW$

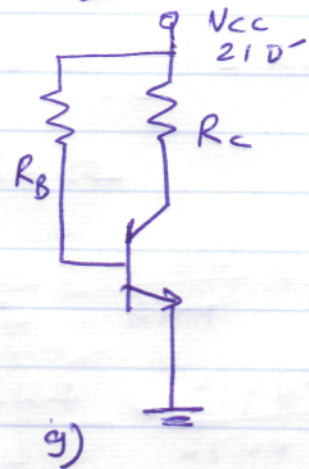i) $P_S = V_{CC} (I_C + I_B) = 21 (3.4mA + 25\mu A) = 71.92mW$

j) $P_R = P_S - P_D = 71.92 - 36.55 = 35.37mW$



Q7.

Homework on BJT DC analysis

From Boylestad

- * 5. Given the BJT transistor characteristics of Fig. 4.76:
- Draw a load line on the characteristics determined by $E = 21\text{ V}$ and $R_C = 3\text{ k}\Omega$ for a fixed-bias configuration.
 - Choose an operating point midway between cutoff and saturation. Determine the value of R_B to establish the resulting operating point.
 - What are the resulting values of I_{C_Q} and V_{CE_Q} ?
 - What is the value of β at the operating point?
 - What is the value of α defined by the operating point?
 - What is the saturation ($I_{C_{sat}}$) current for the design?
 - Sketch the resulting fixed-bias configuration.
 - What is the dc power dissipated by the device at the operating point?
 - What is the power supplied by V_{CC} ?
 - Determine the power dissipated by the resistive elements by taking the difference between the results of parts (h) and (i).


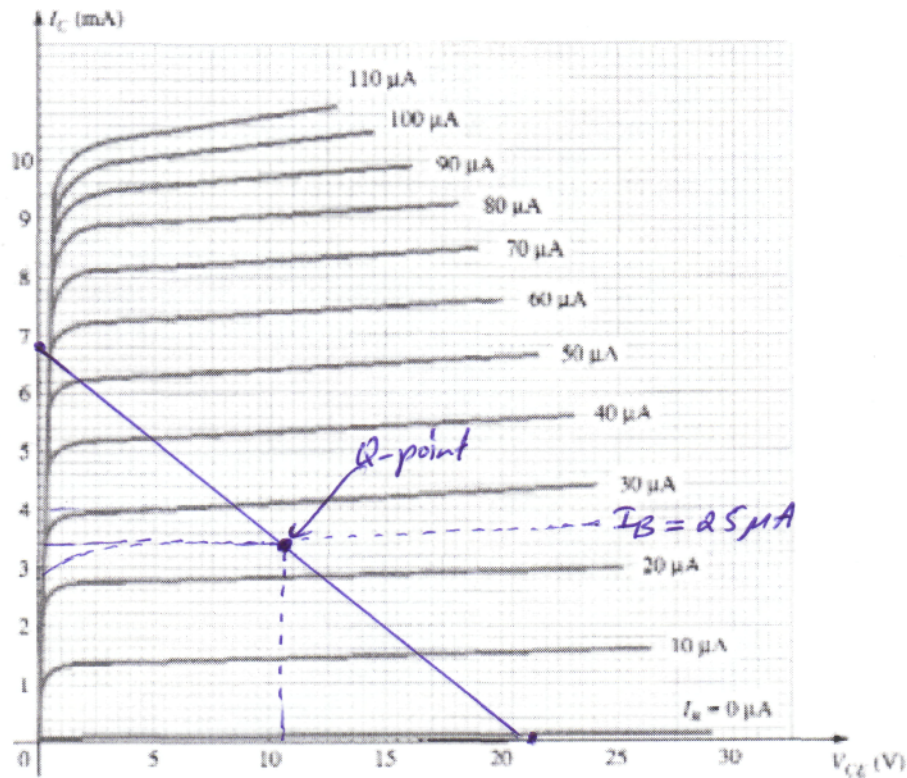


Figure 4.76 Problems 5, 10, 19, 35, 36

Q7.

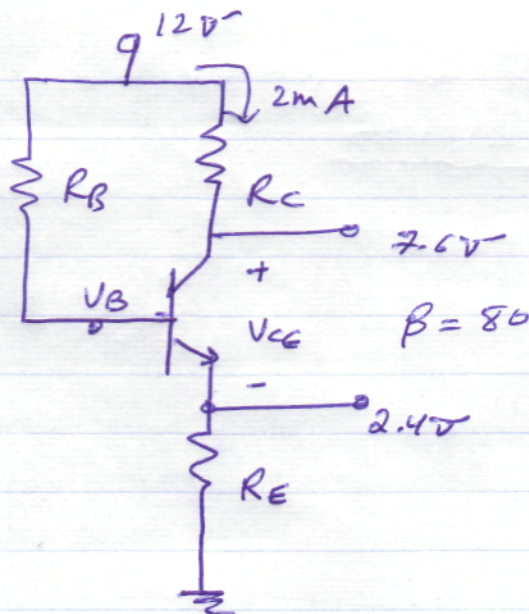

a) $R_C = \frac{V_{CC} - V_C}{I_C} = \frac{12 - 7.6}{2\text{mA}} = \frac{4.4\text{V}}{2\text{mA}} = 2.2\text{k}\Omega$

b) $I_E \approx I_C$, $V_E = I_E \cdot R_E \Rightarrow R_E = \frac{V_E}{I_E} = \frac{2.4\text{V}}{2\text{mA}} = 1.2\text{k}\Omega$

c) $R_B = \frac{V_{RB}}{I_B} = \frac{V_{CC} - V_{BE} - V_E}{I_B} = \frac{12 - 0.7 - 2.4}{\left(\frac{2\text{mA}}{80}\right)} = \frac{8.9\text{V}}{25\mu\text{A}} = 356\text{k}\Omega$

d) $V_{CE} = V_C - V_E = 7.6 - 2.4 = 5.2\text{V}$

e) $V_B = V_{BE} + V_E = 0.7 + 2.4 = 3.1\text{V}$

Q14.

(a) $I_C = \beta I_B = 100 \cdot 20\mu\text{A} = 2\text{mA}$


(b) $I_E = I_C + I_B = 2\text{mA} + 20\mu\text{A} = 2.02\text{mA}$

$V_E = I_E \cdot R_E = 2.02\text{mA} \cdot 1.2\text{k}\Omega = 2.42\text{V}$

(c) $V_{CC} = V_C + I_C R_C$
 $= 10.6 + 5.4\text{V}$
 $= 16\text{V}$

(d) $V_{CE} = V_C - V_E = 10.6 - 2.42 = 8.18\text{V}$

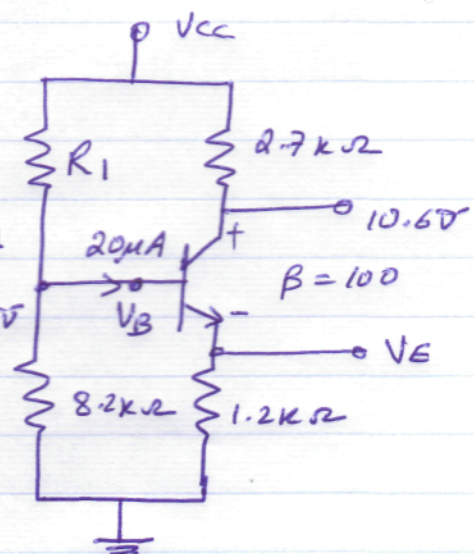(e) $V_B = V_E + V_{BE} = 2.42 + 0.7 = 3.12\text{V}$



Q14.

$$(f) \quad I_{R1} = I_{R2} + I_B \\ = \frac{3.12 \text{ V}}{8.2 \text{ k}\Omega} + 20 \mu\text{A} = 400.5 \mu\text{A}$$

$$R_1 = \frac{V_{CC} - V_B}{I_{R1}} = \frac{16 - 3.12}{400.5 \mu\text{A}} = 32.16 \text{ k}\Omega$$

Q28.


$$(a) \quad I_B = \frac{V_{EE} - V_{BE}}{R_B + (\beta + 1)R_E} \\ = \frac{12 - 0.7}{9 \text{ k}\Omega + (120 + 1)15 \text{ k}\Omega} \\ = 6.2 \mu\text{A}$$

$$(b) \quad I_C = \beta I_B = (120) 6.2 \mu\text{A} \\ = 0.744 \text{ mA}$$


$$(c) \quad V_{CE} = V_{CC} - I_C R_C - I_E R_E + V_{EE} \\ = 16 + 12 - I_C (R_C + R_E)$$

$$= 28 - (0.744 \text{ mA})(12 \text{ k}\Omega + 15 \text{ k}\Omega) \\ = 7.91 \text{ V}$$
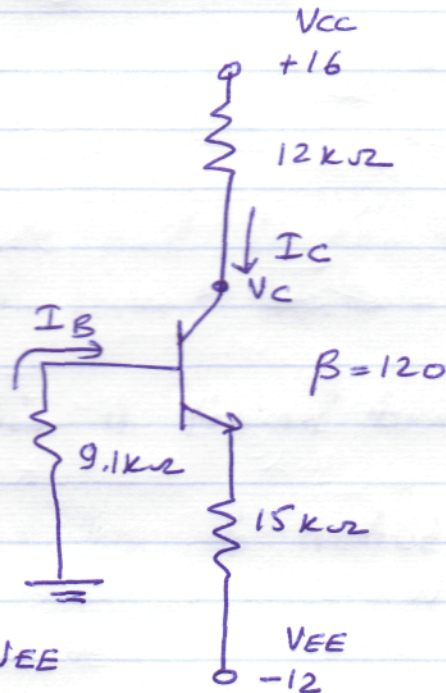
$$(d) \quad V_C = V_{CC} - I_C R_C = 16 - (0.744 \text{ mA})(12 \text{ k}\Omega) \\ = 7.07 \text{ V}$$



Q 36.

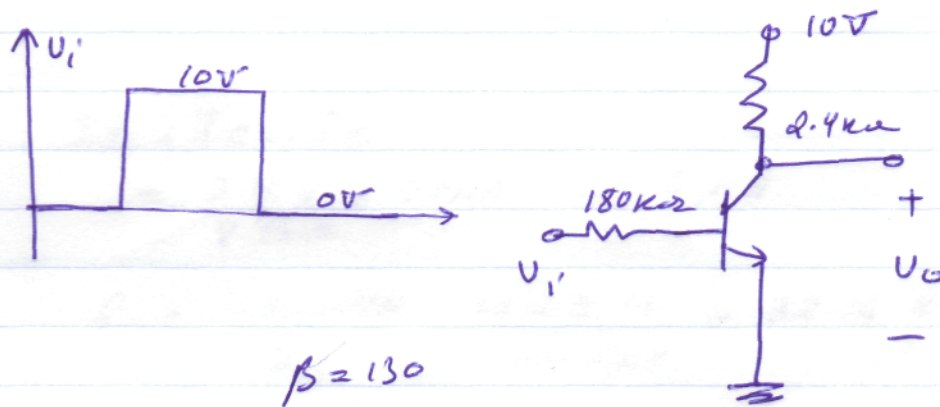

Solution

1) when $U_i = 0$, $I_B = 0$, $I_C = 0$

BJT is in cut-off mode and it can be modeled by an open circuit $\Rightarrow V_0 = 10V$

2) when $U_i = 10V$, BE junction is forward biased and BJT can be either in active mode or in saturation mode

Assume BJT in saturation mode & $V_{CE} = V_{CE(sat)} = \underline{0.2V}$

$$I_{C(sat)} = \frac{V_{CC} - V_{CE(sat)}}{R_C} = \frac{10 - 0.2V}{2.4k\Omega} = 4.167 \text{ mA}$$


$$I_{B(min)} = \frac{I_{C(sat)}}{\beta} = \frac{4.167 \text{ mA}}{30} \approx 32 \mu\text{A}$$

Now calculate actual value of I_B

$$I_B = \frac{U_i - V_{BE}}{R_B} = \frac{10 - 0.7}{180k\Omega} = 51.67 \mu\text{A}$$


Since $I_B > I_{B(min)}$
BJT is in saturation

$$V_0 = V_{CE(sat)} \approx 0.2V$$

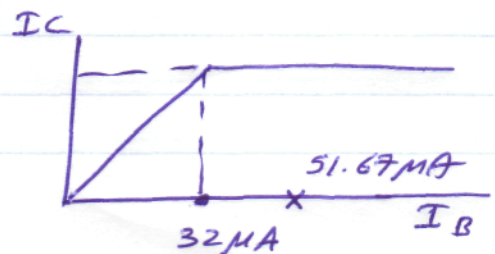

Q36.

sketch of V_o waveform

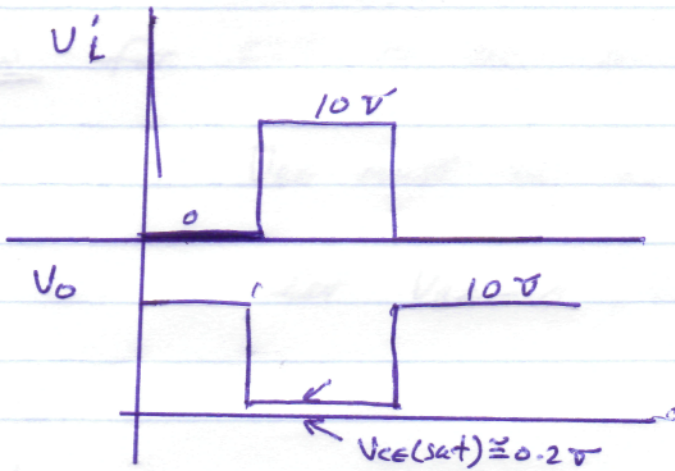

From Floyd


Q4.25

$$I_{C(sat)} = \frac{5 - V_{CE(sat)}}{10k\Omega} = 0.5 \text{ mA}$$

$$I_{B(min)} = \frac{I_{C(sat)}}{\beta} = 3.33 \mu\text{A}$$

$$V_{IN(min)} = R_B I_{B(min)} + 0.7$$

$$= 4.03 \text{ V}$$

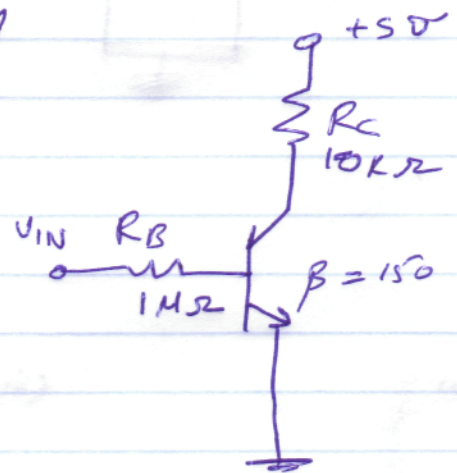


Q.26

$$I_{C(sat)} = \frac{15 - 0}{1.2k\Omega} = 12.5 \text{ mA}$$

$$I_{B(min)} = \frac{I_{C(sat)}}{\beta} = 0.25 \text{ mA}$$

$$I_B = \frac{V_i - 0.7}{R_B} > I_{B(min)}$$
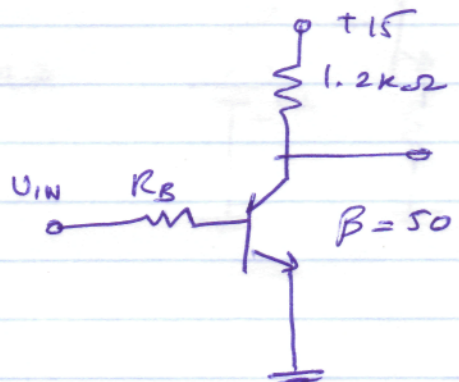
$$R_B < \frac{V_i - 0.7}{I_{B(min)}} = 17.2 \text{ k}\Omega$$



\therefore let $R_B = 15 \text{ k}\Omega$

Now for BJT to be in cut-off,

V_{BE} must be < 0.7 , and $I_B = 0$


let $V_{BE} = 0$, $\therefore V_i = 0$

Q5.10

to be in saturation

$$I_B > I_{B(\min)}$$
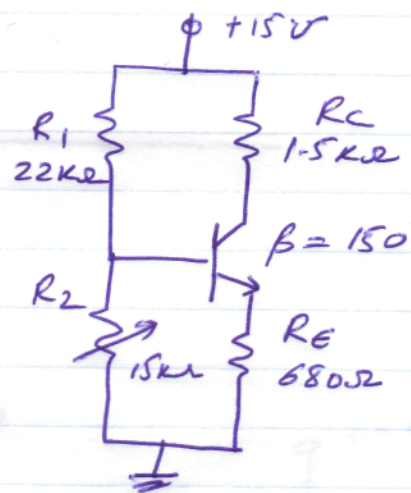
$$\begin{aligned} I_{B(\min)} &= \frac{I_{C(\text{sat})}}{\beta} \\ &= \frac{150 - 0.2}{(0.68 + 1.5) \text{ k}\Omega} \cdot \frac{1}{\beta} \\ &= 0.0453 \text{ mA} \end{aligned}$$




To find $R_2(\min)$ let $I_B = I_{B(\min)}$

$$V_{th} = R_{th} I_B + V_{BE} + I_E R_E$$

$$\begin{aligned} \frac{15 \cdot R_2}{22 + R_2} &= \frac{22 \cdot R_2}{22 + R_2} (0.0453 \text{ mA}) + 0.7 \\ &\quad + 6.834 \text{ mA} \cdot 0.68 \text{ k}\Omega \end{aligned}$$
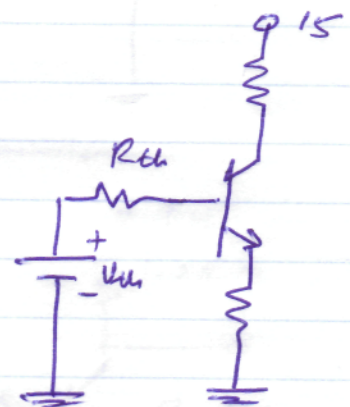
$$\Rightarrow R_2 \approx 14.79 \text{ k}\Omega$$



Q5.25

KVL for Input loop

$$10 = 0.47k\Omega \cdot I_E + V_{EB} + 10k\Omega \cdot I_B$$

$$I_E = (\beta + 1) I_B$$

$$I_B = \frac{10 - V_{EB}}{10k\Omega + 0.47k\Omega(100 + 1)} = 0.162 \text{ mA}$$

$$I_C = \beta I_B = 16.2 \text{ mA}$$

$$V_{EC} \cong 20 - (0.47k\Omega + 0.33k\Omega) \cdot 16.2 \text{ mA}$$

$$= 7 \text{ V}$$

