

ENEE236Solutions Homework on FET DC Analysis

$$1. \quad I_{DQ} = \frac{V_{DD} - V_D}{R_D} = \frac{14 - 9}{1.6 \text{ k}\Omega} = 3.125 \text{ mA}$$


$$V_{DS} = V_D - V_S = 9 - 0 = 9 \text{ V}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 \Rightarrow$$

$$V_{GS} = V_{GS(off)} \left[1 - \sqrt{\frac{I_D}{I_{DSS}}} \right]$$

$$= -4 \left[1 - \sqrt{\frac{3.125 \text{ mA}}{8 \text{ mA}}} \right] = -1.5 \text{ V}$$

$$\therefore V_{GG} = 1.5 \text{ V}$$

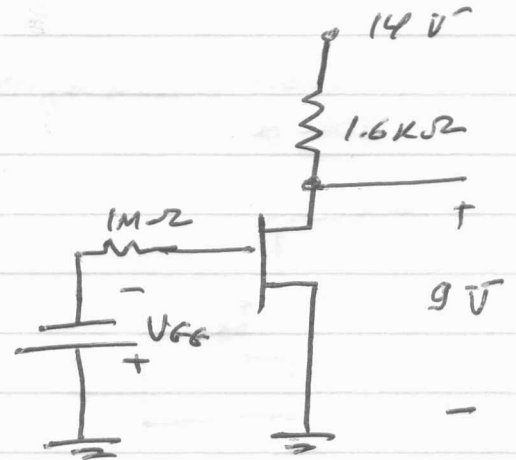

$$2. \quad - I_{DQ} = I_S = \frac{V_S}{R_S} = \frac{1.7 \text{ V}}{0.51 \text{ k}\Omega} = 3.33 \text{ mA}$$

$$- V_{GS(Q)} = -I_{DQ} R_S \quad (\text{since } V_G = 0)$$

$$= -3.33 \text{ mA} \cdot 0.51 \text{ k}\Omega = -1.7 \text{ V}$$

$$- I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = I_{DSS} \left(1 - \frac{-1.7}{-4} \right)^2 = 3.33 \text{ mA}$$

$$\Rightarrow I_{DSS} = 10.06 \text{ mA}$$

$$- V_D = V_{DD} - I_{DQ} R_D = 18 - 3.33 \text{ mA} \cdot 2 \text{ k}\Omega$$

$$= 18 - 6.66 \text{ V}$$

$$= 11.34 \text{ V}$$

$$- V_{DS} = V_D - V_S = 11.34 - 1.7 = 9.64 \text{ V}$$


$$3. - V_{GS} = V_G - V_S = 0 \quad (\text{since } V_G = V_S)$$

$$- I_D = I_{DSS} = 4.5 \text{ mA}$$

$$- V_{DS} = V_{DD} - I_D (R_D + R_S) = 20 - 4.5 \text{ mA} (2.2 \text{ k}\Omega + 0.68 \text{ k}\Omega) = 7.04 \text{ V}$$

$$- V_D = V_{DD} - I_D R_D = 20 - 4.5 \text{ mA} \cdot 2.2 \text{ k}\Omega = 10.1 \text{ V}$$
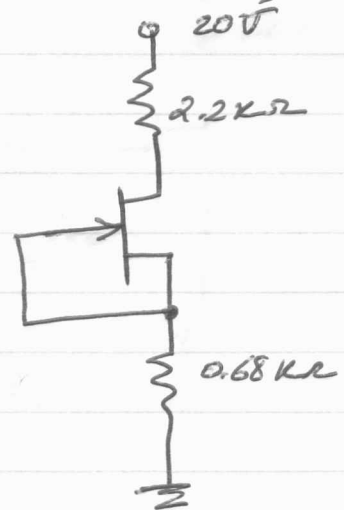
$$- V_S = I_S R_S = I_D R_S = 4.5 \text{ mA} \cdot 0.68 \text{ k}\Omega = 3.06 \text{ V}$$



4. DMOSFET, n-channel

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(\text{off})}} \right)^2$$

$$V_{GS} = V_G - V_S = 0 - (I_S R_S - 4) = 4 - I_S R_S = 4 - (0.39 \text{ k}\Omega) \cdot I_D$$

$$I_D = 8 \text{ mA} \left(1 - \frac{4 - 0.39 \text{ k}\Omega \cdot I_D}{-8} \right)^2$$

solving the quadratic equation, yields

$$\begin{cases} I_{DQ} \approx 9 \text{ mA} \\ V_{GSQ} \approx 0.5 \text{ V} \end{cases}$$

$$- V_{DS} = V_{DD} - I_D (R_D + R_S) + 4 = 18 - 9 \text{ mA} (1.2 \text{ k}\Omega + 0.39 \text{ k}\Omega) + 4 \text{ V} = 22 - 14.31 = 7.69 \text{ V}$$

$$V_S = -V_{GSQ} = -0.5 \text{ V}$$

5) n-channel E-MOSFET

$$I_D = K_n (V_{GS} - V_{GS(th)})^2$$

$$K_n = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(th)})^2} = \frac{5 \text{ mA}}{(7 - 4)^2} = 0.556 \cdot 10^{-3} \text{ A/V}^2$$

$$V_{GS} = V_{DS} = V_{DD} - I_D (1.2 \text{ k}\Omega + 0.51 \text{ k}\Omega)$$

$$V_{GS} = 22 - I_D (1.71 \text{ k}\Omega)$$

$$I_D = 0.556 \cdot 10^{-3} ((22 - I_D \cdot 1.71 \text{ k}\Omega) - 4)^2 \quad \leftarrow \text{quadratic equation}$$

$$1605.7 I_D^2 - 35 I_D + 0.18 = 0$$

$$I_{D1} = 8.31 \text{ mA} \quad \rightarrow \quad V_{GS1} = 22 - 8.31 \text{ mA} \cdot 1.71 \text{ k}\Omega$$

$$I_{D2} = 13.48 \text{ mA} \quad \rightarrow \quad V_{GS2} = 22 - 13.48 \text{ mA} \cdot 1.71 \text{ k}\Omega$$

$$= 7.873 \text{ V} > V_{GS(th)} \quad \checkmark$$

$$= 0.916 \text{ V} < V_{GS(th)} \quad \times \text{ wrong}$$

Solution

$$I_D = I_{D1} = 8.31 \text{ mA}$$

$$V_{GS} = V_{DS} = 7.873 \text{ V}$$

$$V_D = V_{DD} - I_D R_D = 22 - 8.31 \text{ mA} \cdot 1.2 \text{ k}\Omega = 12.028 \text{ V}$$

$$V_S = V_{DD} - I_D R_D = V_{DS} = 12.028 - 7.873$$

$$= 4.155 \text{ V}$$



$$6. \quad V_G = \frac{6.8 \text{ M}\Omega}{10 \text{ M}\Omega + 6.8 \text{ M}\Omega} \cdot 24 \text{ V} = 9.71 \text{ V}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{GS} = 9.71 - I_D (0.75 \text{ k}\Omega)$$

$$I_D = K_n (V_{GS} - V_{GS(th)})^2$$

$$K_n = \frac{5 \text{ mA}}{(6-3)^2 \text{ V}^2} = 0.556 \cdot 10^{-3} \text{ A/V}^2$$

$$\begin{aligned} I_D &= 0.556 \cdot 10^{-3} (9.71 - I_D (0.75 \text{ k}\Omega) - 3)^2 \\ &= 0.556 \cdot 10^{-3} (6.71 - 750 I_D)^2 \\ &= 0.556 \cdot 10^{-3} (45.03 - 10065 I_D - 562500 I_D^2) \end{aligned}$$

$$I_D = 312.52 I_D^2 - I_D 5.592 + 0.02502$$


$$0 = 312.52 I_D^2 - 6.592 I_D + 0.02502$$

$$I_{D1} = 16.129 \text{ mA} \rightarrow V_{GS1} = 9.71 - 16.129 \text{ mA} \cdot 0.75 \text{ k}\Omega = -2.38 \text{ V} \times$$

$$I_{D2} = 4.96 \text{ mA} \rightarrow V_{GS2} = 9.71 - 4.96 \text{ mA} \cdot 0.75 \text{ k}\Omega = 6 \text{ V} \checkmark$$

$$\begin{aligned} V_D &= 24 - I_D \cdot 2.2 \text{ k}\Omega \\ &= 24 - 4.96 \text{ mA} \cdot 2.2 \text{ k}\Omega \\ &= 13.09 \text{ V} \end{aligned}$$
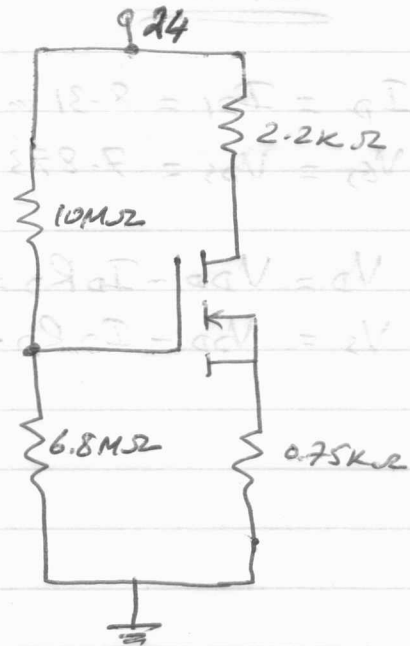
$$V_S = I_D \cdot 0.75 \text{ k}\Omega = 3.72 \text{ V}$$



$$7. \quad V_B = V_G = \frac{10k\Omega}{40k\Omega + 10k\Omega} \cdot 16V = 3.2V$$

$$- V_E = V_B - V_{BE} = 3.2 - 0.7 = 2.5V$$

$$- I_E = \frac{V_E}{R_E} = \frac{2.5}{1.2k} = 2.08mA$$

$$I_C \approx I_E = 2.08mA$$

$$I_D = I_C = 2.08mA$$

$$- I_B = \frac{I_C}{\beta} = \frac{2.08mA}{100} = 20.8\mu A$$

$$- V_C = V_S = V_G - V_{GS}$$

$$- V_{GS} = V_{GS(off)} \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

$$= -6 \left(1 - \sqrt{\frac{2.08mA}{6mA}} \right) = -2.47V$$

$$- V_C = 3.2 - (-2.47) = 5.67V$$

$$- V_D = V_{DD} - I_D R_D = 16 - 2.08mA \cdot 2.2k\Omega = 11.42V$$

$$- V_{CE} = V_C - V_E = 5.67 - 2.5 = 3.17V$$

$$- V_{DS} = V_D - V_S = 11.42 - 5.67 = 5.75V$$

