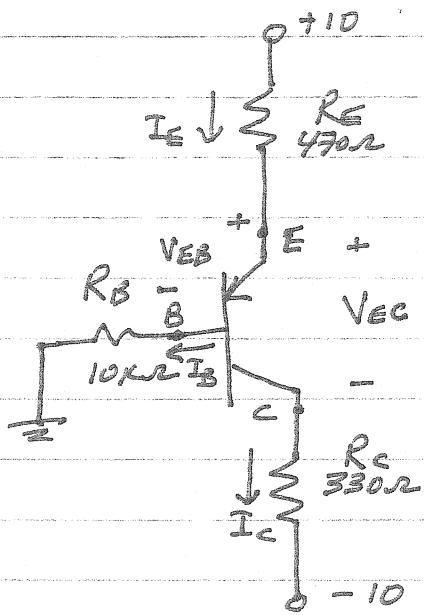


25.



### Solution 1

- Since  $V_E > V_B$ ,  $\therefore$  BJT can be either in linear mode or in saturation mode  
EB junction is forward biased
- Assume BJT in linear (Active) mode

### KVL for input loop

$$10 - I_E R_E - V_{EB} - I_B R_B = 0$$

$$I_E = (\beta + 1) I_B$$

$$I_E = \frac{10 - V_{EB}}{R_E + \frac{R_B}{\beta + 1}} = \frac{10 - 0.7}{470 + \frac{10k\Omega}{101}} = 16.344 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = 16.182 \text{ mA}$$

### KVL for Output loop

$$10 - I_E R_E - V_{EC} - I_C R_C + 10 = 0$$

$V_{EC} = 20 - I_E R_E - I_C R_C = 6.978 \text{ V}$  which is higher than  $V_{EC(\text{sat})} \Rightarrow$

$\therefore$  BJT is in linear mode

### Solution 2

- If we assume BJT in Saturation


$$I_C(\text{sat}) \approx \frac{V_{EE} + V_{CC}}{R_C + R_E} = \frac{20}{330 + 470} = 25 \text{ mA}$$

$$I_B(\text{min}) = \frac{25 \text{ mA}}{100} = 250 \mu\text{A}$$

Now actual value of  $I_B$ ?


$$I_E = \frac{10 - 0.7}{470 + \frac{10 \times 2}{101}} = 16.344 \text{ mA}$$
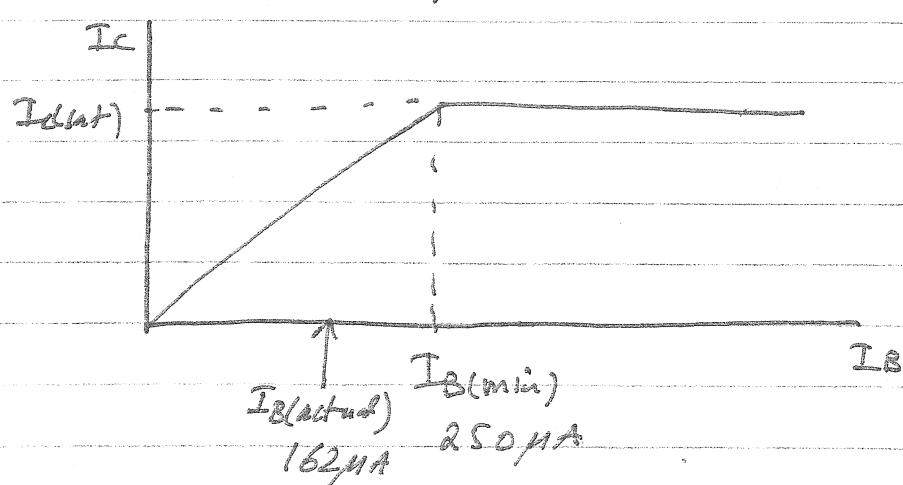
$$I_B(\text{actual}) = \frac{I_E}{\beta + 1} = 162 \mu\text{A}$$



$\therefore$  Since  $I_B(\text{actual}) < I_B(\text{min})$ , BJT is not in saturation  
it is in linear mode

26.

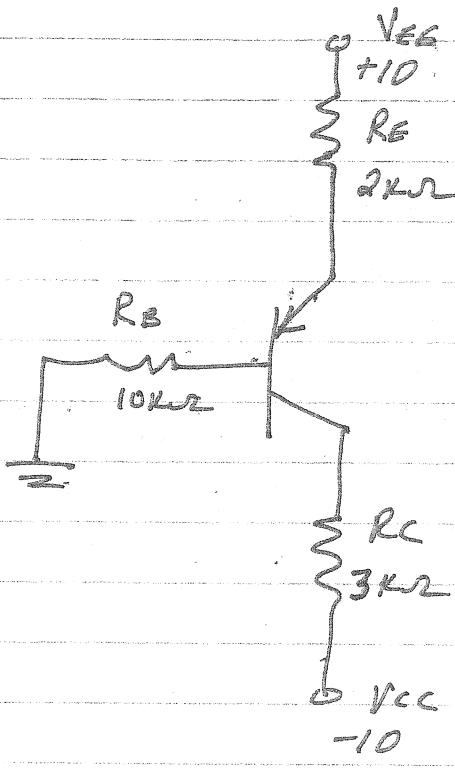

Solution : BJT is either in Saturation or linear Mode since EB junction is forward biased

- Assume it is in linear Mode

$$I_E = \frac{10 - 0.7}{2k\Omega + \frac{10k\Omega}{101}} = 4.43 \text{ mA}$$

$$I_C = \frac{\beta}{\beta+1} I_E = \alpha I_E = 4.39 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = 43.9 \mu\text{A}$$

$$- V_{EC} = 20 - I_E R_C - I_C R_C$$

$$= -2.02 \text{ V} < V_{EC(\text{sat})} \Rightarrow \text{BJT is in saturation Mode \&} \\ V_{EC} = V_{EC(\text{sat})} \approx 0.2 \text{ V}$$

$$I_C = I_{C(sat)} = \frac{V_{EE} + V_{CC} - V_{BE(sat)}}{R_C + \frac{1}{2} R_S} = \frac{20 - 0.2}{3k\Omega + 2k\Omega \times 1.01} =$$

$$= 3.944 \text{ mA}$$