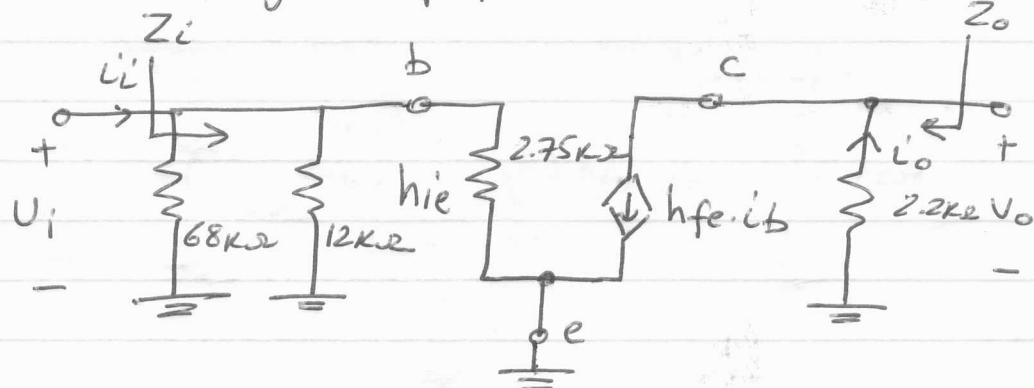


## Solutions BJT AC Analysis

Q23. using simplified BJT small signal model



$$(a) Z_i = 68\text{k}\Omega // 12\text{k}\Omega // h_{ie} =$$

$$Z_o = 2.2\text{k}\Omega$$

$$(b) A_v = \frac{V_o}{U_i} = \frac{V_o}{i_b} \cdot \frac{i_b}{U_i} = -h_{fe} \cdot 2.2\text{k}\Omega \cdot \frac{1}{2.75\text{k}\Omega} = -144$$

$$V_o = -h_{fe} \cdot i_b \cdot 2.2\text{k}\Omega$$

$$i_b = \frac{U_i}{h_{ie}}$$


$$A_i = \frac{i_o}{i_i} = \frac{i_o}{i_b} \cdot \frac{i_b}{i_i} = \frac{h_{fe} \cdot 10 \cdot 2\text{k}\Omega}{10 \cdot 12\text{k}\Omega + 2.75\text{k}\Omega} =$$

$$i_o = h_{fe} \cdot i_b$$

$$i_b = i_i \cdot \frac{(68\text{k}\Omega // 12\text{k}\Omega)}{(68\text{k}\Omega // 12\text{k}\Omega) + h_{ie}} = 141.776$$

Q23.

ac small signal equivalent circuit

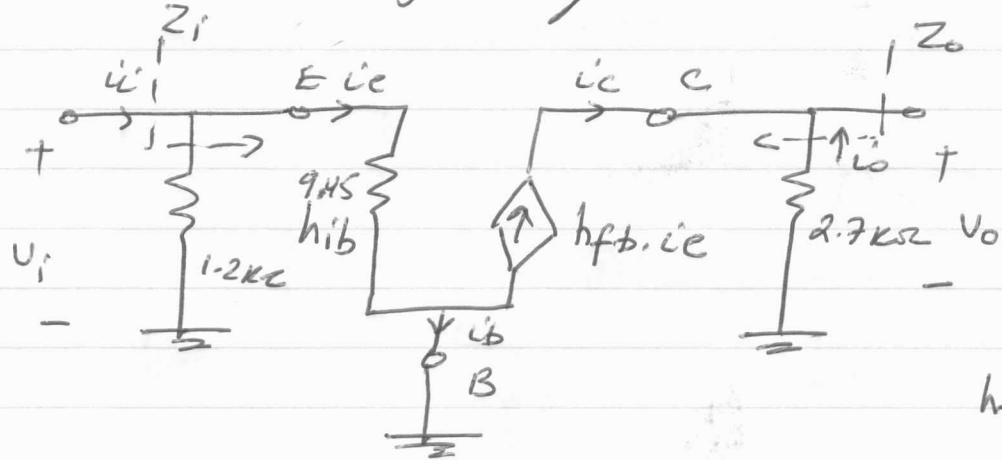

$$h_{fb} = 0.992$$

$$(a) Z_i' = 1.2k\Omega / 9.45\Omega = 9.38 \Omega$$

$$Z_o = 2.7k\Omega$$

$$(b) A_v = \frac{V_o}{U_i} \Rightarrow A_v = h_{fb} \cdot 2.7k\Omega \cdot \frac{1}{h_{ib}} = \frac{0.992 \cdot 2.7k\Omega}{9.45\Omega}$$

$$V_o = h_{fb,ie} \cdot 2.7k\Omega = 283.43$$


$$i'_e = \frac{U_i}{h_{ib}}$$

$$A_i = \frac{i'_o}{i'_i} \Rightarrow A_i = -h_{fb} \cdot \frac{1.2k\Omega}{1.2k\Omega + 9.45\Omega} = -0.9842$$

$$i'_o = -h_{fb,ie}$$

$$i'_e = \frac{1.2k\Omega}{1.2k\Omega + 9.45\Omega} \cdot i'_i$$

Q25. ac small signal equivalent circuit

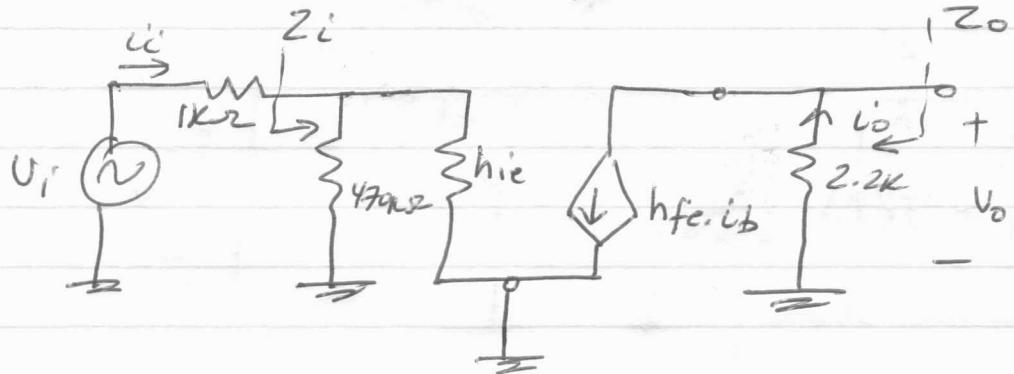

a)  $Z_i = 470k\Omega // h_{ie} = 470k\Omega // 0.86k\Omega = 0.858k\Omega$

d)  $Z_o = 2.2k\Omega$

b)  $A_v = \frac{V_o}{U_i} \Rightarrow A_v = -h_{fe} \cdot \frac{470k}{470k + h_{ie}} \cdot \frac{1 \cdot 2.2k}{0.858k\Omega + 1k\Omega} = -165.47$

$V_o = -h_{fe} \cdot i_b \cdot 2.2k$

$A_v = -165.47$

$$i_b = i_i \cdot \frac{470k\Omega}{470k\Omega + h_{ie}}$$

$$i_i = \frac{U_i}{R_i + 1k} = \frac{U_i}{0.858k\Omega + 1k\Omega}$$

c)  $A_L = \frac{i_o}{i_i} \Rightarrow A_L = h_{fe} \cdot \frac{470k\Omega}{470k\Omega + h_{ie}} = 139.774$

$i_o = h_{fe} \cdot i_b$

$$i_b = i_i \cdot \frac{470k\Omega}{470k\Omega + h_{ie}}$$

Q26. ac small signal equivalent circuit



$$a) Z_i = 1.2k\Omega // h_{ib} = 1.2k\Omega // 9.45\Omega = 9.38 \Omega$$

$$b) A_i = \frac{i_o}{i_i} \Rightarrow A_i = \frac{i_o}{i_e} \cdot \frac{i_e}{i_i} = -h_{fb} \cdot \frac{1.2k\Omega}{1.2k\Omega + 9.45\Omega}$$

$$i_o = -h_{fb} \cdot i_e$$

$$i_e = i_i \cdot \frac{1.2k\Omega}{1.2k\Omega + h_{ib}}$$

$$= -0.997 \cdot 0.992$$

$$= -0.989$$

$$c) A_v = \frac{v_o}{v_i} \Rightarrow A_v = \frac{v_o}{i_e} \cdot \frac{i_e}{i_i} \cdot \frac{i_i}{v_i}$$


$$v_o = +h_{fb} \cdot i_e \cdot 2.2k\Omega$$

$$i_e = i_i \cdot \frac{1.2k\Omega}{1.2k\Omega + 9.45\Omega}$$

$$i_i = \frac{v_i}{0.6k\Omega + Z_i}$$

$$= -h_{fb} \cdot 2.2k\Omega \cdot \frac{1.2k\Omega}{1.2k\Omega + 9.45} \cdot \frac{1}{0.6k\Omega + Z_i}$$

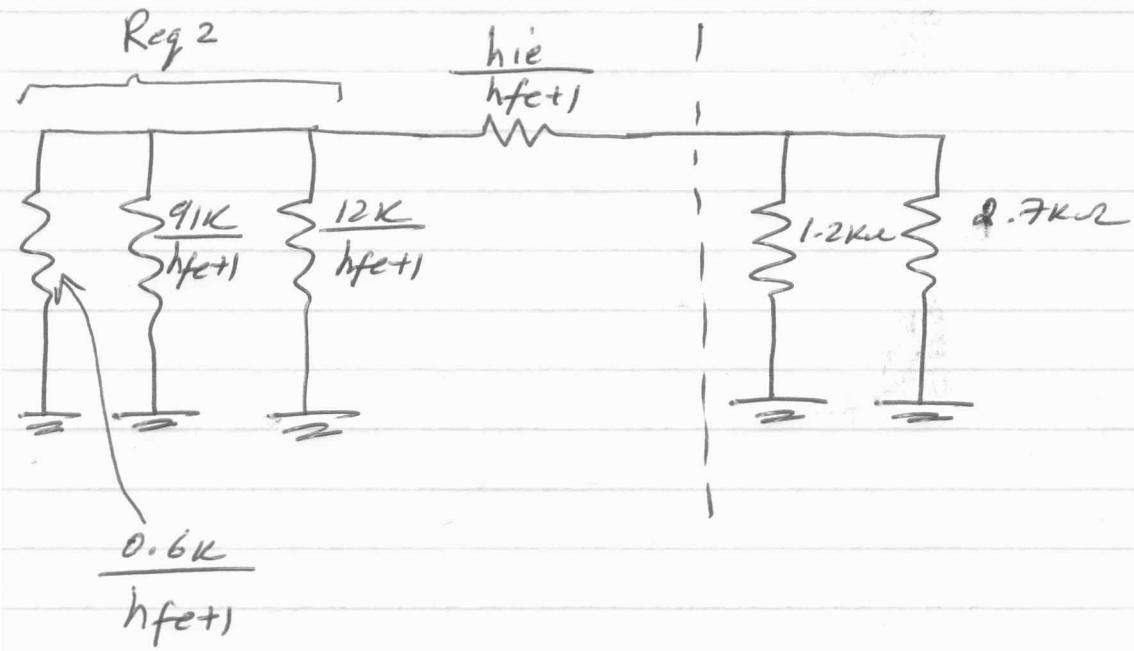3)  $Z_o \rightarrow$  need to reflect all impedances from base to emitter thru, ~~transistor~~



note that input source  $V_i$  was shorted

$$Z_o = (2.7k \parallel 1.2k\Omega) \parallel \left( \frac{hie}{hfe+1} + Req2 \right)$$

where


$$Req2 = \frac{12k}{hfe+1} \parallel \frac{91k}{hfe+1} \parallel \frac{0.6k}{hfe+1}$$

Q10.

DC analysis is required to find  $h_{ie}$ ?

where  $h_{ie} = \frac{V_T}{I_{BQ}}$ ,  $V_T \approx 26 \text{ mV}$

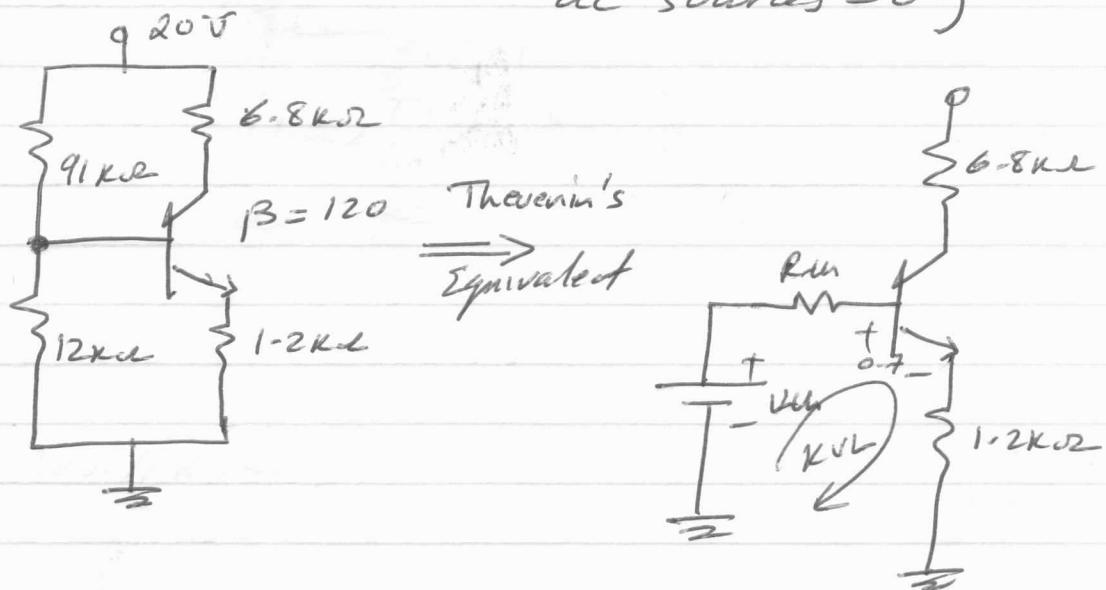DC equivalent circuit (all caps are open & ac sources = 0)



where  $V_{th} = \frac{12k\Omega}{12k\Omega + 9k\Omega} \cdot 20 = 2.33 \text{ V}$

$R_{th} = 9k\Omega // 12k\Omega = 10.6k\Omega$


KVL for input loop

$$V_{th} - I_B R_{th} - 0.7 - I_B (\beta + 1) \cdot 1.2k\Omega = 0 \Rightarrow$$

$$I_{BQ} = \frac{V_{th} - 0.7}{R_{th} + 1.2k\Omega(\beta + 1)} = \frac{2.33 - 0.7}{10.6k\Omega + 1.2k\Omega \cdot 121} = 10.46 \mu\text{A}$$

$$h_{ie} = \frac{26 \text{ mV}}{10.46 \mu\text{A}} = 2485 \text{ S}^{-1}$$

Now ac equivalent circuit

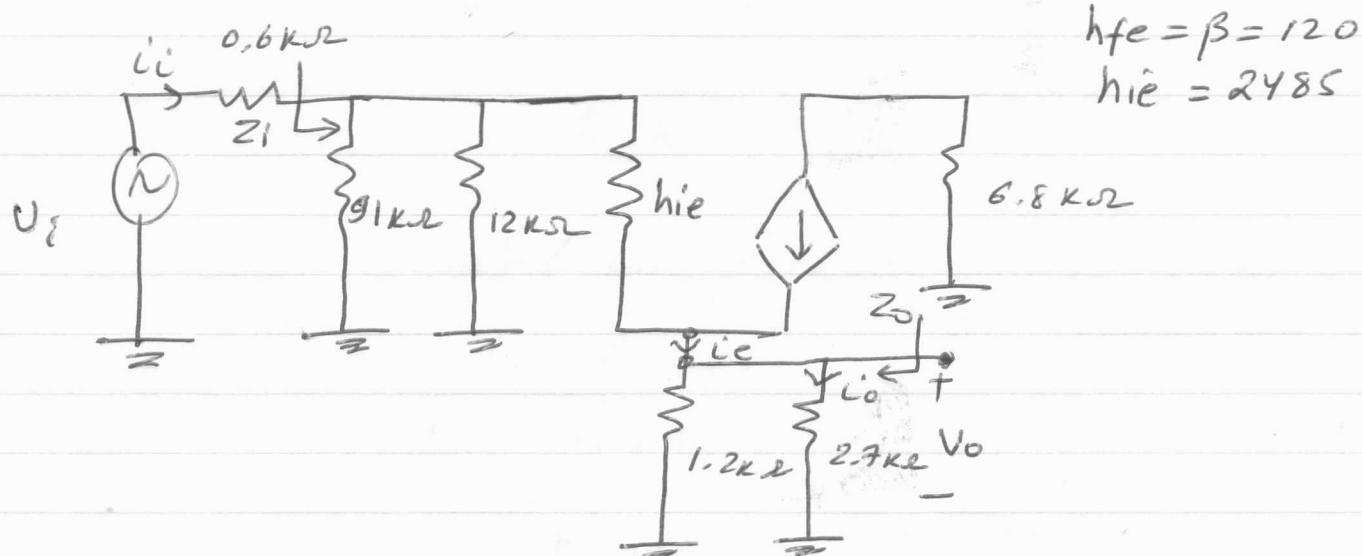

$$1) \quad A_v = \frac{V_o}{U_i}$$

$$V_o = i_e (1.2 k\Omega // 2.7 k\Omega)$$

$$i_e = i_b (h_{fe} + 1)$$

$$i_b = \frac{U_i}{0.6 k\Omega + Z_i}$$

2)  $Z_i \rightarrow$  need to reflect the  $1.2 k\Omega$  &  $2.7 k\Omega$  from emitter to base

