

BJT ac Analysis part2 (Floyd)


$$6.14 \quad V_{TH} = \frac{3.3K}{3.3K+12K} \cdot 8 = 1.725V$$

$$R_{TH} = 3.3K \parallel 12K = 2.59K$$

$$I_E = \frac{1.725 - 0.7}{0.1K + 2.59K} = 8.749mA$$

$$h_{ie} = \frac{\beta V_T}{I_E} = \frac{151}{8.749mA} = 17.25 \Omega$$

as small signal Equivalent circuit

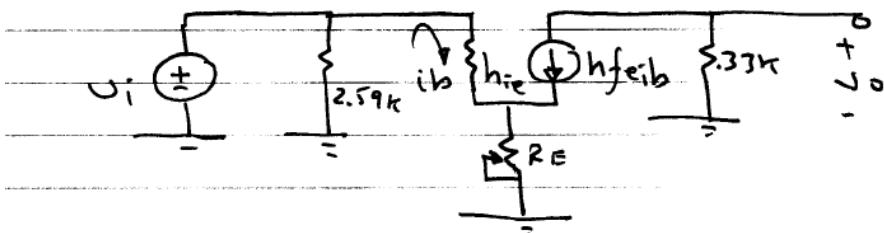

$$V_o = -(0.33K)h_{fe}i_b$$

$$i_b = \frac{U_i}{h_{ie} + (h_{fe} + 1)R_E}$$

$$A_v = \begin{cases} -112.5 & \text{for } R_E = 0 \\ -2.17 & \text{for } R_E = 100\Omega \end{cases}$$


23

$$h_{ie1} = 227.7 \text{ k}$$

$$h_{ie2} = 2h_{ie1} = 455.4 \text{ k}$$

$$h_{fED} = h_{fe}, h_{fer} = 15000$$

ac small signal Equivalent circuit

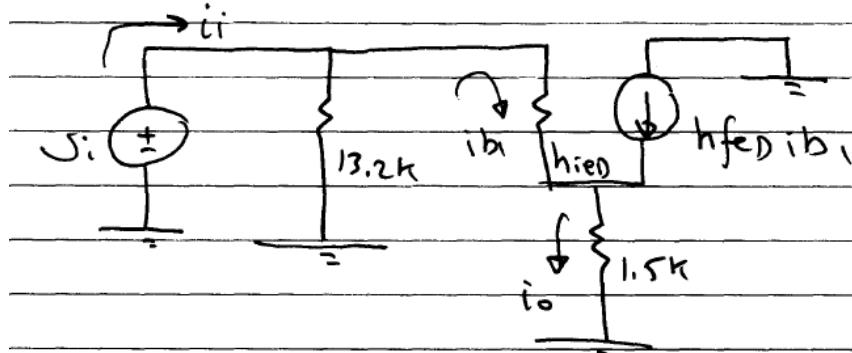

$$i_o = (1 + h_{fED}) i_b$$

$$i_b = \frac{13.2k}{13.2k + h_{ie1} + 1.5k (1 + h_{fED})} i_i$$


$$A_i = \frac{i_o}{i_i} = 8.62$$

6.30

From dc analysis : $h_{ie1} = h_{ie2} = VT/IBQ = 1.97 \text{ k}$

Ac analysis:

Small signal equivalent circuit:

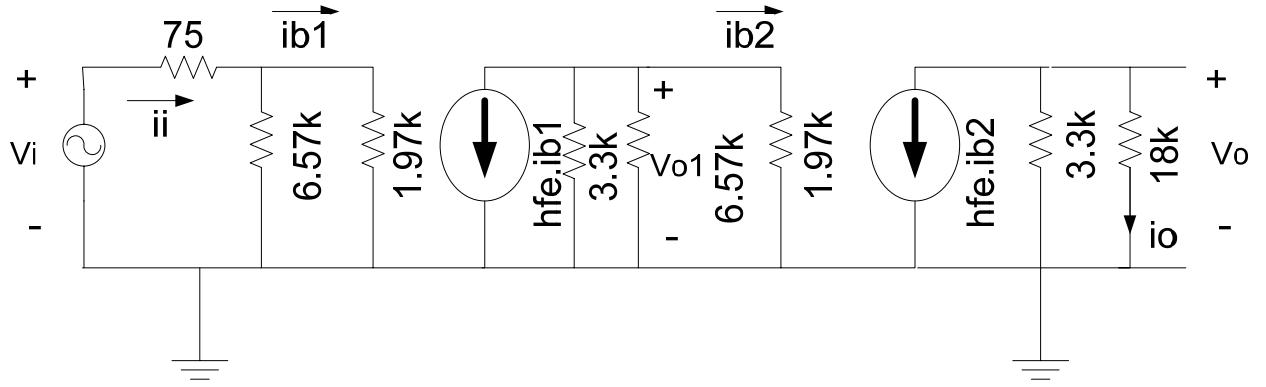

$$Av_2 = V_o / V_{o1}$$

$$Av_2 = V_{o1} / V_i$$

$$V_o = -h_{fe} \cdot ib_2 \cdot (3.3k // 18k)$$

$$ib_2 = [-h_{fe} \cdot ib_1 \cdot (3.3k // 6.57k)] / [(3.3k // 6.57k) + 1.97k]$$

$$V_{o1} = -h_{fe} \cdot ib_1 \cdot (3.3k // 5.67k // 1.97k)$$

$$ib_1 = ii \cdot 6.57k / (6.57k + 1.97k)$$

$$ii = V_i / [(6.57k // 1.97k) + 0.075k]$$

$$\begin{aligned} Av_2 &= (V_o / ib_2) \cdot (ib_2 / ib_1) \cdot (ib_1 / V_{o1}) \\ &= -247.73 \end{aligned}$$

$$\begin{aligned} Av_1 &= V_{o1} / V_i = (V_{o1} / ib_1) \cdot (ib_1 / ii) \cdot (ii / V_i) \\ &= -88.2 \end{aligned}$$

$$Av = Av_1 \cdot Av_2 = 21853.4$$