

ENEE 236Solutions to problems on  
Diodes & Applications

Q5.a

 $I = 0 \text{ mA}$  since diode is reverse biased

b.  $V_{20\Omega} = 20 - 0.7 = 19.3 \text{ V}$  since diode is forward biased  
 $I = 19.3/20 = 0.965 \text{ A}$


c.  $I = \frac{10 \text{ V}}{10\Omega} = 1 \text{ A}$  since center branch is open

Q7. (a)  $V_o = \frac{2k}{2k+2k} (20 - 0.7 - 0.3) = 9.5 \text{ V}$  (since both diodes are ON)


(b)  $I = \frac{10 + 2 - 0.7}{1.2k + 4.7k}$ , since diode is ON and by writing KVL for the loop  
 $= \frac{11.3 \text{ V}}{5.9k\Omega} = 1.915 \text{ mA}$

$$V_o = I \cdot R - 2 \text{ V} = 1.915 \text{ mA} \cdot 4.7k - 2 \text{ V} = 7 \text{ V}$$

Q29.

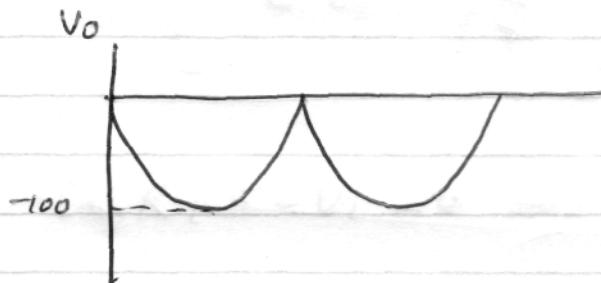


$$\text{PIV} \geq 100 \text{ V}$$

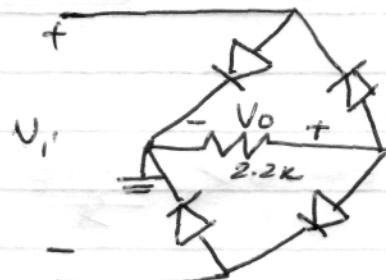


Q32 a. i) Diode open for  $U_i < 0 \Rightarrow V_o = 0$

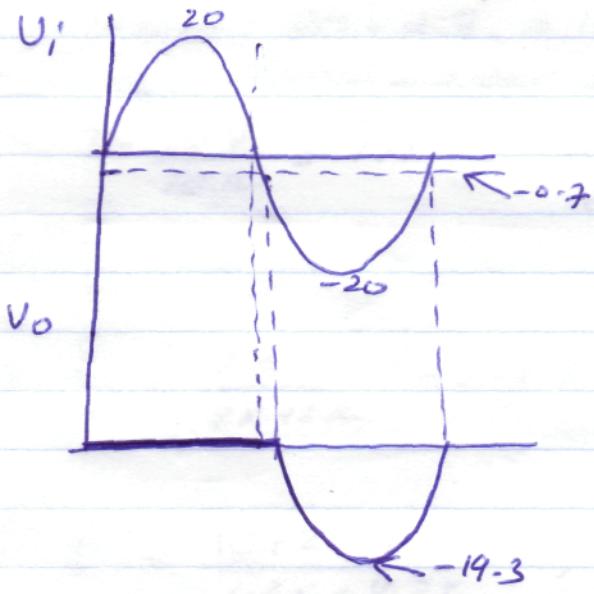2) For  $-20 < U_i \leq -0.7 \text{ V}$  diode ON  $\Rightarrow V_o = U_i + 0.7$

for example for  $U_i = -20 \Rightarrow V_o = -20 + 0.7 = -19.3$   
for  $U_i = -0.7 \Rightarrow V_o = -0.7 + 0.7 = 0 \text{ V}$




b) i) Assume diode ON

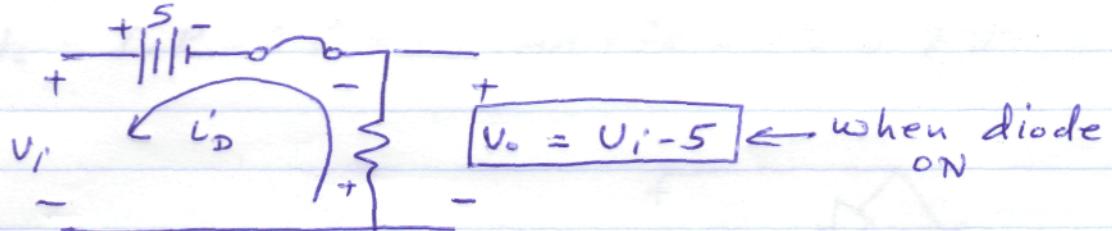


$$-i_D \cdot R + 5 - U_i = 0 \Rightarrow i_D = \frac{5 - U_i}{R} > 0 \Rightarrow$$

$5 - U_i > 0 \Rightarrow U_i < 5$  results in diode being ON

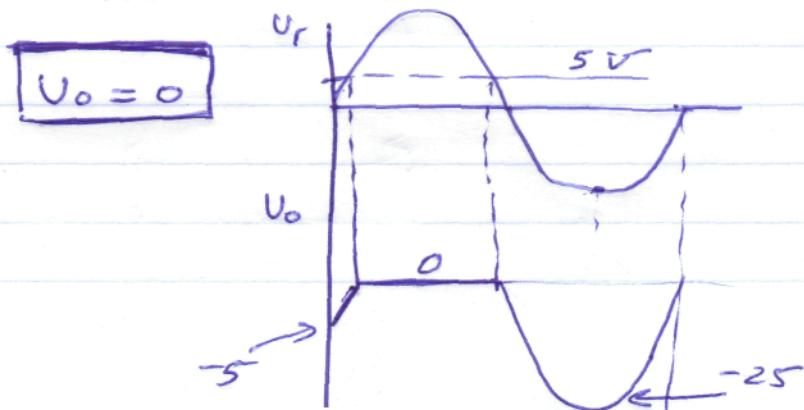
2) otherwise, when  $U_i > 5$  diode is off &  $\Rightarrow$



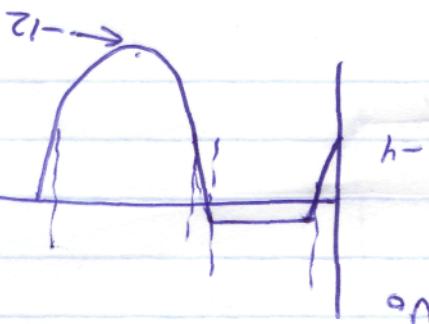


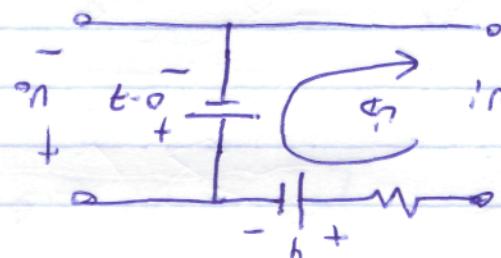
2) otherwise when  $U_i < V_D$  diode is off  $\Rightarrow U_o = U_i - V_D$

$$I_D = \frac{U_i - V_D}{R} \Leftrightarrow U_i < V_D \text{ diode will be on } \Rightarrow U_o = 0$$



$$U_i - I_D R - V_D - V_T = 0$$

1) assume diode is on  $\Leftrightarrow$

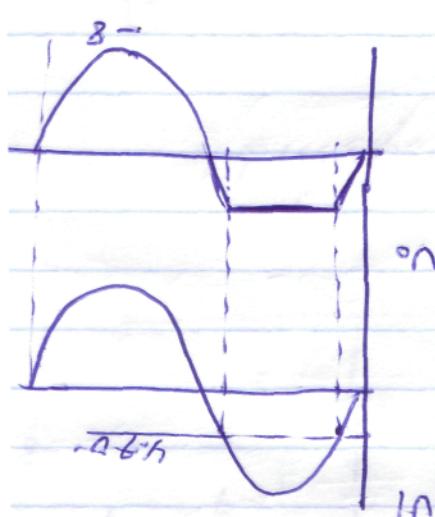
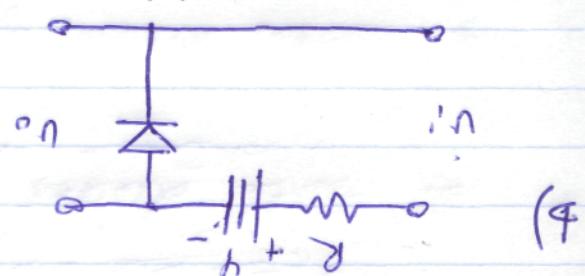


2) otherwise diode is off  $\Rightarrow U_o = U_i$

$$\frac{U_o - U_i}{R + h_f} = 0 \Leftrightarrow U_o = U_i$$

diode is on  $\Leftrightarrow U_i < V_D$
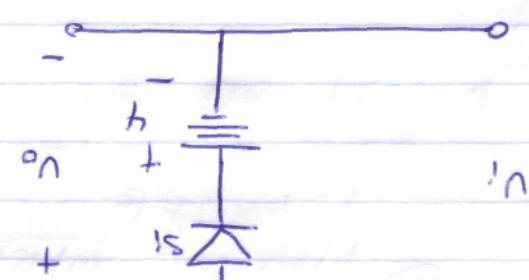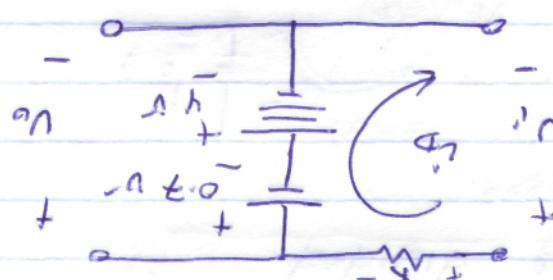
$$U_i - I_D R - h_f V_T = 0 \Leftrightarrow I_D = \frac{U_i - V_D}{R}$$




1) assume diode is on

(a)

Q36. Refer to lecture notes for solution procedure which is divided into 4-possible scenarios

1. D1 ON, D2 off

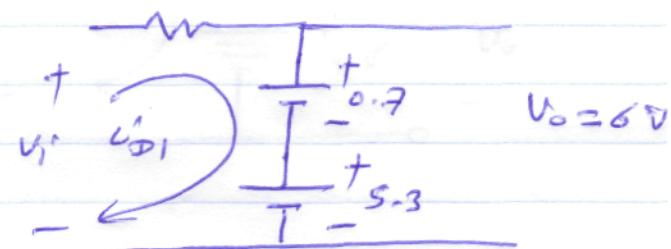

$$V_i - i_{D1} R + 6 = 0$$


$$i_{D1} = \frac{V_i + 6}{R} > 0 \Rightarrow V_i > -6$$

2. D1 OFF, D2 ON

$$V_i + i_{D2} R + 8 = 0$$

$$i_{D2} = -\frac{V_i + 8}{R} > 0$$

$$-V_i - 8 > 0 \Rightarrow V_i < -8$$

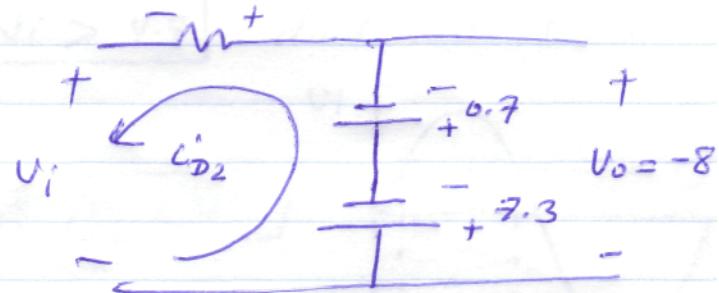


3. Both diodes on which is impossible

4. Both diodes off when


$$-8 < V_i < 6V$$

&  $V_o = V_i$

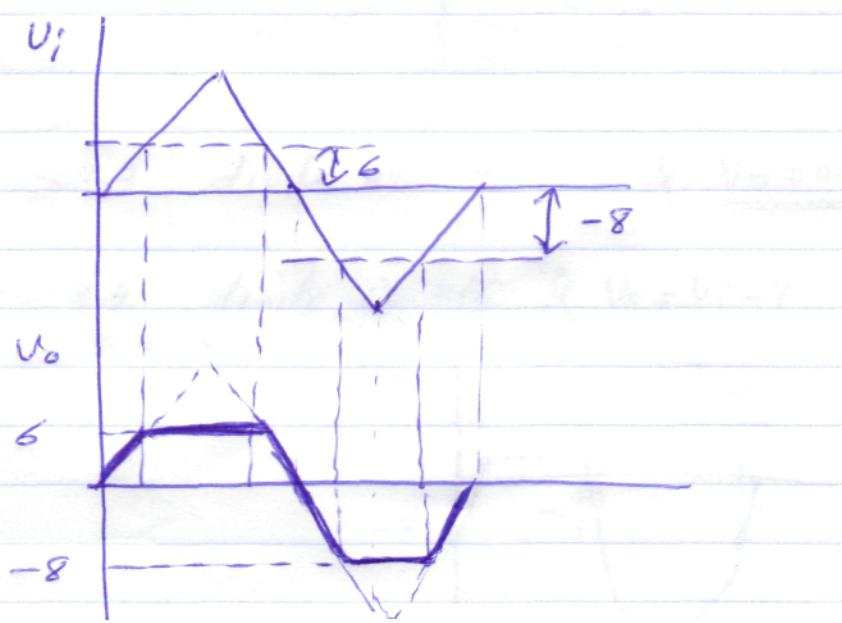


Q37. Both are clapper circuits

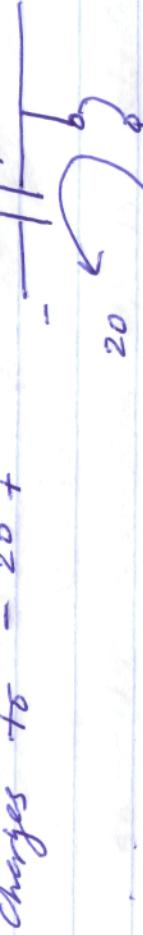
- a) Starting with  $V_i = -20 \text{ V}$  diode is ON & C charges to  $-20 +$




then diode will be off and and  $+20 +$

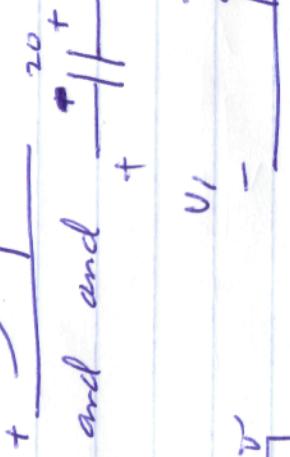

$$V_o = V_i + 20$$


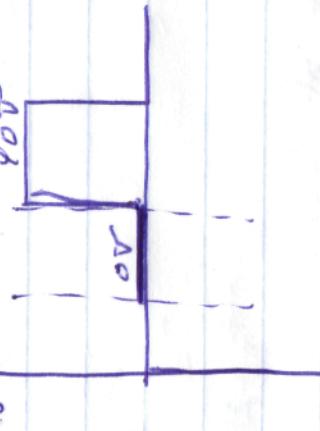


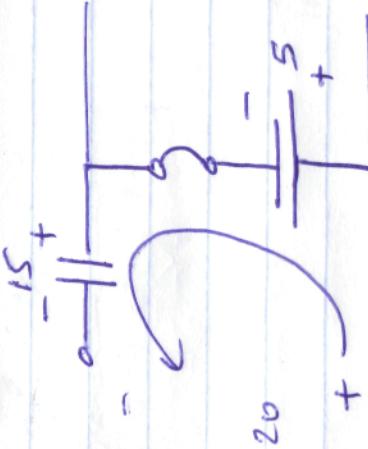- b) starting with  $V_i = -20$ , diode will be on and cap charges to  $-15 +$



$$\text{and } V_o = -5 \text{ V}$$

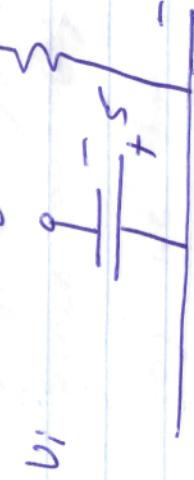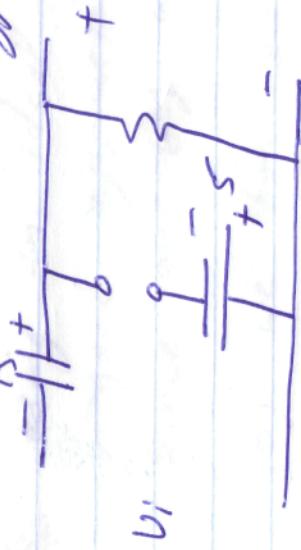
- then diode becomes off with  $V_i = +20$  and afterward



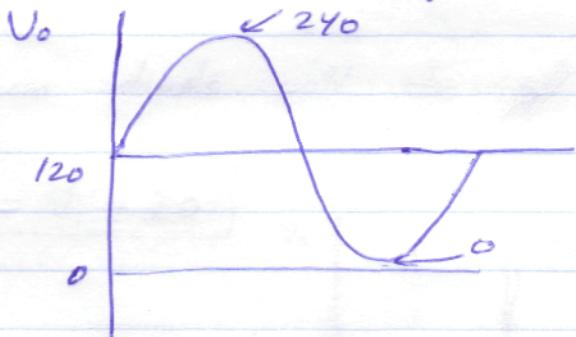Q38 a) starting with  $U_i < 0$ , diode will be on and C will be charged to  $-120$  then diode will be off and

$$V_o = U_i + 120$$


so the waveform  $U_i$  is shifted by  $+120$



b) starting with positive  $U_i \rightarrow$  diode is ON

and C is charged to  $+100$ , then diode will be off after that independant of  $U_i$


$$\boxed{V_o = U_i - 100}$$

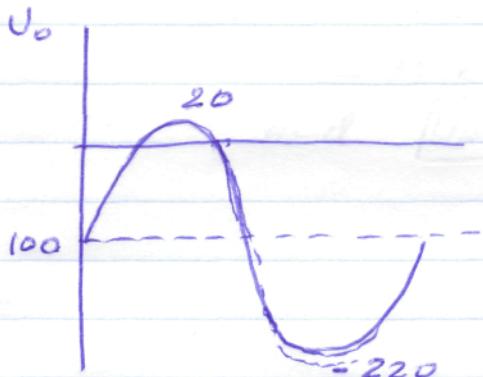

Note using an ideal diode model is a good approximation in both cases since for (a) we have 240 instead of 239.7 V & for (b) we have 20 instead of 20.7

the function required

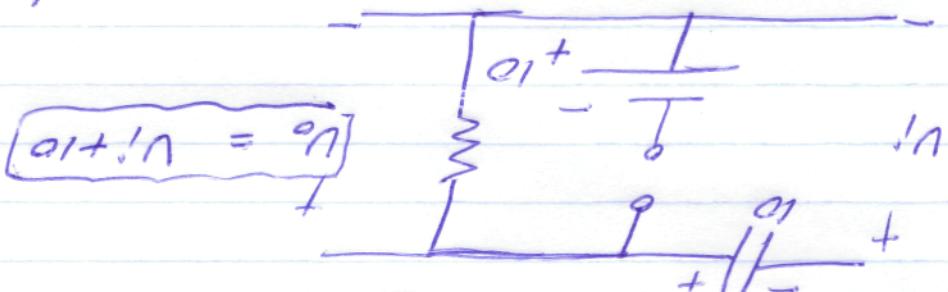
∴ proposed design has been verified to do



and C shunt charged to -10

∴ offshoots diode will be permanently off

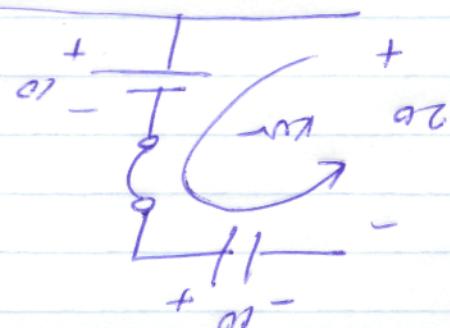
$$U_o = 10 U_i \text{ as shown}$$
$$\Leftrightarrow 0 = 10 - U_i(+) \Rightarrow$$



obtained from the following circuit  
C is charged to  $-10 + U_i$  which is

1. when  $U_i < 0 \Rightarrow U_i = -20V$  diode is on

∴ By analysis of the proposed clamp

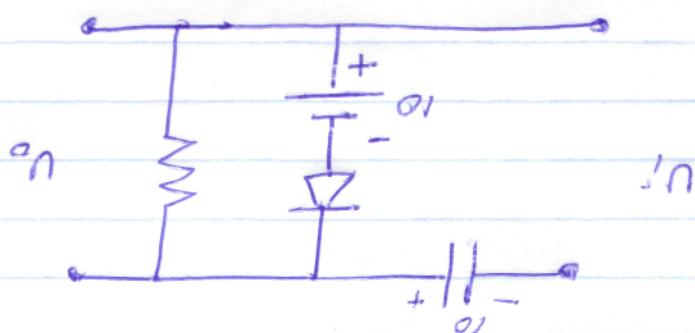

of the following form

can be implemented using a clapper


$U_o$  and this is affection that

the  $U_i$  is shifted by  $+10V$  to get

By closely examining both input and output waveforms it is noted that

Q40.

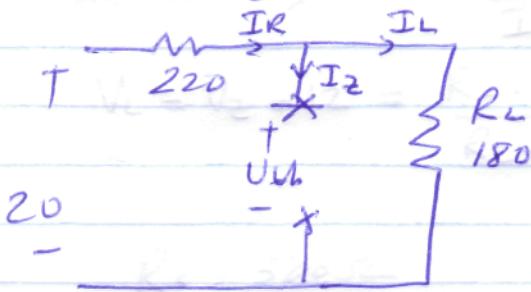Q42. a) Remove zener diode and find  $V_{th}$



$$V_{th} = \frac{180}{180+220} \cdot 20 = 9V$$

$V_{th} < V_Z \Rightarrow$  diode is not conducting

$$I_Z = 0$$

$$I_L = I_R = \frac{20}{180+220} = 50mA$$

b) with  $R_L = 470\Omega$

$$V_{th} = \frac{470}{470+220} \cdot 20 = 13.62 > V_Z$$

Zener is ON &  $V_L = 10V$

$$I_L = \frac{V_L}{R_L} = \frac{10}{470} = 21.28mA$$

$$I_R = \frac{20-10}{220} = 45.45mA$$

$$I_Z = I_R - I_L = 24.17mA$$

c)  $P_{Z(\max)} = 400mW = V_Z \cdot I_Z = 10V \cdot I_Z \Rightarrow$   
 $I_Z = 40mA$

$$I_{L(\min)} = I_R - I_{Z(\max)} = 45.45mA - 40mA \\ = 5.45mA$$

$$R_L = \frac{V_L}{I_{L(\min)}} = \frac{10}{5.45mA} = 1.834k\Omega$$

d) Value of  $R_L$  is chosen such that to ensure  $V_{KA} = V_L \geq V_Z = 10V$

$$V_L = \frac{R_L}{R_L + R_S} \cdot 20 = 10 \Rightarrow$$

$$10R_L + 2200 = 20R_L$$

$$10R_L = 2200 \Rightarrow \boxed{R_L = 220\Omega}$$

$$Q43. \text{ a) } V_2 = 12 \text{ V}, R_L = \frac{V_L}{I_L} = \frac{12}{200 \text{ mA}} = 60 \Omega$$

$$V_L = V_2 = 12 \text{ V}, R_L = \frac{R_s \cdot V_i}{R_L + R_s} = \frac{60 \cdot 16}{60 + R_s} \Rightarrow \text{yields}$$

$$R_s = 500 \Omega$$

$$\text{b) } P_{z(\max)} = V_2 \cdot I_{z(\max)} = 12 \text{ V} \cdot 200 \text{ mA} = \underline{\underline{2.4 \text{ W}}}$$

$$Q44. \text{ since } I_L = \frac{V_L}{R_L} = \frac{V_2}{R_L} \text{ is fixed in magnitude} \Rightarrow$$

$$I_{R(\max)} = I_{z(\max)} + I_L$$

$$I_{z(\max)} = \frac{P_{z(\max)}}{V_2} = \frac{400 \text{ mW}}{8} = 50 \text{ mA}$$

$$I_L = \frac{V_2}{R_L} = \frac{8}{220} = 36.36 \text{ mA}$$

$$I_{R1} = 50 \text{ mA} + 36.36 \text{ mA} = 86.36 \text{ mA}_{\max}$$

$$I_R = \frac{V_i - V_2}{R_S} \Rightarrow V_i = I_R \cdot R_S + V_2 \\ = 2.86 + 8 = 15.86 \text{ V}$$

Also  $V_i$  value must ensure that  
 $V_L \geq V_2$  to have Zener in regulation mode

$$V_L = \frac{R_L}{R_L + R_S} \cdot V_i \geq 10 \Rightarrow$$

$$V_i \geq \frac{10(R_L + R_S)}{R_L} \geq \frac{10(220 + 91)}{220} \geq 14.136 \text{ V}$$

~~(14.136 V)  $\leq V_i \leq 15.86 \text{ V}$~~