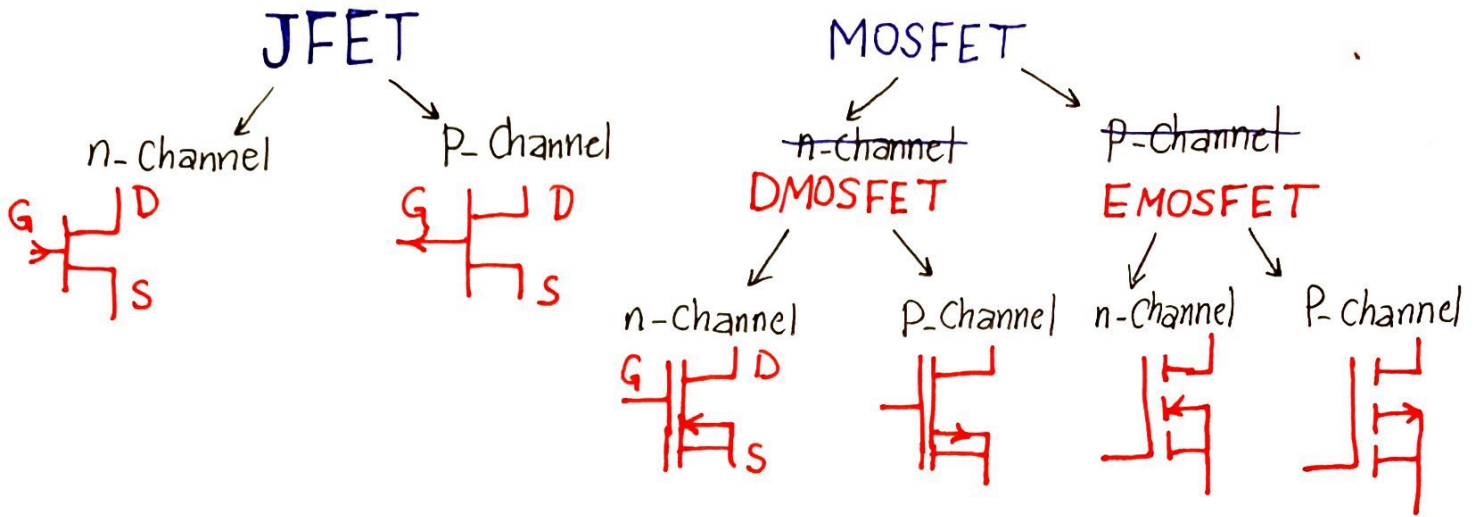


Electronics : ENEE 236 → L14 - JFET Biasing




$V_p =$ $\begin{cases} \text{negative value for n-channel} \\ \text{Positive value for p-channel} \end{cases}$

$$\left[I_{Ds}(t) = I_{DSS} \left(1 - \frac{V_{Gs}(t)}{V_p} \right)^2 \right]$$

In pinch off Region

$V_p < V_{Gs} \leq 0$ "n-channel"

$|V_{Ds}| > |V_p| - |V_{Gs}|$ "p-channel" $V_p < V_{Gs} \leq 0$

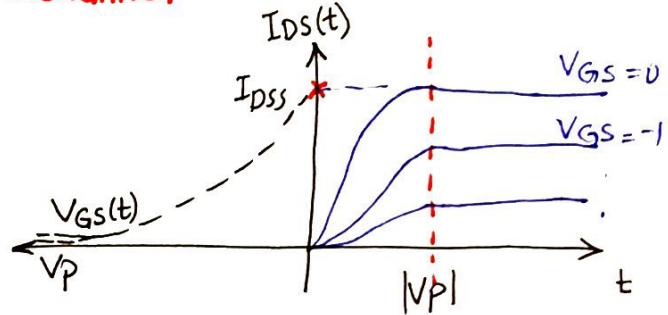

Common JFET Biasing Circuit

- Fixed-Bias
- Self-Bias
- Voltage-Divider Bias

Important

For All FETs:
 $I_G \cong 0A, I_D = I_S = I_{Ds}$
 For All JFETs:
 $I_{Ds}(t) = I_{DSS} \left(1 - \frac{V_{Gs}}{V_p} \right)^2$
 نفسها لـ DMOS.

1 Fixed-Bias : I_{DSS}, V_p

$V_{Gs}?$ $I_D?$ $V_{Ds}?$


$V_{GG} + V_{Gs} = 0 \Rightarrow V_{Gs} = -V_{GG}$

$V_{DD} = I_D R_D + V_{Ds}$


$V_{Ds} = V_D$

$V_{Gs} = V_G$

$0 = V_S$ \leftarrow V_S

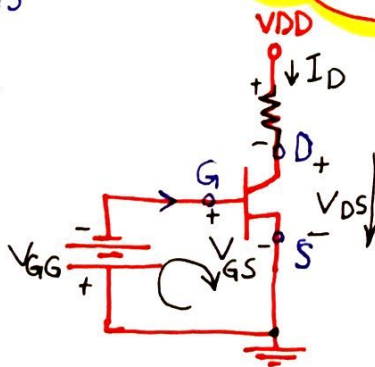

.1.

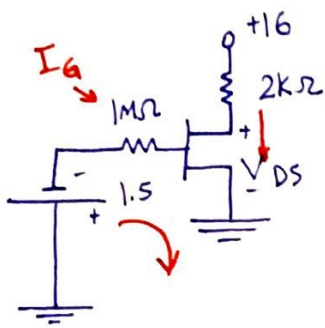

Example

$$I_{DSS} = 10 \text{ mA}$$

$$V_P = -4$$

$$V_{GS} = -1.5 \text{ volt}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 10 \text{ mA} \left(1 - \frac{-1.5}{-4}\right)^2$$

$$V_{DS} = 16 - I_D \cdot 2K = 8.2 \text{ V}$$

Check


$$|V_{DS}| > |V_P| - |V_{GS}|?$$

$$8.2 > |4| - 1.5$$

Graphical method

$$V_{DS} = I_{DSS} - \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$V_{GS} = 1.5 \text{ Fixed}$$

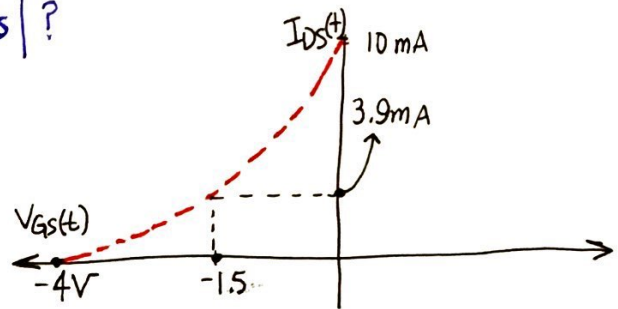

2] Self-Bias Configuration

$$0 + V_{GS} + I_D R_S = 0$$

$$V_{GS} = V_G - V_S = 0 - V_S = -V_S$$


$$V_S = I_D R_S$$

$$V_{GS} = -I_D R_S$$

$$V_D = V_{DD} - I_D R_D$$

$$V_{DS} = V_D - V_S$$
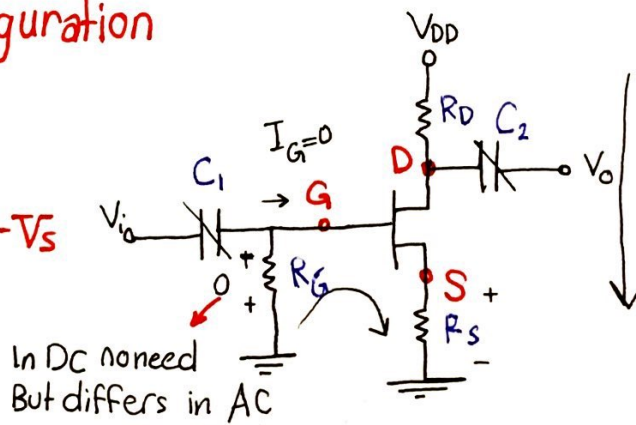
$$= V_{DD} - I_D R_D - I_D R_S = V_{DD} - I_D (R_D + R_S)$$



$$V_{GS} = V_G - V_S$$


$$V_{GS} = 0 - I_S R_S$$

$$V_{GS} = -I_S R_S$$

$$V_{GS} = -600 I_S \rightarrow I_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$
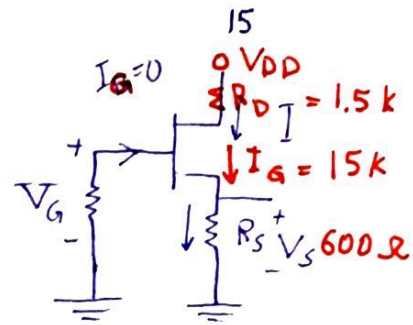
$$= 10 \text{ mA} \left(1 - \frac{-600 I_D}{-4} \right)^2 \Rightarrow \text{معادلتين تربيعية} \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$



Reverse bias

$$I_{D1,2} \rightarrow \begin{cases} 14.77 \text{ mA} > I_{DSS} \\ 3.0 \text{ mA} < I_{DSS} \checkmark \end{cases}$$

$$15 - 1.5k I_D - V_{DS} - 0.6k I_D = 0$$

$$V_{DS} = 10.2 \text{ V}$$

I_{DSS} : IS the Maximum value and its 10 mA which mean that $14.77 > I_{DSS}$ the other solution is 3 mA and its $< I_{DSS}$ then its accepted!

$$V_{GS} = -600 \cdot 3 \text{ mA} \quad (\text{يتبع على } I_D) \\ = -1800 \text{ mV} = -1.8 \text{ V}$$

$$|V_{DS}| > |V_P| |V_{GS}|$$

$$10.2 > |4| \cdot |-1.8| \checkmark \text{ "checked"}$$

2] Graphical method: \Rightarrow Graph بتستخدم المعادلة $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$

$$V_{GS} = (-0.6 \text{ K}) I_{DS}$$

$$\text{لو حطينا } V_{GS} = 0 \Leftrightarrow 0 = I_{DS} \text{ يعني}$$


بتقطع ال origin بتقطع *

بتطاي قيمة ل I_{DS} مثلا 5

ولنفرض طلع $V_{GS} = -3$

$$\text{When } V_{GS} = 0 \rightarrow I_{DS} = 0$$
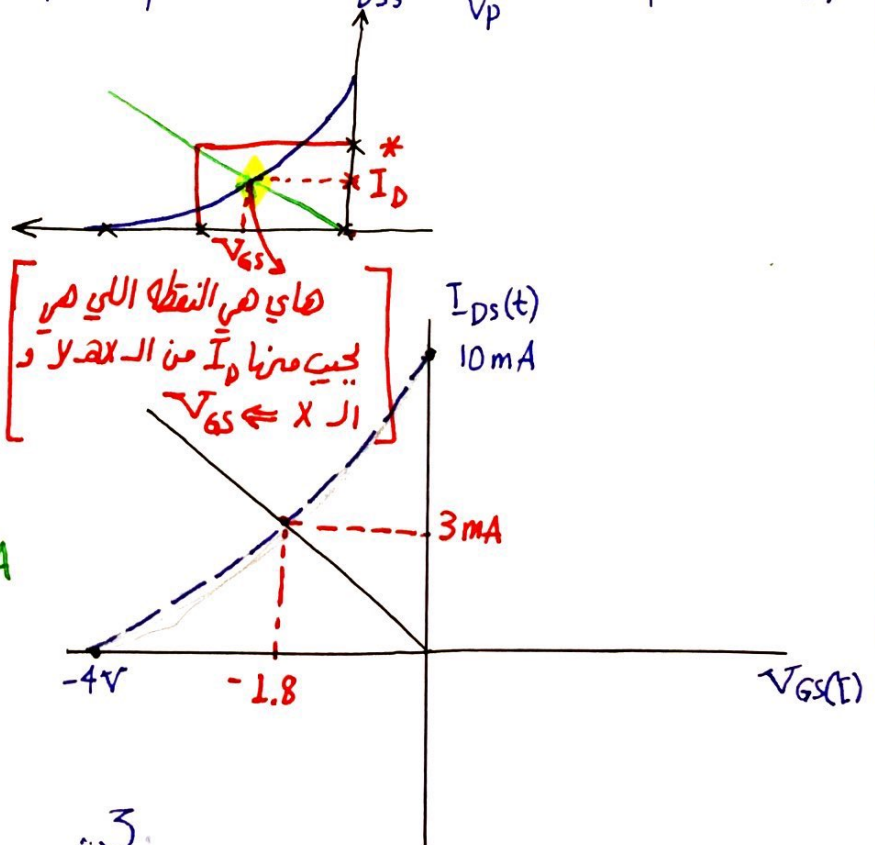
$$\text{When } V_{GS} = -3 \rightarrow I_{DS} = 5 \text{ mA}$$



3.

3 Voltage-Divider Bias

$I_G = 0 \text{ mA}$

I_D responds to changes in V_{GS}



V_G is equal to the voltage across divider resistor R_2

$$V_G = \frac{R_2}{R_1 + R_2} \cdot V_{DD}$$

$$V_S = I_D R_S$$


Using kirchhoff's law: $V_{GS} = V_G - I_D R_S$
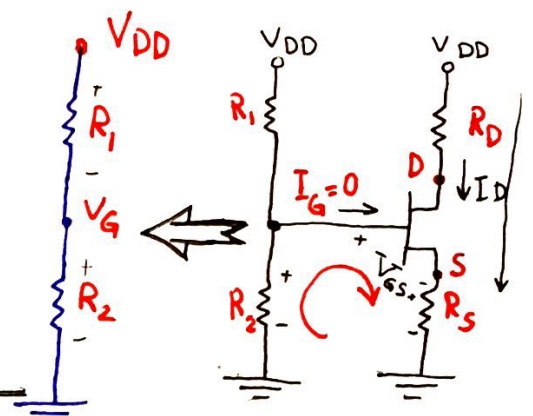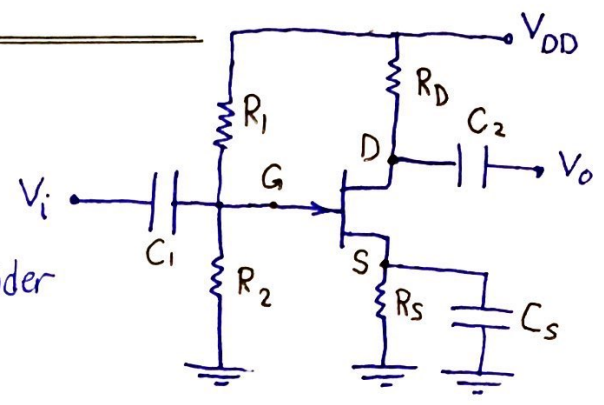
$$V_{GS} = \frac{R_2}{R_1 + R_2} \cdot V_{DD} - I_D R_S$$




Example

$I_D, V_{GS} ?$

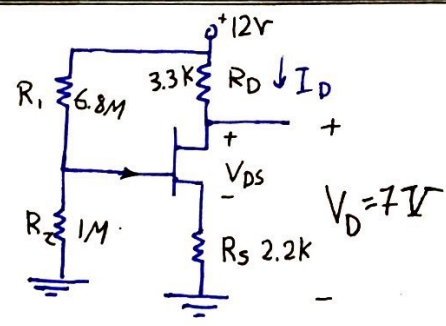
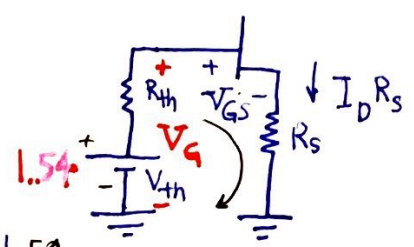
$$I_D = \frac{12 - 7}{3.3k + 3.3k} = \frac{5}{6.6k} = 1.52 \text{ mA}$$



$$V_{th} = \frac{R_2}{R_1 + R_2} \cdot 12$$

$$V_G = \frac{1M}{7.8M} \cdot 12 = 1.54$$

KVL $\Rightarrow V_G - I_D R_S = V_{GS}$

$$1.54 - (1.52 \text{ mA})(2.2k) = V_{GS} =$$

$$V_{GS} = 1.54 - 3.344 = -1.8 \text{ V}$$

$$R_{th} = R_1 \parallel R_2$$

$$V_{th} = \frac{R_2}{R_1 + R_2} \cdot V_G$$

طريقة الكون

$$V_{th} = V_{GS} + I_D R_S$$

$$V_{GS} = V_{th} - I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = I_{DSS} \left(1 - \frac{V_{th} - I_D R_S}{V_P} \right)^2$$

$$\Rightarrow \left[\frac{V_{th} - V_{GS}}{R_S} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \right]$$

تكملة السؤال "الجواب"

لحساب V_D منه معروفة عندي بغير العمل معادلة ترتيبية

$$V_S = I_D R_S = (1.52 \text{ mA}) \cdot (2.2k) = 3.34 \text{ V}$$

$$V_G = \frac{1M}{1M + 6M} \cdot 15 = 1.54 \text{ V}$$

$$V_{GS} = \frac{R_2}{R_1 + R_2} \cdot V_{DD} - I_D R_S$$


Example V_D unknown

$$V_{GS} = \frac{R_2}{R_1 + R_2} \cdot V_{DD} - I_D R_S$$

$$V_{GS} = 1.54 - I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

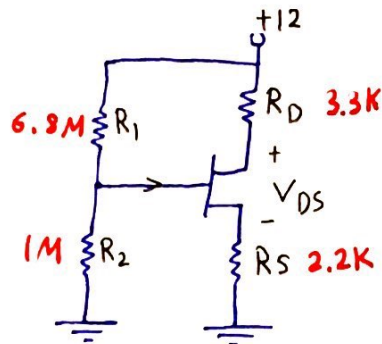
$$= I_{DSS} \left(1 - \frac{1.54 - I_D R_S}{V_P} \right)^2$$



When $I_D = 0 \Rightarrow V_{GS} = 1.54$

When $V_{GS} = 0 \Rightarrow I_D = \frac{1.54}{R_S}$

Voltage-Divider Q point

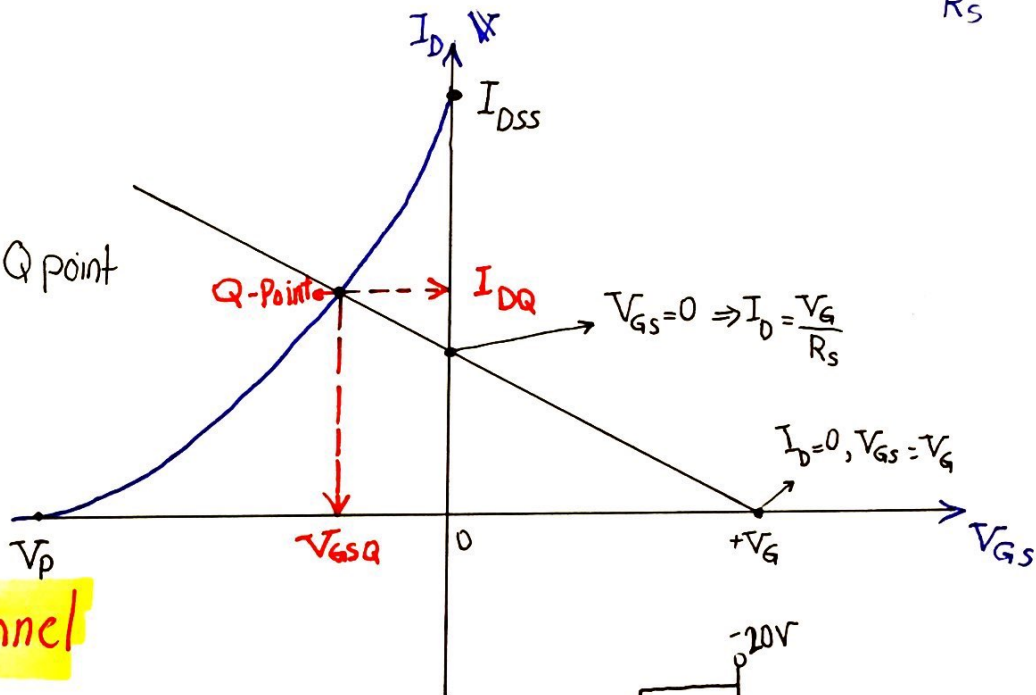

Example p-channel

$$V_P = -5V < 0$$

$$I_{DSS} = 18mA$$


$$V_{GS} = V_G - V_S = \frac{R_2}{R_1 + R_2} \cdot 20 + I_D R_S$$

$$V_{GS} = -4 + I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$= I_{DSS} \left(1 - \frac{-4 + I_D R_S}{5} \right)^2$$
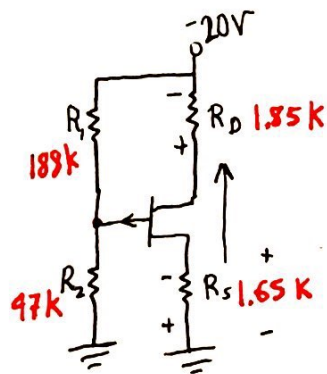
$$= 18mA \left(1 - \frac{-4 + I_D \times 1.65}{5} \right)^2$$



$$I_{D1} = 4.7mA \checkmark < I_{DSS}$$

$$I_{D2} = 7.4mA \checkmark < I_{DSS}$$

ما يقرر الا لما اتوف V_{GS}
 في يكون كل وحدة منهم بتعطين
 كم؟

$$V_{GS} = -4 + (4.7m)(1.65k) = 3.75V$$

$$V_{GS} = -4 + (7.4m)(1.65k) = 8.21V$$

$V_P = 5$
 لازم يكون ايه
 $I_{D1} \checkmark$ ف

5.