

Electronics : ENEE 236 \Rightarrow L15, Part 1 & Part 2 **MOSFET**

Midpoint Bias : For maximum Symmetrical Swing

- Place Qpoint in the middle point of the transfer characteristic to allow for Maximum swing between I_{DSS} & Zero

1] Let $I_D = 0.5 I_{DSS}$

$$0.5 I_{DSS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$0.5 = \left(1 - \frac{V_{GS}}{V_P} \right)^2$$


$$\sqrt{0.5} = 1 - \frac{V_{GS}}{V_P} \Rightarrow \frac{V_{GS}}{V_P} = 1 - \sqrt{0.5}$$

$$V_{GS} = V_P (1 - \sqrt{0.5})$$

$$V_{GS} = V_P (0.2928)$$

$$\therefore V_{GS} \approx \frac{V_P}{3.41}$$

2] Let $V_D = 0.5 V_{DD}$

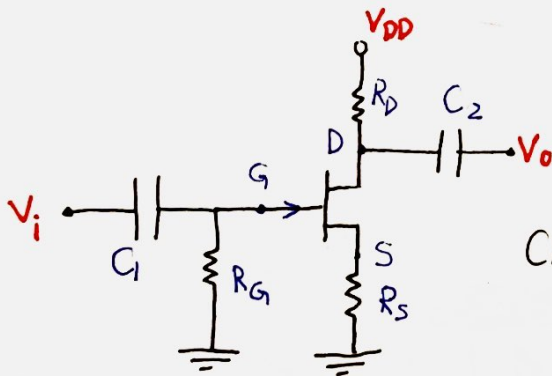

$$V_P = V_{GS}(\text{off}) = -3V$$

$$I_{DSS} = 12 \text{ mA}$$

Choose R_D & R_S for mid point Bias

$$V_D = \frac{1}{2} V_{DD}, \quad 6 \text{ mA} = I_D \text{ بيا} \\ = 6V$$

$$I_D = 0.5 I_{DSS} = 6 \text{ mA}$$

$$V_D = 0.5 V_{DD} = 6V$$

$$\leftarrow V_{GS} = \frac{V_{GS}(\text{off})}{3.4} = \frac{-3}{3.4} = -0.882V$$

$$R_S = \frac{V_S}{I_D} = \frac{0.882}{6 \text{ mA}} = 147 \Omega$$

$$V_{DD} - I_D R_D - V_D = 0 \Rightarrow R_D = \frac{V_{DD} - V_D}{I_D} = 1k \Omega$$

.1.

$$= V_G - V_S$$

$$V_{GS} = 0 - V_S$$



$$V_S = -(-0.882)$$

Electronics : ENEE 236 → L15 : Part 2

Metal Oxide Semiconductor

1 DMO SFET : Depletion type Mosfet

2 EMOSFET : Enhancement type Mosfet

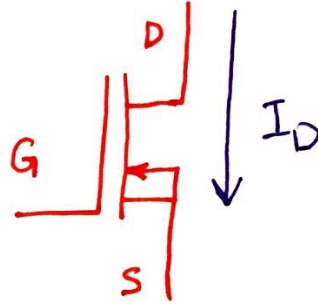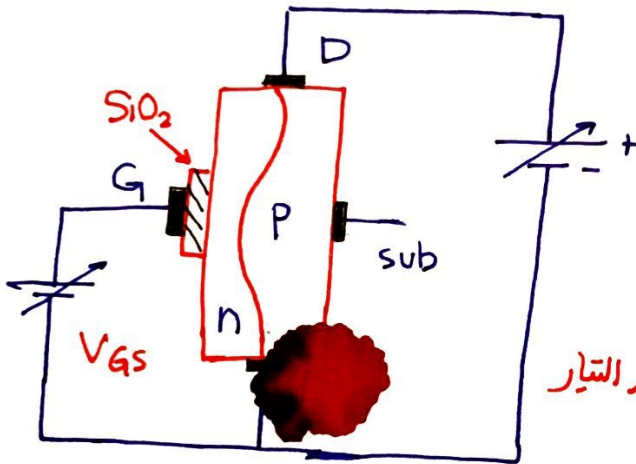

كلما تزيد الالكترونات في من جهة G " RB " بجز التيار لما يوصل لـ V_p


الاختلاف الرئيسي بينه وبين JFET انوما في P_n Junction

Instead, the gate of the MosFET is isolated from the channel by a Silicon dioxide (SiO_2) layer.

Due to this the input resistance of MOSFET is greater than JFET

Input Z "Impedence" very large

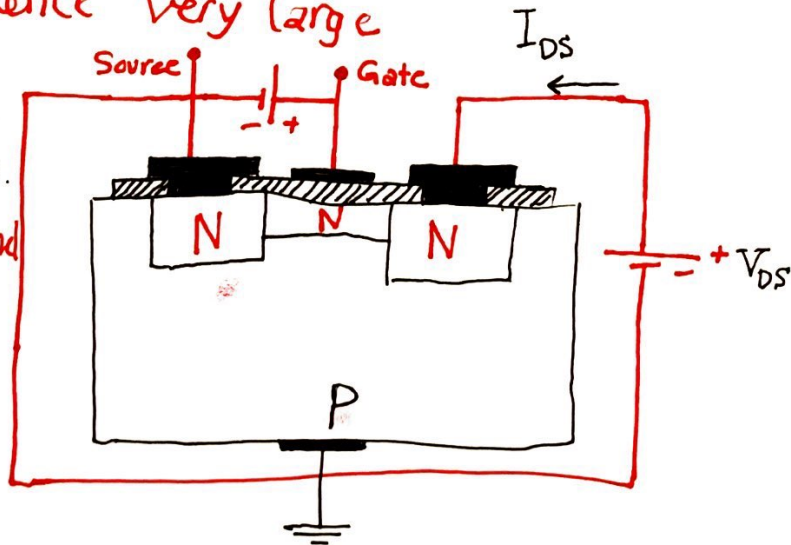Depletion type Mos.
Construction of n-Channel
DMOFET



اذا حصلنا Voltage من جهة Gate ف يجذب P بالتالي يزيد ال Conduction يعني يزيد التيار I_{DSS} electrons

Metal Oxide Semiconductor Field Effect Transistor MOSFET

Depletion Mode

$$0 \geq V_{GS} > V_p$$

$$I_D < I_{DSS}$$

$$V_{GS} > V_p \text{ (negative for n-channel)}$$

can be +ve or -ve

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

* For the n-channel

$$V_{GS} > V_p \text{ "negative"}$$

$$V_{DS} > V_{GS} - V_p$$

Example

$$I_{Ds} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 \dots \square$$

$$V_{GS} = V_G - V_S = V_G$$

$$V_G = \frac{11M}{111M} \times 12 = 1.19V \dots \square$$

$$I_{Ds} = I_{DSS} \left(1 - \frac{V_G}{V_p}\right)^2$$

$$I_{Ds} = 4mA \left(1 - \frac{1.19}{-5}\right)^2 = 6.13mA > I_{DSS}$$

Will operate in Enhancement Mode.

$$V_{DS} = V_{DD} - 0.5K I_{Ds} = 8.93V$$


$$V_{DS} > V_{GS} - V_p = 6.19$$

$$8.93 > 1.19 - 5 = 6.19 \checkmark$$

Enhancement Mode

$$V_{GS} > 0$$

$$I_D > I_{DSS}$$

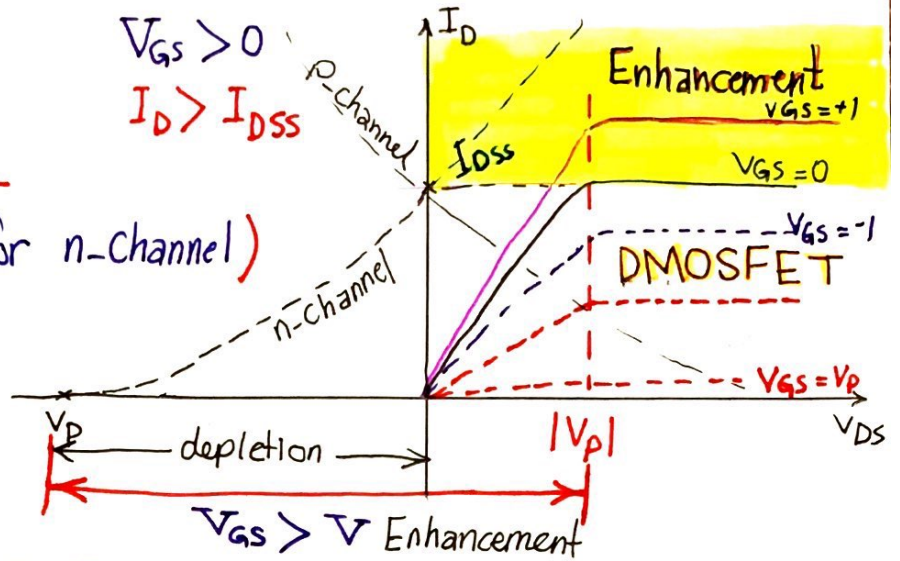


$$I_D < I_{DSS} \iff \text{اذا لاله} \quad // \quad I_D > I_{DSS} \iff 0 < V_{GS} \text{ اذ لاله}$$

* For the p-channel


$$V_{GS} < V_p \text{ "positive"}$$

$$V_{DS} < V_{GS} - V_p$$

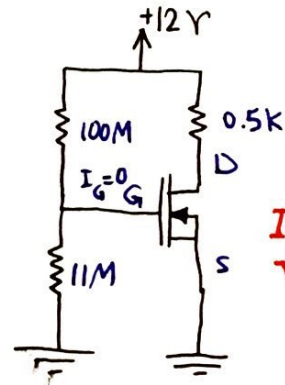

$$I_{DSS} = 4mA$$



$$V_p = -5V$$

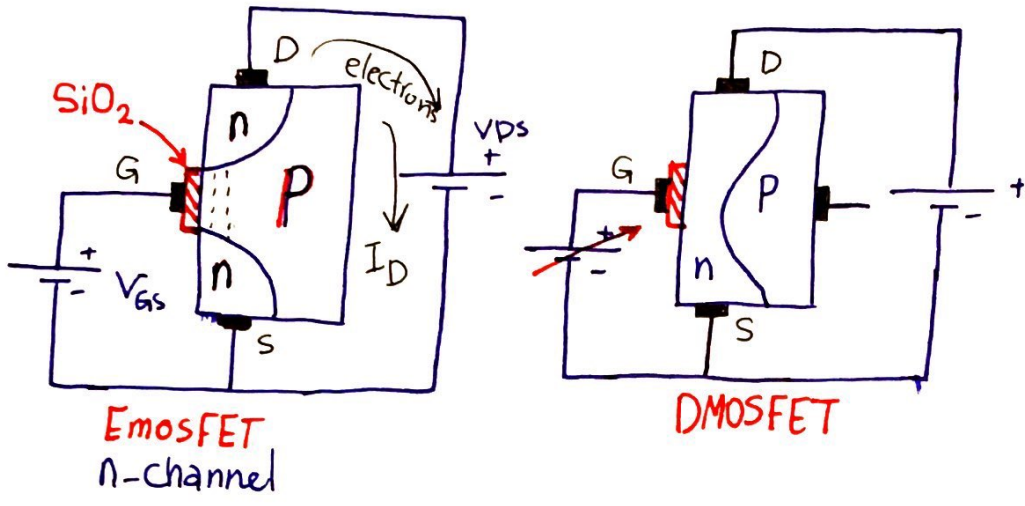


E-MOSFET
n-channel

D-MOSFET

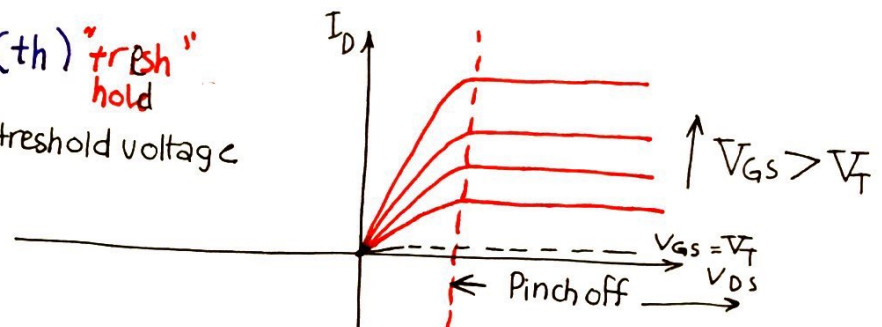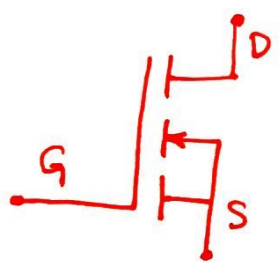$V_{GS} \geq V_{GS(th)}$ "trsh" hold
 V_T threshold voltage



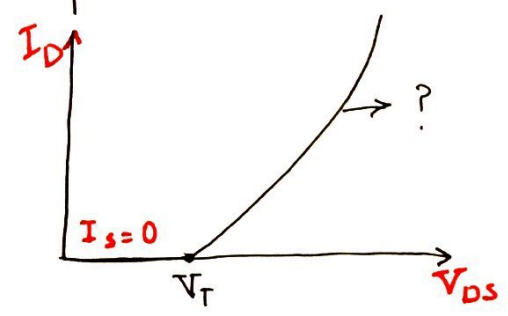$I_D = k_n (V_{GS} - V_T)^2$
 datasheet or calculated



Test point (a) $V_{GS} = 5V$
 $I_D = 4mA$
 $V_T = 3V$ $\Rightarrow k_n = \frac{I_D}{(V_{GS} - V_T)^2} = \frac{4mA}{(5-3)^2} = 1mA/V^2$

In the Pinch off Region - E-MOSFET

$i_{DS}(t) = k_n (V_{GS}(t) - V_T)^2$

$|V_{DS}| > |V_{GS} - V_T|$

$V_{GS} > V_T$ → موجبة n-Channel
 $V_{GS} < V_T$ → سالبة p-Channel