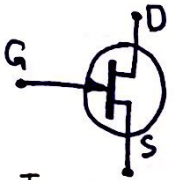
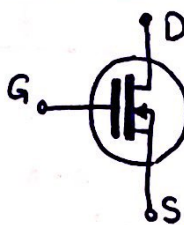
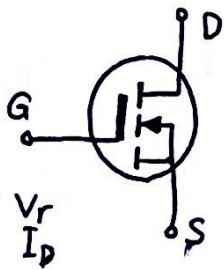
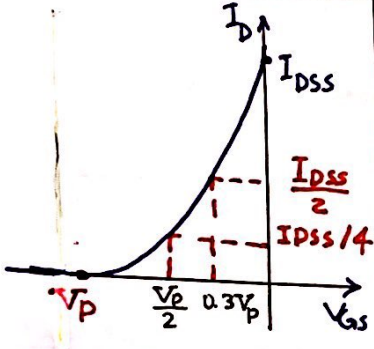
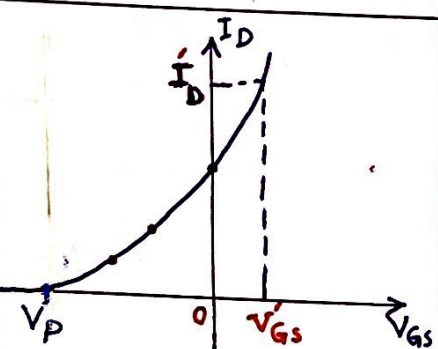
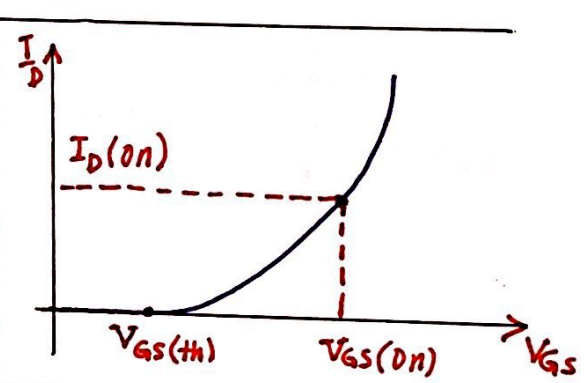


# Electronics : ENEE 236 ⇒ L16 FET ac Analysis

## Summary table

JFET	D-MOSFET	E-MOSFET
 $I_{DSS}$ $V_p$ $I_G = 0, I_D = I_S$ $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$	 $I_{DSS}$ $V_p$ $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$	 $I_D = k (V_{GS} - V_{GS(th)})^2$ $k = \frac{I_D}{(V_{GS} - V_{GS(th)})^2}$ $V_r$ $I_p$ $V_{GS}$
 <p>Graph of <math>I_D</math> vs <math>V_{GS}</math> for JFET. The curve starts at <math>V_p</math> and reaches <math>I_{DSS}</math> at <math>V_{GS} = 0</math>. Key points marked: <math>V_p</math>, <math>\frac{V_p}{2}</math>, <math>0.3V_p</math>, <math>I_{DSS}</math>, <math>\frac{I_{DSS}}{2}</math>, <math>I_{DSS}/4</math>.</p>	 <p>Graph of <math>I_D</math> vs <math>V_{GS}</math> for D-MOSFET. The curve starts at <math>V_p</math> and reaches <math>I_{DSS}</math> at <math>V_{GS} = 0</math>. Key points marked: <math>V_p</math>, <math>0</math>, <math>V_{GS}</math>.</p>	 <p>Graph of <math>I_D</math> vs <math>V_{GS}</math> for E-MOSFET. The curve starts at <math>V_{GS(th)}</math> and reaches <math>I_D(on)</math> at <math>V_{GS(on)}</math>. Key points marked: <math>V_{GS(th)}</math>, <math>V_{GS(on)}</math>.</p>

### Example

$$K_n = 0.25 \times 10^3 \text{ A/V}^2$$

$$V_T = 2V$$

n-channel موجبة معناته  $V_T$   $\ll$   
 P-channel موجبة معناته  $V_T$   $\ll$

$$I_{DS} = K_n (V_{GS} - V_T)^2 \dots \boxed{1}$$

$$V_{GS} = V_G - V_S$$

$$V_G = \frac{22M}{22 + 47M} \cdot 18 = 5.74V$$

$$V_S = (0.5K) I_{DS}$$


$$V_{GS} = 5.74 - 0.5K I_{DS} \dots \boxed{2}$$

$$V_{GS} = 4.78V \checkmark \quad \text{لانم اكبر من } V_T$$

$$= -8.78X$$


$$I_{DS} = 1.92mA$$

$$V_{GS} = 12.82 > |V_{GS} - V_T|$$

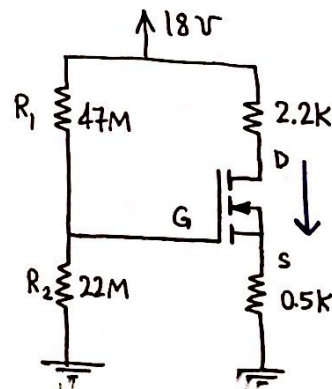



# CMOS Inverter "Complementary MOS"

NOT Gate

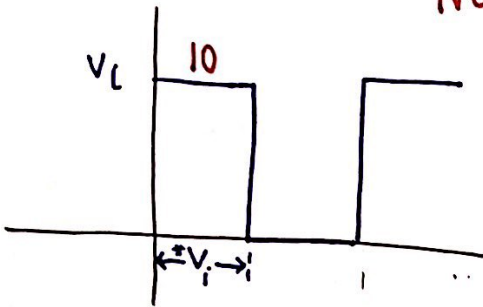


\* $V_i = 10 = V_{GS1} > 2$  → عبر يعني  
 بحت (SC)  
 $V_{GS2} = 0 > -2$  → ~~عبر~~ يعني  
 بحت OC

إذا الاینون 10 ← الاینون 0

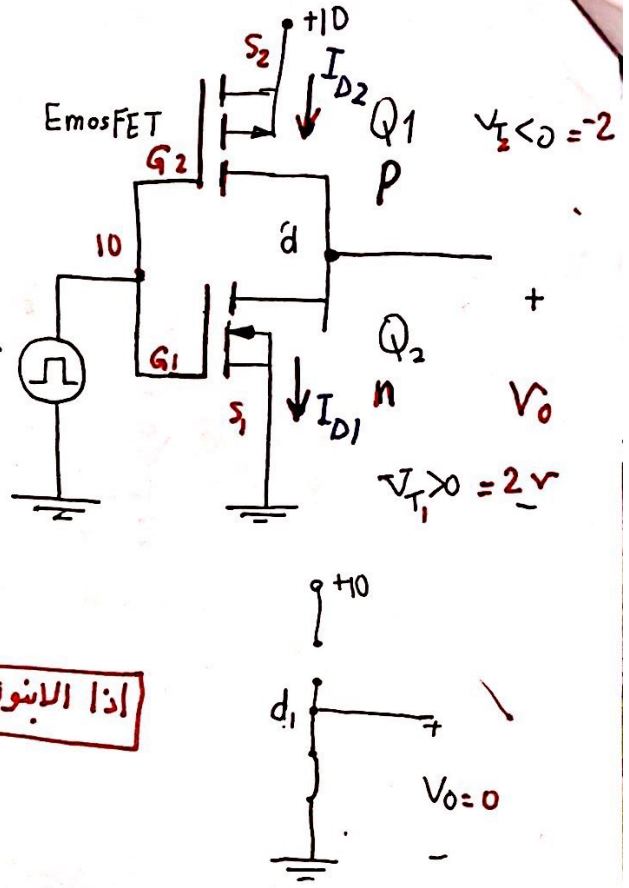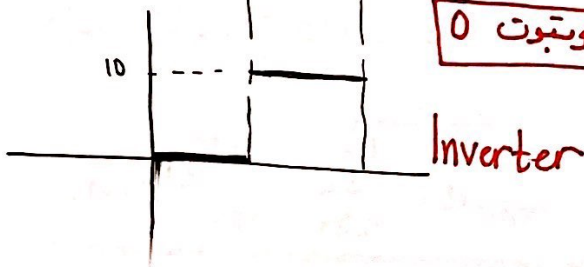

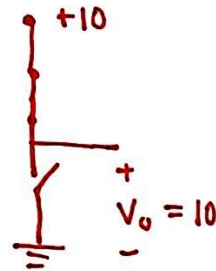2)  $V_i = 0V \Rightarrow V_{GS1} < 2$   
 $Q_1$  - off  
 $\rightarrow V_{GS2} = 0 - 10 = -10 < -2$




هيك خلاصنا لـ 10


# L11@NOTES: FET Amplifiers as small signal analysis

## L16 ASVIDLOS

For all FET Type

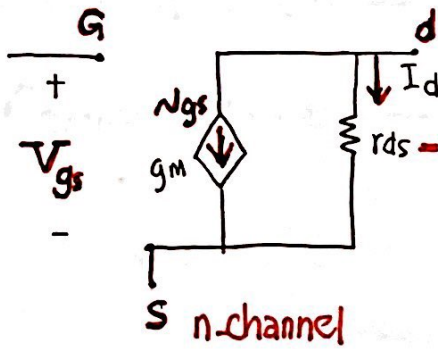

$g_m$  - Transconductance

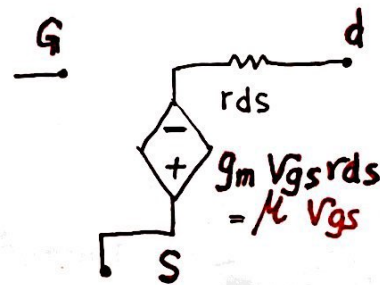

$$\mu = g_m r_{ds}$$

Amplification Factor

$$g_m = \frac{\partial I_D}{\partial V_{GS}} \quad \begin{matrix} \text{ohm}^{-1} \\ \text{mho} \end{matrix} \quad \begin{matrix} \text{[Always +ve]} \\ \text{[Siemens]} \end{matrix}$$

For JFET & DMOSFET

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\frac{\partial I_D}{\partial V_{GS}} = \frac{2 I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right) = g_{m0} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$g_{m0} = g_m |_{V_{GS}=0}$  ← dc value

$$= \frac{2 I_{DSS}}{|V_P|} \sqrt{\frac{I_D}{I_{DSS}}} = \frac{2}{|V_P|} \sqrt{I_D \cdot I_{DSS}}$$

For EMOSFET

$$I_D = k_n (V_{GS} - V_T)^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = 2 k_n (V_{GS} - V_T)$$

$$= 2 k_n \sqrt{\frac{I_D}{k_n}} = 2 \sqrt{I_D k_n}$$

$$k_n = \frac{I_D}{(V_{GS} - V_T)^2} \quad \text{@ the Q-point "dc value"}$$

..3.

# FET Amplifier


Common Source  $\rightarrow$  eq. to CE "Input Gate, Output Drain"

Common Drain  $\rightarrow$  eq. to CC

Common Gate  $\rightarrow$  eq. to CB

all have the same eq. Circuit "n-channel"

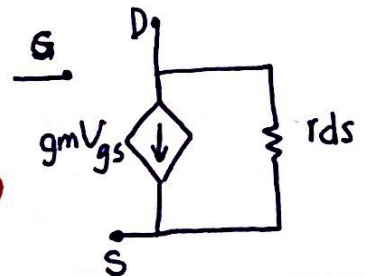For p-channel  $\rightarrow$  current from S to D



## 1] Common Source Amplifier with self Bias "Inverting"

Yup!


Find  $A_v, Z_i, Z_o$

ac SS quantities  $\rightarrow$  Construct ac eq. Circuit

$C_1, C_2$   
"short"

$V_{DD}=0$   
(GND)


JFET  
ac SS Model

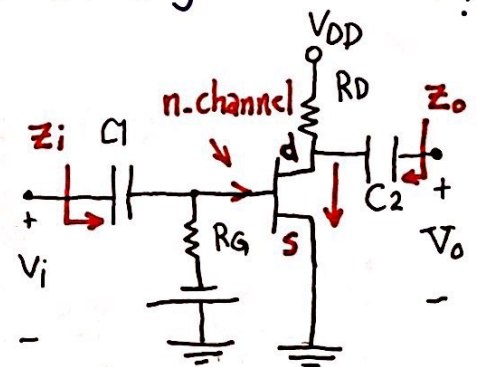

$Z_i = R_G$

$Z_o \downarrow = R_D \parallel r_{ds}$   
*كبيره كثير*  
*لهيك مرات تكون*  
*ساوي ال RD*

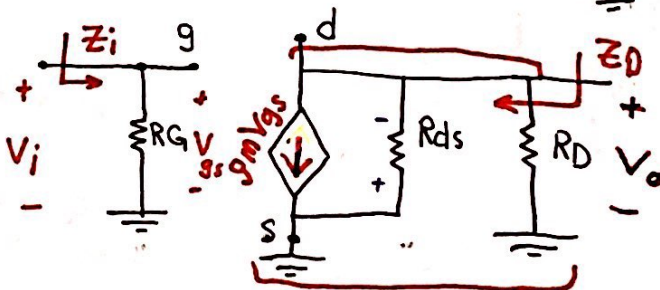For this  $r_{ds} \gg R_D$   
 $\therefore Z_o = R_D$



$r_{ds}, R_D \rightarrow$  Shared Ground & shared Drain



$A_v = \frac{V_o}{V_i}$

$V_o = r_{ds} = -g_m V_{gs} (r_{ds} \parallel R_D)$   
 $V_i = V_{gs}$

$A_v = \frac{-g_m V_{gs} (r_{ds} \parallel R_D)}{V_{gs}} = -g_m (r_{ds} \parallel R_D)$   
 $= -g_m (R_D) \cdot A.$

Inverting Amplifier

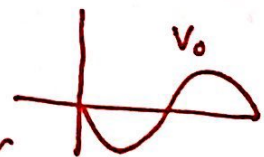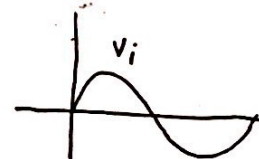$V_o$  is shifted  $180^\circ$  relative to  $V_i$



# Common Source (self Bias)

( $r_{ds} \approx \infty$ )

$$V_{gs} \neq v_i$$

$$V_{gs} = V_g - V_s$$

$$V_{gs} = v_i - g_m V_{gs} R_s$$

$$A_v = \frac{-g_m R_D}{1 + g_m R_s}$$

المقام  $\leftarrow 1 + g_m R_s$

$A_v$  is  $\downarrow$  due to  $R_s$

$$A_v = \frac{V_o}{v_i}$$

$$V_o = -g_m V_{gs} R_D$$

$$\Rightarrow V_{gs} = \frac{v_i}{1 + g_m R_s}$$

$$V_{gs} = V_g - V_s$$

$$= v_i - \dots$$

