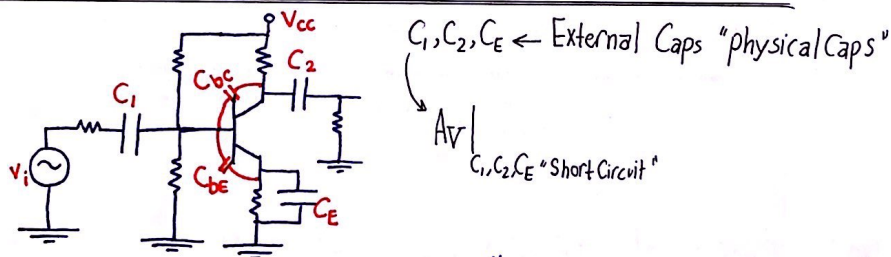



Electronics 236, L22, Part 1 & 2 Amp. Freq. Response

Amplifier Frequency Response : Magnitude Freq Response only!

- We will consider the Impedance of Capacitor ($\frac{1}{j\omega C}$) when Finding AV of BJT & FET amplifiers.
- The Bandwidth of Amplifiers must cover the entire range of frequency of Interest.
- Depending of nature of signals to be amplified, different requirements (BW) is imposed on Amplifiers Band width
- Amplifier frequency response is defined by external & Internal amplifier Caps & Impedence.




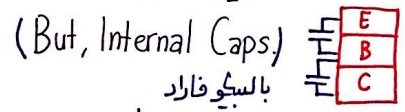$C_1, C_2, C_E \leftarrow$ External Caps "physical Caps"
 $AV \mid_{C_1, C_2, C_E \text{ "Short Circuit"}}$




PCB, mother boards
 Between traces "conductors"

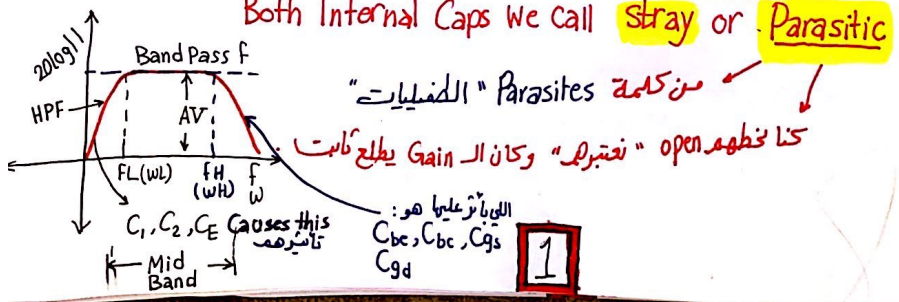Both Internal Caps we call stray or Parasitic



Series Capacitance & w_L

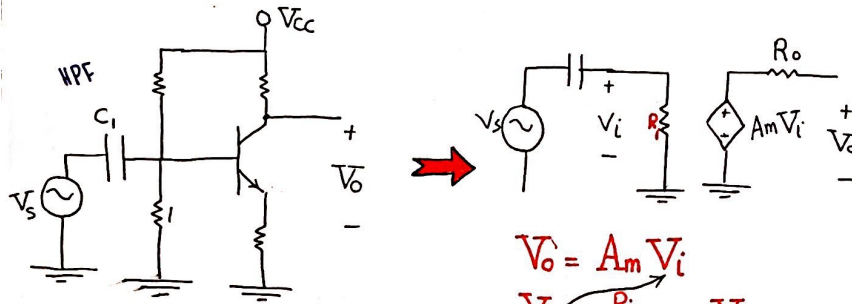

$$V_o = A_m V_i$$

$$V_i = \frac{R_i}{R_i + \frac{1}{j\omega C}} \cdot V_s$$

$$\frac{V_o}{V_s} = \frac{A_m R_i}{R_i + \frac{1}{j\omega C}}, \quad A_m \equiv A_v(\text{mid})$$

$$|A_v(j\omega)| = \frac{A_m R_i}{R_i^2 + (\frac{1}{\omega C})^2}, \quad \text{تعويض محل } 1 \leftarrow \frac{1}{\omega C} \text{ صون ضرب}$$

$\omega_{C1} = \frac{1}{R_i C_1}$
cut-off due to C_1
"مقطع تردد"

$$A_v(j\omega) = \frac{A_m}{\sqrt{1 + (\omega C_1)^2}}$$

HPF

- Let $A_m = 1, \omega = \omega_{C1} \rightarrow | | = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} \rightarrow 20 \log \frac{1}{\sqrt{2}} = -3 \text{ dB}$
- Let $\omega = 0.1 \omega_{C1} \rightarrow | | = \frac{1}{\sqrt{1+100}} \approx 0.1 \rightarrow 20 \log 0.1 \approx -20 \text{ dB}$

1 If only $C_1 \rightarrow \omega_{C1} = \omega_L$

2 If $C_1 \& C_2 \rightarrow \omega_L$?

$$A(j\omega) = A_m \left(\frac{1}{1 + \frac{\omega C_1}{j\omega}} \right) \left(\frac{1}{1 + \frac{\omega C_2}{j\omega}} \right)$$

$$|A(j\omega)| = \dots$$

$$|A(j\omega_L)| = \frac{A_m}{\sqrt{2}} = \dots$$

→ Solving for ω_L :

$$(\omega_L)^2 = \frac{\omega_{C1}^2 + \omega_{C2}^2}{2} + \frac{\omega_{C1}^4 + 6\omega_{C1}^2 \omega_{C2}^2 + \omega_{C2}^4}{2}$$

حل من تمثيل الأوتوسى وعمل ال Magnitude للمقار
ومساواة ال (evaluation for ω_L)

3

1) $\omega_{c1} = 616 \text{ rad/sec}$
 $\omega_{c2} = 17.86 \text{ rad/sec}$
 $\omega_{c3} =$
 $\omega_L = 616.5 \text{ rad/sec}$

2) $\omega_{c1} = 200 \text{ rad/sec}$
 $\omega_{c2} = 750 \text{ rad/sec}$
 $\omega_L = 798 \text{ rad/sec}$

$\omega_L > \max(\omega_s)$ مقبول شو ما كان عدد ال caps // $\sum \omega_s > \omega_L$

$\sum \omega_s \gg \omega_L \gg \max(\omega_s)$

1] Calculate each ω_c alone.


$\omega_{c1} = \frac{1}{C_1 \text{Req1}}$ اللي بيؤنها ال Cap (1)

$\omega_{c2} = \frac{1}{C_2 \text{Req2}}$ اللي بيؤنها ال Cap (2)


2] Estimate ω_L :

$\text{Max of } \omega_s \ll \omega_L \ll \text{sum of } \omega_s$

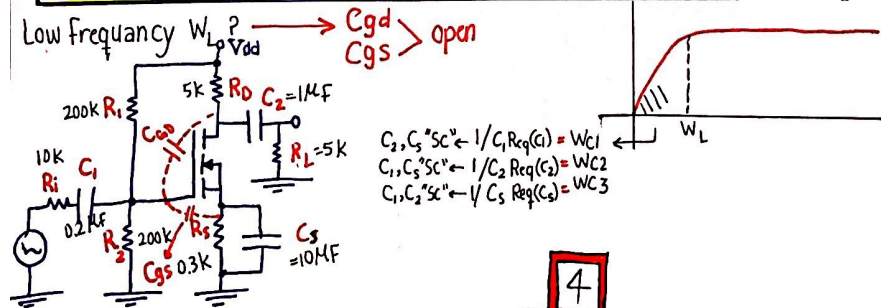L22, Part 2 / Amplifier Frequency Response Example



AC ss Low Frequency Eq. Circuit

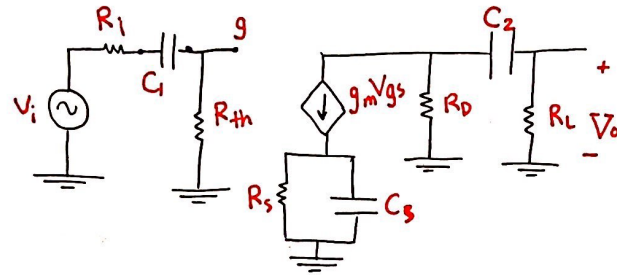

1 $\omega_{C1} = \frac{1}{C_1 \text{Req}(C_1)}$

$\text{Req}(C_1) = R_{th} \parallel R_i = R_{th} \parallel (R_1 + R_{th})$

Kill Indep. Sources \leftarrow seen by C_1 $V_i=0$

Series

$\omega_{C1} = 45.45 \text{ rad/sec}$

2 $\omega_{C2} = \frac{1}{C_2 \text{Req}(C_2)} \Rightarrow [C_1, C_s \Rightarrow \text{Short}]$

$\text{Req}(C_2) = R_D + R_L$

$\omega_{C2} = 100 \text{ rad/sec}$

$V_{gs} = 0$
(حساب الرتبة)
then $V_{gs} \cdot g_m = 0$
'open'

3 $\omega_{Cs} = \frac{1}{C_s R_{th}(3)} \Rightarrow [C_1, C_2 \Rightarrow \text{Short}]$

$R_{th}(3) = R_s \parallel \frac{1}{g_m r_{ds}}$

$r_{ds} \rightarrow \infty$

$\omega_{Cs} = 1050 \text{ rad/Sec}$

$\omega_{C1} = 45.45 \text{ rad/sec}$
 $\omega_{C2} = 100 \text{ rad/sec}$
 $\omega_{Cs} = 1050 \text{ rad/sec}$

$\max \omega < \omega_L < \sum$

$1050 < \omega_L < 1195.45$

5

$$\sum = W_L$$

$$w_{c1} = w_{c2} = (0.1 - 0.15) W_L$$

$$w_{ce} \text{ or } w_{cs} = \left(\frac{70}{80} - \frac{100}{100} \right) W_L = (0.7 - 0.8) W_L$$

بزرگتر از 100 راد/ثانیه

Design Criteria

[بزرگتر از 100 راد/ثانیه]

assume $w_L = w_{c1} + w_{c2} + w_{cs}$

$$\max(w's) < W_L < W_1 + W_2 + \dots + W_n$$

Design for certain $w_L \leftarrow$ given "1000 rad/sec"