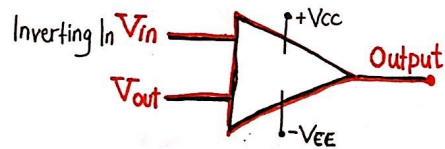


Electronics 236 → L18 Part 1 op-amp1


Operational Amplifier

- Integrated Circuit .
- Used for different Applications
 - Math operations
 - Control systems
 - Comparison
 - Instrumentation
- Filters
- Communications Eng.


OP- Amp "Not design but how to use the op amp as a device .




Equivalent Circuit :

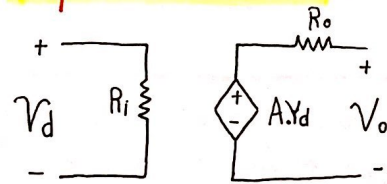

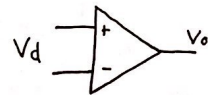- A very high ($A > 100000$)
- R_i very high ($M\Omega$'s)
- R_o very small (Ω 's)



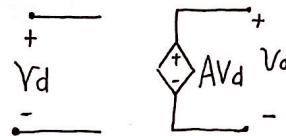
Ideal op-amp : "Equivalent circuit" Considering $\uparrow R_i$ "open circuit" and $\downarrow R_o$ "short circuit"



1




Op-amp characteristic

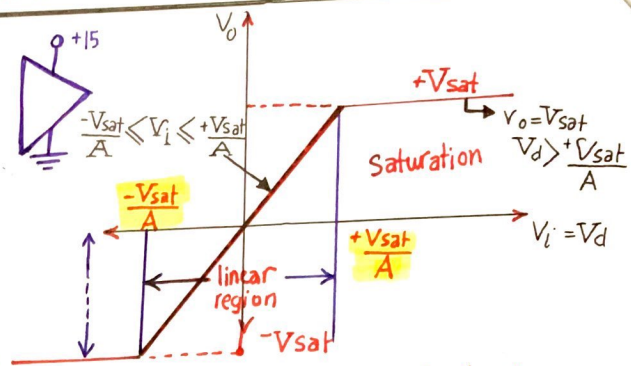$+V_{sat} \cong +V_{cc} - 2$
 $-V_{sat} \cong -V_{cc} + 2$
 "For calculation Purpos in this course"





Op-Amp Ratings

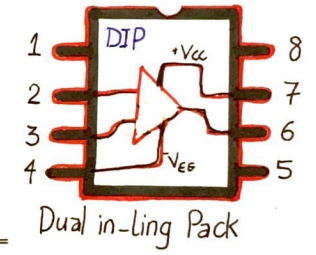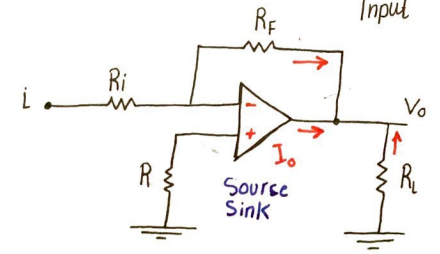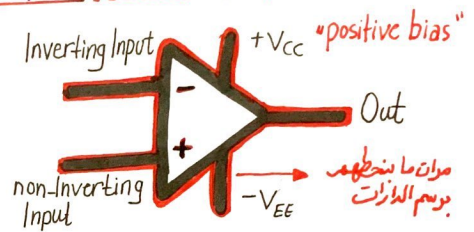
- $-V_{sat} \leq V_o \leq +V_{sat}$
- $I_o \leq I_{o,max}$



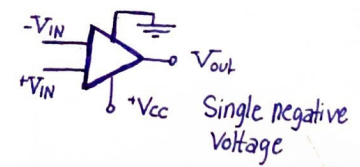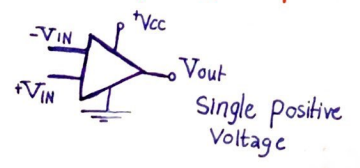Most OP Amps require dual power supply with Common Ground
 & Some Op Amps require single Supply "with some restriction"



OP-Amp Configuration

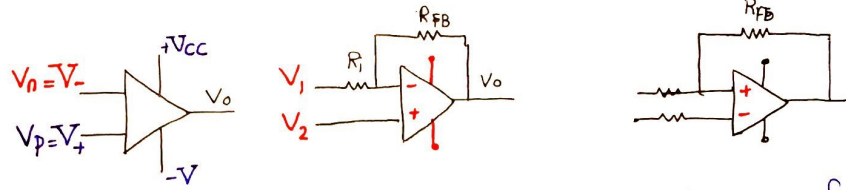

① no feedback

- used as Comparator

$$V_o = \pm V_{sat}$$

② Negative feedback

- used as an Amplifier



$$-V_{sat} < V_o < +V_{sat}$$

③ Positive feedback

- Comparator with Hyst.

$$V_o = \mp V_{sat}$$

Op-Amp as an Amplifier

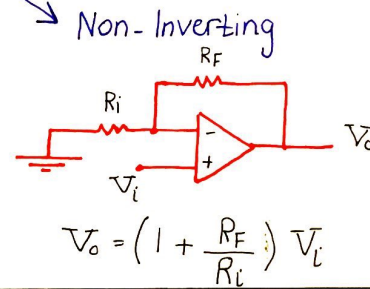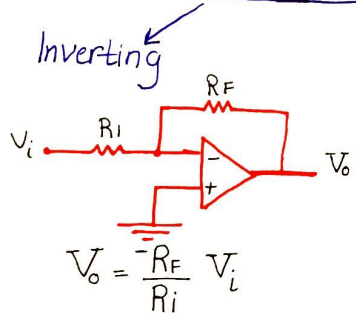


L18-Part 2 Inverting Amp. Analysis

using ideal op-amp Model


$$\begin{cases} I_p = I_n = 0 \\ V_p = V_n \end{cases}$$

only for Amp. with negative feedback

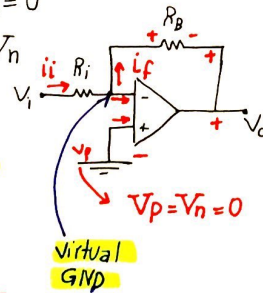

$$I_i = I_f + I_n$$
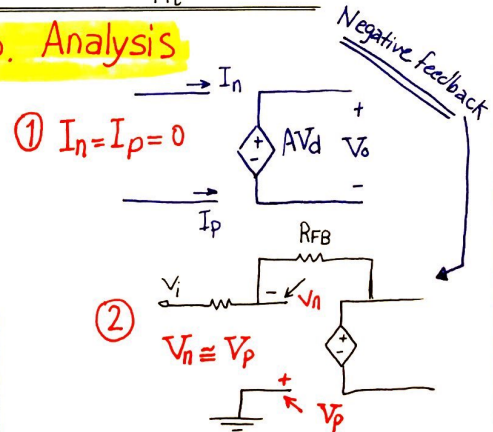
$$I_i = \frac{V_i - V_n}{R_i} = \frac{V_i}{R_i} = I_f$$



$$V_o = -I_f R_f = -\frac{V_i}{R_i} \cdot R_f = -\frac{R_f}{R_i} V_i$$

3

Example


Find the value of V_o and I_o and verify if the opamp is in linear or saturation mode for two values of feedback resistor; assume $I_{o(max)} = 20\text{ mA}$

1) $R_F = 100\text{ k}\Omega$ 2) If $R_F = 2\text{ M}\Omega$

$$-10 + 2 = -8 \quad V_p = 0$$

$$-V_{sat} \leq V_o = -\frac{R_F}{R_i} \cdot V_i \leq +V_{sat}$$

$$I_o \leq I_{o(max)} = 25\text{ mA}$$

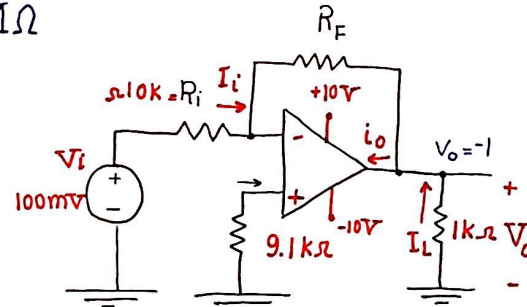

$$V_o = \frac{-100\text{ k}}{10\text{ k}} \cdot V_i = -10 \times 100\text{ mV} = -1\text{ V} \quad \text{ضمن النطاق}$$

$$I_i = I_f = \frac{100\text{ mV}}{10\text{ k}} = 10\text{ }\mu\text{A} \quad \left| \quad I_L = \frac{1}{1\text{ k}} = 1\text{ mA}$$

$$I_o = I_f + I_L = 10\text{ }\mu\text{A} + 1\text{ mA} = 1.01\text{ mA} < 20\text{ mA} \checkmark$$

Op Amp is a low current device

2) $R_F = 2\text{ M}\Omega \Rightarrow 2000\text{ k}$

$$V_o = \frac{-2\text{ M}}{10\text{ k}} * 100\text{ mV} = -20\text{ V}$$

$-V_{sat} \leq V_o \leq +V_{sat}$, but V_o not in the range
 V_o is limited to -8 V

$$I_o = 10\text{ }\mu + \frac{8}{1\text{ k}} = 8\text{ mA} \checkmark$$

Assume $R_L = 200\Omega$

$$I_o = 10\text{ }\mu + \frac{8}{200} = 40.01\text{ mA} > I_{o(max)}, I_o \text{ is limited to } 20\text{ mA}$$

$$V_o = 20\text{ mA} \times 200 = -4\text{ V}$$

