
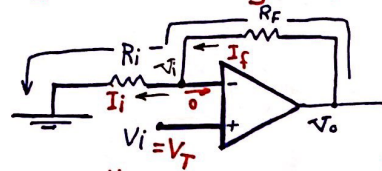


Non-Inverting Amp.

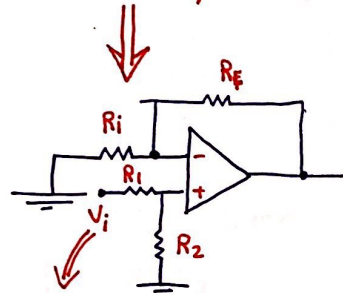

$I_p = I_n = 0$   
 $V_p = V_n = V_+ = V_-$   
 $\rightarrow i_i = \frac{V_i}{R_i}$   
 $\rightarrow i_f = i_i + i_n^0$




$V_o = I_f R_f + I_i R_i$   
 $V_o = I_f (R_f + R_i)$   
 $= \frac{V_i}{R_i} (R_f + R_i)$

$V_+ = \frac{R_2}{R_1 + R_2} \cdot V_i$

$V_o = V_i \left( 1 + \frac{R_f}{R_i} \right)$ , general case  $V_+$  instead of  $V_i$

Example "Non-inverting"

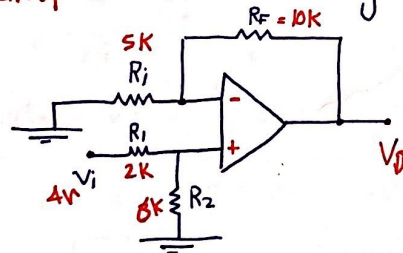

$V_o = V_+ \left( 1 + \frac{R_f}{R_i} \right)$   
 $= 3 \left( 1 + \frac{10k}{5k} \right) = 9 \text{ volt}$


$-V_{sat} \leq V_o \leq +V_{sat}$

$V_+ = \frac{6k}{8k} \cdot 4 = 3$


$1 = \frac{V_o}{V_+}$  يعني Gain=1  
 الحل اننا نجعل  $R_f$  Short و  $R_i$  open

\* الاربعة هي نفس اللي فوق

→ Buffer اول

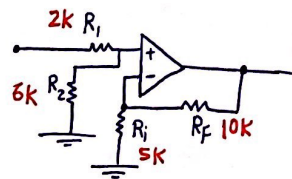


# Non-Inverting Adder

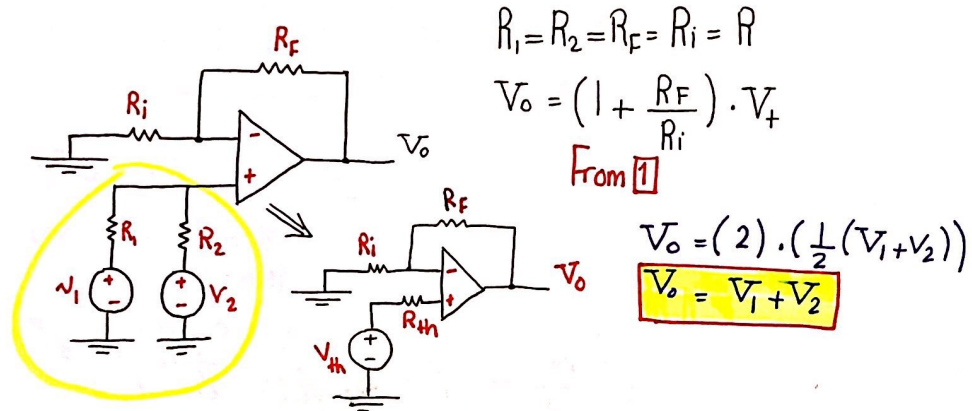

Super Position :

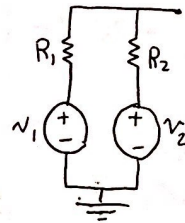
[1] Kill  $V_2$   
 $V_{th}^{\prime} = \frac{R}{R+R} V_1 = \frac{1}{2} V_1$




[2] Kill  $V_1$   
 $V_{th}^{\prime\prime} = \frac{R}{2R} \cdot V_2 = \frac{1}{2} V_2$

[3] Total =  $V_{th}^{\prime} + V_{th}^{\prime\prime} = \frac{1}{2}(V_1 + V_2) \dots [1]$
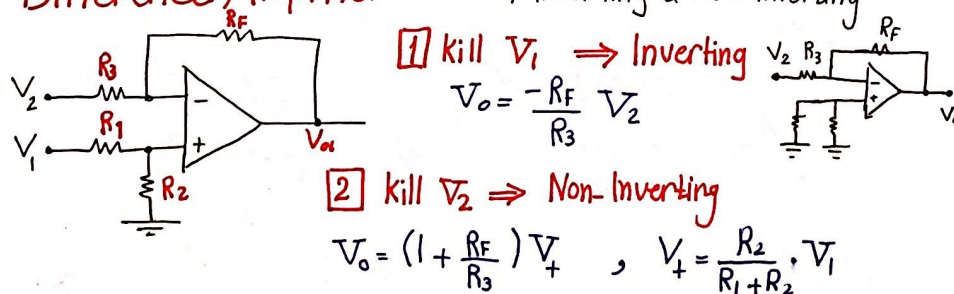
# Difference Amplifier - mix of Inverting & non-Inverting



[2]

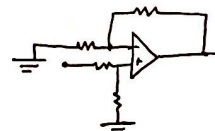

# Difference Amplifier

Continue

$$V_o = \underbrace{\left(1 + \frac{R_F}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right)}_a V_1 - \underbrace{\frac{R_F}{R_3}}_b V_2$$

$$V_o = a V_1 - b V_2$$


let  $R_1 = R_3 = R$   
 $R_2 = R_F = mR$

$$V_o = \left(\frac{R_3 + R_F}{R_3}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_1 - \frac{R_F}{R_3} V_2$$

$$= \frac{R_2}{R_3} V_1 - \frac{R_F}{R_3} V_2 = m V_1 - m V_2 = m(V_1 - V_2) \dots (*)$$

Difference Amplifier

# Instrumentation Amp (IC)

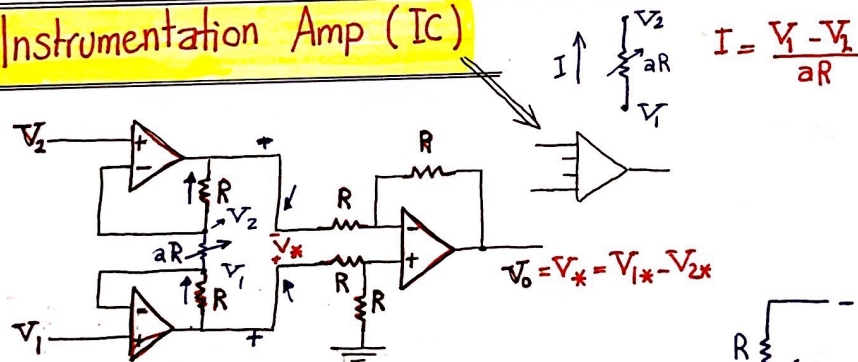

From [1]:  $V_o = V_*$

$$V_o = \left(1 + \frac{2}{a}\right) (V_1 - V_2)$$

هي نفسها (\*)

$$m = 1 + \frac{2}{a} \text{ يعني}$$

$$V_* = I \cdot (R + R_a) \leftarrow \begin{matrix} R \\ aR \\ R \end{matrix} \uparrow V_*$$


$$= \frac{(a+2)R}{aR} (V_1 - V_2)$$

$$V_* = \left(1 + \frac{2}{a}\right) (V_1 - V_2) \dots [1]$$

هذا يعني potentiometer value only changing

Gain is adjusted + Buffers

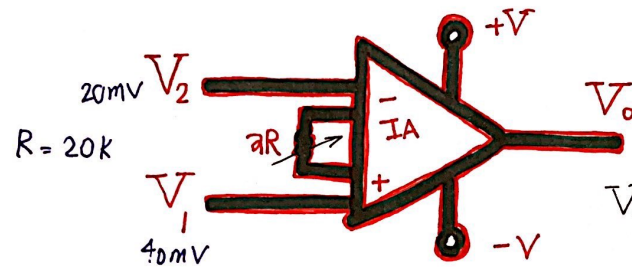يعني لما بدي اغير Gain بي يعني بغير بقيمة a في المقاومة المتغيرة.



$$V_o = \left(1 + \frac{2}{a}\right)(V_1 - V_2)$$

5 = Gain الينا

$$5 = \left(1 + \frac{2}{a}\right)(40m - 20m)$$

$$250 = 1 + \frac{2}{a} \Rightarrow a = \frac{2}{240}$$

$$aR = \frac{2}{240} \times 20k =$$

$$\frac{1}{2}(V_1 + V_2)$$