

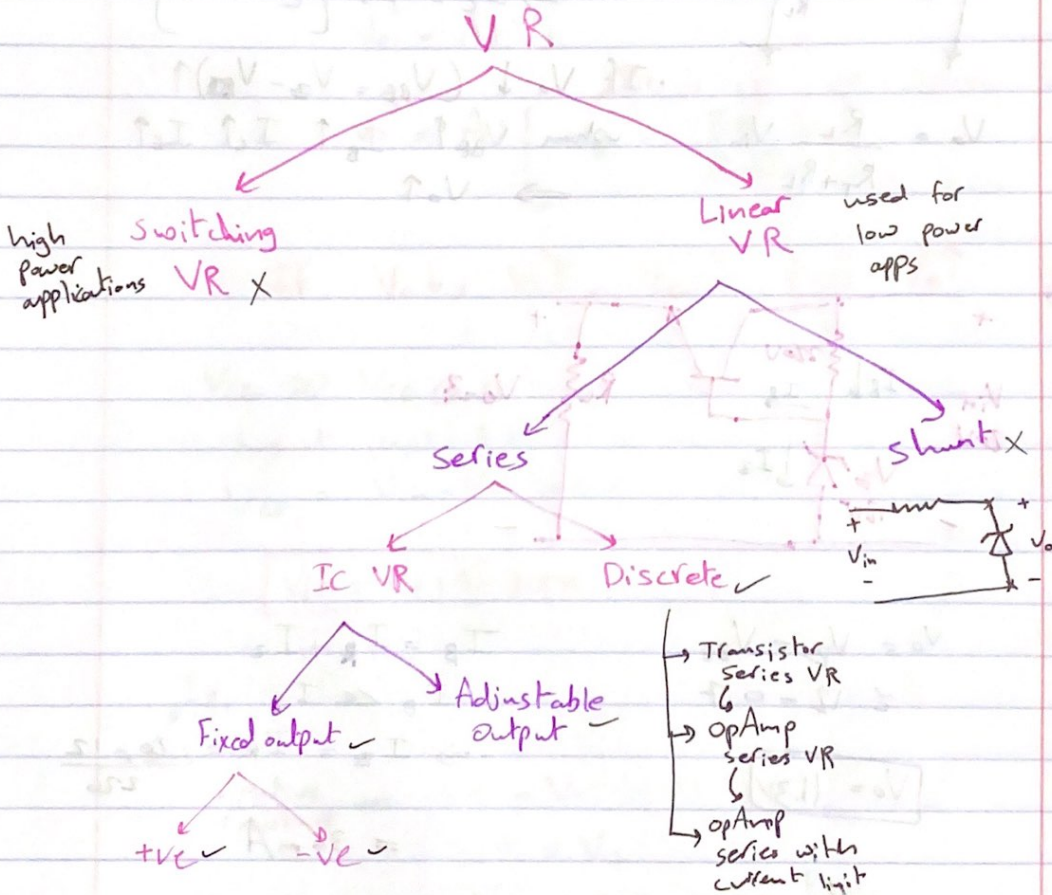


III: Voltage Regulator

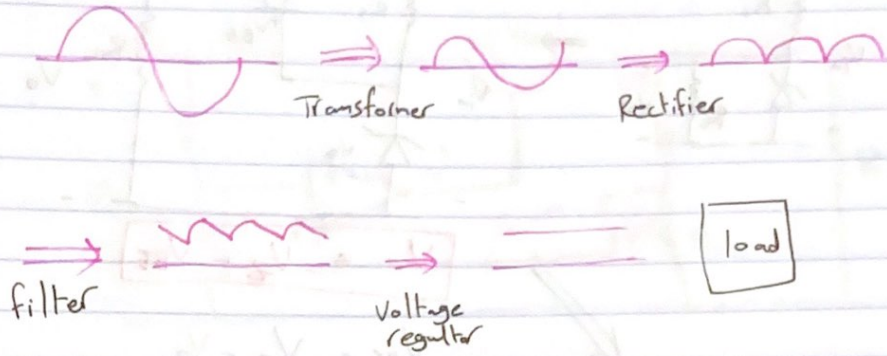

Transistor series VR

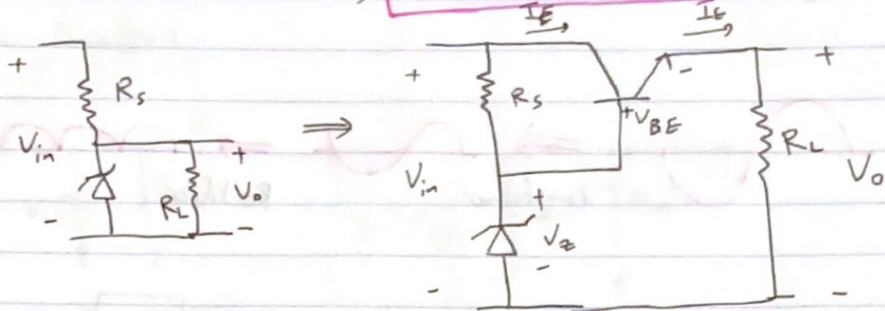

$$V_o = V_Z - V_{BE}$$


$$V_{BE} = V_Z - V_o$$

↳ control signal

$$\Rightarrow I_C = I_S \left[e^{\frac{V_{BE}}{nV_T}} - 1 \right]$$

• If $V_o \downarrow$ ($V_{BE} = V_Z - V_o$) \uparrow
 when $V_{BE} \uparrow$ $I_B \uparrow$ $I_C \uparrow$ $I_E \uparrow$
 $\Rightarrow V_o \uparrow$
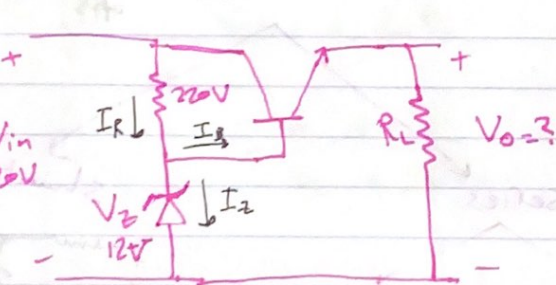
$$V_o = \frac{R_L \cdot V_{in}}{R_T + R_L}$$



$$V_o = V_Z - V_{BE} \approx 12 - 0.7$$

$$V_o = 11.3V$$


$$I_B = I_R + I_Z$$

$$I_B \ll I_Z$$

$$\Rightarrow I_Z = I_R = \frac{20 - 12}{220}$$

$$= 36 mA$$

2) opAmp series VR

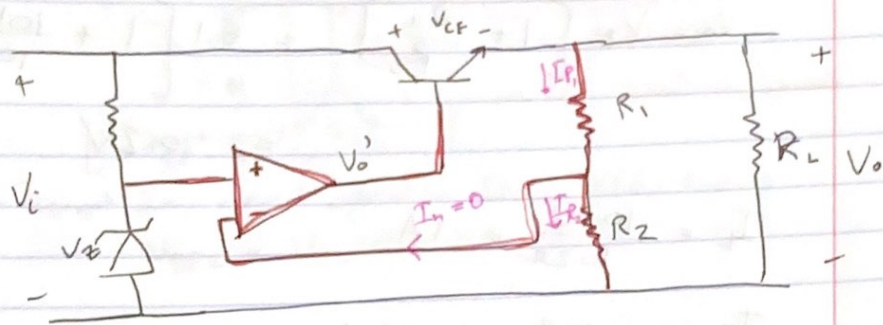

$$V_i = V_o + V_{CE}$$

$$V_o' = A_d V_d$$

$$V_o' = A_d \left[V_{Z} - \frac{R_2}{R_2 + R_1} V_o \right]$$

IF $V_o \downarrow, V_o' \uparrow, V_{be} \uparrow, I_E \uparrow, V_o \uparrow$

$$V_{CE} \Rightarrow V_{CE(sat)}$$

↳ at least 2V

$$V_{CE} = V_{in} - V_o > 2V$$

$$V_{in} > V_o + 2 \quad ***$$

$$I_{R_1} = I_{R_2} = I$$

in mA's

negative feedback \Rightarrow

$$V_+ = V_-$$

$$V_+ = V_Z$$

$$V_- = V_{R_2} = V_o \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow V_Z = V_o \frac{R_2}{R_1 + R_2}$$

$$V_o = V_Z \left[1 + \frac{R_1}{R_2} \right] \quad *$$

$$1) V_Z < V_o$$

$$2) V_{in} > V_o + 2$$

ex slide 7


$$V_o = V_z \left[1 + \frac{R_2}{R_3} \right] = 5.1 \left[1 + \frac{10K}{10K} \right]$$
$$= 10.2V$$

$$I_L = \frac{10.2V}{10.2\Omega} = 1A$$

$$I_{R2} = \frac{10.2}{20K} \approx 0.5mA$$

$$I_E = 1.005A$$

Power rating of BJT

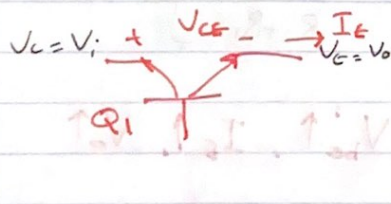
$$P_{Q1} = V_{CE} \cdot I_E$$
$$= (V_{in} - V_o) I_E$$
$$= (15 - 10.2)(1.005)$$
$$= 4.824 \text{ watt}$$

lost \rightarrow heat
use a 5 watt BJT

use a 5 watt BJT


$$I_L = \frac{10.2}{5.1} = 2A$$

$$R_L = 5.1\Omega$$

$$P_{Q1} = (15 - 10.2) \times 2A$$
$$= \underline{9.6 \text{ watt}}$$

in this case BJT will be damaged

3) opAmp series VR with current limit

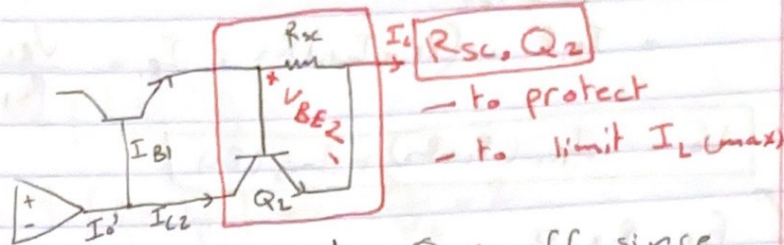

1) $I_L < I_{L(max)}$ In normal operation Q_2 is off since $V_{BE2} = V_{Rsc} < 0.7V$

2) $I_L = I_{L(max)} V_{BE} = V_{Rsc} = I_{L(max)} \cdot R_{sc} = 0.7$

3) when $I > I_{L(max)}$

$I_o' = I_{B1} + I_{C2}$

• for $I_{C2} = 0 \Rightarrow I_o' = I_{B1}$ Q_2 off


2) Q_2 ON $\Rightarrow \downarrow I_{B1} = I_o' - I_{C2} \uparrow$

$\downarrow I_{E1} \Rightarrow \downarrow I_L \leq I_{L(max)}$

~~$V_o = (1 + \frac{R_2}{R_1}) V_z$~~ \Rightarrow not valid in current limit mode

$V_o = I_{L(max)} R_L$

\Rightarrow IC Voltage Regulator

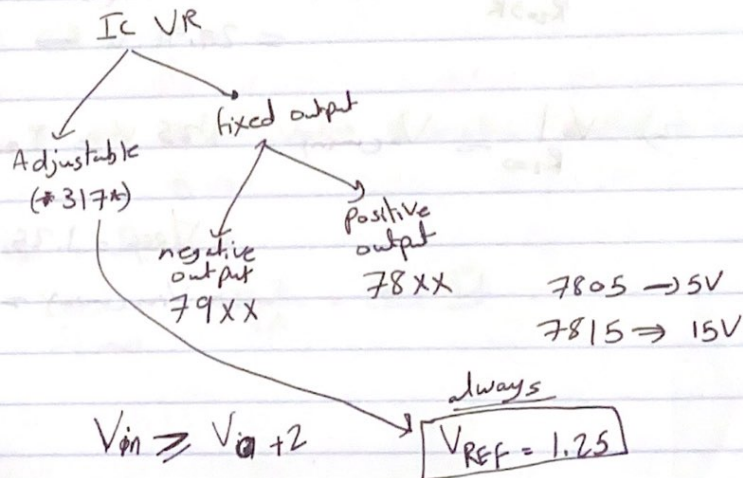

$$V_o = V_{R1} + V_{R2}$$

$$= I_{R1} R_1 + (I_{R1} + I_{adj}) R_2 ; I_{R1} = \frac{V_{R1}}{R_1} = \frac{V_{REF}}{R_1} = \frac{1.25}{R_1}$$

$$V_o = I_{R1} (R_1 + R_2) + I_{adj} (R_2)$$

for $R_2 = 0$

$$V_o = I_{R1} \cdot R_1 = \frac{V_{REF}}{R_1} \cdot R_1 = V_{REF} = 1.25$$

for $R_2 \neq 0$

$V_o =$

ex $R_1 = 220 \Omega$, $R_2 = 5k\Omega$ potentiometer ($R_2(\min) = 5$
 $R_2(\max) = 0$)

$$I_{adj} = -50 \mu A$$

- Find $V_o(\min)$ and $V_o(\max)$

- Find range of V_{in} ?

$$V_o = I_{REF} (R_1 + R_2) + I_{adj} R_2$$

$$I_{R1} = I_{REF} = \frac{1.25}{220} = 5.68 \text{ mA}$$

$$I_{adj} = 50 \mu A$$

$$1) V_o |_{R_2=5k} = V_o(\max) = 5.68 \text{ m} (220 + 5k) + 50 \mu (5k) = 29.91 \text{ V} \rightarrow V_{in(\max)} = 29.91 + 2$$

$$2) V_o |_{R_2=0} = V_o(\min) = 1.25 \text{ V} = I_{REF} \cdot R_1 = \frac{V_{REF} R_1}{R_1}$$

$$= V_{REF} = 1.25$$

$$\Rightarrow V_{in(\min)} = 1.25 + 2$$

ex slide 10

$$1) V_0 = V_Z \left[1 + \frac{R_1}{R_2} \right]$$

$$12 = 4 \left[1 + \frac{R_1}{R_2} \right] \Rightarrow \frac{R_1}{R_2} = 2$$

I_{R_1} must be small $\Rightarrow R_1, R_2$ must be
in 100's of ohms
or k Ω 's

$$\begin{matrix} R_1 = 2 \Omega \\ R_2 = 1 \Omega \end{matrix}$$

$$I_{R_1} = I_{R_2} = \frac{12}{3} = \underline{4A} \times$$

$$\begin{matrix} \text{let } R_1 = 20k\Omega \\ \therefore R_2 = 10k\Omega \end{matrix}$$

$$\times R_3 = ?$$

$$I_Z \geq I_{Z(\min)}; I_Z = I_R = \frac{V_{in} - V_Z}{R_3} \geq 2mA$$

$$R_3 \leq \frac{V_{in} - V_Z}{2mA} = \frac{20 - 12}{2mA}$$

$$\Rightarrow \underline{4k\Omega} \leq R_3 \leq 8k\Omega$$

$$R_3 = 8k\Omega$$

$$2) I_{L(\max)} = 1A$$

$$R_{sc} = ?$$

$$V_{BE} = 0.7 \text{ V} \Leftarrow \text{default value if another value is not given}$$

$$V_{BE} = V_{R_{sc}} = I_L R_{sc}$$

$$R_{sc} = \frac{V_{BE}}{I_{L(\max)}} = \frac{0.7}{1A} = \underline{0.7\Omega}$$

$$3) V_o \Rightarrow R_L = 100\Omega, R_L = 8\Omega$$

$$V_o = 12, R_L = 100\Omega \Rightarrow I_L = \frac{12}{100} = 0.12A < I_{L(max)}$$

$$\Rightarrow V_o = 12V$$

$$V_o = 12, R_L = 8\Omega \Rightarrow I_L = \frac{12}{8} = 1.5A > I_{L(max)}$$

$$V_o = I_{L(max)} * R_L = 1A * 8\Omega = 8V$$


$$\hookrightarrow V_o \neq V_z \left(1 + \frac{R_L}{R_2}\right) \leftarrow \text{since the current limit circuit starts working}$$

$$4) P_{Q1} = V_{CE(max)} * I_{E(max)}$$

$$V_{CE(max)} = V_{in(max)} - V_{o(min)} = 25 - 8 = 17V$$

$$I_{E(max)} = I_{R1} + I_{L(max)} = \frac{8}{30k} + 1A = 1.00026A$$

$$P_{Q1} = 17 * 1.00026 = 17.0068W$$

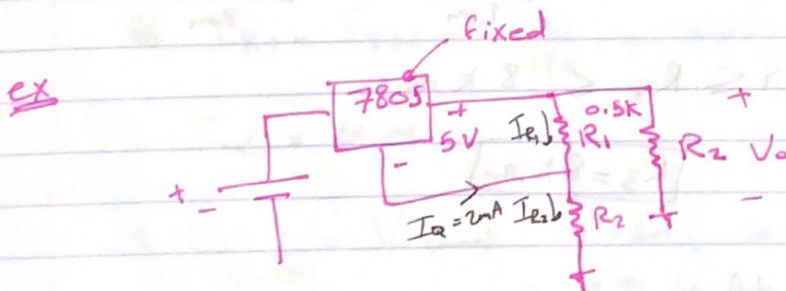

choose value of R_2 in order to have $V_o = 7.4V$

$$V_o = V_{R1} + V_{R2}$$

$$7.4 = 5 + V_{R2}$$

$$V_{R2} = 2.4V$$

$$R_2 = \frac{V_{R2}}{I_{R2}} = \frac{2.4}{12m}$$

$$R_2 = 0.2k\Omega$$

$$I_{R2} = I_{R1} + I_Q$$

$$\frac{5}{0.5k} + 2m =$$

$$12mA = I_{R2}$$


T12: Frequency Response

$$x \begin{cases} f & \text{or } \omega = 2\pi f \\ \log f, \log \omega & \xrightarrow{\text{unit}} \text{[decade]} \end{cases}$$

$$y \begin{cases} A(j\omega) = \frac{V_o}{V_i} \\ |A(j\omega)| \text{ or } 20 \log |A(j\omega)| \Rightarrow \text{in dB} \end{cases}$$

$$f_L, \omega_L = \frac{|A_{v(\text{mid})}|}{\sqrt{2}}$$

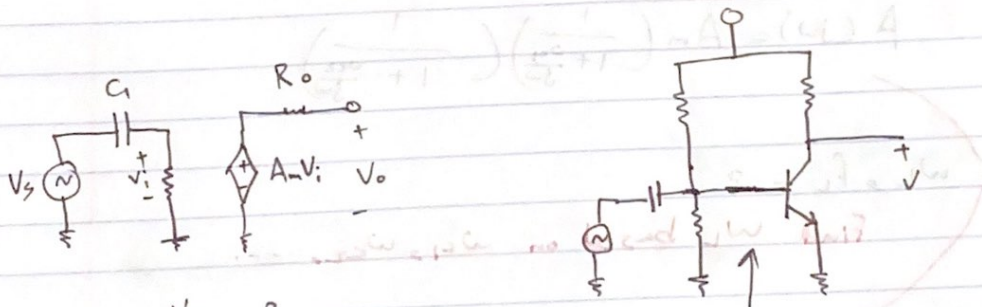1) Consider C_1 only ($C_1, C_2 \Rightarrow$ short, $C_{be}, C_{bc} \Rightarrow$ open)



$$\frac{V_o}{V_s} = ?$$

$$V_o = A_m V_i$$

$$A_m = A_v(\text{mid})$$

$$V_i = \frac{R_i}{R_i + \frac{1}{j\omega C_1}} V_s \Rightarrow V_o = \frac{A_m R_i}{R_i + \frac{1}{j\omega C_1}} V_s$$

$$\frac{V_o}{V_s} = \frac{A_m R_i}{R_i + \frac{1}{j\omega C_1}}$$

$$\Rightarrow |A(j\omega)| = \frac{A_m R_i}{\sqrt{(R_i)^2 + \left(\frac{1}{\omega C_1}\right)^2}}$$

$$\Rightarrow = \frac{A_m}{\sqrt{1 + \left(\frac{\omega C_1}{\omega}\right)^2}} \quad \omega_C = \frac{1}{R_i C_1}$$

for $\omega = \omega_{c1} \rightarrow 20 \log |A(j\omega)| = 20 \log A_m - 20 \log 0.707$
 $= -3dB$

$\omega = 0.1 \omega_c \rightarrow 20 \log |A(j\omega)| = -20dB$ ← High pass filter

together

$$C_1 \rightarrow \omega_{c1} = \frac{1}{C_1 R_{in}}$$

$$A(j\omega) = A_m \left(\frac{1}{1 + \frac{\omega_{c1}}{j\omega}} \right)$$

$$C_2 \rightarrow \omega_{c2} \rightarrow A_m \left(\frac{1}{1 + \frac{\omega_{c2}}{j\omega}} \right)$$

$$A(j\omega) = A_m \left(\frac{1}{1 + \frac{\omega_{c1}}{j\omega}} \right) \left(\frac{1}{1 + \frac{\omega_{c2}}{j\omega}} \right)$$

$\omega_L, f_L = ?$

Find ω_L based on $\omega_{c1}, \omega_{c2}, \dots$

$$|A(j\omega)| = \frac{A_m}{\sqrt{2}}$$


$$\omega_L^2 = \frac{\omega_{c1}^2 + \omega_{c2}^2}{2} + \frac{\sqrt{\omega_{c1}^4 + 6\omega_{c1}^2\omega_{c2}^2 + \omega_{c2}^4}}{2}$$

$$\omega_{c1} < \omega_L < \omega_{c1} + \omega_{c2}$$

$$\max(\omega's) < \omega_L < \text{Sum}(\omega's)$$

Ex slide 13

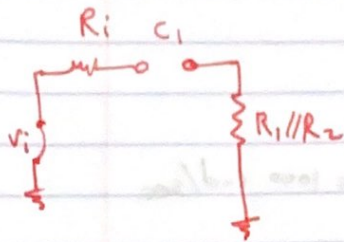
Action Plan: 1) take C_1 (while C_2, C_3 shorted)
and find $\omega_{c1} = \frac{1}{C_1 R_{th1}}$;



$$R_{th1} = (R_1 // R_2) + R_i$$


seen by C_1 & $V_i = 0$

2) take C_2 (while C_1, C_3 shorted)

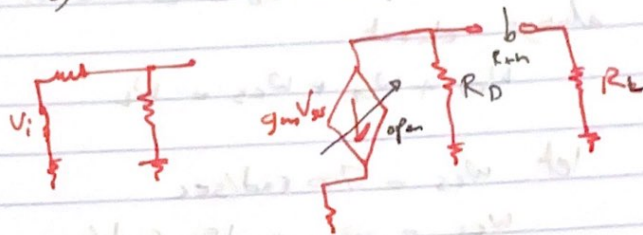

$$V_{gs} = 0, R_{th2} = R_L + R_D$$

3) consider C_3 (while C_1, C_2 shorted)

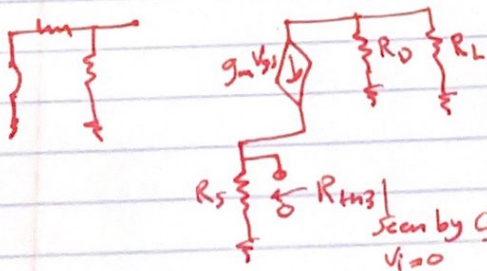

$$= R_S // \frac{1}{g_m}$$

seen by C_3 & $V_i = 0$

$$\lim_{\omega \rightarrow \infty} \left(\frac{r_{ds} + R_D // R_L}{\omega + 1} \right)$$

$$\omega_{c1} = 45.45 \text{ rad/sec}$$

$$\omega_{c2} = 100 \text{ rad/sec}$$

$$\omega_{c3} = 1050 \text{ rad/sec}$$

analysis

$$1050 < \omega_L < 1195.5$$

* Design of ω_L

$$? \leq \omega_L \leq \omega_{c1} + \omega_{c2} + \omega_{cs}$$

$$\omega_{cs} > \omega_{c1}$$

$$\omega_{cs} > \omega_{c2}$$

Design criteria

$$\omega_L = 1000 \text{ rad/sec}$$

assume $\omega_{cs} = (0.7 - 0.8) \omega_L$

(let $\omega_{c1} = \omega_{c2} = (0.1 - 0.15) \omega_L$)

always check

$$\omega_{c1} + \omega_{c2} + \omega_{cs} = \omega_L$$

let $\omega_{cs} = 700 \text{ rad/sec}$

$$\omega_{c1} = \omega_{c2} = 150 \text{ rad/sec}$$

$$\omega_{cs} = \frac{1}{C_s R_{rms}} \Rightarrow C_s = ?$$

$$\boxed{C_s > \frac{1}{\omega_{cs} R_{rms}}}$$