
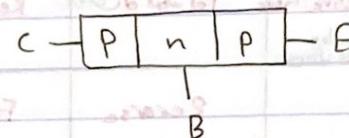
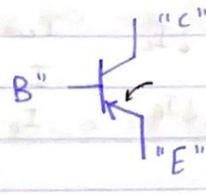
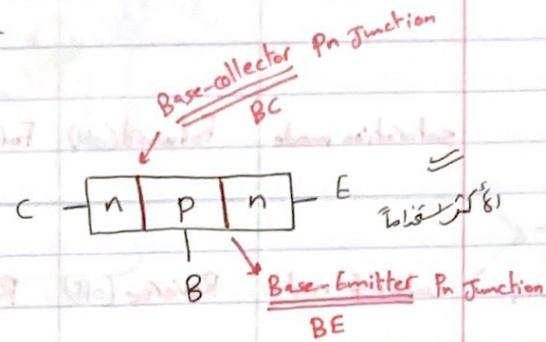


T₆ : BJT Construction & Operation


* Bipolar Junction Transistor

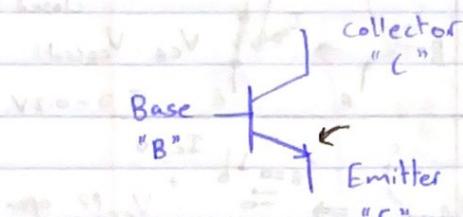


⇒ Transistor Structure

جامعة العلوم الإسلامية



NPN

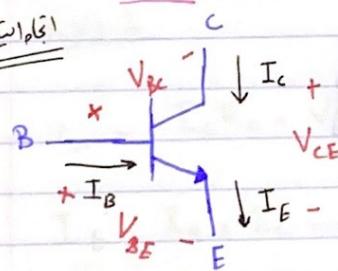

PNP

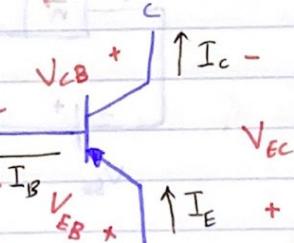

⇒ Transistor Biasing

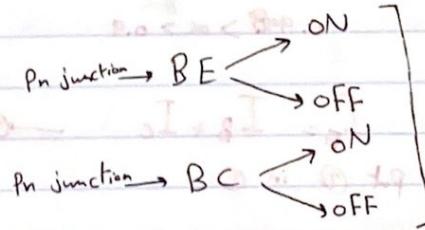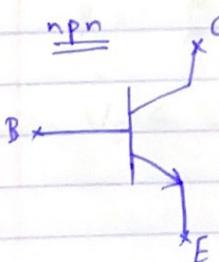

4 possible
combination
↓
4 possible
modes of
operation

$I_B = I_C$

Junction/Mode


BE

BC

Saturation mode

Forward (ON)

Forward (ON)

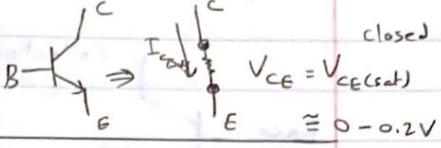


used in
digital
Electronics

Cut-off mode

Reverse (OFF)

Reverse (OFF)

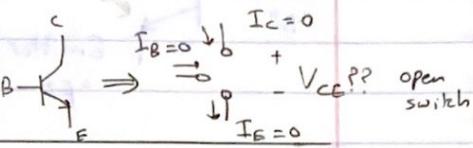

** linear (Active) mode: Forward (ON)
Amplifiers \Rightarrow used in analog electronics


Reverse

Forward

$$\begin{aligned} I_C &= \beta I_B \\ I_C &= \alpha I_E \\ I_E &= I_B + I_C \end{aligned}$$

$V_{CE(sat)} < V_{CE} < V_{CE(max)}$

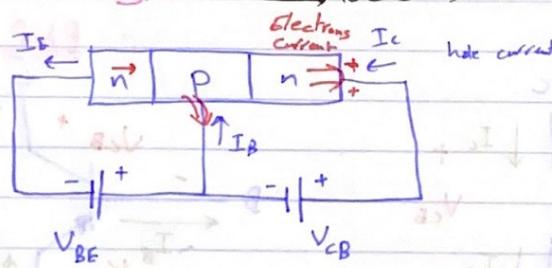\Rightarrow In active region \rightarrow BE (ON) \rightarrow BC (OFF)



$$I_C = \frac{\alpha}{1-\alpha} I_B \quad \text{minority} \quad \rightarrow \textcircled{1}$$


$$0.99\beta > \alpha > 0.9$$

$$I_E = I_B + I_C \quad \rightarrow \textcircled{2}$$

put \textcircled{2} in \textcircled{1}

$$I_C = \frac{\alpha}{1-\alpha} I_B, \quad B = \frac{\alpha}{1-\alpha}$$

$$\Rightarrow I_C = \beta I_B$$

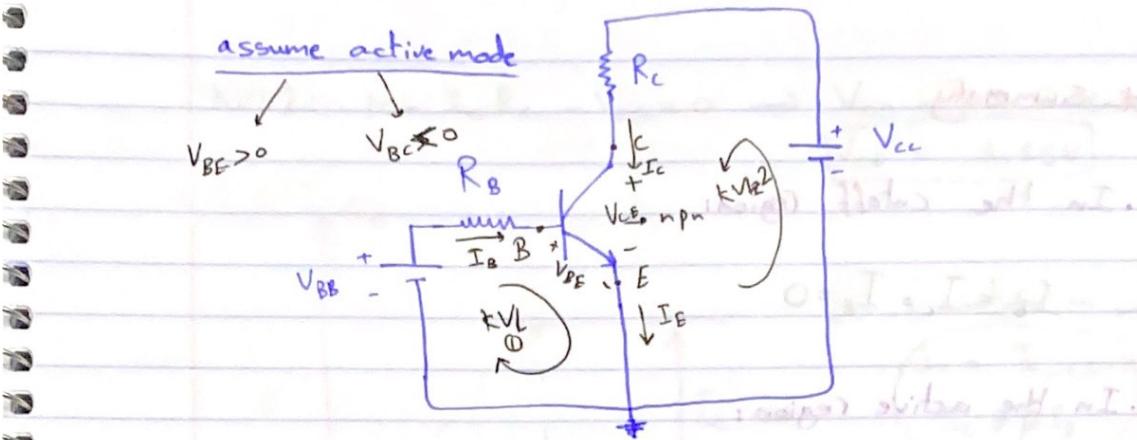

$$V_{BE} > 0 \Rightarrow BE \rightarrow ON$$

$$V_{BC} < 0 \Rightarrow BC \rightarrow OFF$$

KVL1

$$V_{BB} = I_B R_B + V_{BE} \quad \text{--- (1)}$$

KVL2

$$V_{CC} = I_C R_C + V_{CE} \quad \text{--- (2)}$$

$$I_E = I_B + I_C \quad \text{--- (3)}$$

$$\alpha = \frac{I_C}{I_E} \quad \text{--- (4)}$$

$$\beta = \frac{I_C}{I_B} \quad \text{--- (5)}$$

$$\beta = \frac{\alpha}{1-\alpha} \quad \text{--- (6)}$$

$$V_E < V_B < V_C$$

* Summary

. In the cutoff region:

$$I_B = I_C = I_E = 0$$

. In the active region:

$$I_C = \alpha I_E$$

$$I_C = \beta I_B$$


$$I_E = (\beta + 1) I_B$$

$$\text{n-p-n, Si} \Rightarrow V_{BE} = 0.7V$$

$$\text{p-n-p, Si} \Rightarrow V_{BE} = -0.7V$$

$$V_{CE} > V_{CE,\text{sat}} = 0.2V, \text{n-p-n}$$
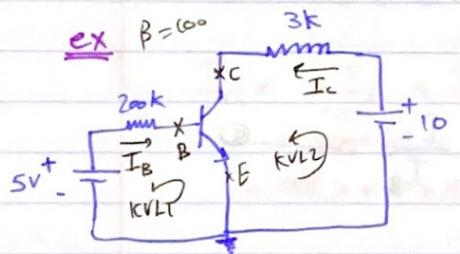
$$V_{CE} < V_{CE,\text{sat}} = -0.2V, \text{p-n-p}$$



Find mode of operation of BJT, I_{CQ} , V_{CEQ} .

BE \rightarrow FW

BC (FW)
↓ saturation

BC (BW)
↓ Active

. Assume BJT is in active mode:


$$\text{KVL1: } 5 - I_B \cdot 200k - V_{BE} = 0 \rightarrow V_{BE} = 0.7 \leftarrow \text{active}$$

$$\therefore I_B = \frac{5 - 0.7}{200k} = 21.5 \mu\text{A}$$

$$I_C = \beta I_B = 2.15 \text{ mA}$$

$$KVL2: 10 - I_C R_C - V_{CE} = 0 \rightarrow V_{CE} = 10 - 2.15m \times 3k$$

V_{CE} = 3.55V

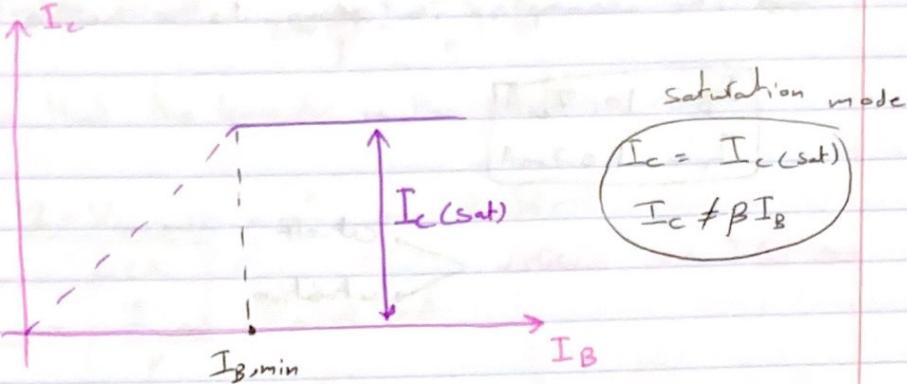

$$V_{CE} = V_{cc} - I_C R_C$$

$$\therefore I_{C(sat)} = \frac{V_{cc} - V_{CE(sat)}}{R_C}$$

$$I_{B(min)} = \frac{I_{C(sat)}}{\beta}$$

\Rightarrow If $I_B > I_{B(min)}$ \Rightarrow saturation mode

\Rightarrow If $I_B < I_{B(min)}$ \Rightarrow Active region


Assume saturation mode:

$$V_{CE} = V_{CE(sat)} = 0.2V, I_C = I_{C(sat)} = ?$$

$$10 = I_C \cdot 3k + I_B \cdot 2k$$


in saturation:
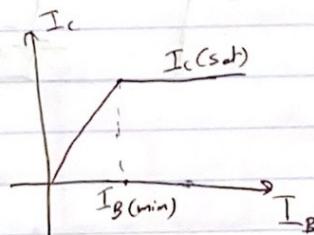
$$I_C \approx I_E = I_{C(sat)}, V_{CE} = V_{CE(sat)} = 0.2$$



$$\therefore I_{C(sat)} = \frac{10 - 0.2}{3k + 2k} = 1.96mA$$
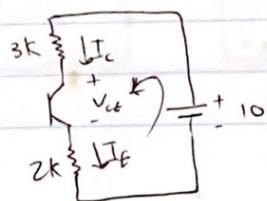
$$I_{B(min)} = \frac{I_{C(sat)}}{\beta} = 19.6mA$$



$$\rightarrow \text{Find } I_{B(\text{actual})} = \frac{5 - 0.7}{20k + 2k(1+1)} = 10.7 \text{ mA} < I_{B(\text{min})}$$

\Rightarrow The assumption is wrong. It's in active mode.

$$\boxed{I_B = 10.7 \text{ mA}}$$

$$\boxed{I_C = 1.07 \text{ mA}}$$


17:01

\Rightarrow BJT as switch

cut-off


saturation

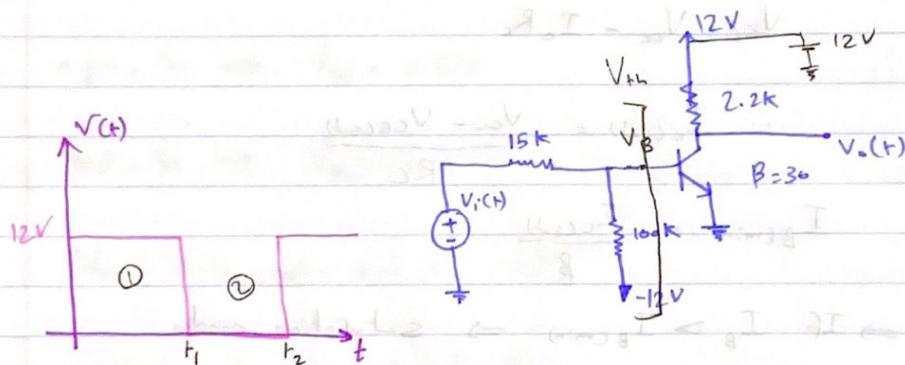ex Find $V_o(t)$ for the input given below:



$$① \quad 0-t_1 \Rightarrow V_i = 12V$$

To Find V_{th} & R_{th}

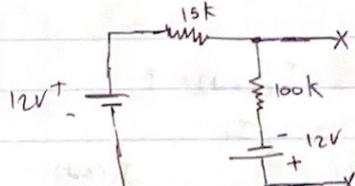

super position


$$V_{th}^1 = \frac{15k}{(15+100)k} \times 12V$$

$$V_{th}^2 = \frac{100k}{(15+100)k} \times 12V$$

$$V_{th} = V_{th}^1 + V_{th}^2 = 8.9V$$

$$R_{th} = 100k // 15k = 13k$$

Base-Emitter: Forward

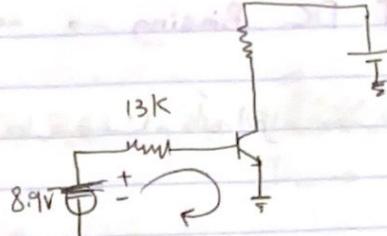

Assume that the transistor is in the saturation mode

$$\frac{12 - V_{CE(sat)}}{2.2k} = I_{c,sat} \rightarrow 5.36 \text{ mA}$$

$$I_{B(min)} = \frac{I_{c,sat}}{\beta} = 0.18 \text{ mA}$$

$$I_{B(actual)} = \frac{V_{th} - V_{BE}}{13k} = \frac{8.9 - 0.7}{13k} = 0.63 \text{ mA}$$

Since $I_B > I_{B(min)}$, our assumption is right

$$V_{CE(sat)} = V_o = 0.2 \text{ V}$$

$$I_c = 5.36 \text{ mA}$$

$$\textcircled{2} \quad t_1 - t_2 \Rightarrow V_i = 0 \text{ volt}$$

$$V_{th} = \frac{15}{15+100} \times 12 = -1.56 \text{ V}$$


$$R_{th} = 13k$$

Base-Emitter: Reverse

cutoff region

$$I_B = 0 \Rightarrow V_o = V_{CE} = 12 \text{ V}$$

inverter/not gate

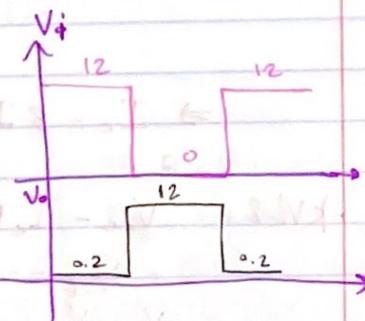

T₇: BJT DC Biasing → active/linear mode

البياس هو مصدر قوسيّة خارجية تأمّل أنّ الترانزistor يدخل باتجاه إيجابي.

① Fixed-bias circuit



dc Analysis

⇒ ac sources killed

⇒ f = 0

$$X_C = \frac{1}{2\pi f C} \approx \infty$$

caps are treated
as open circuit

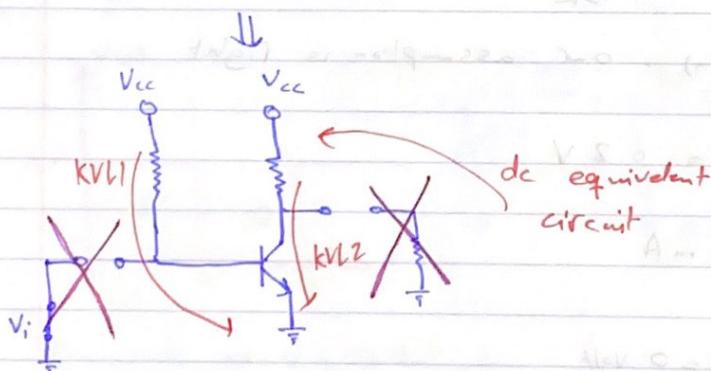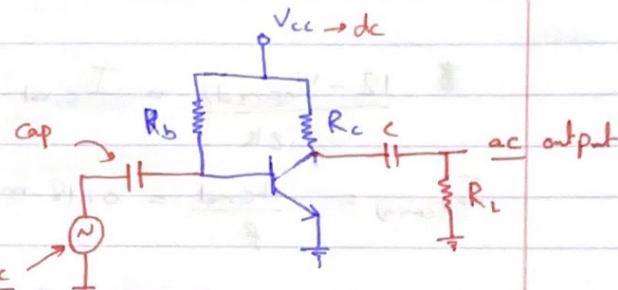

$$\cdot \text{KVL1: } V_{cc} - I_B R_B - V_{BE} = 0$$

$$\Rightarrow I_B = \frac{V_{cc} - V_{BE}}{R_B}$$

I_B هو المقدار الذي يتدفق من R_B في المقاومة.

I_C هو المقدار الذي يتدفق في المقاومة.

$$\Rightarrow I_C = \beta I_B$$

$$\cdot \text{KVL2: } V_{cc} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{cc} - I_C R_C$$

$$V_C - V_F = V_{cc} - I_C R_C$$

$$V_E = 0$$

$$\Rightarrow V_C = V_{CC} - I_C R_C \rightarrow I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$$V_{BE} = V_B - V_E$$

$$V_E = 0$$

$$\therefore V_{BE} = V_B$$

$$V_{BE} - V_{CE} - V_{BC} = 0$$

$$\therefore V_{BC} = V_{BE} - V_{CE}$$

ex $V_{CC} = 10V$, $\beta_{nominal} = 100$, $\beta_{min} = 50$, $\beta_{max} = 150$

$$V_{CEQ} = 5V, I_{CA} = 1mA$$

Find R_B & R_C

$$I_B = \frac{I_C}{\beta} = \frac{1mA}{100} = 10\mu A$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$10\mu A = \frac{10 - 0.7}{R_B}$$

$$R_B = 930k\Omega$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{10 - 5}{1mA} = 5k\Omega$$

$$R_C = 5k\Omega$$

• IF $\beta = \beta_{min} = 50$

$$I_B = 10\mu A$$

$$I_C = \beta I_B = 50(10\mu A) = 0.5mA$$

$$V_{CE} = V_{CC} - I_C R_C \Rightarrow V_{CE} = 7.5V$$

• IF $\beta = \beta_{max}$

$$I_B = 10\mu A$$

$$I_C = \beta I_B = 1.5mA$$

$$V_{CE} = 2.5V$$

\Rightarrow for $50 \leq \beta \leq 150$

$$I_B = 10 \text{ mA} \quad \text{fixed}$$

$$0.5 \text{ mA} \leq I_C \leq 1.5 \text{ mA}$$

$$2.5 \text{ V} \leq V_{CE} \leq 7.5 \text{ V}$$

$$\therefore \frac{I_{C(\max)}}{I_{C(\min)}} = \frac{1.5 \text{ mA}}{0.5 \text{ mA}} = 3 \text{ V} \quad \text{not very stable}$$

② Emitter-stabilized Bias Circuit

* KVL ①:

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E = (\beta + 1) I_B$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$\Rightarrow I_E = \frac{V_{CC} - V_{BE}}{\frac{R_B}{\beta + 1} + R_E} \quad (\beta \text{ is constant for small } I_E)$$

$$R_E \gg \frac{R_B}{\beta + 1}$$

$$I_E = \frac{V_{CC} - V_{BE}}{R_E}$$

Design rule / Assumption: $0.1 V_{CC} \leq V_E < 0.2 V_{CC}$

(Design I_E , choose R_E , R_B)

* KVL ②

$$-V_{CC} + I_C R_C + V_{CE} + I_B R_B = 0$$

$$\text{since } I_E \approx I_C \Rightarrow V_{CE} = V_{CC} - I_C (R_C + R_E)$$

ex $V_{cc} = 10V$, $B_{nominal} = 100$, $\beta_{min} = 50$, $\beta_{max} = 150$

$$V_{CE} = 5V, I_C = 1mA$$

Assumption to be used in design problem only if R_E is unknown

$$0.1 V_{cc} \leq V_E \leq 0.2 V_{cc}$$

① let $V_E = 0.1 V_{cc} = 1V$

$$I_E = \frac{V_E}{R_E}$$

$$R_E = \frac{1V}{0.99mA} \approx 1k\Omega = R_E$$

$$I_B = \frac{V_{cc} - V_{BE}}{R_B + (\beta+1)R_E}$$

$$R_B = 829k\Omega$$

$$R_C = \frac{V_{cc} - V_{CE} - V_E}{I_C} = \frac{10 - 5 - 1}{1mA} = 4k\Omega = R_C$$

If $\beta = \beta_{min} = 50$

$$I_B = \frac{10 - 0.7}{829k + (50)(1k)} = 10.56mA$$

$$I_C = \beta I_B = 0.528mA$$

$$V_{CE} = V_{cc} - I_C R_C - V_E = 10 - (0.528mA)(4k) - 1 \\ = 6.89V = V_{CE}$$

If $\beta = \beta_{max} = 150$

$$I_B = 9.489mA$$

$$I_C = 1.423mA$$

$$V_{CE} = 3.31V$$

$$50 \leq \beta \leq 150$$

$$10.56mA \geq I_B \geq 9.489mA$$

$$1.423mA \geq I_C \geq 0.528mA$$

$$6.89V \geq V_{CE} \geq 3.31V$$

$$\frac{I_{Cmax}}{I_{Cmin}} = \frac{1.423}{0.528} \approx 2.7$$

Improved but not very stable

③ DC Bias with Voltage Feedback

* KVL ①


$$V_{cc} - I R_L - I_B R_B - V_{BE} = 0$$

$$I = I_c + I_B$$

$$I_c = \beta I_B$$

$$I = (\beta + 1) I_B$$
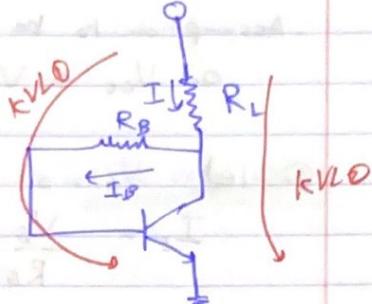
$$\Rightarrow I_B = \frac{V_{cc} - V_{BE}}{R_L(\beta + 1) + R_B}$$



* KVL ②

$$V_{cc} = I R_L + V_{ce}$$

$$V_{ce} = V_{cc} - (I_c + I_B) R_L$$

ex $V_{cc} = 10V$, $\beta_{\text{nominal}} = 100$, $\beta_{\min} = 50$, $\beta_{\max} = 150$

$V_{ce} = 5V$, $I_c = 1mA$

$$R_L = \frac{V_{cc} - V_{ce}}{I} = \frac{V_{cc} - V_{ce}}{I_B + I_c} = \frac{10 - 5}{1m + \frac{1m}{100}}$$

$$\Rightarrow R_L = 4.95k\Omega$$

$$I_B = \frac{V_{cc} - V_{BE}}{R_L(\beta + 1) + R_B} \Rightarrow [430\text{ f}\Omega] = R_B$$

• If $\beta = \beta_{\min} = 50$

$$I_B = 0.013627 \text{ mA}$$

$$I_C = 0.68 \text{ mA}$$

• If $\beta = \beta_{\max} = 150$

~~similarly find~~

$$I_B = 0.00793 \text{ mA}$$

$$I_C = 1.19 \text{ mA}$$

for $50 \leq \beta \leq 150$

$$0.68 \text{ mA} \leq I_C \leq 1.19 \text{ mA}$$

$$\therefore \frac{I_{C(\max)}}{I_{C(\min)}} = \frac{1.19 \text{ mA}}{0.68 \text{ mA}} \approx 1.75 \quad \text{Better Q-point stability}$$

④ Voltage Divider Bias

• Approximate Analysis

$$I_B \ll I_1$$

$$I_2 = I_B + I_1 \Rightarrow I_2 = I$$

$$V_B = \frac{R_1}{R_1 + R_2} V_{cc}$$

$$I_E (\text{approximate}) = \frac{V_E}{R_E} = \frac{V_B - V_{BE}}{R_E}$$

KVL

$$V_{CE} = V_{cc} - I_C R_C - I_E R_E$$

$$I_E \approx I_c$$

$$V_{CE} = V_{cc} - I_C (R_C + R_E)$$

Exact Analysis

Thevenin Equivalent circuit for the circuit left


$$V_{th} = \frac{R_1 V_{cc}}{R_1 + R_2}$$

$$R_{th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E$$

$$\text{but } I_B = \frac{I_E}{\beta + 1}$$
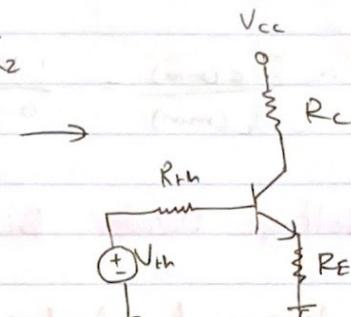
$$\therefore I_E(\text{exact}) = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$$



* $R_E \gg 10 R_{th}$ at least 10 in order to get I_E almost indep. of β

ex $V_{cc} = 10V$, $\beta_{\text{nominal}} = 100$, $\beta_{\min} = 50$, $\beta_{\max} = 150$

$V_{CE} = 5V$, $I_E = 1mA$

① let $V_E = 0.1 V_{cc} \Rightarrow V_E = 1V$

$$I_E = \frac{V_E}{R_E} \Rightarrow R_E = \frac{1V}{1.01mA} \approx 1k\Omega$$

$$\text{② let } R_{th} = \frac{R_E \cdot \beta_{(\text{nominal})}}{50} = \frac{1k(100)}{50} = 2k\Omega$$

$$\text{③ } V_{cc} = R_c I_c + R_E I_E + V_{CE}$$