



T8: BJT AC Models and Analysis

* We will deal with small signal amplifier (not power amplifier)

. There are two models used in small signal AC analysis
of a transistor:

- 1) r_e model X
- 2) Hybrid equivalent model \leftrightarrow (h -parameter)

Two-port networks

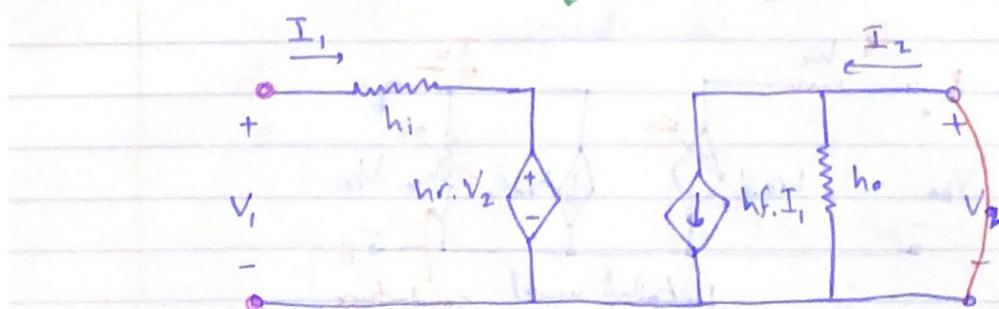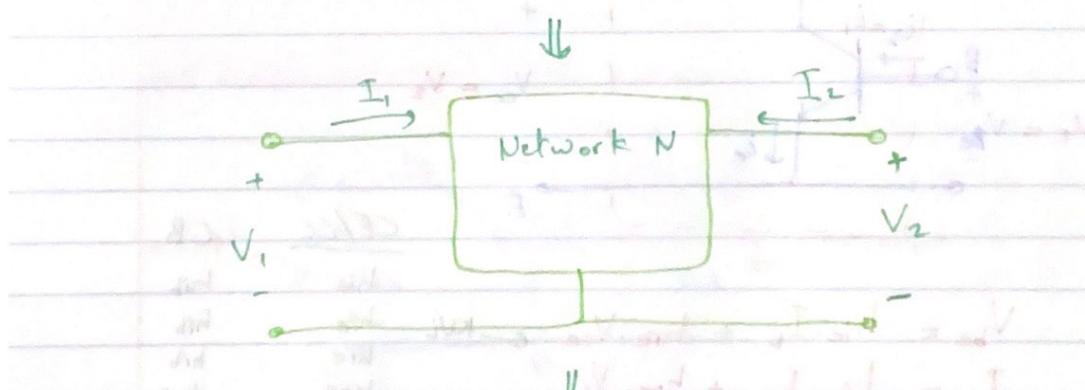

h -parameter equations:

$$KVL \rightarrow V_1 = h_i I_1 + h_r V_2$$

$$KCL \rightarrow I_2 = h_f I_1 + h_o V_2$$

$$h_i = \frac{V_1}{I_1} \Big|_{V_2=0}$$


$$h_f = \frac{I_2}{I_1} \Big|_{V_2=0}$$

$$h_r = \frac{V_1}{V_2} \Big|_{I_1=0}$$


$$h_o = \frac{I_2}{V_2} \Big|_{I_1=0}$$

→ BJT configurations

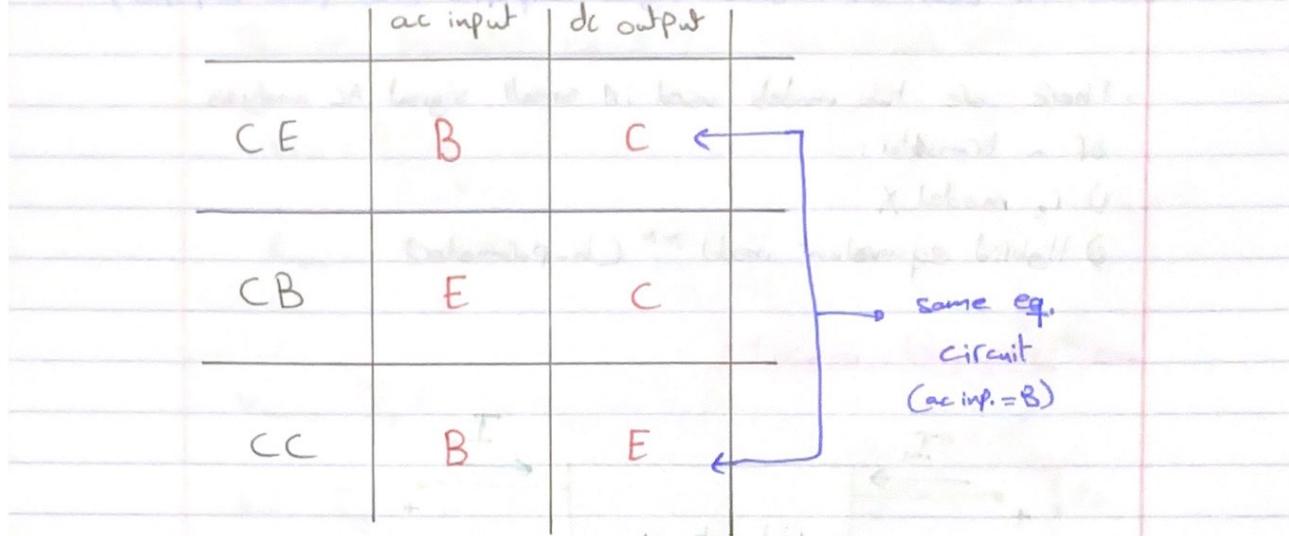(with biasing) with three bases, three collector currents




→ Common Emitter Configuration

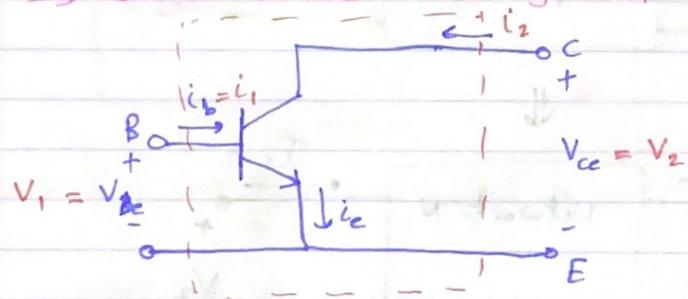

$$V_{be} = h_{ie} \cdot I_b + h_{re} \cdot V_{ce} \leftarrow \text{KVL}$$

$$I_c = h_{fe} \cdot I_b + h_{oe} \cdot V_{ce}$$

CE/CC	CB
h_{ie}	h_{ib}
h_{fe}	h_{fb}
h_{re}	h_{rb}
h_{oe}	h_{ob}

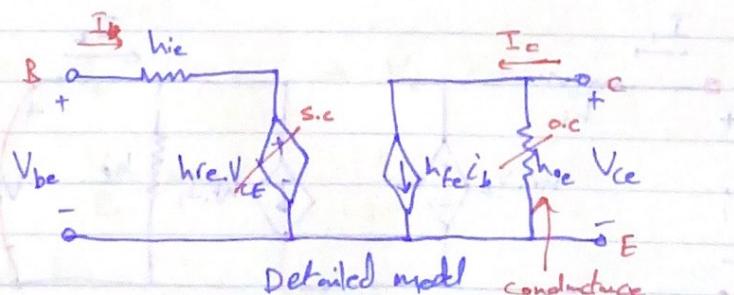


$$h_{re} \times 0.0002 \times$$

$$h_{oe} \times 2 \times 10^{-6} \text{ Siemens} \times$$

$$\frac{1}{2} = \text{Siemens} \times$$

$$V_{be} + V_{ce} = T + 1.2$$

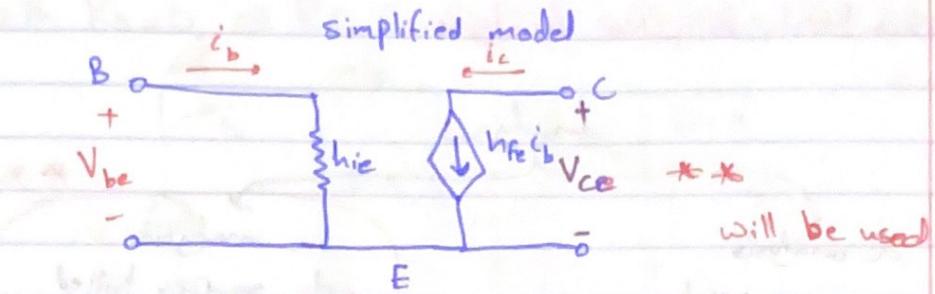

$$h_{fe} = \frac{i_c}{i_b} = \beta$$


$$h_{ie} = \frac{V_T}{I_{EQ}} \approx = \frac{V_T}{\frac{I_{EQ}}{h_{fe}}} = \frac{h_{fe} V_T}{I_{EQ}}$$

$$V_T = 25.69 \text{ mV} @ 25^\circ \text{C}$$


⇒ Common Collector

• Same as common emitter

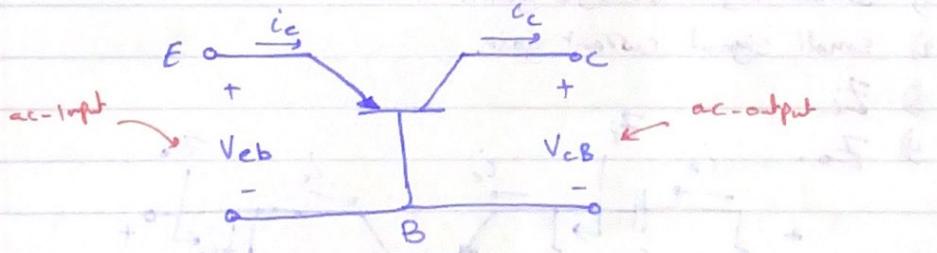⇒ Common-Base Configuration will not be the best



simplified model

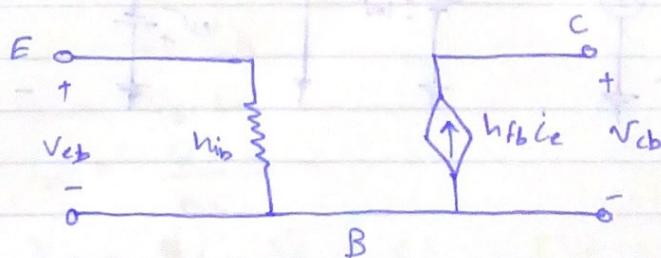

$$h_{ib} = \frac{V_T}{I_{EQ}}$$

$$h_B = \alpha = \frac{i_c}{i_e}$$

$$h_{ie} \rightarrow h_{ib}$$

⇒ BJT Amplifier Analysis

analysis

dc analysis

- ac source killed
- caps ~~circuit~~ open

ac analysis

- dc sources killed

$V \rightarrow 0 \rightarrow$ short

$I \rightarrow 0 \rightarrow$ open

$$- X_C = \frac{1}{2\pi f_C}; f_C \uparrow$$


$X_C \approx 0 \rightarrow$ Caps short

• small signal voltage gain = $A_V = \frac{V_o}{V_i}$


• small signal current gain = $A_i = \frac{i_o}{i_i}$

ex find all of the following quantities with and without R_S :

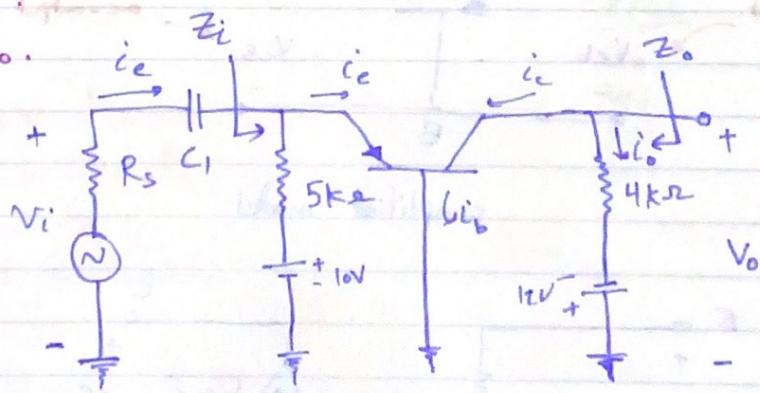- 1) small signal voltage gain.
- 2) small signal current gain.
- 3) Z_i .
- 4) Z_o .



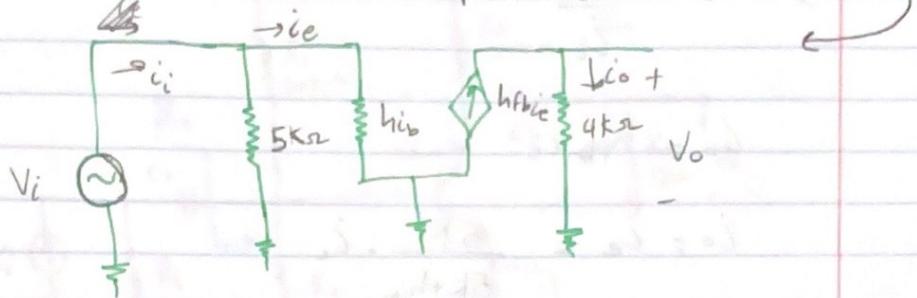
a) with $R_s = 0 \Rightarrow RC$ (s.c), Caps (s.c), DC sources (killed)



$$h_{fb} = \alpha \approx 1$$

$$h_{ib} = \frac{V_T}{I_{EQ}} ; I_{EQ} \text{ must be calculated from dc analysis}$$

DC Analysis

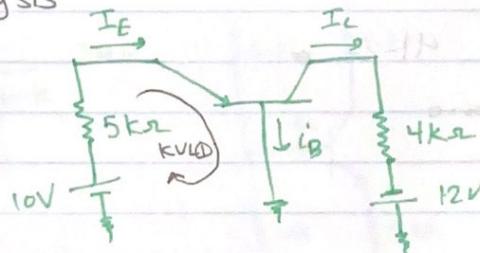

$$\text{KVL: } 10 = 5kI_{EQ} + V_{EB}$$

$$10 = 5k I_{EQ} + 0.7 \Rightarrow I_{EQ} = 1.86 \text{ mA}$$

$$h_{ib} = \frac{25.69 \text{ mV}}{1.86 \text{ mA}} = 13.98 \Omega = h_{ib}$$

$$A_v = \frac{V_o}{V_i}$$

$$V_o = i_o \cdot 4k$$

$$i_o = h_{fb} \cdot i_e$$

$$i_e = \frac{V_i}{h_{ib}}$$

$$\Rightarrow V_o = 1 \cdot \frac{V_i}{13.98} \cdot 4k \Rightarrow 286 = \frac{V_o}{V_i}$$

$$(b_2) A_i = \frac{i_o}{i_i}$$

$$i_o = h_{fb} \cdot i_e$$

$$i_o = i_e = \frac{5k}{5k+h_{ib}} \cdot i_i$$


$$\frac{i_o}{i_i} = \frac{5k^2}{5k^2 + 13.98} < 1$$

$$3) Z_i = 5k // h_{ib} = \frac{5k \cdot 13.98}{5k + 13.98} = id$$

$$4) Z_o = 4k \Omega$$

ind. sources = 0

b) with R_s

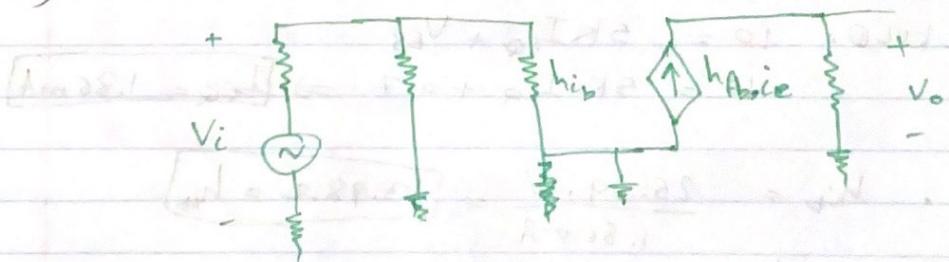


$$i_i = \frac{V_i}{Z_i + R_s} \quad \text{for } R_s = 50\Omega \quad A_v = 62.5$$

$$\text{for } R_s = 10k\Omega \quad A_v = 286$$

$$i_e = \frac{5k}{5k + h_{ib}} \cdot i_i \quad A_v = 286$$

$$\Rightarrow R_s \propto \frac{1}{A_v}$$

ex

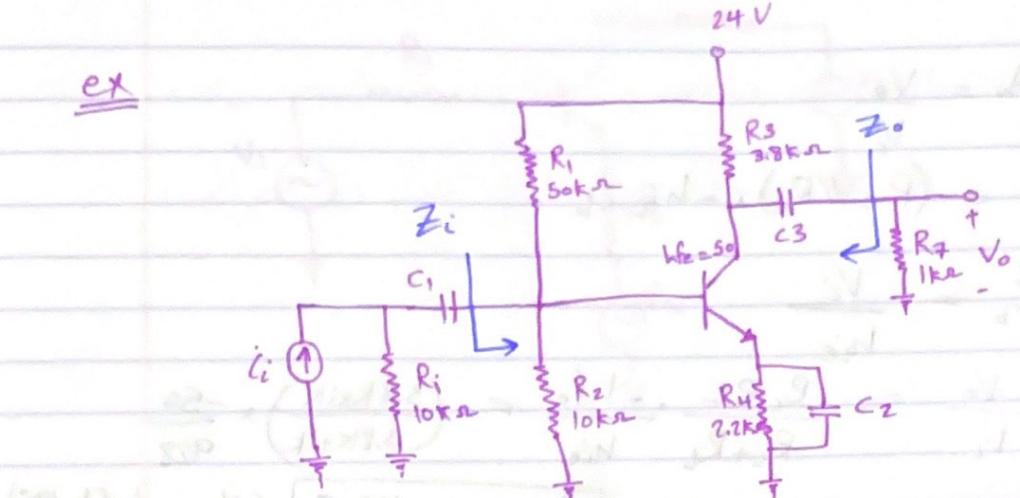

$$h_{ie} = \frac{V_T}{I_{BQ}}$$


To find I_{BQ} :

$$V_{TH} = \frac{10k}{10k + 50k} \cdot 24V$$

$$V_{TH} = 4V$$

$$R_{TH} = 10k // 50k$$

$$R_{TH} = 8.33k\Omega$$

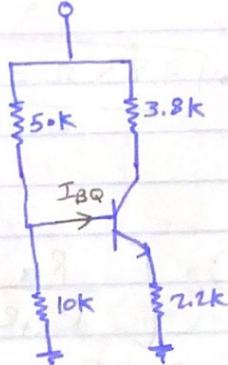


$$I_E = I_B (\beta + 1)$$

$$I_B = \frac{V_{TH} - 0.7}{R_{TH} + R_E(\beta + 1)} = \frac{4 - 0.7}{8.33k + 2.2k(50+1)} \quad \text{(By KVL)}$$

Base equivalent circuit
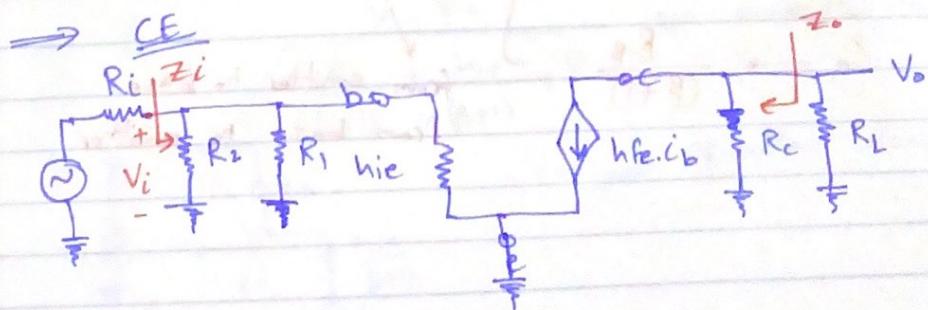
$$I_E = \frac{V_{TH} - 0.7}{R_E + R_m \frac{\beta + 1}{\beta + 1}} \quad \text{(emitter equivalent circuit)}$$



$$* A_v = \frac{V_o}{V_i}$$

$$V_o = (R_C // R_L) \times -h_{FE} \cdot i_b$$

$$i_b = \frac{V_i}{h_{IE}}$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{R_C R_L}{R_C + R_L} \cdot \frac{-h_{FE}}{h_{IE}} = \left(\frac{3.8k \times 1k}{3.8k + 1k} \right) \times \frac{-50}{928}$$

$$A_v = -42.7 \text{ (phase shift } 180^\circ)$$

$$* Z_i = (R_1 // R_2) // h_{IE}$$

$$* Z_o = R_3 = 3.8k \Omega = Z_o$$

$$* A_i = \frac{i_o}{i_i}$$

$$i_o = -h_{FE} \cdot i_b \left[\frac{R_3}{R_3 + R_2} \right]$$


$$i_b = i_i \left[\frac{R_1 // R_{th}}{(R_1 // R_{th}) + h_{IE}} \right]$$

$$A_i = \frac{i_o}{i_i} = -33 = A_i$$


⇒ Impedance Reflection Concept

$$i_b \rightarrow R_E(\beta + 1) \quad \left. \begin{array}{l} \text{simplification} \\ \text{Reflection} \end{array} \right\} \rightarrow \text{technique}$$
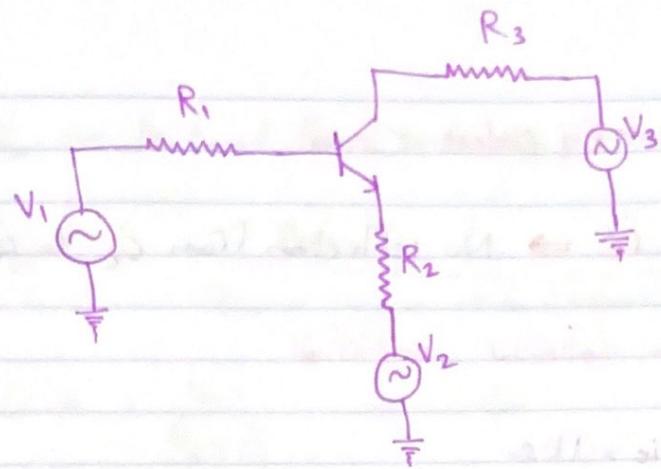
$$i_e \rightarrow \frac{R_B}{(\beta + 1)} \quad \left. \begin{array}{l} \downarrow \\ \text{from emitter to base} \\ \text{from base to emitter} \end{array} \right\}$$




\Downarrow

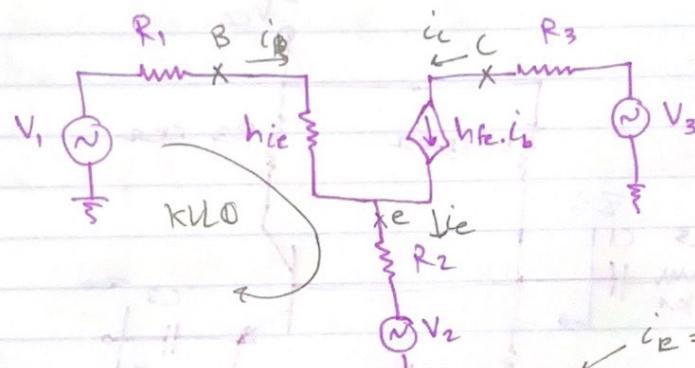


$$V_1 = R_1 i_b + h_{ie} i_b + R_2 (\beta + 1) i_b + V_2$$
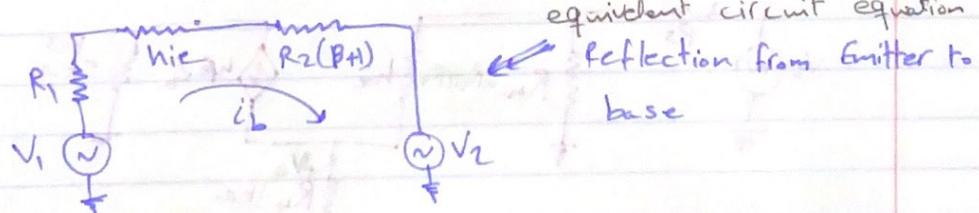
$$* i_b = \frac{V_1 - V_2}{R_1 + h_{ie} + R_2 (\beta + 1)} \leftarrow \text{base loop}$$


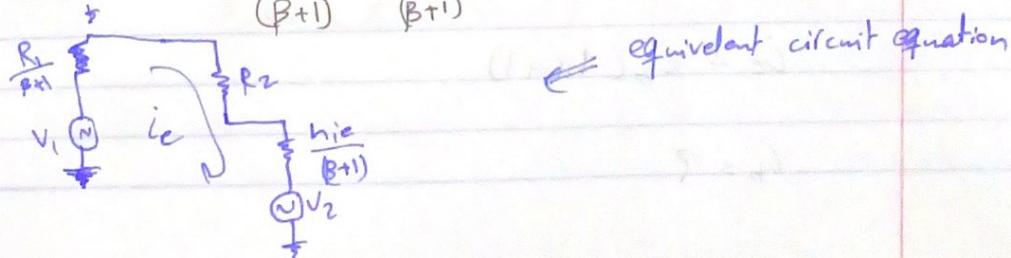
$$* i_e = \frac{V_1 - V_2}{\frac{R_1}{(\beta + 1)} + \frac{h_{ie}}{(\beta + 1)} + R_2} \leftarrow \text{emitter loop}$$



→ Collector Equivalent Circuit



$i_c \approx i_e \Rightarrow$ No reflection from i_c to i_e

→ Common Collector Amplifier

ex Given $h_{ie} = 1\text{k}\Omega$

$h_{fe} = \beta = 50$

Find A_v, A_i, Z_i, Z_o

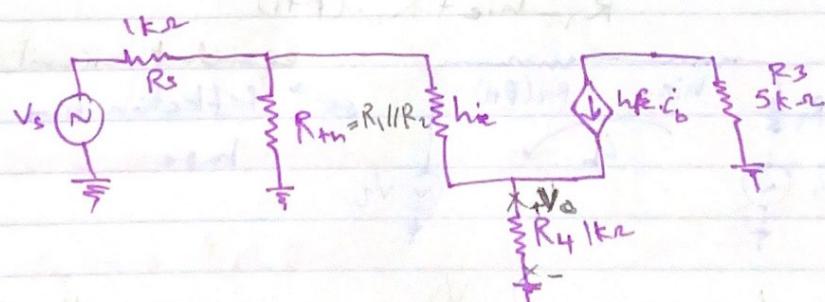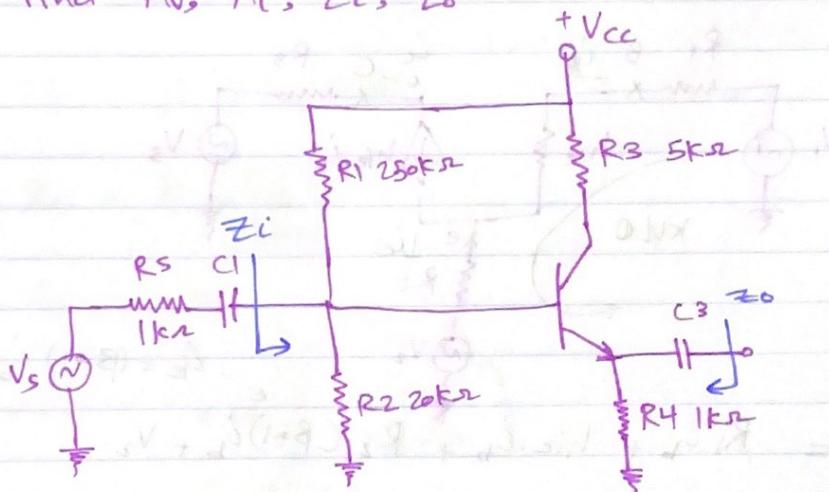

$$1) V_o = 1\text{k}\Omega \cdot i_e \quad \text{--- (1)}$$


$$\text{at } i_c = i_e (h_{fe} + 1)$$

$$i_b = ?$$

i_b can be found from base equivalent circuit

$$i_b = i_i \cdot \frac{R_{th}}{R_{th} + h_{ie} + 1k\Omega(h_{fe}+1)} \quad \textcircled{2}$$
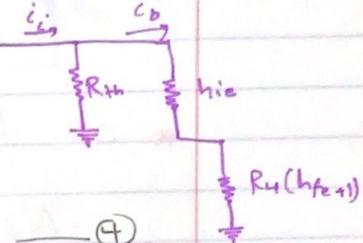
$$i_i = \frac{V_i}{R_s + Z_i} \quad \textcircled{2}$$



$$Z_i = R_{th} // (h_{ie} + 1k\Omega(h_{fe}+1)) \quad \textcircled{4}$$

$$AV = \frac{V_o}{V_i} = \frac{i_e}{i_b} \times \frac{i_b}{i_i} \times \frac{i_i}{V_s}$$

$$AV = 0.915 < 1$$

* CC amplifier doesn't provide any voltage gain

$$\Rightarrow AV \leq 1$$

$$2) A_i = \frac{i_o}{i_i}$$

$$i_o = \frac{V_o}{1k\Omega}$$

$$i_o = i_e = i_b(h_{fe}+1)$$

$$i_b = i_i \frac{R_{th}}{R_{th} + (h_{ie} + 1k\Omega(h_{fe}+1))}$$

$$A_i = 13.39 > 1$$

$$3) Z_i = R_{th} // (h_{ie} + 1k\Omega(h_{fe}+1))$$

Reflection
from
emitter
to
base

$$= 13.66 k\Omega (\text{high})$$

$$Z_{o1} = \left[\left(\frac{R_s}{(h_{fe}+1)} + \frac{R_{th}}{(h_{fe}+1)} \right) + \frac{h_{fe}}{(h_{fe}+1)} \right] \parallel 1k\Omega$$

amitter's input is at collector

$$= 36.8 \Omega \text{ (low)}$$

* CC Amplifier

$$A_v \leq 1$$



$$A_i \gg 1$$

$$Z_i \uparrow \uparrow \text{ Kt's}$$

$$Z_o \downarrow \downarrow \text{ s's}$$

~~high output impedance~~ \Rightarrow CC amplifier as a buffer

- Used to remove loading effect

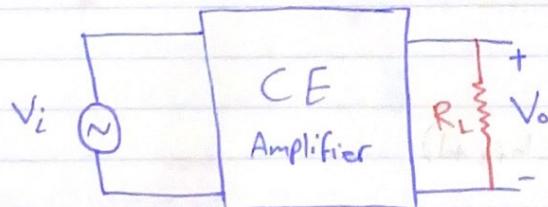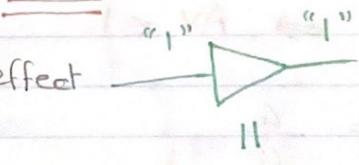


without Load $R_L = \infty$

$$A_{VN} = \frac{V_o}{V_i} \mid R_L = \infty$$


$$A_{VL} = \frac{V_o}{V_i} \mid R_L \neq \infty$$

$A_{VL} \ll A_{VN}$ (This is called loading effect)

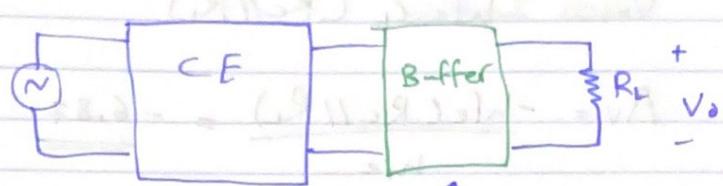
- A solution is to add a buffer between the original Amplifier and the load



Amplifier stage 1
Amplifier stage 2

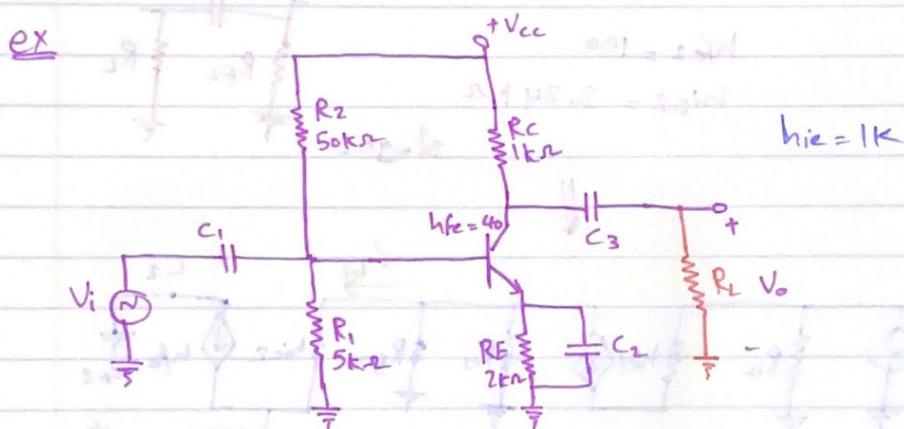

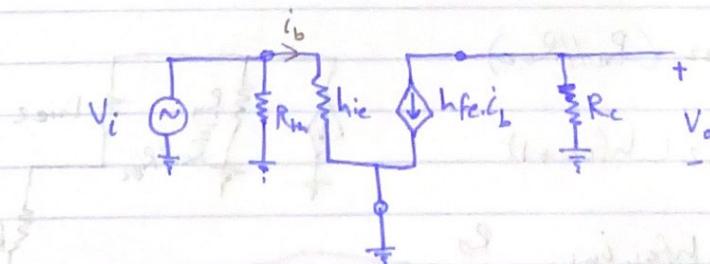i) without $R_L \Rightarrow R_L = \infty$



$$* V_o = -h_{fe} \cdot i_b \cdot R_c$$



$$i_b = \frac{V_i}{h_{ie}}$$

$$A_v = \frac{V_o}{i_b} \cdot \frac{i_b}{V_i} = -\frac{h_{fe} \cdot R_c}{h_{ie}} = -140$$

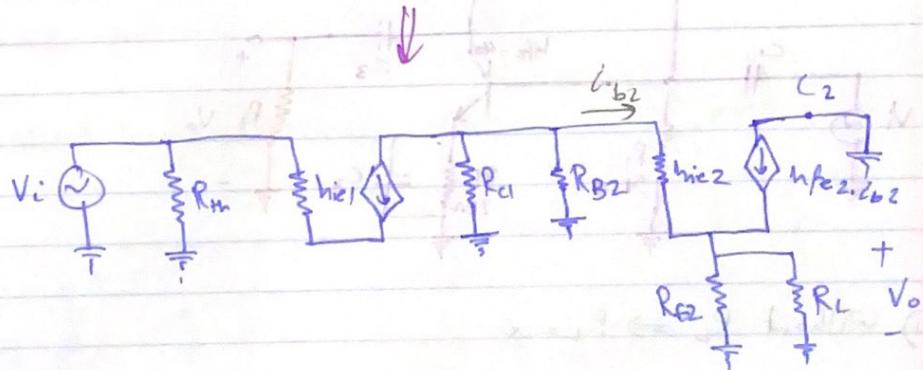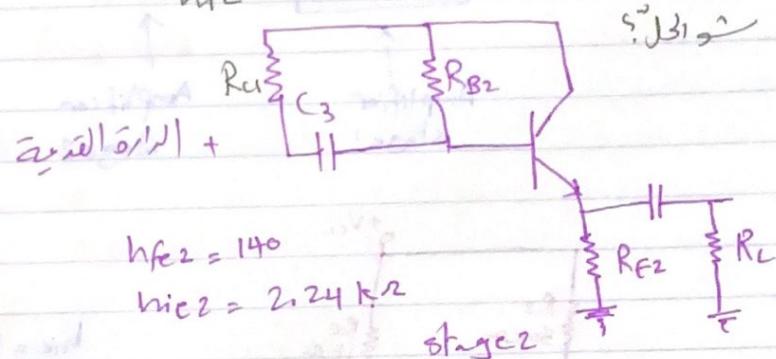2) with $R_L = 50\Omega$

$$V_o = -h_{FE} \cdot i_b (R_C // R_L)$$


$$A_v = \frac{-h_{FE}(R_C // R_L)}{h_{ie}} = -6.87$$



$$V_o = i_{e2} (R_L // R_E2)$$

$$i_{e2} = i_{b2} (h_{FE2} + 1)$$
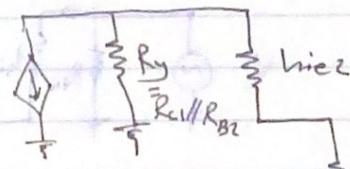
$$i_{b2} = -h_{FE1} \cdot i_{b1} \frac{R_y}{R_y + (h_{ie2} + (R_E2 // R_L)(h_{FE2} + 1))}$$



$$i_{b1} = \frac{V_i}{h_{ie1}} \quad \textcircled{1} \quad \textcircled{2} \quad \textcircled{4}$$

$$A_v = \frac{V_o}{i_{e2}} \cdot \frac{i_{e2}}{i_{b2}} \cdot \frac{i_{b2}}{i_{b1}} \cdot \frac{i_{b1}}{V_i} = -95.6$$

$CE + CC$
multistage Amplifier

← This is much
better than
without Buffer