

ENEE2360 Project1

Dear students

The report consists of the following parts:

Part1: Description of the circuit function and peration

Part2: Simulation

- a) Replace the lamp by a resistance between 100Ω and 10000Ω**
- b) Using Orcad , simulate the Circuit for three different values for the sensor resistor (the selected values of the resistance must cover the two states of the lamp.**
- c) Plot the waveform of the capacitor voltage and calculate the ripple factor for the three simulations**
- d) Indicate the settings of the center tapped transformer**
- e) Depending on the current through the lamp determine the state of the lamp (on or off) in the three simulations**

Part3 : Analysis

Circuit analysis for the same values of the resistances of the sensor in part2.(use V_{cc} obtained in part 2)

Part4 : Conclusion

The project is due to 24-4-2021