



Faculty of Information Technology

Electrical Engineering Department

ANALOG ELECTRONICS

ENEE 236\_Q1

- Name: Anas Nimer.
- ID#: 1180180.
- Instructor: Dr. Nasser Ismail.
- Section: 2.

## ❖ Table of Contents:

❖ Question1 .....	3
❖ The Work: .....	4
1. Half Wave rectifier: .....	4
2. Bridge Full Wave rectifier: .....	7
3. Center tapped Full Wave rectifier: .....	10
❖ Reference: .....	13

## ❖ Question1:

Design a rectifier with filter to provide a load ( $R_L=0.75 \text{ kohm}$ ) with an average voltage equal to 30 Vdc with a ripple factor = ~7%,  
Input voltage  $V_{in}$  is sinusoidal with 110Vrms,  $f=60 \text{ Hz}$ : assume practical diodes perform the design using all three rectifier types:


1. Half Wave rectifier
2. Bridge Full wave rectifier
3. Center tapped transformer full wave rectifier

Simulate the designed circuits using Pspice student edition


## ❖ The Work:
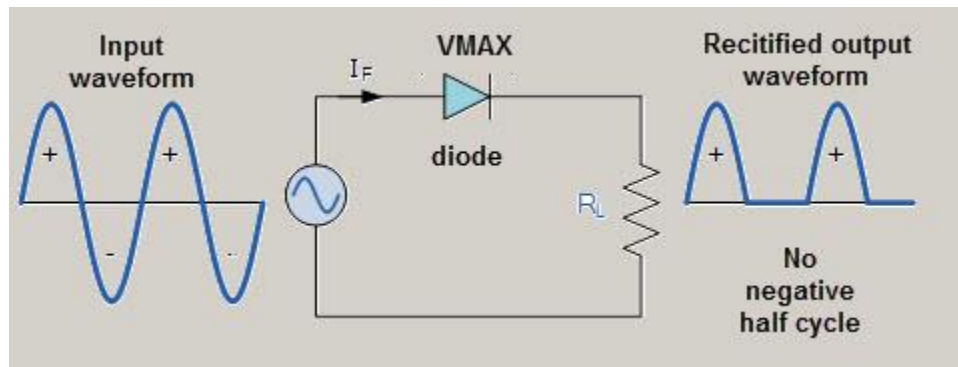
### 1. Half Wave rectifier:

In Half wave rectifier during the positive half cycle, the diode is under forwarding bias condition and it conducts current to  $R_L$  (Load resistance). A voltage is developed across the load, which is the same as the input AC signal of the positive half cycle [1].



Design →

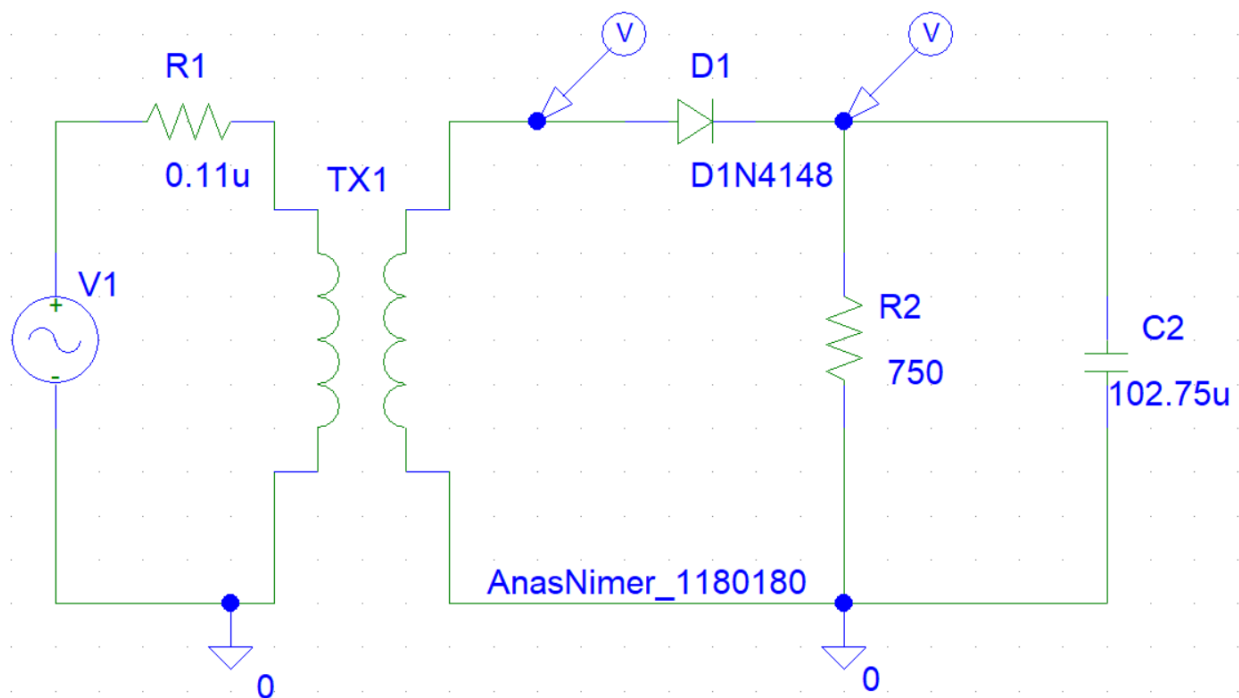

## The Solution →

Half Wave Rect:

\* Freq = 60 Hz

$$* r\% = \frac{V_{P-P}}{2\sqrt{3} * V_{dc}} * 100\% \Rightarrow V_{P-P} = (0.07) (2\sqrt{3}) (30) = 7.275 \text{ v}$$

$$* V_{dc} = V_m - \frac{V_{P-P}}{2} \Rightarrow V_m = 30 + \frac{1}{2} * 7.275 = 33.637 \text{ v}$$


$$* V_{ms} = V_m + 0.7 = 33.637 + 0.7 = 34.337 \text{ v}$$

$$* V_{P-P} = \frac{V_m}{fRC} \Rightarrow C = \frac{33.637}{7.275 * 60 * 750} = 102.75 \text{ } \mu\text{F}$$

$$* V_p = V_{rms} * \sqrt{2} = 110 * \sqrt{2} = 155.56 \text{ v}$$

$$* n = \frac{V_s}{V_p} = \frac{34.337}{155.56} = 0.2$$

## Simulate →

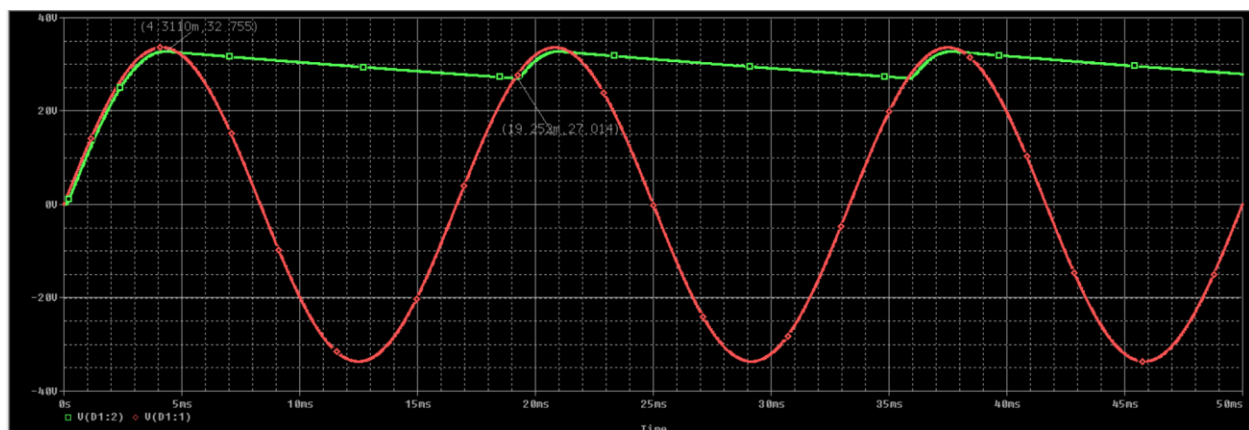

## The Solution →

$$\begin{aligned} * V_{p-p} &= y_{\max} - y_{\min} = 32.755 - 27.014 \\ &= 5.741 \text{ v} \end{aligned}$$

$$* V_{Rms} = \frac{V_{p-p}}{2\sqrt{3}} = \frac{5.741}{2\sqrt{3}} = 1.657 \text{ v}$$

$$\begin{aligned} * V_{dc} &= V_m = \frac{V_{p-p}}{2} = \frac{32.755 - 5.741}{2} \\ &= 29.88 \text{ v} \end{aligned}$$

$$* r\% = \frac{V_{rms}}{V_{dc}} \times 100\% = 5.546\%$$

\* we need to find  $L_1$  and  $L_2$

Suppose  $L_2 = 1 \text{ mH}$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}}$$

$$\frac{1}{n} = \sqrt{\frac{L_1}{L_2}}$$


$$\frac{1}{0.2} = \sqrt{\frac{L_1}{1}} \Rightarrow L_1 = 21.4 \text{ mH}$$

## 2. Bridge Full Wave rectifier:

A diode bridge is an arrangement of four (or more) diodes in a bridge circuit configuration that provides the same polarity of output for either polarity of input.

When used in its most common application, for conversion of an alternating-current (AC) input into a direct-current (DC) output, it is known as a bridge rectifier. A bridge rectifier provides full-wave rectification from a two-wire AC input [2].

Design →

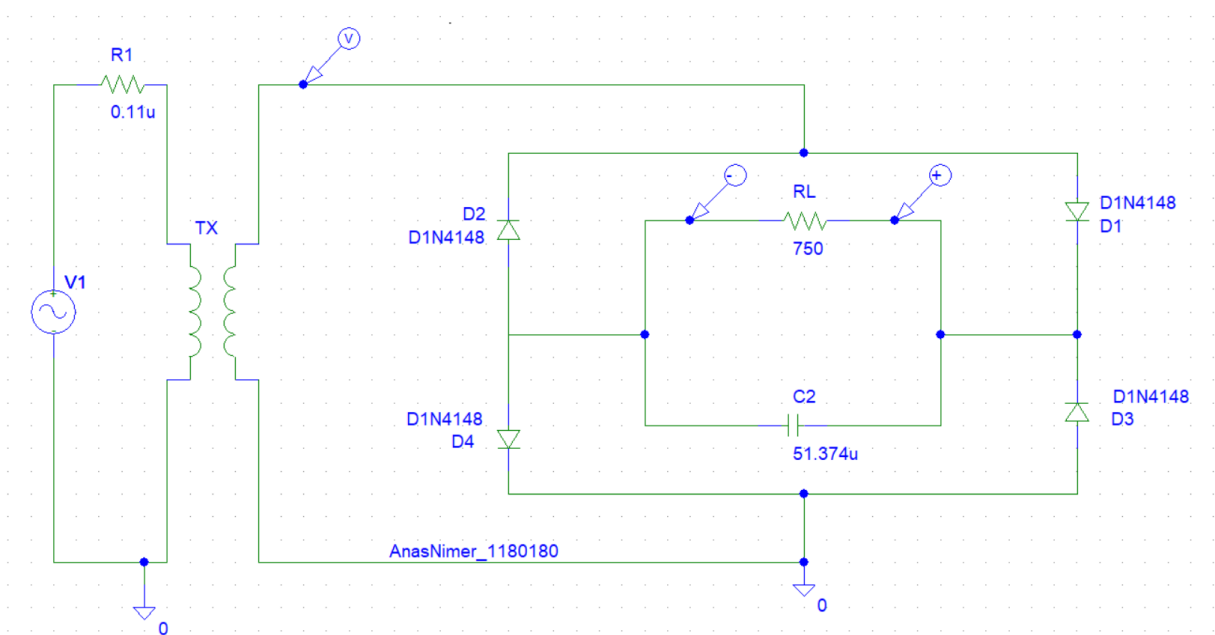


## The Solution →

Bridge Full-wave Rect:

- \*  $f_{\text{req}} = 60 \text{ Hz}$
- \*  $V_{p-p} = 7.275 \text{ V}$
- \*  $V_m = 33.637 \text{ V}$       \*  $V_{\text{ms}} = V_m + 1.4 = 33.637 + 1.4 = 35.037 \text{ V}$
- \*  $V_{p-p} = \frac{V_m}{2f_0RC} \Rightarrow C = \frac{V_m}{2f_0R(V_{p-p})} = \frac{33.637}{2 \times 60 \times 750 \times 7.275} = 51.374 \mu\text{F}$

## Simulate →

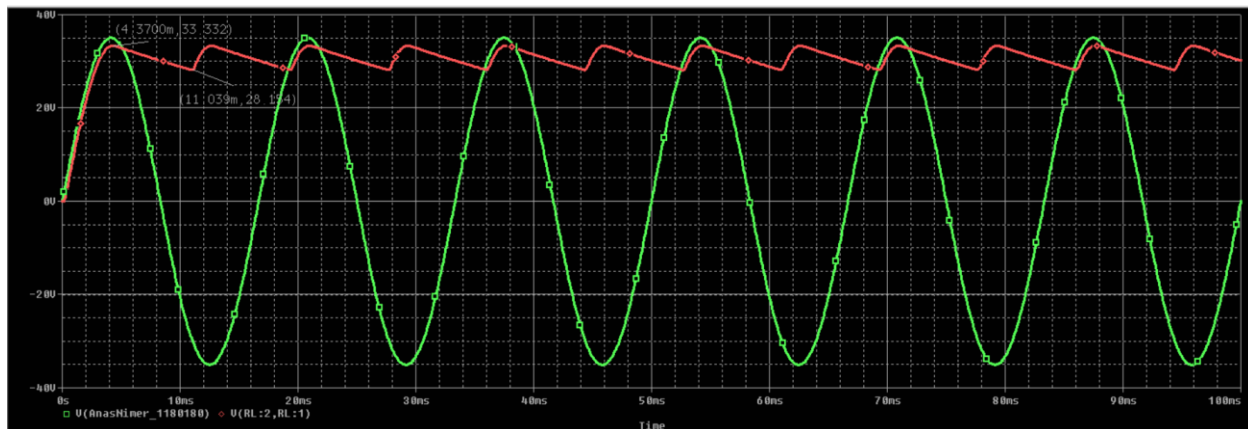



## The Solution →

$$\begin{aligned} * V_{p-p} &= y_{\max} - y_{\min} = 33.332 - 28.154 \\ &= 5.178 \text{ V} \end{aligned}$$

$$* V_{rms} = \frac{V_{p-p}}{2\sqrt{3}} = \frac{5.178}{2\sqrt{3}} = 1.495 \text{ V}$$

$$\begin{aligned} * V_{dc} &= V_m - \frac{V_{p-p}}{2} = 33.332 - \frac{5.178}{2} \\ &= 30.743 \text{ V} \end{aligned}$$

$$* r\% = \frac{V_{rms}}{V_{dc}} * 100\% = \frac{1.495}{30.743} * 100\% = 4.862\%$$

\* We need to find  $L_1$  and  $L_2$

\* suppose  $L_2 = 1 \text{ mH}$


$$\propto \frac{V_p}{V_s} = \sqrt{\frac{L_1}{L_2}}$$

$$\frac{155.56}{35.037} = \sqrt{\frac{L_1}{1}} \Rightarrow L_1 = 19.7 \text{ mH}$$

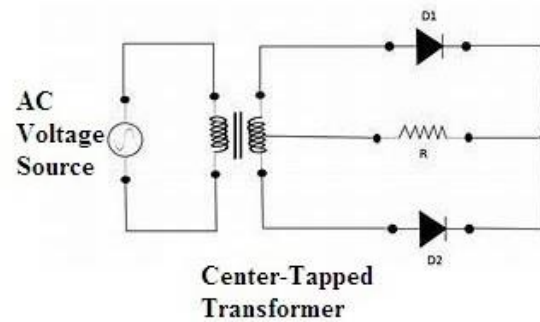
### 3. Center tapped Full Wave rectifier:

A rectifier that utilizes both the cycles during rectification is said to be a full wave rectifier. If the rectification is done by the usage of the center tapped transformer in the full wave. It is said to be a center tapped full wave rectifier [3].

A full wave rectifier based on center tap consists of two diodes in it as well as a center tapped transformer along with that a resistive load is connected across it [3].



#### Design →

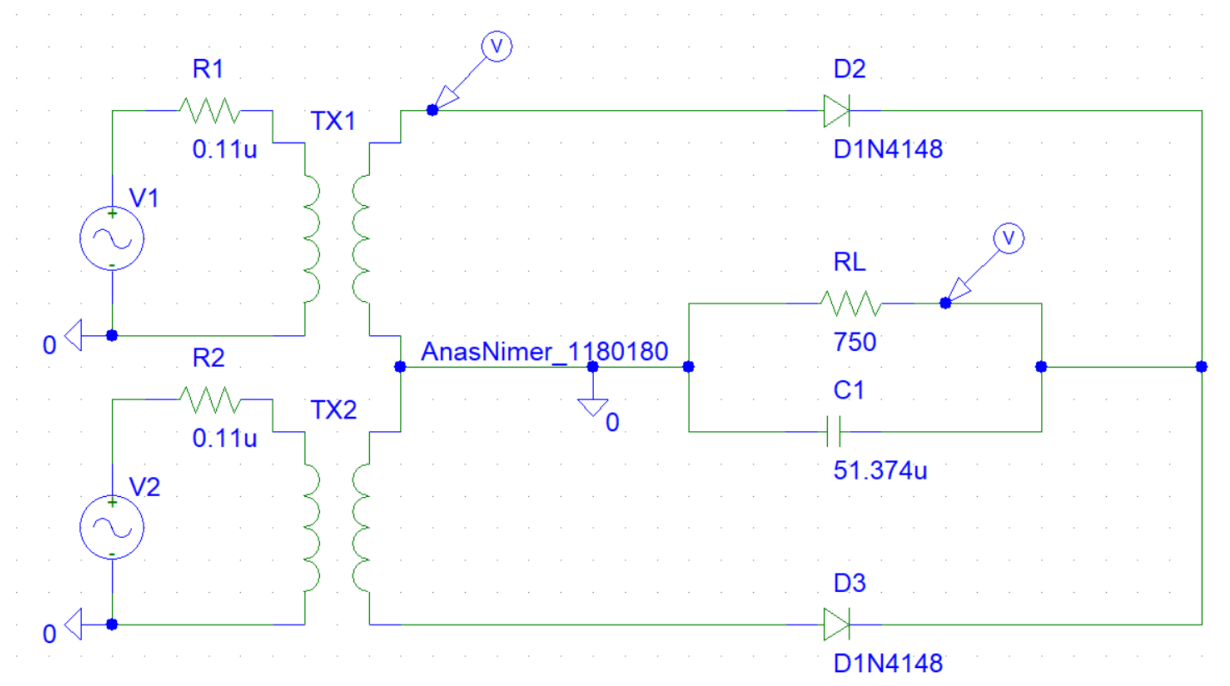

## The Solution →

Center tapped full wave rectifier;

\*  $f_{req} = 60 \text{ Hz}$


\*  $V_{p-p} = 7.275 \text{ V}$

\*  $V_m = 33.637 \text{ V}$

\*  $V_{ms} = 33.637 + 0.7 = 34.337 \text{ V}$

\*  $V_{p-p} = \frac{V_m}{2fRC} \rightarrow C = \frac{33.637}{2 \times 60 \times 750 \times 7.275} = 51.374 \text{ } \mu\text{F}$

## Simulate →

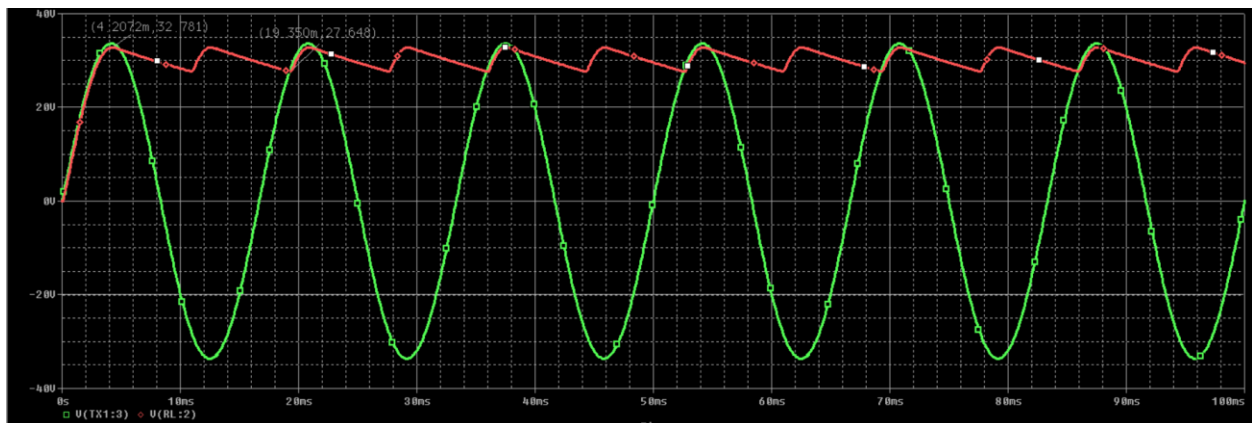

## The Solution →

$$\begin{aligned} \star V_{p-p} &= y_{\max} - y_{\min} \\ &= 32.781 - 27.640 \\ &= 5.141 \text{ v} \\ \star V_{rms} &= \frac{V_{p-p}}{2\sqrt{3}} = \frac{5.141}{2\sqrt{3}} = 1.484 \text{ v} \\ \star V_{dc} &= V_m = \frac{V_{p-p}}{2} = \frac{32.781}{2} = \frac{5.141}{2} \\ &= 30.21 \text{ v} \\ \star r\% &= \frac{V_{rms}}{V_{dc}} \times 100\% = \frac{1.484}{30.21} \times 100\% = 4.912\% \end{aligned}$$

## ❖ Reference:

- [1] : <https://www.elprocus.com/half-wave-rectifier-circuit-working-principle-and-characteristics-2/>.
- [2]: [https://en.wikipedia.org/wiki/Diode\\_bridge](https://en.wikipedia.org/wiki/Diode_bridge).
- [3]: <https://www.watelectronics.com/center-tapped-full-wave-rectifier-circuit-working-equations/>.