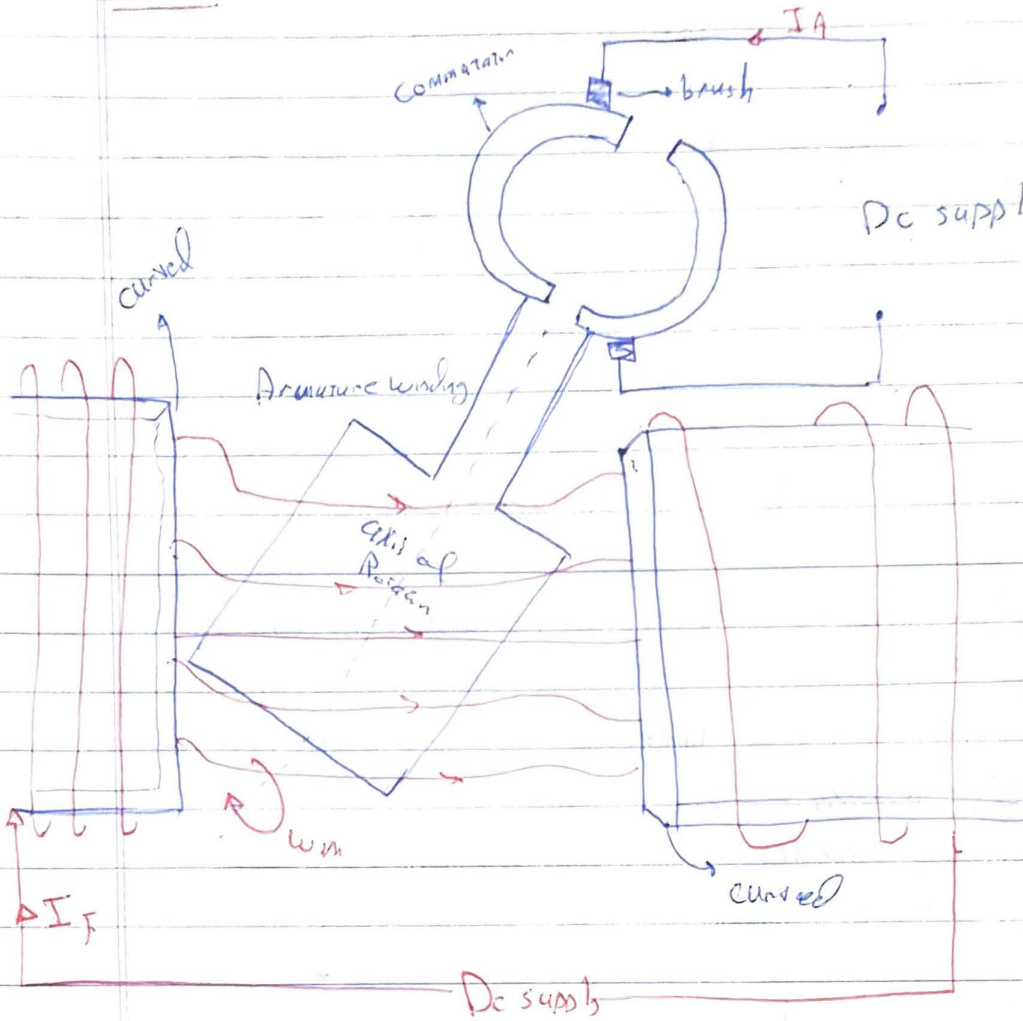


# CH2 Dc Motors & Generators



⊗ الرقبة طاب وانوار  
 هذه اكو حركات حركية  
 High Torque و  $\omega$

Armature → Rotor  
 Field → stator  
 $I_A$ : Armature current  
 $I_F$ : Field current

AC  $\otimes$

## ⊗ Operating principle of Dc machine (Motors Mode)

- ⊗ an electric current is supplied through the commutator & brushes
- ⊗ The current ( $I_A$ ) passes through the armature windings, in the presence of magnetic field, and produces a magnetic force ( $F_{ind} = I_a \vec{L} \times \vec{B}$ )
- ⊗ The magnetic force will produce a torque which is able to rotate the Dc motor. ( $T_{ind} = \vec{r} \times \vec{F}_{ind}$ )

## ⊗ Types of Dc motors


(parallel)

- ① Separately excited Dc motors
- ② shunt Dc motor
- ③ series Dc motor
- ④ compound Dc motors
- ⑤ permanent magnet Dc motor

• low power efficiency, Dc Motor  $\otimes$

• Drive is easier than Ac induction motor

# General equivalent circuit

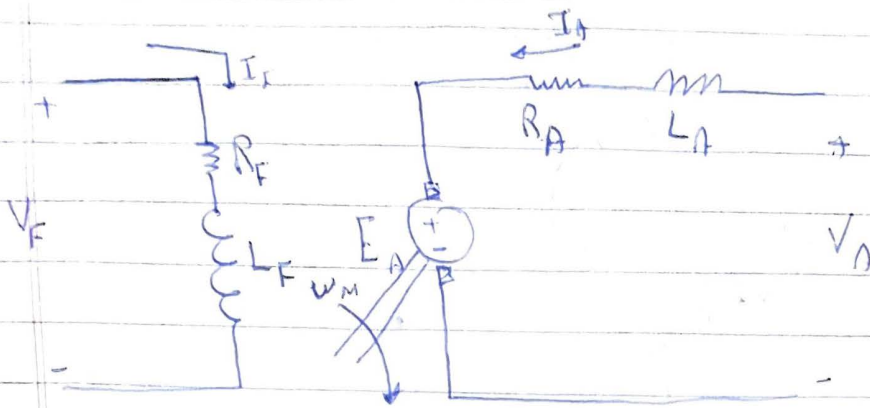

Field circuit

Armature circuit.

$R_F, L_F$   $\Rightarrow$  Resistance and inductance of field winding.

$R_A, L_A$   $\Rightarrow$  Resistance and inductance of armature winding.

$E_A$   $\Rightarrow$  Internal voltage or induced or back EMF voltage.

$$E_A = K \phi \omega_m$$



$I_A$   $\Rightarrow$  Armature current

$I_F$   $\Rightarrow$  Field current

$$\phi = C I_F$$

$$E_A = K \phi \omega_m, \text{ when } \omega_m \text{ IS CONSTANT}$$


$$E_A = K' \phi$$

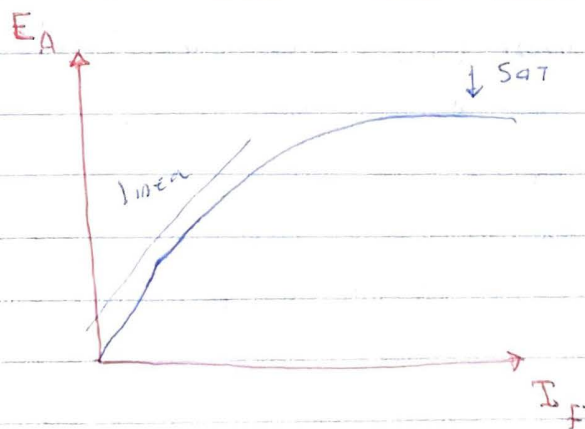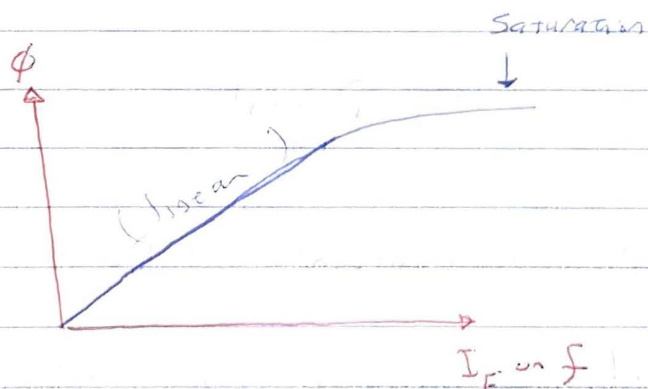

$V_A$   $\Rightarrow$  Armature voltage

$V_F$   $\Rightarrow$  Field voltage
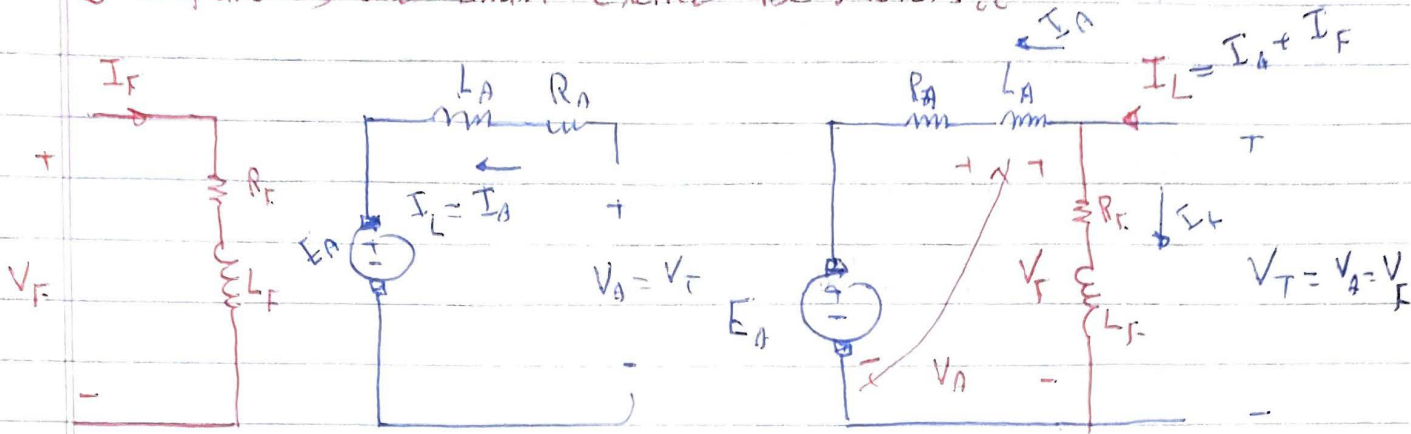
# ① Separately and shunt excited DC Motors etc



Separately excited

Shunt excited

$V_T$  : Terminal or motor voltage

$I_L$  : Motor or line current

## ⊗ equation of DC machine "separately & shunt excitation"

KVL in the armature circuit

- $V_T = R_A I_A + L_A \frac{dI_A}{dt} + E_A$

- Back emf voltage

$$E_A = K \phi \omega_m$$

- Induced Torque

$$T_{ind} = K \phi I_A$$

- Newton second law

$$T_{ind} - T_{Load} = J \frac{d\omega_m}{dt} + B \omega_m$$

Friction factor

## ⊗ Torque speed characteristics

under steady state condition, the motor voltage is given by

$$V_T = R_A I_A + L_A \frac{dI_A}{dt} + E_A$$

$$V_T = R_A I_A + E_A = R_A I_A + K\phi\omega_m, \text{ solve for } I_A$$

$$I_A = \frac{V_T - K\phi\omega_m}{R_A}$$

$$T_{ind} = K\phi I_A = K\phi \left( \frac{V_T - K\phi\omega_m}{R_A} \right)$$


$$T_{ind} = \frac{K\phi}{R_A} (V_T - K\phi\omega_m)$$

$$\frac{R_A}{K\phi} T_{ind} = V_T - K\phi\omega_m \Rightarrow \frac{R_A}{(K\phi)^2} T_{ind} = \frac{V_T}{K\phi} - \omega_m$$

$$\omega_m = \frac{V_T}{K\phi} - \frac{R_A}{(K\phi)^2} T_{ind}$$

No Load  
speed

shunt  
separately

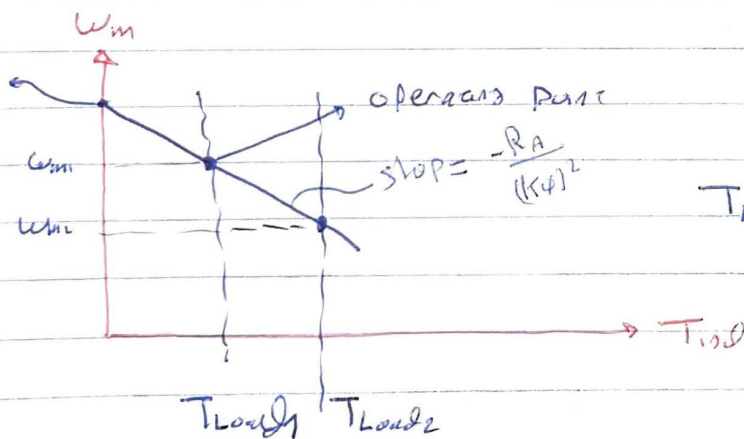

$$T_{Load2} > T_{Load1} \Rightarrow \omega_m < \omega_{m1}$$

$\leftarrow \omega_{m, No Load}$

$$\omega_{m, I_A=0} = \frac{V_T}{K\phi}$$

$$\text{OR } V_T = E_A$$



$$T_{load} \uparrow \Rightarrow \omega_m \downarrow \Rightarrow (E_A = K\phi\omega_m \downarrow)$$

$$\Rightarrow \left( I_A = \frac{V_T - E_A \downarrow}{R_A} \right) \uparrow \Rightarrow (T_{ind} = K\phi I_A) \uparrow \text{ until equals } T_{Load}$$

$T_{ind} \downarrow$   
 $\downarrow$   
 $T_{Load}$


# Method to control the speed

## ① Adjusting The Field resistor &

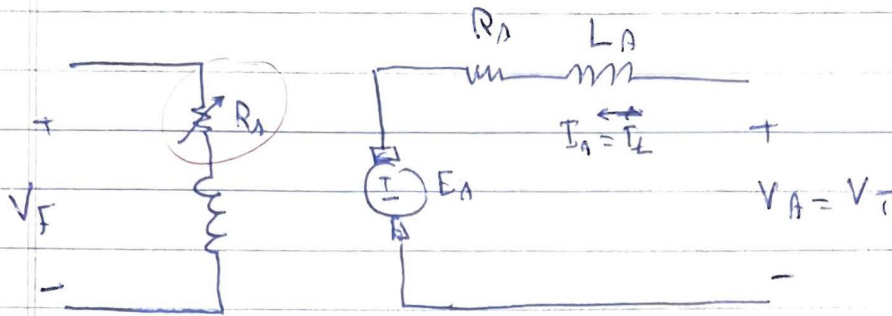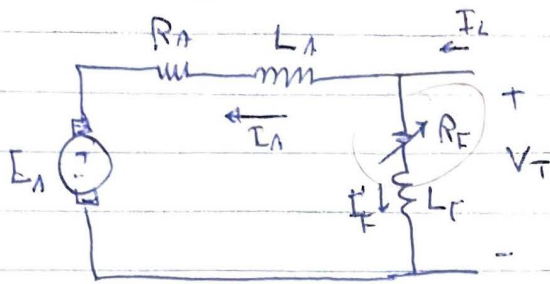


$$R_A \uparrow \Rightarrow I_F \downarrow \Rightarrow \phi \downarrow$$

$$I_F = c\phi$$

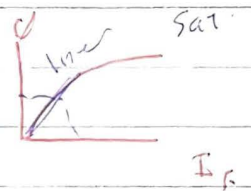
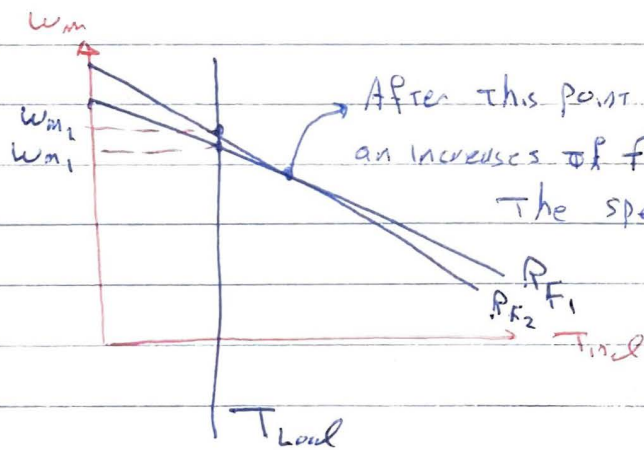
$$\omega_m = \frac{V_T}{K\phi} - \frac{R_A}{K\phi^2} T_{ind}$$




because  $\frac{-1}{(K\phi)^2}$  slope decrease more.

After this point an increase of  $R_F$  decreases and No load  $\omega$  increased The speed

بعد هذه النقطة زيادة المقاومة الحثية تقل السرعة عند الحمل الثابت وتزيد السرعة عند الحمل الخفيف

$$R_{F2} > R_{F1} \Rightarrow \omega_{m2} > \omega_{m1} \text{ (Field weakening)}$$

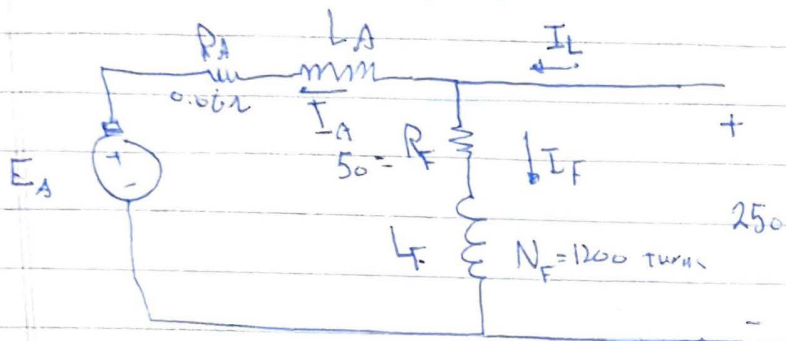Example A 50 hp, 250 V, 1200 rpm DC shunt motor has armature resistance of 0.06 Ω. Its field circuit has a total resistance of 50 Ω which produces a no-load speed of 1200 rpm. There are 1200 turns per pole on the shunt field winding.



a) Find the speed of this motor when its field input current is 100 A?

مؤلف  
 لا تغير  $V_L$   
 لا تغير  $I_A$   
 لا تغير  $E_A = V_T$

$$V_L = R_A I_A + E_A$$

$$I_A = I_L - I_F \rightarrow I_A = 100 - \frac{250}{50} = 95 \text{ A}$$

$$E_A = 250 - 0.06(95) = 244.3 \text{ V}$$

$$E_A = 250 \text{ V (at No Load)}$$

$$E_A = K \phi \omega_m$$

$$250 = K \phi (1200)$$

$$244.3 = (K \phi) (\omega_m')$$

$\phi$  is not changed since  $V = 250$   
 constant of field circuit

$$\boxed{\omega_m' = 1173}$$

b) Find the speed of this motor when its input current is 300 A?

$$V_L = R_A I_A + E_A$$

$$250 = (0.06)(I_A) + E_A$$

$$\boxed{I_A = 295 \text{ A}}$$

$$\boxed{E_A = 232.3}$$

$$E_A = K \phi \omega_m \Rightarrow 250 = (K \phi) (1200) \rightarrow$$

$$232.3 = K \phi \omega_m' \Rightarrow \boxed{\omega_m' = 1115 \text{ RPM}}$$

separately excited

## Converted power in shunt Dc motors

$$V_L = R_A I_A + E_A \quad , \text{ Multiplies the eq by } I_A$$



$$V_L I_A = R_A I_A^2 + E_A I_A$$

$\underbrace{\hspace{10em}}_{\text{input power}} \quad \underbrace{\hspace{5em}}_{\text{Copper losses in } R_A} \quad \underbrace{\hspace{5em}}_{\text{Converted power}}$


$$P_{\text{conv}} = E_A I_A = T_{\text{ind}} \omega_m \Rightarrow T_{\text{ind}} = \frac{P_{\text{conv}}}{\omega_m}$$
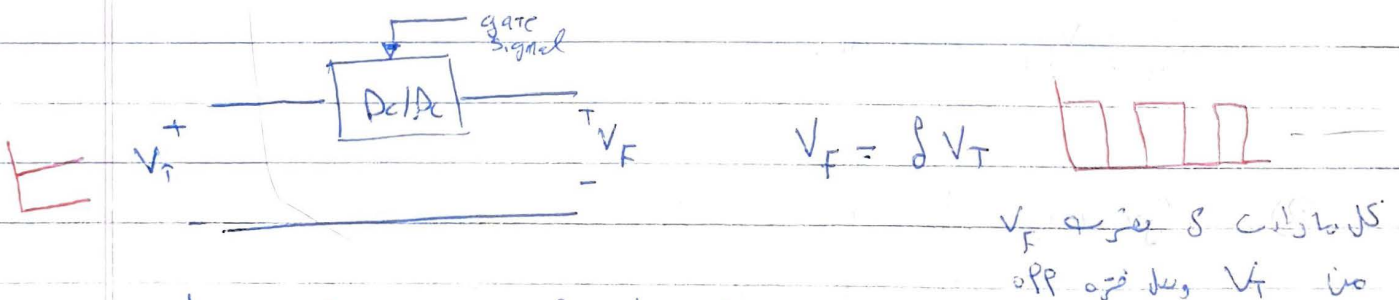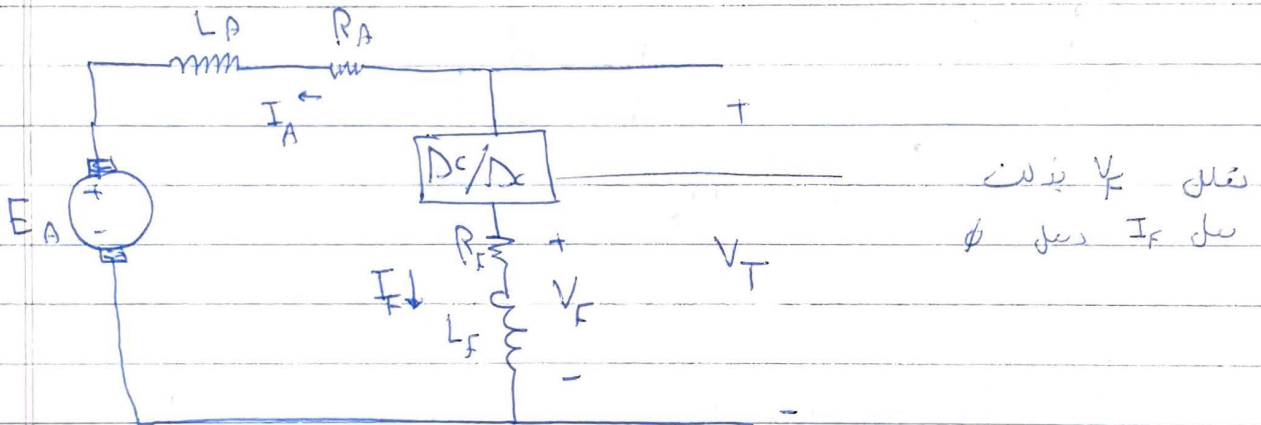
### ⊕ Method to control the speed (Repear)

- ① adjusting the field resision or adjust the field voltage.




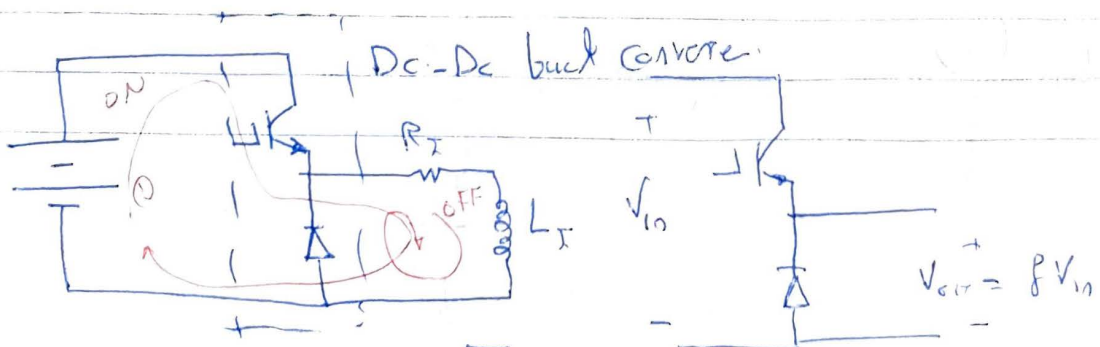where f is called the duty cycle 0.5, 0.8, 1




$$V_F \downarrow \Rightarrow (I_F = \frac{V_F}{R_F}) \downarrow \Rightarrow (\phi = CI_F) \downarrow \Rightarrow \omega \uparrow$$

① adjusting the field Resistance

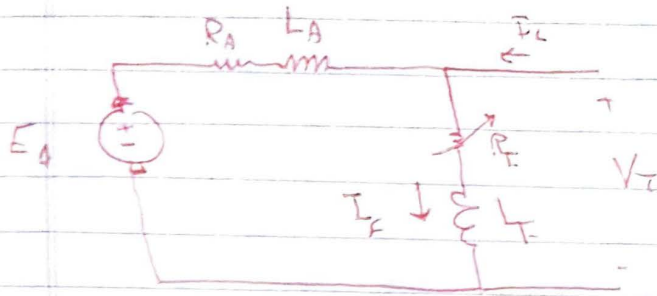

$$R_F \uparrow \Rightarrow (I_F = \frac{V_F}{R_F}) \downarrow \Rightarrow (\phi = CI_F) \downarrow$$

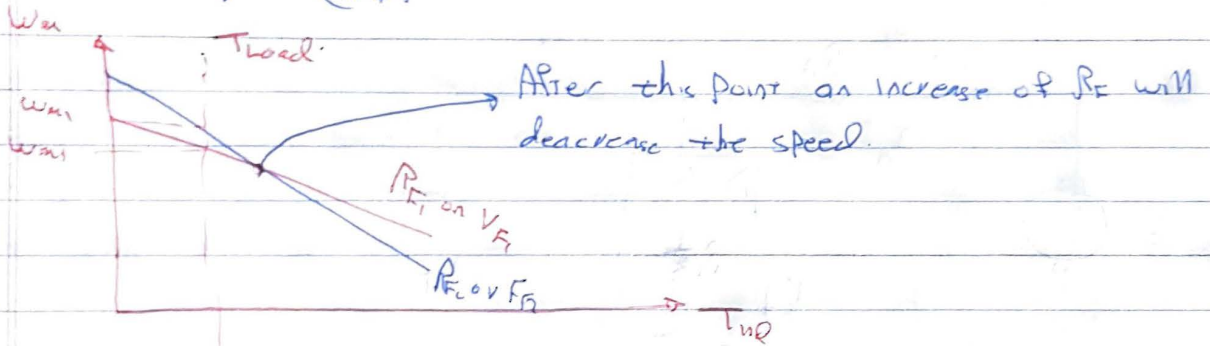
$$\omega_m = \frac{V_T}{K\phi} - \frac{R_A}{K\phi^2} T_{ind}$$



$$R_{F1} < R_{F2} \Rightarrow \omega_{m1} > \omega_{m2}$$

$$V_{F1} > V_{F2} \Rightarrow \omega_{m1} > \omega_{m2}$$

② adjusting the armature voltage.

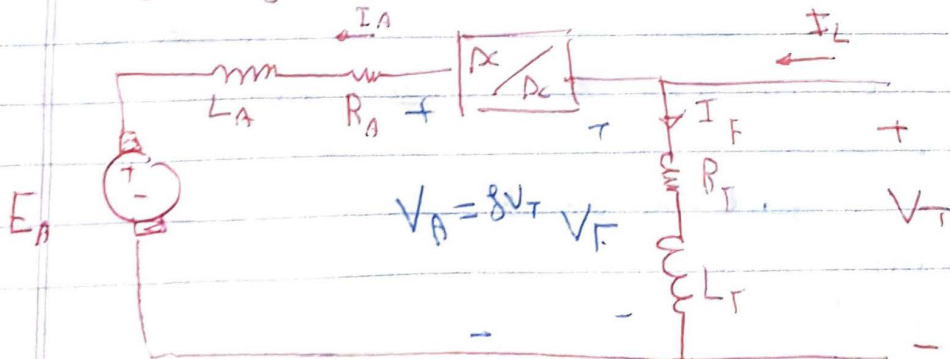


$$V_A = \delta V_T$$

|P|

,  $\delta$  is the duty cycle


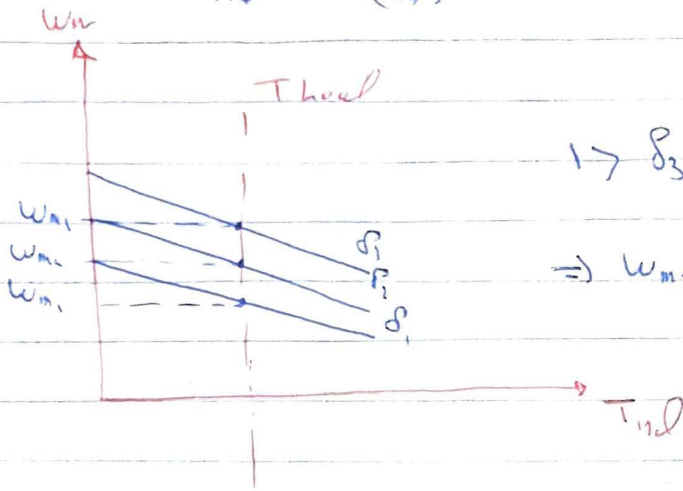
$$\omega_m = \frac{s V_T}{K\phi} - \frac{R_A}{(K\phi)^2} \cdot T_{ind}$$



$$\Rightarrow \phi_3 > \phi_2 > \phi_1 > 0$$

$$\Rightarrow \omega_{m3} > \omega_{m2} > \omega_{m1}$$

Note  $V_A = R_A I_A + E_A = R_A I_A + K\phi \omega_m$

في كل Voltage الجهد في كل  $\phi$   $\otimes$   
 Full استيعاب Rated volt في  
 عند الارتفاع في السرعة

$$V_A = R_A I_A + K\phi \omega_m$$

$\phi = \phi_r$  [ when  $\omega_m \leq \omega_{m,r}$  where  $\omega_{m,r}$  is the rated speed  
 $\Rightarrow$  Armature control is used  $\Rightarrow V_A$  increase with  $\omega_m$  (linearly)

when  $\omega_m > \omega_{m,r} \Rightarrow$  Field control is used

$$V_A = V_{A,r} = \text{rated motor voltage}$$

$$\Rightarrow \phi \propto \frac{1}{\omega_m} \text{ "Field weakening"}$$

②  $T_{ind} = K\phi I_A$

$$P_{conv} = T_{ind} \omega_m$$

$\phi$  في هذا Rated speed  $\otimes$

$\phi = \frac{c}{\omega}$   $\Rightarrow$   $V_A$   $\Rightarrow$   $V_A = R_A I_A + K\phi \omega$

constant  $\Rightarrow V_A = R_A I_A + K\phi \omega$

$\omega_m \leq \omega_{m,r} \Rightarrow \phi = \phi_r \Rightarrow T_{ind} = \text{constant}$


$\omega_m > \omega_{m,r} \Rightarrow \phi = \phi_r \frac{\omega_{m,r}}{\omega_m} \Rightarrow T_{ind} = K\phi_r \frac{\omega_{m,r}}{\omega_m}$

$$P_{conv} = \text{constant}$$

$$\text{constant} = P = K\phi_r \frac{\omega_{m,r}}{\omega_m} \cdot \omega_m$$


$$P = T_{ind} \omega_m$$

$$T_{ind} = K\phi \omega_m$$

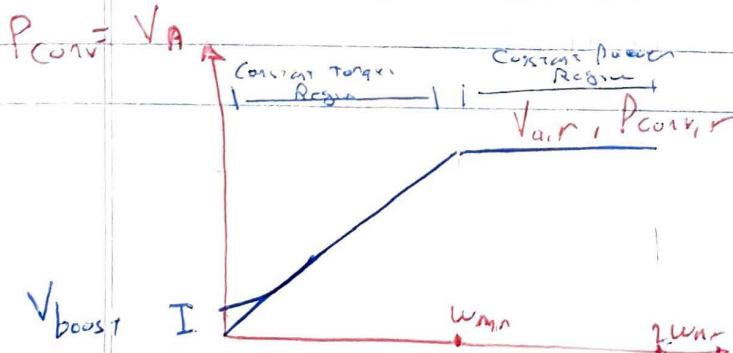


$$P \Rightarrow T_{ind} = K\phi \omega_m \leq \text{const}$$


$$P = \text{constant} \cdot \omega_m$$

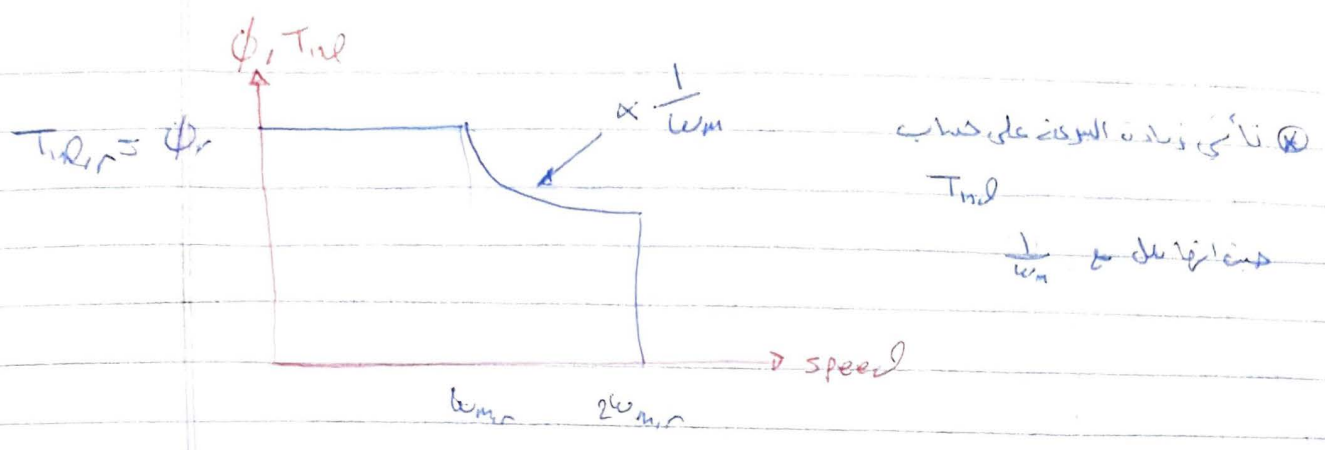

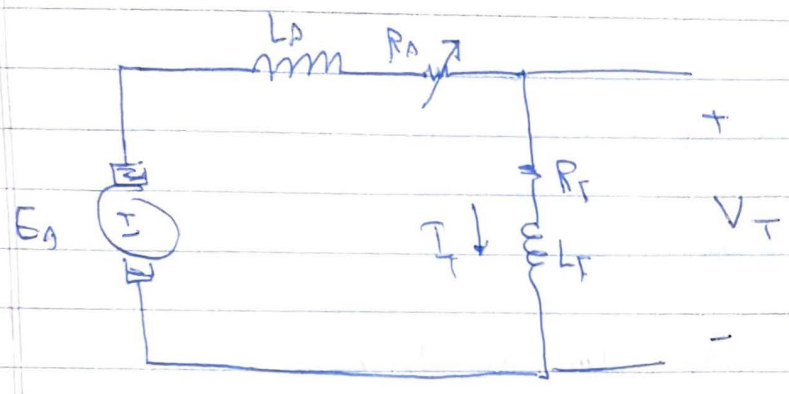③ Inserting a resistor to the armature circuit.


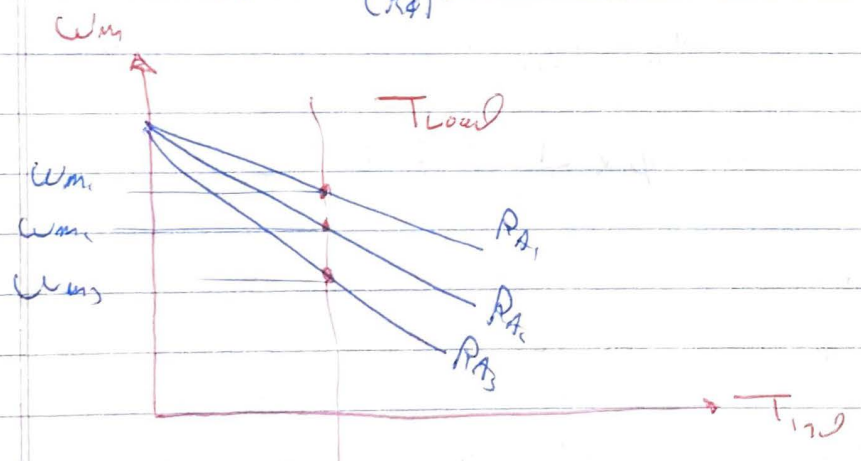
$$\omega_m = \frac{V_T}{k\phi} - \frac{R_a}{k\phi} \cdot T_{ind}$$



$$R_{a1} > R_{a2} > R_{a3} \Rightarrow \omega_{m3} < \omega_{m2} < \omega_{m1}$$

$\Rightarrow$  This method is inefficient because the power losses are very large  $\Rightarrow$  its rarely used.


Note: The direction of shunt on separately excited Dc motor is reversed by switching the terminals of armature or field windings

$$T_{ind} = k \phi I_A$$


$$\phi = k_f I_F$$

$$T_{ind} = k_c I_F I_A$$


∴ Indirectly proportional to  $I_F$

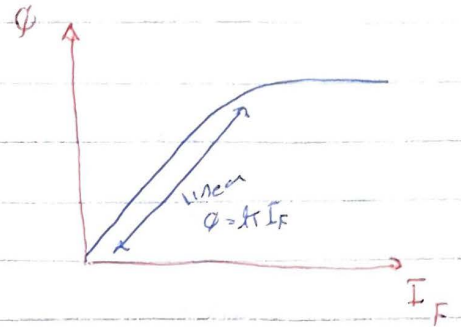


Shunt

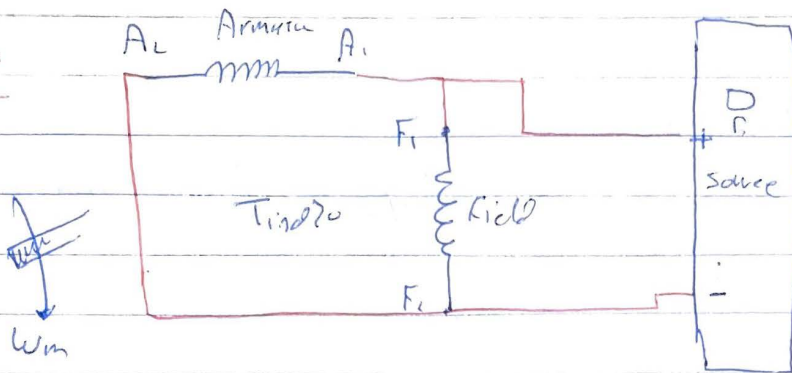

How?

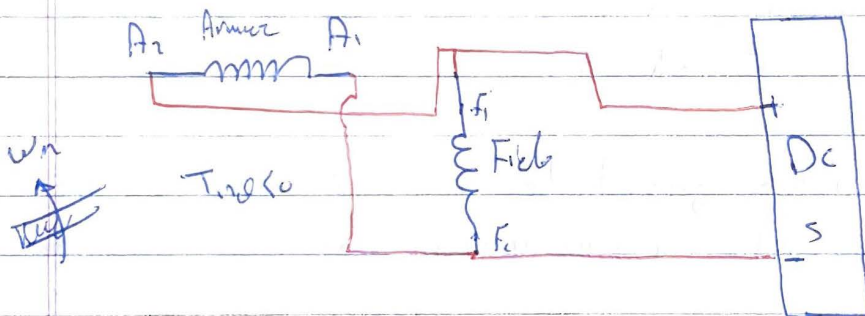


OR

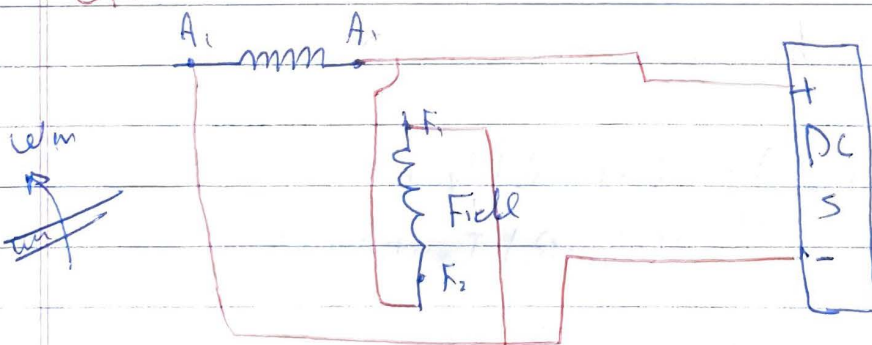


② SCA:
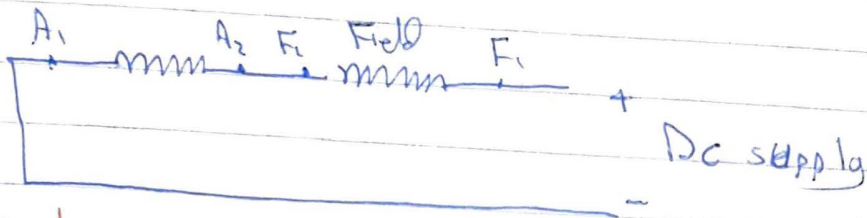
## ② Series DC motor

The field winding is connected in series with the armature coil,



equivalent circuit is

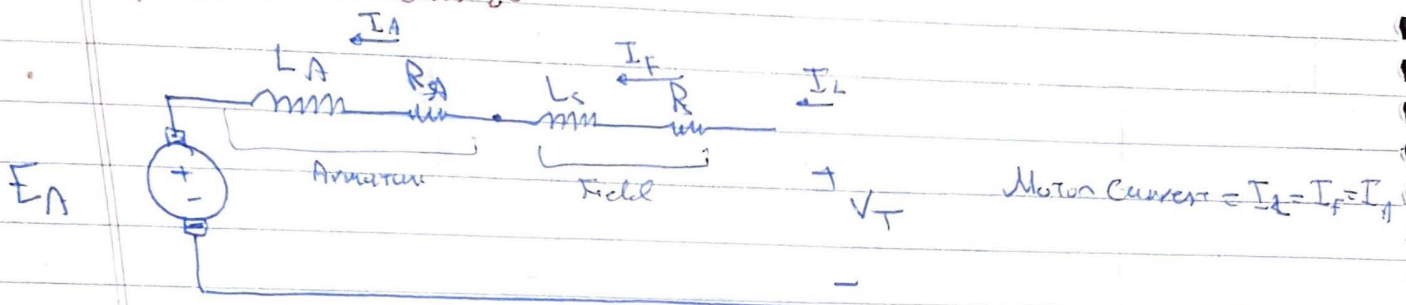

Induced Torque:  $T_{ind} = k\phi I_A$

$$T_{ind} = k_c I_F I_A \rightarrow I_F = I_A$$

$$T_{ind} = k_c I_A^2 \rightarrow T_{ind} \propto I_A^2$$

The series DC motor gives higher torque / Ampere ratio than other DC motor. It is usually used in applications requiring high torques.

Torque speed characteristics of series DC motor?

$$\text{Kvl in the loop } V_T = (R_A + R_S) I_A + E_A \rightarrow E_A = k\phi \omega_m$$

$$V_T = (R_A + R_S) I_A + k\phi \omega_m$$

$$\phi = c I_F, \quad I_F = I_A$$

$$V_T = (R_A + R_S) I_A + k_c I_A \omega_m \quad \text{--- (1)}$$

$$T_{ind} = k_c I_A^2$$

$$\Rightarrow I_A = \frac{T_{ind}}{\sqrt{k_c}} \cdot \sqrt{T_{ind}} \quad \text{--- (2)}$$

$$\textcircled{1}, \textcircled{2} \quad V_T = (R_A + R_S) \frac{I}{\sqrt{K_c}} \sqrt{T_{ind}} + \frac{K_c}{\sqrt{K_c}} \sqrt{T_{ind}} \omega_m$$

$$\frac{V_T}{\sqrt{T_{ind}}} = \frac{R_A + R_S}{\sqrt{K_c}} + \sqrt{K_c} \omega_m$$

$$\omega_m = \frac{V_T}{\sqrt{K_c}} \cdot \frac{1}{\sqrt{T_{ind}}} - \frac{(R_A + R_S)}{K_c}$$

Starting Torque


$$T_{start} = T_{ind} \Big|_{\omega=0} \Rightarrow 0 = \frac{V_T}{\sqrt{K_c}} \cdot \frac{1}{\sqrt{T_{ind}}} - \frac{(R_A + R_S)}{K_c}$$

After solving it  $\Rightarrow$   $T_{start} = \left( \frac{V_T}{R_A + R_S} \right)^2 K_c$

OR by  $E_A = K_c \omega_m = 0$  At starting

$$T = K_c I_A^2, \quad I_A = \frac{V_T - E_A}{R_A + R_S}$$
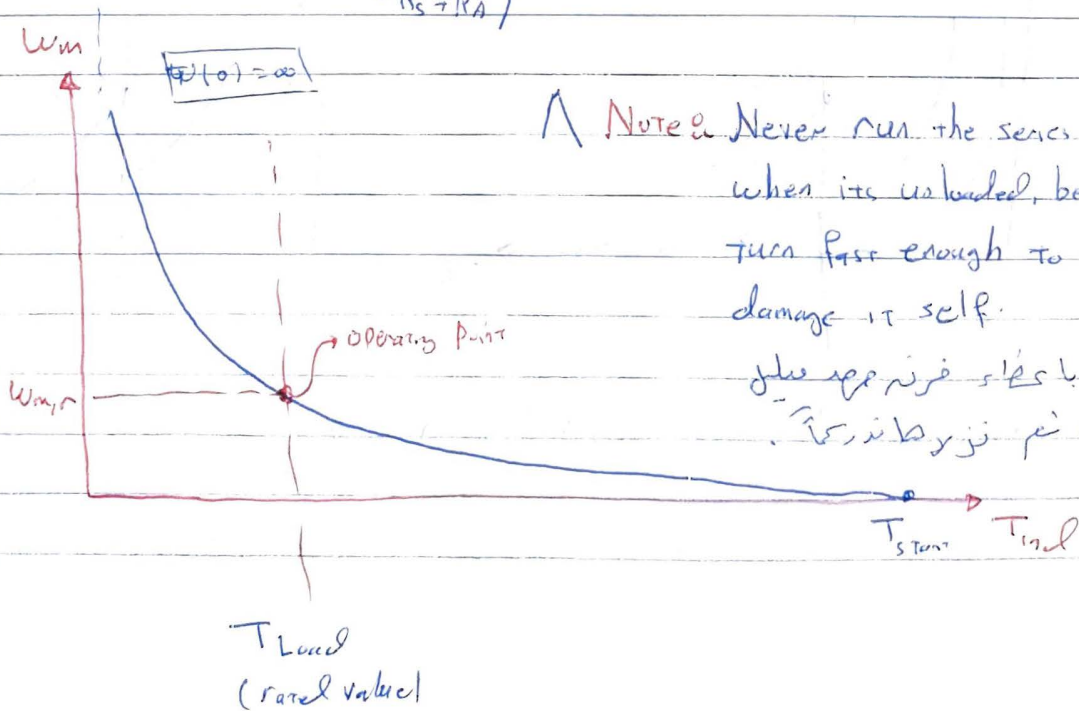
$$\omega T_{start} = K_c \left( \frac{V_T}{R_S + R_A} \right)^2$$




NOTE: Never run the series DC motor when its unloaded, because it may turn fast enough to seriously damage it self.

جس سلسلے میں سٹیٹس کے لیے  
 یہ سلسلے میں سٹیٹس کے لیے

⊗ Method to control the speed of

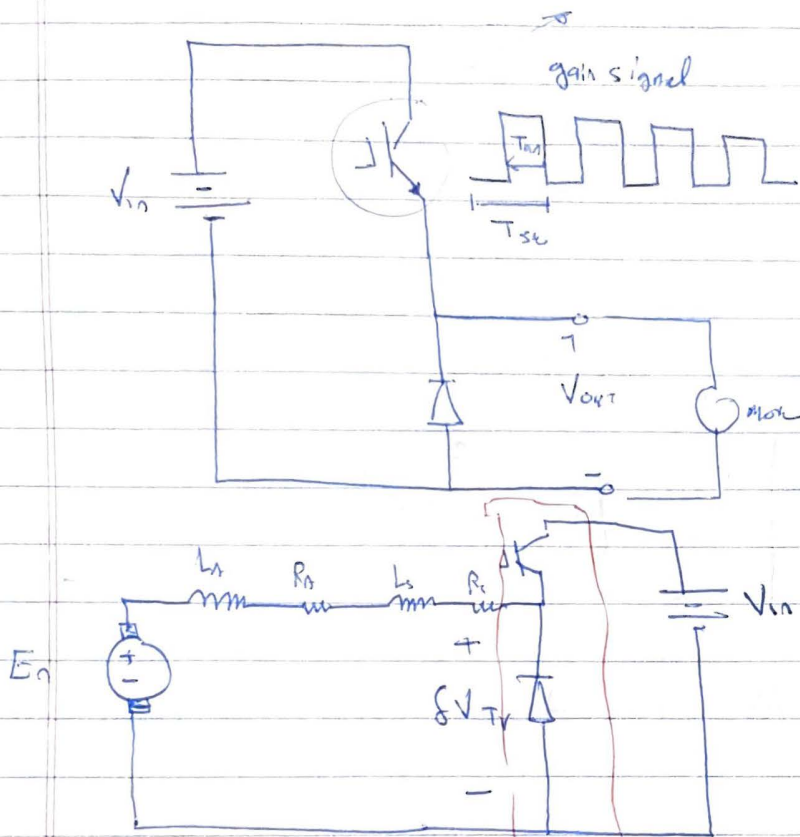1) Adjust the motor voltage using Dc/Dc buck converter (chopper circuit)


یعنی اس کے ذریعے High speed لیا جاسکتا ہے



$$V_{out} = \delta V_{in}$$

$$\delta = \frac{T_{on}}{T_{sw}}$$


DC-DC Converter

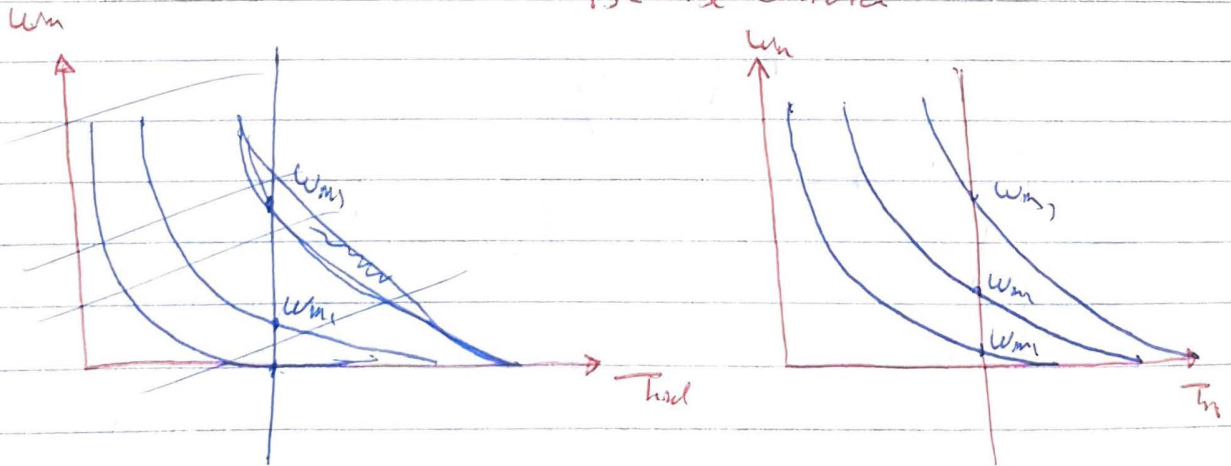

$$V_1 < V_2 < V_3, \quad \omega_{m1} < \omega_{m2} < \omega_{m3}$$

⊗ ادا بدي انزل في voltage بول في الفکر صحیح

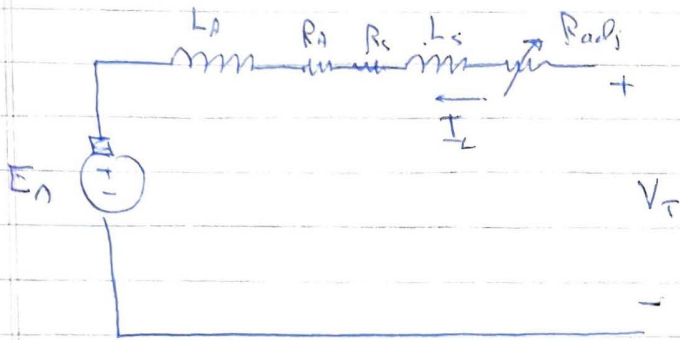
2) Adding a resistor in series with the field & armature windings.



$R_{adj} \uparrow \Rightarrow \omega_m \downarrow \Rightarrow$  This method is inefficient because the power losses are very large  $\rightarrow$  its rarely used.

Note: This method is usually used for starting up the DC motor.



### ③ Compound DC Motors

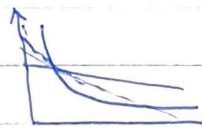

It consists of 3 windings:

- 1) Armature winding.
- 2) Series field winding.
- 3) shunt field winding.

unloaded  $I_A = 0$

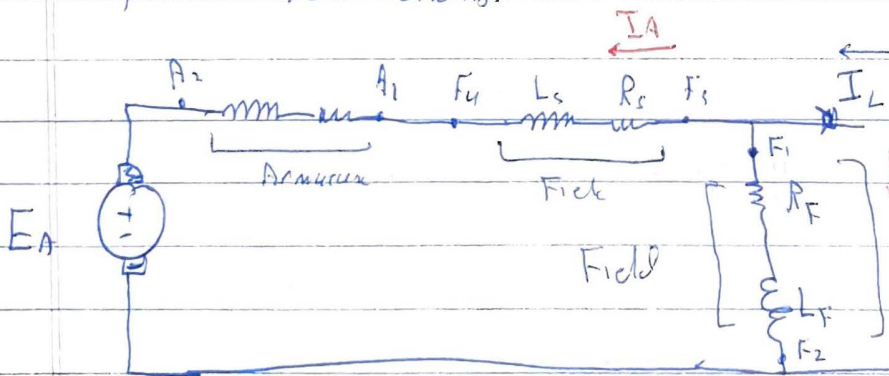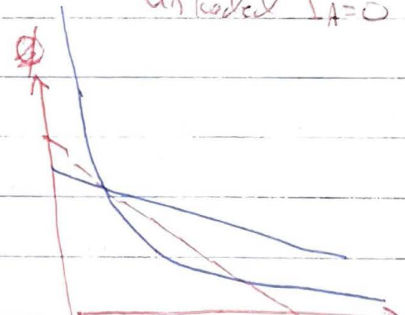

Compound flux  $\Phi$   
 $\omega_s \propto I_A \propto I_F$   
 $I_F \propto I_A$   
 $\omega_s \propto I_A$

عوض  
 الموصل  
 بوس  
 د

The net mmf is giving by  $F_{net} = F_F + F_s$

$$F_{net} = N_F I_F + N_s I_A = N_F I_F^*$$


$I_F^*$  : effective field current

$$I_F^* = I_F + \left( \frac{N_s}{N_F} \cdot I_A \right)$$

$0 = I_A$  No load | j |

$$I_F^* = I_F$$


15

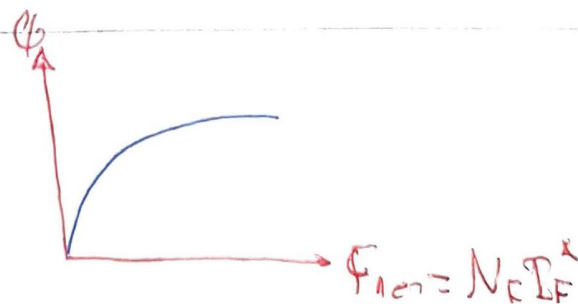

⊗ Its combines the best features of both series and shunt DC motors

Series DC motors → high Torque

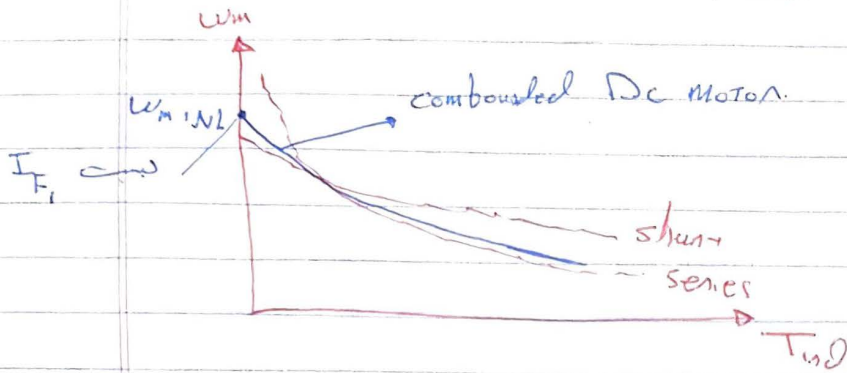Shunt DC motors → it doesn't overspeed when its unloaded.




⊕ Methods, to control the speed?

- 1) changing the terminal voltage (Buck converter)
  - 2) changing the field <sup>shunt</sup> resistor
  - 3) changing the field series resistor
- } Power losses ↑

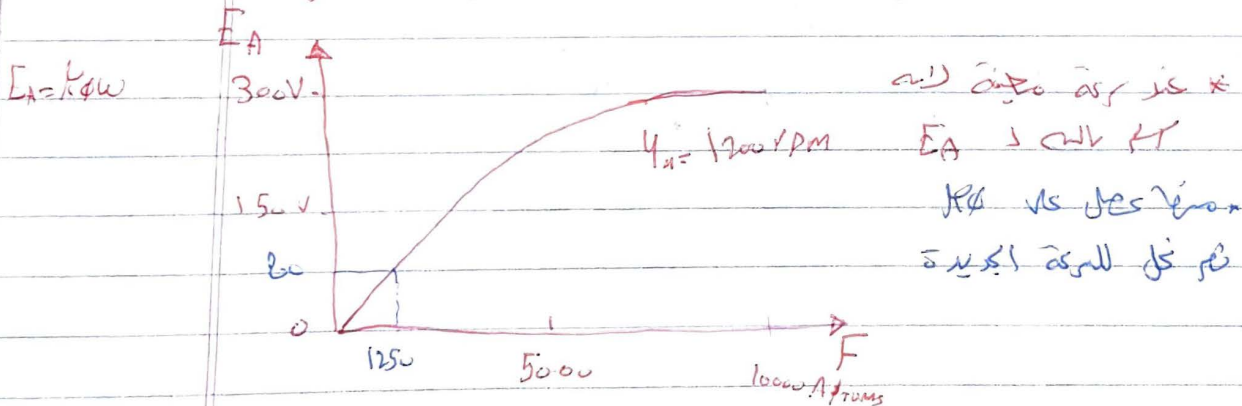
Example

A 250V series DC motor has a total series resistance of 0.02Ω. The series field consists of 25 turns per-pole, with the magnetizing curve shown in Figure



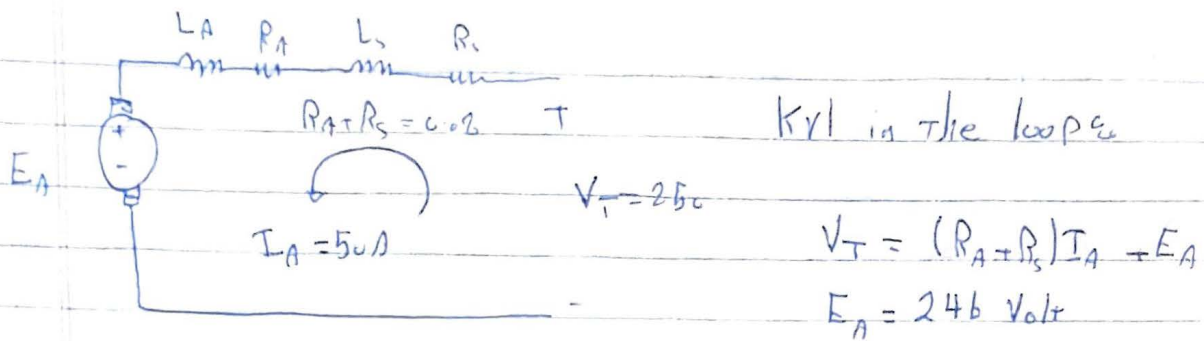⊕ Find the speed & induced Torque when the motor current is 50 A?





$$E_A = K \phi \omega_m$$

$$F = \frac{N_s I_A}{F} = N_s I_A = (25)(50) = 1250 \text{ A.turn}$$

From magnetizing curve  $\Rightarrow E_{A0} = 250 \text{ V} = K \phi \left( \frac{1250}{30} \right)$

$$K \phi = \frac{246}{6369} \Rightarrow \omega_m = 3696 \frac{\pi}{30} \text{ rad/sec}$$

$$\omega_m = 3690 \text{ rpm}$$

$$T_{ind} = K \phi I_A$$

or  $P_{conv} = T_{ind} \omega_m = E_A I_A \Rightarrow T_{ind} = 31.8 \text{ N.m}$

## Control circuit in DC motors

### ⊗ Function of control circuits

- ① Protection against short circuit (Fuses)
- ② Protection against overloading (OL heater)
- ③ Protection against high starting current
- ④ Speed control

## Starting problems in DC motors

The armature current of the DC motor is given by  $(K \phi / \omega_m)$

$$I_A = \frac{V_T - E_A}{R_A} \quad \text{"separately or shunt excited"}$$

At starting  $\Rightarrow \omega_m = 0 \Rightarrow E_A = K\phi\omega_m = 0 \Rightarrow I_{A, \text{start}} = \frac{V_T}{R_A}$


ممكن

EA من 0 الى  
التيه  
R في 0 الى  
من اليمين  
التيه  
E0

$$R_A = (3\% - 6\%) (P) \Rightarrow I_{A, \text{start}} \approx (20-30) I_{A, \text{rated}}$$

STARTERS of DC MOTORS

① Manual starter

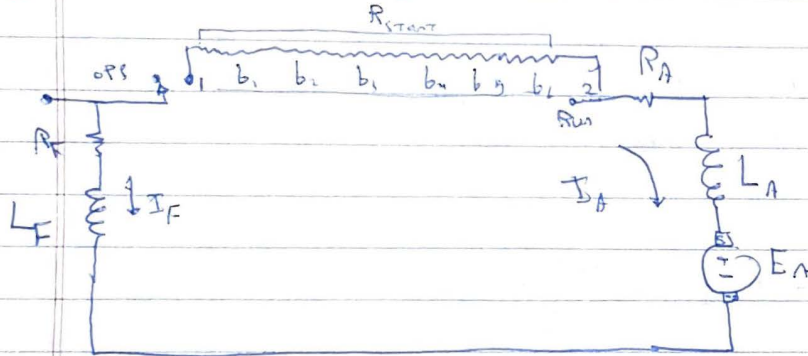


⊙ مع الارتفاع  
من اليمين  
للتيه  
↑

⊙ Continuous starting resistor, which is gradually cut out of the circuit by a person moving his handle.

⊙ The handle shouldn't be moved slowly to prevent burning up the resistor.

⊙ The handle shouldn't be moved quickly to prevent the resulting current of being large.

② Automatic starter

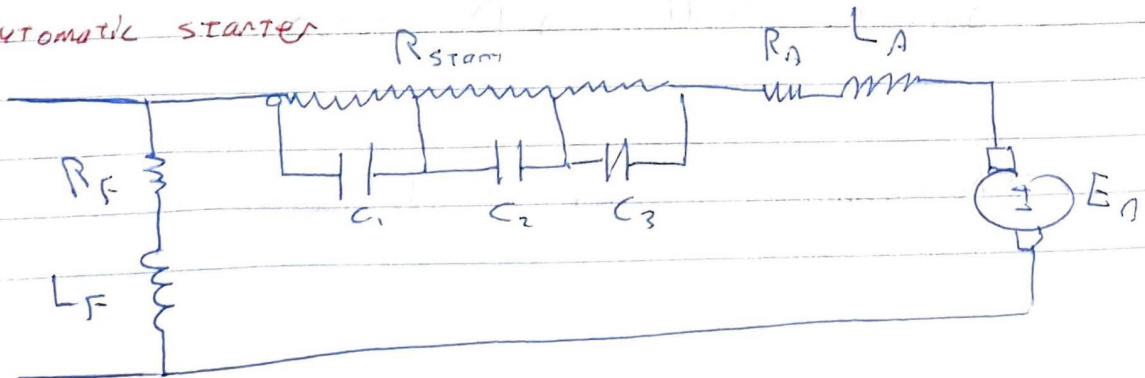


$$I_{\text{start}} = \frac{V_T - E_A}{R_A + (R_{\text{start}} - 1)}$$

$C_1, C_2, C_3 \rightarrow$  CONTACTS OF RELAY  $C_1, C_2$  &  $C_3$  (Normally OPENED CONTACTS)

The Resistor,  $R_{START}$  is divided into 3 parts, which are Removed sequentially via the CONTACT  $C_1, C_2$  &  $C_3$

$C_1, C_2$  &  $C_3$  ARE 3 CONTACTS OF time delay relays on armature Voltage sensing relays.


Video

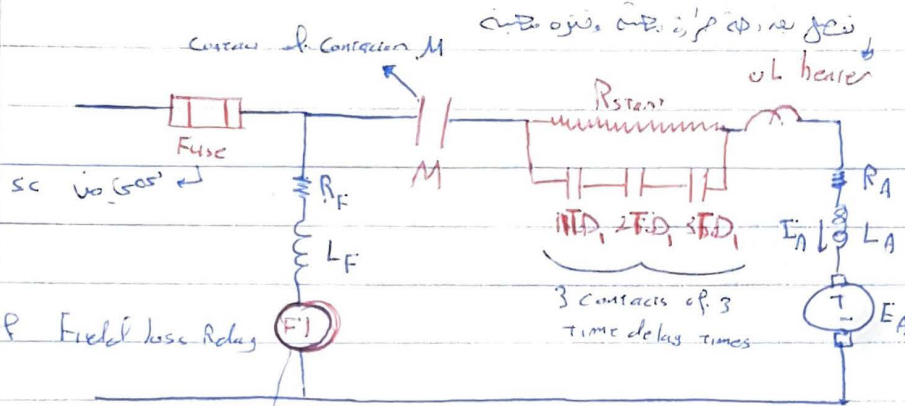


Coil of Field loss Relay (FL)

التيار الذي يمر في ملف الـ Field loss  
 في حالة انقطاع التيار من المحرك  
 (M) في حالة انقطاع التيار

Control Circuit

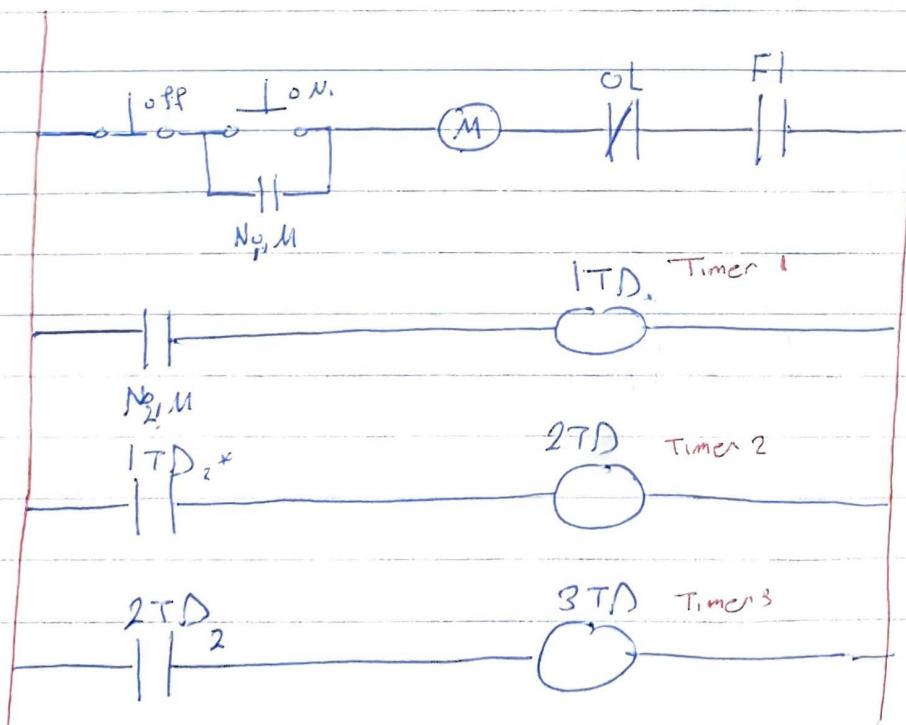


2

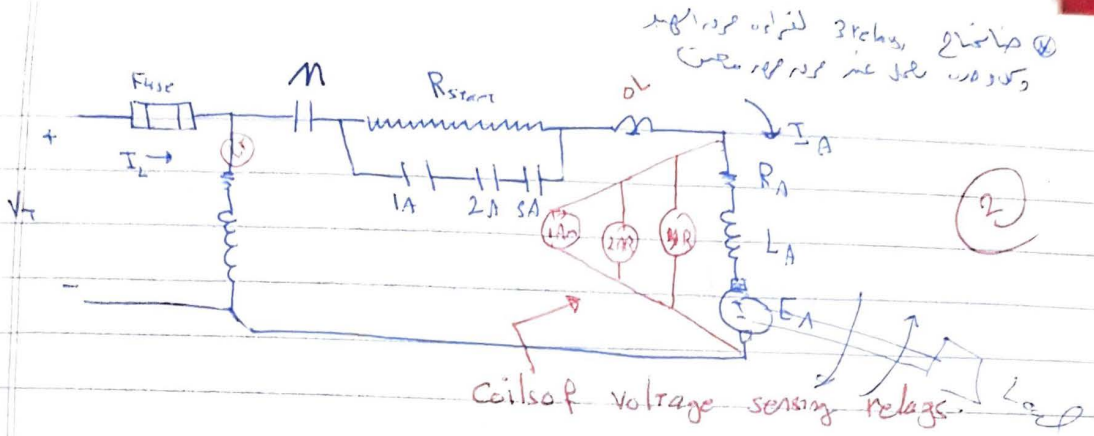

2

### Control circuit

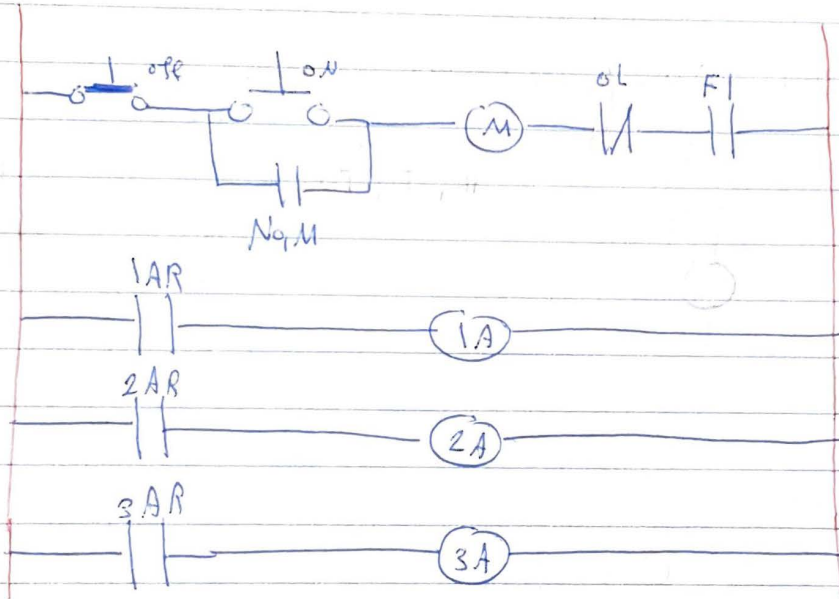

Fuse To protect the motor and the source from short circuit.

OL: Cut off the current when the Temp increased too much than Normal's Temp (for long time)

Chapter 8 circuit 1, 2, 3, 5, 6, 8, 9, 12, 13, 14, 21

RP