

CHAPTER 6: Induction Motors.

* The distinguishing feature of induction motor is that no DC field current is required to run the machine.

→ The construction of the induction motor

It has the same stator construction of synchronous motor with different rotor construction.

The induction motor has two rotor types:

1) The squirrel cage rotor.

2) The wound rotor.

→ Explanation of the two rotor types:

① The cage rotor:


It consists of series conducting bars laid into slots carved in the face of the rotor and shorted at either end by large shorting rings.

② The wound rotor:

It consists of a set of three-phase windings, that are mirror images of the windings of the stator. The windings are usually Y-connected.

The terminals a, b & c are tied to the slip-rings on the rotor's shaft.

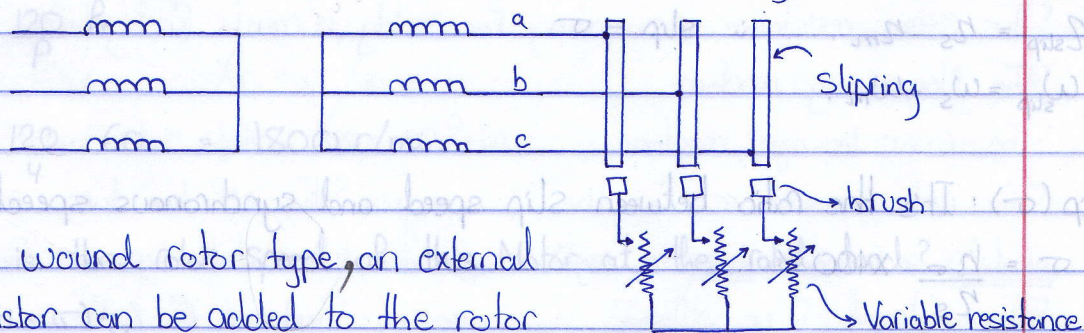The rotor windings are shorted via brushes riding on the sliprings.



Note: ① In wound rotor type, an external resistor can be added to the rotor circuit to modify the torque-speed characteristics.

② The wound rotor is more expensive and requires much more maintenance.

→ Operating principle of induction motor:

A set of 3- ϕ voltages is applied to the stator windings and a set of 3- ϕ stator currents is flowing.

The currents will produce a rotating magnetic field which rotates at synchronous speed (n_s) where n_s is given by:

$$n_s = \frac{120 f_e}{p} \quad \therefore f_e: \text{ is the system freq. in hertz.}$$

The rotating magnetic field will pass over the rotor conducting bars and induce voltages on them by the relation:

$$e_{ind} = (v \times B) \cdot l$$

$\therefore v$: is the velocity of the bar relative to the magnetic field B_s .

The induced voltages will produce a rotor current I_r .

The rotor current I_r produces a rotor magnetic field B_r .

Now the rotor magnetic field B_r interacts with the stator magnetic field B_s to produce the induced torque in the machine.

$$T_{ind} = k B_r \times B_s$$

Note: The rotor can speed-up to synchronous speed but it can never reach it.

→ The Concept of Rotor Slip:

Two terms are commonly used to define the relative motion of the rotor and the magnetic fields:

① Slip speed: It's the difference between the synchronous speed & rotor speed.

$$\rightarrow n_{slip} = n_s - n_m \quad \therefore \text{slip} \equiv \sigma$$

$$\rightarrow \omega_{slip} = \omega_s - \omega_m$$

② Slip (σ): It's the ratio between slip speed and synchronous speed.

$$\rightarrow \sigma = \frac{n_s - n_m}{n_s} \times 100\%$$

$$\rightarrow \sigma = \frac{n_s - n_m}{n_s} \times 100\%$$

$$\rightarrow \sigma = \frac{\omega_s - \omega_m}{\omega_s} \times 100\%$$

Solving the last equation for η_m :

$\eta_m = (1 - \sigma)\eta_s$

$\omega_m = (1 - \sigma)\omega_s$

Notice that is the rotor is rotating at η_s then $(\sigma = 0)$, while if it is locked ($\eta_m = 0$) then $(\sigma = 1)$.

The Electric frequency on the rotor:

If the rotor is locked ($\eta_m = 0$) $(\sigma = 1)$, then it will have the same frequency as the stator. ($f_r = f_s = f_e$)

On the other hand, when the rotor turns at synchronous speed ($\eta_m = \eta_s$) $(\sigma = 0)$, then the rotor frequency will be zero ($f_r = 0$).

At any other speed between 0 & η_s the rotor's frequency is directly proportional to the slip (σ).

$f_r = \sigma f_e$

$f_r = \frac{120}{P} (\eta_s - \eta_m)$

Example:

A 208V, 10-hp, 4-pole, 60-Hz, Y-connected IM has a full load slip of 5%.

a) What is the synchronous speed of this Motor?

$\eta_s = \frac{P}{4} = 1800 \text{ r/min}$

$= \frac{120}{4} \cdot 60 = 1800 \text{ r/min}$

b) What is the rotor speed of this Motor at the rated load?

$\eta_m = (1 - \sigma)\eta_s$

$= (1 - 0.05)(1800)$

$= 1710 \text{ rpm}$


c) What is the rotor frequency of this motor at the rated load?
 $r = g_e$
 $= 0.05 (60)$
 $= 3 \text{ Hz}$

d) What is the shaft torque of this motor at the rated load?

$R_{out} = T_{load} \omega_m$
 $T_{load} = R_{out} / \omega_m$
 $= (10 \text{ hp}) (746) / (1710) (2\pi/60)$
 $= 41.7 \text{ N.m}$

The Equivalent Circuit of an Induction Motor:

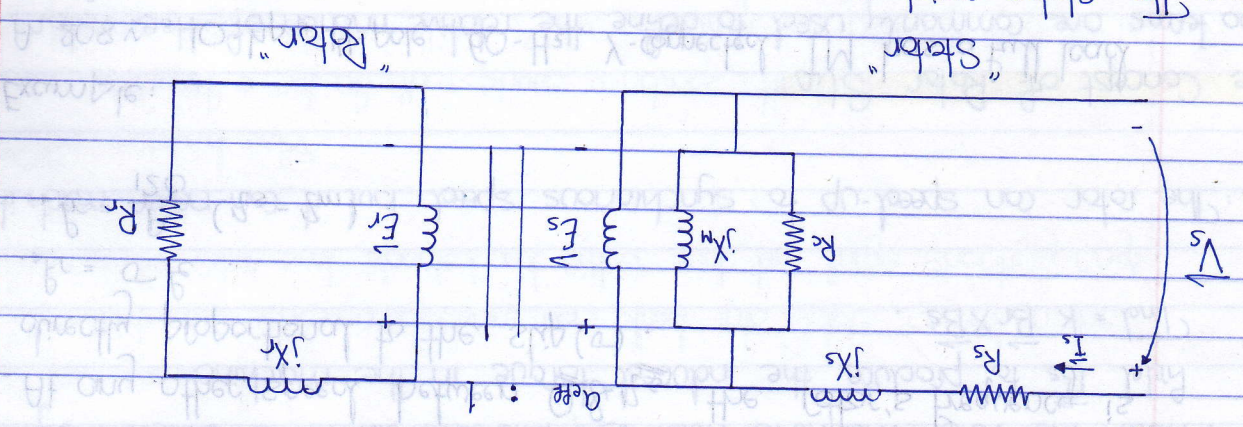
It is very similar to the per-phase equivalent circuit of the transformer.



- Rs: The stator resistance.
- Xs: The stator leakage reactance.
- Rc: The core resistance accounting for eddy currents & hysteresis.
- Xm: The Magnetizing reactance.
- Xr: The rotor leakage reactance.
- Rr: The rotor resistance, for the windings in (wound) bars in (cage).
- Es: The internal stator voltage.
- Er: The induced rotor voltage.
- Is: The stator (source) current.
- Ir: The rotor current.
- Vs: The stator (source) phase voltage.

Note: a_{eff} is fairly easy to determine for the wound-rotor motor.

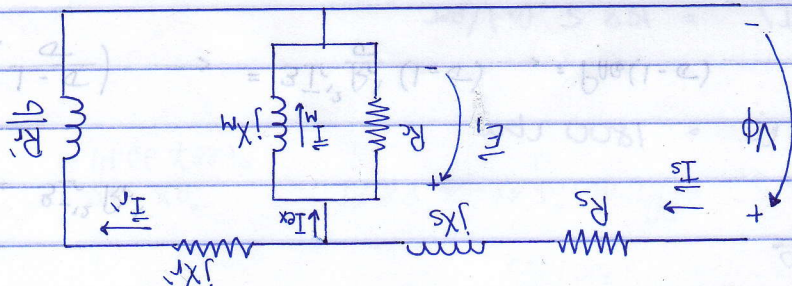the motor which couples between \vec{E}_s & \vec{E}_r .



→ The per-phase equivalent circuit of an induction motor.

at the locked rotor state $X_a = 2\pi f L_a$

$X_r = 2\pi(\sigma)l_e$, $X_r = \sigma X_a$

So, since $f_r = \sigma f$

$X_r = \omega_r L_r = 2\pi f_r L_r$

of the rotor and its voltage frequency:

The reactance of an induction motor rotor depends on the inductance

$$f_r = \sigma f$$

$$E_r = \sigma E_a$$

directly proportional to the slip of the rotor.

At any other speed, the voltage and frequency of the rotor is

$f_r = 0$ "The smallest rotor frequency"

$\sigma = 0$ and $E_r = 0$ "The smallest rotor Voltage"

resulting in no relative motion,

(When the rotor moves at the same speed as the stator magnetic field,


$f_r = 1 \cdot f$ "The largest rotor frequency"

$\sigma = 1$ and $E_r = 1 \cdot E_a$ "The largest rotor Voltage"

The largest relative motion occurs when the rotor is locked,


stator magnetic fields, the greater the resulting rotor voltage & rotor frequency.

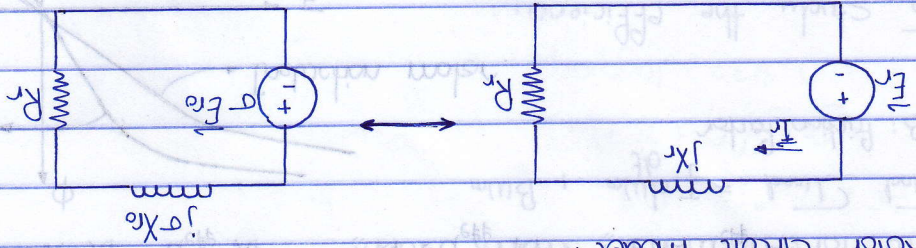In general, the greater the relative motion between the rotor & the




Rotor circuit model:

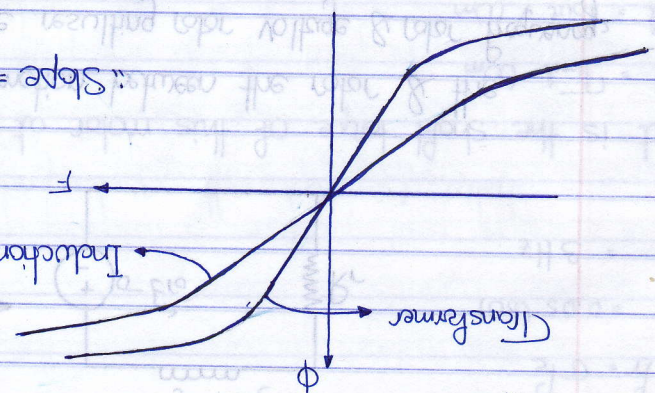$\therefore \frac{I_1}{I_2} = \frac{1}{a_{eff}}$
 $\therefore X_1' = a_{eff}^2 X_2$
 $\therefore R_1' = a_{eff}^2 R_2$
 $\therefore E_1 = a_{eff} E_2$



Power Calculations:

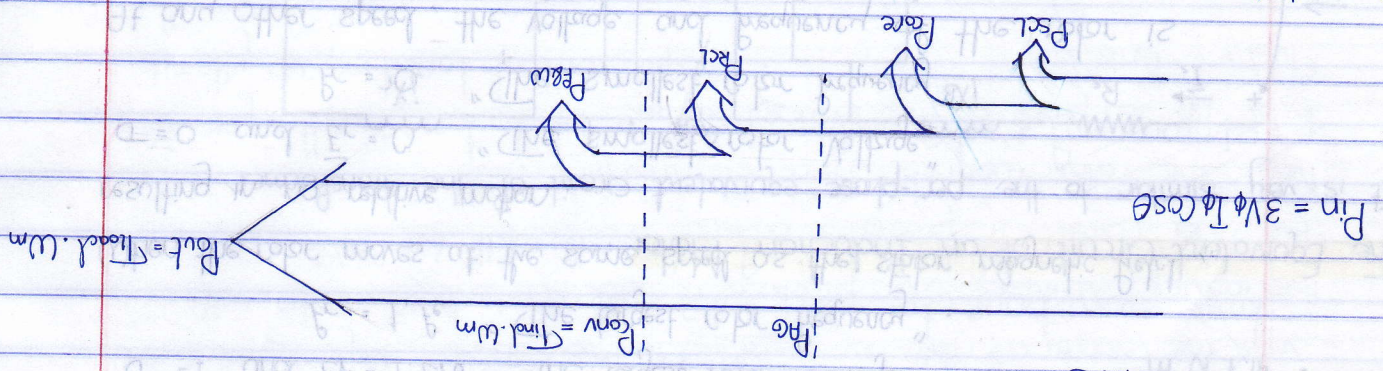

- Psc: Stator copper losses = $3 I_1^2 R_1$ ①
- Pcore: Core losses = $3 E_1^2 / R_c$ ②
- Prc: Rotor copper losses = $3 I_2^2 R_2$ ③
- Pmech: Converted power to Mechanical ④
- Pwind: Friction & Windage losses
- Pcu: Air Gap power consumed in "R2"

- Prc: Rotor copper losses = $3 I_2^2 R_2$ ③
- Pcu: Air Gap power = $3 I_2^2 R_2'$ ④

From the power flow diagram:

1) $P_{in} = P_{sc} + P_{core}$
 2) $P_{cu} = P_{rc} + P_{rc}$
 3) $P_{out} = P_{mech} - P_{wind}$

$= 3 I_2^2 R_2' - \frac{d}{dt} 3 I_2^2 R_2'$

$P_{out} = 3 I_2^2 R_2' \left(\frac{d}{dt} (1 - \sigma) \right) = 3 I_2^2 R_2' (1 - \sigma) = P_{ag} (1 - \sigma)$

Now from Newton's second law:

$$T_{ind} = J \frac{d\omega}{dt} + B\omega$$

B: Friction factor

To study the efficiency:

① Rotor efficiency:

$$\eta_r = \frac{P_{mech}}{P_{ag}} = (1 - \sigma)$$

② Motor efficiency:

$$\eta_m = \frac{P_{out}}{P_{in}}$$

Induced Torque:

$$P_{mech} = T_{ind} \omega_m$$

$$\omega_m = (1 - \sigma) \omega_s$$

$$P_{mech} = (1 - \sigma) P_{ag}$$

$$T_{ind} = \frac{P_{mech}}{\omega_m} = \frac{3 I_r^2 R_r'}{s \omega_s}$$

Example:

A 460-V, 25-hp, 60-Hz, 4-pole, Y-connected induction motor has the following impedances in Ohms per phase referred to the stator circuit:

$$R_s = 0.641 \Omega, R_r' = 0.332 \Omega, X_m = 26.3 \Omega$$

$$X_s = 1.106 \Omega, X_r' = 0.464 \Omega$$

The total rotational losses are 100 W and are assumed to be constant. The core losses are lumped in with the rotational losses.

For a rotor slip of 2.2% at the rated voltage & rated frequency:

Find:

a) The Motor's Speed:

$$\omega_s = 120 \frac{P}{f} = 120 \frac{4}{60} = 1800 \text{ rpm}$$

$$\omega_m = \omega_s (1 - s) = 1800 \cdot 0.978 = 1760.4 \text{ rad/sec}$$

* To Find the Motor's speed (n_m)


$$n_m = (1 - s) n_s$$

$$= (1 - 0.022)(1800)$$

$$= 1760 \text{ rpm.}$$

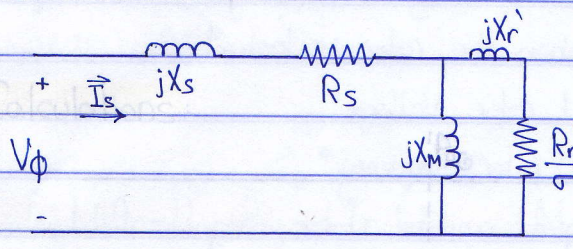b) The Motor's stator current:

To find the stator current we should get the equivalent impedance of the circuit:



To Find Req:

1) $jX_M \parallel (jX_r' + \frac{R_r'}{s})$

$\therefore jX_M = 26.3j$

$jX_r' + \frac{R_r'}{s} = 0.464j + \frac{0.332}{0.022} \Rightarrow 15.1 \angle 1.76^\circ$

$\rightarrow (26.3j \parallel (15.1 \angle 1.76^\circ))$

Req1 $\rightarrow \frac{1}{\frac{1}{26.3j} + \frac{1}{15.1 \angle 1.76^\circ}} = 12.92 \angle 31.2^\circ$

2) $jX_s + R_s + Req1$

$= 1.106j + 0.641 + 12.92 \angle 31.2^\circ$

$= 14.06 \angle 33.7^\circ$

Then Find V_ϕ :

$V_L = \sqrt{3} V_\phi \rightarrow V_\phi = \frac{V_L}{\sqrt{3}} = \frac{460}{\sqrt{3}} = 266 \angle 0^\circ \text{ V}$

Now the current:

$\vec{I}_s = \frac{V_\phi \angle 0^\circ}{Z_{eq}} = \frac{266 \angle 0^\circ}{14.06 \angle 33.7^\circ} = 18.88 \angle -33.7^\circ \text{ A}$

c) The Motor's PF:

$$\begin{aligned} PF &= \cos^*(\theta_v - \theta_i) \\ &= \cos^*(0 + 33.7) \\ &= 0.832 \text{ lagging} \end{aligned}$$

d) The Motor's P_{conv} & P_{out} :

i. $P_{conv} = (1 - \sigma) P_{AG}$, so we need to find P_{AG} :

$$P_{AG} = P_{in} - P_{scl}$$

$$\begin{aligned} \therefore P_{in} &= 3V\phi I\phi \cos\theta \\ &= 3(266)(18.88)(0.832) \\ &= 12.53 \text{ kW} \end{aligned}$$

$$\begin{aligned} P_{scl} &= 3I_s^2 R_s \\ &= 3(18.88)^2(0.641) \\ &= 0.685 \text{ kW} \end{aligned}$$

$$\begin{aligned} P_{AG} &= (12.53 \text{ k} - 0.685 \text{ k}) \text{ W} \\ &= 11.845 \text{ kW} \end{aligned}$$

$$\begin{aligned} P_{conv} &= (1 - 0.022)(11.845 \text{ k}) \\ &= 11.585 \text{ kW} \end{aligned}$$

$$\begin{aligned} \text{ii. } P_{out} &= P_{conv} - P_{f\&w} \\ &= (11.585 \text{ k} - 1.1 \text{ k}) \text{ W} \\ &= 10.485 \text{ kW} \end{aligned}$$

e) T_{ind} & T_{load} for the Motor:

$$\text{i. } T_{ind} = \frac{P_{conv}}{\omega_s} \Rightarrow \frac{11585}{1800 \cdot \frac{\pi}{30}} = 62.8 \text{ N.m}$$


$$\text{ii. } T_{load} = \frac{P_{out}}{\omega_m} \Rightarrow \frac{10485 \text{ k}}{1760 \left(\frac{\pi}{30}\right)} = 56.9 \text{ N.m}$$

f) The Motor's efficiency:

$$\eta_s = \frac{P_{out}}{P_{in}} \times 100\%$$


$$= \frac{10485}{12530} \times 100\% = 83.7\%$$

Derivation of induced torque equation:

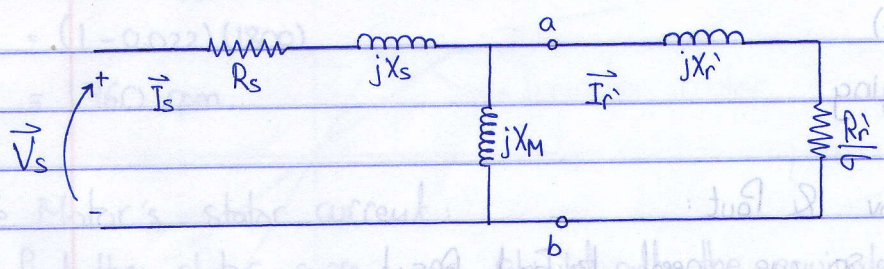

$T_{ind} = \frac{P_{ag}}{\omega_s} = \frac{3I_r'^2 R_r'}{\omega_s}$; I_r' is the magnitude of the current.

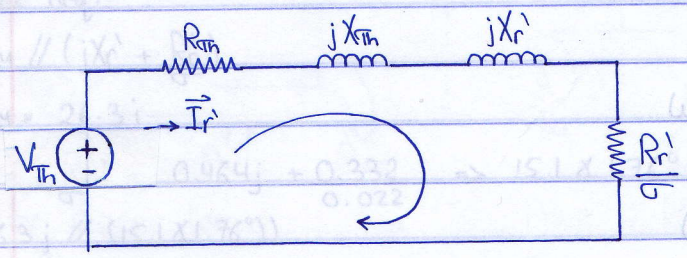From the equation it's clear that we need I_r' to calculate the T_{ind} , but in fact there is no access on the rotor so it's difficult to find it. The solution is to get the thevinin of the stator part from points (a, b).



① $\vec{V}_{th} = \vec{V}_{oc} = \frac{jX_m}{R_s + j(X_s + X_m)} \vec{V}_s$

$Z_{th} = R_s \frac{X_m}{X_s + X_m} + j \frac{X_s X_m}{X_s + X_m}$

$\therefore X_m + X_s \gg R_s$

$R_{th} = R_s \frac{X_m}{X_s + X_m}$ ②

$\vec{V}_{th} = \frac{X_m}{(X_s + X_m)} \vec{V}_s$ ①

$X_{th} = X_s \frac{X_m}{X_s + X_m}$ ③

② $Z_{th} = (R_s + jX_s) // jX_m$
 $= \frac{(R_s + jX_s)(jX_m)}{R_s + j(X_s + X_m)}$

$\therefore X_m + X_s \gg R_s$

$Z_{th} = \frac{(R_s + jX_s)(X_m)}{(X_s + X_m)}$

i

ii

To find I_r' :

$$\vec{I}_r' = \frac{\vec{V}_{Th}}{(R_{Th} + \frac{R_r'}{\sigma}) + j(X_{Th} + X_r')}$$

, but to find the T_{ind} we need the magnitude.

$$|\vec{I}_r'| = \frac{|\vec{V}_{Th}|}{\sqrt{(R_{Th} + \frac{R_r'}{\sigma})^2 + (X_{Th} + X_r')^2}}$$

Now: $T_{ind} = \frac{3 I_r'^2 R_r'}{\sigma \omega_s}$, substitute I_r' in T_{ind} .

$$T_{ind} = \frac{3 V_{Th}^2}{\omega_s \left[\left(R_{Th} + \frac{R_r'}{\sigma} \right)^2 + \left(X_{Th} + X_r' \right)^2 \right]} \cdot \frac{R_r'}{\sigma}$$

* Note: In Calculations we can make an approximation in:

$$\frac{X_M}{X_s + X_M} \approx 1 \text{ since } X_M \gg X_s.$$

Therefore, $R_{Th} \approx R_s$
 $X_{Th} \approx X_s$
 $V_{Th} \approx V_s$


$$T_{ind} = \frac{3 V_s^2}{\omega_s \left[\left(R_s + \frac{R_r'}{\sigma} \right)^2 + \left(X_s + X_r' \right)^2 \right]} \cdot \frac{R_r'}{\sigma}$$

Induction Motor Torque-Speed characteristics:

From the T_{ind} equation we can see that the torque is a function of slip, and since the slip is changing by γ_m so it's also a function of γ_m .

$$T_{ind} = f(\sigma) = g(\gamma_m)$$

$$\gamma_m = (1 - \sigma) \gamma_s$$

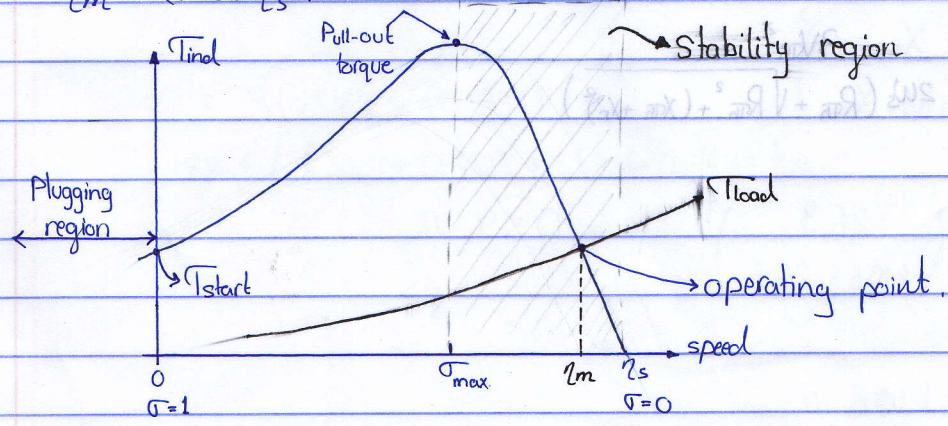

Notes on the Curve:

① When the slip range is very small, the induced torque is approximately proportional to the slip (linear relationship).

$$T_{ind} \approx \frac{3V_{th}^2}{\omega_s (R_r')^2} \cdot \frac{R_r'}{s} \rightarrow T_{ind} \approx \frac{3V_{th}^2}{\omega_s R_r'} \cdot s \rightarrow T_{ind} = Ks$$

② Under steady state (speed is constant)

From Newton's second law:

$$T_{ind} - T_{load} = J \frac{d\omega}{dt} \rightarrow \text{So } T_{ind} = T_{load}$$

Plugging Region:

It's used to stop the motor rapidly by switching any two of the three phases.

Starting torque (T_{start}):

It's slightly higher than the motor rated torque.


$T_{pull-out} = T_{max}$: The maximum torque

$$T_{max} = (2-3) T_{rated}$$


To find the maximum torque:

$$\frac{\partial T_{ind}}{\partial s} = 0 \rightarrow s_{max} = \frac{R_r'}{\sqrt{R_{th}^2 + (X_{th} + X_r')^2}}$$

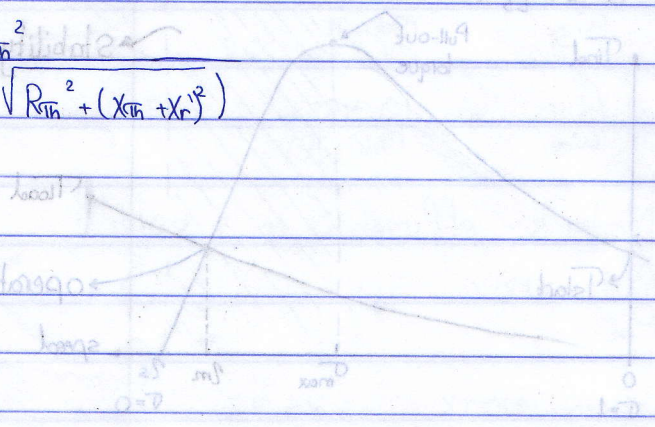
$$T_{max} = \frac{3V_{th}^2}{2\omega_s (R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_r')^2})}$$



In Wound Rotor Induction Motor

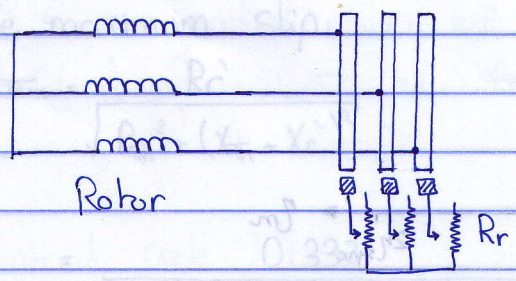

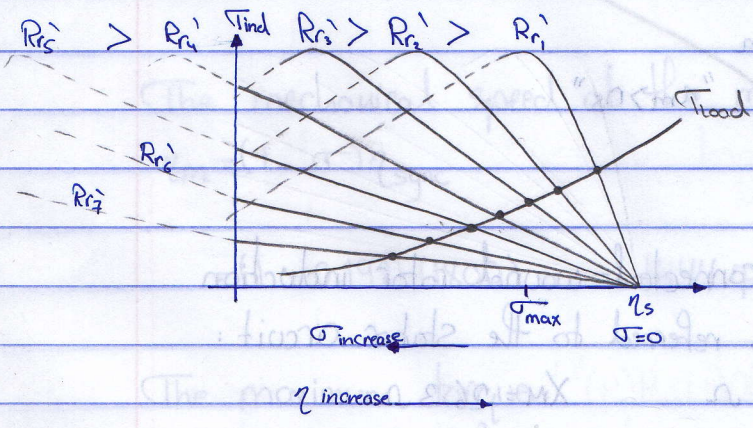
* Only in the wound rotor we can change "Rr"



When $R_r' \leq R_r' \leq R_{r4}' \rightarrow$ Then $R_r' \uparrow \rightarrow \sigma_{max} \uparrow \rightarrow \sigma \uparrow \rightarrow \eta \downarrow$
 So $\eta_r = (1 - \sigma) [\text{Rotor efficiency}] \downarrow$
 and $\eta \downarrow \rightarrow [\text{Motor efficiency}]$
 and $T_{start} \uparrow$

When $R_r' > R_{r4}' \rightarrow T_{start} \downarrow \Rightarrow \eta (\text{efficiency}) \downarrow$

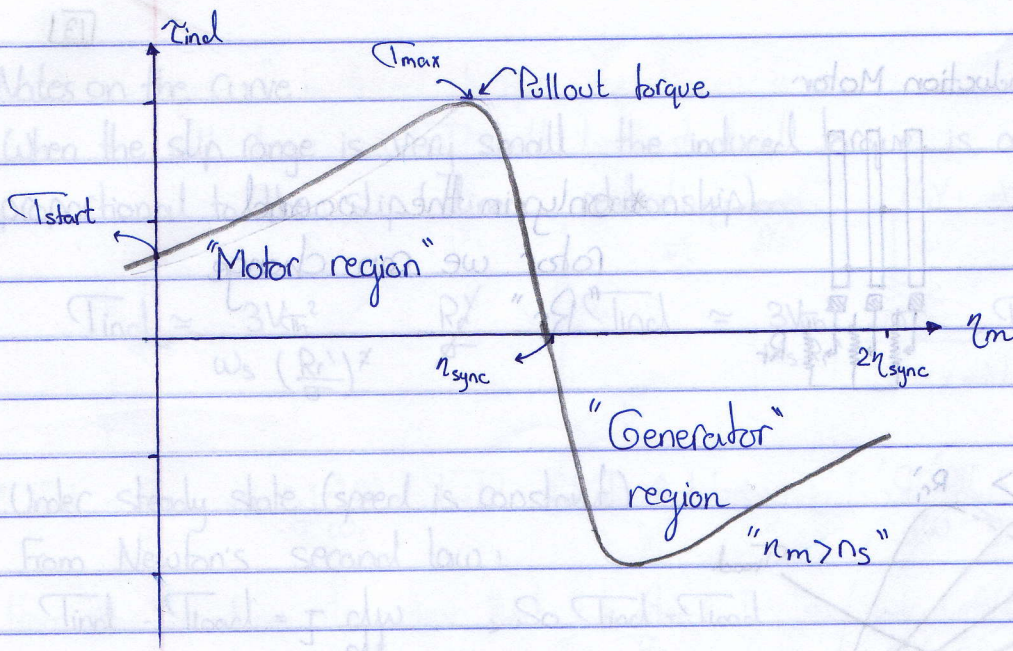The Rotor resistance in the wound Rotor Induction Motor is a method to control the speed & the starting torque.



Example: A 460-volt, 25-hp, 4-pole, Y-connected wound rotor induction motor has the following impedances referred to the stator circuit:

$R_s = 0.641 \Omega$ $R_r' = 0.332 \Omega$ $X_M = 26.3 \Omega$
 $X_s = 1.106 \Omega$ $X_r' = 0.464 \Omega$

a) What is the maximum torque of this motor? At what speed & slip does it occur?

[1] Find $V_{th} = V_\phi \frac{X_M}{\sqrt{R_s^2 + (X_s + X_M)^2}}$
 $= 266 \frac{26.3}{\sqrt{(0.641)^2 + (1.106 + 26.3)^2}} = 255.2 \text{ V}$

[2] Find $R_{th} = R_s \left(\frac{X_M}{X_s + X_M} \right)^2$
 $= 0.641 \left(\frac{26.3}{1.106 + 26.3} \right)^2 = 0.59 \Omega$

[3] Find $X_{th} = X_r' = 1.106 \Omega$

Now:

The maximum slip:

*Note: $n_s = \frac{120}{4} \cdot 60 = 1800 \text{ rpm}$

$$\sigma_{\max} = \frac{R_r'}{\sqrt{R_{th}^2 + (X_{th} + X_r')^2}}$$

$$= \frac{0.332}{\sqrt{(0.59)^2 + (1.106 + 0.464)^2}} = 0.198$$

The mechanical speed at the maximum slip:

$$n_m = (1 - \sigma) n_{sync}$$

$$= (1 - 0.198)(1800) = 1444 \text{ rpm}$$

The maximum torque:

*Note: $\omega_s = n_s \cdot \frac{2\pi}{60}$

$$T_{\max} = \frac{3V_{th}^2}{2\omega_s [R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_r')^2}]}$$

$$= \frac{3(255.2)^2}{2(188.5)[0.59 + \sqrt{0.59^2 + (1.106 + 0.464)^2}]} = 229 \text{ N.m}$$

b) What is the starting torque of the motor?

In the torque equation set the σ to $\frac{1}{s}$ & solve it as T_{start} :

$$T_{start} = \frac{3V_{th}^2 R_r'}{\omega_s [(R_{th} + R_r')^2 + (X_{th} + X_r')^2]}$$

$$= \frac{3(255.2)^2 (0.332)}{188.5 [(0.59 + 0.332)^2 + (1.106 + 0.464)^2]} = 104 \text{ N.m}$$

c) When the Rotor resistance is doubled, What is the speed at which the max torque occurred? What is the new starting torque?

→ if we double the rotor resistance then the σ will be doubled
So

$$\sigma_{max} = 0.396$$

→ The speed at which this slip occurs is:


$$\begin{aligned} n_{pm} &= (1 - \sigma) n_s \\ &= (1 - 0.396)(1800) \\ &= 1087 \text{ rpm} \end{aligned}$$

→ The max torque will not be changed.

$$T_{max} = 229 \text{ N.m}$$

→ The starting torque will change.
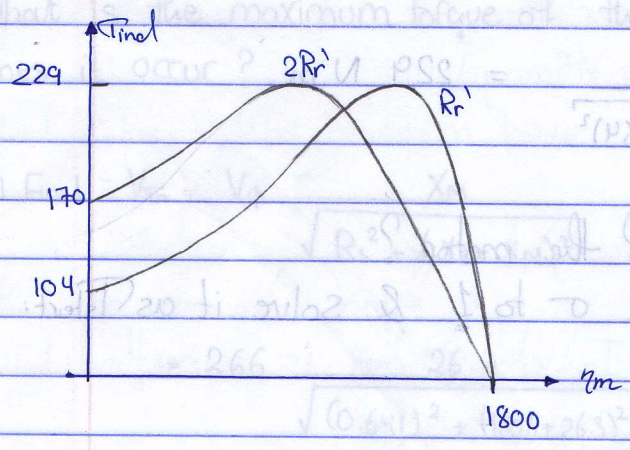
$$\begin{aligned} T_{start} &= \frac{3(255.2)^2 (0.664)}{188.5 [(0.59 + 0.664)^2 + (1.106 + 0.464)^2]} \\ &= 170 \text{ N.m} \end{aligned}$$



1) Find $R_m = R_s \left(\frac{X_m}{X_s} \right)$

$$= 0.641 \left(\frac{26.3}{1.106 + 26.3} \right)^2 = 0.59 \Omega$$

3) Find $X_m = X_r' = 1.106 \Omega$

Calculations of Motor Starting current:

$$I_{L \text{ start}} = \frac{S_{\text{start}}}{\sqrt{3} V_L} \quad \text{ii } S_{\text{start}} : \text{Rated power (hp)} * \text{"code letter Factor"}$$

Nominal code letter	locked Rotor [KVA/hp]
A	0 - 3.15
B	3.15 - 3.55
C	3.55 - 4.00
D	4.00 - 4.50
E	4.50 - 5.00
F	5.00 - 5.60
⋮	⋮

Example:


What's the starting current of a 15 hp, 208 v, code letter F 3- Φ induction Motor.

$$I_{L \text{ start}} = \frac{S_{\text{start}}}{\sqrt{3} V_L} = \frac{15 (5.6) \text{ k}}{\sqrt{3} (208)} = 233 \text{ Amp.}$$

Relay logic control of 3- Φ induction Motor: (ON-OFF control).


Relay: It is an electromagnetic switch that has a coil and a set of auxiliary contacts.

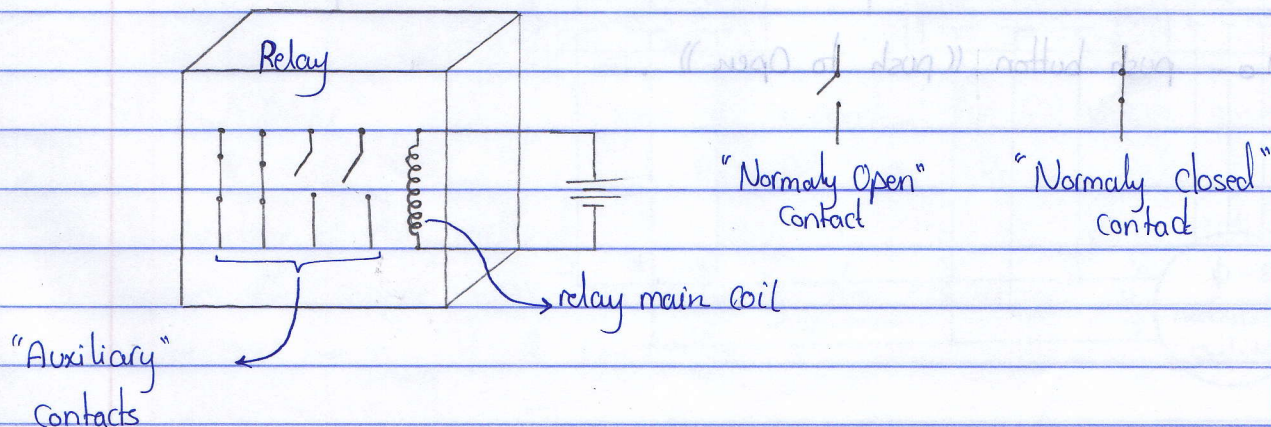The contacts can be either normally open or normally closed.



When the main coil is energized, the normally open contact will close & the normally close contact will open.

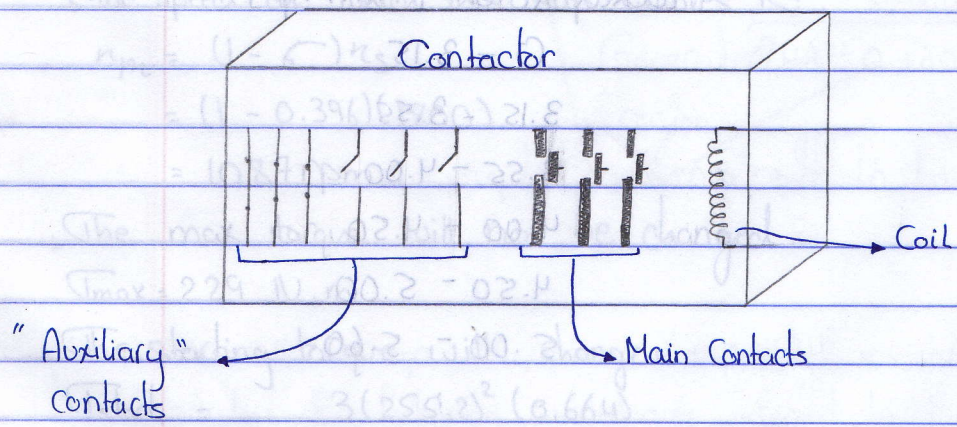Contactor: It is an electromagnetic switch that has three main contacts with a set of auxiliary contacts.




The auxiliary contacts can be either normally open or normally closed.



Symbols:

- ① or coil of relay or contactor.
- ② Normally Open.
- ③ Normally closed.
- ④ push button ((push to close)).
- ⑤ push button ((push to Open)).

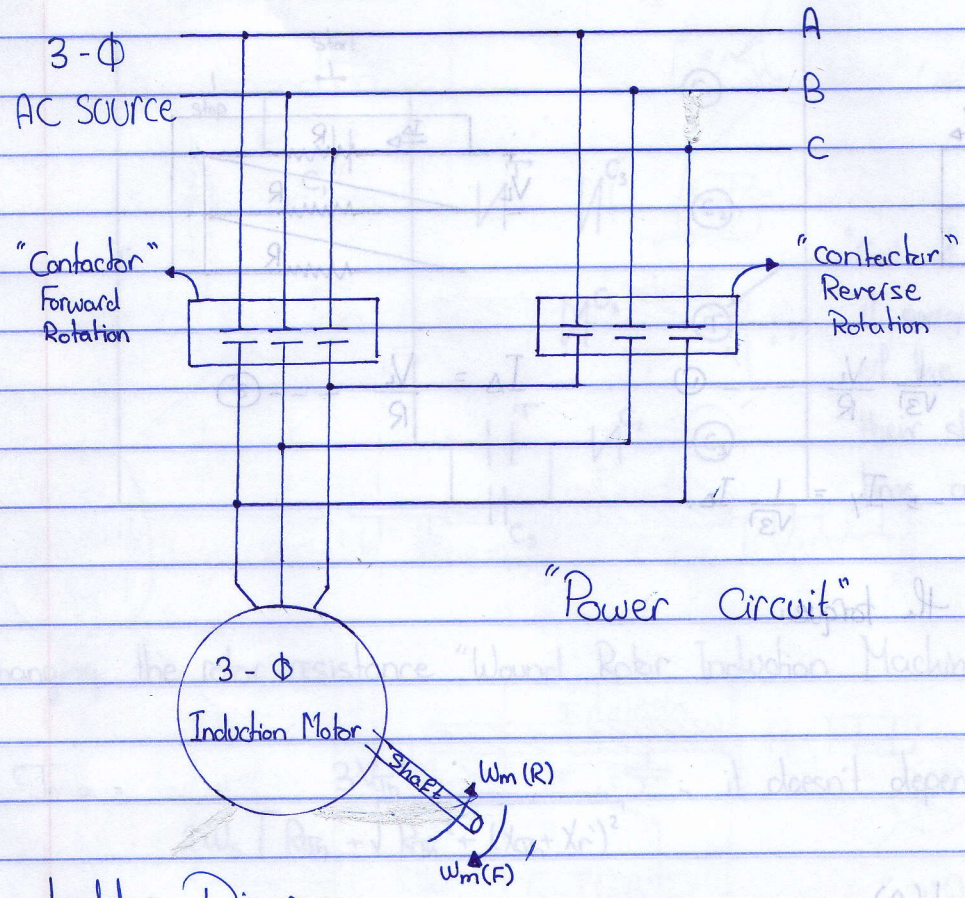Example: Control & power circuits to reverse the direction of motor





Ladder Diagram:
For the control circuit:

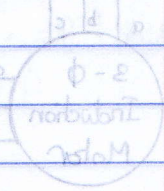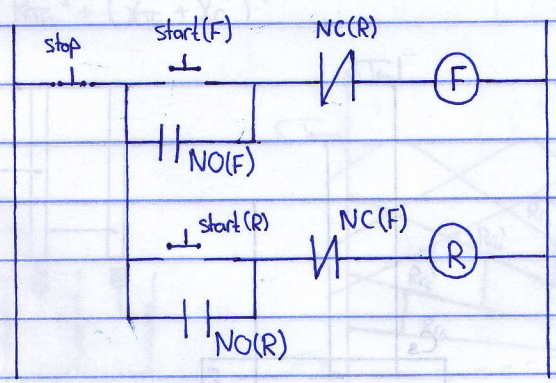

→ Methods to reduce the starting current of the 3-φ induction Motor:

□ Y-Δ starter:

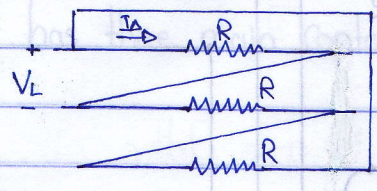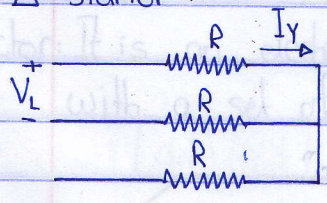

$$I_Y = \frac{V_L / \sqrt{3}}{R} = \frac{1}{\sqrt{3}} \frac{V_L}{R} \quad \text{--- (1)}$$

$$I_{\Delta} = \frac{V_L}{R} \quad \text{--- (2)}$$

→ From (1) & (2) → $I_Y = \frac{1}{\sqrt{3}} I_{\Delta}$


We can also study the torque:

$$T_{ind} = \frac{3 I_r^2 R_r'}{\omega_s}$$


$$T_{ind, start} = \frac{3 I_r^2 R_r'}{\omega_s}$$

$$T_{ind, start (Y)} = \frac{1}{3} T_{ind, start (\Delta)}$$

The Power circuit:

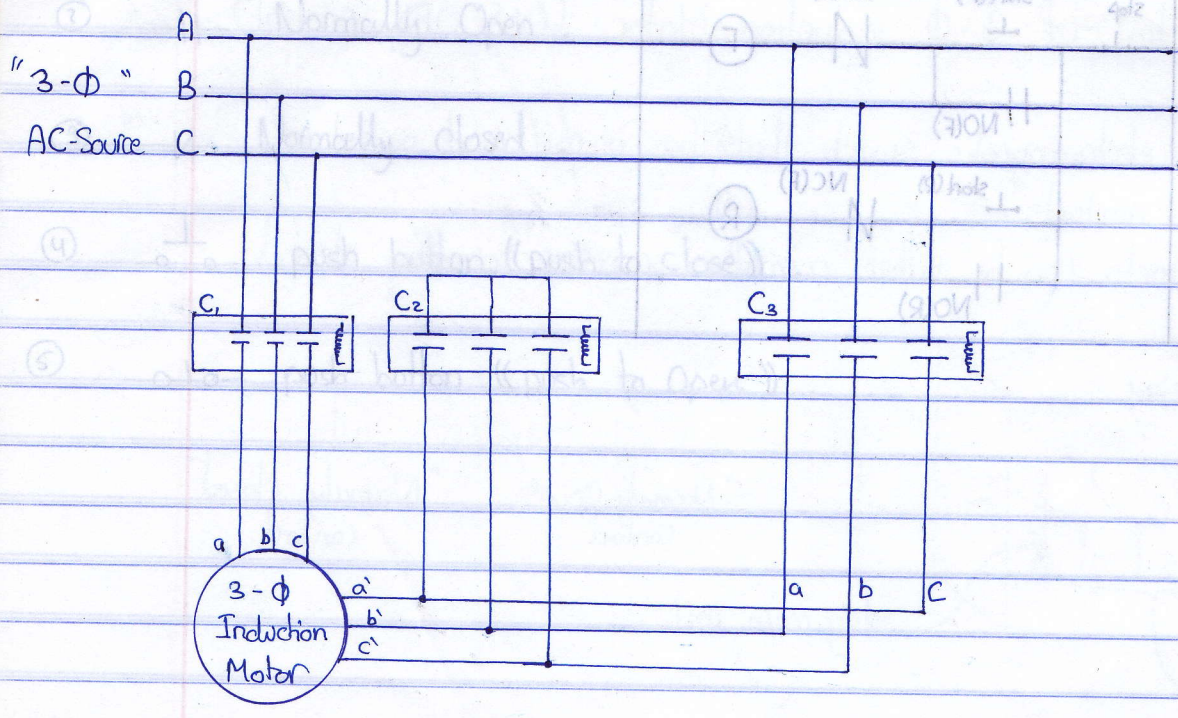

The control circuit: For Y-Δ starter.

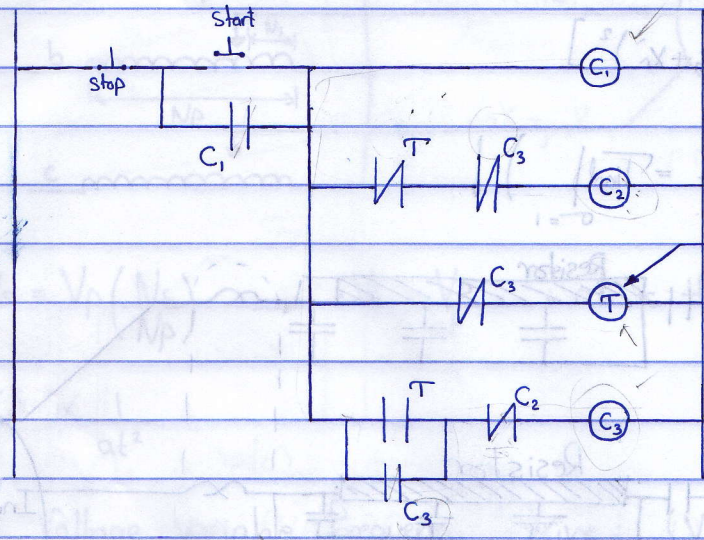

"Coil of timer, when it energized the contactor of the timer will change their state after present time or time delay"



② Changing the rotor resistance "Wound Rotor Induction Machine":

$$T_{max} = \frac{3V_{th}^2}{2W_s [R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_r')^2}]}$$

∴ it doesn't depend on R_r'

$$\sigma_{max} = \frac{R_r'}{\sqrt{R_{th}^2 + (X_{th} + X_r')^2}}$$

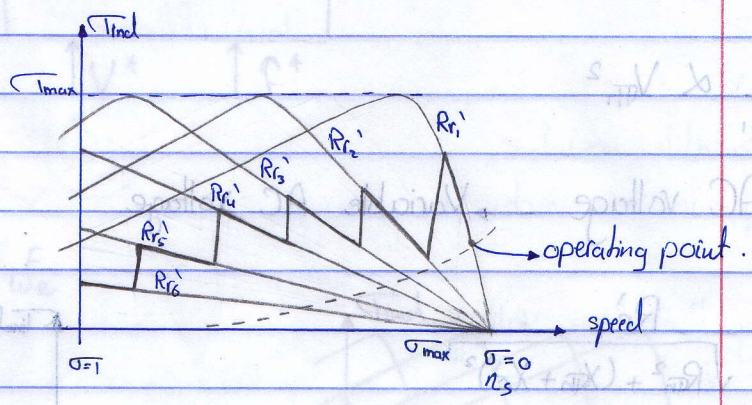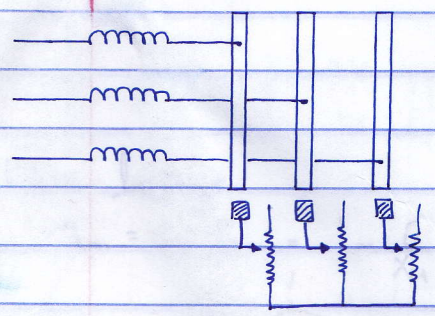∴ if $R_r' \uparrow \Rightarrow \sigma_{max} \uparrow$



"Variable Rotor Resistance"
"Potential Meter"

Note: η_s is constant for R_r' values since $\eta_s = 1 - \sigma$
 $R_{r6}' > R_{r5}' > R_{r4}' > R_{r3}' > R_{r2}' > R_{r1}'$


The disadvantage of this method:

It increases the copper losses so reducing the efficiency
 $R_r' \uparrow \rightarrow P_{cu} \uparrow \Rightarrow \eta_{motor} \downarrow$ & $\eta_p = (1 - \sigma) \downarrow$

3] Stator resistance or inductance stator

$$T_{ind} = \frac{3V_{th}^2 R_r'}{\sigma \omega_s [(R_r' + R_{th})^2 + (X_{th} + X_r')^2]}$$

$$\left(R_{th} \approx \frac{X_m}{X_m + X_s} \cdot R_s \uparrow \right) \Rightarrow \left(T_{start} = T_{ind} \Big|_{\sigma=1} \right) \downarrow$$

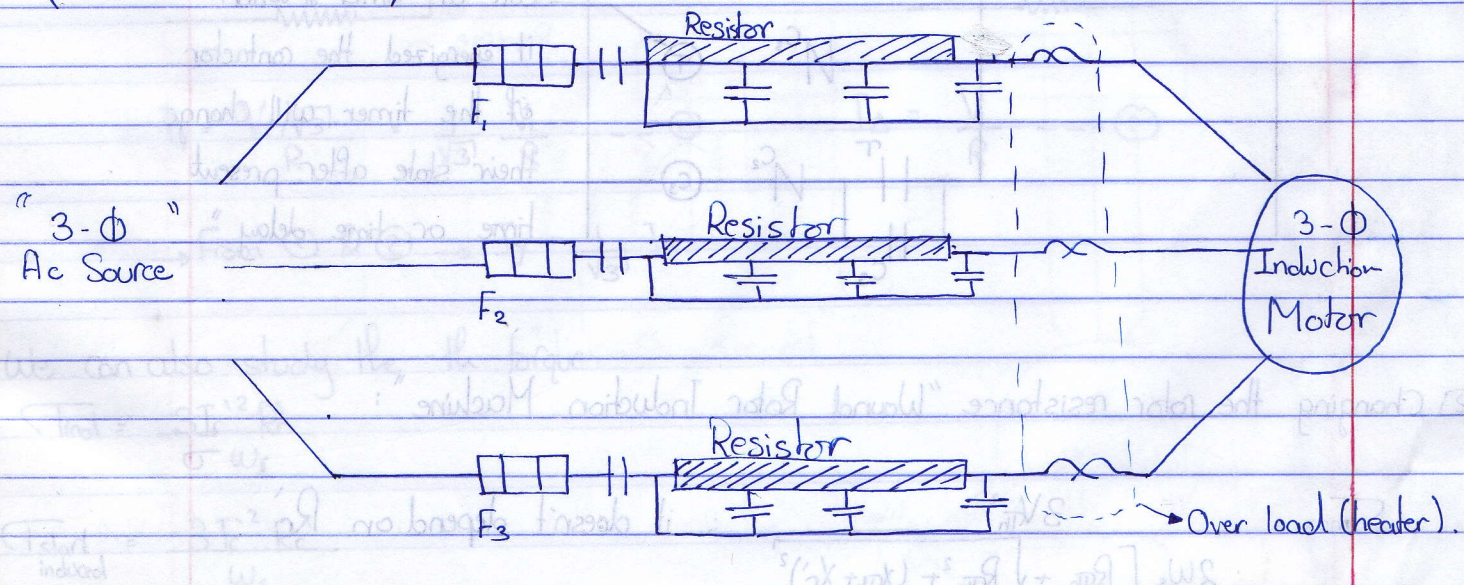

4] Auto-transformer "VARIC"


$$T_{ind} = \frac{3V_{th}^2}{\omega_s [(R_r' + R_{th})^2 + (X_{th} + X_r')^2]} \cdot \frac{R_r'}{\sigma}$$

$$T_{start} \Big|_{\sigma=1} \propto V_{th}^2$$


Fixed AC voltage → Variable AC voltage

$$\sigma_{max} = \frac{R_r'}{\sqrt{R_{th}^2 + (X_{th} + X_r')^2}}$$
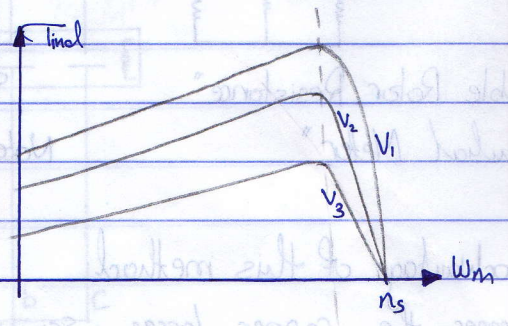
$$T_{max} = \frac{3V_{th}^2}{2\omega_s [R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_r')^2}]}$$




* $V_1 > V_2 > V_3$
 $T_1 > T_2 > T_3$

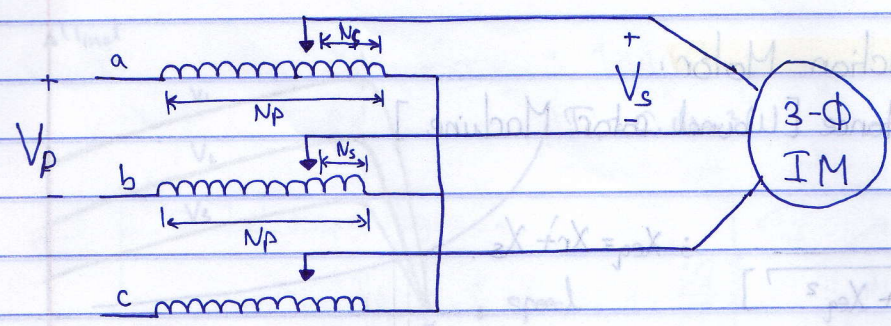

$V_s = V_p \left(\frac{N_s}{N_p} \right) \rightarrow V_s = \frac{V_p}{at}$; at is the turns ratio.

$T_{ind} \propto \frac{1}{at^2}$

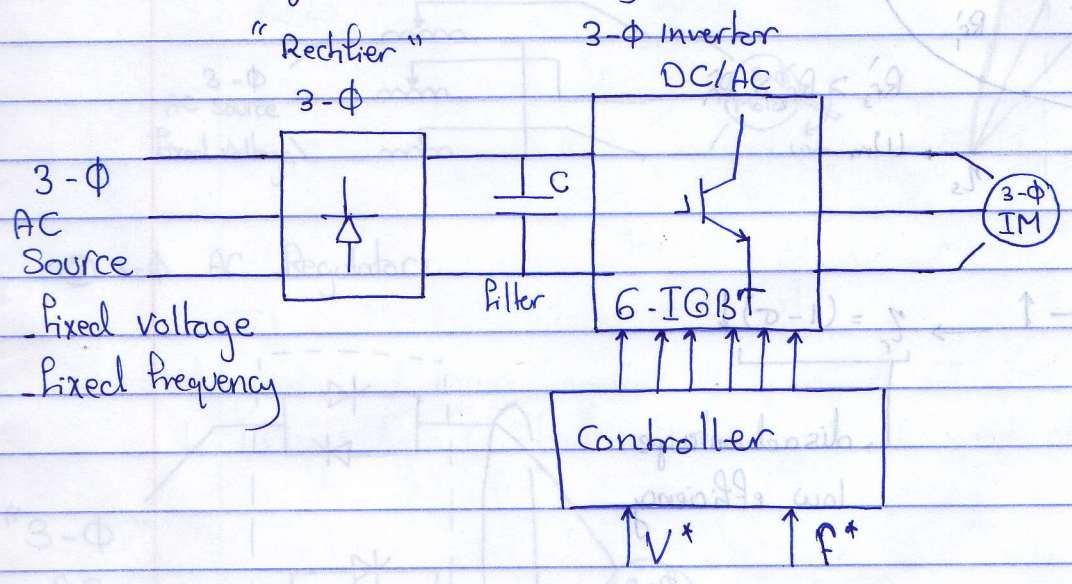5] Variable Voltage variable Frequency Drive: (VVVF)




Flux linkage:

$\lambda_m = L_m I_m = L_m \frac{E}{X_m} = \frac{E}{\omega_e}$

Machine Flux $\propto \frac{V}{f}$

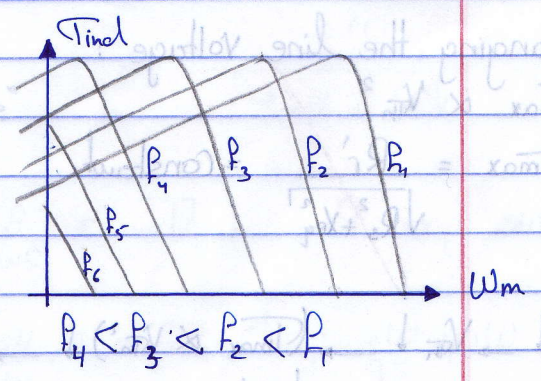The Voltage and Frequency must decrease by the same factor to keep the Flux constant and not let it saturated.





$T_{max} = \frac{3V_{tn}^2}{2\omega_s \left(R_{tn} + \sqrt{(X_{tn} + X_r')^2 + R_{tn}^2} \right)}$

Speed control of induction Motor.


① Changing the rotor resistance [Wound rotor Machine]

$$T_{max} = \frac{3 V_{in}^2}{2 W_s [R_s + \sqrt{R_s^2 + X_{eq}^2}]} ; X_{eq} = X_r + X_s$$
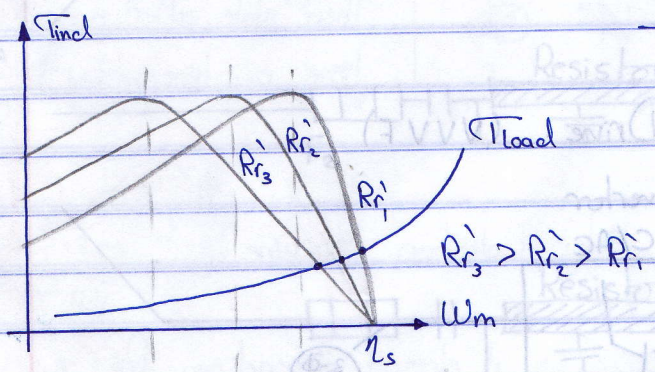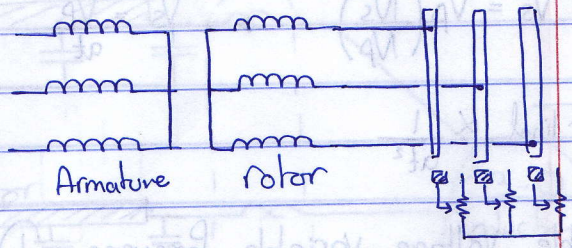
$$\sigma_{max} = \frac{R_r'}{\sqrt{R_s^2 + X_{eq}^2}}$$



Tmax is constant.

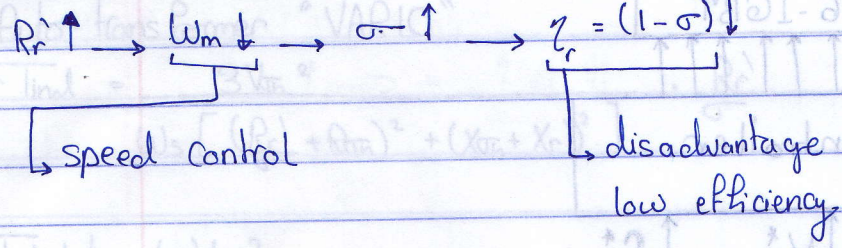



- * Using variable resistor
- Using power Converter

② Changing the line voltage:

$$T_{max} \propto V_{in}^2$$
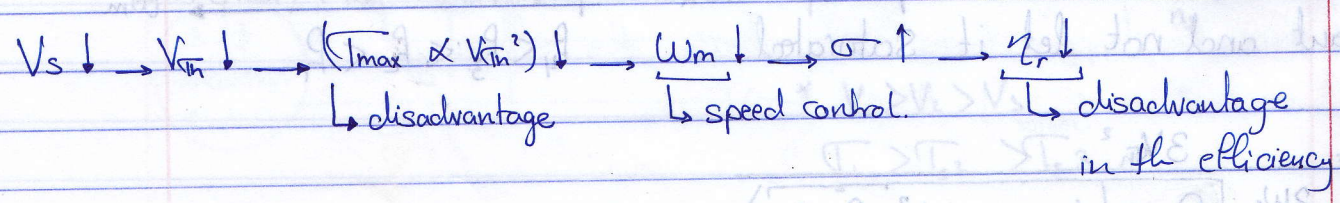
$$\sigma_{max} = \frac{R_r'}{\sqrt{R_s^2 + X_{eq}^2}} = \text{Constant.}$$




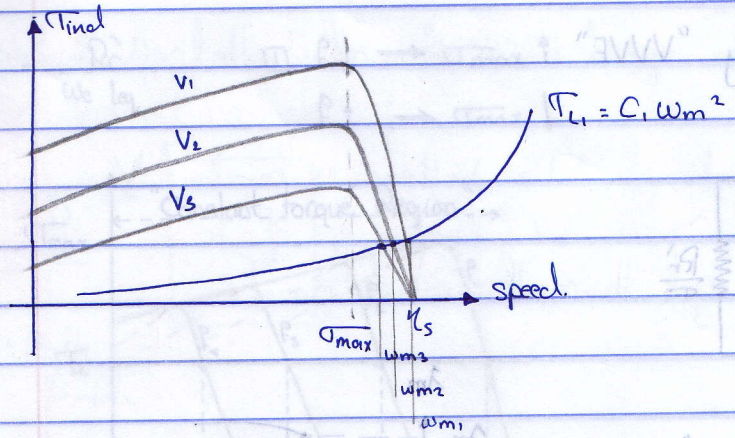


$V_1 > V_2 > V_3 \rightarrow \omega_{m1} > \omega_{m2} > \omega_{m3}$

Note: Methods to change the motor voltage:

① Auto-transformer: (VARIAC)

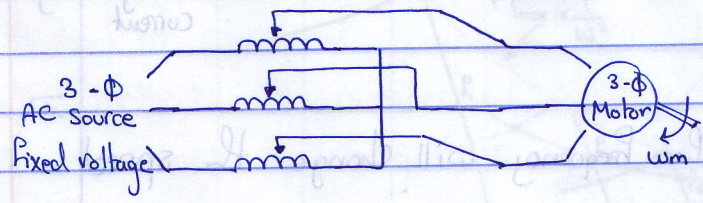


② 3-φ AC Regulator:

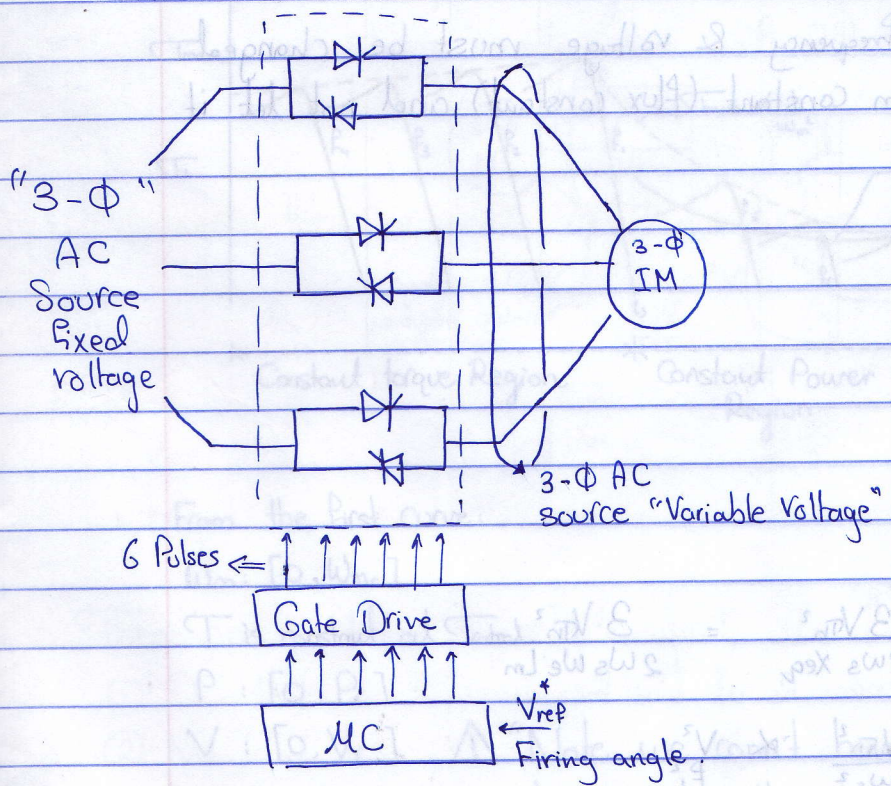

* The Note ends here

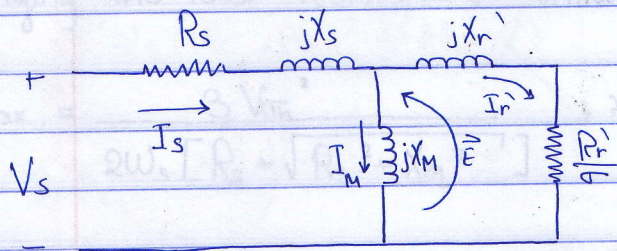
③ Variable Voltage Variable Frequency "VVVF" :



Flux linkage : $\lambda_m = L_m I_m$

$$\lambda_m = L_m \left(\frac{E}{X_m} \right) = L_m \frac{E}{\omega_e L_m} = \frac{E}{\omega_e}$$
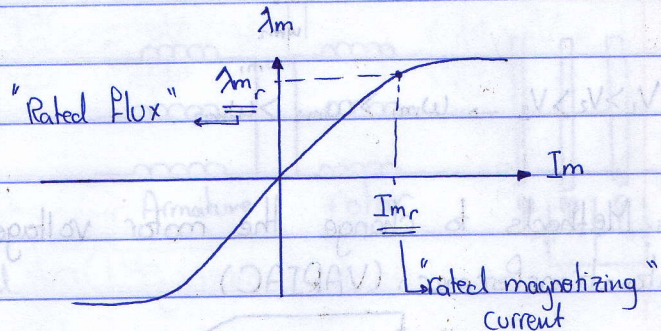
$$\lambda_m = \frac{E}{\omega_e} = \frac{E}{2\pi f_e}$$



Recall : $\gamma_s = \frac{120}{p} f_e$, so changing the frequency will change the speed.

$$\lambda_m = \frac{E}{2\pi f_e} \sim \frac{V_s}{2\pi f_e} \rightarrow \lambda_m \propto \frac{V_s}{f_e}$$

When $\omega_m < \text{rated speed}$ → The frequency & voltage must be changed by the same factor to keep λ_m constant (Flux constant) and not let it saturated.

$$T_{max} = \frac{3 V_{tn}^2}{2 \omega_s [R_s + \sqrt{R_s^2 + X_{eq}^2}]}$$

$$\sigma_{max} = \frac{R_r'}{\sqrt{R_s^2 + X_{eq}^2}}$$

If we ignore R_s → $T_{max} = \frac{3 V_{tn}^2}{2 \omega_s X_{eq}} = \frac{3 V_{tn}^2}{2 \omega_s \omega_e L_m}$

but : $\omega_e = \frac{\omega_s}{2p}$ → $T_{max} \propto \frac{V_{tn}^2}{\omega_s^2} \propto \frac{V^2}{f^2}$