

## Solving the last 10 questions of Chapter 6: Induction Motors.

\* The distinguishing feature of induction motor is that no DC field current is required to run the machine.

### → The construction of the induction motor

It has the same stator construction of synchronous motor with different rotor construction.

The induction motor has two rotor types:

1) The squirrel cage rotor.

2) The wound rotor.

### → Explanation of the two rotor types:

#### ① The cage rotor:


It consists of series conducting bars laid into slots carved in the face of the rotor and shorted at either end by large shorting rings.

#### ② The wound rotor:

It consists of a set of three-phase windings, that are mirror images of the windings of the stator. The windings are usually Y-connected.

The terminals a, b & c are tied to the slip-rings on the rotor's shaft.

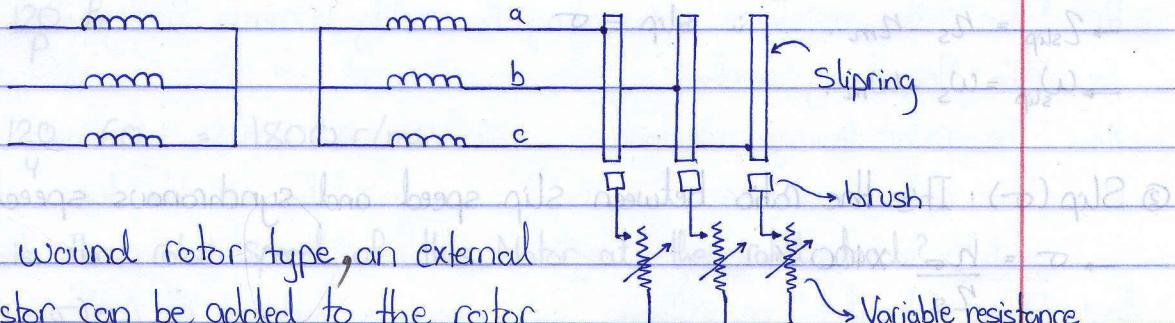The rotor windings are shorted via brushes riding on the sliprings.



Note: In wound rotor type, an external resistor can be added to the rotor circuit to modify the torque-speed characteristics.

② The wound rotor is more expensive and requires much more maintenance.

## Operating principle of induction motor

A set of 3-Φ voltages is applied to the stator windings and a set of 3-Φ stator currents is flowing.

The currents will produce a rotating magnetic field which rotates at synchronous speed ( $\nu_s$ ) where  $\nu_s$  is given by:

$$\nu_s = 120 f_e \quad : f_e \text{ is the system freq in hertz.}$$

The rotating magnetic field will pass over the rotor conducting bars and induce voltages on them by the relation:

$$e_{ind} = (V \times B) \cdot l$$

$\therefore V$  is the velocity of the bar relative to the magnetic field  $B_s$ .

The induced voltages will produce a rotor current  $I_r$ .

The rotor current  $I_r$  produces a rotor magnetic field  $\vec{B}_r$ .

Now the rotor magnetic field  $\vec{B}_r$  interacts with the stator magnetic field  $\vec{B}_s$  to produce the induced torque in the machine.

$$T_{ind} = k \vec{B}_r \times \vec{B}_s$$

Note: The rotor can speed-up to synchronous speed but it can never reach it.

## The Concept of Rotor Slip:

Two terms are commonly used to define the relative motion of the rotor and the magnetic fields:

① Slip speed: It's the difference between the synchronous speed & rotor speed.

$$\rightarrow \nu_{slip} = \nu_s - \nu_m \quad : \text{slip} \equiv \sigma$$

$$\rightarrow \omega_{slip} = \omega_s - \omega_m$$

② Slip ( $\sigma$ ): It's the ratio between slip speed and synchronous speed.

$$\rightarrow \sigma = \frac{\nu_{slip}}{\nu_s} \times 100\%$$

$$\rightarrow \sigma = \frac{\nu_s - \nu_m}{\nu_s} \times 100\%$$

$$\rightarrow \sigma = \frac{\omega_s - \omega_m}{\omega_s} \times 100\%$$

[3]

Solving the last equation for  $\eta_m$ :

$$\rightarrow \eta_m = (1 - \sigma) \eta_s .$$

$$\rightarrow \omega_m = (1 - \sigma) \omega_s .$$

Notice that if the rotor is rotating at  $\eta_s$  then ( $\sigma = 0$ ), while if it is locked ( $\eta_m = 0$ ) then ( $\sigma = 1$ ).

→ The Electric Frequency on the rotor:

If the rotor is locked ( $\eta_m = 0 \Leftrightarrow \sigma = 1$ ), then it will have the same frequency as the stator. ( $f_r = f_s = f_e$ )

On the other hand, when the rotor turns at synchronous speed ( $\eta_m = \eta_s \Leftrightarrow \sigma = 0$ ), then the rotor frequency will be zero ( $f_r = 0$ ).

At any other speed between  $0 \& \eta_s$  the rotor's frequency is directly proportional to the slip ( $\sigma$ ).

$$\rightarrow f_r = \sigma f_e$$

$$\rightarrow f_r = \frac{P}{120} (\eta_s - \eta_m)$$

→ Example:

A 208 V, 10-hp, 4-pole, 60-Hz, Y-connected IM has a full load slip of 5%.

a) What is the synchronous speed of this Motor?

$$\eta_s = \frac{120}{P} f_e$$

$$= \frac{120}{4} \cdot 60 = 1800 \text{ r/min.}$$

b) What is the rotor speed of this Motor at the rated load?

$$\eta_m = (1 - \sigma) \eta_s$$

$$= (1 - 0.05)(1800)$$

$$= 1710 \text{ rpm.}$$

c) What is the rotor frequency of this motor at the rated load?

$$f_r = \sigma f_e$$

$$= 0.05 (60)$$

$$= 3 \text{ Hz}$$

d) What is the shaft torque of this motor at the rated load?

$$P_{\text{out}} = T_{\text{load}} \cdot \omega_m$$


$$T_{\text{load}} = P_{\text{out}} / \omega_m$$

$$= (10 \text{ hp}) (746) / (1710) \cdot (2\pi/60)$$

$$= 41.7 \text{ N.m}$$
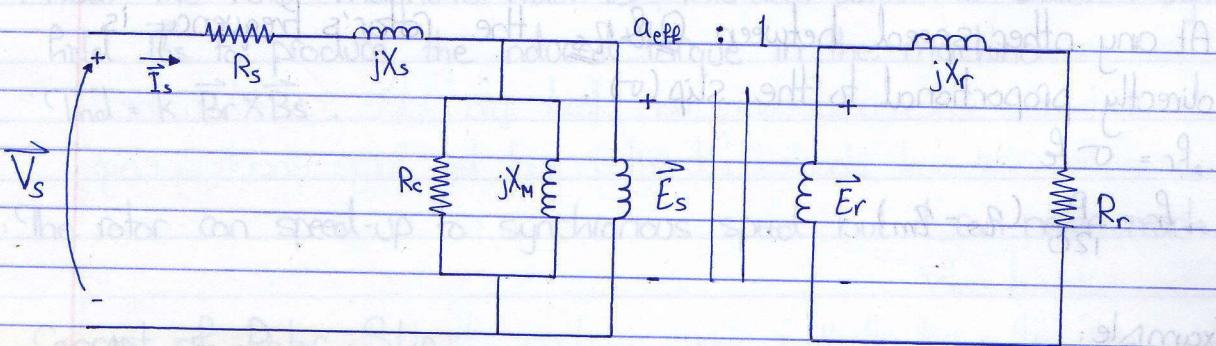
### The Equivalent circuit of an Induction Motor

It is very similar to the per-phase equivalent circuit of the transformer.



$R_s$ : The stator resistance.

$X_s$ : The stator leakage reactance.

$R_c$ : The core resistance accounting for eddy currents & hysteresis.

$X_m$ : The Magnetizing reactance.

$X_r$ : The rotor leakage reactance.

$R_r$ : The rotor resistance, for the windings in (wound), bars in (cage).

\*  $a_{\text{eff}}$ : The effective turns ratio of

the motor which couples between  $\vec{E}_s$  &  $\vec{E}_r$ .

$E_s$ : The internal stator voltage.

Note:  $a_{\text{eff}}$  is fairly easy to

determine for the wound-rotor motor.


$E_r$ : The induced rotor voltage.

$I_s$ : The stator (source) current.

$I_r$ : The rotor current.

$V_s$ : The stator (source) phase voltage.

Rotor circuit model:

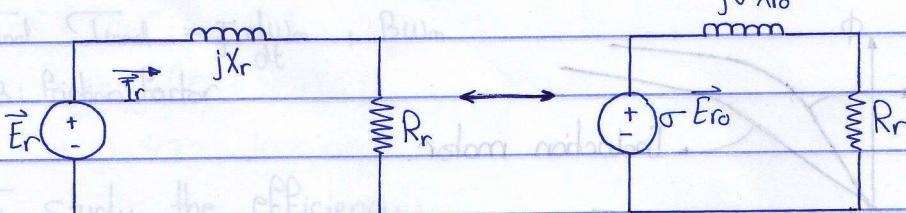

In general, the greater the relative motion between the rotor & the stator magnetic fields, the greater the resulting rotor voltage & rotor frequency.

The largest relative motion occurs when the rotor is locked,

$\sigma = 1$  and  $\vec{E}_r = 1 \cdot \vec{E}_o$  "The largest rotor Voltage".

$f_r = 1 \cdot f_e$  "The largest rotor Frequency".

When the rotor moves at the same speed as the stator magnetic field, resulting in no relative motion,

$\sigma = 0$  and  $\vec{E}_r = 0$  "The smallest rotor Voltage".

$f_r = 0$  "The smallest rotor Frequency".

At any other speed, the voltage and frequency of the rotor is directly proportional to the slip of the rotor.

$$\vec{E}_r = \sigma \vec{E}_o$$

$$f_r = \sigma f_e$$

The reactance of an induction motor rotor depends on the inductance of the rotor and its voltage frequency:


$$X_r = \omega_r L_r = 2\pi f_r L_r$$

So, since  $f_r = \sigma f_e$


$$X_r = 2\pi(\sigma f_e) L_r, \quad X_r = \sigma X_o$$

at the locked rotor state  $X_o = 2\pi f_e L_r$

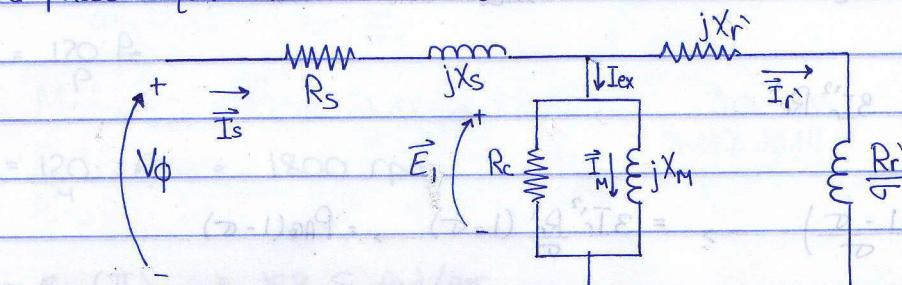The per-phase equivalent circuit of an induction motor.


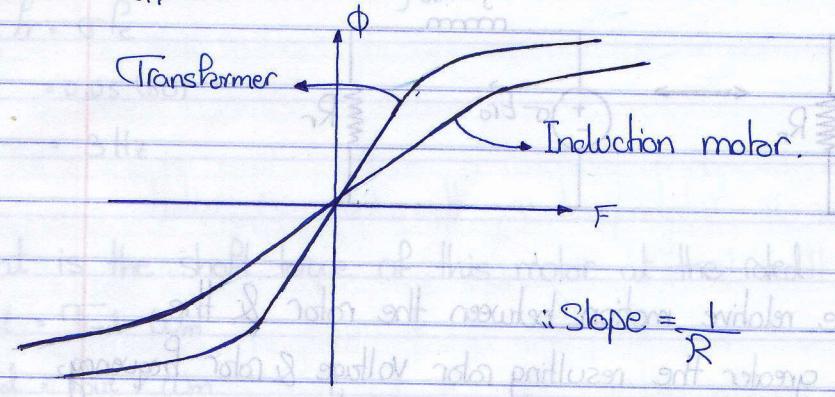
$$\therefore \vec{I}_r' = \frac{1}{\alpha_{eff}} \vec{I}_r \quad \therefore X_r' = \alpha_{eff}^2 X_r \quad \therefore R_r' = \alpha_{eff}^2 R_r \quad \therefore \vec{E}_i' = \alpha_{eff} \vec{E}_i$$




### → Power Calculations:

$$P_{in} = 3V_\phi I_\phi \cos\theta$$

$$P_{AG} = \text{Air Gap Power}$$

$$P_{conv} = T_{ind} \cdot W_m$$

$$P_{out} = T_{mach} \cdot W_m$$

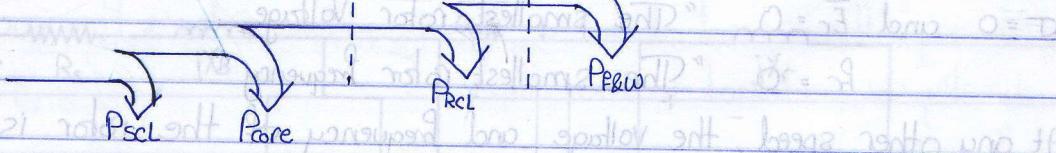

→  $P_{scl}$ : Stator copper losses.

$$= 3 I_s^2 R_s \quad \textcircled{1}$$

→  $P_{few}$ : Friction & Windage losses.

→  $P_{conv}$ : Converted power to Mechanical.

→  $P_{AG}$ : Air Gap power consumed in " $R'_r$ ".

→  $P_{core}$ : Core losses.

$$= 3 E_i^2 / R_c \quad \textcircled{2}$$

→  $P_{rcl}$ : Rotor copper losses.

$$= 3 I_r'^2 R_r' \quad \textcircled{3}$$

→  $P_{AG}$ : Air Gap power

$$= 3 I_r'^2 \frac{R_r'}{\sigma} \quad \textcircled{4}$$

From the power flow diagram:

$$1) P_{AG} = P_{in} - P_{scl} - P_{core}$$

$$2) P_{conv} = P_{AG} - P_{rcl}$$

$$= 3 I_r'^2 \frac{R_r'}{\sigma} - 3 I_r'^2 R_r'$$

$$P_{conv} = 3 I_r'^2 R_r' \left( \frac{1-\sigma}{\sigma} \right) \rightarrow = 3 I_r'^2 \frac{R_r'}{\sigma} (1-\sigma) \rightarrow = P_{AG}(1-\sigma)$$

Now from Newton's second law:

$$T_{ind} - T_{load} = \int \frac{dW_m}{dt} + B_w m$$

$B$ : friction factor.

To study the efficiency:

① Power efficiency:

$$\eta_r = \frac{P_{conv}}{P_{AG}} = (1 - \sigma)$$

② Motor efficiency:

$$\eta_M = \frac{P_{out}}{P_{in}}$$

Induced Torque:

$$P_{conv} = T_{ind} W_m$$

$$\therefore W_m = (1 - \sigma) W_s$$

$$P_{conv} = (1 - \sigma) P_{AG}$$

$$T_{ind} = \frac{P_{AG}}{W_s} \rightarrow T_{ind} = \frac{3\pi r^2 R_c}{\sigma W_s} I^2$$

Example:

A 460-V, 25-hp, 60-Hz, 4-pole, Y-connected induction motor has the following impedances in Ohms per phase referred to the stator circuit:

$$R_s = 0.641 \Omega \quad R_r' = 0.332 \Omega \quad X_m = 26.3 \Omega$$

$$X_s = 1.106 \Omega \quad X_r' = 0.464 \Omega$$

The total rotational losses are 100 W and are assumed to be constant.

The core losses are lumped in with the rotational losses.

For a rotor slip of 2.2% at the rated voltage & rated frequency:

Find:

a) The Motor's Speed:

$$\eta_s = \frac{120 f_e}{P}$$

$$= \frac{120}{4} \cdot 60 = 1800 \text{ rpm.}$$


$$W_s = \eta_s \left( \frac{\pi}{30} \right) = 188.5 \text{ rad/sec.}$$

\* To Find the Motor's speed ( $\nu_m$ )

$$\begin{aligned}\nu_m &= (1 - \sigma) \nu_s \\ &= (1 - 0.022)(1800) \\ &= 1760 \text{ rpm.}\end{aligned}$$

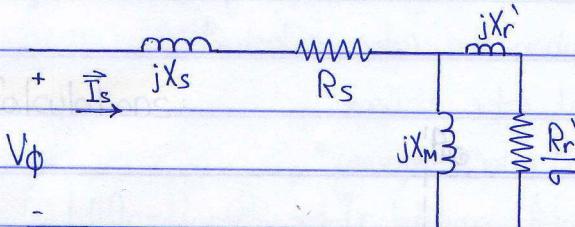b) The Motor's stator current:

To find the stator current we should get the equivalent impedance of the circuit:



To find  $R_{eq}$ :

$$jX_m // (jX_r' + R_r')$$

$$\therefore jX_m = 26.3j$$

$$jX_r' + \frac{R_r'}{j} = 0.464j + \frac{0.332}{0.022} \Rightarrow 15.1 \times 1.76^\circ \quad \rightarrow (26.3j // (15.1 \times 1.76^\circ))$$

$$R_{eq} \rightarrow \frac{1}{\frac{1}{26.3j} + \frac{1}{15.1 \times 1.76^\circ}} = 12.92 \angle 31.2^\circ$$

$$2) jX_s + R_s + R_{eq}$$

$$= 1.106j + 0.641 + 12.92 \times 31.2^\circ$$

$$= 14.06 \times 33.7^\circ$$

Then find  $V_\phi$ :

$$V_L = \sqrt{3} V_\phi \rightarrow V_\phi = \frac{V_L}{\sqrt{3}} = \frac{208}{\sqrt{3}} \angle 46^\circ = 266 \times 0^\circ \text{ V}$$

Now the current:

$$\vec{I}_s = \frac{V_\phi \angle 0^\circ}{Z_{eq}} = \frac{266 \times 0^\circ}{14.06 \times 33.7^\circ} = 18.88 \times -33.7^\circ \text{ A}$$

c) The Motor's PF:

$$PF = \cos^*(\theta_v - \theta_i)$$

$$= \cos^*(0 + 33.7)$$

$$= 0.832 \text{ lagging}$$

d) The Motor's  $P_{conv}$  &  $P_{out}$ :

i.  $P_{conv} = (1 - \sigma) P_{AG}$ , so we need to find  $P_{AG}$ :

$$P_{AG} = P_{in} - P_{SCL}$$

$$\therefore P_{in} = 3V\phi I\phi \cos\theta$$

$$= 3(266)(18.88)(0.832)$$

$$= 12.53 \text{ kW}$$

$$P_{SCL} = 3I_s^2 R_s$$

$$= 3(18.88)^2 (0.641)$$

$$= 0.685 \text{ kW}$$

$$P_{AG} = (12.53k - 0.685k)W$$

$$= 11.845 \text{ kW}$$

$$P_{conv} = (1 - 0.022)(11.845k)$$

$$= 11.585 \text{ kW}$$

ii.  $P_{out} = P_{conv} - P_{friction}$

$$= (11.585 k - 1.1k)W$$

$$= 10.485 \text{ kW}$$

e)  $T_{ind}$  &  $T_{load}$  for the Motor:

$$i. T_{ind} = \frac{P_{conv}}{\omega_m} \Rightarrow \frac{11585}{1800 \cdot \frac{\pi}{30}} = 62.8 \text{ N.m}$$


$$ii. T_{load} = \frac{P_{out}}{\omega_m} \Rightarrow \frac{10.485k}{1760(\frac{\pi}{30})} = 56.9 \text{ N.m}$$

f) The Motor's efficiency:

$$\eta_s = \frac{P_{out}}{P_{in}} \times 100\%$$

$$= \frac{10485}{12530} \times 100\% = 83.7\%$$


→ Derivation of induced torque equation:

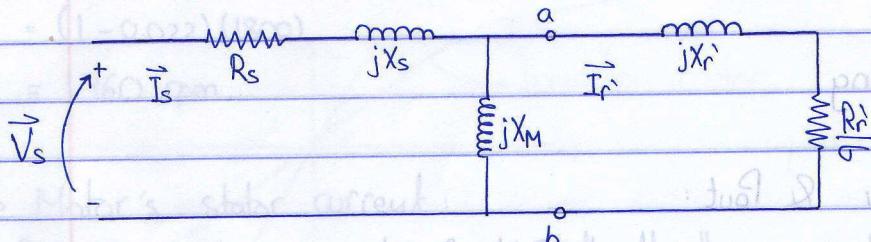

$$T_{ind} = P_{AC} = \frac{3I_r'^2 R_r'}{\sigma w_s} \quad \because I_r' \text{ is the magnitude of the current.}$$

From the equation it's clear that we need  $I_r'$  to calculate the  $T_{ind}$ , but in fact there is no access on the rotor so its difficult to find it.

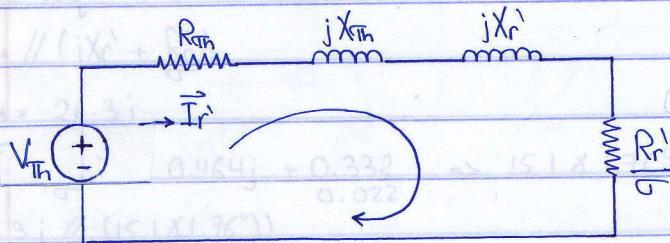The solution is to get the thevinin of the stator part from points (a, b).



$$\textcircled{1} \quad \vec{V}_{Th} = \vec{V}_{oc} = \frac{jX_M}{R_s + j(X_s + X_M)} \vec{V}_s$$

$$Z_{Th} = R_s \frac{X_M}{X_s + X_M} + j \frac{X_s X_M}{X_s + X_M}$$

$$\because X_M + X_s \gg R_s$$

$$R_{Th} = R_s \frac{X_M}{X_s + X_M} \quad \textcircled{2}$$

$$\vec{V}_{Th} = \frac{X_M}{(X_s + X_M)} \vec{V}_s \quad \textcircled{1}$$

$$X_{Th} = X_s \frac{X_M}{X_s + X_M} \quad \textcircled{3}$$

$$\textcircled{2} \quad Z_{Th} = (R_s + jX_s) // jX_M$$

$$= \frac{(R_s + jX_s)(jX_M)}{R_s + j(X_s + X_M)}$$

$$\because X_M + X_s \gg R_s$$

$$Z_{Th} = \frac{(R_s + jX_s)(X_M)}{(X_s + X_M)}$$

(II)

To find  $\vec{I}_r'$ : the Induction Motor

$$\vec{I}_r' = \frac{\vec{V}_{Th}}{(R_{Th} + R_r') + j(X_{Th} + X_r')} \text{, but to find the } T_{Ind} \text{ we need the magnitude.}$$

$$|\vec{I}_r'| = \frac{|\vec{V}_{Th}|}{\sqrt{(R_{Th} + R_r')^2 + (X_{Th} + X_r')^2}}$$

$$\text{Now: } T_{Ind} = \frac{3 I_r'^2 R_r'}{\sigma \omega_s}, \text{ substitute } I_r' \text{ in } T_{Ind} \text{ above which is } ③$$

$$T_{Ind} = \frac{3 V_{Th}^2}{\omega_s \left( [R_{Th} + R_r']^2 + [X_{Th} + X_r']^2 \right)}$$

\* Note: In Calculations we can make an approximation in:

$$\frac{X_M}{X_s + X_M} \approx 1 \text{ since } X_M \gg X_s.$$

Therefore,  $R_{Th} \approx R_s$


$$\begin{cases} X_{Th} \approx X_s \\ V_{Th} \approx V_s \end{cases} \rightarrow T_{Ind} = \frac{3 V_s^2}{\omega_s \left( [R_s + R_r']^2 + [X_{Th} + X_r']^2 \right)}$$

### Induction Motor Torque-Speed characteristics:

From the  $T_{Ind}$  equation we can see that the torque is a function of slip, and since the slip is changing by  $\gamma_m$  so it's also a function of  $\gamma_m$ .

$$T_{Ind} = f(\sigma) = g(\gamma_m)$$

$$\gamma_m = (1 - \sigma) \gamma_s$$

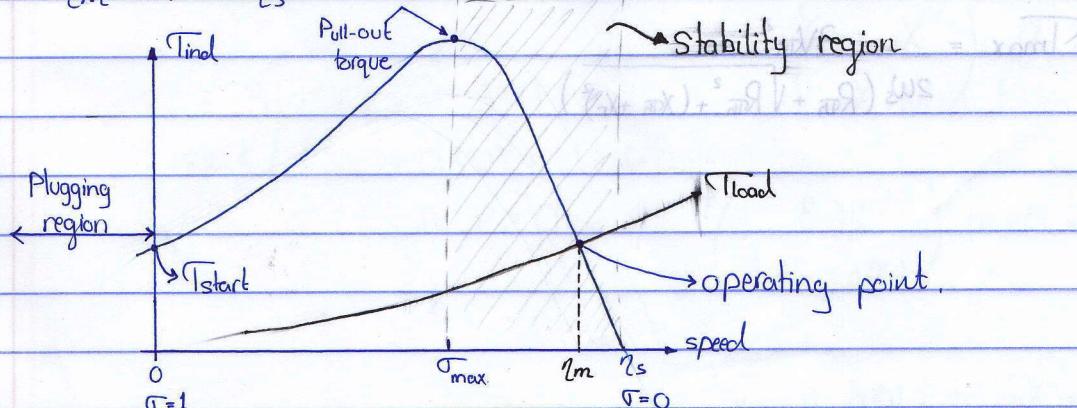

## Notes on the Curve:

- ① When the slip range is very small, the induced torque is approximately proportional to the slip (linear relationships).

$$T_{ind} \approx \frac{3V_{th}^2}{w_s \left(\frac{R_r}{F}\right)^2} \cdot \frac{R_f}{f} \rightarrow T_{ind} \approx \frac{3V_{th}^2}{w_s R_r} \cdot \sigma \rightarrow T_{ind} = K\sigma$$

- ② Under steady state (speed is constant)

From Newton's second law:

$$T_{ind} - T_{load} = \int \frac{dw}{dt} \rightarrow \text{So } T_{ind} = T_{load}.$$

## Plugging Region:

It's used to stop the motor rapidly by switching any two of the three phases.

Starting torque ( $T_{start}$ ) :

It's slightly higher than the motor rated torque.

$T_{\text{pull-out}} = T_{\text{max}}$  : The maximum torque


$$T_{max} = (2-3) T_{rated}$$

To find the maximum torque:


$$\frac{\partial T_{\text{ind}}}{\partial \sigma} = 0 \rightarrow \sigma_{\max} = \frac{Rc'}{\sqrt{R_{\text{Th}}^2 + (X_{\text{Th}} + X_r')^2}}$$

$$T_{max} = \frac{3V_{th}^2}{2U_s \left( R_{th} + \sqrt{R_{th}^2 + (X_{th} + Y_s)^2} \right)}$$

→ In Wound Rotor Induction Motor

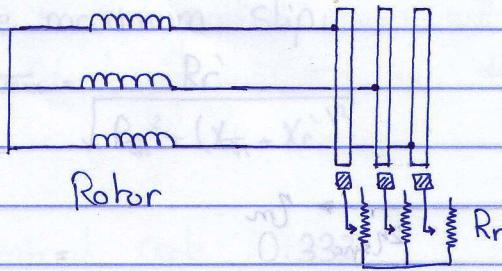

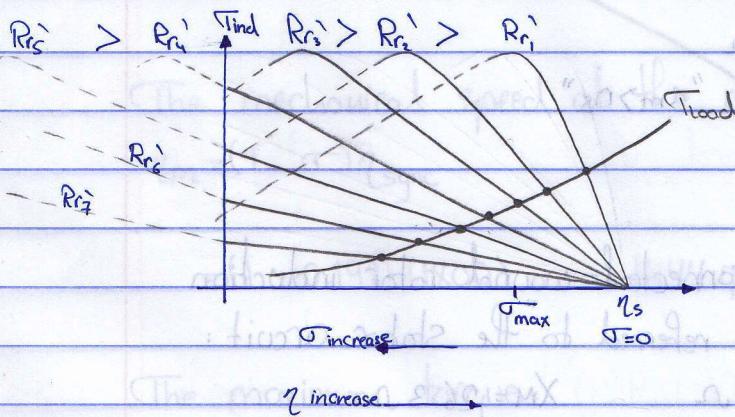\* only in the wound rotor we can change "Rr"



When  $R_r' \leq R_r \leq R_{r_1}'$  → Then  $R_r' \uparrow$  the  $\sigma_{max} \uparrow$  →  $\sigma \uparrow$  →  $\gamma \downarrow$

So  $\gamma_r = (1-\sigma)$  [Rotor efficiency] ↓

and  $\gamma \downarrow$  [Motor efficiency].

and  $T_{start} \uparrow$


when  $R_r > R_{r_1}'$  →  $T_{start} \downarrow \Rightarrow \gamma$  (efficiency) ↓

The Rotor resistance in the wound Rotor Induction Motor is a method to control the speed & the starting torque.

$$182.5 / [(0.59 + 0.33)^2 + (1.06 + 0.46)^2]$$

$$(0.828 - 1.030) / (2.88 + 0.11)$$
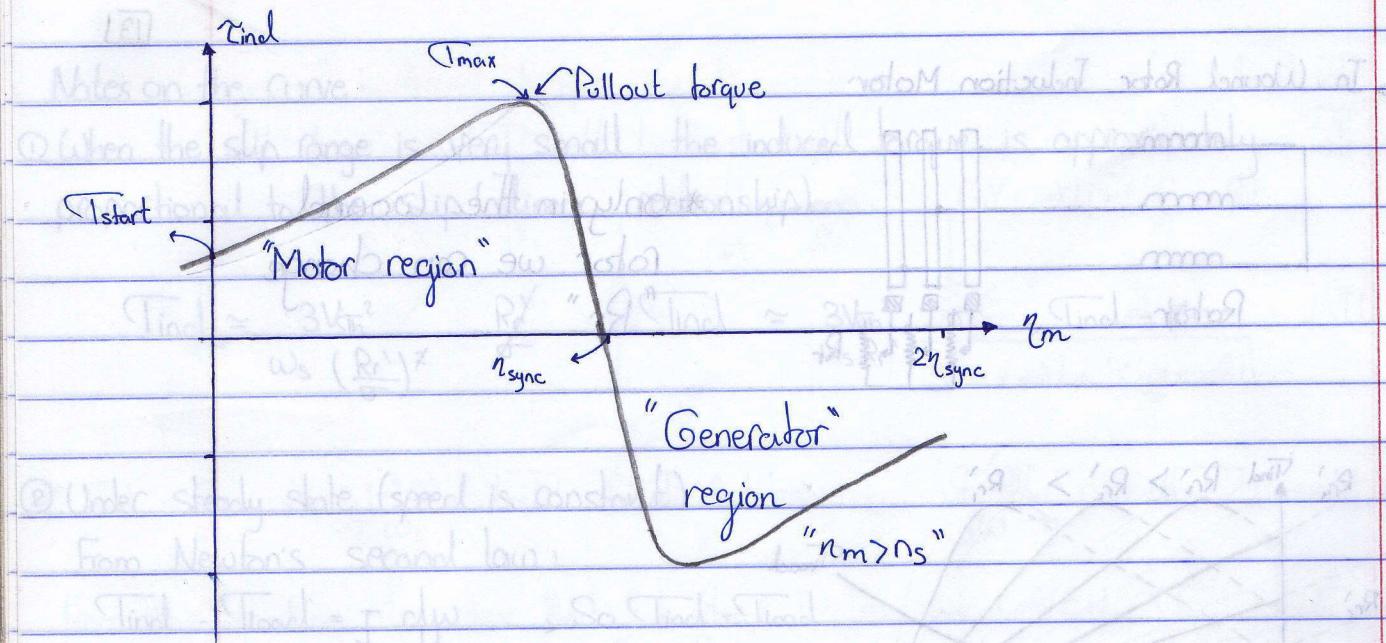
$$0.2011 = \frac{1}{X} = \frac{1}{0.717}$$



Example: A 460-volt, 25-hp, 4-pole, Y-connected wound rotor induction motor has the following impedances referred to the stator circuit:

$$\text{phases } R_s = 0.641 \Omega \quad R_r' = 0.332 \Omega \quad X_M = 26.3 \Omega$$

$$X_s = 1.106 \Omega \quad X_r' = 0.464 \Omega$$

a) What is the maximum torque of this motor? At what speed & slip does it occur?

① Find  $V_{in} = V_\phi \frac{X_m}{\sqrt{R_s^2 + (X_s + X_m)^2}}$

To find the maximum torque:

$$\text{Find current} = 266 \frac{26.3}{\sqrt{(0.641)^2 + (1.106+26.3)^2}} = 255.2 \text{ A}$$

② Find  $R_{in} = R_s \left( \frac{X_m}{X_s + X_m} \right)^2$

$$= 0.641 \left( \frac{26.3}{1.106 + 26.3} \right)^2 = 0.59 \Omega$$

③ Find  $X_{in} = X_r' = 1.106 \Omega$

Now:

The maximum slip:  $\sigma_{\max} = \frac{R_r}{R_m + (X_m + X_r)^2}$  \*Note:  $n_s = \frac{120}{4} \cdot 60 = 1800 \text{ rpm}$

$$\sigma_{\max} = \frac{R_r}{\sqrt{R_m^2 + (X_m + X_r)^2}}$$

$$\sigma_{\max} = \frac{0.332}{\sqrt{(0.59)^2 + (1.106 + 0.464)^2}} = 0.198$$

The mechanical speed at the maximum slip:

$$n_m = (1 - \sigma) n_{sync}$$

$$= (1 - 0.198) (1800) = 1444 \text{ rpm}$$

The maximum torque:

$$T_{max} = \frac{3V_m^2}{2\omega_s} [R_m + \sqrt{R_m^2 + (X_m + X_r)^2}]$$

$$= \frac{3(255.2)^2}{2(188.5)[0.59 + \sqrt{0.59^2 + (1.106 + 0.464)^2}]} = 229 \text{ N.m.}$$

b) What is the starting torque of the motor?

In the torque equation set the  $\sigma$  to  $\frac{1}{2}$  & solve it as  $T_{start}$ :

$$T_{start} = \frac{3V_m^2 R_r}{2\omega_s} [(R_m + R_r)^2 + (X_m + X_r)^2]$$

$$= \frac{3(255.2)^2 (0.332)}{188.5 [(0.59 + 0.332)^2 + (1.106 + 0.464)^2]} = 104 \text{ N.m.}$$

$$= 104 \text{ N.m.}$$

c) When the Rotor resistance is doubled, What is the speed at which the max torque occurred? What is the new starting torque?  
 → If we double the rotor resistance then the  $\sigma$  will be doubled

So

$$\sigma_{max} = 0.396$$

→ The speed at which this slip occurs is:

$$n_m = (1 - \sigma) n_s$$

$$= (1 - 0.396)(1800)$$

$$= 1087 \text{ rpm.}$$

→ The max torque will not be changed.


$$T_{max} = 229 \text{ N.m.}$$

→ The starting torque will change:

$$T_{start} = 3(255.2)^2 (0.664)$$

$$188.5 [(0.59 + 0.664)^2 + (1.106 + 0.464)^2]$$

$$= 170 \text{ N.m}$$

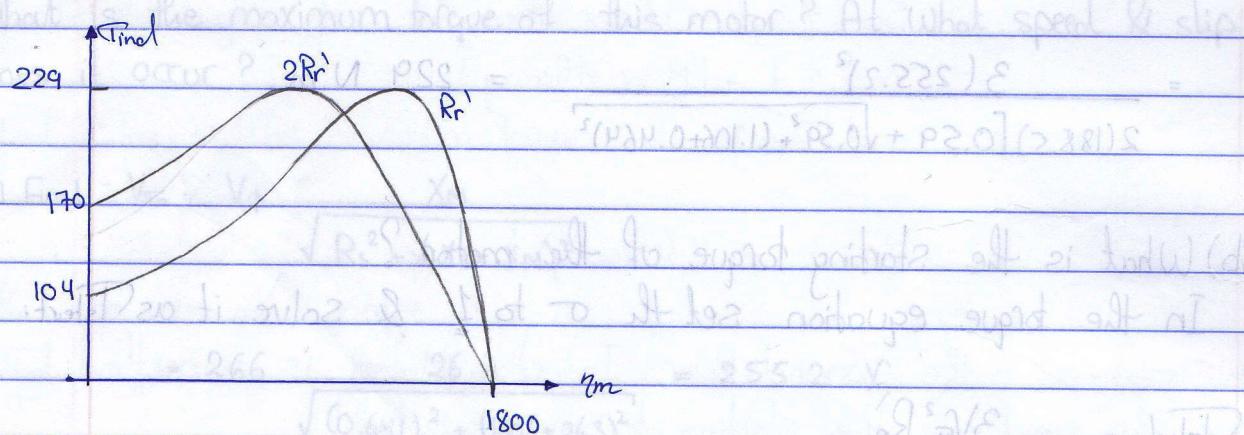

Q1 Find  $R_{rot} = R_s (X_m / X_r)$

$$= 0.664 \left( \frac{26.3}{106.2} \right)^2 = 0.59 \Omega$$

$$[(P2R_0 + 20.1) + (S2E_0 + P2.0)] 2.881$$

$$= 0.664 \left( \frac{26.3}{106.2} \right)^2 = 0.59 \Omega$$

Q3 Find  $X_m = X_r = 1.106 \Omega$

→ Calculations of Motor Starting current:

$$I_{\text{start}} = \frac{S_{\text{start}}}{\sqrt{3} V_L} \quad ; \quad S_{\text{start}} : \text{Rated power (hp)} * \text{"code letter Factor"}$$

Nominal code letter	locked Rotor [KVA/hp]
A	0 - 3.15
B	3.15 - 3.55
C	3.55 - 4.00
D	4.00 - 4.50
E	4.50 - 5.00
F	5.00 - 5.60
:	:

Example:


What's the starting current of a 15 hp, 208 v, code letter F, 3-Φ induction Motor.

$$I_{\text{start}} = \frac{S_{\text{start}}}{\sqrt{3} V_L} = \frac{15(5.6)k}{\sqrt{3}(208)} = 233 \text{ Amp.}$$

→ Relay logic control of 3-Φ induction Motor: (ON-OFF control).


Relay: It is an electromagnetic switch that has a coil and a set of auxiliary contacts.

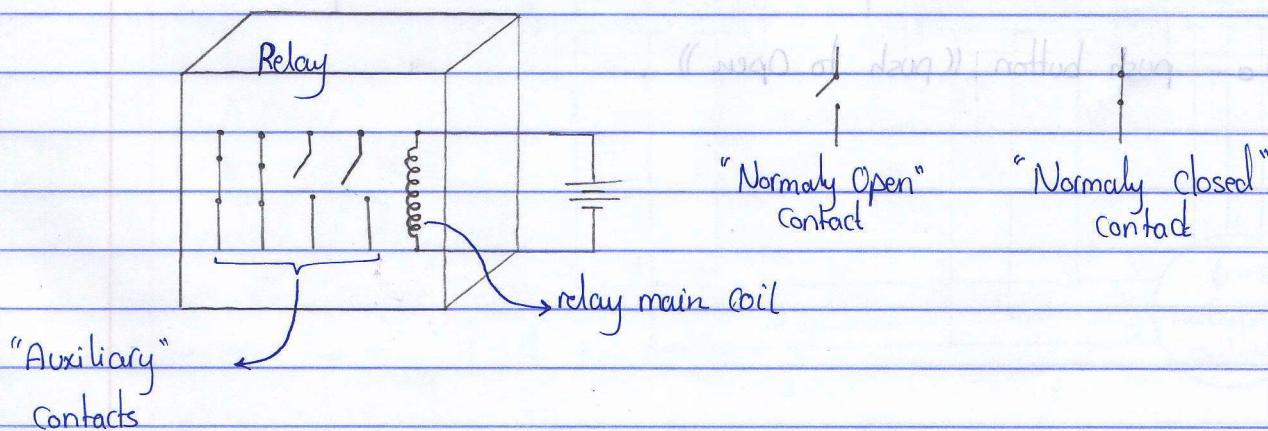The contacts can be either normally open or normally closed



When the main coil is energized, the normally open contact will close & the normally close contact will open.

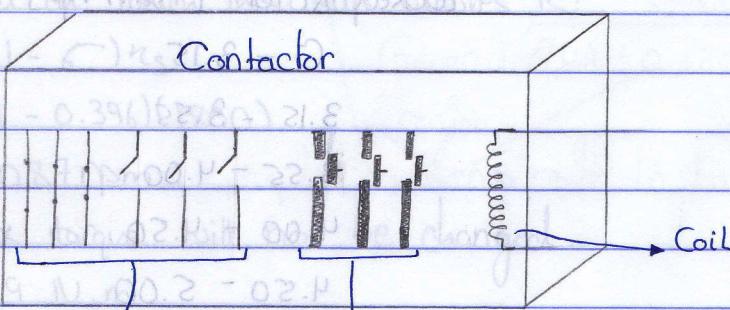**Contactor:** It is an electromagnetic switch that has three main contacts with a set of auxiliary contacts.




The auxiliary contacts can be either normally open or normally closed.


Symbols:

① or coil of relay or contactor.

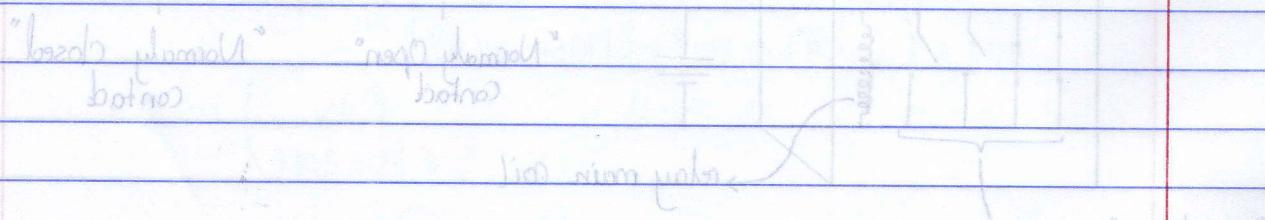- ② Normally Open.
- ③ Normally Closed.
- ④ push button ((push to close)).
- ⑤ push button ((push to open)).




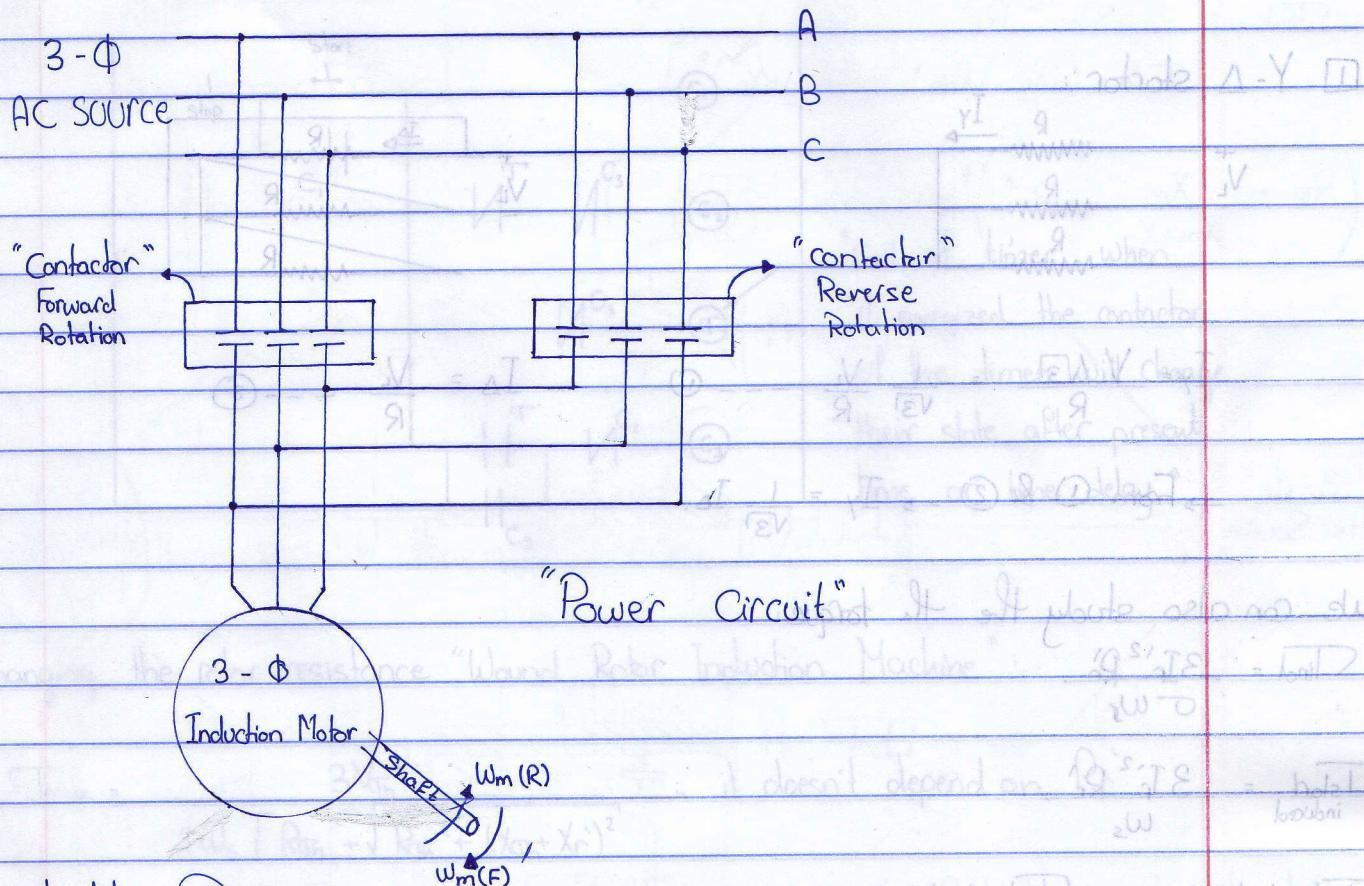Example: Control & power circuits to reverse the direction of motor.





Ladder Diagram:

For the Control Circuit:

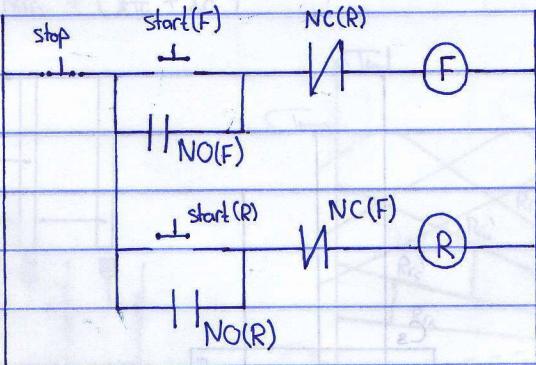

→ Methods to reduce the starting current of the 3-φ induction Motor.

### ① Y-Δ startor:

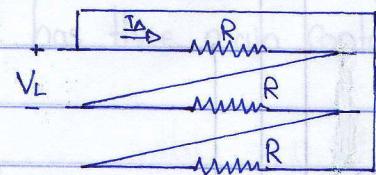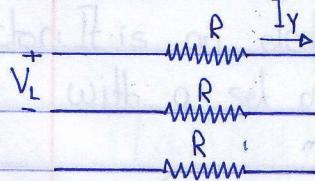

$$I_Y = \frac{V_L / \sqrt{3}}{R} = \frac{1}{\sqrt{3}} \frac{V_L}{R} \quad \textcircled{1}$$

$$I_D = \frac{V_L}{R} \quad \textcircled{2}$$

$$\rightarrow \text{From } \textcircled{1} \text{ & } \textcircled{2} \rightarrow I_Y = \frac{1}{\sqrt{3}} I_D$$


We can also study the torque:

$$T_{ind} = \frac{3 I_r^2 R_r}{\omega_s}$$

$$T_{start, induced} = \frac{3 I_r^2 R_r}{\omega_s}$$


$$T_{ind, start(Y)} = \frac{1}{3} T_{ind, start(\Delta)}$$

The Power circuit:

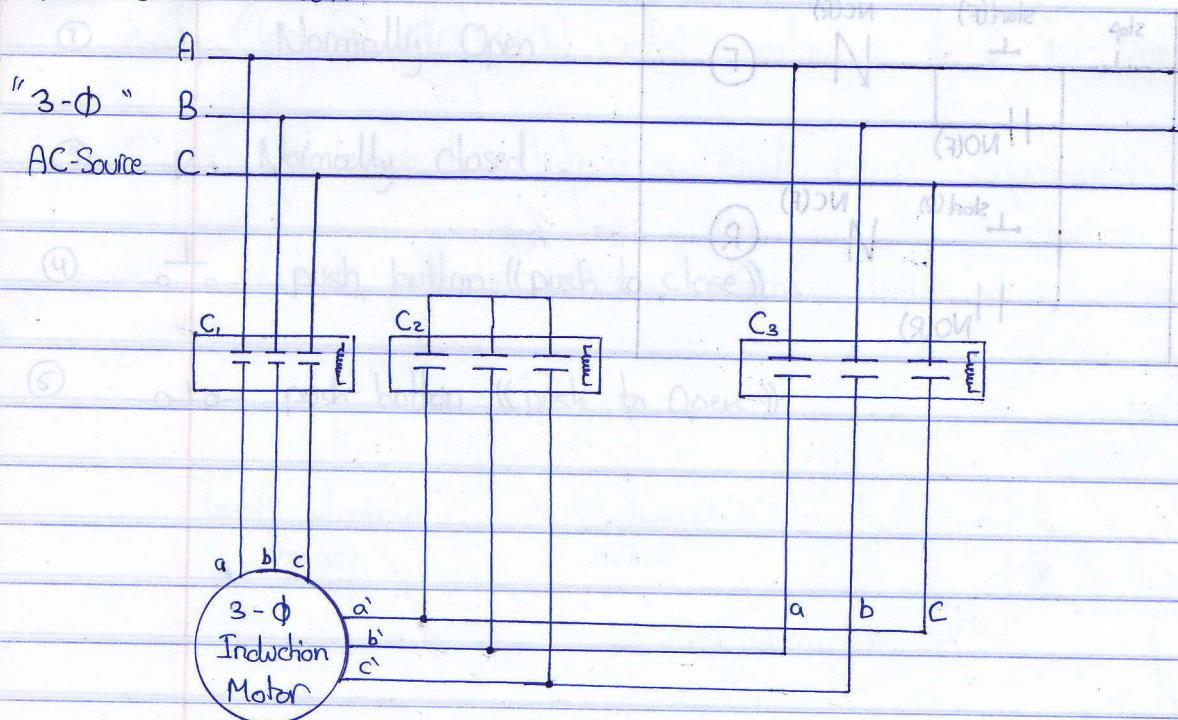

(21)

The Control circuit: For Y-Δ startor.

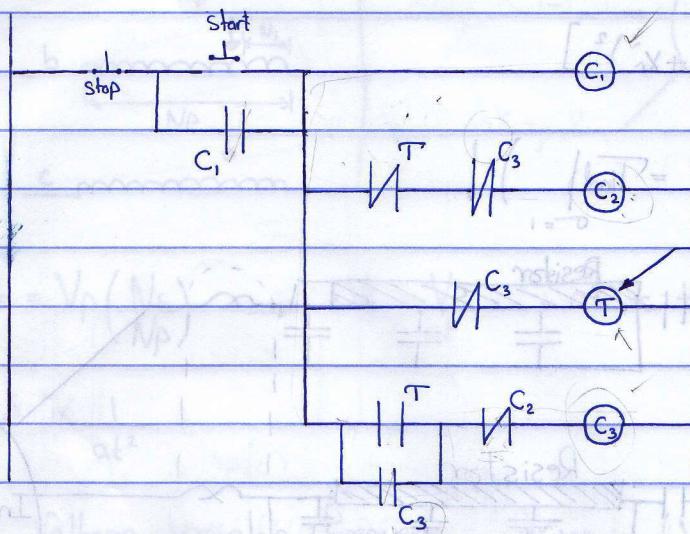


"Coil of timer, when it energized the contactor of the timer will change their state after present time or time delay"

② Changing the rotor resistance "Wound Rotor Induction Machine":


$$T_{max} = \frac{3V_{th}^2}{2\omega_s [R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_r)^2}]} \quad \therefore \text{it doesn't depend on } R_r'$$
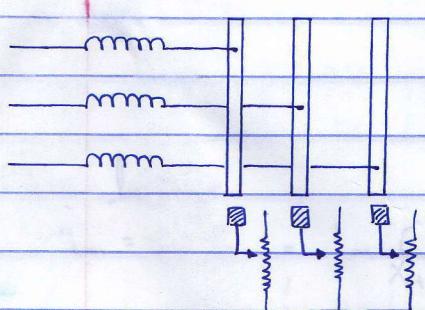
$$\omega_{max} = \frac{R_r'}{R_{th}^2 + (X_{th} + X_r')^2} \quad \therefore \text{if } R_r' \uparrow \Rightarrow \omega_{max} \uparrow$$



"Variable Rotor Resistance"

"Potential Meter"

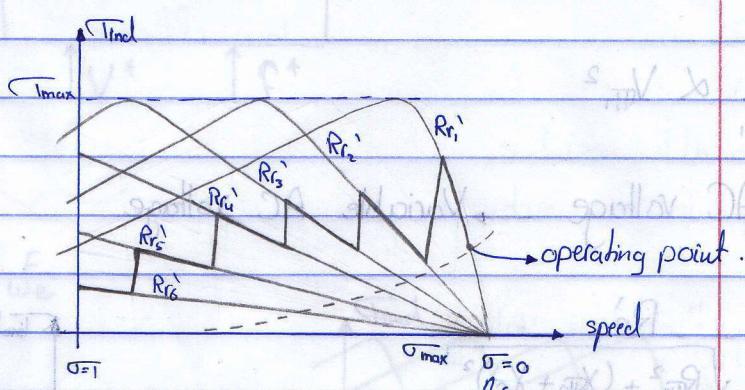

Note:  $\eta_s$  is constant for  $R_r'$  values since  $\eta_s = 120 \text{ p.c.}$

$$Rr_6' > Rr_5' > Rr_4' > Rr_3' > Rr_2' > Rr_1'$$

The disadvantage of this method:


It increases the copper losses so reducing the efficiency

$$R_r' \uparrow \rightarrow P_{cu} \uparrow \rightarrow \eta_{motor} \downarrow \quad \& \quad \eta_r = (1 - \sigma) \downarrow$$
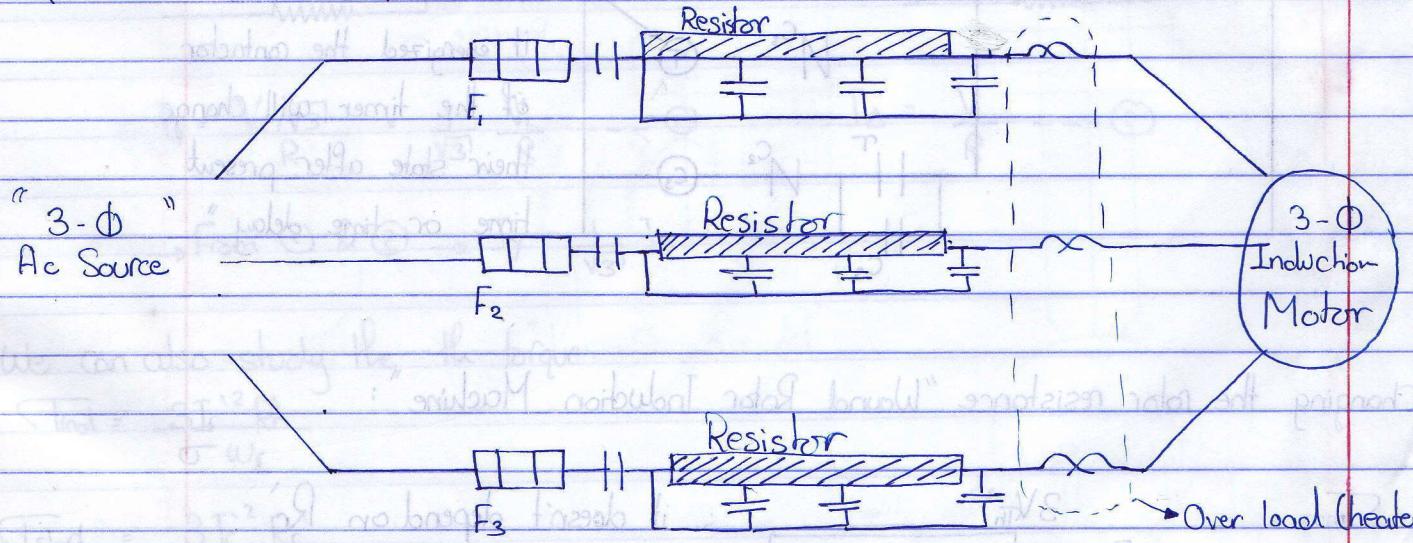
### 3) Stator resistance or inductance stator

$$T_{ind} = \frac{3V_{th}^2 R_r}{\sigma W_s [(R_r' + R_{th})^2 + (X_{th} + X_r)^2]}$$

$$\left( R_{th} \approx \frac{X_m}{X_m + X_s} \cdot R_s \uparrow \right) \Rightarrow \left( T_{start} = T_{ind} \right) \quad \sigma=1$$



### 4) Auto-transformer "VARIC"


$$T_{ind} = \frac{3V_{th}^2}{\sigma W_s} \cdot \frac{R_r'}{\sigma}$$

$$T_{start} \propto V_{th}^2$$

Fixed AC voltage  $\rightarrow$  Variable AC voltage


$$\sigma_{max} = \frac{R_r'}{\sqrt{R_{th}^2 + (X_{th} + X_r)^2}}$$
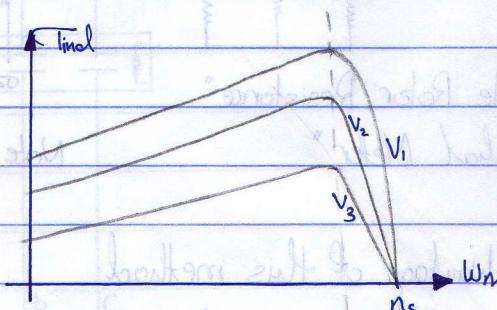
$$\sigma_{max} = \frac{3V_{th}^2}{2W_s [R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_r)^2}]}$$



$$V_1 > V_2 > V_3$$


$$\tau_1 > \tau_2 > \tau_3$$

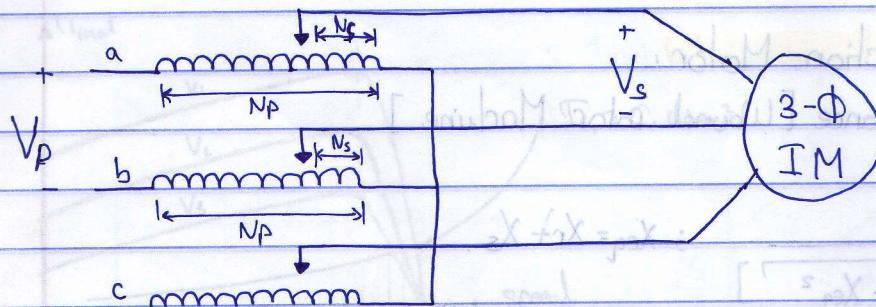

$$V_s = V_p \left( \frac{N_s}{N_p} \right) \rightarrow V_s = \frac{V_p}{at} \quad ; \text{ at is the turns ratio.}$$

$$T_{\text{ind}} \propto \frac{1}{at^2}$$
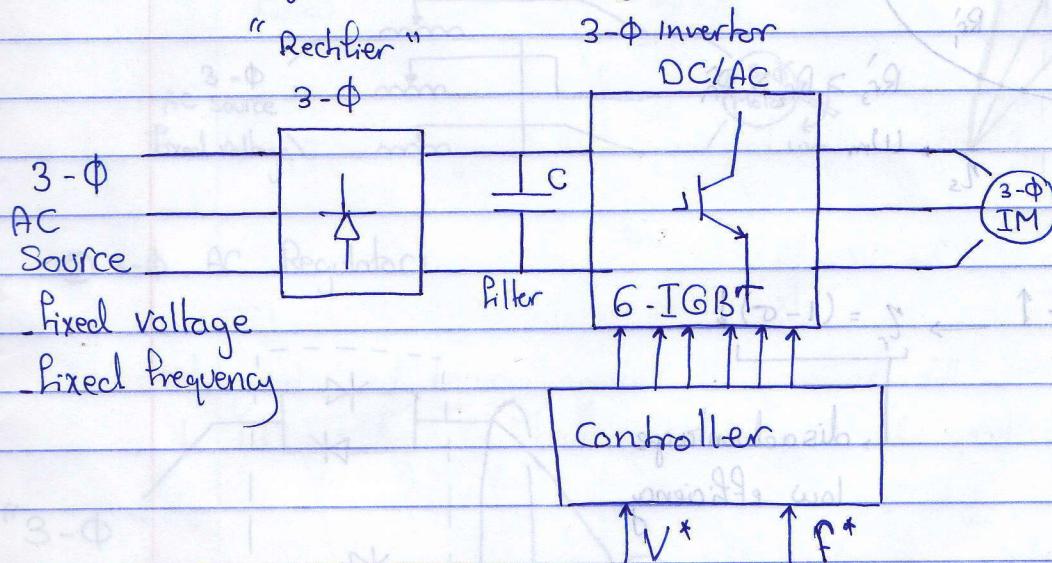
### 5] Variable Voltage Variable Frequency Drive : (VVVF)




Flux linkage :

$$\lambda_m = L_m I_m = L_m \frac{E}{X_m} = \frac{E}{w_m}$$

Machine Flux  $\propto \frac{V}{f}$

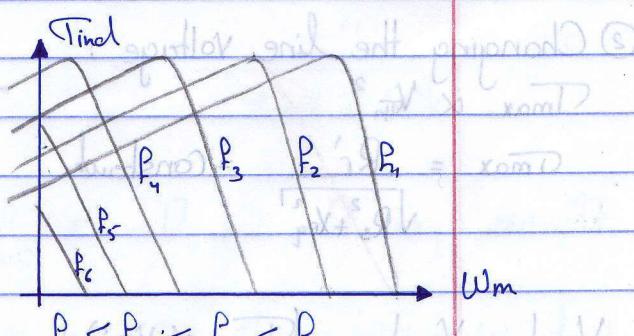The Voltage and Frequency must decrease by the same factor to keep the Flux constant and not let it saturated.





$$T_{\text{max}} = \frac{3V_{thm}^2}{2w_s (R_{thm} + \sqrt{(X_{thm} + X_r)^2 + R_{thm}^2})}$$

## Speed control of induction Motor.
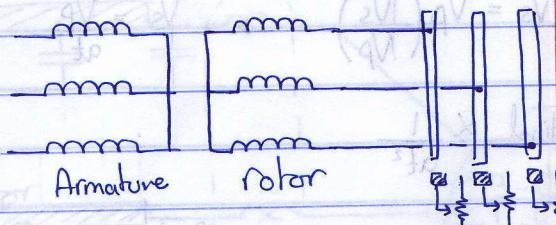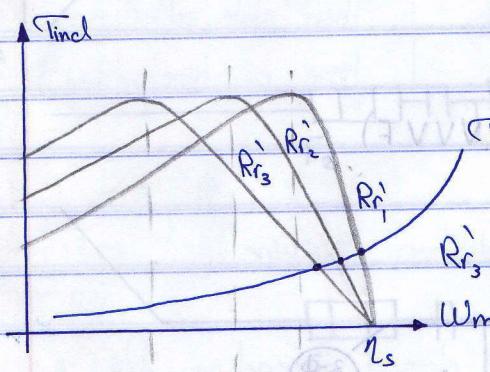
### ① Changing the rotor resistance [Wound rotor Machine]

$$T_{max} = \frac{3 V_m^2}{2 \omega_s [R_s + \sqrt{R_s^2 + X_{eq}^2}]} ; X_{eq} = R_r + X_s$$

$$\omega_{max} = \frac{R_r'}{\sqrt{R_s^2 + X_{eq}^2}}$$



$T_{max}$  is constant.

$$R_r' \uparrow \rightarrow \underline{W_m \downarrow} \rightarrow \underline{\sigma \uparrow} \rightarrow \underline{\eta_r = (1-\sigma) \downarrow}$$

speed control

disadvantage  
low efficiency

\* Using variable resistor

Using power converter

### ② Changing the line voltage:

$$T_{max} \propto V_m^2$$

$$\omega_{max} = \frac{R_r'}{\sqrt{R_s^2 + X_{eq}^2}} = \text{constant.}$$


$$V_s \downarrow \rightarrow V_m \downarrow \rightarrow (T_{max} \propto V_m^2) \downarrow \rightarrow \underline{W_m \downarrow} \rightarrow \underline{\sigma \uparrow} \rightarrow \underline{\eta_r \downarrow}$$

disadvantage

speed control.

disadvantage


in the efficiency

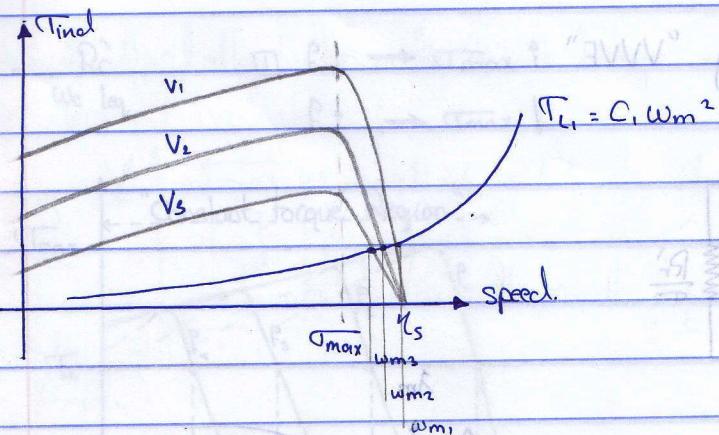


$$V_1 > V_2 > V_3 \rightarrow \omega_{m1} > \omega_{m2} > \omega_{m3}$$

Note: Methods to change the motor voltage:

### ① Auto-transformer : (VARIAC)

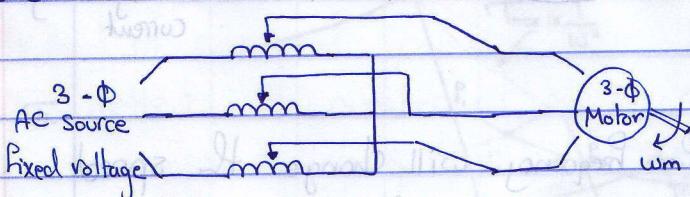


### ② 3-Φ AC Regulator:

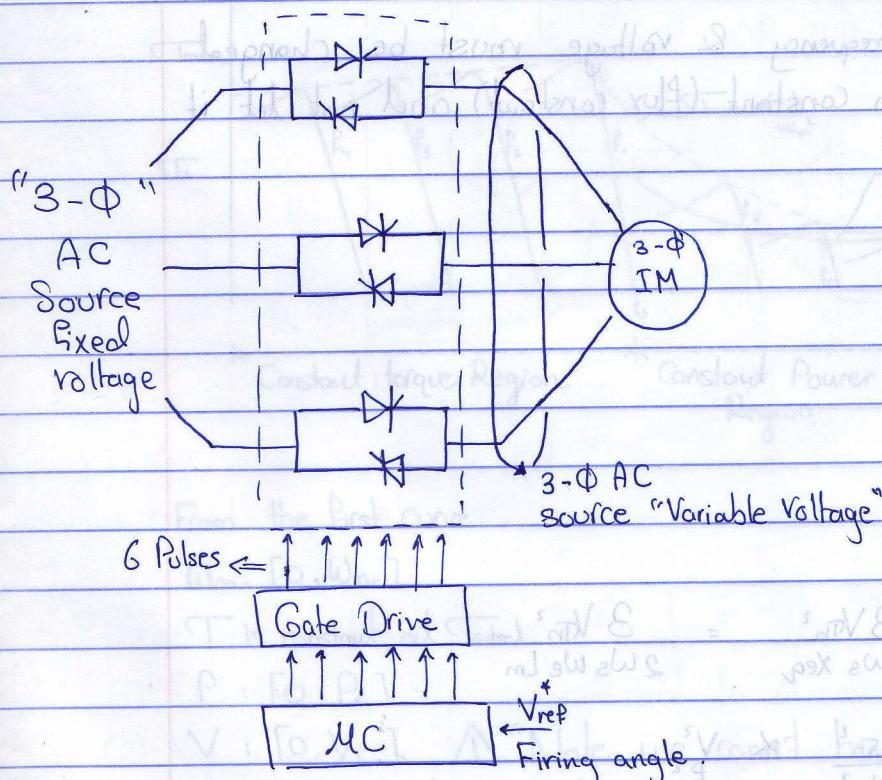

\* The Note ends here we are going to discuss what will

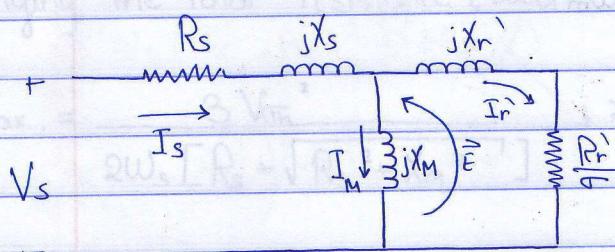
### ③ Variable Voltage Variable Frequency "VVVF":



$$\text{Flux linkage: } \lambda_m = L_m I_m$$

$$\lambda_m = L_m \left( \frac{E}{jX_m} \right) = L_m \cdot \frac{E}{\omega_e L_m} = \frac{E}{\omega_e}$$
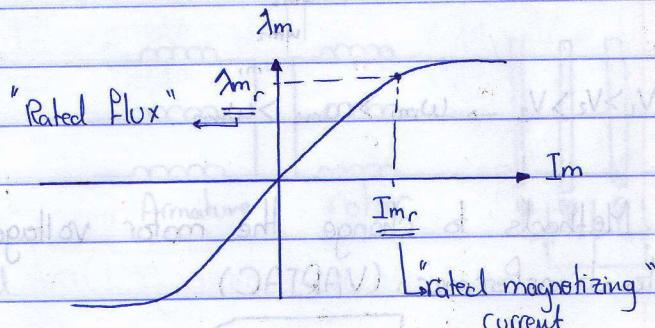
$$\lambda_m = \frac{E}{\omega_e} = \frac{E}{2\pi f_e}$$



Recall:  $\gamma_s = \frac{120 f_e}{P}$ , so changing the frequency will change the speed.

$$\lambda_m = \frac{E}{2\pi f_e} \approx \frac{V_s}{2\pi f_e} \rightarrow \lambda_m \propto \frac{V_s}{f_e}$$

When  $\omega_m <$  rated speed  $\rightarrow$  The frequency & voltage must be changed by the same factor to keep  $\lambda_m$  constant (flux constant) and not let it saturated.


$$T_{max} = \frac{3 V_{fb}^2}{2 W_s [R_s + \sqrt{R_s^2 + X_{eq}^2}]}$$

$$\sigma_{max} = \frac{R_r}{\sqrt{R_s^2 + X_{eq}^2}}$$



$$\text{If we ignore } R_s \rightarrow T_{max} = \frac{3 V_{fb}^2}{2 W_s X_{eq}} = \frac{3 V_{fb}^2}{2 W_s \omega_e L_m}$$

$$\text{but: } \omega_e = \frac{\omega_s}{2f} \rightarrow T_{max} \propto \frac{V_{fb}^2}{\omega_s^2} \propto \frac{V^2}{f^2}$$

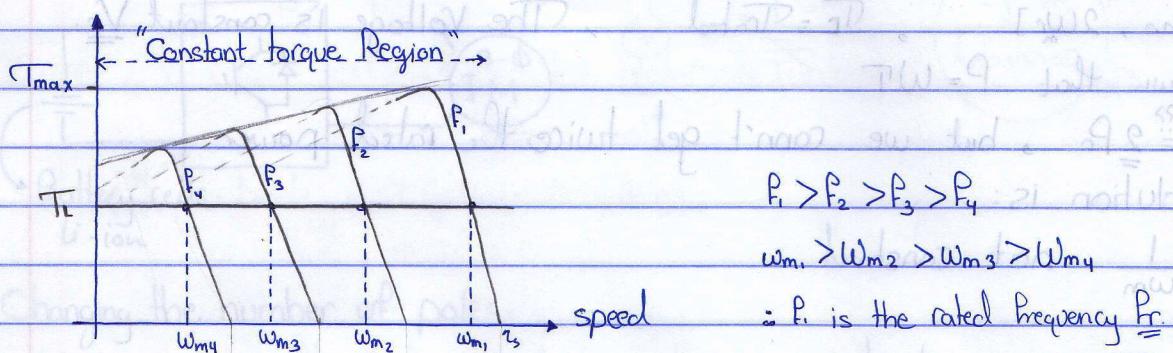$\omega_{\max} = \frac{Rr}{We \log} \quad \boxed{F!} \rightarrow \omega_{\max} \uparrow$  torque soft demand at low speed  
 $F! \rightarrow \omega_{\max} \downarrow$  torque hard soft demand


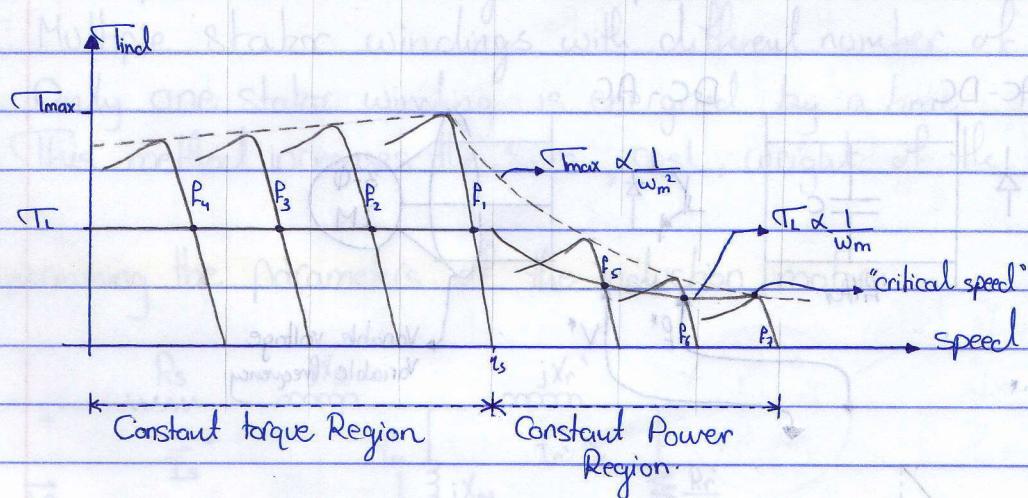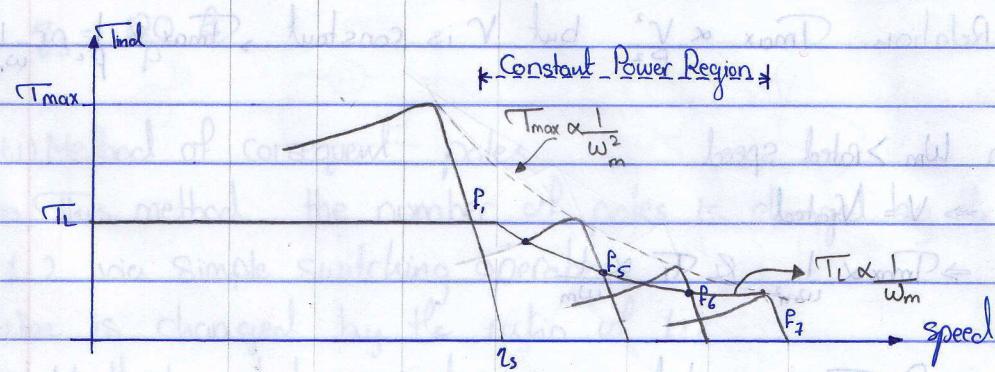
$$\begin{aligned} P_1 &> P_2 > P_3 > P_4 \\ \omega_m &> \omega_{m2} > \omega_{m3} > \omega_{m4} \\ \therefore f_s &\text{ is the rated frequency } P_r \end{aligned}$$



From the first curve:

$$\omega_m: [0, \omega_{m_r}]$$

$T$  is constant at  $T_{rated}$ .

$$P: [0, P_r]$$

$V: [0, V_r]$   $\Delta$  "Note we can't have a voltage higher than the rated voltage"

From the last note, we are going to discuss what will

happen if we want to increase the speed more than the rated speed.  
From the second curve:

$\omega_m : [\omega_{mr}, 2\omega_{mr}]$ ,  $T_r = \text{Trated}$ , The Voltage is constant  $V_r$

It's known that  $P = WT$

So  $P \stackrel{?}{=} 2P_r$ , but we can't get twice the rated power

The Solution is:

$T_r \propto \frac{1}{\omega_m}$  not constant

So  $P = TW \Rightarrow \text{constant}$ .


Now from the Relation  $T_{max} \propto \frac{V^2}{P^2}$  but  $V$  is constant  $\Rightarrow T_{max} \propto \frac{1}{P^2}$  or  $\frac{1}{\omega_m^2}$

To conclude: When  $\omega_m > \text{rated speed}$

$$\Rightarrow V = V_{rated}$$

$$\Rightarrow T_{max} \propto \frac{1}{\omega_m^2} \quad \& \quad T_r \propto \frac{1}{\omega_m}$$

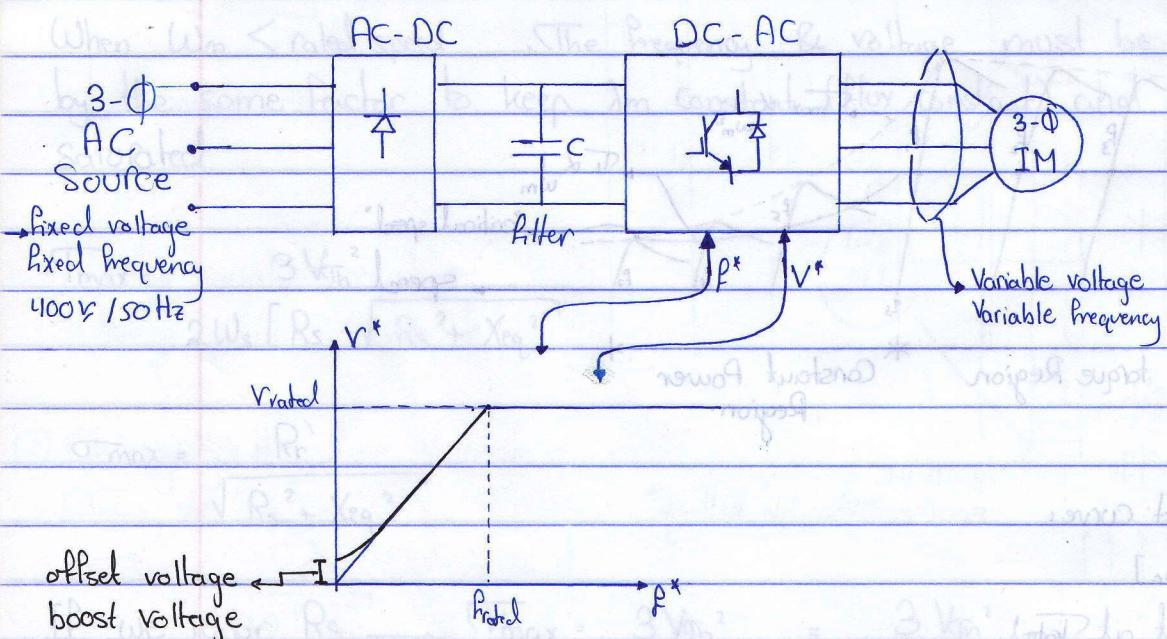
$$\Rightarrow P_m = T_r \omega_m = \text{rated power}$$



To make up the voltage drop across  $R_s$  at low frequencies.

\* Industrial Application on the VVVF:

The electrical vehicle

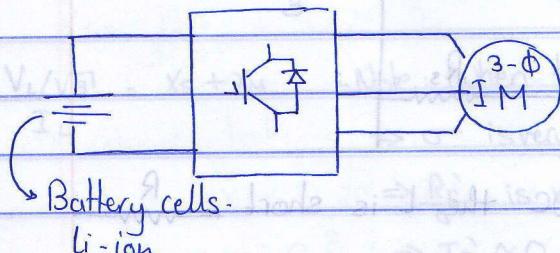

④ Changing the number of poles:

$$z_s = \frac{120 f_e}{P}$$

4.1) Method of consequent poles:

In This method , the number of poles is changed by the ratio of

1:2 via simple switching operation.

$W_m$  is changed by the ratio of 1:2.


4.2) Multiple stator windings:

Multiple stator windings with different number of poles.

Only one stator winding is energized by a time.

This method increases the size , cost , weight of the machine.


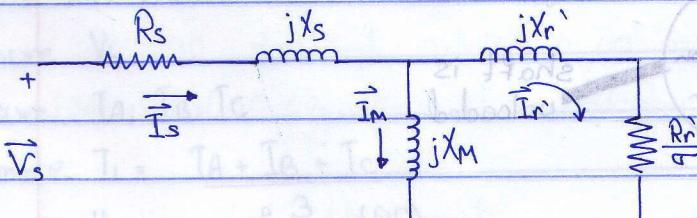
→ Determining the parameters of the induction motor:



There are 3 tests for Determining the IM parameters:

- ① DC test .
- ② No load test .
- ③ Locked rotor test .

## ① DC test:

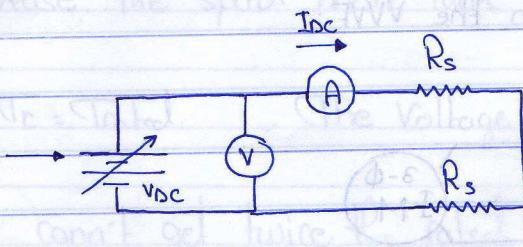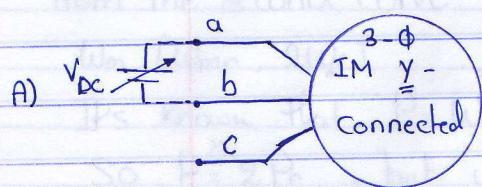



\* Windings → L → R → in the DC the L is short →  $\frac{R}{R+L}$

### Procedures:

1) Adjust the current in the stator windings to be equal to the motor's rated current.


2) Measure  $V_{DC}$  &  $I_{DC}$        $\left\{ \begin{array}{l} V_{DC} = 2R_s \\ I_{DC} \end{array} \right.$

3) Calculate  $R_s$ .

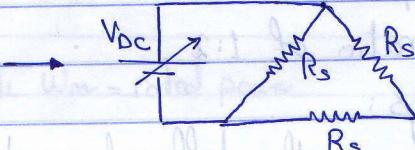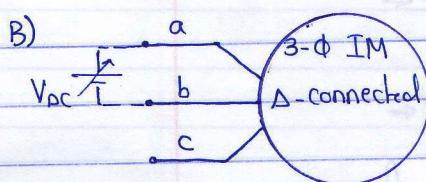

$$\frac{V_{DC}}{I_{DC}} = R_{eq} \rightarrow R_{eq} = R_s // 2R_s \rightarrow \frac{V_{DC}}{I_{DC}} = \frac{2}{3} R_s$$

## ② No load test:

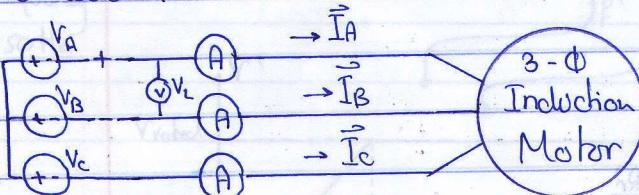

shaft is unloaded

$$|V_A| = |V_B| = |V_C| = \text{Motor's rated voltage.}$$

Frequency: Rated Frequency.

### Procedure:

① Make sure the shaft is unloaded

② Connect the motor to a 3-phase source ( $V$ =rated voltage,  $f$ =rated frequency).

③ measure  $V_L$

④ Measure  $I_A, I_B, I_C$  per phase equivalent circuit for the Motor:  $(R_s + R_r) = 0.023 \Omega \approx 1\Omega$


$$⑤ \text{estimate } I_L = \frac{I_A + I_B + I_C}{3} \quad \omega X = jX + \omega X \quad Z_{LR} = (R_s + R_r) + j(X_s + X_r) = 0.023 + j1.51$$

$\rightarrow \frac{V_L/\sqrt{3}}{I_L} = X_s + X_m$  Note: When the motor is unloaded  $\sigma$  is very small

$$\Rightarrow \frac{R_r}{\sigma} \text{ is very high}$$

$$\Rightarrow I_r' \approx 0$$

③ Locked rotor test:

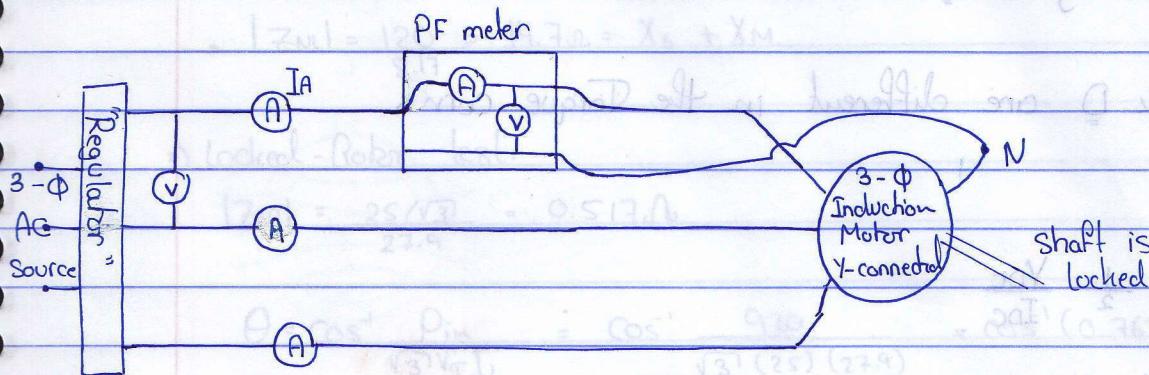


Procedure:

- ① Connect the motor terminal to Variable voltage Variable Frequency drive.
- ② Set the motor voltage initially to zero and then increase it gradually.
- ③ Set or Adjust the motor frequency to be equal 25% of the rated frequency.
- ④ Adjust the motor current to be equal the motor's rated current.
- ⑤ Measure  $V_L$
- ⑥ Measure  $I_A, I_B, I_C$
- ⑦ estimate  $I_L = I_A + I_B + I_C$
- ⑧ Measure the power factor (PF)

Note: Since the shaft is locked  $\Rightarrow \sigma = 1$

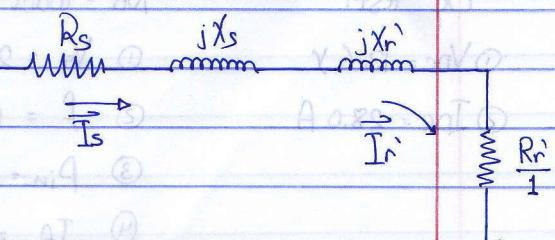$R_r'$  is very small  $\Rightarrow \vec{I}_s \approx \vec{I}_r$



$$* \frac{V_L/\sqrt{3}}{I_L} = |Z_{LR}| \quad \theta_{LR} = \cos^{-1}(PF) \quad Z_{LR} = (R_s + R_r') + j(X_s + X_r)$$

$$|Z_{LR}| \cos \theta_{LR} = R_s + R_r$$

$$|Z_{LR}| \sin \theta_{LR} = (X_s + X_r) \frac{f_{test}}{f_{rated}} \quad \therefore X_s + X_r = X_{LR}$$

Rotor Design: Wound Rotor

$$X_s = 0.5 X_{LR} \quad X_r = 0.5 X_{LR}$$

Cage Rotor :-

$$\textcircled{1} \text{ Design } A \quad X_s = 0.5 X_{LR} \quad X_r = 0.5 X_{LR}$$

$$\textcircled{2} \text{ Design } B \quad X_s = 0.4 X_{LR} \quad X_r = 0.6 X_{LR}$$

$$\textcircled{3} \text{ Design } C \quad X_s = 0.3 X_{LR} \quad X_r = 0.7 X_{LR}$$

$$\textcircled{4} \text{ Design } D \quad X_s = 0.5 X_{LR} \quad X_r = 0.5 X_{LR}$$

Note: Design A & D are different in the Torque curves.

To summarize:

$$\textcircled{1} \text{ DC test: } R_s = \frac{1}{2} \frac{V_{DC}}{I_{DC}}$$

$$\textcircled{2} \text{ No-load test: } X_s + X_m = \frac{V_L / \sqrt{3}}{I_L}$$

$$\textcircled{3} \text{ Locked rotor test: } \textcircled{1} R_r = |Z_{LR}| \cos \theta - R_s$$

$$\textcircled{2} X_{LR} = X_s + X_r = |Z_{LR}| \sin \theta \cdot \frac{f_{rated}}{f_{test}}$$

$$\textcircled{3} Z_{LR} = \frac{V_L / \sqrt{3}}{I_L} ; \chi_{ZLR} = \cos^{-1}(PF) = \theta_{LR}$$

Example: The following test data were taken on a 7.5-hp, four-pole, 208-V, 60-Hz, Design A, Y-connected induction motor having a rated current of 28 A.

Dc test:

$$\textcircled{1} V_{DC} = 13.6 \text{ V}$$

$$\textcircled{2} I_{DC} = 28.0 \text{ A}$$

No-load test

$$\textcircled{1} V_T = 208 \text{ V}$$

$$\textcircled{2} f = 60 \text{ Hz}$$

$$\textcircled{3} P_{in} = 420 \text{ W}$$

$$\textcircled{4} I_A = 8.12 \text{ A}$$

$$\textcircled{5} I_B = 8.20 \text{ A}$$

$$\textcircled{6} I_C = 8.18 \text{ A}$$

locked-rotor test

$$\textcircled{1} V_f = 25 \text{ V}$$

$$\textcircled{2} f = 15 \text{ Hz}$$

$$\textcircled{3} P_{in} = 920 \text{ W}$$

$$\textcircled{4} I_A = 28.1 \text{ A}$$

$$\textcircled{5} I_B = 28.0 \text{ A}$$

$$\textcircled{6} I_C = 27.6 \text{ A}$$

a) Sketch the per-phase equivalent circuit for this Motor:

i) DC test:

$$R_s = \frac{13.6}{2(28)} = 0.243 \Omega$$

ii) No-load test:

$$I_{L,av} = \frac{8.12 + 8.20 + 8.18}{3} = 8.17 A$$

$$V_{\phi, NL} = \frac{208}{\sqrt{3}} = 120 V$$

$$|Z_{NL}| = 120 = 14.7 \Omega = X_s + X_M$$

iii) Locked-Rotor test:

$$|Z_{LR}| = \frac{25\sqrt{3}}{27.9} = 0.517 \Omega$$

$$\theta = \cos^{-1} \frac{P_{in}}{\sqrt{3} V_{\phi} I_L} = \cos^{-1} \frac{920}{\sqrt{3} (25) (27.9)} = \cos^{-1} (0.762) = 40.4^\circ$$

$$R_{LR} = 0.517 \cos(40.4)$$

$$= 0.394 \Omega \rightarrow R' + R_s = 0.394 \rightarrow R' = 0.151$$

$$X_{LR} = (X_s + X') = \frac{60}{15} (0.517) \sin 40.4 = 0.335 (4) = 1.34 \Omega$$

Since it's design A:  $X_s \neq X' = 0.67 \Omega$

$$X_M = 14.7 - 0.67 = 14.03 \Omega$$

