
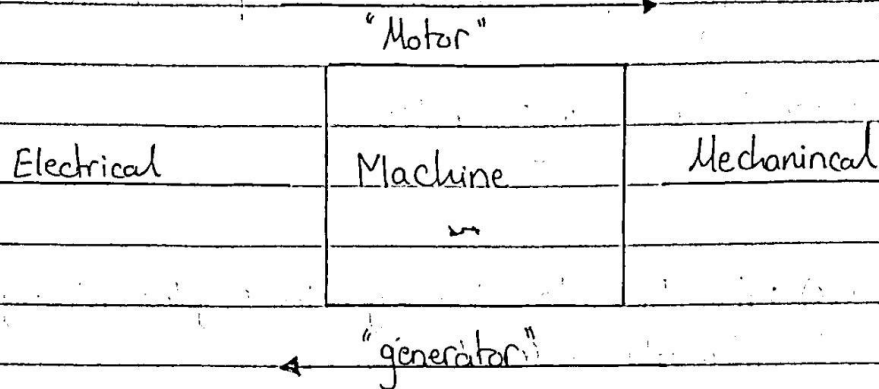


Electrical Machines

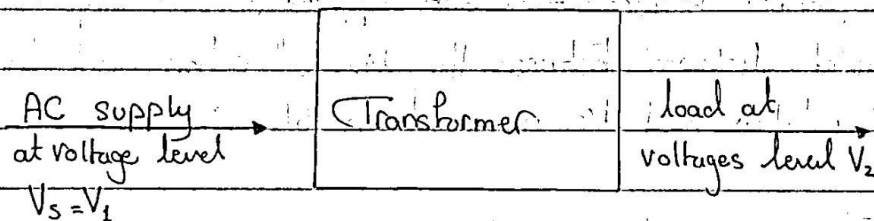→ An electrical machine is a device that converts either electrical energy to mechanical energy. Or mechanical energy to electrical energy through the action of magnetic field.



→ Transformer is a device that converts the AC electrical energy at a voltage level to AC electric energy at another voltage level.



if $V_1 > V_2 \Rightarrow$ step down

$V_2 > V_1 \Rightarrow$ step up

→ Rotational motion :

① angular position (θ) : it's measured in (rad).

② angular velocity (ω) : it's the rate of change of angular position and it's measured by (rad/sec)

$$\omega = \frac{d\theta}{dt}$$

Another unit for ω is the (rpm) = revolution per minute.

The rpm can be converted to ω and vice versa by the relation:

$$n = \frac{60}{2\pi} \omega$$

where n is the speed in (rpm).

Example: If the speed is 1000 rpm calculate the speed in rad/sec?

$$n = 1000 \rightarrow \omega = ??$$

$$\omega = \frac{2\pi}{60} \cdot 1000 \rightarrow \omega = \frac{100\pi}{3} \text{ rad/sec}$$


③ angular acceleration (α): it's the rate of change in angular velocity and measured in (rad/sec²).

$$\alpha = \frac{d\omega}{dt} = \frac{d^2\theta}{dt^2}$$

④ Torque (τ): It's the product between the force applied on the object and the smallest distance between the line of action and the axis of rotation and it's measured in (N.m).

$$\tau = \vec{r} \times \vec{F}$$

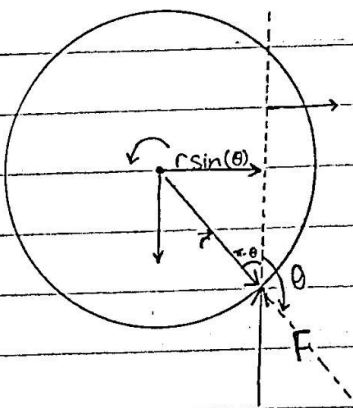= $rF \sin\theta$. where θ is the angle between the vectors \vec{r} and \vec{F} .



line of action. $\tau = rF \sin\theta$

The axis of rotation is about the center.

→ Newton's second law :

In linear motion → $\sum F = ma = m \frac{dv}{dt}$
net force

In Rotational motion → $\sum \tau = J \alpha = J \frac{d\omega}{dt}$
net torque

where J is called the moment of inertia and measured in $(\text{kg} \cdot \text{m}^2)$.

إذا السرعة ثابتة التorque صفر


إذا تزايد التorque موجب

" تناقص التorque السالب "

القدرة تعتمد على التorque والسرعة

إذا $\sum F$ أو $\sum \tau$ تساوي صفر يعني أن الجسم ثابت بل يمكن أن يكون في حركة ثابتة

→ High voltage cable :

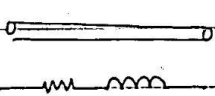

$$P_{\text{loss}} = 3 I^2 R \quad [\text{in three phase}]$$

$$S = VI = \text{constant value.}$$

$$\uparrow V \downarrow I = \text{constant}$$

Then $P_{\text{loss}} \downarrow$

→ Work (W) :

$$W = \int F \cdot dl \quad \text{in linear motion.}$$

$$W = \int \tau \cdot d\theta \quad \text{in angular motion.}$$

if τ is constant then $W = \tau \theta$ (steady state).

→ Power (P) is the rate of change of work done

$$P = \frac{dW}{dt} \Rightarrow \text{if } \tau \text{ is constant then } P = \tau \frac{d\theta}{dt} = \tau \omega.$$


From $P = \tau \omega$ we will find or calculate the torque.

$$\text{Power in (rpm)} \Rightarrow P = \tau \cdot \frac{2\pi n}{60}$$

→ Magnetic field: It's the fundamental mechanism of energy conversion in transformers and electric machines.

The Basic principles of the magnetic field:

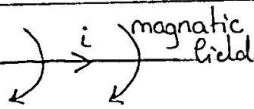① A current-carrying wire produces a magnetic field around it.



② A time-changing magnetic field produces a voltage across the coil when it passes through it. (transformer) . قانون فاراداي .

إذا كان المجال المغناطيسي يتغير مع الزمن في ملف نحاسي فإنه يولد قوة دافعة كهربية في الملف .

③ A current-carrying wire (in the presence of magnetic field) has a force induced on it.

$$F_{in} = i l \times B \quad \text{"Motor"}$$

$$= i l B \sin \theta$$

④ A moving wire in the presence of magnetic field has induced voltage across it "Generator"

$$e_{in} = (v \times B) \cdot l$$


$$= v B l \sin \theta \cos \alpha$$

→ Ampere's law: The basic law governing the production of a magnetic field by a current

$\oint H dl = I_{net}$; H is the magnetic field intensity produced by the current I_{net} .

dl: The differential element of length along the path of integration

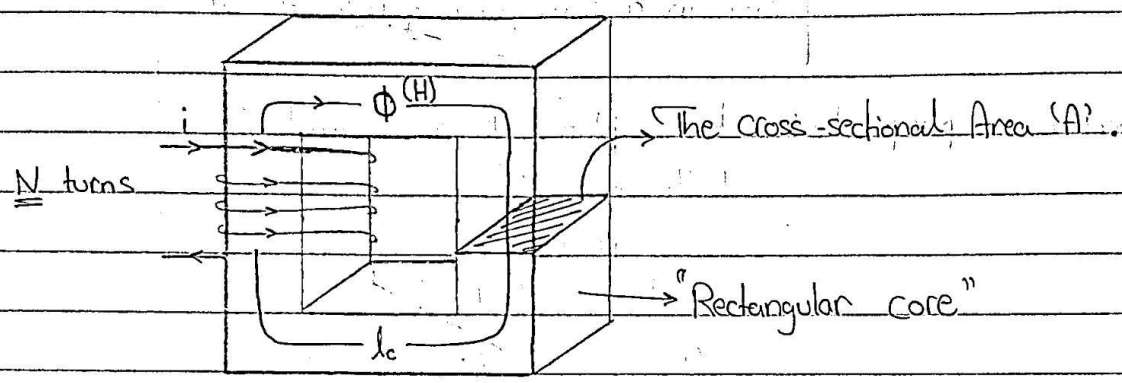I_{net} : the current in the loop [I(enc)].



$H l_c = Ni \rightarrow H = \frac{Ni}{l_c}$; H is measured by (Amp. turns)/meter

→ Magnetic field density (B):

$B = \mu H$

where μ is called the permeability of the material which represents the relative ease of establishing a magnetic field in a given material and its unit is (H/m).

Def: Magnetic field intensity (H): The effort required to induce magnetic field.

The unit of (B) is (weber / m²) or (Tesla)

The permeability of free space is called μ_0 and its value is:
 $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$

μ can be also represented by :

$\mu = \mu_0 \mu_r$, where μ_0 is the permeability of free space and μ_r is the relative permeability.

μ_r of the steel is located between (2000-6000)

→ Magnetic Flux: (Φ)

It's measured in weber (wb).

$$\Phi = \int_A B \cdot dA$$

$\mu_r = (2000-6000)$ means that: 2000-6000 times more flux is established in a piece of steel than in a corresponding area of air.


if the flux density vector is perpendicular to the plane of area, and it's constant then,

$$\Phi = B \cdot A$$


Now we have $\rightarrow B = \mu H = \frac{\mu_0 \cdot \mu_r \cdot N \cdot i}{l_c}$

So $\Phi = \frac{\mu_0 \cdot \mu_r \cdot N i A}{l_c}$ or $\Phi = \frac{\mu N i A}{l_c}$

→ Magnetic Circuits :-

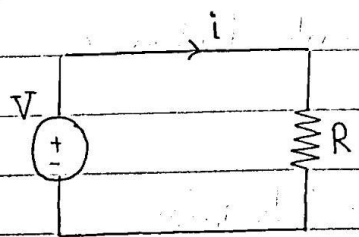

electrical circuit

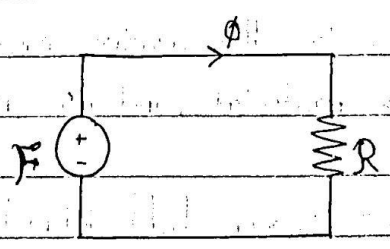

magnetic circuit

$$I = \frac{V}{R} \text{ [ohm's law]}$$

$$\Phi = \frac{F}{R}$$

$$F = Ni$$

F : is called the magnetomotive force

Φ : is the flux

R : is called the Reluctance

Note: $\frac{1}{R}$ is called the permeance

We know that the flux from the core is equal to:

$$\phi = \frac{\mu N i A}{l_c}$$

and it's also equal to $\phi = Ni/R$ from the magnetic circuit, combining the two results gives us:

$$R = \frac{l_c}{\mu A}$$

Reluctance in magnetic circuit behave the same as the resistance in electrical circuit.

① The equivalent reluctance of series:

$$R_{eq} = R_1 + R_2 + R_3 + \dots + R_n$$

② Similarly, reluctances in parallel combine as:



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

Flux calculations in a core by using the magnetic circuit concepts are always approximated within about 5% error

Reasons of inaccuracy of flux calculations:


① leakage flux: A small amount of magnetic flux escapes from the core into the surrounding low-permeability air

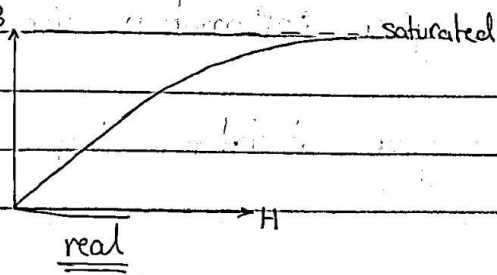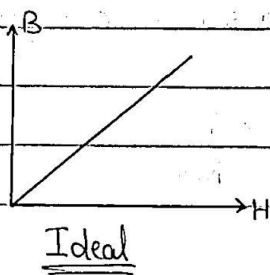② non-linear effects: In reality the permeability is not constant



③ Errors in measuring the cross-sectional area (A) and the mean path length (l_c)

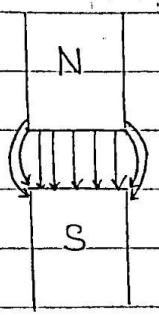④ Fringing effect: If there are air gaps in the flux path in a core, the effective cross-sectional area of the air gap will be larger than the cross-sectional area of the iron core




* See Example 1-1 page 15.

How to think :-

① determine the number of reluctances in the magnetic circuit by determining the following:

Since $R = \frac{l}{\mu A}$

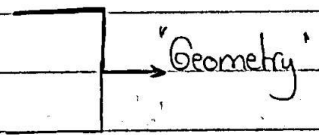- any change in: 1) the mean path length
- 2) the material (permeability)
- 3) Area



Note: Be aware while calculating the mean-path length.

All the units should be standard.

$\mu = \mu_0 \mu_r$ ⚠ Don't forget

② Draw the magnetic circuit, and label each part of it with the given information. Also determine if it's a series or a parallel.

③ make your calculations by :- ① $F = NI$; ② $\Phi = \frac{F}{R_{eq}}$

See example 1-2 page 17.

How to think:-

① Determine the two reluctances in the example, Notice that each reluctance will be different by changing l , μ or A .

② Be notice that the 5% increase in the air gap area will be calculated as: $A + 0.05A = "1.05A"$.

③ Memorizing all the formulas will be the only way to pass this example.

1) $\phi = BA$ since B is constant.

2) $\phi = \frac{F}{R}$

3) $Ni = BA \frac{l}{\mu A} \rightarrow i = \frac{Bl}{\mu N}$

See example 1-3 page 19.


How to think:-

① Notice that every change in l , μ or A will leads to a new reluctance. 'Here we have 4 reluctances'.

② Using the previous formulas find the Flux, then the Flux density in the gap.

→ Note: All the core & the gaps & the rotor have the same Flux.

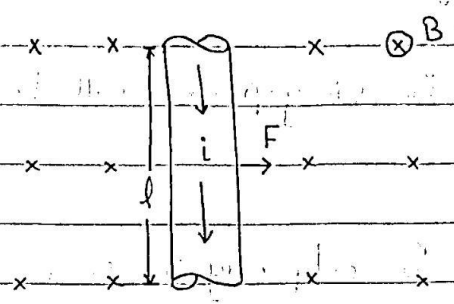→ Production of induced force on a wire:
 A major effect of a magnetic field on its surrounding is that it induces a force on a current-carrying wire within the field.



$F = i(l \times B)$
 where the direction of l is in the direction of current flow.


$F = i l B \sin \theta$, where θ is the angle between the wire & the P. density.

التيار i في السلك l يتحرك في اتجاه B القوة F

see example 1-7 page 33

Notes: The induction of a force in a wire by a current in the presence of a magnetic field is the basis of "Motor action"

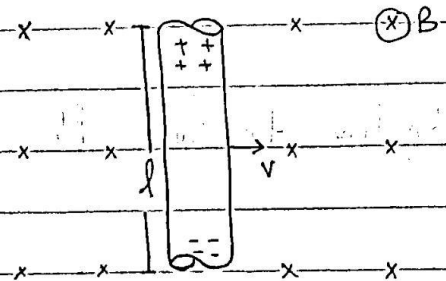→ Induced voltage on a conductor moving in a magnetic field:
 If a wire with proper orientation moves through a magnetic field a voltage is induced in it.



$\mathcal{E}_{ind} = (v \times B) \cdot l$
 v is the velocity.
 l is length of conductor, it points along the direction of the wire toward the end making the smallest angle with the vector $(v \times B)$.

* The voltage in the wire will be built up so that the positive end is in the direction of $(v \times B)$.

→ See example 1-8 page 34:

How to think:

① lets write the formula $e_{ind} = (v \times B) \cdot l$ in its expansion

Formula:

$e_{ind} = vB \sin\theta \cdot l \cos\alpha$ → What are θ & α ??

→ θ is the angle between the velocity direction & the B density direction:

(The $(v \times B)$ can be obtained by the right hand laws.

$(v \times B)$ direction is perpendicular to the plane formed by v and B .


→ α is the angle between $(v \times B)$ and l "the smallest angle"

→ Also see example 1-9 page 34:

Note: "The induction of voltages in a wire moving in a magnetic field is fundamental to the operation of all types of "Generators"

→ it's called the generator action.

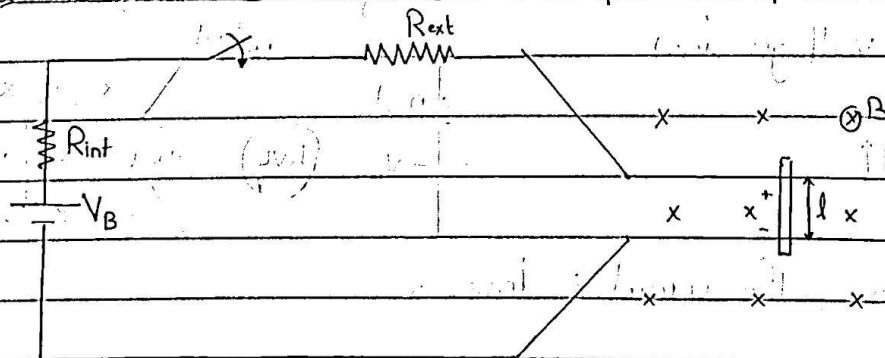→ The linear DC machine - a simple example:



→ R_{int} : The internal resistance of the DC battery.

R_{ext} : An external resistance which is used to limit the starting current.

How is this simple DC Machine works :

When the switch is closed the current will flow through the conducting bar. This current is initially given by :

$$i = \frac{V_{oc}}{R_{eq}} \quad ; \quad R_{eq} = R_{ext} + R_{int}$$

Since the current passes through the bar in the presence of the magnetic field; an induced force will be applied on the bar :

$$F_{ind} = i(l \times B) = i l B \quad \text{since } \theta = 90^\circ$$

The bar will accelerate according to Newton's second law :

$$\Sigma \vec{F} = m \vec{a} = F_{ind}$$


The bar now is moving in the presence of the magnetic field (B) and an induced voltage will appear across it :

$$e_{ind} = (v \times B) \cdot l = v B l \quad \text{since } \theta = 90^\circ \text{ \& } \alpha = 0^\circ$$

From here : $e_{ind} \uparrow = v \uparrow B l$ [the emf is increasing]

The voltage now reduces the current flowing in the bar, since by kirchhoff's voltage law
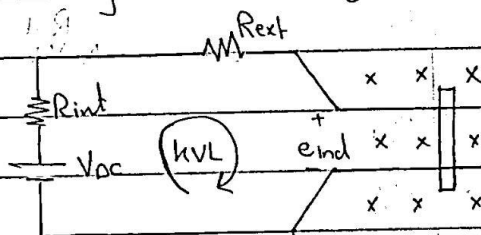
$$i \downarrow = \frac{V_{DC} - e_{ind} \uparrow}{R_{eq}}$$



As e_{ind} increases, the current i decreases.

When the net force on the bar equals zero then the bar will reach the steady-state and it will move with constant speed

$F_{ind} = 0$ when $e_{ind} = V_{DC}$ since i will be zero :

$$i = \frac{V_{DC} - e_{ind}}{R_{eq}} = 0$$

So $\Sigma \vec{F} = 0 = m \vec{a} \Rightarrow$ So $\vec{a} = 0 \Rightarrow$ the bar is moving at constant speed. = V_s

V_s is given by 8


$e_{ind} = V_{DC} = \underbrace{vBl}_{\text{velocity}} \rightarrow v \text{ is now } V_s \rightarrow \boxed{V_s = \frac{V_{DC}}{Bl}}$

The bar will continue to move with this speed unless some external force disturbs it


Charts & Graphs

When the motor is started then:


1) Velocity (t)

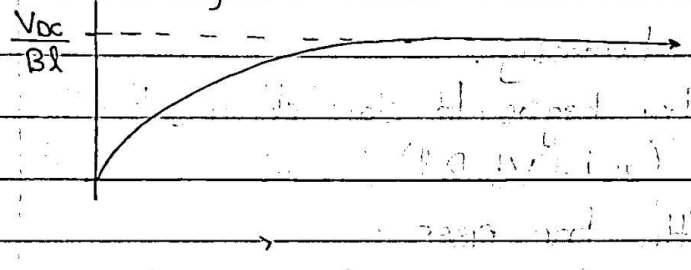


2) $e_{ind}(t)$

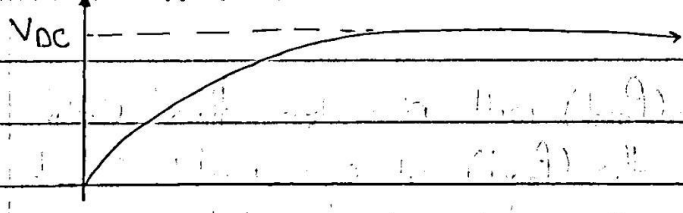

3) $i(t)$

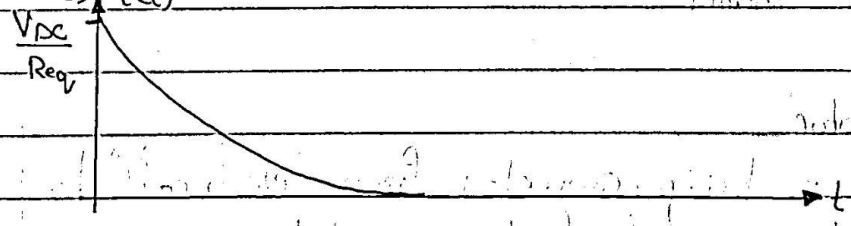

4) induced force (t) " f_{ind} "

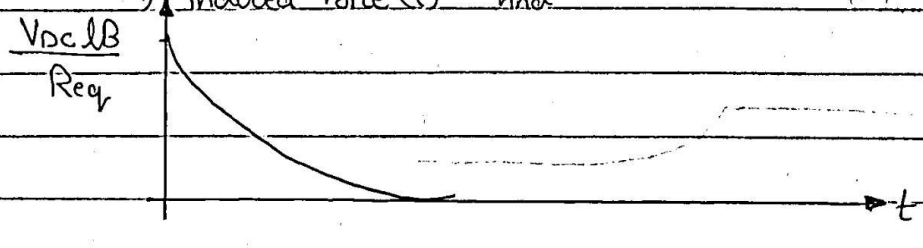


The linear DC Machine as a "Motor":

Assume that the machine is initially running under the steady state condition with no load (force) acting on it. Then the speed (V_s) is given by: $V_s = \frac{V_{DC}}{Bl}$

Now, Assume that a load force (F_{load}) is applied with opposite direction of motion,

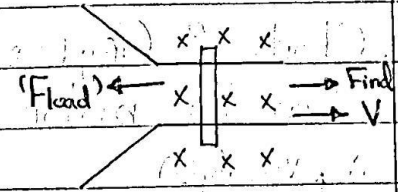$\Sigma F = F_{ind} - F_{load}$, since F_{ind} is zero initially
then $\Sigma F = -F_{load} = m\ddot{a}$



$= a < 0$, so V is decreasing

But just as soon as the bar begins to slow down, the induced voltage (e_{ind}) will drop ($e_{ind} = v \downarrow Bl$).


So, the current flow in the bar rises:


$$i \uparrow = \frac{V_{DC} - e_{ind}}{R_{eq}}$$

Therefore the induced force (F_{ind}) will rise too, this chain of events will result in that the (F_{ind}) will rise until it equals the (F_{load}). [The bar will reach a steady-state again]
But now V_s will be smaller

The power now is being converted from "electrical" to "Mechanical". And the amount of it is equal to:

$$P_{conv} = e_{ind} i = F_{ind} v$$

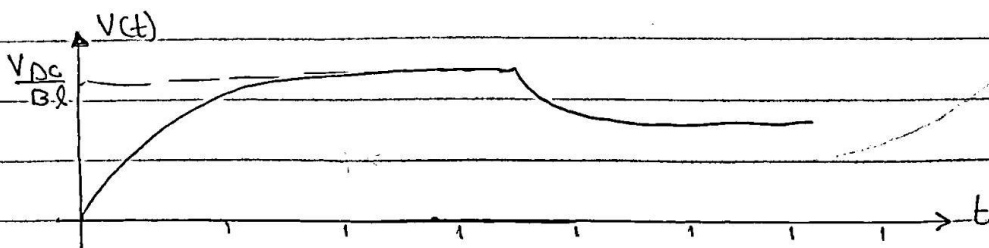

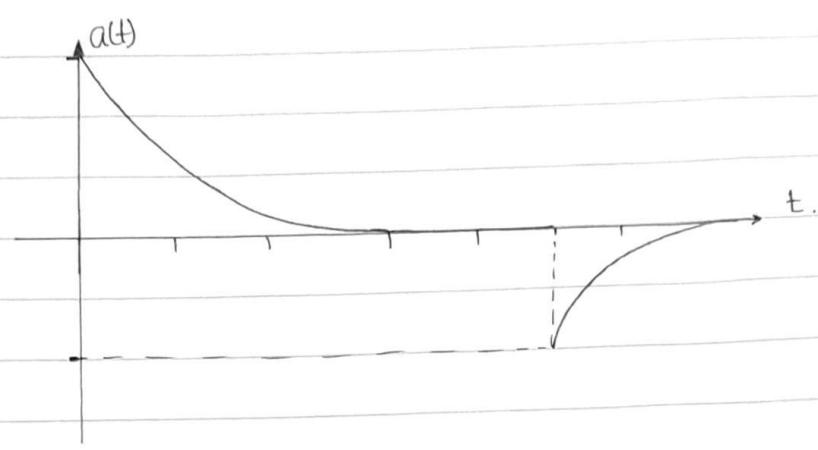

Note: In the Power conversion Formula we use (e_{ind}) not (V_{DC}) ; because some power has been lost in the resistors.


The linear DC Machine as a Generator:

Assume that the Machine is running under steady-state with no load.
 The speed in this state is: $V_s = \frac{V_{DC}}{Bl}$

Assume now that an external force is applied on the bar in the direction of motion.

The idea here is to make $e_{ind} > V_{DC}$ So V increases.


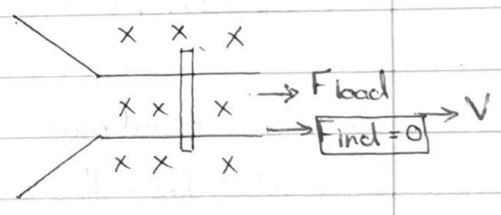
$\Sigma F = F_{ind} + F_{load} \rightarrow F_{ind} = 0$ initially.
 $\Sigma F = F_{load} = m\vec{a}$
 $\Sigma F > 0 \rightarrow a > 0 \rightarrow V$ increases.



$\rightarrow e_{ind} \uparrow = V \uparrow Bl$, also i will increase but in the negative direction.

$\rightarrow |F_{ind}| \uparrow = i l B$ in the opposite direction. It will rise until it reaches the F_{load} , Then:
 $\Sigma F = 0 \rightarrow m\vec{a} = 0 \rightarrow V_s'$ is the constant velocity.
 Such that $V_s' > V_s$

subic
 . 10/20
 ?

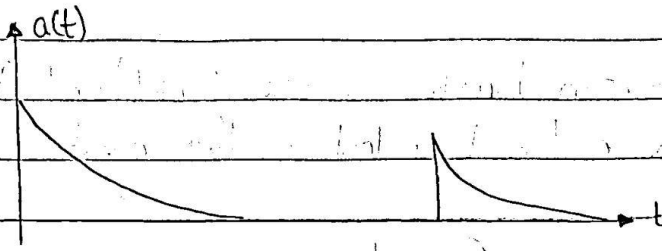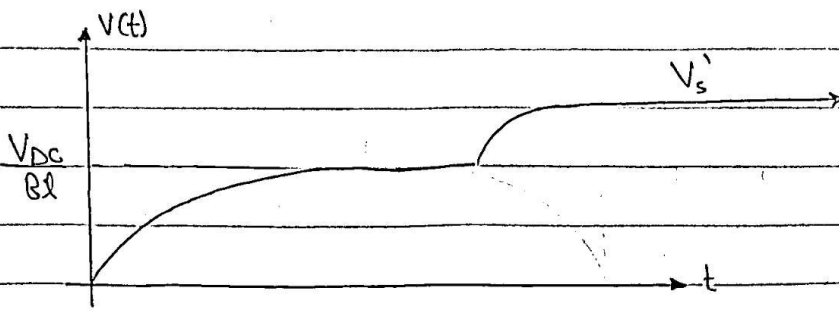

See example 1-10 page 438

How to think:-

i) In the steady state condition $V_{DC} = \epsilon_{ind}$

ii) if a force acting in an opposite direction of the original (ϵ_{ind}) then it will act like a motor. However, if the force act in a direction of the original (ϵ_{ind}) then it will act like a generator.

3) When an external force is applied, the following procedures should be followed:-

i - determine the ϵ_{ind} in the steady-state, $\epsilon_{ind} = \epsilon_{applied} = i l B$

ii - Then a KVL over the mesh to find ϵ_{ind} , but before that you should find i .

iii - Now $V_{ss} = \epsilon_{ind} / Bl$.

iv - You can be verify from your answer if it's true, by:-

1- if it's a motor V_{ss} should be less than V_{ss}

2- if it's a generator V_{ss} should be more than V_{ss} .

?

4) The power can be studied as follows:

i. in the Motor:

1. The bar is consuming power. $P = e_{ind} \cdot V_{ss}$

2. The battery is producing power. $P = V_{oc} \cdot i$

ii. in the Generator:


1. The bar is producing power.

2. The battery is consuming power.

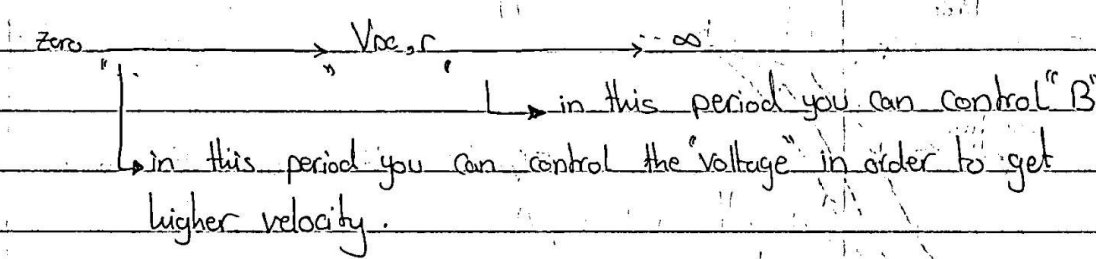5) Notes for (e) :-

$V_{oc,r}$ is Rated (Nominal) DC Voltage of the machine,

في هذا المجال، يمكن التحكم في الجهد لإنتاج سرعة أعلى.





$V_s = \frac{e_{ind}}{B\ell}$ at s.s "eind & l" are constants so $V_s \propto \frac{1}{B}$

from $F_{ind} = I\ell \times B \rightarrow F_{ind} \propto \frac{1}{V_s} \times B$

\Rightarrow Power = $F_{ind} \cdot V_s \rightarrow$ Power = $k \cdot \frac{1}{V_s} \cdot V_s = k$ a "constant" when $V_s > V_{s,r}$
 i.e. $V_{s,r}$ is the "rated speed"!

Energy losses in the Ferromagnetic Material:

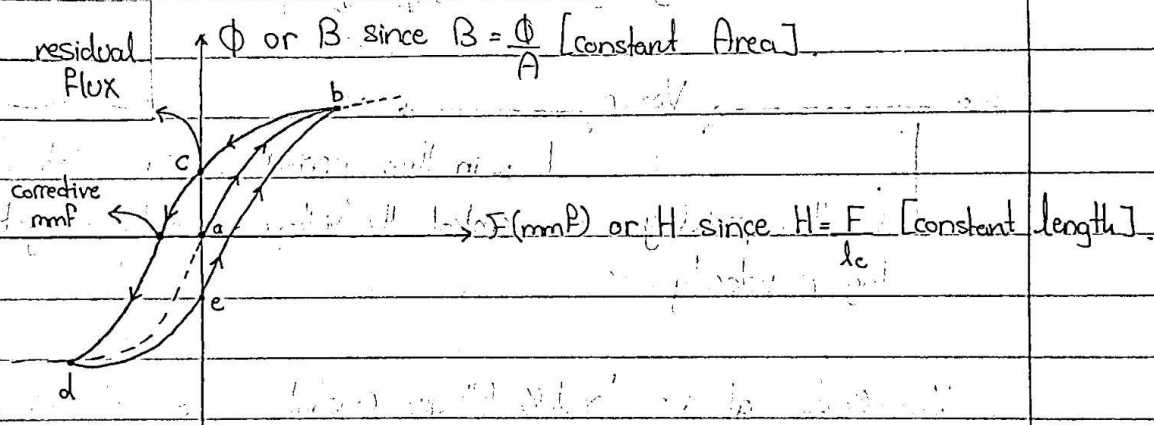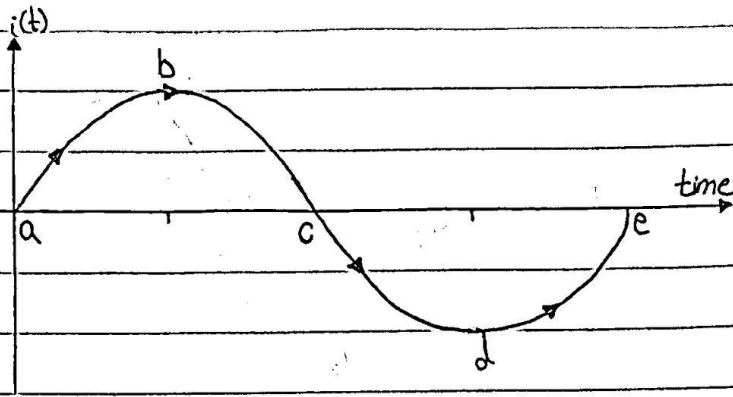Assume that an AC current is applied to the windings of the core, and the Flux is initially zero.



The above figures represents the hysteresis loop traced out by the Flux in the core when the current is applied to it.

Notes: The ab part represents the saturation curve.

The Flux depends not only on the current but also on the previous history of the Flux in the core. This dependency is called "Hysteresis".


$$\Phi = F(i) + \Phi_i$$

When a large magnetomotive force is applied to the core and then removed, the path of the flux is abc. The flux doesn't go to zero when mmf is removed. Therefore a corrective mmf is applied in the opposite direction to force the flux to go to zero.


Residual flux: it is the flux left in the core when the mmf is removed.

Corrective mmf: it is the mmf that should be applied in the opposite direction to force the flux to go to zero in the core.


The structure of ferromagnetic materials

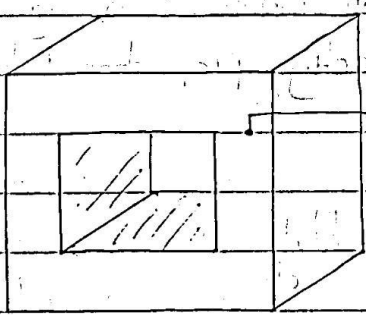

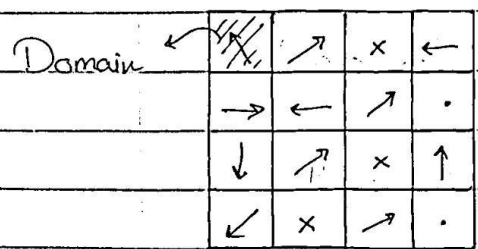
A point on the core
The ferromagnetic material has domains where each domain consists of set of atoms (Nickel, Cobalt, Iron).



"Magnetic domains oriented randomly"

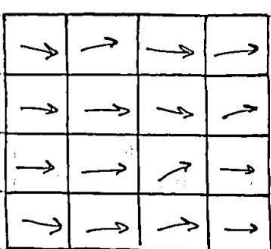

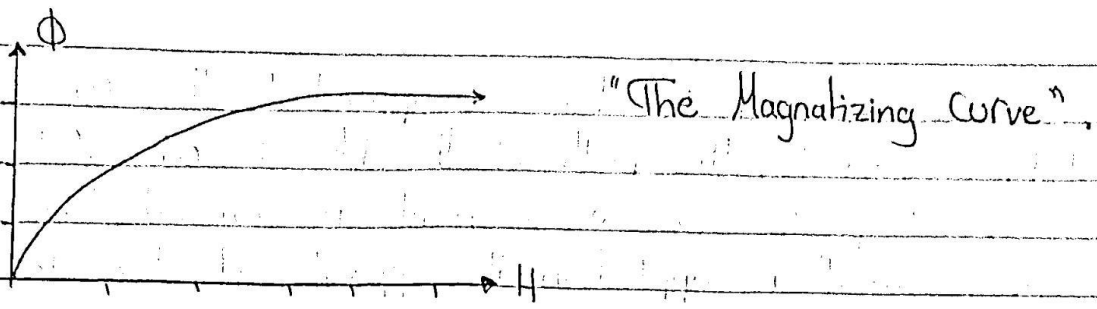"Magnetic domains lined up in the presence of an external magnetic field"



→ Hysteresis loss:

it is the energy required to accomplish reorientation of magnetic domains per each cycle of applied AC curve. This energy is converted to heat in the core.

→ Faraday's law:-

It is the fundamental property of magnetic field involved in Transformer operation.

If a flux passed through a coil, it will induce a voltage across the coil. The voltage is directly proportional to the rate of change of the flux.

$$e_{ind} \propto \frac{d\Phi}{dt} \rightarrow \text{for } N \text{ turns: } e_{ind} = N \frac{d\Phi}{dt}$$

When Leakage Flux is considered:


if there is a leakage flux outside the core (in the air), each turn might have a slightly different flux.

The e_{ind} ith term: $e_i = \frac{d\Phi_i}{dt}$; $i = 1, 2, 3, 4, \dots$

The e_{ind} across the N turns is:

$$e_{ind} = \sum_{i=1}^N e_i = \sum_{i=1}^N \frac{d\Phi_i}{dt} = \frac{d}{dt} \sum_{i=1}^N \Phi_i \text{ where } \sum_{i=1}^N \Phi_i \text{ is the "flux linkage"}$$

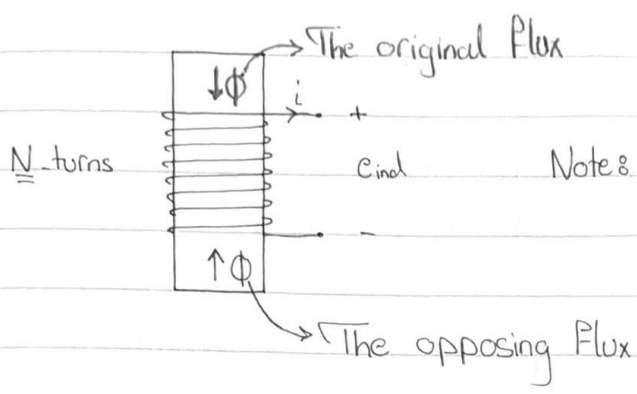
$$e_{ind} = \frac{d\lambda}{dt} \rightarrow \text{where } \lambda = \sum_{i=1}^N \Phi_i \text{ (wb.tums).}$$



Note: The polarity of e_{ind} is determined by Lenz law.

Eddy currents: The time-changing flux $\frac{d\Phi}{dt}$ induced a voltage within the core. The induced voltage causes eddy currents to flow in the core. The eddy currents flow through the ~~core~~ resistive material of the core which causes energy loss that heats up the core.

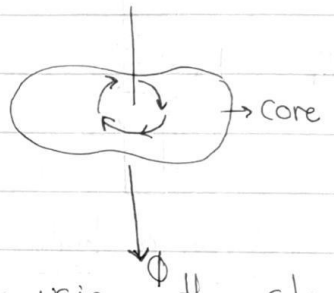eddy current $\vec{j} \propto \frac{d\Phi}{dt}$



The paths of eddy currents are broken using the steel laminations with high permeability [to transfer flux] and low conductivity. The sheets are isolated from each other using insulating material.


→ We can see that energy loss comes from two major things:

Energy loss = Hysteresis_{loss} + Eddy currents_{loss}


Example: A coil of wire wrapped around an iron core. The flux in the core is: $\Phi = 0.05 \sin 377t$ Wb. There are 100 turns on the core.
Ans:

$$e_{ind} = N \frac{d\Phi}{dt} \rightarrow e_{ind} = 100 [0.05 \cdot 377 \cos 377t]$$

$$= 1885 \cos 377t \cdot V$$

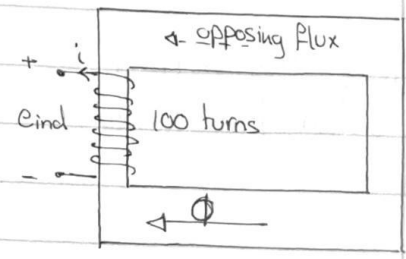

ideal transformers

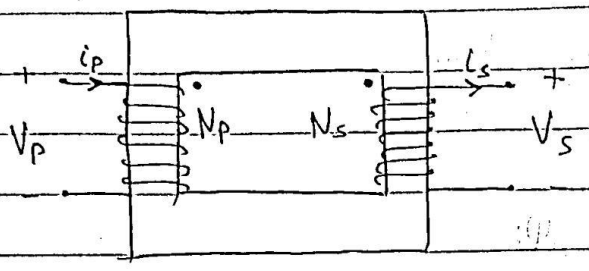

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} = a \text{ [turns ratio]}$$

$$\frac{i_p}{i_s} = \frac{N_s}{N_p} = \frac{1}{a}$$

Dot Convention:

- If i_p flows into the dotted end and i_s flows out the dotted end.
- if V_p is positive at the dotted end and V_s is positive at the dotted end.


input power: $V_p I_p \cos(\theta_p) \quad \therefore \theta_p = \theta_{V_p} - \theta_{i_p}$

output power: $V_s I_s \cos(\theta_s) \quad \therefore \theta_s = \theta_{V_s} - \theta_{i_s}$


in ideal transformer: $\theta_p = \theta_s$

$$P_{in} = P_{out}$$

Model of ideal transformer:

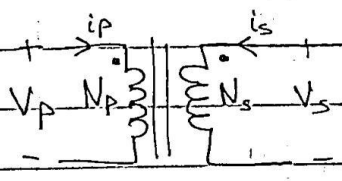


t-domain

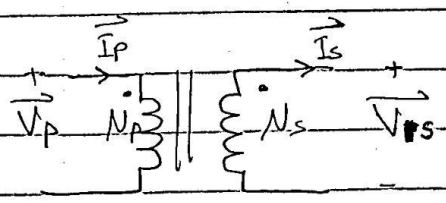

phasor-domain: $x(t) = X_m \cos(\omega t + \phi)$

$$x(t) = X_m \angle \theta \text{ "steady-state"}$$

Reflected impedance:

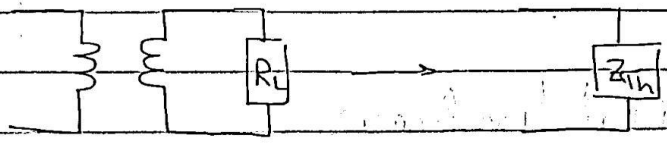

$$Z_{th} = a^2 Z_L$$

→ Theory of operation of 1- Φ Real transformer :

The induced voltage is given by "Faraday's law" :

$$e_{ind} = \frac{d\lambda}{dt} \quad ; \quad \lambda : \text{Linkage Flux} \quad , \quad \lambda = \sum_i \Phi_i$$

The average flux $\bar{\Phi} = \frac{\sum_i^N \Phi_i}{N} \rightarrow N\bar{\Phi} = \sum_i^N \Phi_i$

induced voltage $e_{ind} = N \frac{d\bar{\Phi}}{dt}$

→ The average flux $\bar{\Phi}$ has two components :-

$$\bar{\Phi} = \Phi_M + \Phi_L$$

= Mutual Flux + leakage Flux

Primary Flux = $\bar{\Phi}_p = \Phi_M + \Phi_{lp}$

secondary Flux = $\bar{\Phi}_s = \Phi_M + \Phi_{ls}$

By applying Faraday's law we get :-

$$V_p = N_p \frac{d\bar{\Phi}_p}{dt} = N_p \frac{d\Phi_M}{dt} + N_p \frac{d\Phi_{lp}}{dt} = \underline{e_p} + \underline{e_{pL}}$$

$$V_s = N_s \frac{d\bar{\Phi}_s}{dt} = N_s \frac{d\Phi_M}{dt} + N_s \frac{d\Phi_{ls}}{dt} = \underline{e_s} + \underline{e_{sL}}$$

Now : $\frac{e_p}{e_s} = \frac{N_p}{N_s}$


When design transformer :

→ $\Phi_M \gg \Phi_{pL}$ & $\Phi_M \gg \Phi_{sL}$

So → $V_p \sim e_p$ & $V_s \sim e_s$

→ $V_p/V_s = N_p/N_s$ close to ideal transformer.

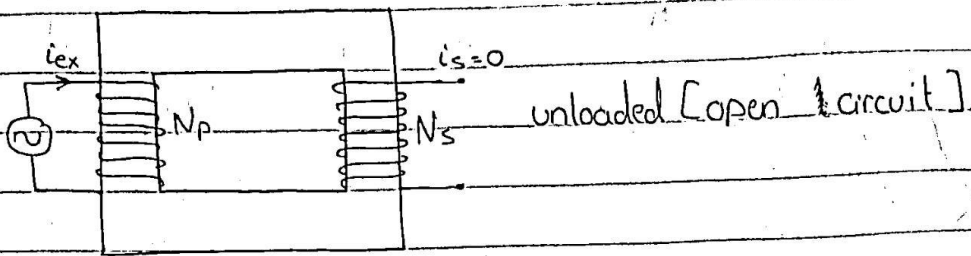The excitation current in real transformer:



Assume, the primary is connected to an AC source, secondary is unloaded.

The primary unloaded current is called "excitation current" (\$i_{ex}\$)

This current has two components:

- 1) Magnetizing current (\$i_m\$): it produces a flux in the core "Mutual Flux"
- 2) Core losses current (\$i_{c+H}\$): it makes up the eddy current and Hysteresis losses

→ Magnetizing Current (\$i_m\$):

The primary voltage is given by:

$$V_p = N_p \frac{d\Phi_p}{dt} \approx N_p \frac{d\Phi_m}{dt}$$



$$\Phi_m = \frac{1}{N_p} \int V_p dt$$

Assume that \$V_p = V_m \cos(\omega t)\$

$$\text{Then } \Phi_m = \frac{1}{N_p} \frac{V_m}{\omega} \sin(\omega t)$$


\$\frac{V_m}{\omega}\$ is the value of flux

Charts 8:-

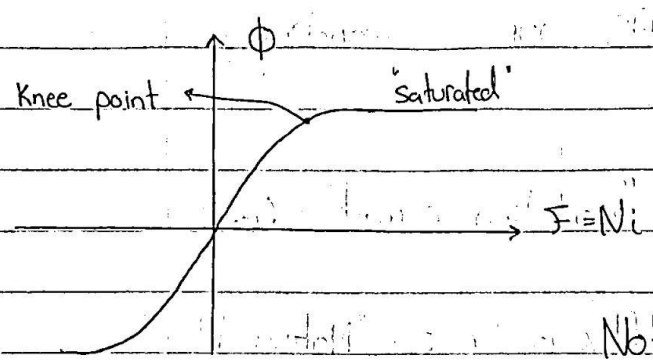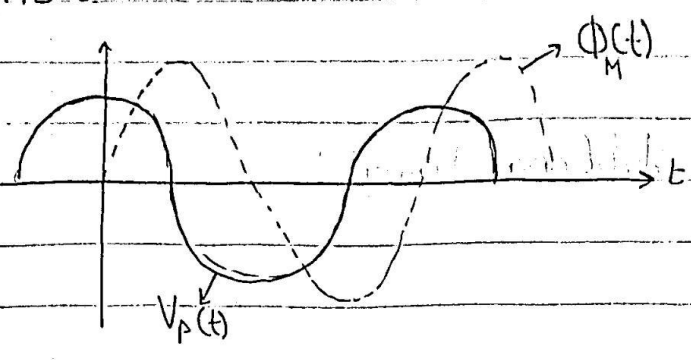

Note: see page (82)

Notes:

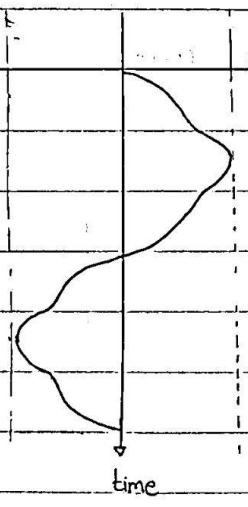


- ① The magnetizing current (i_m) in the transformer is not sinusoidal. The higher frequency components [the peaks] in the curve are due to magnetic saturation in the core.
- ② When the flux reaches its saturation level in the core, a small increase in the flux (Φ_M) requires a very large increase in the magnetizing current.

③ The fundamental component of the magnetizing current (i_m) lags the applied voltage (V_p) by 90° .

④ The higher frequency components in the magnetizing current (i_m) can be large compared to the fundamental component.

2) Core-loss current (i_{e+h}):

By assuming the flux in the core is sinusoidal. Since the eddy currents in the core are proportional to $d\Phi/dt$, then the eddy currents are largest when the flux in the core is passing through 0 Wb. Therefore, the core-loss current (i_{e+h}) is greatest when the flux passes through zero.

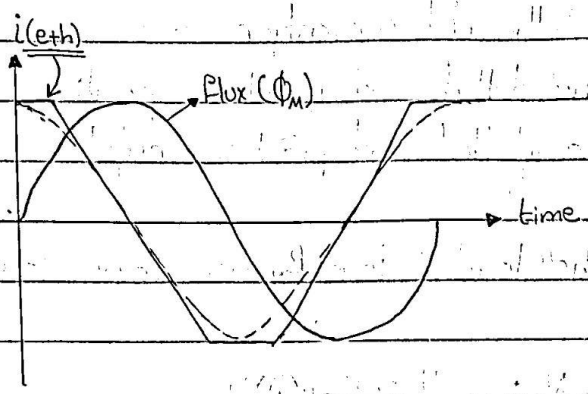


Notes 8:


① $i_{(e+h)}$ is non-linear because of the non-linear effects of hysteresis.

② The fundamental component of the core-loss current ($i_{(e+h)}$) is in phase with the voltage applied to the core (V_p).

Recalls: The total no-load current in the core is called the "excitation current"

$$i_{ex} = i_m + i_{(e+h)}$$

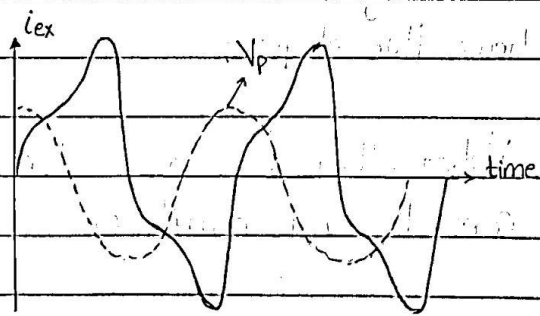

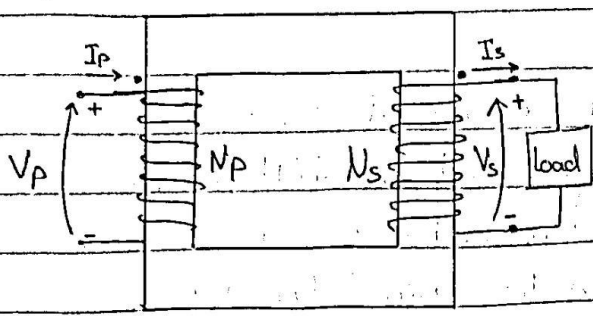


The current ratio on a transformer and the dot convention:

Assume that a load is connected to the secondary of the transformer.

The physical significance of the dot convention is:

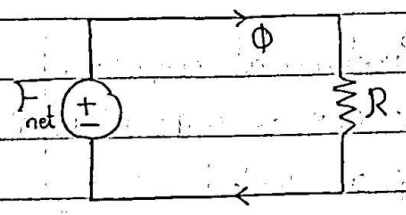1. A current flowing into the dotted end produces positive mmf.
2. A current flowing out the dotted end produces negative mmf.

The magnetic circuit of the loaded transformer core is:




$$F_{net} = N_p i_p - N_s i_s = \Phi R$$

if $R = 0$ [very small (nearly zero)]

$$\text{Then, } N_p i_p - N_s i_s \approx 0 \rightarrow \frac{i_p}{i_s} = \frac{N_s}{N_p}$$

Assumptions to convert a real transformer to ideal transformer:

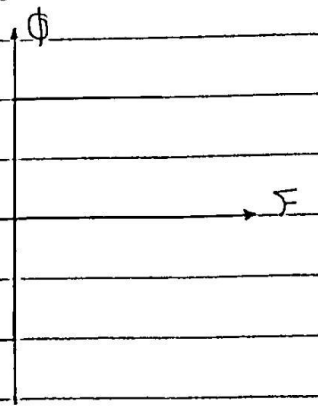- ① core-loss current must be zero ($i_{e+h} = 0$).
- ② The leakage flux in the core must be zero, $\Phi_{lp} = \Phi_{ls} = 0$
- ③ The resistance of the transformer windings must be zero.
- ④ The magnetization curve must have this shape:



Notice that for an unsaturated core the net mmf = 0

The equivalent circuit of a transformer:

The losses that occur in real transformer's:

- 1) Copper losses (I^2R): 1) primary circuit \rightarrow Resistance R_p
- 2) secondary circuit \rightarrow Resistance R_s

2) leakage flux: These escaped fluxes produce a leakage inductance in the primary and secondary coils.

$$i_p V_p = e_{lp} + e_p \quad [\text{due to leakage flux} + \text{due to mutual flux}]$$

$$e_{lp} = N_p \frac{d\Phi_{lp}}{dt} = N_p \frac{d(N_p i_p)}{dt} = \frac{N_p^2}{R_p} \frac{di_p}{dt}$$


From this equation we can see that the leakage flux is represented by an inductor.

The same steps for $V_s = e_{ls} + e_s$, we get $\Rightarrow e_{ls} = \frac{N_s^2}{R_s} \frac{di_s}{dt}$
 also we can represent it with an inductor.

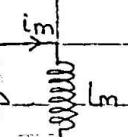3) Magnetizing current (i_m): i_m is proportional to V_p ,

i_m lags V_p by 90°


it's modeled by an inductance (L_m) [magnetizing inductance]



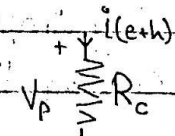
4) Core-loss current (i_{e+w}): is proportional to V_p

is in phase with V_p

it's represented as a resistance: [core resistance]




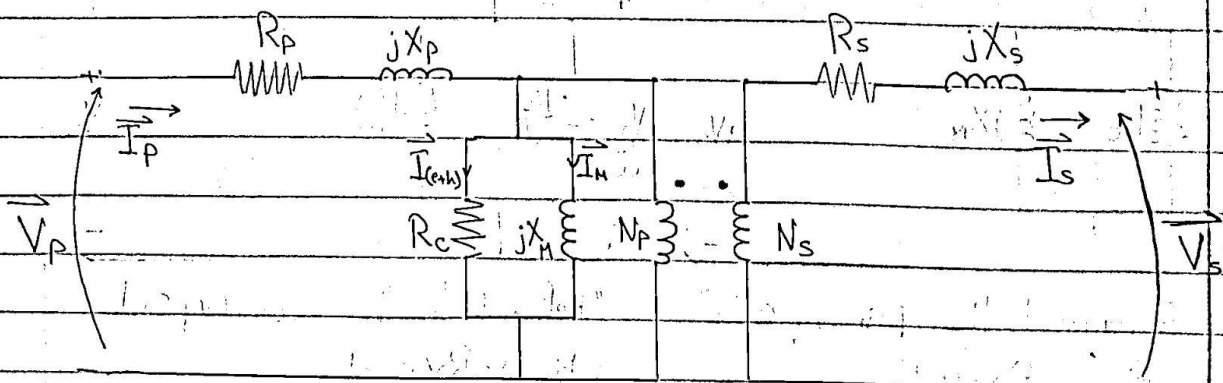The model of a real transformer: [In phasor domain]




Ideal transformer

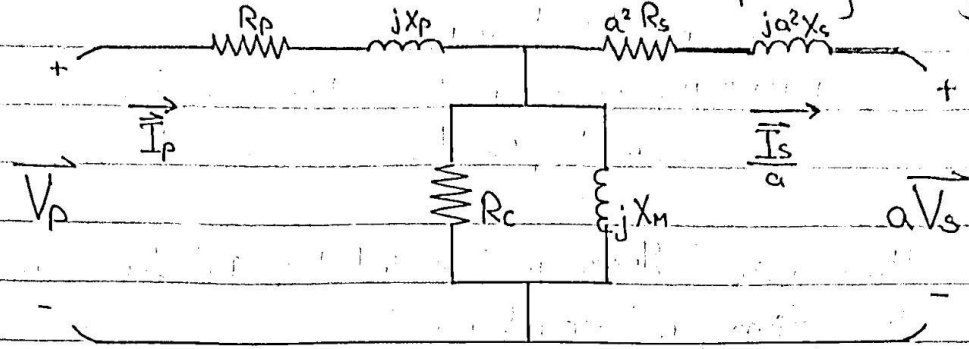→ The transformer model referred to its primary voltage level:




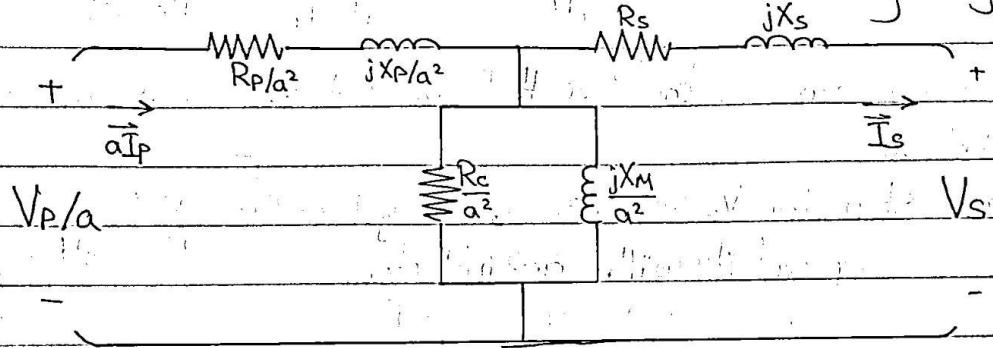→ The transformer model referred to its secondary voltage level:



→ Approximate Equivalent circuits of a transformer:

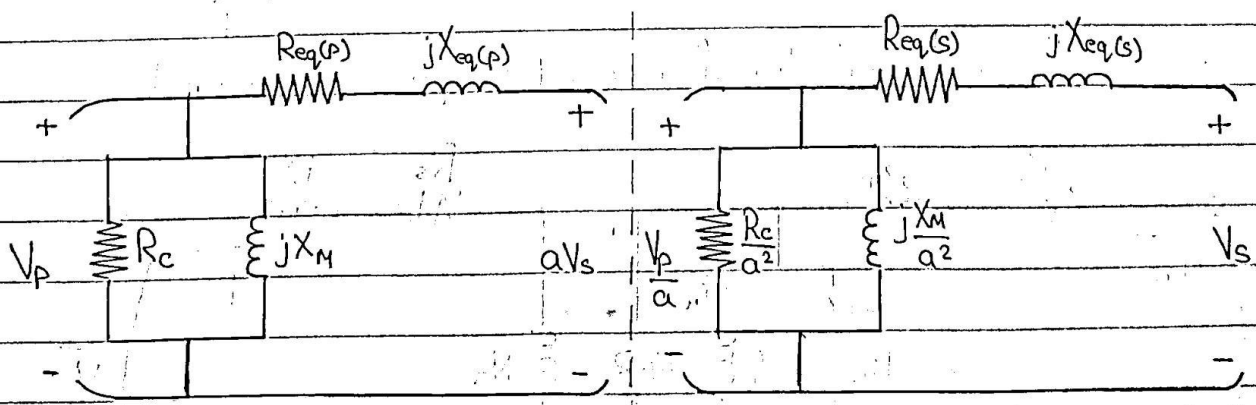The excitation branch has a very small current compared to the load current of the transformer. The excitation branch is simply moved to the front of the transformer and the primary and secondary impedances are left in series with other. This will leave us creating the approximate equivalent circuit showing below:



"Referred to the primary side"

$$i. Req(p) = Rp + a^2Rs$$


$$j. Xeq(p) = jXp + a^2jXs$$

"Referred to the secondary side"

$$i. Req(s) = Rp/a^2 + Rs$$

$$j. Xeq(s) = jXp/a^2 + jXs$$

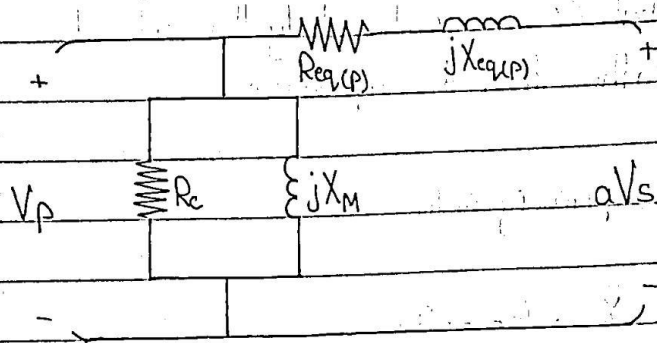→ Determining the values of components in the transformer Model:
 [The parameter of the transformer]




An adequate approximation of $[R_c, jX_m, R_{eq(p)} \& jX_{e(p)}]$ can be obtained with only two tests, the open circuit and the short circuit:

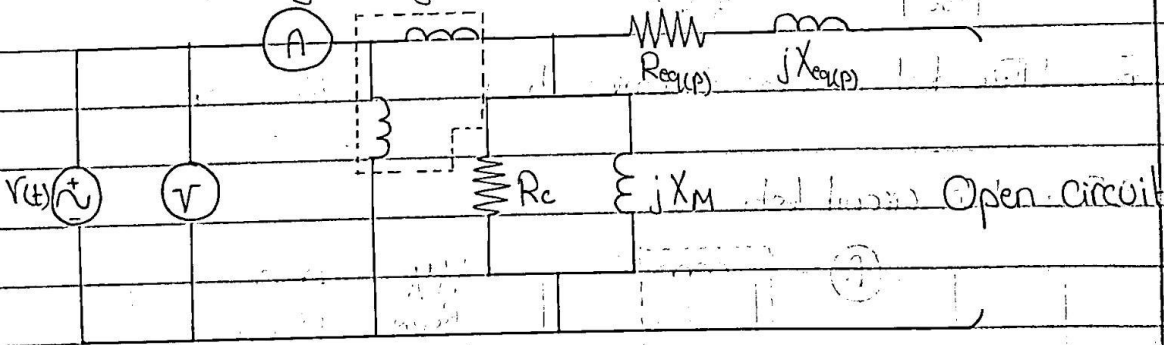1) The open circuit test:

→ The secondary is opened, the primary is connected to full rated line voltage [Ac voltage source].

Note: The primary voltage equals the rated voltage of the transformer



→ The series elements, R_p & X_p are too small in comparison to R_c and X_m to cause a significant voltage drop, so all the input voltage is dropped across the excitation branch.

→ After a full line voltage is applied to one side of the transformer we can measure (read) the input voltage (V_{oc}), the input current (I_{oc}) and the input power (P_{oc}).

→ The impedance seen by the primary side:

$$\vec{Z}_{oc} = \frac{\vec{V}_{oc}}{\vec{I}_{oc}} = R_c \parallel jX_M, \text{ but it's easier to study the admittance rather than the impedance.}$$

→ The admittance seen by the primary side:

$$\vec{Y}_{oc} = \frac{1}{\vec{Z}_{oc}} = \frac{1}{R_c} + \frac{1}{jX_M} \Rightarrow \vec{Y}_{oc} = G_c - jB_M$$

∴ $G_c = \frac{1}{R_c}$ & $B_M = \frac{1}{X_M}$ [The conductance and susceptance]


$$\vec{Y}_{oc} = \frac{\vec{I}_{oc}}{\vec{V}_{oc}} = \frac{|I_{oc}| \angle (\theta_{I_{oc}} - \theta_{V_{oc}})}{|V_{oc}|} = \frac{|I_{oc}|}{|V_{oc}|} \angle -(\theta_{V_{oc}} - \theta_{I_{oc}})$$

we know that the PF = $\cos(\theta_{V_{oc}} - \theta_{I_{oc}}) = \frac{P_{oc}}{V_{oc} I_{oc}}$

So, $\vec{Y}_{oc} = \frac{|I_{oc}|}{|V_{oc}|} \angle -\cos^{-1}\left(\frac{P_{oc}}{I_{oc} V_{oc}}\right)$

From this test we can determine the values of R_c & X_M .

2) The short circuit test:

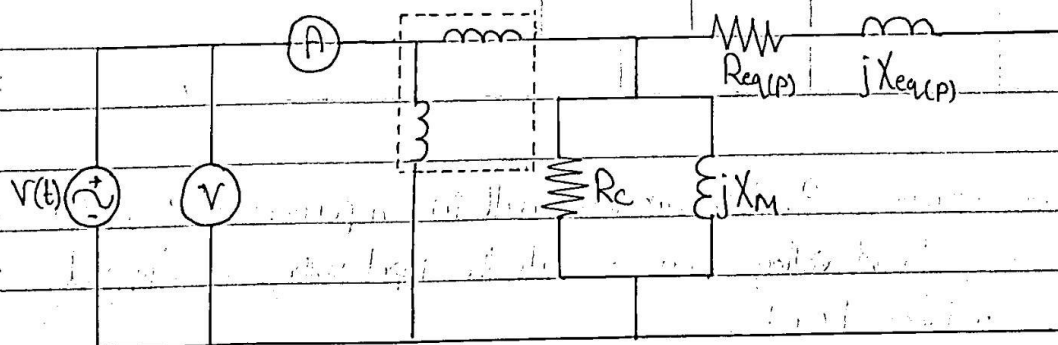

→ The secondary is shorted, and the input AC voltage source is set initially to zero then it's increased gradually until the current in the short circuit is equal to it's rated value.

Note: Be sure to keep the primary voltage at a safe level. If not you will burn the transformer's windings while you test it.

Since the input voltage is low then the load current $\gg i_{e1}$. Then all the voltage drop in the transformer can be attributed to the series elements $[R_{eq(p)} \& X_{eq(p)}]$.

The impedance seen by the primary side:

$$\vec{Z}_{sc} = \frac{\vec{V}_{sc}}{\vec{I}_{sc}} = [(R_{eq(p)} + jX_{eq(p)}) // (R_c // jX_m)] \approx R_{eq(p)} + jX_{eq(p)}$$

$$\vec{Z}_{sc} = \frac{\vec{V}_{sc}}{\vec{I}_{sc}} = \frac{|V_{sc}|}{|I_{sc}|} \angle (\theta_{V_{sc}} - \theta_{I_{sc}}) \quad \text{PF} = \cos(\theta_{V_{sc}} - \theta_{I_{sc}})$$

$$\vec{Z}_{sc} = \frac{|V_{sc}|}{|I_{sc}|} \angle \cos^{-1} \left(\frac{P_{sc}}{V_{sc} I_{sc}} \right)$$

From this test we can determine the values of $R_{eq(p)}$ & $X_{eq(p)}$.

* See example 2-2 page 92-93, [4th & 5th]

The per-unit system (PU):

In this system each electrical quantity is not measured in its SI unit, but it is measured in decimal fraction of some base value.

$$\text{The per-unit quantity} = \frac{\text{Actual quantity}}{\text{base quantity}}$$

Voltage (V), Current (I), Power (Q, P, S), impedance (X, R, Z)

S_b and V_b are selected.

Z_b and I_b are calculated.

$$I_b (\text{magnitude}) = \frac{S_b}{V_b} \quad \& \quad Z_b = \frac{V_b}{I_b} \quad \text{or} \quad \frac{V_b^2}{S_b}$$

S_b [base value of Power, the base value of P, S, Q]

Z_b [base value of impedance, the base value of X, R, Z]

V_b [base value of voltage]

I_b [base value of current]

Note: In power systems, S_b is always constant [since power in equals power out], and V_p changes according to transformer turns ratio.

→ Converge from one base to another base!

$$\textcircled{1} (P, Q, S)_{\text{actual}} = (P, Q, S)_{\text{PU1}} \cdot S_{b1} = (P, Q, S)_{\text{PU2}} \cdot S_{b2}$$

$$\Rightarrow (S, P, Q)_{\text{PU2}} = (S, P, Q)_{\text{PU1}} \cdot \frac{S_{b1}}{S_{b2}}$$

$$\textcircled{2} V_{\text{actual}} = V_{\text{PU1}} \cdot V_{b1} = V_{\text{PU2}} \cdot V_{b2}$$

$$\Rightarrow V_{\text{PU2}} = V_{\text{PU1}} \cdot \frac{V_{b1}}{V_{b2}}$$

$$\textcircled{3} I_{\text{actual}} = I_{\text{PU1}} \cdot I_{b1} = I_{\text{PU2}} \cdot I_{b2} \rightarrow I_{\text{PU2}} = I_{\text{PU1}} \cdot \frac{I_{b1}}{I_{b2}}$$


$$\Rightarrow I_{\text{PU2}} = I_{\text{PU1}} \cdot \frac{S_{b1}}{S_{b2}} \cdot \frac{V_{b2}}{V_{b1}}$$

$$\textcircled{4} (R, X, Z)_{\text{actual}} = (R, X, Z)_{\text{PU1}} \cdot Z_{b1} = (R, X, Z)_{\text{PU2}} \cdot Z_{b2}$$

$$\rightarrow (R, X, Z)_{\text{PU2}} = (R, X, Z)_{\text{PU1}} \cdot \frac{Z_{b1}}{Z_{b2}}$$

$$\Rightarrow (R, X, Z)_{\text{PU2}} = (R, X, Z)_{\text{PU1}} \cdot \left(\frac{V_{b1}}{V_{b2}}\right)^2 \cdot \frac{S_{b2}}{S_{b1}}$$

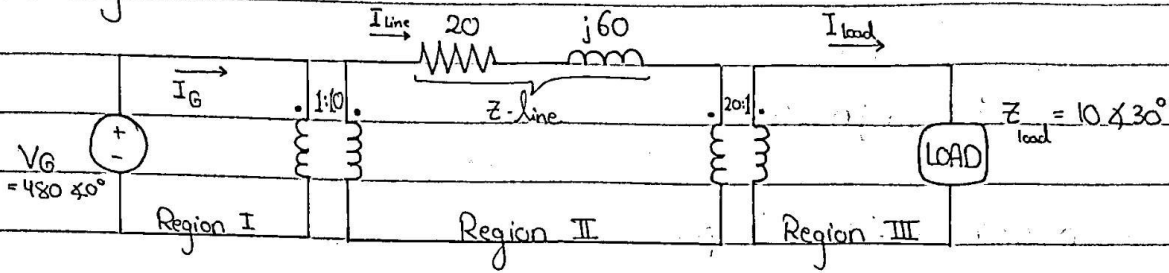Example: A simple power system contains a 480 V generator connected to an ideal 1:10 step-up transformer, a transmission line, an ideal 20:1 step-down transformer and a load. The impedance of the transmission line is $20 + j60 \Omega$ and the impedance of the load is $10 \angle 30^\circ \Omega$. The base values for this system are chosen to be 480 V and 10 KVA at the generator.



a) Find the base Voltage, current, impedance and apparent power at every point in the power system:

Region I	Region II	Region III
1) $S_b = 10,000 \text{ VA}$	1) $S_b = 10,000 \text{ VA}$	1) $S_b = 10,000 \text{ VA}$
2) $V_b = 480 \text{ V}$	2) $V_b = 4800 \text{ [step-up]}$	2) $V_b = 240 \text{ [step-down]}$
3) $I_b = \frac{10,000}{480} = 20.83 \text{ A}$	3) $I_b = \frac{10,000}{4800} = 2.083 \text{ A}$	3) $I_b = \frac{10,000}{240} = 41.67$
4) $Z_b = \frac{480}{20.83} = 23.04 \Omega$	4) $Z_b = \frac{4800}{2.083} = 2304 \Omega$	4) $Z_b = \frac{240}{41.67} = 5.76 \Omega$


b) Convert this system to its per-unit equivalent circuit:

→ Each component must be divided by its base value in its region of the system:

1) $V_{G_{pu}} = \frac{480 \angle 0^\circ}{480} = 1 \text{ pu } \angle 0^\circ$

2) $Z_{line_{pu}} = \frac{20 + j60}{2304} = 0.0087 + j0.026 \text{ pu}$

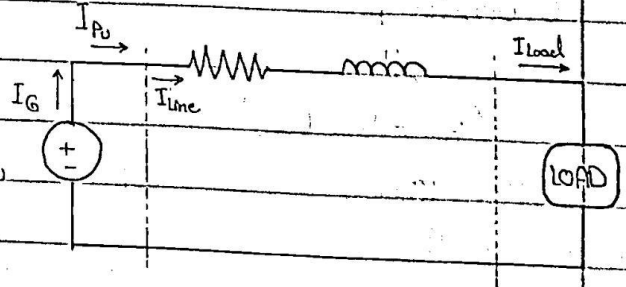3) $Z_{load_{pu}} = \frac{10 \angle 30^\circ}{5.76} = 1.736 \angle 30^\circ \text{ pu}$



Note: $I_{G_{pu}} = I_{line_{pu}} = I_{load_{pu}} = I_{pu}$

c) Find the power supplied to the load:

⚠ The power only dissipated in the resistance Δ

→ The current flowing in this pu system is:

$$I_{pu} = \frac{V_{pu}}{Z_{pu}} = \frac{1 \angle 40^\circ}{(1.736 \angle 30^\circ) + j0.0087 + j0.026}$$

$$= \frac{1 \angle 40^\circ}{1.512 + j0.894}$$

$$= 0.569 \angle -30.6^\circ \text{ pu}$$

The per-unit power $\Rightarrow P_{load \text{ pu}} = (I_{pu})^2 R_{load \text{ pu}}$
 $= (0.569)^2 (1.736 \cos(30))$
 $= 0.487 \text{ pu}$

The power in Watt $\Rightarrow P_{load} = P_{load \text{ pu}} \cdot S_b = \text{VA/S}$
 $= 0.487 \cdot 10,000 \text{ VA}$
 $= 4870 \text{ watt}$

d) Find the power lost in the transmission line:

$$P_{line \text{ pu}} = (I_{pu})^2 R_{line \text{ pu}}$$

$$= (0.569)^2 \cdot 0.0087$$

$$= 0.00282 \text{ pu}$$

The power in watt:

$$P_{line} = P_{line \text{ pu}} \cdot \text{Power base } (S_b)$$

$$= 0.00282 \cdot 10,000$$

$$= 28.2 \text{ watt}$$

Note: We can find the generated power by:

- ① $P_{line} + P_{load}$
- ② $P = VI \cos(\theta_v - \theta_i)$

→ The voltage Regulation of transformer, it's given by,

$$VR = \frac{V_{s, nl} - V_{s, FL}}{V_{s, FL}} \times 100\% \rightarrow \text{but } V_{s, nl} = V_p/a \rightarrow \frac{V_p/a - V_{s, FL}}{V_{s, FL}} \times 100\%$$

$V_{s, nl}$: is the output voltage at no load, [No. current is used].
 $V_{s, FL}$: is the output voltage at full load, [rated current is used].

For the ideal transformer $VR = 0\%$


→ The Transformer phasor Diagram:

To determine the voltage regulations of a transformer, it is necessary to understand the voltage drop within it.

The easiest way to determine the effect of the impedances and the current phase angles is to examine a phasor diagram.

Applying KVL to find the primary voltage:

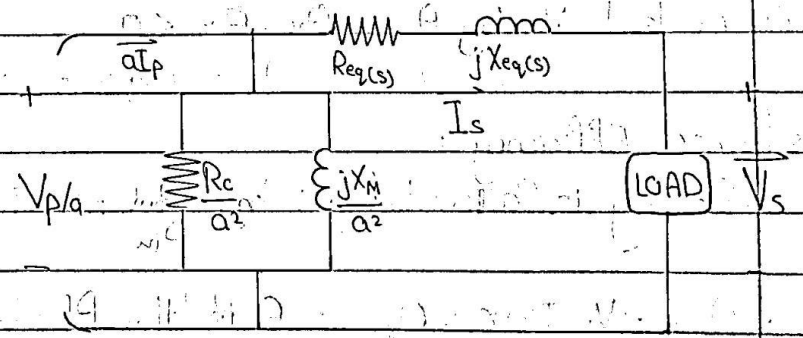
$$V_p/a = V_s + R_{eq} I_s + j X_{eq} I_s$$



The phasor voltage V_s is assumed to be at angle 0°


A Transformer phasor diagram is a visual representation of the KVL equation.

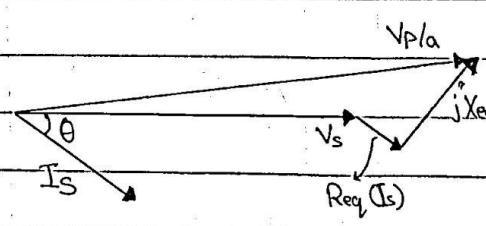□ A Transformer operating at a lagging power factor:




- 1) $V_p/a > V_s \rightarrow VR$ is positive > 0
- 2) losses are small $\rightarrow R$ is small
So, $R_{eq}(I_s)$ is smaller than I_s .
- 3) is lags V_s by θ
 $\theta = \theta_{Vs} - \theta_{Is} > 0$

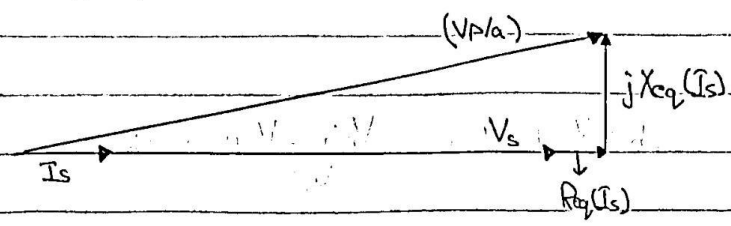2) The unity power factor: $\theta_{V_s} = \theta_{I_s} \rightarrow \theta = 0$



- ① $V_{p/a} > V_s \rightarrow V_R$ is positive > 0
- ② V_R is smaller than V_R in the lagging case.

3) The leading power factor:

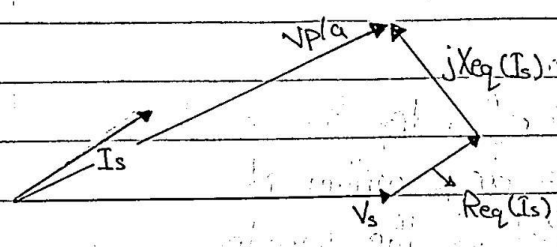

- ① $V_{p/a} < V_s \rightarrow V_s$ is negative
- ② I_s leads V_s by $\theta \rightarrow \theta_{V_s} - \theta_{I_s} < 0$.

Transformer Efficiency:


The efficiency is calculated as: $\eta = \frac{P_{out}}{P_{in}} \times 100\%$

where: $P_{out} = V_s I_s \cos \theta_s$; θ is the PF angle

$P_{in} = P_{losses} + P_{out}$

∴ Losses are presented in three types:

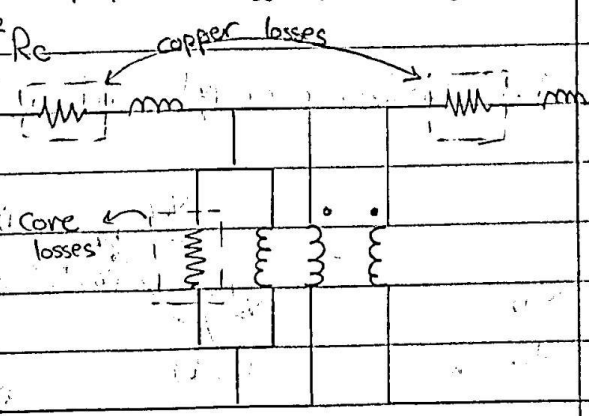- 1) Copper losses (I^2R) $\Rightarrow R_s I_s^2 + R_p I_p^2 = R_{eq(p)} I_p^2 = R_{eq(s)} I_s^2$
- 2) Hysteresis losses $\rightarrow [i(\epsilon + \omega)]^2 R_c$
- 3) Eddy current losses $\rightarrow [i(\epsilon + \omega)]^2 R_c$




Then the efficiency can be expressed as:

$\eta = \frac{V_s I_s \cos \theta_s}{P_{copper} + P_{core} + V_s I_s \cos \theta_s} \times 100\%$


Simplified VR calculations:

For lagging PF operation, the vertical components of $R_{s,eq} + X_{s,eq}$ will partially cancel each other. Therefore, the angle of $\vec{V}_{p/a}$ will be small.

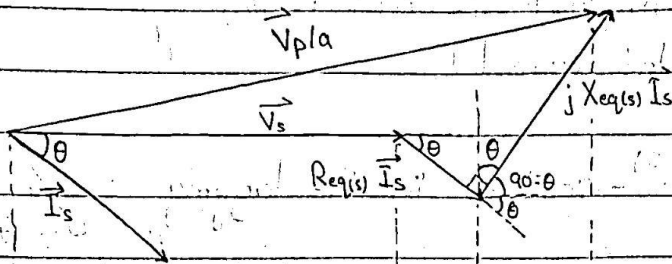* $\vec{V}_{p/a}$ can be assumed horizontal



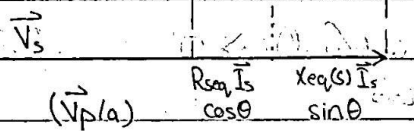$\vec{V}_{p/a}$ can be replaced by a horizontal vector:



Since the angle between \vec{V}_s & $\vec{V}_{p/a}$ is too small

$$\left[\frac{V_p}{a} = V_s + R_{eq(s)}I_s \cos\theta + X_{eq(s)}I_s \sin\theta \right] \text{ as magnitudes}$$

* See example 2-5 page 103 4th & page 102 5th

How to think:

- ① Note: Notice the data, is it taken from the primary or the secondary?
- ② To find the equivalent circuit: i - Find Y_{oc} from the open circuit test. ii - Find Z_{sc} from the short circuit test.

Since the data is on the primary we can draw the equivalent circuit referred to the primary. we can simply find the equivalent referred to the secondary [low voltage] by changing $V_p \rightarrow V_{p/a}, Z_p \rightarrow Z_p/a^2, I_p \rightarrow aI_p$.
 ③ $aV_s \rightarrow V_s, I_s/a \rightarrow I_s$.

③ In VR calculations:

① write the equation: $\vec{V}_{P/a} = (R_{eq}(s) + jX_{s,eq}) \vec{I}_s + \vec{V}_s$

② you have $(R_{eq}(s) \& jX_{eq}(s))$, $(V_{s,PL})$ so you need to find only \vec{I}_s :-

↳ it has a magnitude & angle:

Magnitude: $\frac{S_{rated}}{V_{rated}}$ [rated current]

To find the angle: a) $-\cos^{-1}(PF)$ in the lagging :- $\theta_v - \theta_i > 0$
 $0 - \theta_i > 0 \rightarrow \theta_i > 0$

$\theta_i < 0$

b) $\cos^{-1}(PF)$ in the leading

in $\theta_v - \theta_i < 0 \rightarrow -\theta_i < 0 \rightarrow \theta_i > 0$

③ $VR = \frac{V_{P/a} - V_{s,P}}{V_{s,P}} \times 100\%$

Notes :- in the unity PF $\rightarrow \theta = 0 \rightarrow \theta_v - \theta_i = 0 \rightarrow \theta_i = 0$

* We can find $V_{P/a}$ in the lagging part in the simplified calculations:

$|V_{P/a}| = R_{eq}(s) |I_s| \cos(\theta) + X_{eq}(s) |I_s| \sin(\theta) + |V_s|$

④ The efficiency: $\eta = \frac{P_{out}}{P_{out} + P_o + P_{loss}}$ find all these powers.

→ The problem of the Magnetic Inrush current:

This problem is related to the voltage level in the transformer at the starting.

Inrush current: It's a huge current that will flow in the primary windings when the secondary is first connected to the power line. At this moment the primary voltage is passing through zero.

Assume that the primary voltage $V_p(t) = V_m \sin(\omega t + \theta)$ volt, and by assuming (ω) the frequency is constant then by "Farady's Law":

$$V_p(t) = N_p \frac{d\Phi}{dt}$$

Then the Flux in the core $\Phi(t)$ is:

$$\begin{aligned} \Phi(t) &= \frac{1}{N_p} \int V_p(t) dt \\ &= \frac{1}{N_p} \int V_m \sin(\omega t + \theta) dt \\ &= -\frac{V_m}{\omega N_p} \cos(\omega t + \theta) + A \end{aligned}$$

; $\frac{V_m}{\omega N_p}$ is the max Flux Φ_m

$$\Phi(t) = -\Phi_m \cos(\omega t + \theta) + A$$

At the starting moment ($t=0$), there is a flux lefted in the core:

$$\Phi(0) = \Phi_R \text{ [Residual Flux]} = -\Phi_m \cos(\theta) + A$$

$$\text{So, } A = \Phi_R + \Phi_m \cos(\theta)$$

$$\text{Then, } \Phi(t) = -\Phi_m \cos(\omega t + \theta) + \Phi_R + \Phi_m \cos(\theta)$$

Assuming that $\phi_r = 0$, Then the Flux is given by:


$$\phi(t) = -\phi_m \cos(\omega t + \theta) + \phi_m \cos(\theta)$$

Another Assumption that $\theta = 0^\circ$ & $\omega t = \pi$, then the Flux is:

$$\phi(t) = -\phi_m \cos(\pi) + \phi_m \Rightarrow \phi(t) = 2\phi_m \quad \therefore t = \frac{\pi}{\omega} = \frac{1}{2f}$$


→ The worst case: $[\theta = 0 \text{ \& } \omega t = \pi, t = \frac{1}{2f}]$

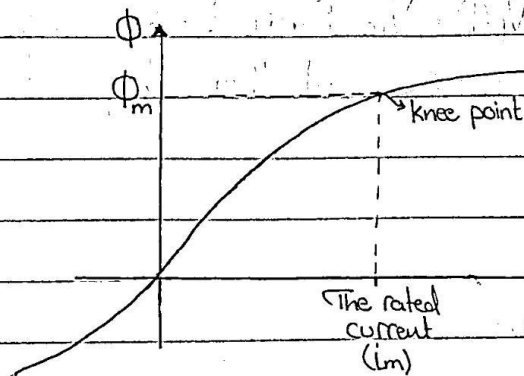In this case the maximum value of the Flux will be twice the normal steady-state peak value of the Flux.



From the curve it is easy to notice that doubling ϕ_m will result in an enormous magnetization current.

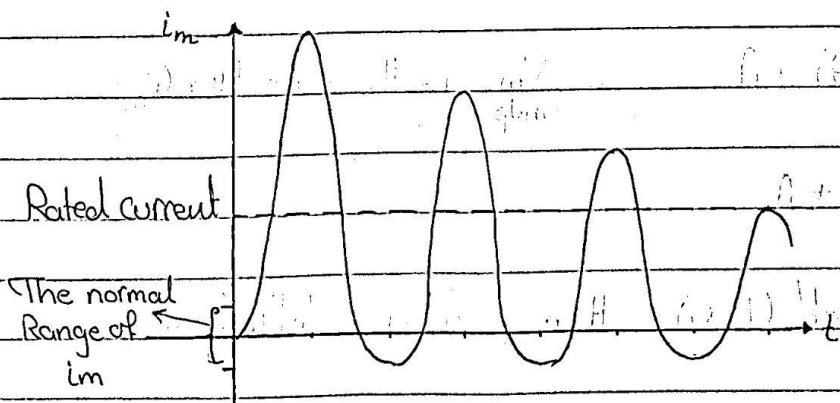So, since the core is designed to operate at the knee point on the magnetizing current, a huge starting current will flow for part of the cycle.



→ The transformer must be able to withstand the starting inrush current.

→ Transformer differential protection:

The transformer should be able to discriminate between the fault current and the inrush current.

Note: The inrush current contain a significant 2nd harmonic component.

There are two ways to avoid this:

- 1) The 2nd harmonic component protection
- 2) Gap protection technique

→ The Autotransformer:

Some-times it's needed to change voltage levels by a small amount, such as, increasing the voltage drops that occur in power systems a long way from the generator, but it's expensive to wind a two windings transformer. So, a special purpose transformer called "Autotransformer" is used.

It converts a fixed AC voltage to variable AC voltage:


It consists of two windings:

a) The common winding:

- i it's common between input and output parts
- ii it has N_c turns, V_c voltage, I_c current

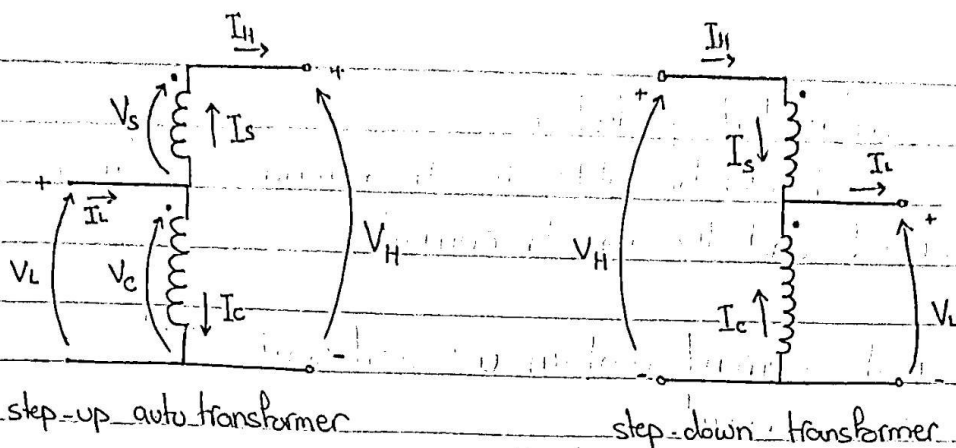b) The series winding:

- i it's connected in series with the common coil & smaller
- ii it has N_s turns, V_s voltage, I_s current.



From the step-up autotransformer figure:

$$\textcircled{1} V_s = N_s \frac{d\Phi}{dt} \quad \& \quad V_c = N_c \frac{d\Phi}{dt}$$

$$\rightarrow \frac{V_c}{V_s} = \frac{N_c}{N_s} \quad \textcircled{1}$$

$$\left. \begin{array}{l} * V_H = V_c + V_s \\ V_L = V_c \end{array} \right\} \rightarrow \frac{V_H}{V_L} = \frac{V_s}{V_c} + 1 \quad \text{OR} \quad \frac{V_L}{V_H} = \frac{N_s}{N_s + N_c} + 1$$

* in terms of the turns:

$$\frac{V_L}{V_H} = \frac{N_c}{N_s + N_c} \quad \text{Note } V_H \text{ is Fixed.}$$

$$\rightarrow N_c I_c = N_s I_s \quad \textcircled{2}$$

$$\left. \begin{array}{l} * I_L = I_c + I_s \\ I_H = I_s \end{array} \right\} \rightarrow \frac{I_L}{I_H} = \frac{I_c}{I_s} + 1$$

* in terms of the turns:

$$\frac{I_L}{I_H} = \frac{N_c + N_s}{N_c}$$

② Apparent power

The input apparent power [low voltage side] equals the output apparent power [high voltage side].

$$S_{in} = S_{out}$$

$$V_L I_L = V_H I_H$$

Three-phase transformers:

Transformers for three-phase circuits can be constructed in two ways:


① A Bank composed of three single-phase transformers.

This type has an advantage in:

→ That each unit in the bank could be replaced individually in the event of trouble

And has some disadvantages in:

→ That it's heavy and expensive.

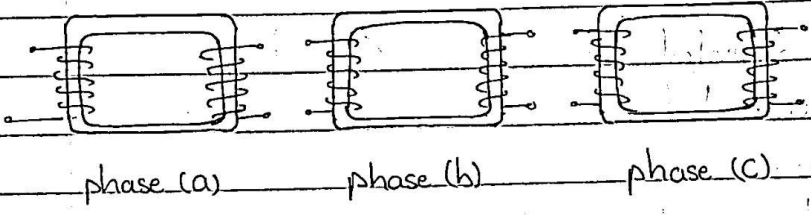


② A common Ferromagnetic core with 3- Φ transformers windings wrapped on it.

This type has some advantages in:

→ That it's smaller, cheaper, lighter and more efficient

And has some disadvantages in:

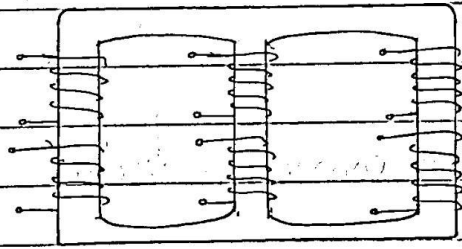→ That any problem in the core will affect the total work of the transformer.



phase (a) phase (b) phase (c)

There are four possible connections for a 3- Φ transformer

① Wye - Wye [Y-Y]

② Wye - delta [Y- Δ]

③ delta - Wye [Δ -Y]

④ delta - delta [Δ - Δ].

→ Winding connection and Vector Diagram:

Example: Yd11: Y is the connection of the high voltage side.
d is the connection of the low voltage side.
11 is the rotation from Y to d in hours.


Notes: Y: High voltage side Y-connected
D: High voltage side Δ-connected

y: low voltage side Y-connected
d: low voltage side Δ-connected

→ In the step-up transformer:


The primary is the low voltage.
The secondary is the high voltage.

Again looking into "Yd11" example:

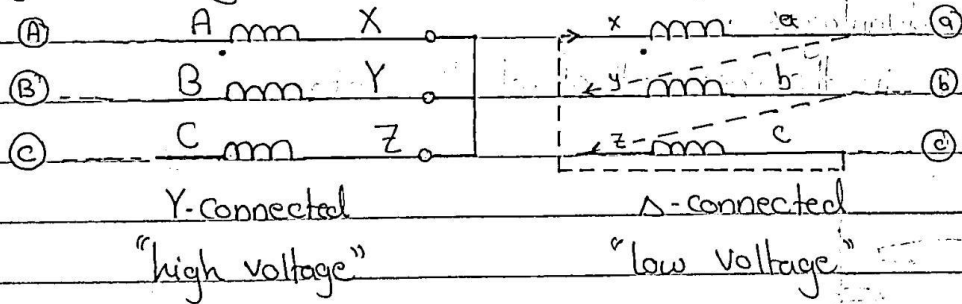


The question is: How can we determine the Δ-connection vectors or directions?

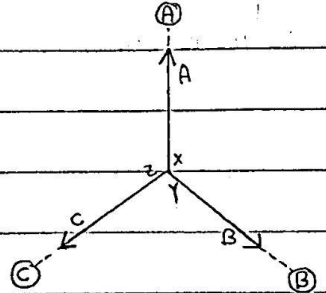① Draw the Y-connected side as the reference, let it take the shape of the clock [12 hours]



Rotate the abc sequence clock wise

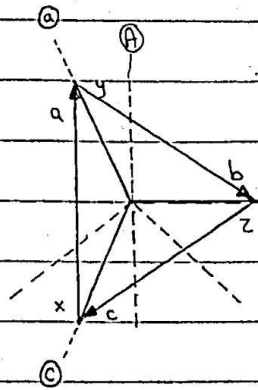② Draw the delta connection, be aware of the rotation Δ . Here it is 11 hours, which mean that you should rotate the high voltage diagram 11 hours to get the starting point of the low voltage diagram.




Studying this diagram leads to:


- ① The $\vec{x}\vec{a}$ vector is in the direction of the $\vec{X}\vec{A}$ vector in the Y-connection
- ② The rotation has been done clockwise
- ③ (a) & (y) are both connected at (a) terminal
(b) & (z) " connected at (b) terminal
(c) & (x) are connected at (c) terminal

these three connections have determined the Δ -connection shape

Another example: "Yd1"

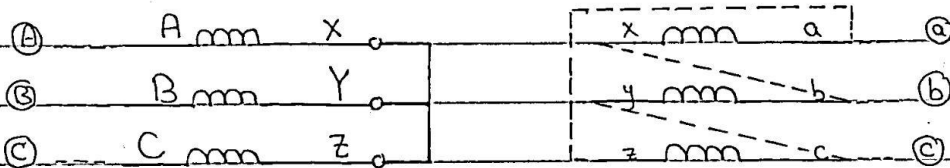

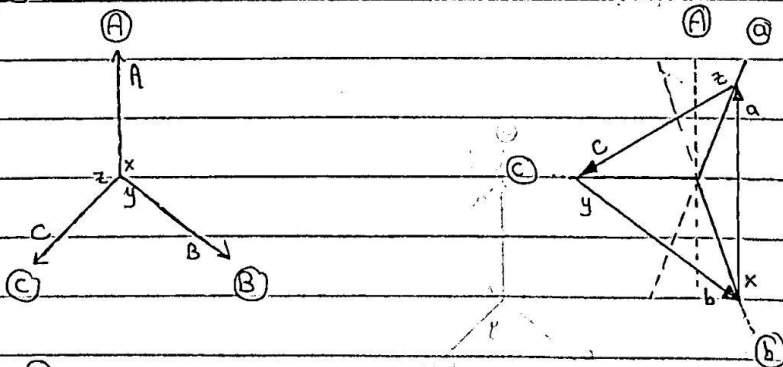
To draw the vector diagram we will follow the previous steps:



Note: ① in the Δ -connection it's not the vector's direction which is in the clockwise rotation, but it's abc sequence

- ② The direction of $\vec{X}\vec{A}$ is the same as $\vec{x}\vec{a}$
- " " " $\vec{Y}\vec{B}$ is the same as $\vec{y}\vec{b}$
- " " " $\vec{Z}\vec{C}$ is the same as $\vec{z}\vec{c}$

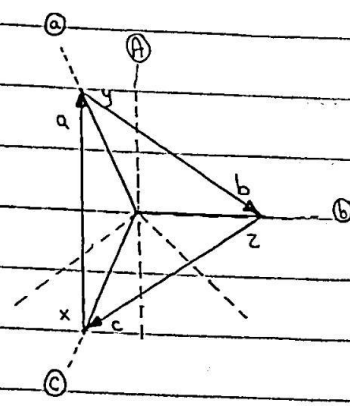② Draw the delta connection, be aware of the rotation Δ . Here it is 11 hours, which means that you should rotate the high voltage diagram 11 hours to get the starting point of the low voltage diagram.




Studying this diagram leads to:


- ① The $\vec{x}\vec{a}$ vector is in the direction of the $\vec{X}\vec{A}$ vector in the Y-connection
- ② The rotation has been done clockwise
- ③ (a) & (y) are both connected at ① terminal
(b) & (z) " connected at ② terminal
(c) & (x) are connected at ③ terminal

these three connections have determined the Δ -connection shape.

Another example: "Yd1"

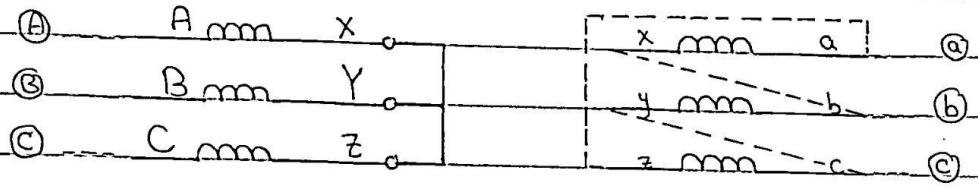

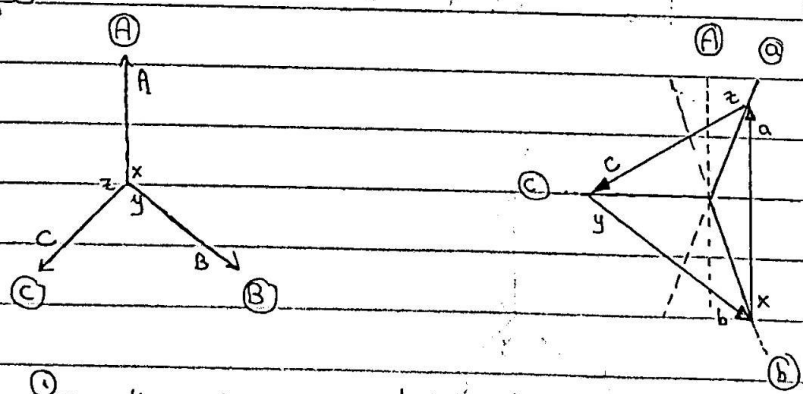To draw the vector diagram we will follow the previous steps:




Note: ① in the Δ -connection it's not the vector's direction which is in the clockwise rotation, but it's abc sequence


- ② The direction of $\vec{X}\vec{A}$ is the same as $\vec{x}\vec{a}$
- " " " $\vec{Y}\vec{B}$ is the same as $\vec{y}\vec{b}$
- " " " $\vec{Z}\vec{C}$ is the same as $\vec{z}\vec{c}$

The previous two examples, the high voltage was connected as Y-connection, in the next two examples the high voltage will be connected as Δ -connection.


Example: "Dy5"

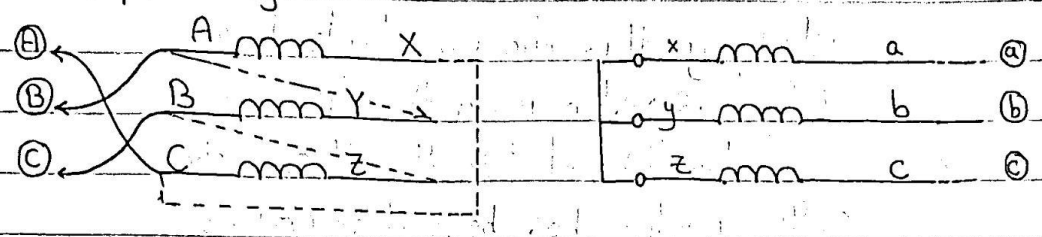


Now the vector diagram:

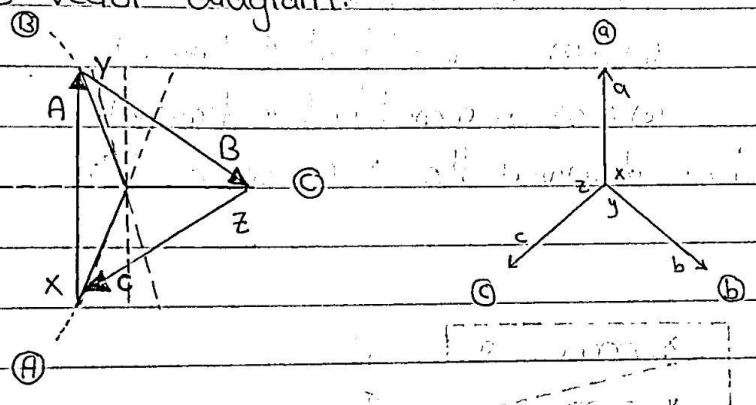

Example: "Dy7"

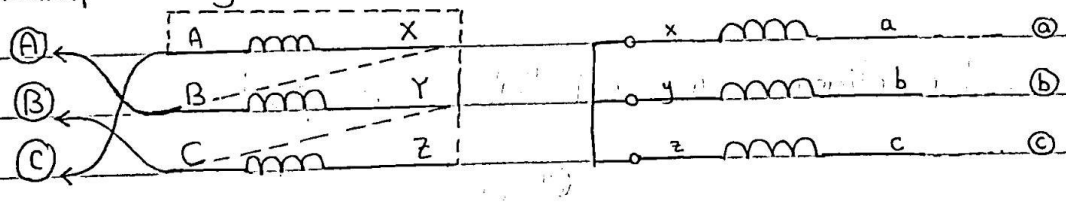


The vector diagram:

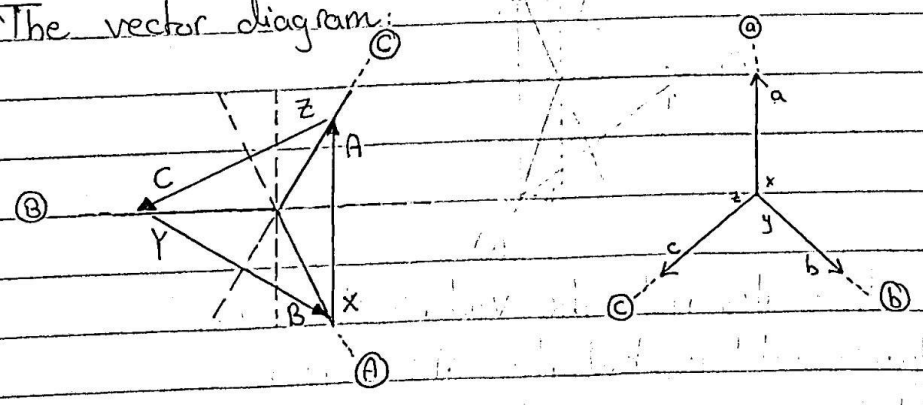

Winding connection in 3- ϕ transformer.

1] Wye-Wye connection (Y-Y):

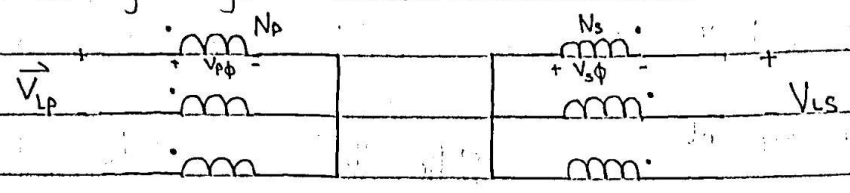


$$\frac{\vec{V}_{lp}}{\vec{V}_{ls}} = \frac{\vec{V}_{p\phi}}{\vec{V}_{s\phi}} = \frac{N_p}{N_s} = a$$

This type has two very serious problems:

① If the loads on the transformer circuit are unbalanced, then the voltages on the phases of the transformer can become severely unbalanced.

② Third-harmonic problem due to non-linearity of the core.

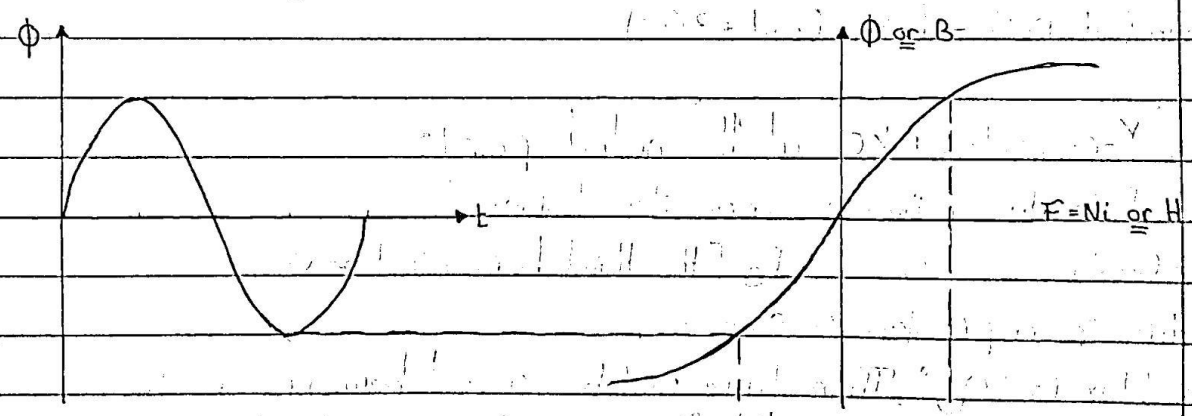
The non-linearity because of [saturation, hysteresis].



if the Flux ϕ is sinusoidal then i_m is peaky in "nature". Since i_m is periodic signal then we can represent it using Fourier series:


$$i_m = \sum_{n=1}^{\infty} C_n \sin(n(\omega t + \phi))$$

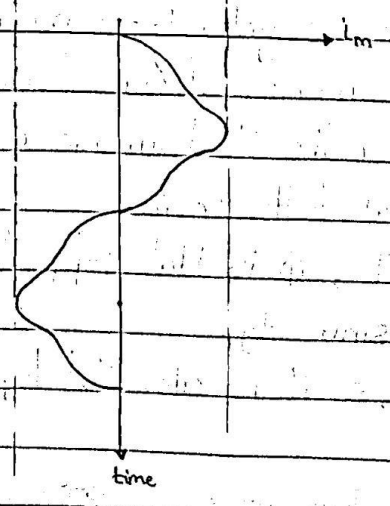when $n=1$, The fundamental component while $n=2, 3, 4, \dots, n$ they are all harmonics.



→ Since i_m is half-wave symmetry, i_m has only odd harmonics [3, 5, ...] and the 3rd harmonic causes the peaky nature.

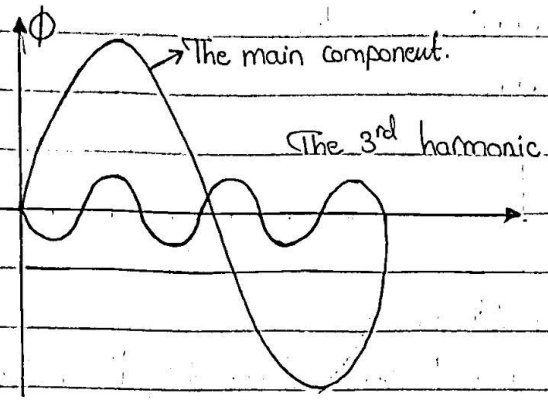→ The fundamental component and the 3rd harmonic can be represented as:



* Notice that each 3rd harmonic rise the peak of the main component

* $i_m = i_{m1} + i_{m3} + i_{m5} + \dots$
"The main component & the harmonics"

As we are talking about three phase, Then:

$$I_a = I_1 \sin(\omega t) - I_3 \sin(3\omega t) + \dots$$

$$I_b = I_1 \sin(\omega t - 120^\circ) - I_3 \sin(3\omega t - 360^\circ) + \dots$$

$$I_c = I_1 \sin(\omega t + 120^\circ) - I_3 \sin(3\omega t + 360^\circ) + \dots$$

Since it's Y-connected: KCL at the neutral points:

$$I_a + I_b + I_c = I_n \quad ; \quad I_n = 0 \text{ since it's balanced}$$

$$-3I_3 \sin(3\omega t) = 0 \quad \rightarrow \quad I_3 \text{ [the third harmonic]} = 0$$

But this is a problem :- Since:

① If the flux is "flat topped", Then there will be a 3rd harmonic in i_m .


② If the i_m is "flat topped", Then the flux is flat top [saturated]

The result we get: $I_3 = 0$ means that:

No triple harmonics of current will flow in Y-Y connection if there is no return path for the 3rd harmonic currents between the neutral of the transformer and the neutral of the source.

As a result, ϕ is flat topped, which does not vary sinusoidally.

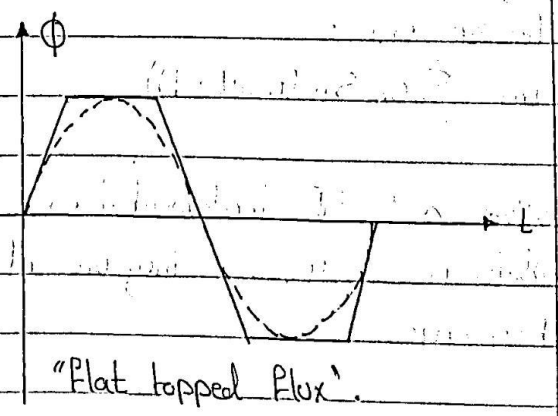$e_{ind} \propto \frac{d\phi}{dt}$, so it is also flat topped.



* Math Note: Any three waves are 120° separated from each other, their sum is zero.

Solution to the Y-Y problems:

- 1) Solidly grounding the neutral point of the transformer especially the primary windings.


This allow the 3rd Harmonic current to flow in the neutral instead of building up large 3rd Harmonic voltages.

$$I_N = 3i_3 \neq 0 \rightarrow i_m = i_1 + i_2 + i_3$$

2) ϕ is sinusoidal

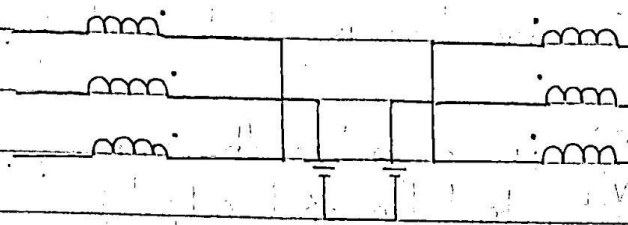3) e_{ind} is sinusoidal.

This also provides a return path for any current imbalances in the load.



- 2) Adding a tertiary (trith) winding connected in Δ .

This winding allows the 3rd Harmonic current to flow as a circulating current in the Δ winding. Hence, restoring the flux to be sinusoidal again.


This winding is usually used to feed light loads in the substation [small motors].

Rated power of tertiary winding = $\frac{1}{3}$ rated power of the main winding.

In the case of unbalanced load the current which is imbalances will circulate in the Δ winding.

This tends to equalize the phase voltages and distribute the unbalances load more equally among the primary phases.

2] Wye-Delta connection (Y- Δ)

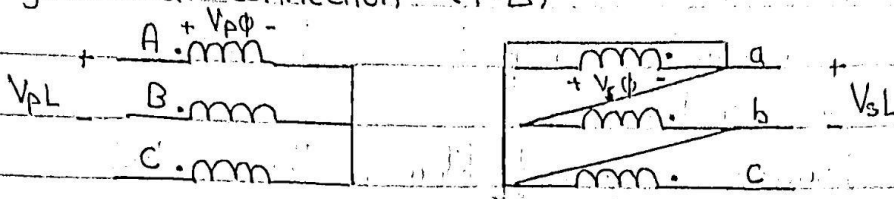

$$\vec{V}_{pL} = \sqrt{3} \angle 30^\circ \vec{V}_{p\phi} \Rightarrow \frac{\vec{V}_{pL}}{\vec{V}_{sL}} = \frac{N_p}{N_s} \sqrt{3} \angle 30^\circ = a \sqrt{3} \angle 30^\circ$$

$$\vec{V}_{sL} = \vec{V}_{s\phi}$$


* \vec{V}_{sL} lags V_{pL} by 30° , this can be assumed as a disadvantage.

* While the advantages are:

1) No 3rd Harmonic problem. The connection is stable with respect to unbalanced load.

2) Since " $\sqrt{3}$ " has appeared in \vec{V}_{pL} , we can reduce the primary windings and gets the same \vec{V}_{sL} output [required output].

3] Delta-Wye connection (Δ -Y)

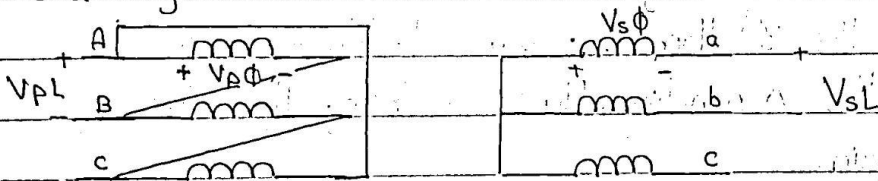


$$\vec{V}_{pL} = \vec{V}_{p\phi} \Rightarrow \frac{V_{pL}}{V_{sL}} = \frac{a}{\sqrt{3}} \angle -30^\circ$$

$$\vec{V}_{sL} = \sqrt{3} \angle 30^\circ \vec{V}_{s\phi}$$

Disadvantage: $V_{L_s}(t)$ leads $V_{p}(t)$ by 30° .

Advantage: The same advantages of Y- Δ connection.

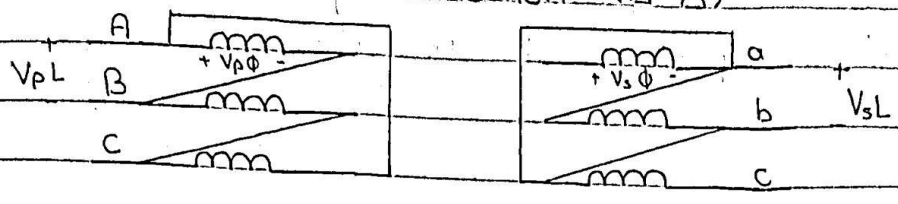4) Delta-Delta connection ($\Delta-\Delta$)



$$\vec{V}_{pL} = \vec{V}_{p\phi} \rightarrow \vec{V}_{pL} = a$$

$$\vec{V}_{sL} = \vec{V}_{s\phi}$$

Advantages:

- 1) No phase shift between V_{pL} and V_{sL}
- 2) No third Harmonic
- 3) stable with respect to unbalanced load

Disadvantage:

A detection of (line to ground) faults can not be done using $\Delta-\Delta$

→ The Per-Unit system for Three-Phase Transformers:

1) If the total base complex power of the three-phase transformer is S_{base} , then one of the transformer's base complex power is $S_{1\phi, base}$

$$S_{base} = 3S_{1\phi, base} \quad \text{①}$$

$$S_{base} = 3S_{1\phi, base} \quad \text{②}$$

$$S_{base} = \sqrt{3} V_{L, base} I_{L, base} = 3V_{\phi, base} I_{\phi, base} \quad \text{③}$$

2) Current:

$$I_{L, base} = \frac{S_{base}}{\sqrt{3} V_{L, base}}$$

3) impedance:

$$Z_{base} = \frac{V_{\phi, base}^2}{S_{1\phi, base}} = \frac{3V_{\phi, base}^2}{S_{base}}$$

* The relationship between the base line voltage and the base phase voltage depends on the connection:

In delta (Δ):

$$1) V_{L, \text{base}} = V_{\phi, \text{base}}$$

In Wye (Y):

$$1) V_{L, \text{base}} = \sqrt{3} V_{\phi, \text{base}}$$

* The base line current:

$$I_{L, \text{base}} = \frac{S_{\text{base}}}{\sqrt{3} V_{L, \text{base}}}$$

Example (2-9) :-

A 50-kVA, 13800/208-V, Δ -Y distribution transformer has a resistance of 0.01 & a reactance of 0.07 per-unit.

a) What is the transformer's phase impedance referred to the high voltage side?

Notes:

1) The 50-kVA is the $S_{3\phi}$ rating.

2) The 13800/208-V are the line-to-line (rms) value.

How to start solving such questions:

① High-voltage side has 13800 base line voltage and has a 50-kVA base power.

② Since it's Δ connected: $V_L = V_{\phi}$

③ Use the equation: $Z_{\text{base}} = \frac{3 V_{\phi, \text{base}}^2}{S_{\text{base}}} = \frac{3 \cdot (13800)^2}{50000} = 11426 \Omega$

④ $Z_{\text{eq}}(\text{pu}) = \frac{Z_{\text{eq}}}{Z_{\text{base}}} \Rightarrow Z_{\text{eq}} = Z_{\text{base}} \cdot Z_{\text{eq}}(\text{pu})$


$$\begin{aligned} Z_{\text{eq}} &= 11426 \cdot (0.01 + j0.07) \\ &= 114.2 + j800 \Omega \end{aligned}$$

b) Calculate this transformer's voltage regulation at Full Load and 0.8 PF lagging, use the calculated high-side impedance.

→ To calculate the voltage regulation of a 3- ϕ transformer, you can determine the VR of any single phase transformer. So, The voltages on a single phase are phase voltages:

① $VR = \frac{V_{\phi p} - aV_{\phi s}}{aV_{\phi s}} \times 100\%$ ② $VR = \frac{V_{\phi p}}{a} - V_{\phi s} \times 100\%$

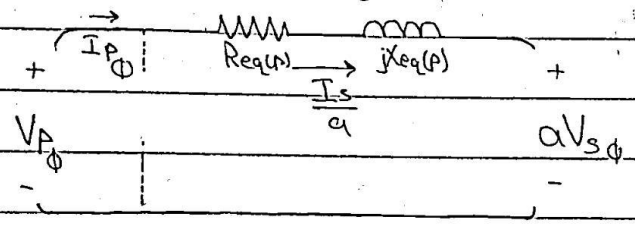We use equation ① if the transformer model is drawn referred to the primary, and since the question ask to use the equivalent primary impedance:



$V_{\phi p} = (R_{eq(p)} + jX_{eq(p)})I_{\phi p} + aV_{\phi s}$

$\therefore i) aV_{\phi s} = \frac{13800}{\sqrt{3}} \cdot \left(\frac{208}{\sqrt{3}}\right) = 13800$ Note $a \neq \frac{13800}{208}$ because the connection is Δ -Y.

$ii) I_{\phi p} = \frac{S_{1\phi}}{V_{\phi}} = \frac{50000}{3 \cdot 13800} = 1208 \text{ A}$

$V_{\phi p} = (114.2 + j800)1208 \angle -\cos^{-1}(PF) + 13800 \angle 0^\circ$


Note: The current angle is $-\cos^{-1}(PF)$ since θ is lagging.

$V_{\phi p} = 14506 \angle 2.73^\circ$

→ $VR = \frac{14506 - 13800}{13800} \times 100\% = \underline{\underline{5.1}}$

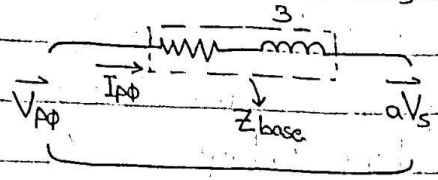c) Calculate the voltage regulation under the same conditions using the per-unit system.

Take $S_{base} = 50000$, $V_{base} = 13800$, $I_{base} = 1.208$



1) Z_{pu} (given) $= (0.01 + j0.07)$


2) $aV_s = 13800 \rightarrow aV_s(pu) = \frac{aV_s}{V_{base}} = \frac{13800}{13800} = 1 \angle 0^\circ$

3) $I_\phi = 1.208 \angle -36.87^\circ \rightarrow I_\phi(pu) = \frac{I_\phi}{I_{base}} = 1 \angle -36.87^\circ$

$V_{\phi p}(pu) = aV_s(pu) + (0.01 + j0.07) I_\phi(pu)$
 $= 1.051 \angle 2.73^\circ$

$VR(pu) = \frac{1.051 - 1}{1}$ since it's $\frac{V_{\phi p} - aV_s}{aV_s} \Rightarrow \boxed{5.1\%}$


The Open- Δ connection

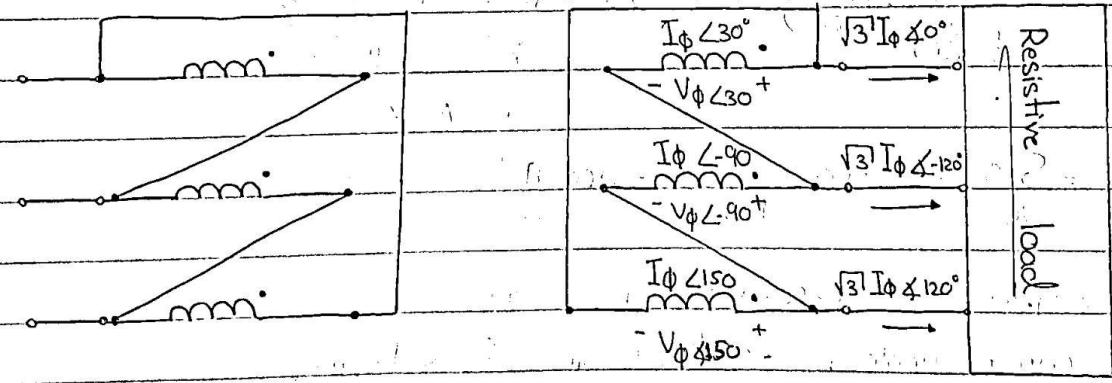

In Δ - $I_L = \sqrt{3} I_\phi \angle -30^\circ$

Since the load is Resistive, then $\theta = \theta_v - \theta_i = 0$

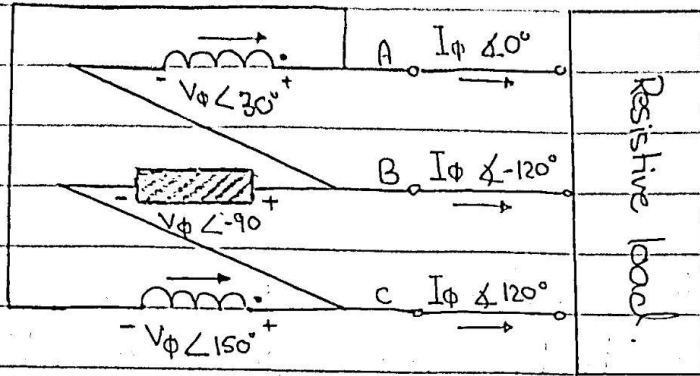
Assume that one of the phases is damaged, and hence it is removed for repair.



* It's important to note the angles on the voltages and currents in the 3- ϕ transformer.

1] Because one transformer is missing; the transmission line current is now equal to the phase current in magnitude. So " $\sqrt{3}$ " is gone now.

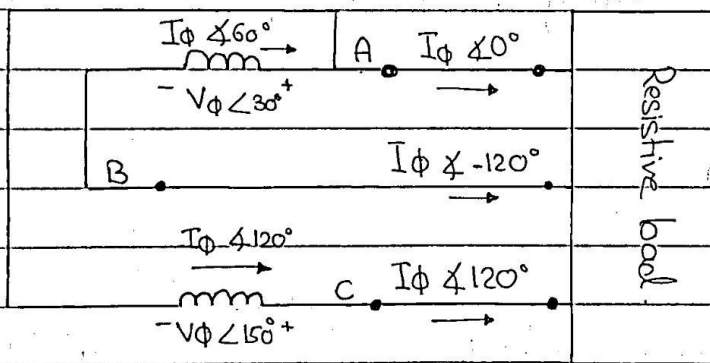2] The currents and voltages in the transformer's bank differ in angle by 30° .



Note: How the angle of the phase current is 60° ?

$$I_\phi \angle +60^\circ = -I_\phi \angle -120^\circ \rightarrow I_\phi \angle -120^\circ + 180^\circ = I_\phi \angle 60^\circ \quad \#$$

Note: Since one transformer has gone we expect the power to be dropped to $\frac{2}{3}$ of the original power. But: Studying each remaining transformer lead to a different conclusion:

$$i. P_1 = V_\phi I_\phi \cos(30 - 60) \\ = \frac{\sqrt{3}}{2} V_\phi I_\phi \quad \text{--- (1)}$$

$$\text{ii. } P_2 = V_\phi I_\phi \cos(150 - 120) \\ = \frac{\sqrt{3}}{2} V_\phi I_\phi$$

iii. $P_3 = 0$ since it's gone.

$$\text{The total power} = \sqrt{3} V_\phi I_\phi$$

Notice that the ratio of the output power available from the open-delta 3- ϕ transformer, to the output power available from the normal 3- ϕ transformer is:

$$\frac{P_{\text{open-}\Delta}}{P_{\Delta-\Delta}} = \frac{\sqrt{3} V_\phi I_\phi}{3 V_\phi I_\phi} = 57.7\% \text{ which is less than } \frac{2}{3} \text{ as expected.}$$

Now another question appears, where has the Power difference gone?


To understand that let's study the reactive power:

$$1) Q_1 = V_\phi I_\phi \sin(30 - 60) \\ = -\frac{1}{2} V_\phi I_\phi$$

$$2) Q_2 = V_\phi I_\phi \sin(150 - 120) \\ = \frac{1}{2} V_\phi I_\phi$$

Therefore, one transformer producing reactive power while other is consuming.

Chapter 3: AC Machinery Fundamentals

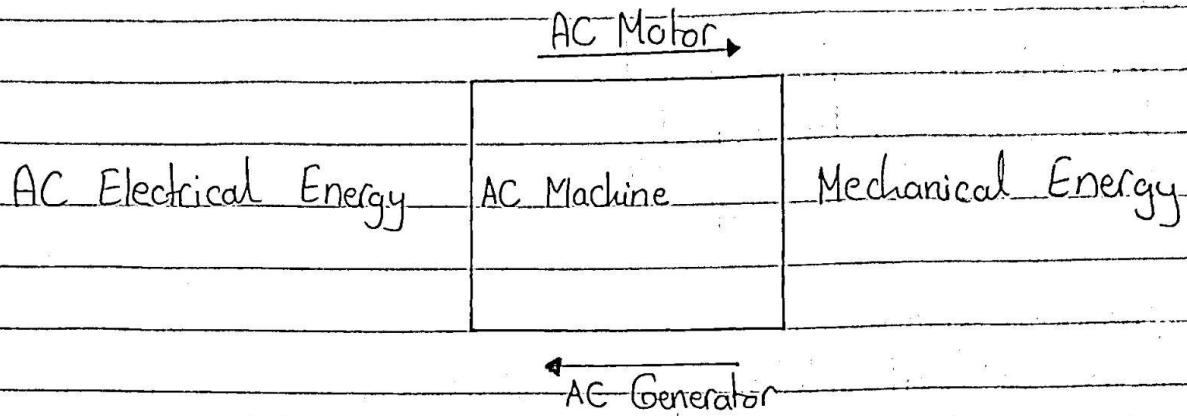

→ Types of AC Machine:

1) Synchronous Machine:

They are generator or motors whose field current is supplied by a separate [external] DC source.


2) Induction Machine:

They are generators or motors whose magnetic field current is supplied by magnetic induction [transformer action] into their field windings.

→ Construction of AC-Machine:

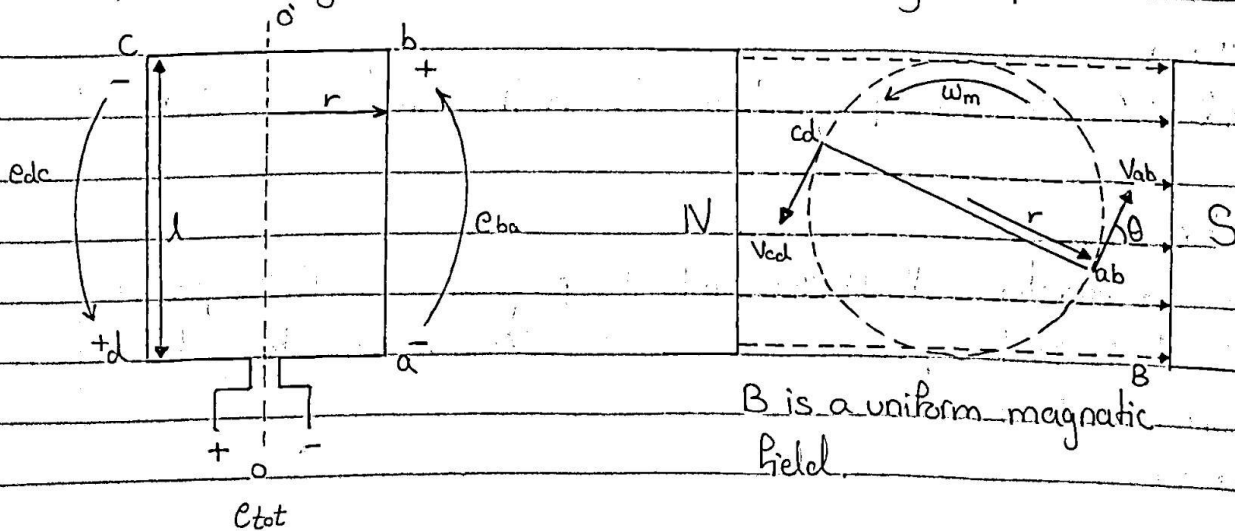- 1) Rotor: The rotating part in the machine.
- 2) Stator: The stationary part [which carries a high current].

→ The Voltage induced in a simple rotating loop:



Each segment will induce a voltage from the relation:

$$e_{ind} = (V \times B) \cdot l$$

\therefore V is the velocity of the conductor.

B is the Magnetic field density.

l is the length of the segment.

From the previous figures:

OO' is the axis of rotation

ω_m is the speed of rotation [The mechanical speed]

Some Facts:

1) To find the linear velocity of a rotating body:

$V = \omega r$, to find the direction make a tangent in the direction of ω .


2) One loop coil has an Area $(A) = 2r \cdot l$

$$3) e_{ind} = VB \sin \alpha \cdot l \cos \theta$$

$\therefore \alpha$: the angle between \underline{V} & \underline{B} , θ : the angle between $(\underline{V} \times \underline{B})$ & \underline{l}

Now let's examine each segment to find the total e_{ind} :

1) Segment ab :

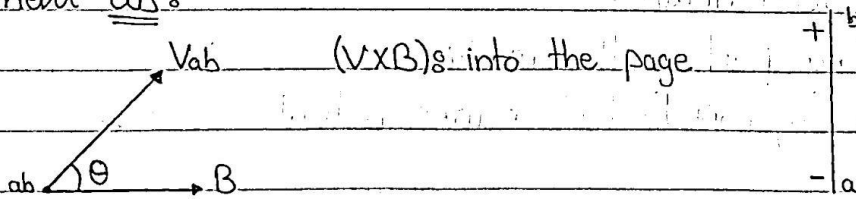

$(V \times B)$ is into the page

$$e_{ab} = (V \times B) \cdot l$$

$= v \cdot B \cdot l \sin \theta$ into the page * since l is in the direction of $(V \times B)$


2) Segment bc :

Regardless the direction of $(V \times B)$ [into the page or out of the page].

The length l is in the plane of the page, $(V \times B)$ is \perp to l for any direction of $(V \times B)$.

$$\text{So } e_{cb} = 0$$

3) Segment cd:

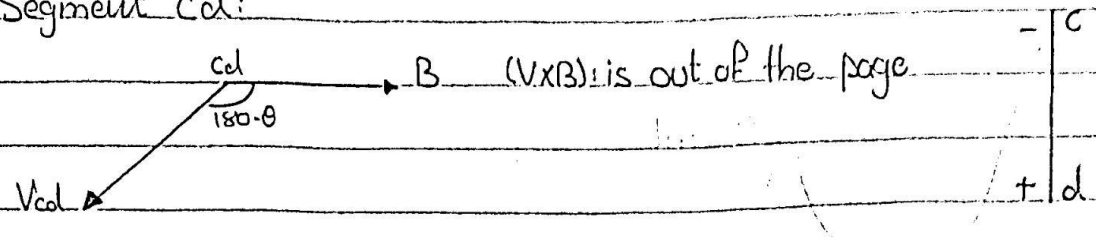

$(V \times B)$ is out of the page

$$e_{cd} = (V \times B) \cdot l$$

$$= VB l \sin(180-\theta) = VB l \sin \theta \text{ "out of the page"}$$

Since l is in the direction of $(V \times B)$, [smallest angle].

4) segment da:

Just as in segment bc, $(V \times B)$ is perpendicular to l .

$$\text{So, } e_{da} = 0$$

The total induced voltage on the loop "cnd" is the sum of the voltages in each segment.

A KVL loop:

$$e_{ind} = e_{bc} + e_{cd} + e_{dc} + e_{ad}$$

$$= 2VB l \sin \theta$$

We can express this equation in a way that we can study a larger, real AC Machine.

$\theta = \omega t$, if the loop is rotating at a constant angular velocity.

Since $\theta = \int \omega dt$

2) $v = r\omega$

3) $A = 2rl$

So:

$$e_{ind} = AB \omega_m \sin(\omega t)$$

4) $\Phi_{max} = AB$

$$e_{ind} = \Phi_{max} \omega_m \sin(\omega t)$$

For N loops:

$$e_{ind} = N \Phi_{max} \omega_m \sin(\omega t)$$


and,

In general:

$$e_{ind} = KN \Phi_{max} \omega_m \sin(\omega t)$$

$$e_{ind} = e_{max} \sin(\omega t)$$

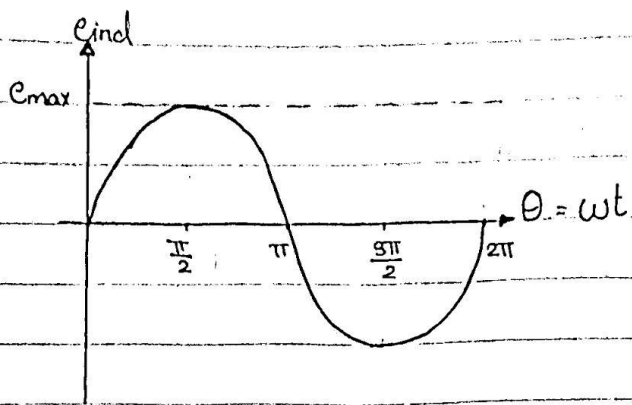
$$\therefore e_{max} = KN \Phi_{max} \omega_m$$



→ The induced voltage depends on:

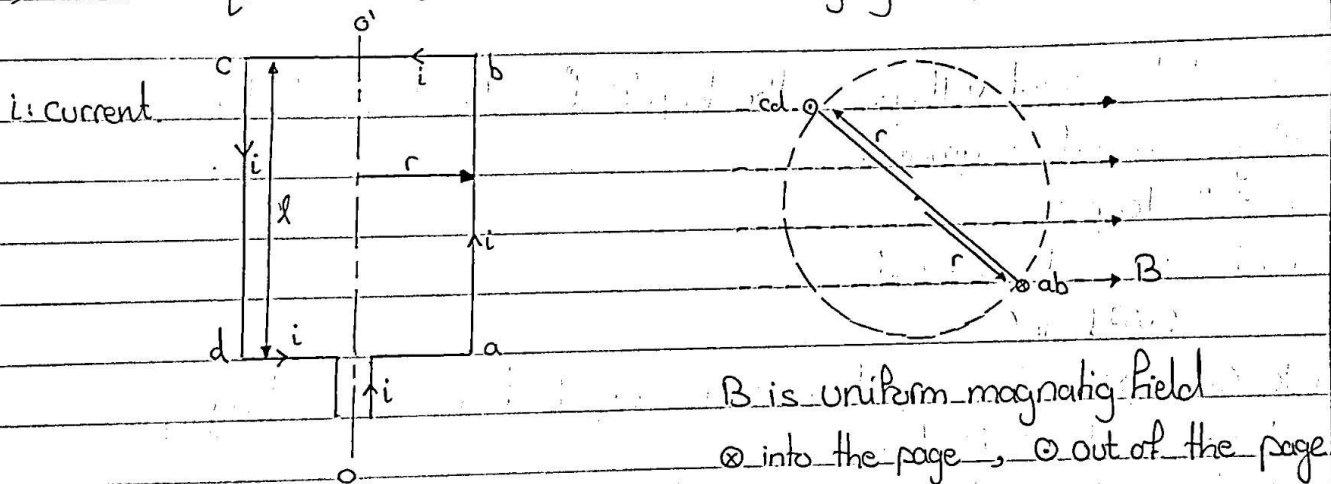- 1) The Magnetic Flux of the Machine.
- 2) The speed of rotation.
- 3) A constant representing the construction of the Machine.

→ The Torque Induced in a Current-Carrying loop:



If a current flows in the loop, then a torque will be induced on the wire loop. To determine the magnitude and direction of the loop's torque we will study each segment.

But before that let's talk about what we are going to study:

Since the Torque = $r \times F_{ind}$, we shall first study the force on each segment:


$$F_{ind} = i(\vec{l} \times \vec{B})$$

i = Magnitude of current in the segment.

l = Length of the segment, with direction in the current flows direction.

B = Magnetic Flux density vector.

1] Segment ab:

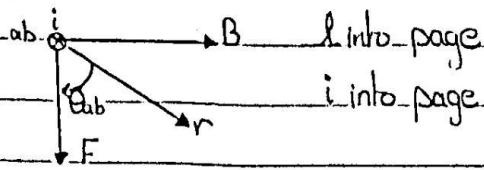


$$\vec{F}_{ind} = i(l \times B)$$

$$= i l B \text{ down.}$$

$$\vec{T}_{ind} = r F_{ind} \sin \theta_{ab}$$

$$= r i l B \sin \theta_{ab} \text{ clockwise.}$$


2] Segment bc:

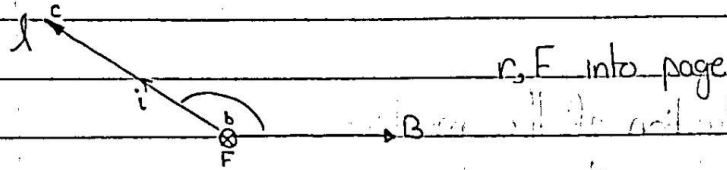

$$\vec{F}_{ind} = i l B \text{ into page}$$

$$\vec{T}_{ind} = 0 \text{ since } \vec{r} \text{ \& } \vec{F}_{ind} \text{ are parallel.}$$

3] Segment cd:

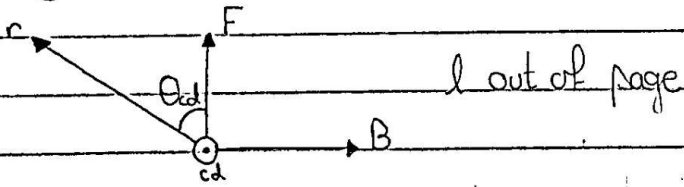

$$\vec{F}_{ind} = i l B \text{ up}$$

$$\vec{T}_{ind} = r i l B \sin \theta_{cd} \text{ clockwise.}$$

4] Segment da:

Just as segment bc
 $\vec{T}_{ind} = 0$ \vec{r}, \vec{F}_{ind} out of page.

The total induced torque on the loop T_{ind} :

$$T_{ind} = T_{ab} + T_{bc} + T_{cd} + T_{da}$$

$$= 2rilB \sin \theta$$

Noting that:

$$\left. \begin{matrix} 2rl = A \\ AB = \Phi \end{matrix} \right\} \rightarrow T_{ind} = \Phi i \sin \theta$$


For N turns: $T_{ind} = N \Phi i \sin \theta$

In general Torque induced by the machine is: $T_{ind} = k \Phi i \sin \theta$

$$T_{ind} = T_{max} \sin \theta$$

Torque induced depends on:

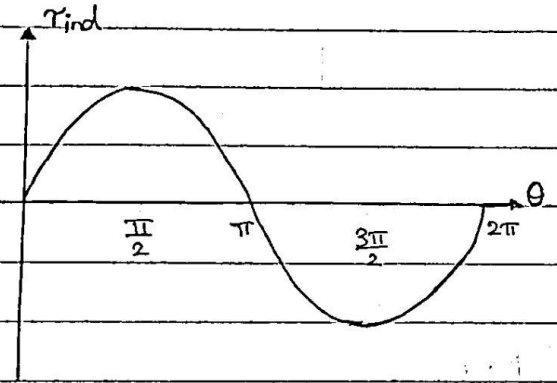- 1) The Flux of the machine.
- 2) The current in the loop.
- 3) A constant representing the construction of the machine such as: Number of turns, geometry, shape, etc.



Note: The expression of the torque with the Area

$T_{ind} = ABi \sin \theta$ lead us to the following conclusion:

- 1) Since the area vector is perpendicular to the loop, then The torque is maximum when the plane of the loop is parallel to the magnetic field.
- 2) The torque is zero when the plane is perpendicular to the magnetic field.

An Alternative way to express T_{ind}
 Any current flows in the loop will generate the magnetic field $[B_r \text{ or } B_{loop}]$, where B_r is the rotor magnetic flux density

From Ampere's law: $\oint H_r \cdot dl = I_{enc}$
 where H_r is the rotor magnetic field intensity

$H_r G = i$, where G is a factor that depends on the geometry of the loop

Knowing that $H_r = \frac{B_r}{\mu}$, and by equalizing the two equations:


The magnitude of the B_r will equal: $B_r = \frac{\mu i}{G}$, then

$$i = \frac{G B_r}{\mu}$$

Now, recalling the induced torque equation from the stator:
 $T_{ind} = A i B_s \sin \theta$, B_s is the stator magnetic field.

Substituting i from the first & put it in the second equation:
 $T_{ind} = \frac{AG}{\mu} B_r B_s \sin \theta$, where AG are constants

$$= k B_r B_s \sin \theta$$

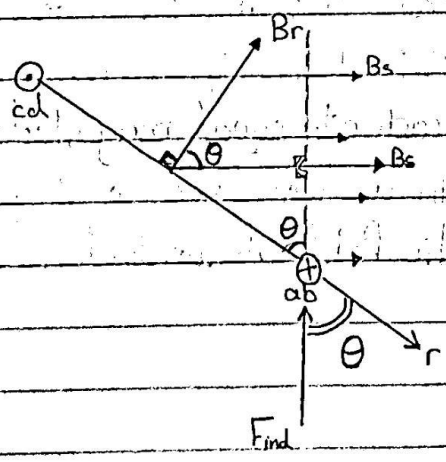

a) The current in the loop produces a magnetic flux density B_r perpendicular to the plane of the loop

From the previous figure it's seen that θ is the angle between the force and length vectors, but it's also the angle between \vec{B}_r & \vec{B}_s , this will lead to the following equation:

$$T_{ind} = k \vec{B}_r \times \vec{B}_s$$

From this equation both the magnitude and direction of the T_{ind} can be determined.

In general, the torque in any real machine will depend on two four factors:

- ① The strength of the rotor magnetic field.
- ② The strength of the external magnetic field.
- ③ The sin of the angle between \vec{B}_r & \vec{B}_s .
- ④ A constant representing the construction of the machine.

→ The Rotating Magnetic Field:

Note: If two magnetic fields are present in a machine, then the torque will be created which will tend to line up (align) the two magnetic fields.

From this, the torque induced in the rotor by \vec{B}_r will cause the rotor to turn and align it-self with \vec{B}_s from the stator.


From this concept, if we can make \vec{B}_s rotating then the rotor will constantly chase it around in a circle.

↑ The question now is How to make a stator magnetic field?

The fundamental principle of AC Machine Operation:-

If a three-phase set of currents, each of equal magnitude and different in phase by 120° , flows in a three-phase winding, then it will produce a rotating magnetic field of constant magnitude.

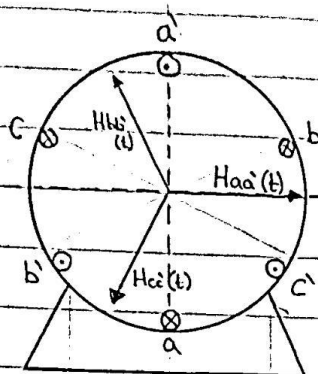Assume that we have the windings shifted from each other by 120° .



A simple three-phase stator.

Assume that the phase currents applied to the coil are,

$$① i_{aa'}(t) = I_m \sin(\omega_e t) \quad A$$

$$② i_{bb'}(t) = I_m \sin(\omega_e t - 120^\circ) \quad A$$

$$③ i_{cc'}(t) = I_m \sin(\omega_e t + 120^\circ) \quad A$$

where ω_e is the electric radian frequency.

Each current in a coil will produce a magnetic field intensity:

$$① H_{aa'}(t) = H_m \sin(\omega_e t) \angle 0^\circ \quad A \cdot \text{turns} / m$$

$$② H_{bb'}(t) = H_m \sin(\omega_e t - 120^\circ) \angle +120^\circ \quad A \cdot \text{turns} / m$$

$$③ H_{cc'}(t) = H_m \sin(\omega_e t + 120^\circ) \angle -120^\circ \quad A \cdot \text{turns} / m$$

Each intensity will produce a Magnetic field density:

$$① B_{aa'}(t) = B_m \sin(\omega_e t) \angle 0^\circ \quad T$$

$$② B_{bb'}(t) = B_m \sin(\omega_e t - 120^\circ) \angle +120^\circ \quad T$$

$$③ B_{cc'}(t) = B_m \sin(\omega_e t + 120^\circ) \angle -120^\circ \quad T$$

Now the currents and their corresponding Flux densities will be examined at specific times to determine the resulting net magnetic field in the stator:

$$\vec{B}_{s(\text{net})} = \vec{B}_{aa'} + \vec{B}_{bb'} + \vec{B}_{cc'}$$

① When $\omega_e t = 0$:-

$$i. \vec{B}_{aa'} = 0$$

$$ii. \vec{B}_{bb'} = -\frac{\sqrt{3}}{2} B_m \angle 120^\circ$$

$$iii. \vec{B}_{cc'} = \frac{\sqrt{3}}{2} B_m \angle -120^\circ$$

$$\vec{B}_{s(\text{net})} = -j \frac{3}{2} B_m = \frac{3}{2} B_m \angle -90^\circ$$

$B_{s(\text{net})}$ when $\omega_e t = 0$.



In general, the net magnetic density can be given by:

$$B_{net}(t) = 1.5 B_m \sin(\omega_e t) \hat{x} - 1.5 B_m \cos(\omega_e t) \hat{y}$$

For the proof see pages 163-164 in the book.

The following table represent some values to $\omega_e t$:

$\omega_e t$	0°	90°	180°	270°
B_{net}	$\downarrow -1.5 B_m \hat{y}$	$\rightarrow 1.5 B_m \hat{x}$	$\uparrow 1.5 B_m \hat{y}$	$\leftarrow -1.5 B_m \hat{x}$

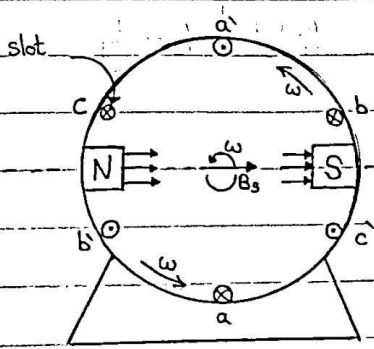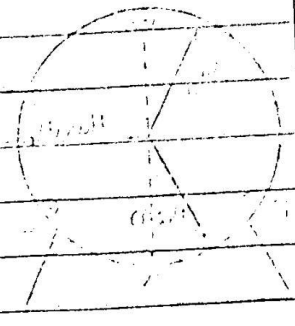

The rotating magnetic field in a stator represented as moving north and south stator poles.

Relationship between Electrical Frequency and the speed of Magnetic Field rotation:

We can represent the rotating magnetic field in the stator as a north pole and a south pole.

Before we start studying the relation we should know the:

Winding Sequence: [The sequence of the stator windings]:

From the figure, the counter-clockwise sequence is:

"a'c'b a'c'b"

For this sequence, we have [2-poles] or [1 pair of poles]. These magnetic poles complete one mechanical rotation around the stator surface for each electrical cycle of the applied current.

Therefore:

(i) $\theta_e = \theta_m \rightarrow$ The mechanical angular position.

\hookrightarrow The electrical angular position.


② $\omega_e = \omega_m \rightarrow$ The mechanical speed of rotation [rad/sec]

\hookrightarrow The electrical rotation frequency [rad/sec]

③ $f_e = f_m \rightarrow$ [revolutions per second]

\hookrightarrow [Hertz]

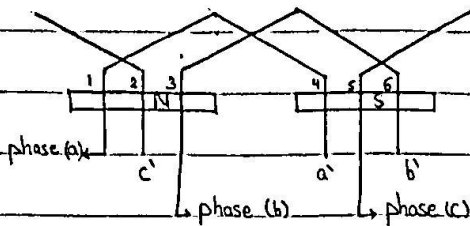The winding diagram of: [6 slots, 3 ϕ , 2 poles AC MACHINE]



To calculate the phase difference [The slots \times between the phases]

$$\text{phase difference} = \frac{120^\circ}{360} \times \frac{\text{slots}}{\text{Pole Pair}}$$

$$= \frac{1}{3} \times \frac{6}{1} = [2]$$

If phase a at slot $\times 1$

Then phase b at $1+2 = \times 3$


and phase C at $3+2 = \times 5$

What if the winding sequence was repeated?

Then we will get a 4-pole AC Machine

The sequence of the stator winding is:

"ac'ba'cb' ac'ba'cb'"

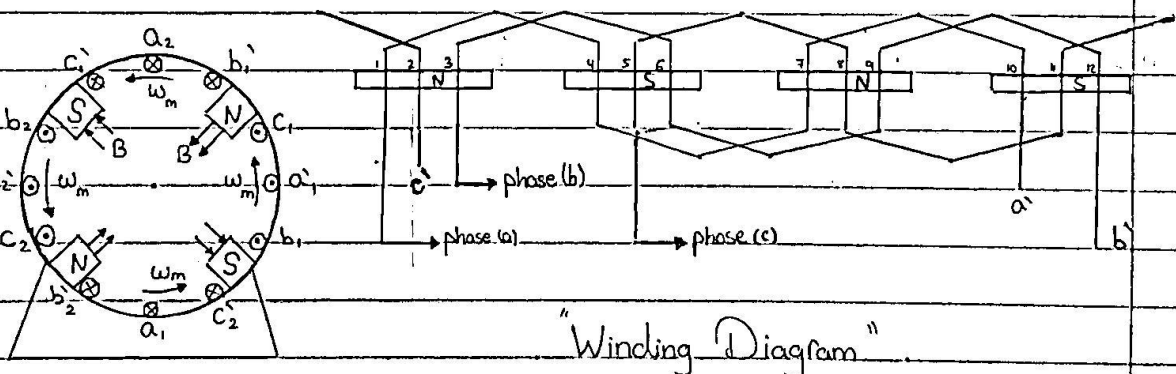

In this sequence the net magnetic flux density field will move half a cycle per each electrical cycle.

1) $\Theta_m = \frac{\Theta_e}{2}$ 2) $P_m = \frac{P_e}{2}$

2) $W_m = \frac{W_e}{2}$

The phase difference = $\frac{120}{360} \cdot \frac{12}{2} = 2$

- a → 1
- b → 1+2 = 3
- c → 3+2 = 5

In general the relationship between W_m & W_e is given by:


$$W_m = \frac{W_e}{\text{pole-pair}} = \frac{W_e}{\text{poles}/2}$$

$$= \frac{2 W_e}{\text{poles}} = \frac{4 \pi P_e}{\text{poles}}$$

and since: $\eta_m = \frac{W_m \cdot 60}{2\pi}$

$\eta_m = \frac{120 P_e}{\text{poles}}$

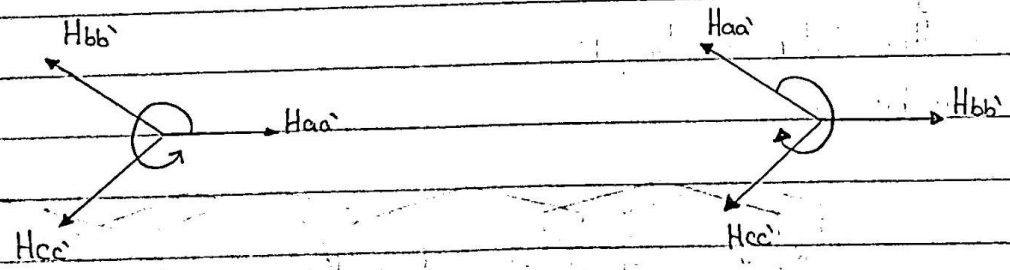The direction of the rotating magnetic field is reversed by swapping the phase current in any two coils.



Induced Voltage in a three-phase set of coil

Assume that the rotor is rotating at angular speed of ω_m and the magnetic flux density is uniform, then the magnetic flux density in the air gap between the rotor and stator varies sinusoidally with mechanical angle (α):

$$B = B_m \cos(\alpha)$$

If N_c is the number of turns per each coil, then the induced voltage across the coil of phase (a) is:

$$e_{aa'} = N_c \Phi \omega \sin(\omega t)$$

and in phase (b) & (c) are:

$$e_{bb'} = N_c \Phi \omega \sin(\omega t - 120^\circ)$$

$$e_{cc'} = N_c \Phi \omega \sin(\omega t + 120^\circ)$$

The peak value of induced voltage is:


$$e_{peak} = N_c \Phi \omega = 2\pi N_c \Phi f$$

The rms value of the induced voltage:

$$e_{rms} = e_{peak} / \sqrt{2}$$

$$= \sqrt{2} \pi N_c \Phi f$$

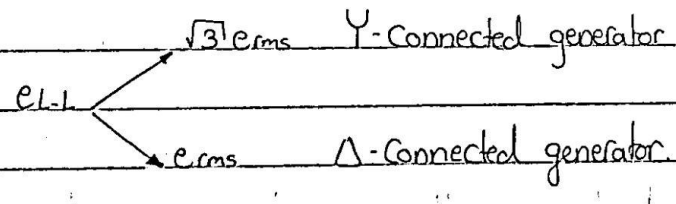The line to line rms value of the induced voltage:



Torque induced in AC Machine: "Motor"



Assume that the field distribution of stator is given by:

$$B_s = B_s \sin \alpha$$

In general,

$$F_{ind} = i l \times B$$

$$= i l B \sin \alpha$$

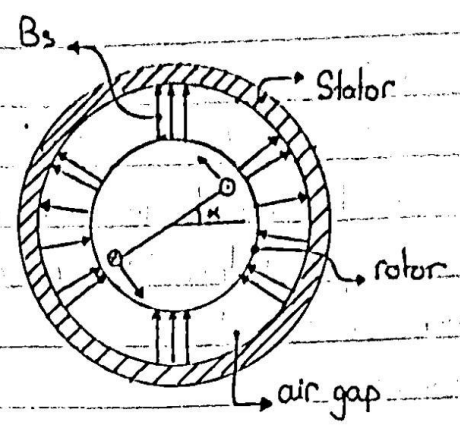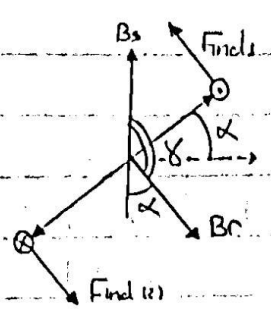

Note:

From the first figure:
 δ is the angle between B_r & B_s
 $\delta + \alpha = 180^\circ$
 $\sin \alpha = \sin \delta$
 So
 $T_{ind} = k B_r \times B_s$

$$F_{ind(w)} = i_1 l_1 B_s \sin \alpha \quad \text{C.C.W}$$

$$F_{ind(s)} = i_2 l_2 B_s \sin \alpha \quad \text{C.C.W}$$

$$T_{ind(w)} = r_1 i_1 B_s \sin \alpha$$

$$T_{ind(s)} = r_2 i_2 B_s \sin \alpha$$

The net induced torque is:

$$T_{ind} = 2 r i l B_s \sin \alpha$$

According to Ampere's law:

$$\oint H \cdot dl = I_{enc}$$

$H_r = C i$, where C is constant.

$$T_{ind} = \frac{2 r l}{\mu c} B_r B_s \sin \alpha$$

$$= \frac{2 r l}{\mu c} B_r B_s \sin(180 - \delta)$$

$= k B_r \times B_s$ \rightarrow k is not constant since the magnetic permeability varies with the amount of magnetic saturation in the machine.

The net magnetic field in the Machine:


$$\vec{B}_{net} = \vec{B}_r + \vec{B}_s \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \rightarrow T_{ind} = k \vec{B}_r \times \vec{B}_{net}$$

$$\vec{B}_s = \vec{B}_{net} - \vec{B}_r \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} = k \vec{B}_r B_{net} \sin \delta \quad \text{where } \delta \text{ is the angle between } \vec{B}_r \text{ \& } \vec{B}_{net}.$$

Note:

1] If the direction of induced torque is opposite to the direction of rotation, then the Machine acts like a generator.

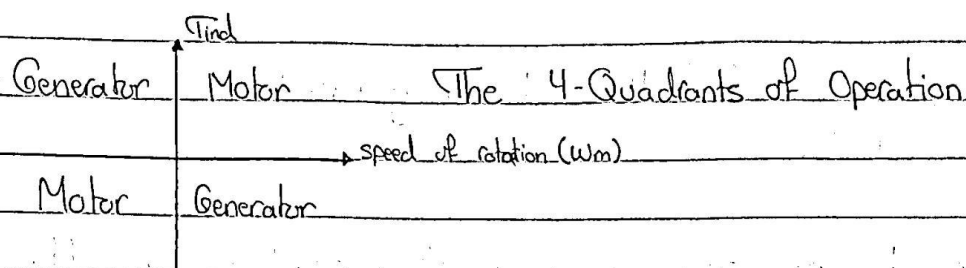2] If the direction of induced torque is the same as the direction of rotation, then the Machine acts like a Motor.



The efficiency of the Machine:

Power losses in AC Machines:

1] Electrical (current) copper losses

This is due to the winding resistance

a) $P_{sc} = 3I_s^2 R_s$, resistance winding of the stator / phase.
 ↳ stator copper losses

b) $P_{rc} = I_r^2 R_r$, resistance winding of the rotor
 ↳ rotor copper losses

Note: The power of the stator is a 3- Φ power.

2] Core losses:

Eddy currents & Hysteresis

core losses $\propto B_r^2 \omega_m^{3/2}$

3) Mechanical losses:

- i) Friction: due to bearings
- ii) Windage: Friction between air and any of the moving parts of the machine.

Mechanical losses, $a_0 \omega_m + a_1 \omega_m^2 + a_2 \omega_m^3$

4) Stray losses:

They represent 1% of Full-load. They are losses, which are not accounted for.

* Note: The mechanical and core losses of a machine are often lumped together and called the no-load rotational loss of the machine. At no-load, all the input power must be used to overcome these losses. Therefore, measuring the input power to the stator of an AC machine acting as a motor at no-load will give an approximate value for these losses.

Efficiency calculations:

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

= $\frac{P_{in} - P_{loss}}{P_{in}} \times 100\%$, since the difference between the input power and output power is the losses occur inside AC Machine.

For generator operation:

$P_{in} = T_{app} \omega_m$ → speed * This power is mechanical
 ↳ Torque applied

$P_{out} = 3 V_{\phi} I_{\phi} \cos \theta_{\phi}$ → The power factor.

= $\sqrt{3} V_L I_L \cos \theta_{\phi}$ → The phases angle.

For Motor calculations:

$$P_{in} = 3 V_{\phi} I_{\phi} \cos \theta_{\phi}$$

$$= \sqrt{3} V_L I_L \cos \theta_{\phi}$$


$$P_{out} = T_L \cdot \omega_m$$

↳ Torque load applied to the shaft.

Power-Flow Diagram:

It's one of the most convenient techniques for accounting for power losses

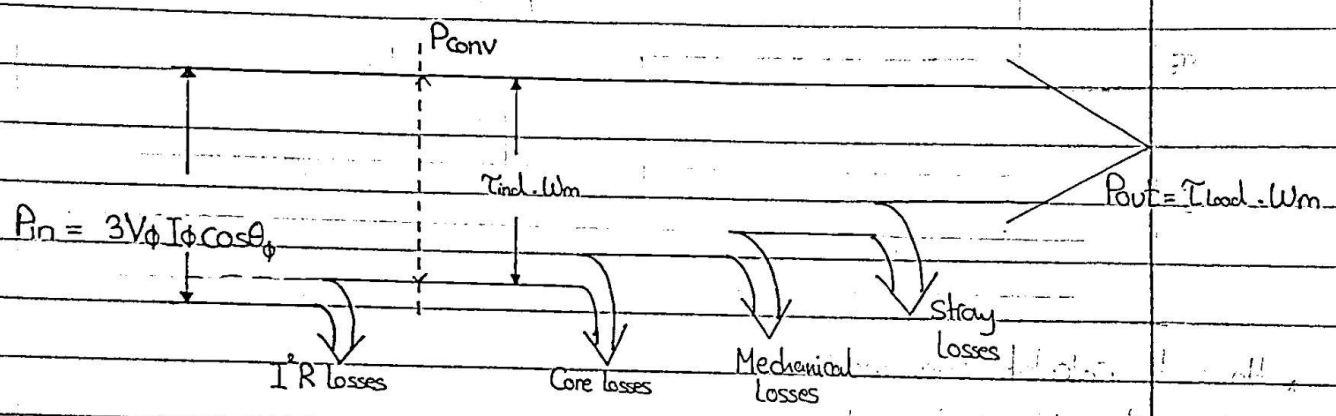The Power-Flow diagram of a 3-φ ac Motor:



P_{conv} : is the converted power } to mechanical if Motor
 } to electrical if Generator.

It's given by:

$$P_{conv} = T_{ind} \cdot \omega_m$$

↳ The induced torque

From Newton's second law:



$$\sum \tau = J \frac{d\omega_m}{dt}$$

∴ $\sum \tau$: The net torque, J : inertia,

$\frac{d\omega_m}{dt}$: acceleration.

$$T_{ind} - T_f = J \frac{d\omega_m}{dt} + T_{friction}$$

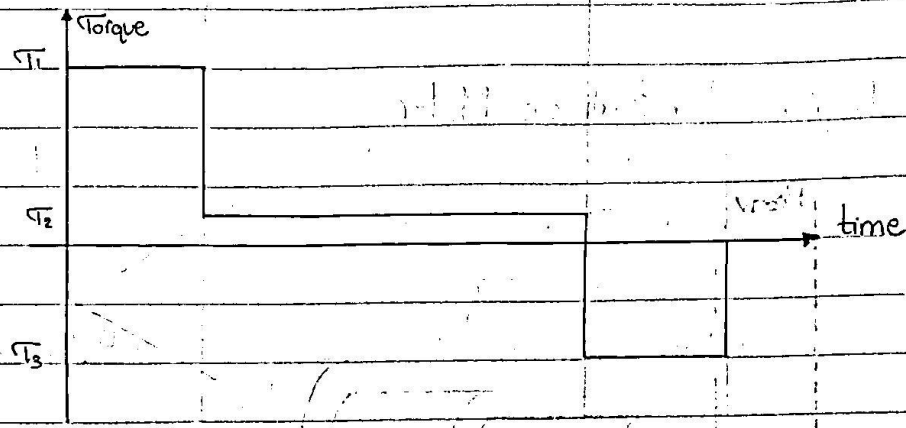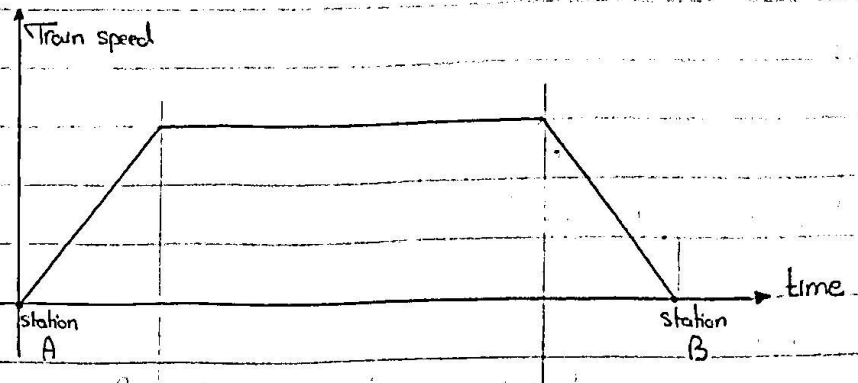To understand the previous law, let's study the Train example:



How to calculate the inertia:

$$\frac{1}{2} m V^2 = \frac{1}{2} J \omega_m^2$$


$$J = m \left(\frac{V}{\omega_m} \right)^2, \text{ but } V = \omega \cdot r$$

$$= m \left(\frac{\omega \cdot r}{\omega_m} \right)^2, \text{ if the shaft speed} = \text{wheel speed} \Rightarrow [\omega = \omega_m]$$

$$J = m \left(\frac{r}{\omega_m / \omega} \right)^2$$

$$= m \left(\frac{r}{\tau} \right)^2 \text{ where } \tau \text{ is the gear box ratio.}$$

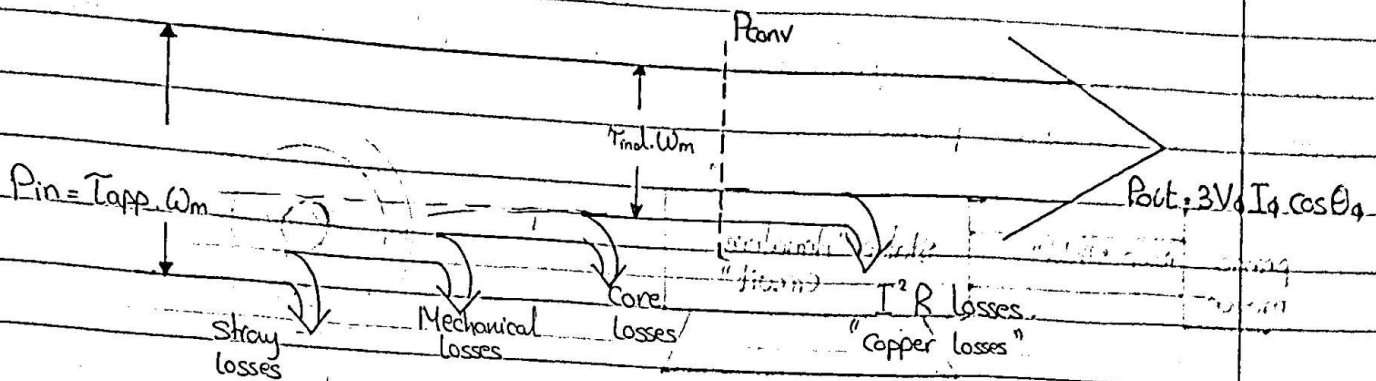2] The Power-Flow diagram of the 3- ϕ ac Generator:



→ Voltage Regulation and Speed Regulation:

VR: It's a measure of generator ability to keep a constant voltage under load condition (as load varies).

$$VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$\therefore V_{NL}$: The no-load terminal voltage of the generator

V_{FL} : The full-load terminal voltage of the generator.


SR: It's the ability of Motor to keep constant speed as load varies.

$$SR = \frac{n_{NL} - n_{FL}}{n_{FL}} \times 100\%$$

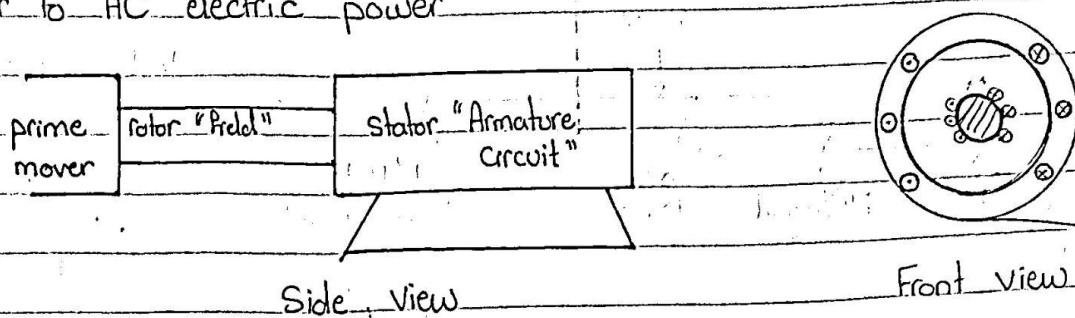- i) positive SR means, The motor's speed drops with increasing load
- ii) negative SR means, The motor's speed rises with increasing load.
- iii) if $SR = 0$, Then $n_{NL} = n_{FL}$

Chapter 4: Synchronous generators.

Synchronous generators are synchronous machines used to convert mechanical power to AC electric power.



Prime mover: It's the initial source of mechanical energy. It's any machine that converts (Fuel/Steam) into a mechanical energy.

The synchronous machine has two main windings:

[1] The "rotor" or "field" windings, where the machine Flux is induced (produced).

[2] The "stator" or "armature" windings, where the 3- ϕ voltages are induced (produced).

Operating principle:

A DC current is supplied to the rotor coil to produce a rotating Magnetic field.

The rotor rotates by means of external prime mover to produce a rotating magnetic field.

The rotating magnetic field will induce 3- ϕ voltages across the stator or armature windings.


Types of rotor in synchronous generator:

1 Salient polar rotor:

The poles are sticking out from the rotor surface.


2 Cylindrical rotor:

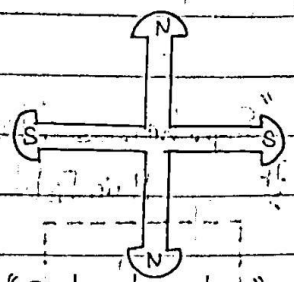The poles are constructed flush with the rotor surface.



"Salient rotor"

P = 4

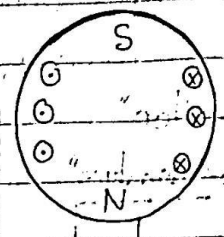

"cylindrical rotor"

P = 2

Notes:

When $P > 4$, salient pole machine is selected.


When $P = 2, 4$, cylindrical pole machine is used.

Methods to feed the rotor coil

1 Slip-rings and brushes:

slip-rings: Are Metal rings encircling the shaft, but insulated from it.

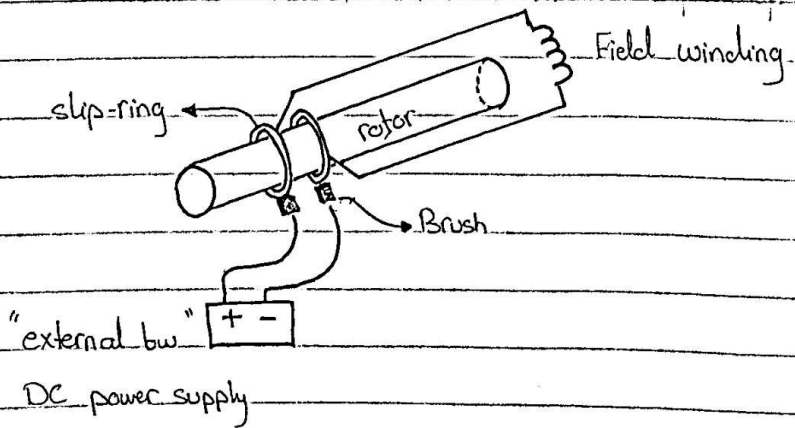Brush: It's a block of carbon compound that conducts electricity freely, but has very low friction.




Sliprings and brushes problems:

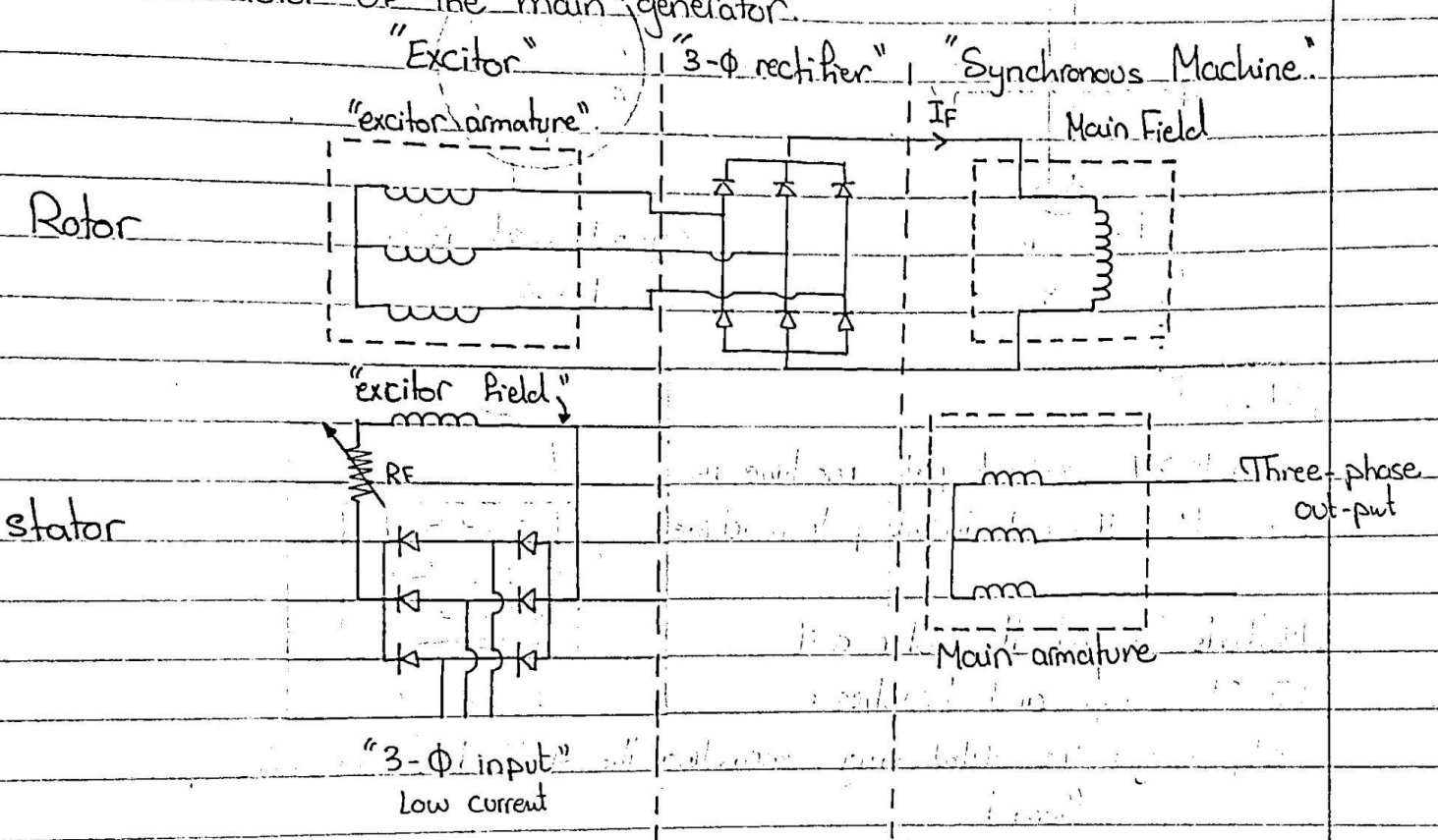
- 1) The brushes need regular maintenances
- 2) The voltage drop across brushes may cause a power losses.

2] Brushless excitor:

It's a small ac generator with it's field circuit mounted on the stator of main generator, and it's armature windings mounted on the rotor of the main generator.




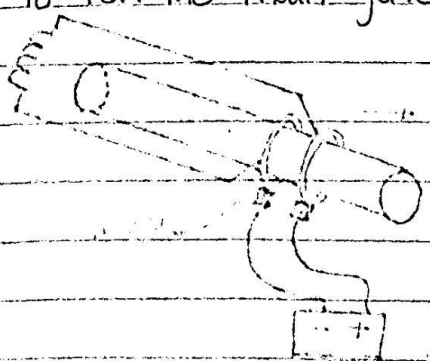The drawback or disadvantage of the Brushless excitor is it needs a 3-φ input power to run the main generator



③ Pilot excitor:

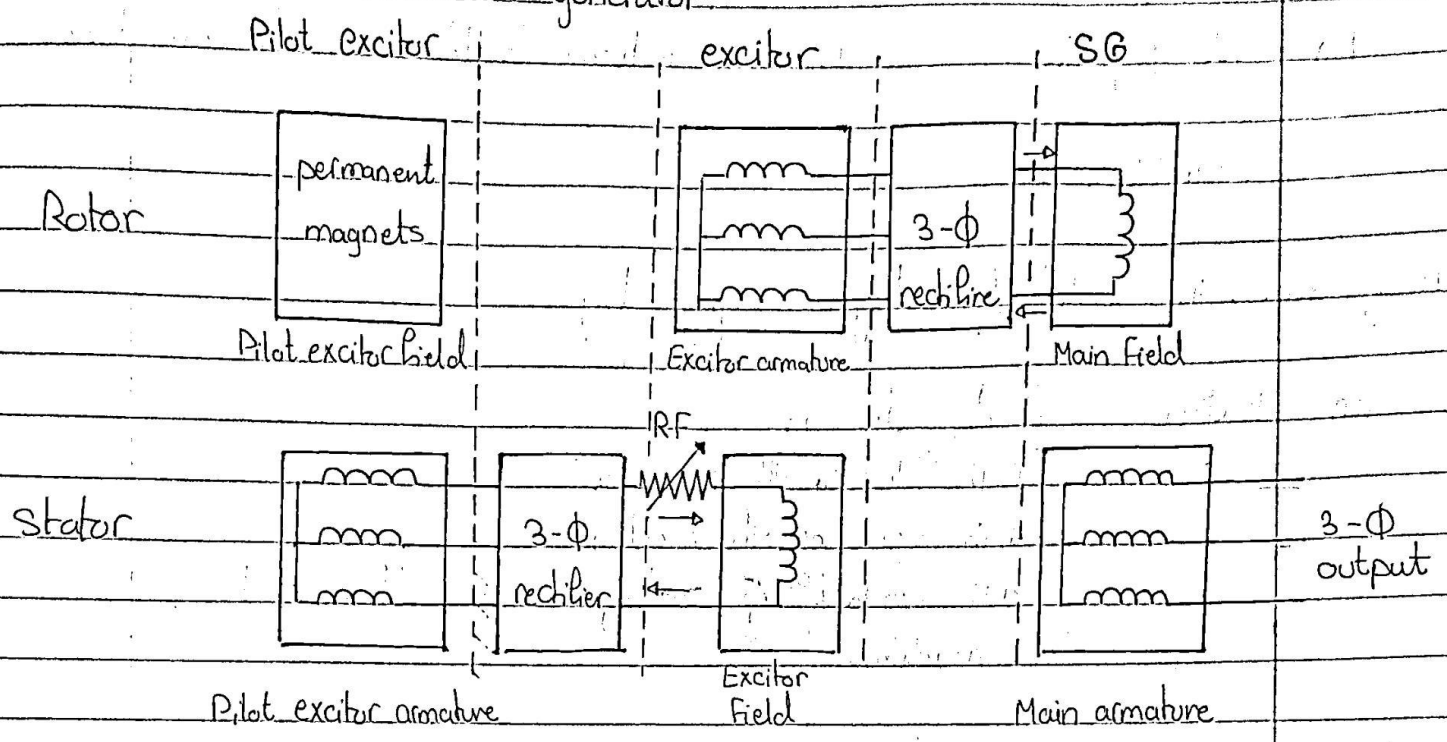It's a small ac generator with permanent magnet mounted on the rotor, and its armature circuit mounted on the stator of the main generator



▷ Mechanical speed of synchronous Generator:

Synchronous mechanical speed of the rotor is synchronized with the electric frequency.

$$n_m = n_s = \frac{120 f_e}{p}$$

n_m : is the speed of the rotor [Mechanical speed]

n_s : is the synchronous speed

p : The number of poles

f_e : Electrical frequency in Hertz

Notes:

① $n = 60 f \rightarrow n_m = \frac{2}{p} n_e$

② $\omega_m = \frac{2}{p} \omega_e$

→ Internal voltage of Synchronous generator:

The RMS value of the Line-Neutral [L-N] induced voltage in Synchronous generator is given by:

$$E_A = \frac{N_c \phi \omega_e}{\sqrt{2}} \quad \therefore E_A \text{ is (The induced voltage) on the armature.}$$

$$= \sqrt{2} \pi N_c \phi P_e$$


In general, the induced voltage is given by:

$E_A = k \phi \omega_e$, it depends on:

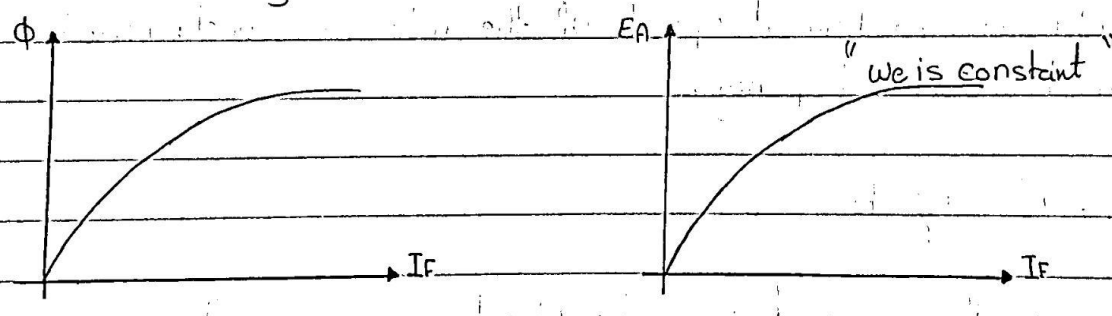- (1) The flux of the machine
- (2) The speed of the machine
- (3) A constant representing the construction of the machine.

Note:

The flux is linearly proportional to the field current (I_f)




→ The equivalent circuit of synchronous machine:

The terminal voltage (V_ϕ) of synchronous machine [generator] is not equal to the induced voltage (E_A), because of the following:

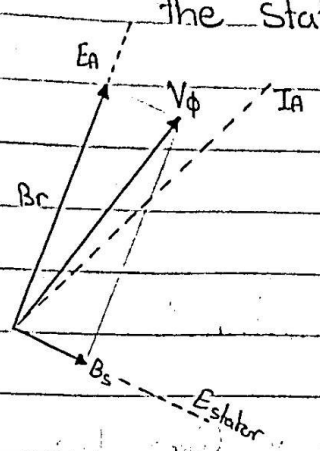- (1) Armature reaction
- (2) Self inductance of armature circuit [L_A]
- (3) Self resistance of armature circuit [R_A]

Armature reaction is a distortion of air gap magnetic flux due to the current flowing in the stator winding.



$$\vec{V}_\phi = \vec{E}_A + \vec{E}_{stator}$$

$$\vec{E}_{stator} = -jX\vec{I}_A$$

$$\vec{V}_\phi = \vec{E}_A - jX\vec{I}_A$$

→ reactance of the armature reaction.

[2] + [3]: The inductance & resistance of the armature windings.


$$\vec{V}_\phi = \vec{E}_A - jX\vec{I}_A - jX_A\vec{I}_A - R_A\vec{I}_A$$

X_A : The self reactance of the stator armature winding


Then we can conclude that the equivalent circuit is:

$$\vec{V}_\phi = \vec{E}_A - j(X_A + X)\vec{I}_A - R_A\vec{I}_A$$

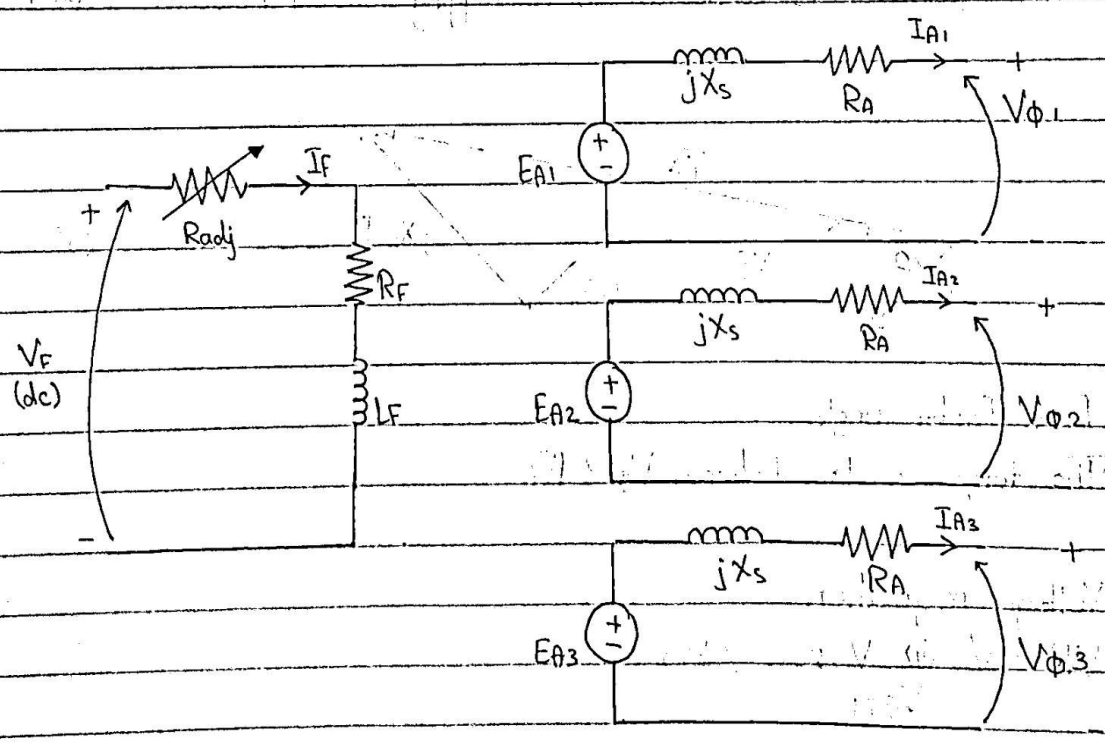∴ $X_A + X = X_s$, synchronous reaction [synchronous reactance]



The per-phase equivalent circuit:

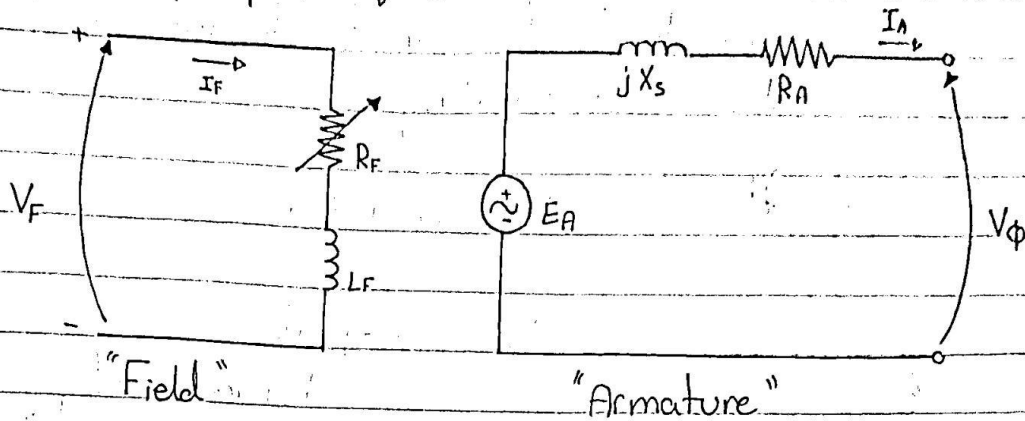

Phase Diagram of 3φ synchronous Generator:

By applying KVL in the per-phase armature circuit, we get:


$$\vec{E}_A = R_A \vec{I}_A + jX_s \vec{I}_A + \vec{V}_\phi$$

Assume that the angle of \vec{V}_ϕ is zero, (reference angle):

$$\vec{V}_\phi = |V_\phi| \angle 0^\circ$$

□ Lagging PF:

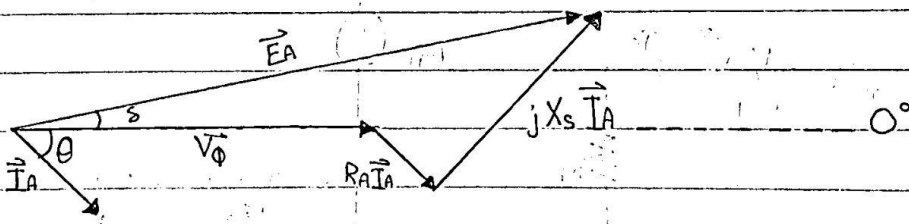"The generator is connected to a lagging loads [inductive load]"



θ : Power Factor angle

δ : The torque angle, between V_ϕ & E_A


→ Voltage regulation

$$VR = \frac{V_\phi(NL) - V_\phi FL}{V_\phi FL} \times 100\%$$

$$= \frac{E_A - V_\phi}{V_\phi} \times 100\% > 0$$

2] Unity PF:

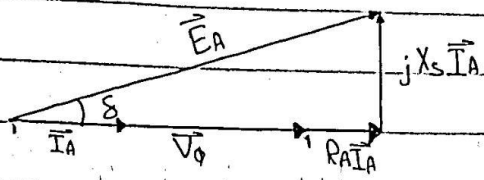"The generator is connected to resistive load"




V_R is also positive

3] Leading PF:

"The generator is connected to a leading load [capacitive load]"

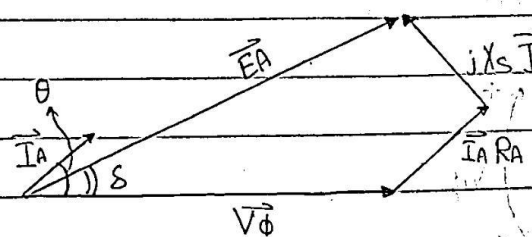
Note: This type is not used in real life application.



$$E_A < V_\phi \rightarrow V_R = \frac{E_A - V_\phi}{V_\phi} \times 100\% < 0$$

Power and Torque equations of synchronous generator:

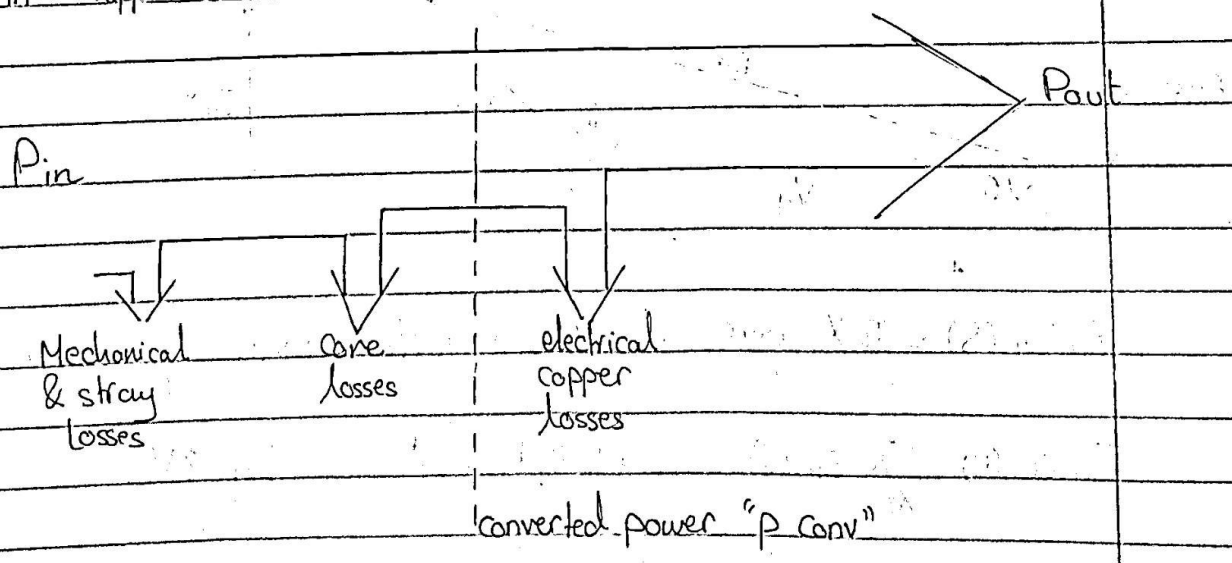
$$P_{in} = T_{app} \cdot \omega_m \quad \rightarrow \quad P_{out} = 3V_\phi I_\phi \cos \theta_\phi$$




$$P_{conv} = \sqrt{3} I_{ind} W_{ms} = 3 E_A I_A \cos(\delta)$$

- ① from \vec{B}_r & \vec{B}_s ② δ : The angle between \vec{E}_A & \vec{I}_A .

∴ electro-magnet torque developed torque

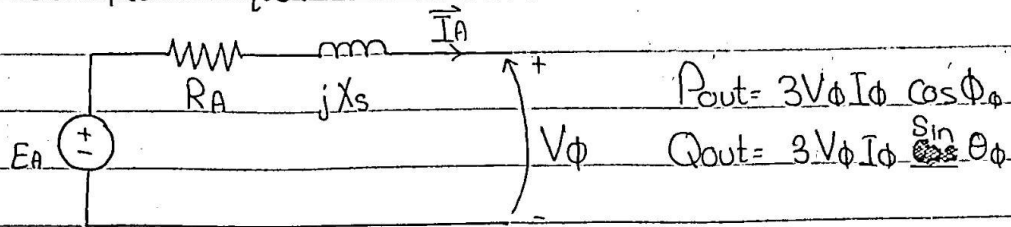


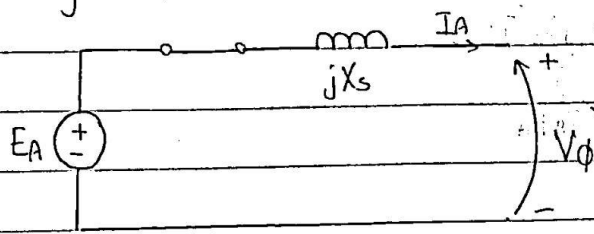Assume that the load is connected to an inductive load. Since R_A is smaller than X_s ($X_{se} + X_A$), then we can neglect it.



$$\vec{E}_A = \vec{V}_\phi + jX_s \vec{I}_A$$

Phasor Diagram:

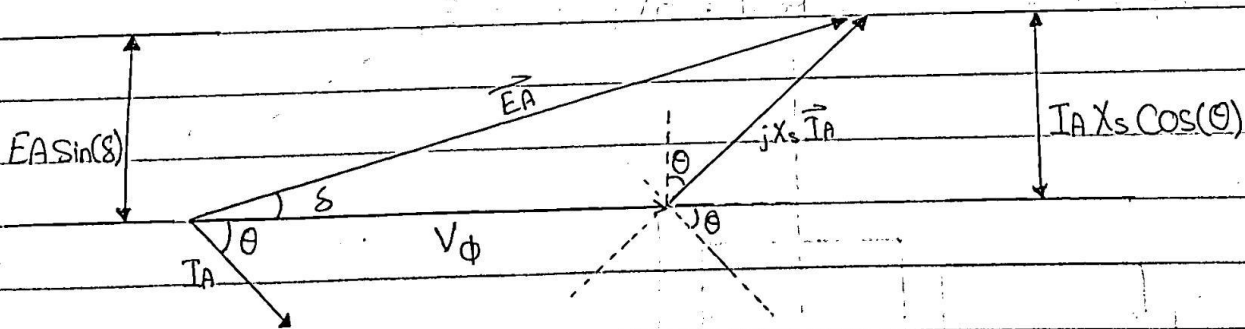

$$E_A \sin(\delta) = I_A X_s \cos(\theta) \text{ if } R \text{ is neglected, since } \frac{X_s}{R} \gg 10$$

$$I_A \cos(\theta) = \frac{E_A \sin(\delta)}{X_s} \text{ Multiply both sides by } 3V_\phi$$

$$3V_\phi I_A \cos(\theta) = 3V_\phi \frac{E_A \sin(\delta)}{X_s}$$

$$P_{out} = P_{conv} \text{, since } R \text{ is neglected.}$$

$$P_{out} = P_{conv} = T_{ind} \omega_{ms}$$

The induced torque in synchronous machine is:

$$T_{ind} = \frac{3EA}{X_s} \cdot \frac{V_t}{\omega_{ms}} \cdot \sin(\delta)$$


Since P_{out} is a sin function:

$$P_{out} = \frac{3V_t EA}{X_s} \sin(\delta), \text{ it has a max value:}$$

$$P_{out \text{ max}} = \frac{3V_t EA}{X_s}, \text{ ; } \delta_{\text{max}} = 90^\circ \text{ [Steady-state stability limit]}$$

Effect of load changes on SG operation:

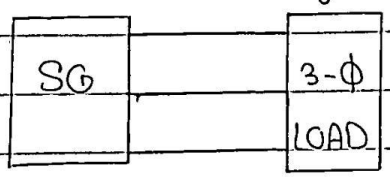1) Assume that the generator is connected to 3- ϕ load



2) Assume that the machine flux is constant:

Φ is constant mean that the field current (I_f) is constant.

3) Assume that the prime-mover is rotating at constant speed


ω_{ms} is constant, so the induced voltage (E_A):

$$E_A = k\Phi\omega_{ms} \text{ is constant}$$

4) Assume that the load increased at the same PF:

Note: load increased means that a higher (I_A) is consumed

(i) Lagging PF:

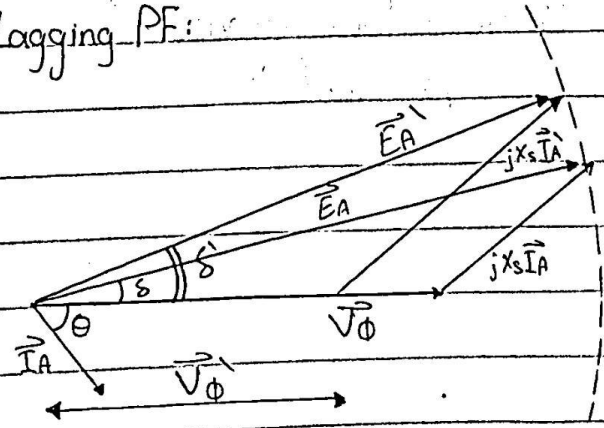


Notes:

1) The terminal voltage decreases as the load increases.


$$2) |I_A'| > |I_A|$$

(ii) Unity P.F.

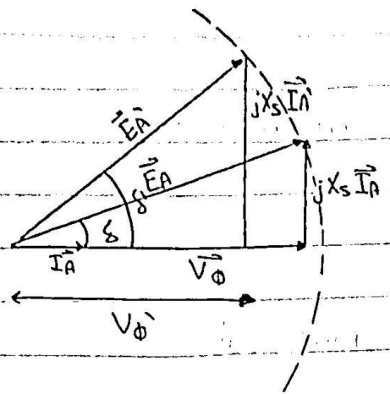

Note:
 ① The terminal voltage decreases as the load increases.


(iii) Leading P.F.

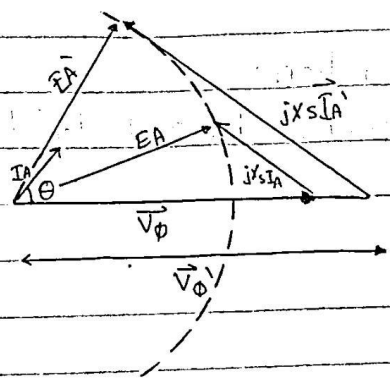

Note:
 ① The terminal voltage increases as the load increases.

→ The Automatic Voltage regulator (AVR)
 It's a closed controller to keep the terminal voltage of synchronous generator constant.

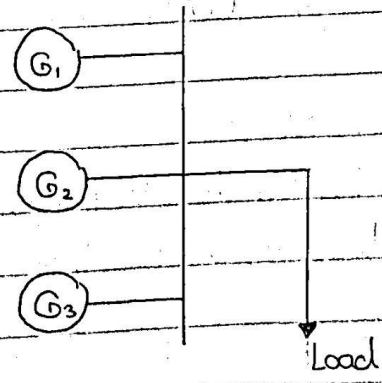→ Parallel operation of synchronous generator:
 Other than emergency generators, rarely there is a case where a single (isolated) generator supplies a load in power systems.




"3-generators connected in parallel"

Major Advantages:

- 1) Supplies a larger load in the system
- 2) high reliability of power system
- 3) One or more generators can be removed for shutdown a preventive maintenance.
- 4) If only one generator is used and it's not running at full load then it will be relatively inefficient process.


Conditions required for paralleling:

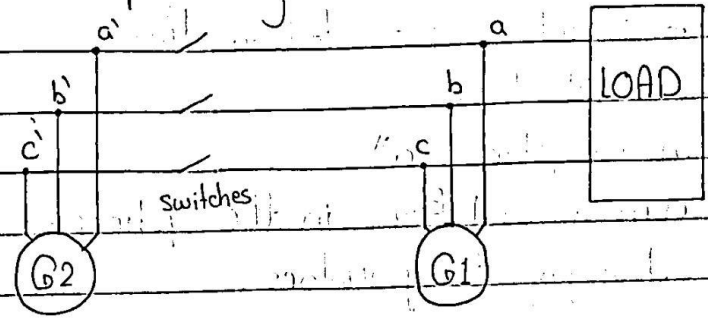


G1: The running generator

G2: The oncoming generator.

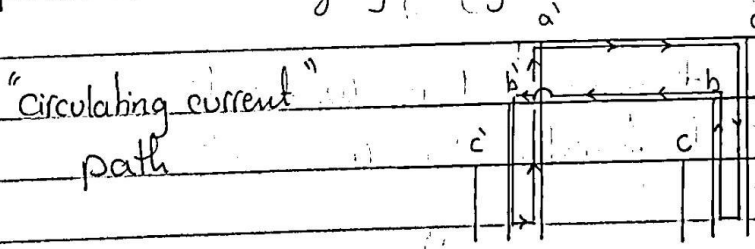- 1) The generator's must have the same RMS line voltages: To avoid huge circulating current that may flow in the phases, so damaging the generator.




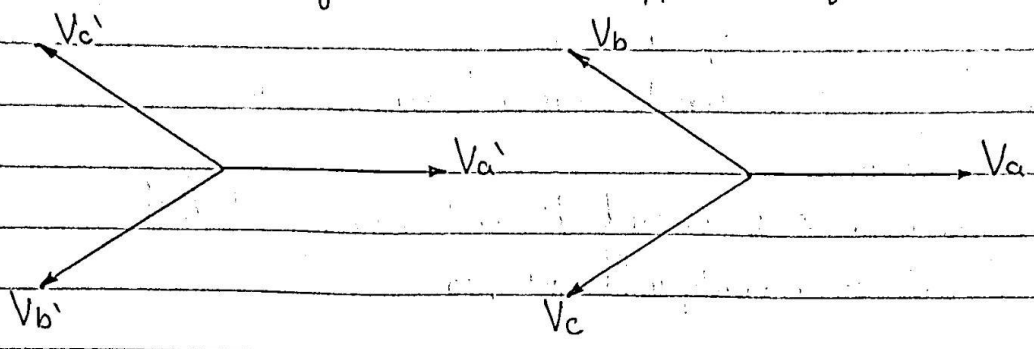② The phase sequence of the generators must be the same.
 Assume that the generators has an opposite sequence:



If the generators where connected in this manner, there would be:

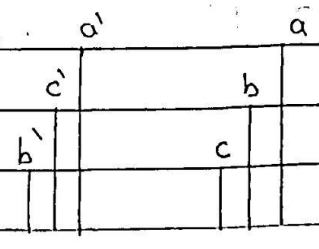- 1) no problem in phase "a"
- 2) a huge current will flow in the phases "b" & "c" damaging the generators.



To correct the phase sequence, simply swap any two of the three phases on the generator.





③ The phase angle of the "a", "b", "c" phases must be equal.

④ The frequency of the on-coming generator must be slightly higher than the frequency of the running generator.

Explanation for ③ & ④:

Assume that the frequency of generator 1 is $\omega_1 = 2\pi f_1$

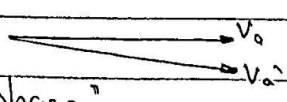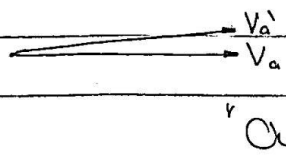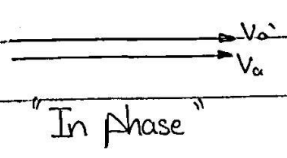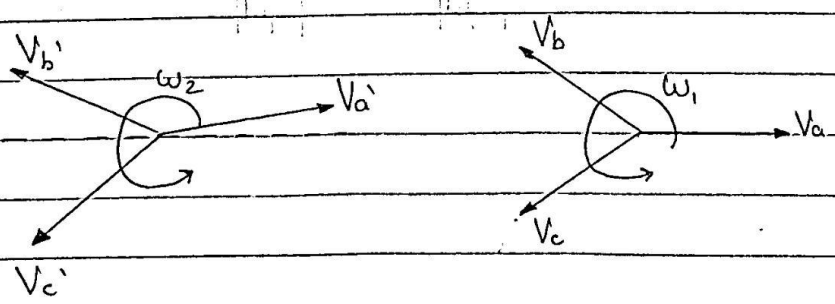Assume that the frequency of generator 2 is $\omega_2 = 2\pi f_2$




To study the importance of slightly different between the frequencies:

lets study the two cases:


□ Case 1,

$\omega_2 \neq \omega_1$, and the difference $(\omega_2 - \omega_1)$ is high.


V_a'  V_a → light bulb [on-off quickly].

Assume $V_a = A \sin(\omega t)$

$V_a' = A \sin(2\omega t)$

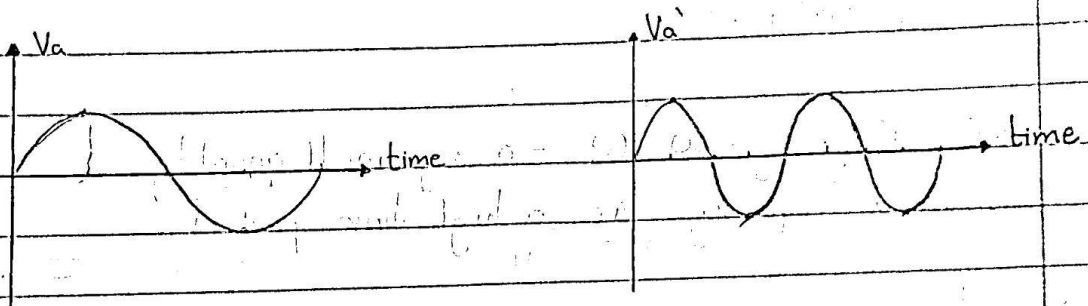

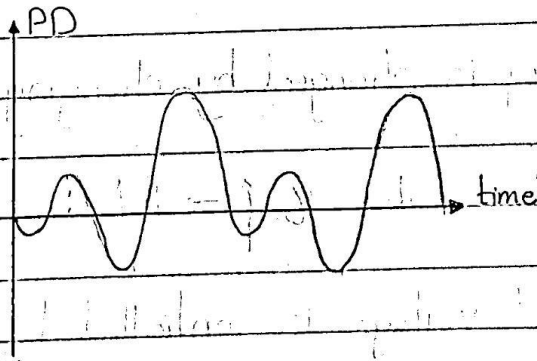∴ $PD = V_a - V_a'$
 "The Potential difference"




At $t=0$: $V_a = V_a'$ [They are in phase].

At the peak, They are 180° out of phase.


Notation: Flicker Frequency : $2\omega - \omega = \omega$.

Case #2:

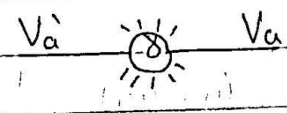$\omega_2 \neq \omega_1$, and the difference $(\omega_2 - \omega_1)$ is very small.



$\therefore PD = V_a - V_{a'}$

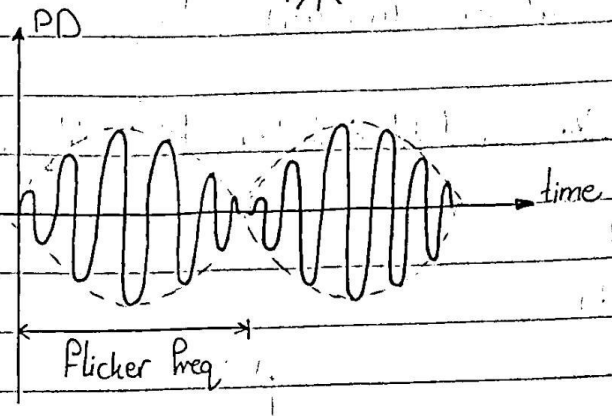


Flicker Frequency = $\omega_2 - \omega_1$ = a very small quantity.
 a small frequency gives a high time period.

* Note:

The frequency is changed by changing the speed of the prime mover.

$n_{s,m} = 120 \frac{P_e}{P}$ when $n_m \uparrow \rightarrow P_e \uparrow$

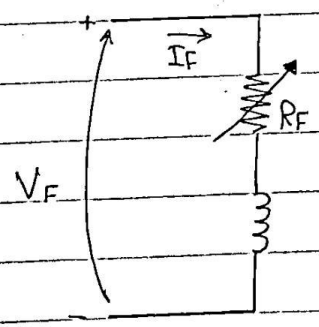
The terminal voltage is controlled by changing R_F :



$R_F \downarrow \rightarrow I_F \uparrow \rightarrow \Phi \uparrow \rightarrow (E_A = k\Phi\omega_m) \uparrow \rightarrow V_\phi \uparrow$

$R_F \uparrow \rightarrow I_F \downarrow \rightarrow \Phi \downarrow \rightarrow (E_A = k\Phi\omega_m) \downarrow \rightarrow V_\phi \downarrow$

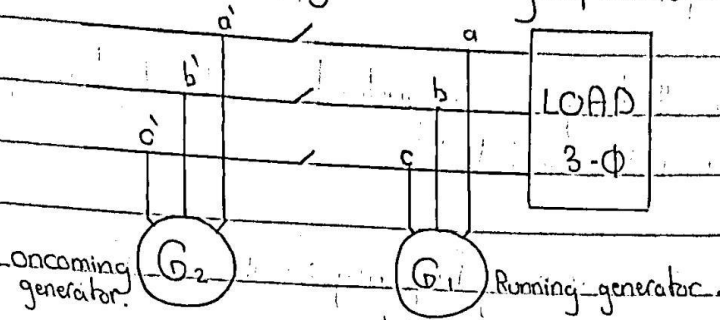
Procedure of synchronizing parallel generator.




- 1] Adjust the speed of G_2 to match the speed of G_1 .
- 2] Using voltmeters adjust V_T (terminal voltage) of G_2 to be equal to V_T of G_1 .

Note: " V_T is controlled via I_f "

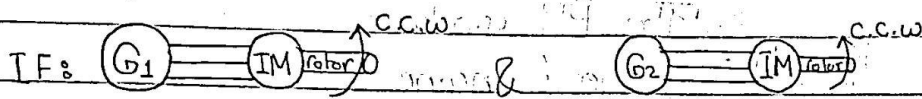- 3] Phase sequence: We can adjust it by two methods:
 - i) Using small 3-phase induction motor



Then they have the same phase sequence.

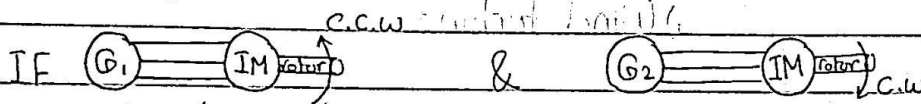

Then they have opposite phase sequence, so two of the three phases of G_2 must be reversed.

- ii) Three light bulb method:

IF G_1 & G_2 have the same phase sequence then the three lamps will glow together and turn off together.

IF G_1 & G_2 have opposite phase sequence then the three lamps will glow in succession.


- 4] Set the frequency of G_2 to be slightly higher than the frequency of G_1 .

When the bulbs (lamps) are turned off V_a is in phase with V_a' and paralleling can be done.

"See case 2 in the previous page".

This method is not very accurate, a better approach is to use a synchroscope.

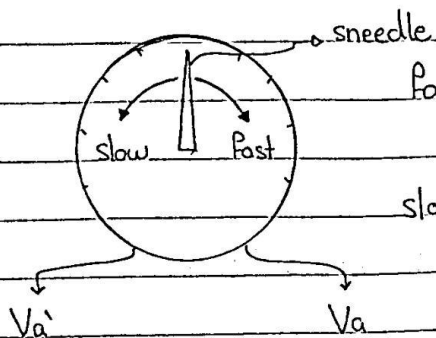
ii Synchroscope: is a device that gives an indication about the phase shift between V_a and V_a'




Fast: The oncoming frequency \gg The running frequency
 The needle will rotate C.W.
 slow: The oncoming frequency \ll The running frequency
 The needle will rotate C.C.W.

Frequency - Power and Voltage - Reactive Power characteristics:

The PM can be:

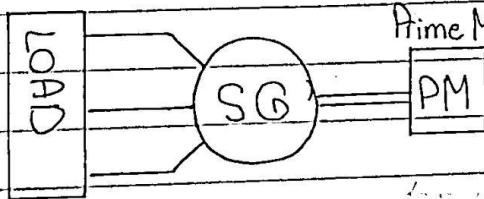

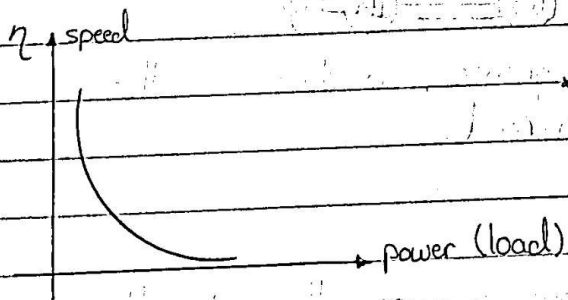
- 1) Diesel engine.
- 2) Water turbine.
- 3) Wind turbine.



The speed droop is non-linear.

To study this curve it's important to find some way to make it linear:

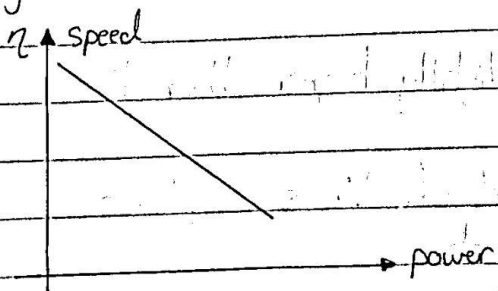The governor mechanism makes the droop characteristics linear.




* a missing note of the "Synchroscope".

When the sneedle is in vertical position as shown in the figure, V_a is in phase with V_a' , you can close the switch.


95

The speed droop (S.D) = $\frac{\eta_{NL} - \eta_{FL}}{\eta_{FL}} \times 100\%$

it's usually fall between (2-4)%.

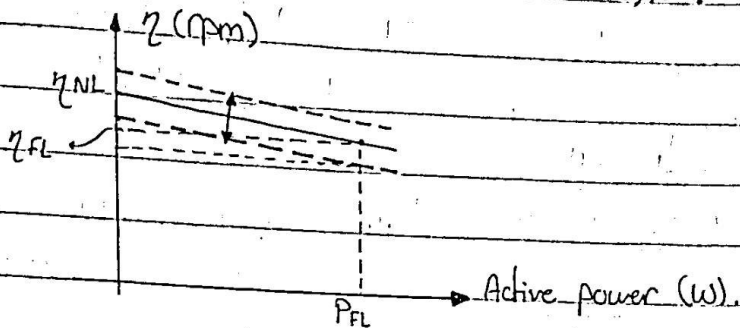

Since $\eta = 120 \frac{f}{P}$, then:

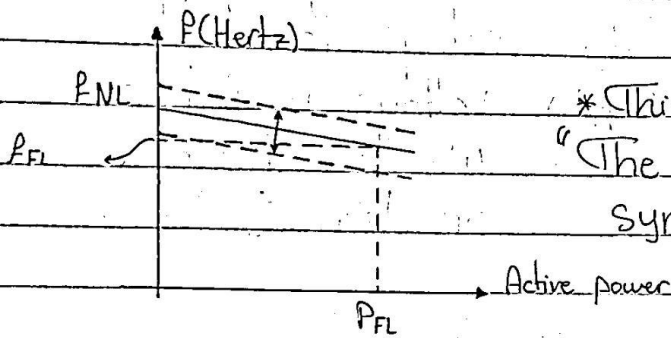

* This curve is known as:
"The droop characteristic of synchronous generator."

Note: While adjusting the set points of governor mechanism you can increase or decrease η_{NL} "see the 1st figure".

To study the Power from the figures above, we need to study the slope;

$$\text{slope} = \frac{\Delta Y}{\Delta X} \rightarrow \frac{f_{FL} - f_{NL}}{P_{FL}} \quad [\text{Hertz / kW}]$$

$$P_{FL} = \frac{1}{\text{slope}} (f_{FL} - f_{NL})$$

$$= \frac{1}{\text{slope}} (f_{NL} - f_{FL})$$


In general, $P = S_p (f_{NL} - f_{FL})$

$\therefore S_p$ is the power slope [kW / Hertz]

By increasing the lagging loads,

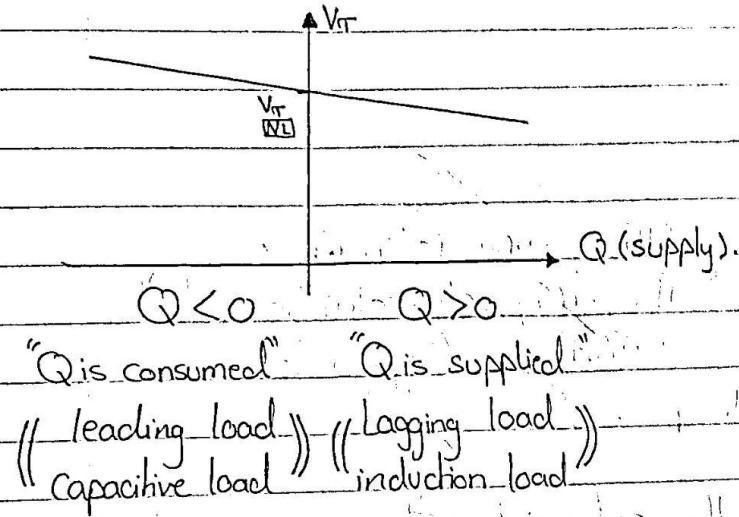- 1) The load will consume more Q.
- 2) The generator will supply more Q.
- 3) The terminal voltage (V_T) will decrease; The relation between the voltage and the reactive power is non-linear, but they found a way to solve this:


By "The AC Voltage regulation", this device will make the relation linear



* Note:
 While adjusting the set points of the voltage regulation we can increase or decrease $V_T(1-l)$.

Example: The figure shows a generator supplying a load. A second load is to be connected in parallel with the first one. The generator has a no load frequency of 61 Hz and a slope $sp = \underline{1 MW/Hz}$. load 1 consumes a real power of 1000 kW = 1 MW at PF 0.8 lagging, while the second load consumes a real power of 800 kW at 0.707 lagging PF.

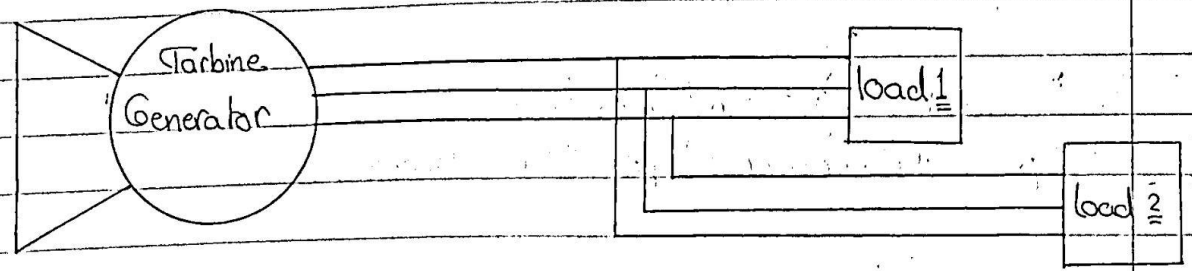- a) Before the switch is closed, what is the operating frequency of the system?
- b) After load 2 is connected, what is the operating frequency of the system?
- c) After load 2 is connected, what action could an operator take to restore the system frequency to 60 Hz.



Solution:

1) let's summarize the given info:

$S_p = 1 \text{ MW/Hz}$ $P_{\text{load1}} = 1000 \text{ kW}$

$f_{NL} = 61 \text{ Hz}$ $P_{\text{load2}} = 800 \text{ kW}$

2) we know the relation:

$$P = S_p(f_{NL} - f_{FL}) \rightarrow f_{FL} = f_{NL} - \frac{P}{S_p}$$

a) $f_{FL} = f_{\text{system}}$

$= 61 - \frac{1000 \text{ k}}{1000 \text{ k}} \Rightarrow \boxed{60 \text{ Hz}}$ $\therefore P$ here is only the load 1 power.

b) $f_{FL} = 61 - \frac{1800 \text{ k}}{1000 \text{ k}} \Rightarrow \boxed{59.2 \text{ Hz}}$ $\therefore P$ here = $P_{\text{load1}} + P_{\text{load2}}$

c) $60 = f_{NL} - \frac{1800 \text{ k}}{1000 \text{ k}} \rightarrow f_{NL} = 61.8$, let's study what's happened here:

when load 2 is connected the frequency falls to 59.2 Hz, we need to restore the system to its proper operating frequency, we know that f_{NL} at the starting was 61, so we need to use the governor to rise the f_{NL} 0.8 Hz so we will restore the system frequency to 60 Hz.


Operation of generators in Parallel with large power systems

This idea is idealized in the concept of an infinite bus;





Infinite Bus: Is a large power system that its voltage and frequency do not vary regardless of how much real and reactive power is drawn from or supplied to it.

1) "The frequency is" constant

2) "The voltage is" constant

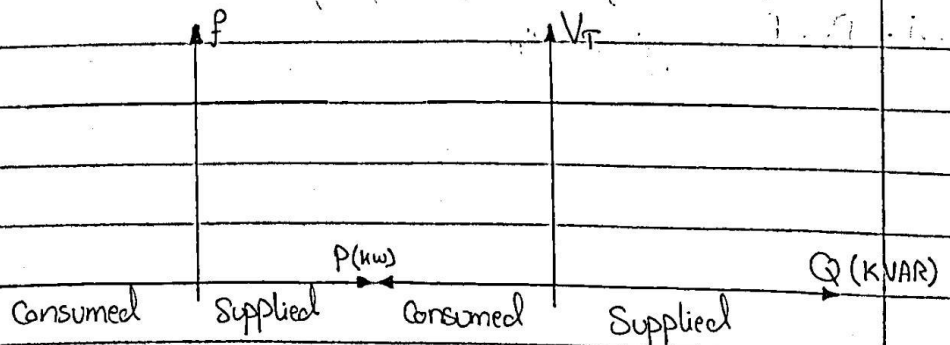


Parallel operation with generators:

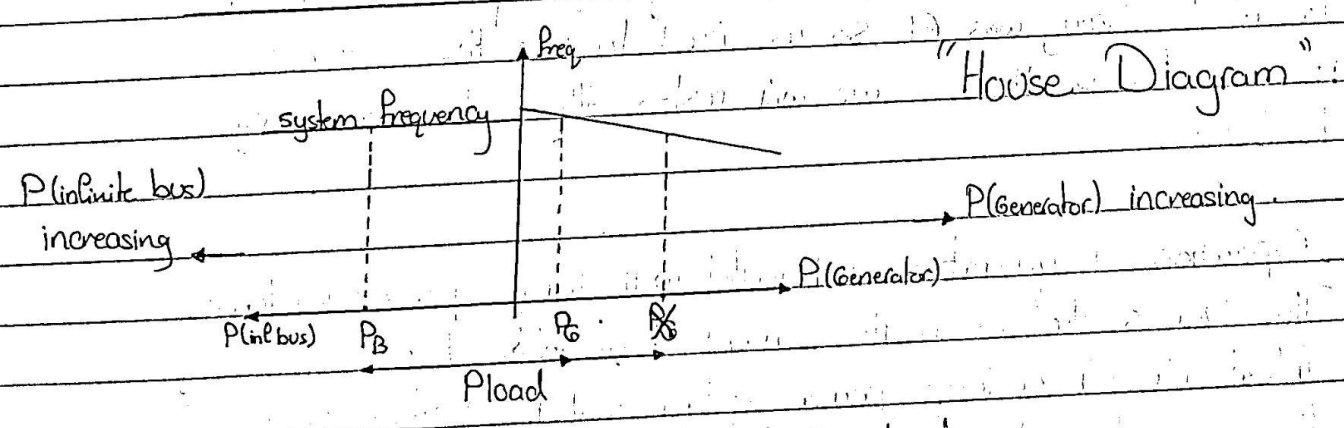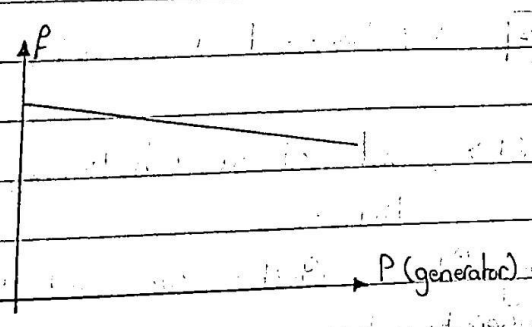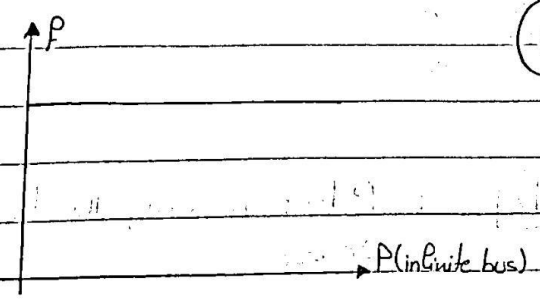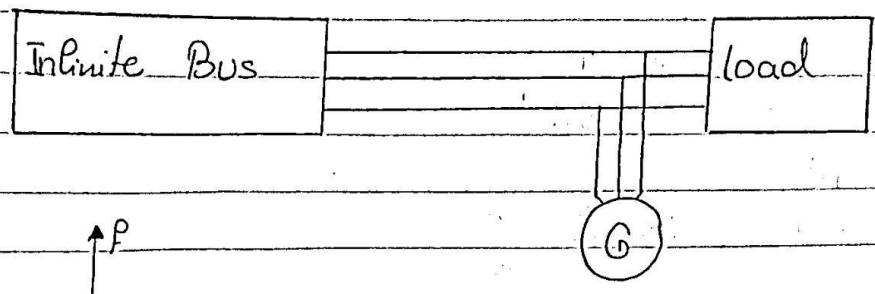

- P_B : Power supplied by the infinite bus to the load.
- P_G : Power supplied by the oncoming generator to the load.
- $P_{load} = P_B + P_G$

At J Synchronizing:

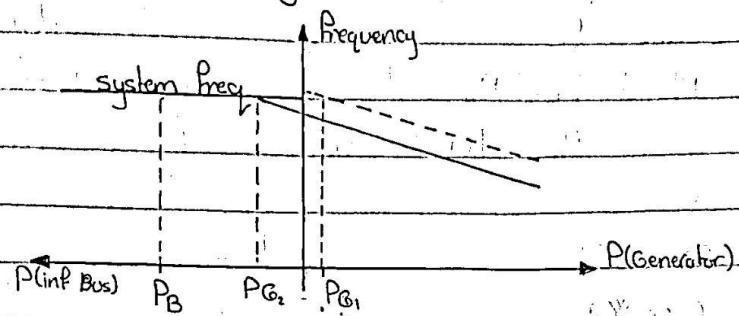

If the frequency of the oncoming generator is slightly higher than the system frequency, then:

- ① P_G is small and positive.
- ② The oncoming machine acts like a generator.

If the frequency of the oncoming generator is slightly lower than the system frequency, then:


- ① P_G is small and negative.
- ② The oncoming machine acts like a Motor.

Note: This connection is a bad one.

Recall: The important of the Governor:

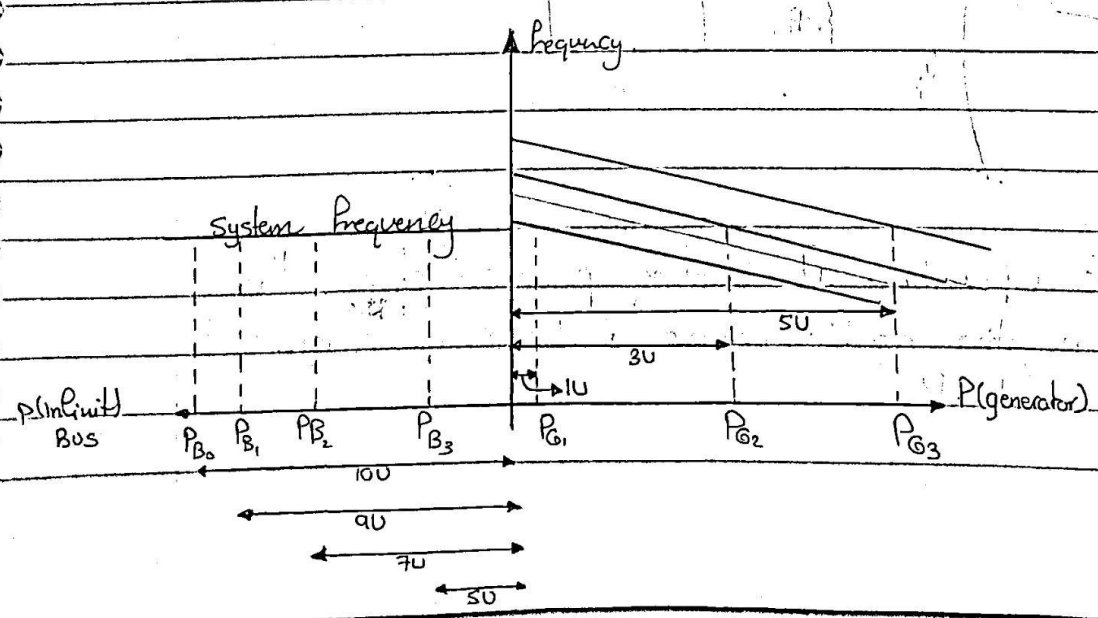- 1) Transform the non-linear "F vs P" curve to linear.
- 2) Move the curve up & down.

Increasing the governor's setting: [Moving]



see the
** as example.

III let the load need 10U of power, U: Unit (KW, MW, GW)

Case #0:

$$P_{load} = P_{B0} + P_{G0}$$

$$= 10U + 0$$

Case #1

$$P_{load} = P_{B1} + P_{G1}$$

$$= 9U + 1U$$

Case #2:

$$P_{load} = P_{B2} + P_{G2}$$

$$= 7U + 3U$$

Case #3

$$P_{load} = P_{B3} + P_{G3}$$

$$= 5U + 5U$$

IF the generator settings ↑ Then P_G ↑ & P_B ↓

The Phasor Diagram:

$$P_{(generator)} = 3V_{\phi} \frac{EA}{X_s} \sin \delta$$

V_{ϕ} is constant → From the infinite bus.


$X_s = \omega L_s$ is constant → From the infinite bus.

$EA = k\Phi\omega$, Φ is constant since we don't change field current (I_f)

ω is constant

→ EA is constant.

$$P_G \propto EA \sin \delta$$

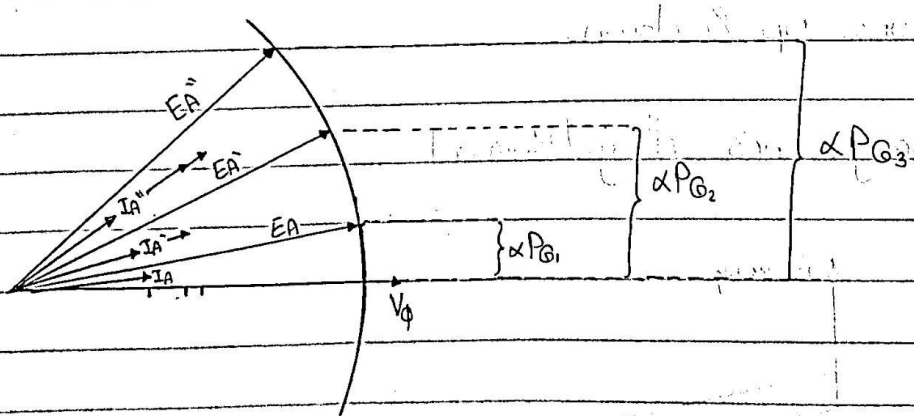


The generator is operating at leading power factor, the generator supplies negative reactive power or it absorbs reactive power from the infinite Bus.

Now a new question appears "How Can the Generator be adjusted to supply reactive power"

By Changing the excitation (field current) & The Q_G is supplied by controlling the field current.
Adjustment of generator reactive power.

P_G is constant.
 $P_G = 3 V_\phi \frac{E_A}{X_s} \sin \delta = 3 V_\phi I_A \cos \theta$, $\therefore V_\phi$ is constant [infinite bus].

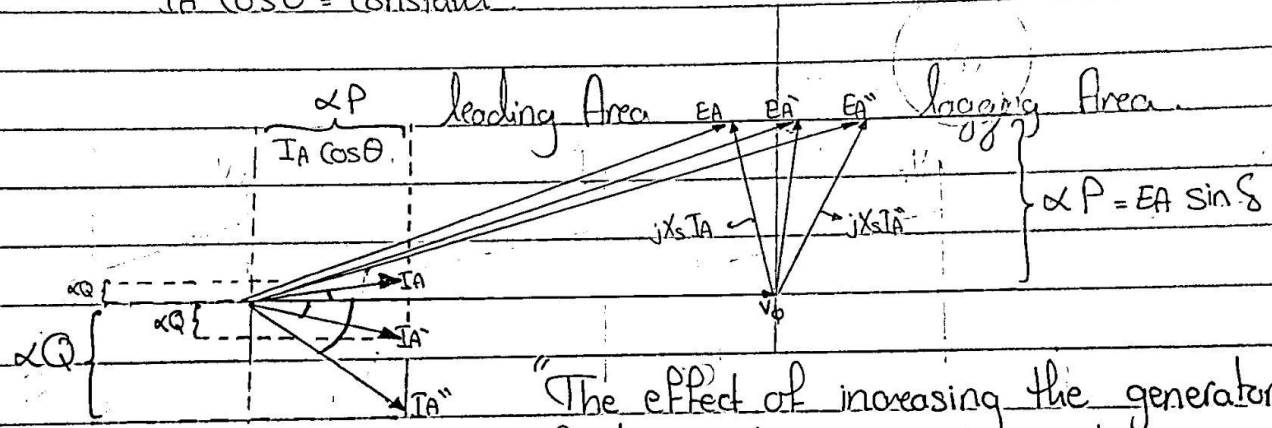Since $P_G \propto E_A \sin \delta$, $P_G \propto I_A \cos \theta$, and it's constant.
 $\rightarrow E_A \sin \delta = \text{constant}$
 $I_A \cos \theta = \text{constant}$



"The effect of increasing the generator's field current on the phasor diagram of the Machine"

The generators consume Q from the infinite bus "under-excitation" process, leading Area.

IF $I_F \downarrow$ then $Q_{\text{absorbed}} \uparrow$
 $\theta \uparrow$, $PF [\cos \theta] \downarrow$




The generators supply Q [reactive power] "Over-excitation" lagging Area,

IF $I_F \uparrow$ then $Q_{\text{supplied}} \uparrow$


Conclusion:

- ① V_T & f_{sys} are controlled via the infinite bus.
- ② P_G is controlled via the governor setting.
- ③ Q_G is controlled via the excitation.

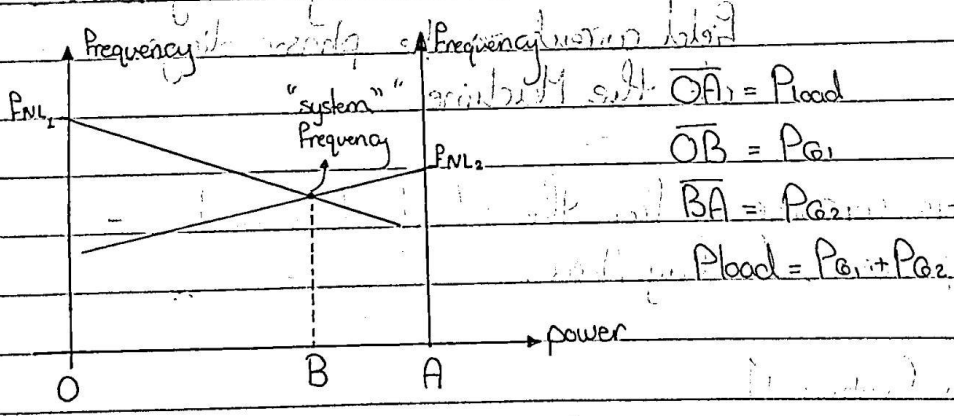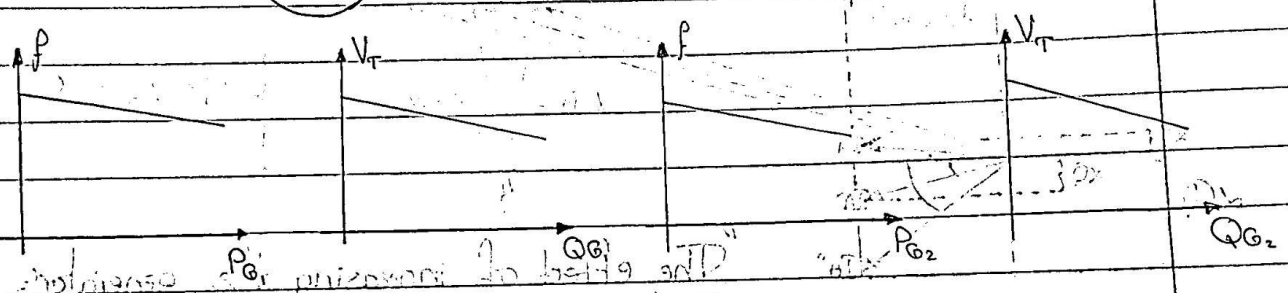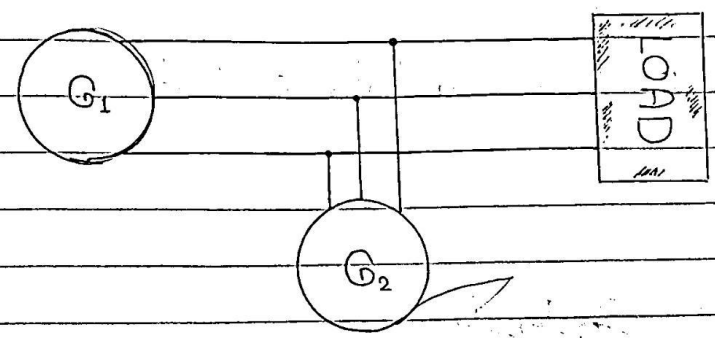→ Parallel operation of generators with other generators of the same size:



Changing the governor setting:

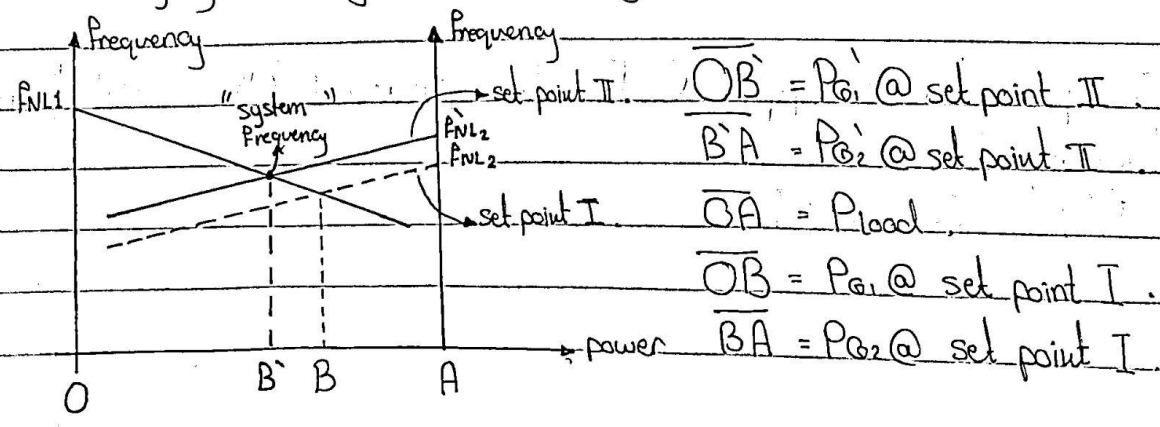


Conclusion :

Changing the governor setting " P_{G_2} "

Then the system frequency \uparrow

$P_{G_1} \downarrow, P_{G_2} \uparrow$ such that $P_{G_1} + P_{G_2} = P_{load}$.

Changing the excitation.

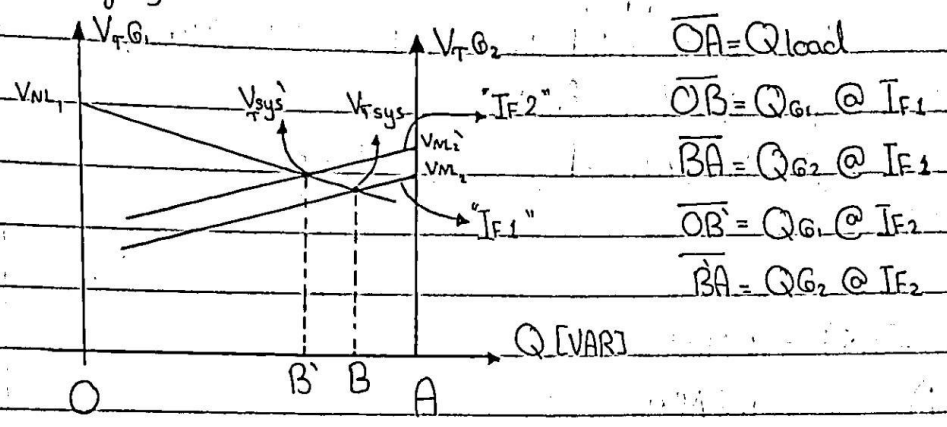

Conclusion :

$I_F \uparrow \rightarrow V_T \uparrow \rightarrow Q_{G_1} \downarrow \& Q_{G_2} \uparrow$

Examples :

1] Two generators supplying a load,

$G_1: f_{NL} = 61.5 \text{ Hz}$ and $sp = 1 \text{ MW/Hz}$

$G_2: f_{NL} = 61.0 \text{ Hz}$ and $sp = 1 \text{ MW/Hz}$

The two generators are supplying a real load totaling 2.5 MW at 0.8 PF lagging.

a) At what frequency is the system operating? How much power is supplied by each generator?

$$P_1 = S_{P_1} (f_{NL1} - f_{sys})$$

$$P_2 = S_{P_2} (f_{NL2} - f_{sys})$$

$$P_{load} = P_1 + P_2$$

$$2.5 \text{ MW} = \frac{1 \text{ M}}{\text{Hz}} (61.5 - f_{sys}) + \frac{1 \text{ M}}{\text{Hz}} (61 - f_{sys}) \quad \text{solving}$$

$$f_{sys} = 60 \text{ Hz}$$

Now $P_1 = 1 \text{ MW} (61.5 - 60) = 1.5 \text{ MW}$.

$P_2 = P_{\text{load}} - P_1 = 1 \text{ MW}$.

b) Suppose an additional 1 MW load were attached to this power system. What would the new system frequency be? How much power would G_1 and G_2 supply now?

When the 1 MW load is added, the total load will be 3.5 MW.

$P_{\text{load}} = sP_1 (F_{NL1} - P_{\text{sys}}) + sP_2 (F_{NL2} - P_{\text{sys}})$

$3.5 \text{ M} = 1 \text{ M} (61.5 - P_{\text{sys}}) + 1 \text{ M} (61.0 - P_{\text{sys}})$ → Solving ...

$P_{\text{sys}} = 59.5 \text{ Hz}$.

Now $P_1 = 1 \text{ M} (61.5 - 59.5) = 2 \text{ MW}$

$P_2 = P_{\text{load}} - P_1 = 1.5 \text{ MW}$

c) With the system in part b, what will the system frequency and generators powers be if the governor set points on G_2 are increased by 0.5 Hz?

$P_{\text{load}} = sP_1 (F_{NL1} - P_{\text{sys}}) + sP_2 (F_{NL2} - P_{\text{sys}})$

$3.5 \text{ M} = 1 \text{ M} (61.5 - P_{\text{sys}}) + 1 \text{ M} (61.5 - P_{\text{sys}})$ solving ...

$P_{\text{sys}} = 59.75 \text{ Hz}$

Note they have the same frequency & slope so $P_1 = P_2$

$P_1 = P_2 = sP (F_{NL} - P_{\text{sys}})$

$= 1 \text{ M} (61.5 - 59.75)$

$= \boxed{1.75 \text{ MW}}$

Notice: The P_{sys} rose, Power of G_2 rose, Power of G_1 fell.

2] A 480-V, 50-Hz, Y-connected, 6-poles SG is rated at 50 KVA at 0.8 PF lagging, It has a synchronous reactance of 1Ω per-phase [Assume that this generator is connected to a steam turbine capable of supplying up to 4500 W]

The friction and winding losses are 1.5 kW and the core losses are 1 kW. It's rated current is 60 A at 0.8 lagging

The field current has been adjusted so that $V_T = 480V$ at no-load.

a) What is the speed of rotation of this generator:

$$\omega_m = \frac{2}{P} \omega_e$$


Note: $\eta = \frac{120}{P} \text{ Hz}$

$$= \frac{2}{6} (2\pi(50))$$

$$\omega_m = 1000 \frac{\pi}{30} \text{ rad/sec}$$

b) What is the terminal voltage of the generator at full load:

Per-phase equivalent circuit:

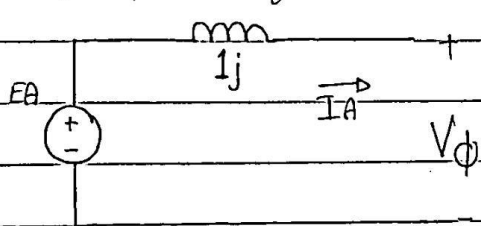

$$I_A = 60 \angle -\cos^{-1}(0.8)$$

$E_A = 480 \text{ volt}$ at no-load.

$$\vec{E}_A = jX_s \vec{I}_A + \vec{V}_\phi \Rightarrow \sqrt{\frac{2}{3}} (480) \angle 0 = j(60 \angle -36.87) + \vec{V}_\phi$$

$\sqrt{\frac{2}{3}}$ is added $\Rightarrow \sqrt{2}$ to have the peak value

$1/\sqrt{3}$ to have a phase voltage, not line voltage.

Math note: $\vec{E}_A = jX_s \vec{I}_A + \vec{V}_\phi$ is two equations not one.

one is the magnitude & the other is the angle.

Since we need $|V_\phi|$, we will use the magnitude equation:

$$j(60 \angle -36.87) = 36 + 48j$$

$$\sqrt{\frac{2}{3}} (480) = \sqrt{(V_\phi + 36)^2 + (48)^2}$$

$$V_\phi = 352.96 \text{ volt "peak value"} \rightarrow V_\phi = 250 \text{ volt rms}$$

V_T is the terminal voltage, the line voltage

$$= \sqrt{3} V_\phi \Rightarrow 410 \text{ volt}$$

c) What is the efficiency under full-load condition?

$$\eta = \frac{P_{out}}{P_{in}}$$

$$P_{out} = \sqrt{3} V_T I_A PF$$
$$= \sqrt{3} (410) (60) 0.8$$
$$= 34.1 \text{ kW}$$

$$P_{in} = P_{out} + P_{core \text{ losses}} + P_{copper \text{ windage}}$$
$$= 34.1 + 1 + 1.5$$
$$= 36.6 \text{ kW}$$

$$\eta = \frac{34.1}{36.6} = 93.2\%$$

d) Calculate the applied Torque

$$T_{app} = \frac{P_{in}}{\omega_s}$$

$$= \frac{36.6 \text{ kW}}{1000 \left(\frac{\pi}{30}\right)}$$

$$= 350 \text{ N.m}$$

Chapter 5: Synchronous Motor

Principle of Operation.


- i. The field current produces the ~~stator~~ rotor magnetic field \vec{B}_s .
- ii. A set of 3 ϕ voltage is applied to stator windings which produces a set of 3 ϕ current to flow in the stator windings.
- iii. The current will produce a rotating stator magnetic field \vec{B}_s which rotates at synchronous speed ω_s .
- iv. The rotor is rotating at starting by some external means to obtain a magnetic locking between the rotor & stator poles, then produce a continuous induced torque " T_{ind} ".

Recall:

$$T_{ind} = k \vec{B}_r \times \vec{B}_s = k \vec{B}_r \times B_{net}$$

$$= k B_r B_{net} \sin \delta \quad \text{ii } \delta = \text{"Torque angle"}$$

The Equivalent circuit (per-phase):

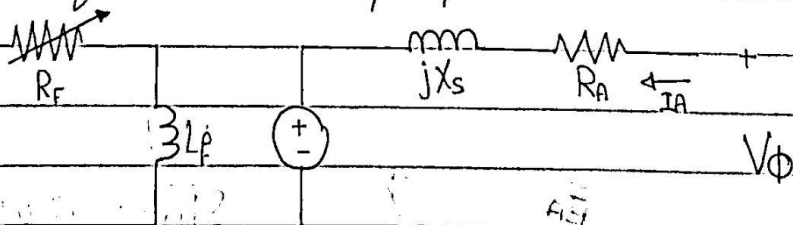

Field

Armature

ii R_a : Is the armature Resistance


X_s : Synchronous Resistance

→ KVL at the armature circuit:


$$\vec{V}_\phi = \vec{E}_A + R_A \vec{I}_A + jX_s \vec{I}_A$$

→ Phasor Diagram:

A) "Motor" :

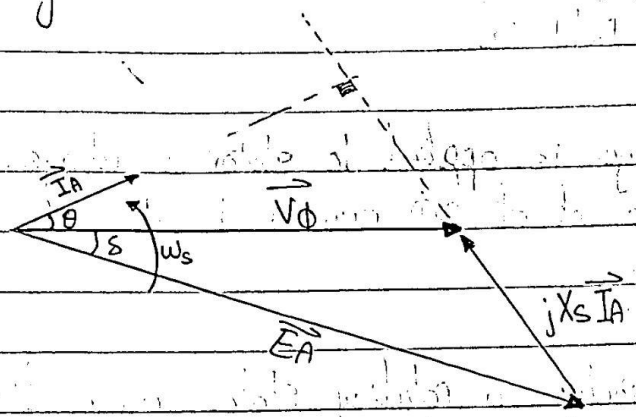


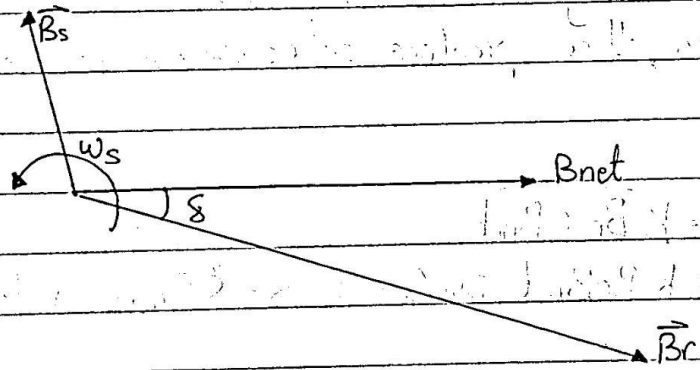- \vec{B}_r corresponds to \vec{E}_A
- \vec{B}_{net} " " \vec{V}_ϕ
- \vec{B}_s " " $jX_s \vec{I}_A$




Note:
 $\omega_s \Rightarrow$ C.C.W
 $T_{ind} \Rightarrow$ C.C.W

B) "Generator" :

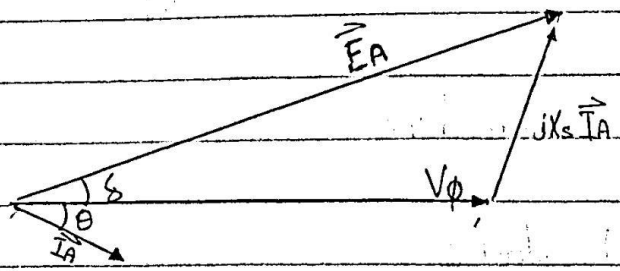


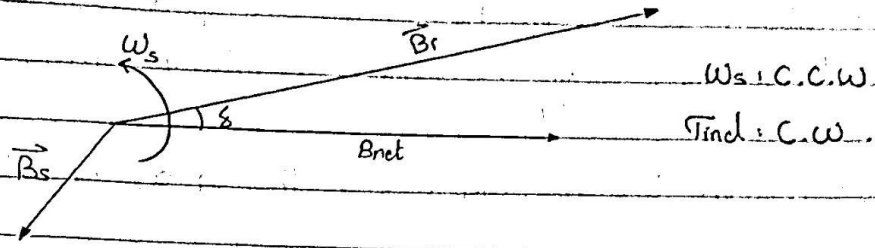Note:
 $T_{ind} \Rightarrow$ C.W
 $\omega_s \Rightarrow$ C.C.W



Torque speed characteristics:
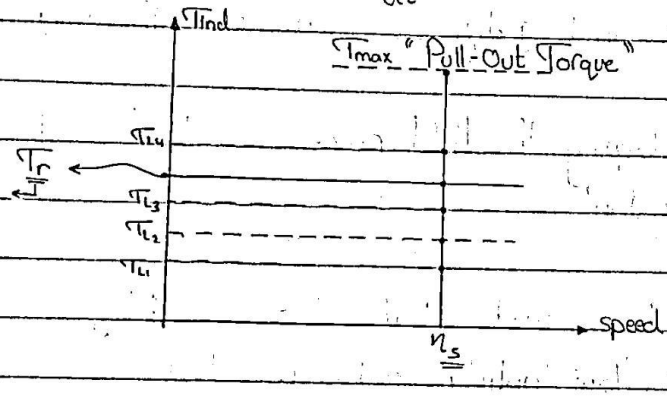
$$T_{ind} - T_{load} = J \frac{d\omega}{dt}$$



*Note: Another Name for the rated torque is the nominal torque

n_s : Synchronous speed

The induced torque is always equal the load torque so,
 $T_{ind} = T_{load} \rightarrow T_{ind} - T_{load} = 0$; $0 = J \frac{d\omega}{dt} \rightarrow \omega$ is constant $= \omega_s$

Def: Pull-Out torque: It is the maximum operating torque of "SM"

$$* T_{max} = (2.5 - 3) T_r$$

Torque equation:

$$T_{ind} = \frac{3V\phi EA}{X_s \omega_s} \sin \delta$$

$$T_{max} = T_{pull-out} = \frac{3V\phi EA}{X_s \omega_s} \text{ since } \delta = 90^\circ \text{ "max-torque angle"}$$

If $T_{load} > T_{max}$, The motor will lose the synchronism.

"Slipping pole phenomenon"

Speed Regulation: :

Since the SM always operates at the synchronous speed we can see that its speed regulation = $\frac{\omega_{NL} - \omega_{EL}}{\omega_{FL}} \times 100\%$ is always zero.

" $\omega_{NL} = \omega_{FL} = \omega_s$ " , from this we can consider the SM as an ideally performed Machine.

SR = 0%

Effect of load changes:

$T_{ind} = \frac{3V\phi EA}{X_s \omega_s} \sin \delta$


① $T_{ind} - T_{load} = J \frac{d\omega_r}{dt}$

② ω_r : The rotor speed.

Since we are changing the load but keeping the field current constant the induced voltage (EA) = $k\phi\omega_s$ is constant.

Assume that $T_{load} \uparrow$, from Newton's law $\omega_r \downarrow$, but $\delta \uparrow$ so $\sin \delta \uparrow$ $\rightarrow T_{ind} \uparrow$ from ① $\rightarrow \omega_r \uparrow$ from Newton's law until it reaches ω_s but at larger δ .

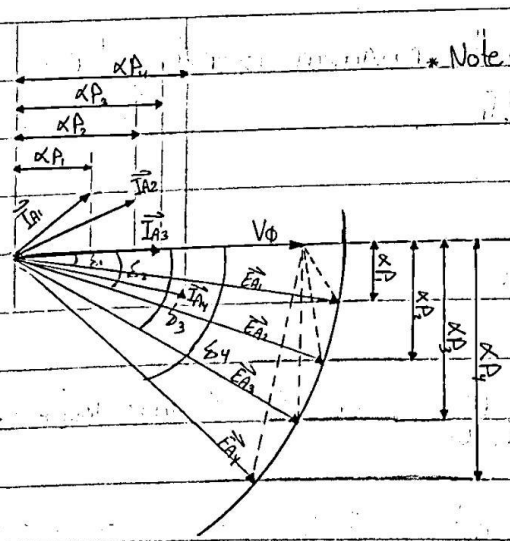Phasor Diagram: "load increases $\Rightarrow \vec{I}_A$ increases"



* Note: leading: Q is supplied from the Motor.
 unity: Q = 0
 lagging: Q is absorbed by the Motor.

$EA_1 = EA_2 = EA_3 = EA_4$

When the load \uparrow \rightarrow The PF becomes less leading \rightarrow unity \rightarrow lagging \rightarrow more lagging.


Effect of the Field current changes:

Assume P is constant.

$$P = \frac{3V\phi EA \sin \delta}{X_s} = 3V\phi I_A \cos \theta = \text{Constant}$$

$$EA \sin \delta = \text{constant}, I_A \cos \theta = \text{constant}$$
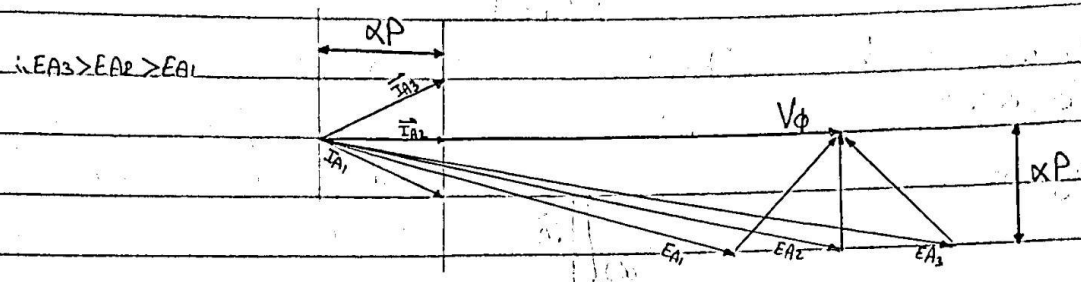
$$EA = k\phi\omega \therefore \phi \propto I_f$$



when \vec{I}_A lags \vec{V}_ϕ then we are operating in the "Under-excited region"

when \vec{I}_A leads \vec{V}_ϕ then we are operating in the "Over-excited region"

Under-excited means EA is less than the Unity EA

Over-excited means EA is more than the Unity EA

When $I_f \uparrow$, The PF becomes less lagging \rightarrow unity \rightarrow leading \rightarrow more leading

- Conclusion:
- 1) The real power is controlled by the load changes.
 - 2) The reactive power is controlled by the Field current.

V curves of SM:


1) The lagging PF region:

The field current is small "underexcited";

Q is consumed, the motor is operating

as an inductive load

$$EA \cos \delta < V_\phi$$

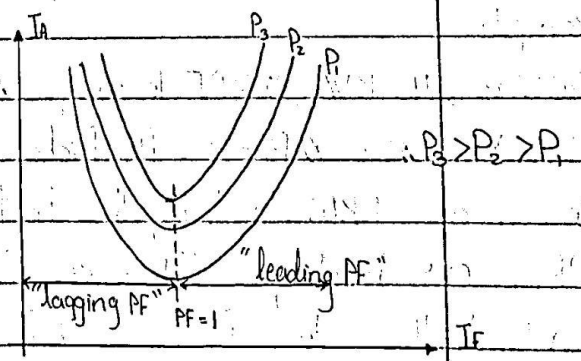

2) The leading PF region:

The field current is large "Overexcited", Q is supplied. The Motor

operates as a capacitive load $EA \cos \delta > V_\phi$.

→ Synchronous Condenser: "Synchronous Capacitor"


It is a synchronous motor without shaft operated at no load "P=0" and it is over-excited, [Q is supplied].

It was used historically as a power factor correction device.

$$P = \frac{3V\phi EA \sin \delta}{X_s} = 3V\phi IA \cos \theta$$
, and [since "P=0" and (EA & IA) have numerical values]

then the only way to have a "P=0":
 "δ=0 & θ=90°"


Phasor Diagram:

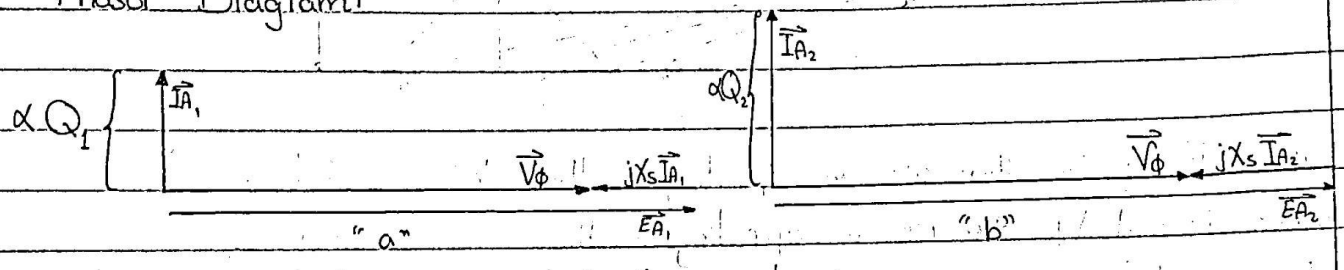

"a" & "b" represent how to control the reactive power

Power Factor Correction can be adjusted by:

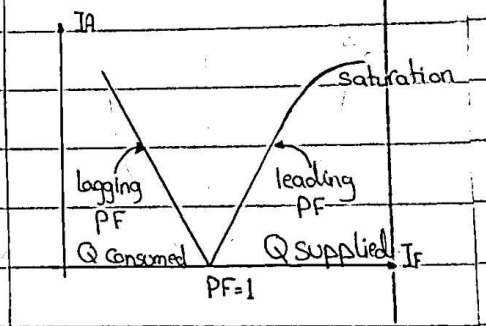- 1] Synchronous condenser.
- 2] Static Capacitor.
- 3] Power electronics, "Static VAR compensator"



"V curve for SC"


Example:

208 v, 45 KVA, 0.8 PF leading, Δ-connected, 60 Hz, synchronous machine. Has $X_s = 2.5 \Omega$ & $R_s = 0$. Its friction and windage losses are 1.5 kW and its core losses are 1 kW. Initially the shaft is supplied a 15 hp load and the motor PF is 0.8 leading "1 hp = 746 W"

a) Find the value of \vec{I}_ϕ , \vec{I}_L , \vec{E}_A ?

b) Assume that the shaft load is now increased to 30 hp, Find \vec{I}_ϕ , \vec{I}_L & \vec{E}_A ?
 what is the new motor PE?

Solution:

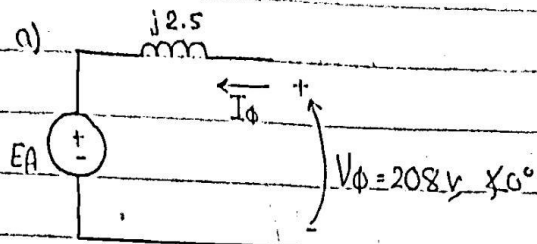

$V_\phi = V_L$ since its Δ connected.

KVL on the armature circuit:

$$\vec{V}_\phi = X_s \vec{I}_A + \vec{E}_A$$

$$208 \angle 40^\circ = (j2.5) \vec{I}_A + \vec{E}_A \quad \text{two unknowns and one equation:}$$

given the output power = 15 hp.

$$P_{out} [\text{mechanical}] = 15 \times 746 = 11.19 \text{ kW}$$

to find $\vec{I}_\phi = \vec{I}_A$, $P_{in} = P_{out} + P_{losses}$

$$P_{in} = 13.69 \text{ kW} = 3 V_\phi I_\phi \cos \theta$$

$$\Rightarrow I_\phi = \frac{13.69 \text{ k}}{3(208)(0.8)} \Rightarrow 27.4 \angle 36.87^\circ \text{ A} \quad (1)$$

$$I_L = \sqrt{3} I_\phi = 47.5 \text{ A} \quad (2)$$

$$\begin{aligned} \vec{E}_A &= 208 \angle 40^\circ - j(2.5)(27.4) \angle 36.87^\circ \\ &= 255 \angle -12.4^\circ \end{aligned}$$

b) KVL on the armature circuit:

$$208 \angle 40^\circ = 2.5j \vec{I}_A + \vec{E}_A$$

since $\vec{E}_A = k\phi\omega$ and we don't change the ϕ so $|\vec{E}_A|$ is constant.

$$\vec{E}_A = 255 \angle \delta'$$

To find \vec{I}_A lets go back to the KVL

$$\vec{I}_A = \frac{208 \angle 40^\circ - \vec{E}_A}{(2.5)j}$$

$$I_A \angle \theta = \frac{208 \angle 40^\circ - 255 \angle \delta'}{(2.5)j}, \text{ the challenge now to find } \delta'$$

$$P_{out} = 30 \text{ hp} = 22.38 \text{ kW}$$

$$P_{in} = P_{out} + P_{losses}$$

$$= (22.38 \text{ k} + 2.5 \text{ k})$$

$$= 24.88 \text{ k}$$

$$\Rightarrow 24.88 \text{ k} = 3 V_\phi I_A \sin \delta'$$


$$\delta' = 23^\circ$$

$$\vec{I}_A = \frac{208 \angle 40^\circ - 255 \angle -23^\circ}{(2.5)j} = 41.27 \angle 15^\circ \text{ A}$$

$$PF = \cos^{-1}(-15) = 0.966 \text{ leading.}$$

Starting of Synchronous Motor

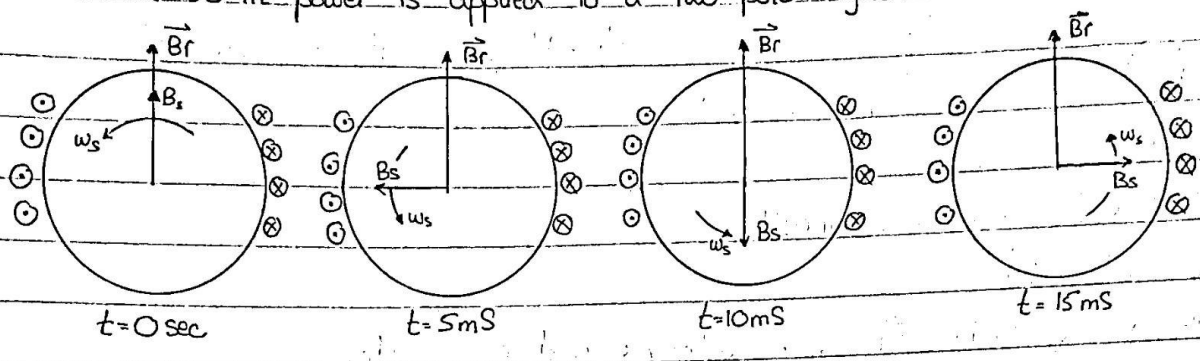Assume that a 50 Hz power is applied to a two-pole synchronous machine "Motor".



$\omega_s = \text{Synchronous Speed}$

Note: 5ms, 10ms & 15ms are chosen since $f = 50 \text{ Hz}$, so $T = \frac{1}{50} = 20 \text{ ms}$

and we are dealing with 2-pole Motor " $\omega_m = \omega_s$ "

$T_{ind} = k \vec{B}_r \times \vec{B}_s$, So at:

- $t = 0 \text{ sec} \rightarrow T_{ind} = 0$ * Here the problem has appeared,
- $t = 5 \text{ sec} \rightarrow T_{ind} : C.C.W$ The Motor will vibrate heavily causing overheating
- $t = 10 \text{ sec} \rightarrow T_{ind} = 0$
- $t = 15 \text{ sec} \rightarrow T_{ind} : C.W$

Methods to start the synchronous Motor:

1. Using external prime mover:

Run the machine as a generator using the prime mover
 increase the rotor speed up to ω_s
 Disconnect the prime mover

2. Using damper winding or amortisseur windings:

This method will start up the synchronous motor like 3- ϕ induction Motor.


3. Reducing the electric frequency

$$n_s = \frac{120}{P} f_e$$

When f_e is small the speed of (B_s) will be also small

The rotor can accelerate and lock in with (B_s)

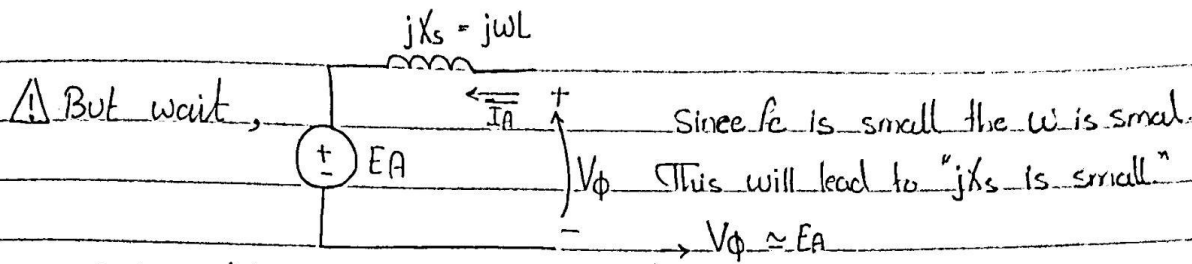
When the motor is started, increase the electric frequency gradually up to its normal value.



Therefore, $V_\phi = k\phi\omega$; SO:

$\phi \propto \frac{V_\phi}{\omega}$, to avoid increasing the flux to the saturation, the ratio of $\frac{V_\phi}{\omega}$ should be appropriate.

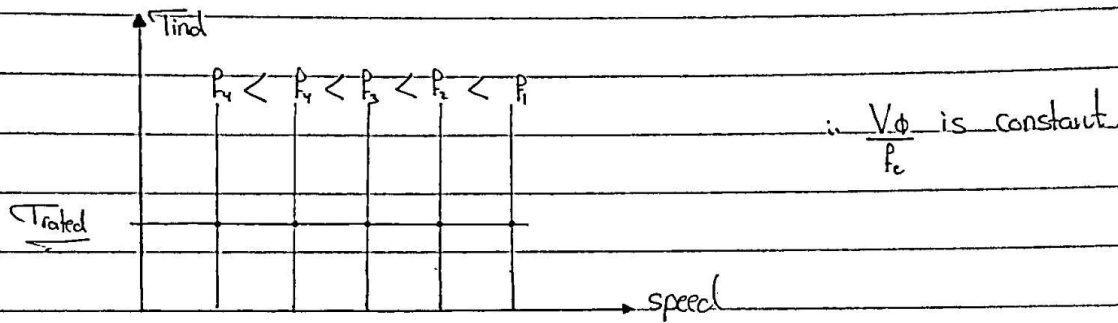Thus, the voltage must be decreased with ρ_c by the same factor to keep ϕ constant and not get saturated.



"VVVF Drive" Variable Voltage Variable Frequency
 Block Diagram:

