



BIRZEIT UNIVERSITY

Faculty of Engineering and Technology
Electrical and Computer Engineering Department
Electronics LAB (ENEE3102)
Report of Experiment #3
The Transistor Biasing and the DC Parameters

Prepared by:

Name: Sara Totah

Student ID: 1181779

Instructor:

Mohammad Jihad Al Jubeh

Date:

20/9/2020

Section: #1

Table of Contents

Abstract:	2
Theory:	2
Procedure, Data and results:	5
I. COMMON EMITTER TRANSISTOR AMPLIFIER:	5
II. COMMON COLLECTER TRANSISTOR AMPLIFIER:	6
III. COMMON BASE TRANSISTOR AMPLIFIER:	8
Conclusion:	11
References:	11

Abstract:


The aim of this experiment was investigating the properties of the transistor amplifier in its three configuration, common emitter, common collector and common base connection, also in this experiment the effect of applying sinusoidal signal to a transistor connected in common emitter was investigated.

Theory:

There are two types of transistor npn and pnp types, both of them can work in three regions: Active, Saturation and cut-off region.


Transistor amplifier properties:

1. Common emitter:

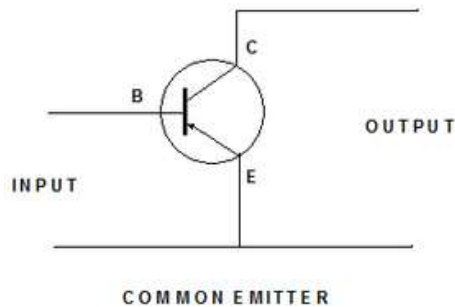

- Voltage gain ($A_v > 1$).
- Current gain ($A_i > 1$).
- Input Impedance (Z_i) is large.
- Output Impedance (Z_o) is large.


2. Common Collector:

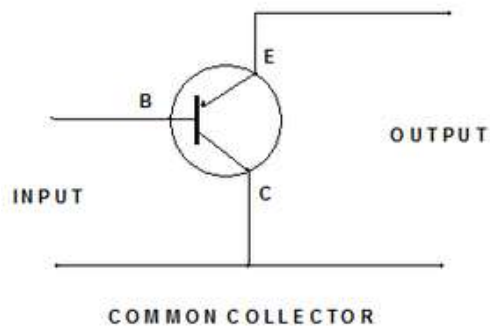

- Voltage gain ($A_v < 1$).
- Current gain ($A_i > 1$).
- Input Impedance (Z_i) is very large.
- Output Impedance (Z_o) is very small.

Note: The small signal gain voltage less than 1 is used to improve total voltage gain of multistage amplifier.


3. Common Base:

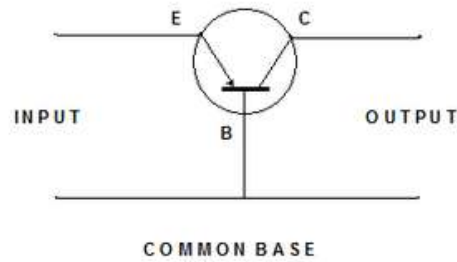

- Voltage gain (A_v) > 1 .
- Current gain (A_i) < 1 .
- Input Impedance (Z_i) is very small.
- Output Impedance (Z_o) is large.

Approximate BJT models:

1. Common Emitter & Common Collector:

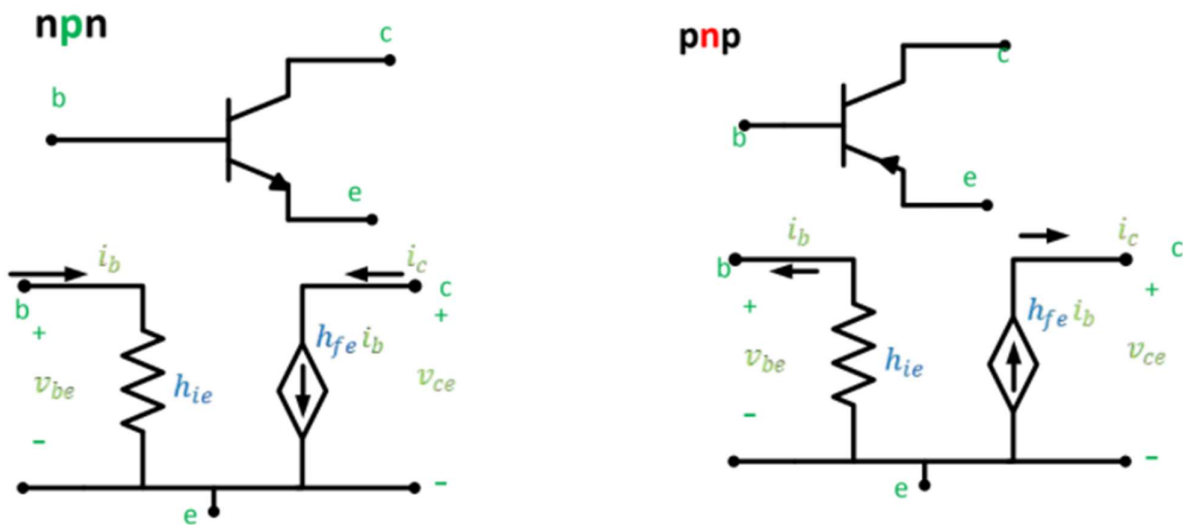


$$I_c = h_{fe} \cdot i_b = \beta i_b \quad (1)$$

$$h_{fe} = \beta \quad (2)$$

$$h_{ie} = \frac{V_T}{I_B} = \frac{\beta V_T}{I_C} = \frac{(\beta + 1)V_T}{I_E} \quad (3)$$

2. Common Base:

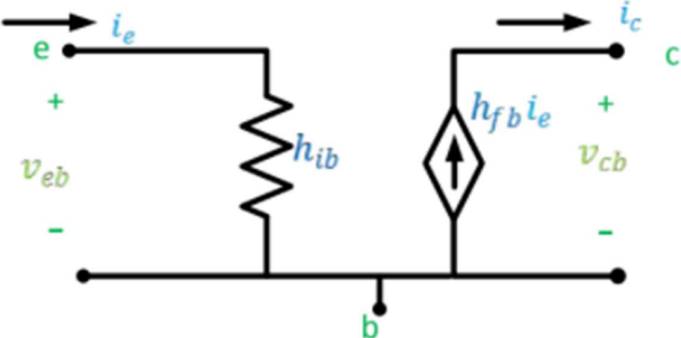

$$I_c = h_{fb} \cdot i_e = \alpha i_e \tag{1}$$

$$h_{fb} = \alpha \tag{2}$$

$$h_{ib} = \frac{V_T}{I_E} \tag{3}$$

$$h_{ie} = (h_{fe} + 1) \cdot h_{ib} \tag{4}$$

Procedure, Data and results:

I. COMMON EMITTER TRANSISTOR AMPLIFIER:

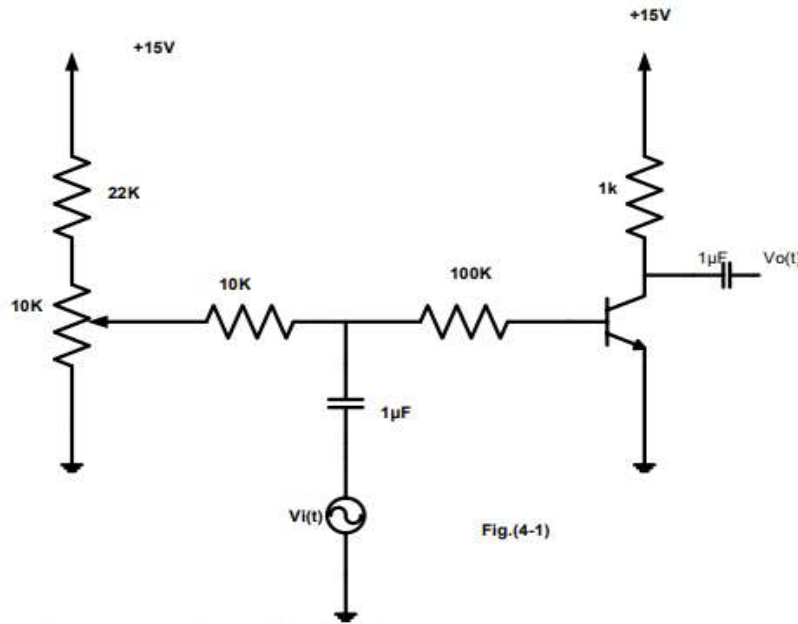


Figure (4 - 1)

First, the circuit in figure (4 – 1) was connected, the power supply and the function generator were connected, then the frequency of the function generator was set to 1KHz, and the amplitude to zero, the DC collector voltage (V_c) was adjusted to 8 volts, then the oscilloscope channels was connected to the base and to the output of the circuit, and the function generator was adjusted till the output voltage of the circuit = 8 volts peak-peak, and the measures were taken.

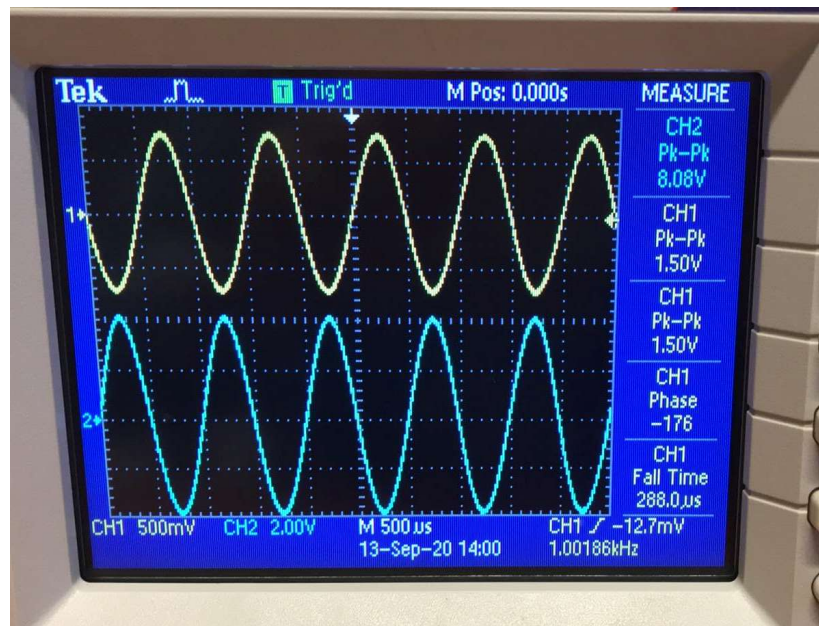


Figure (4 – 1)-wave

$$V_o = 4 \text{ volts}$$

$$V_{be} = 0.614 \text{ volts}$$

$$V_i = 1.50 \text{ volts}$$

$$I_c = 2.4\text{mA}$$

$$I_b = 34.7\mu\text{A}$$

$$I_i = I_b = 34.7\mu\text{A}$$

$$I_o = 15\text{mA}$$

- Voltage gain of the transistor: $A_v = V_o/V_{be} = 4 / 0.614 = 6.5$
- Voltage gain of the amplifier: $A_v = V_o/V_i = 4 / 1.5 = 2.6$
- Current gain of the transistor: $A_i = I_c / I_b = 69.1$
- Current gain of the amplifier: $A_i = 432.2$
- Input Impedance: 43.23k

II. COMMON COLLECTOR TRANSISTOR AMPLIFIER:

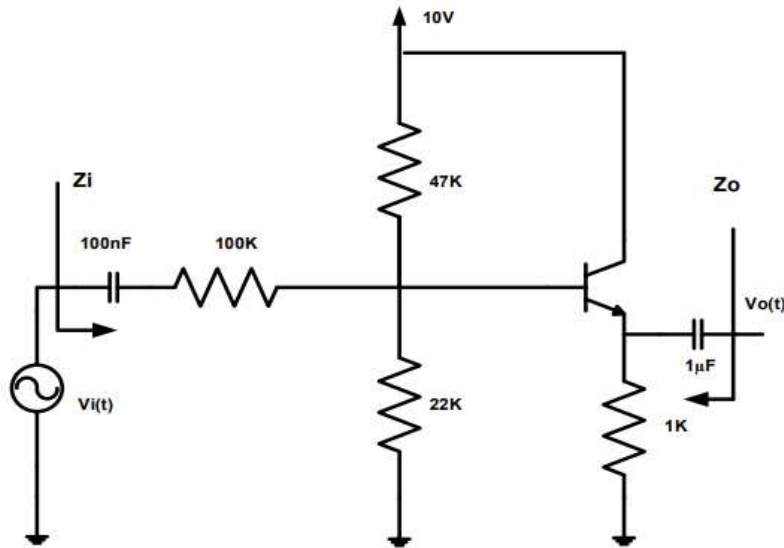


Fig.(4-2)

Figure (4 - 2)

First, the circuit in figure (4 – 2) was connected, the variable dc control was set to minimum, then the power supply was switched on and the variable dc voltage was adjusted to give a V_{cc} of +10v, then the frequency of the sine wave generator of 1kHz, and the output of the generator was set to zero by disconnecting its output, then some measures were taken:

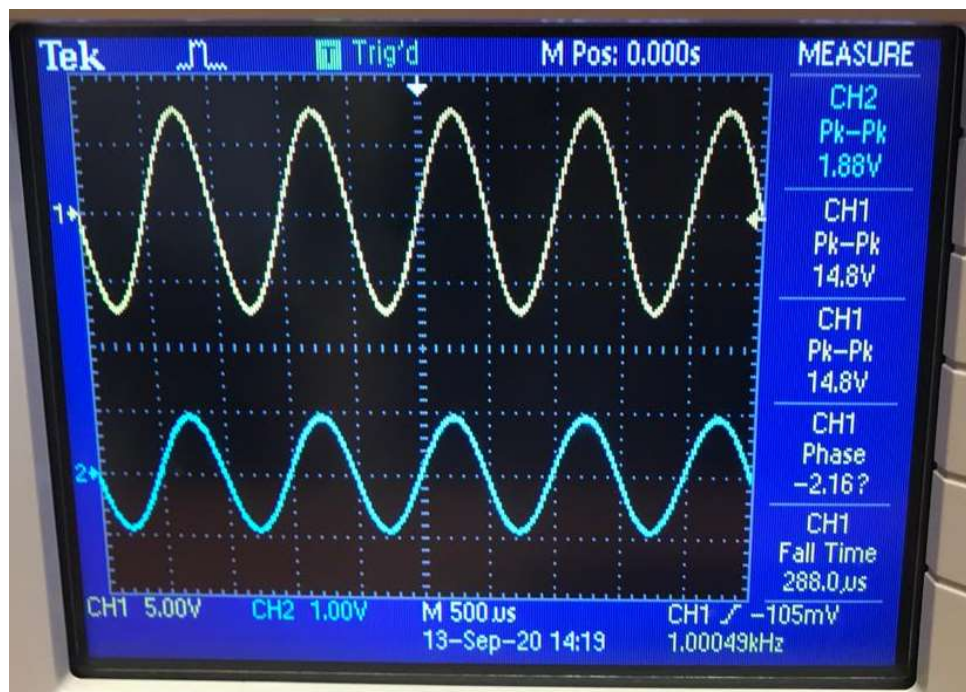


Figure (4 - 2) - wave 1
Output Voltage vs input voltage

$$V_E = 2.3\text{v}$$

$$V_B = 3\text{v}$$

Then the output amplitude was adjusted until the output amplitude is 2 volts peak-peak, and the input voltage needed to achieve this output was measured:

$$V_{in} = 15/2 = 7.5\text{v}$$

$$V_{out} = 2/2 = 1\text{v}$$

→ Voltage gain: $A_v = V_o/V_i = 0.13$

Then the voltage around 100k was measured:

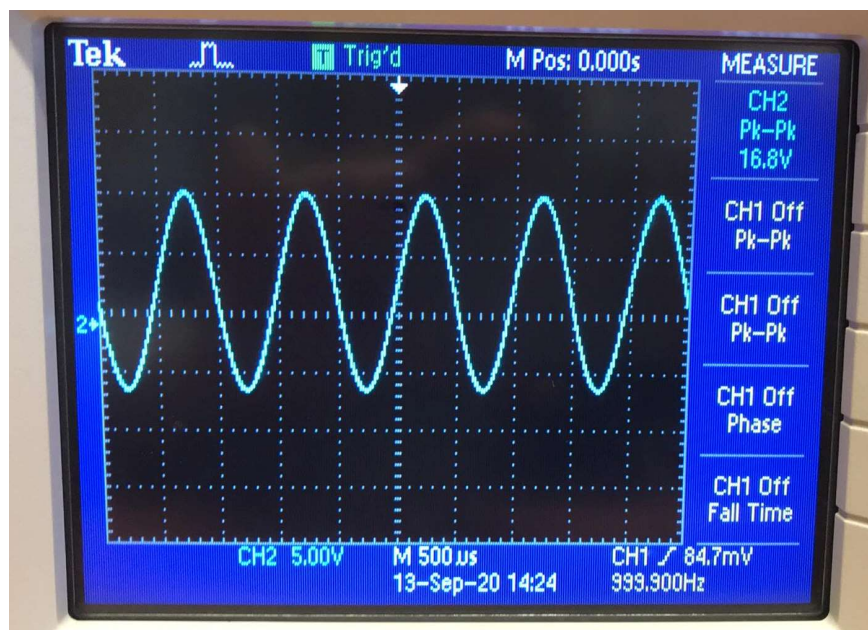


Figure (4 – 2) - wave 2

- $i_{in} = V_{100k\Omega} / 100K\Omega = 16.8 / 100k = 0.168mA$
- $i_{out} = V_{out} / 1k\Omega = 1mA$
- $A_i = i_{out} / i_{in} = 1m / 0.168m = 5.95$
- $Z_i = V_{in} / i_{in} = 7.5/0.168m = 44.6k$
- $Z_{out} = V_T / I_T = 7mV / 37.77 \mu A = 185.3$

Quantity	Measured Values
V_{in}	7.5v
V_{out}	1v
i_{in}	0.168mA
i_{out}	1mA
	Calculated Values
$A_v = V_{out}/V_{in}$	0.13
$A_i = i_{out} / i_{in}$	5.95
$Z_{in} = V_{in} / i_{in}$	44.6k
Z_{out}	185.3

III. COMMON BASE TRANSISTOR AMPLIFIER:

Note: this part was done theoretically using Pspice.


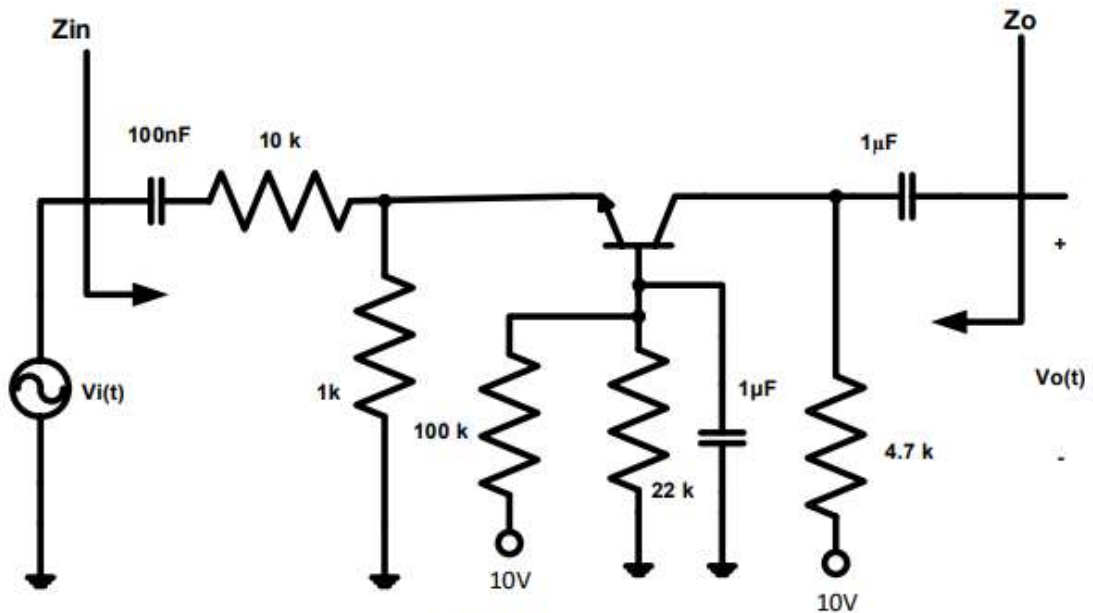


Fig.(4-3)

Figure (4 - 3)

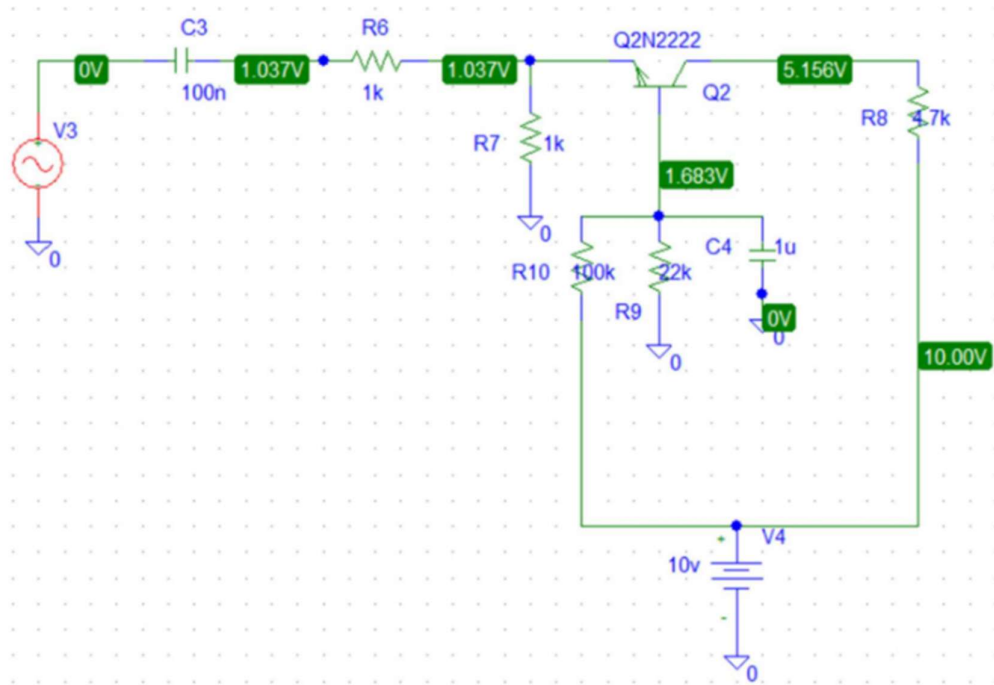First the circuit in Figure (4 – 3) was connected, the variable dc control was set to minimum, then the power supply was switched on and the variable dc voltage was adjusted to give a V_{cc} of +10v, then the frequency of the sine wave generator of 1kHz, and the output of the generator was set to zero by disconnecting its output, then some measures were taken:




$V_{BE} = 0.651\text{v}$

$V_{CE} = 4.12\text{v}$

$V_{BC} = -3.45\text{v}$

$I_A = 1.03\text{mA}$

$I_B = 6.7\mu\text{A}$

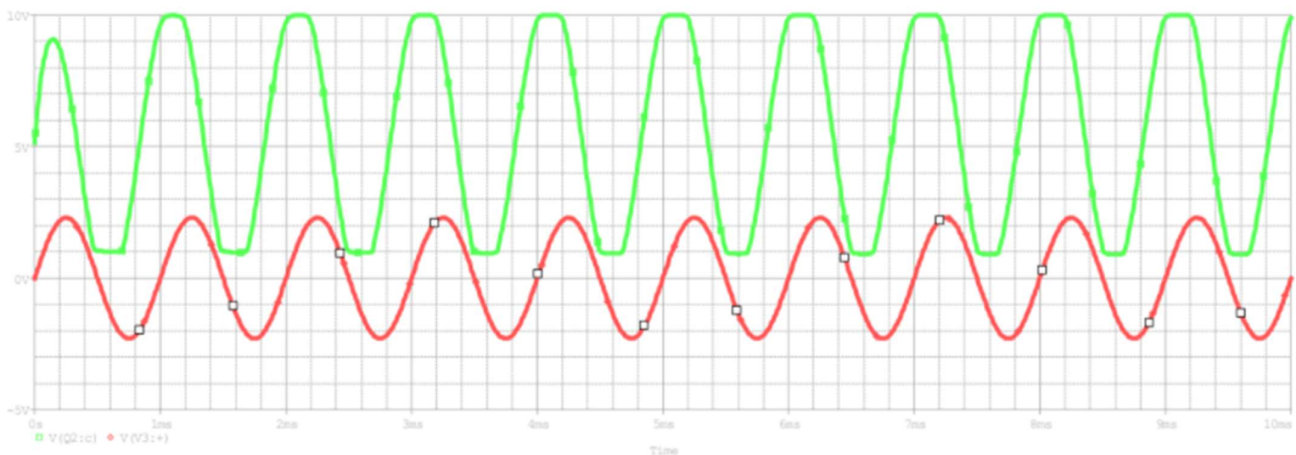

Output voltage vs input voltage

Figure (4-3) – wave 1

→ The voltage gain: $A_v = V_o / V_{in} = 1 / 2.3 = 0.435$

The AC voltage across the 10k resistor was measured:

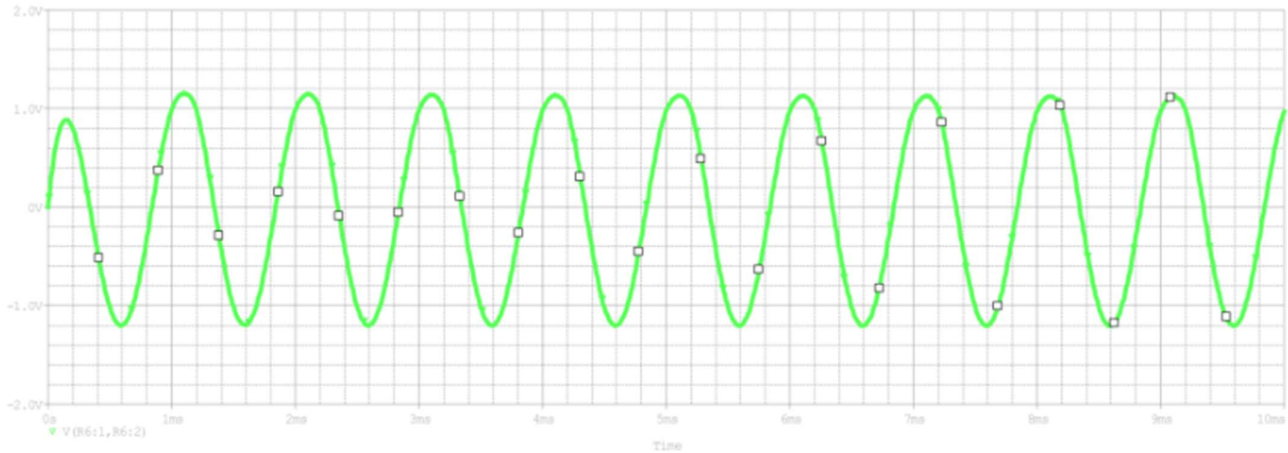


Figure (4 -2)-wave 2
Voltage across 10k

- The input current: $I_{in} = V_{in} / R = 2.3/10k = 0.23mA$
- The output current: $I_{out} = V_o / R = 1/4.7k = 0.21mA$
- Current gain: $A_i = I_{out} / I_{in} = 0.91$
- The input impedance: $Z_i = V_i / I_{in} = 2.3/0.23m = 10k\Omega$
- The output impedance $= V_o / I_o = 4.8k\Omega$

Quantity	Measured Values
V_{in}	1v
V_{out}	2.3v
I_{in}	0.23mA
I_{out}	0.21mA
	Calculated Values
$A_v = V_{out}/V_{in}$	0.435
$A_i = I_{out} / I_{in}$	0.91
$Z_{in} = V_{in} / I_{in}$	10k
Z_{out}	4.8k

Conclusion:

As mentioned before, the common emitter is supposed to make the output signal bigger than the input signal, which was proven by finding the voltage and current gain (both were larger than 1), and the input and output impedances were as supposed large.

In the common collector, the current gain was larger than 1, while the voltage gain was less than 1, and the output impedance was very small compared with the input impedance.

In the common base, we were expecting a voltage gain higher than 1, but the opposite is what happened because of the 10k resistor, while the current gain was very small and the input & output impedances were large.

The Data calculated and measure in this report matches the data in the pre-lab that we handed week ago.

References:

1. <https://www.electrical4u.com/bipolar-junction-transistor-or-bjt-n-p-n-or-p-n-p-transistor/>
2. Electronics Lab ENEE3102 Lab Manual
3. Microelectronic_Circuits_6th_Edition