
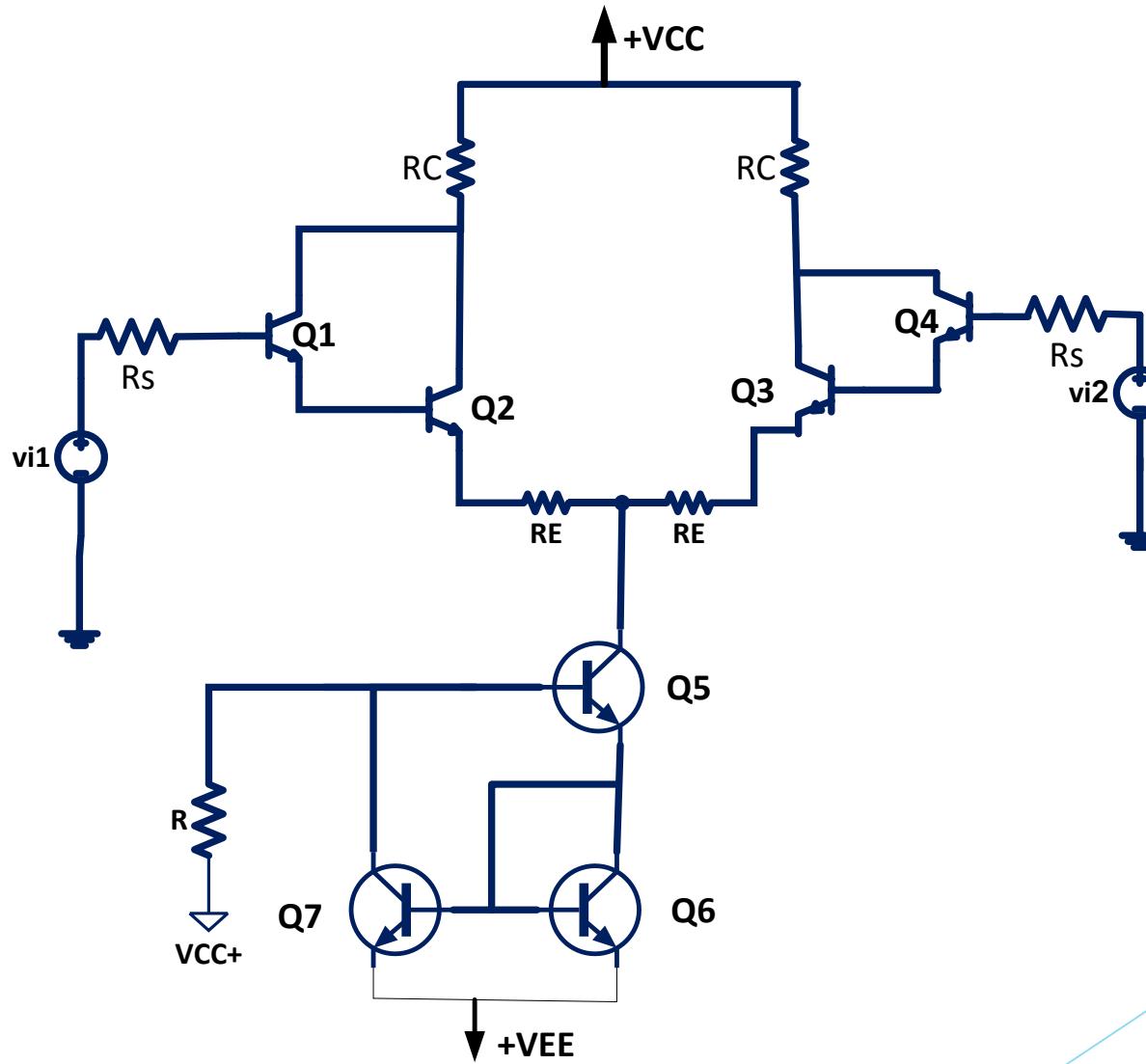


Differential Amplifiers

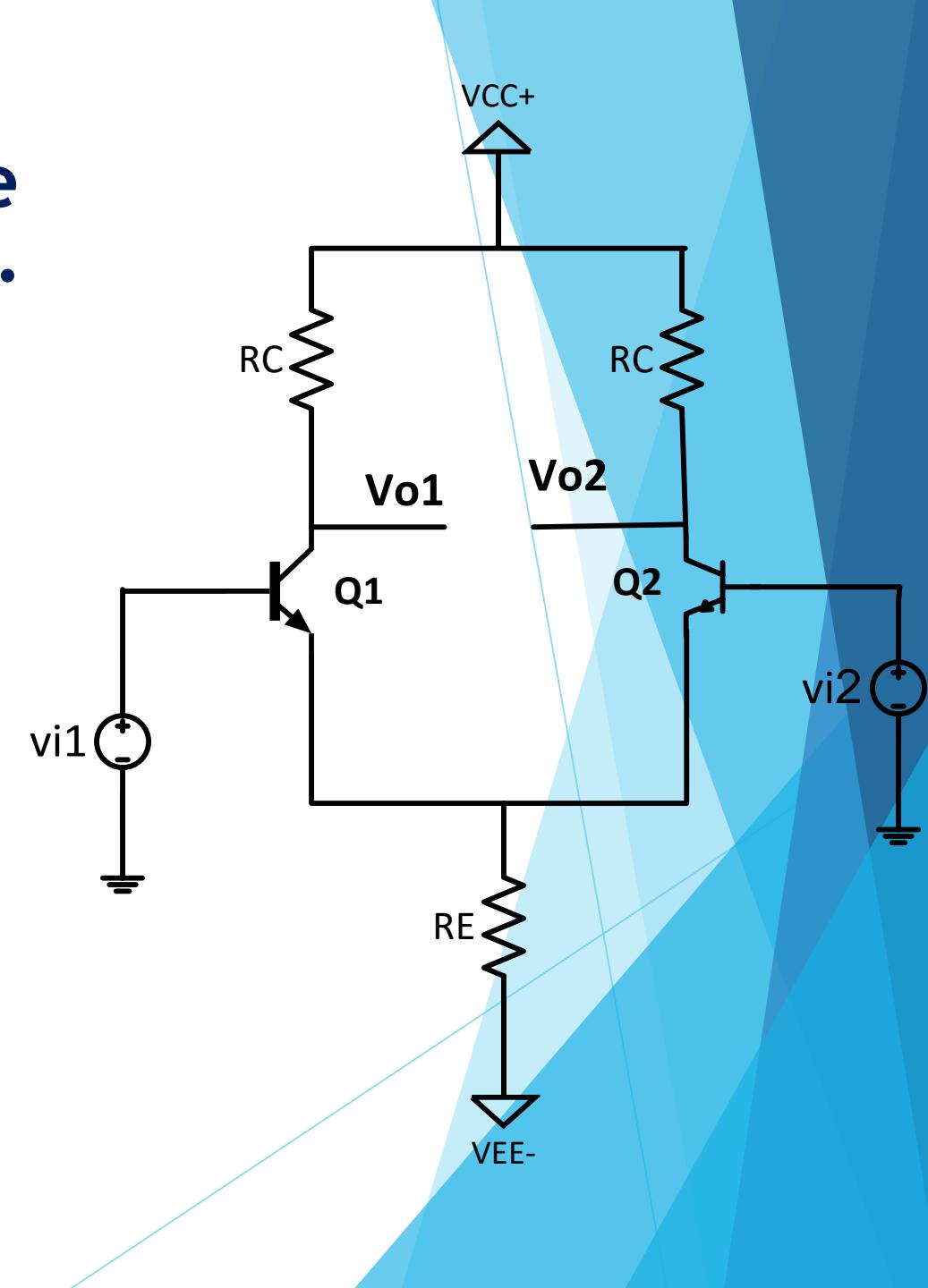

Differential Amplifiers

- ▶ Designed to amplify the difference between two input signal voltages.
- ▶ Found in many electronic circuits, including low and high frequency amplifiers.
- ▶ Almost always used as the input stage inside an IC operational amplifier to provide :
 - Large input impedance .
 - Rejection of the noise .



Differential Amplifiers

Simple Differential Amplifier

DC Analysis:

$$V_{B1} = V_{B2} = 0 \quad \text{since } v_{i1} = v_{i2} = 0$$

$$V_{E1} = V_{E2} = -0.7 \text{ v}$$


$$I = \frac{-0.7 + V_{EE}}{R_E}$$

$$I_{E1} = I_{E2} = \frac{1}{2} I$$

symmetry

Q1 & Q2 are identical.

$$\therefore \beta_1 = \beta_2$$

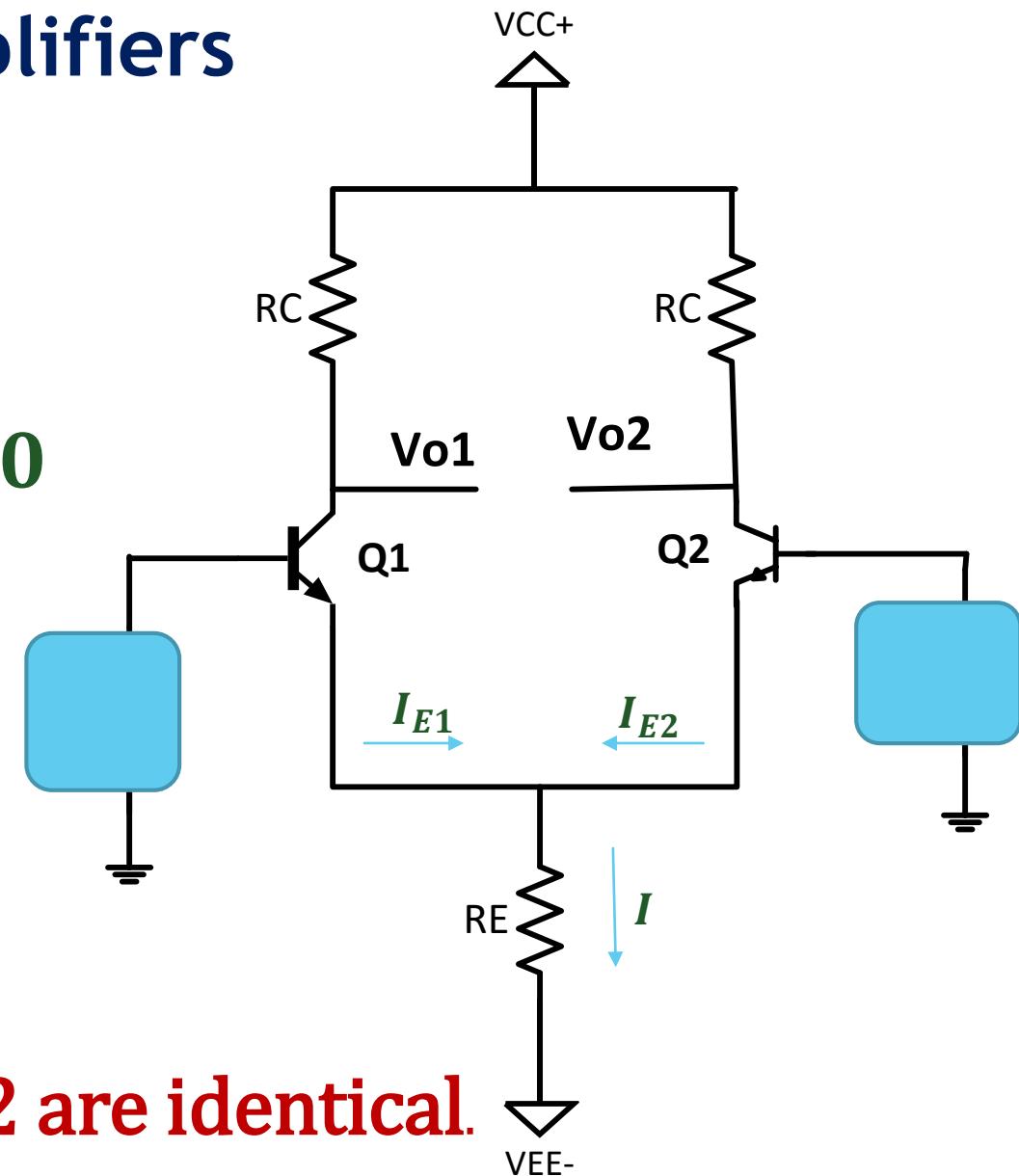

Differential Amplifiers

Simple Differential Amplifier

Ac small Signal Analysis:

Calculate and sketch $V_o1(t)$ and $V_o2(t)$ if
 $V_{i1}(t) = V_{i2}(t) = 100\text{mV}$ Peak sinusoidal


assuming

$$\beta_1 = \beta_2$$

and



$$\frac{v_{c1}}{v_{be1}} = \frac{v_{c2}}{v_{be2}} = -100$$
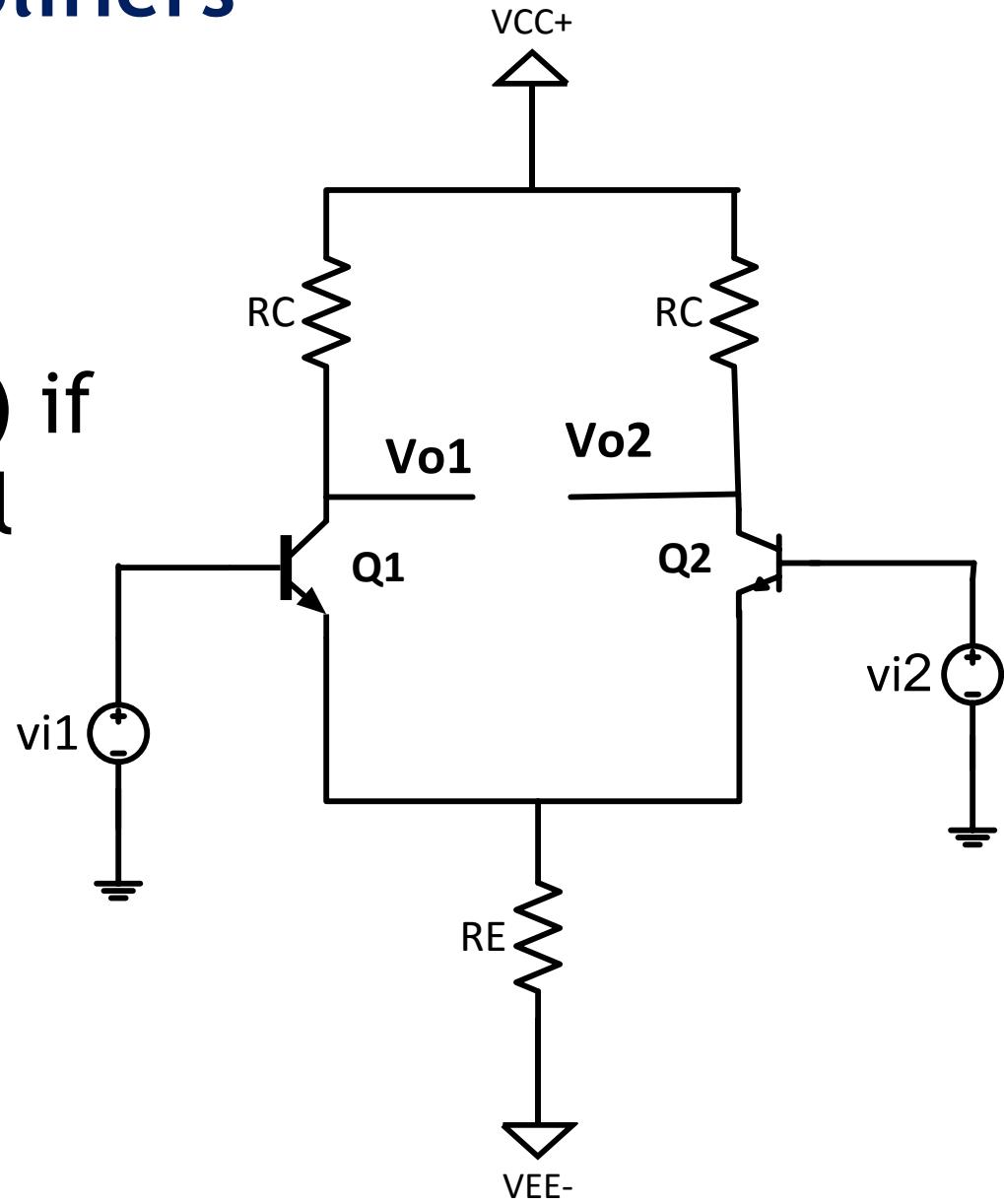
$$\frac{v_{o1}}{v_{be1}} = \frac{v_{o2}}{v_{be2}} = -100$$




Using superposition

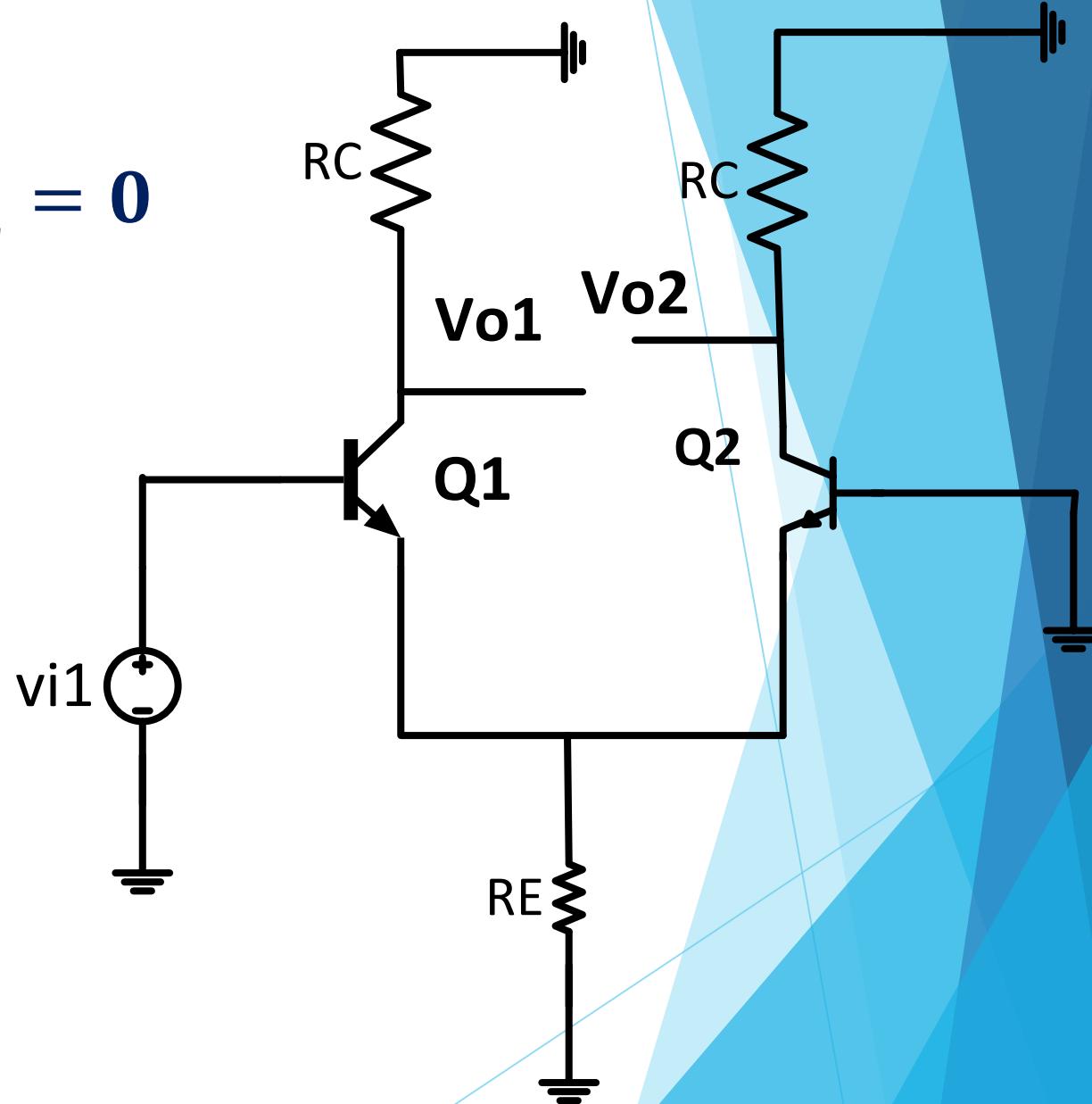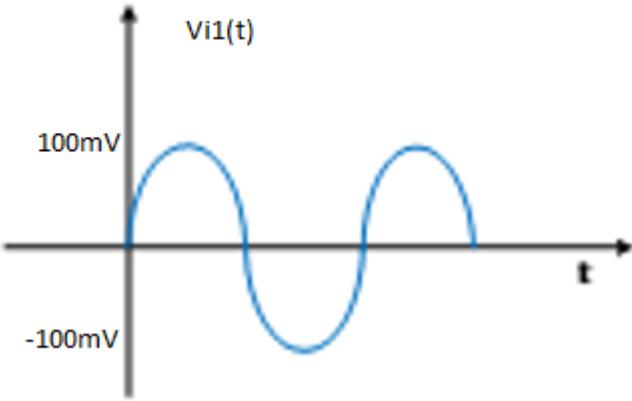1) let $v_{i1} = 100 \text{ mV peak}$, $v_{i2} = 0$



Simple Differential Amplifier

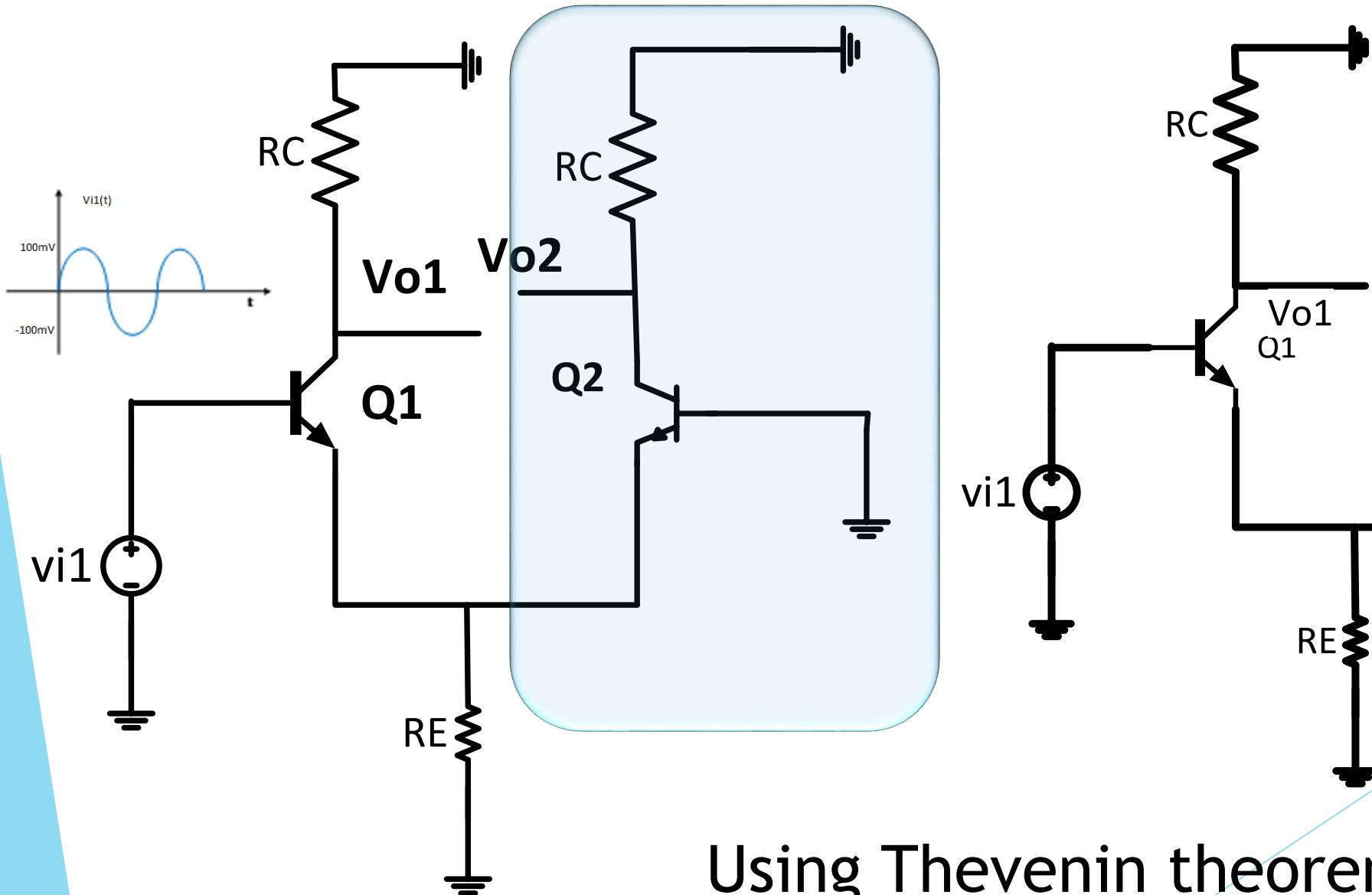
1) let $v_{i1} = 100 \text{ mV peak}$, $v_{i2} = 0$



$$\frac{h_{ie2}}{h_{fe+1}} = h_{ib2}$$


Using Thevenin theorem

Differential Amplifiers

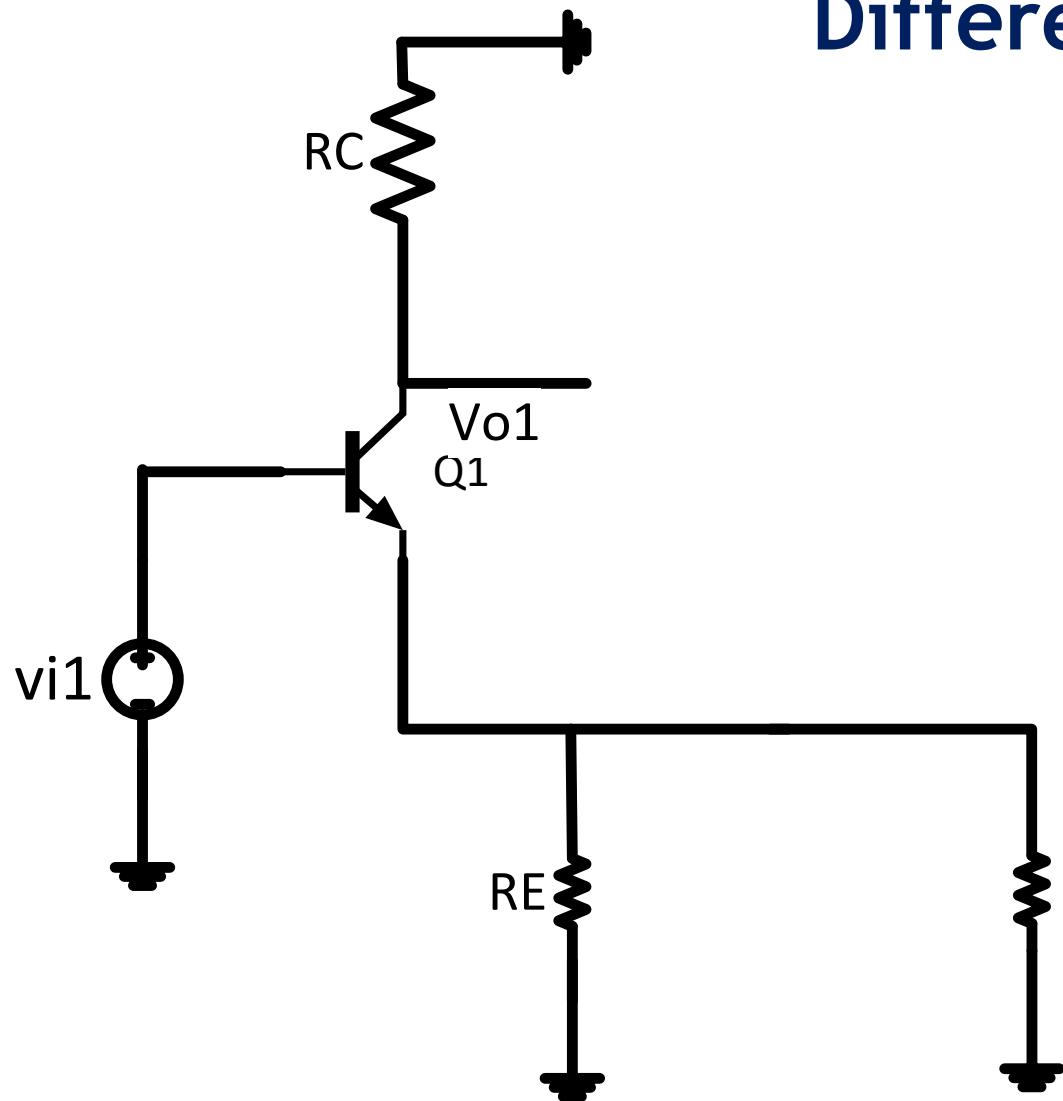


if $R_E \gg h_{ib2}$
 $\therefore R_E \parallel h_{ib2} \approx h_{ib2}$

$$\frac{h_{ie2}}{h_{fe+1}} = h_{ib2}$$

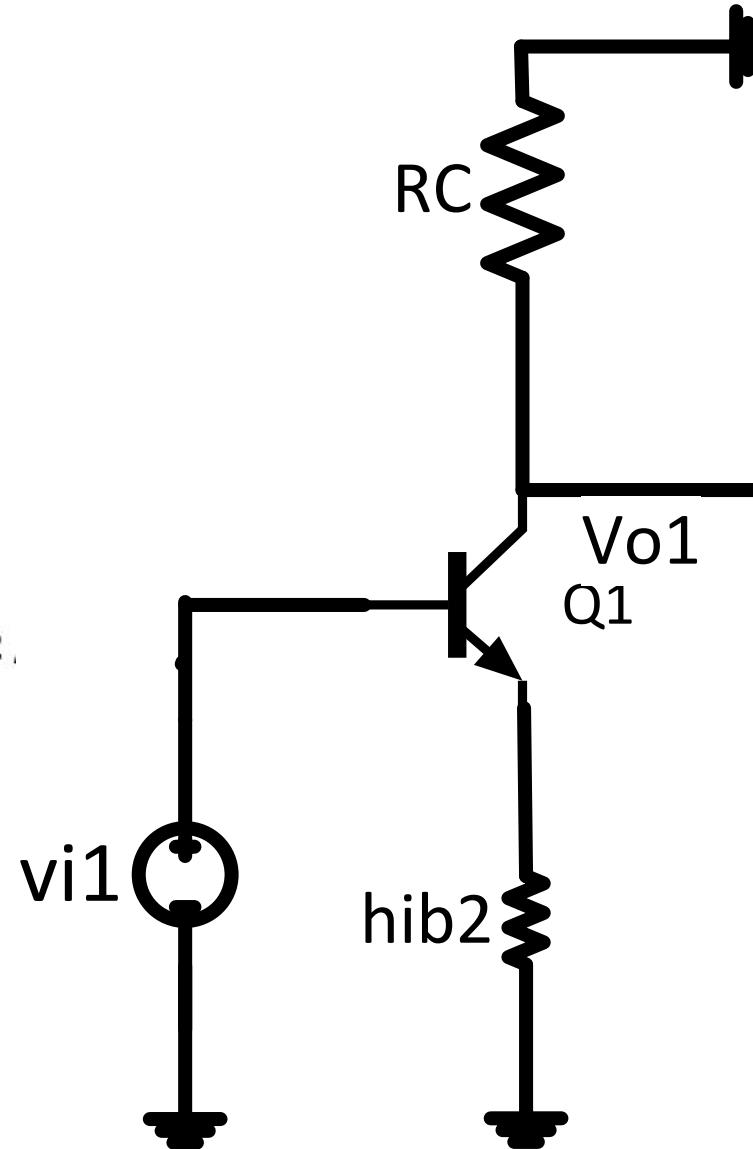


$$\frac{v_{o1}}{v_{be1}} = \frac{v_{o2}}{v_{be2}} = -100$$

Ac small signal equivalent circuit

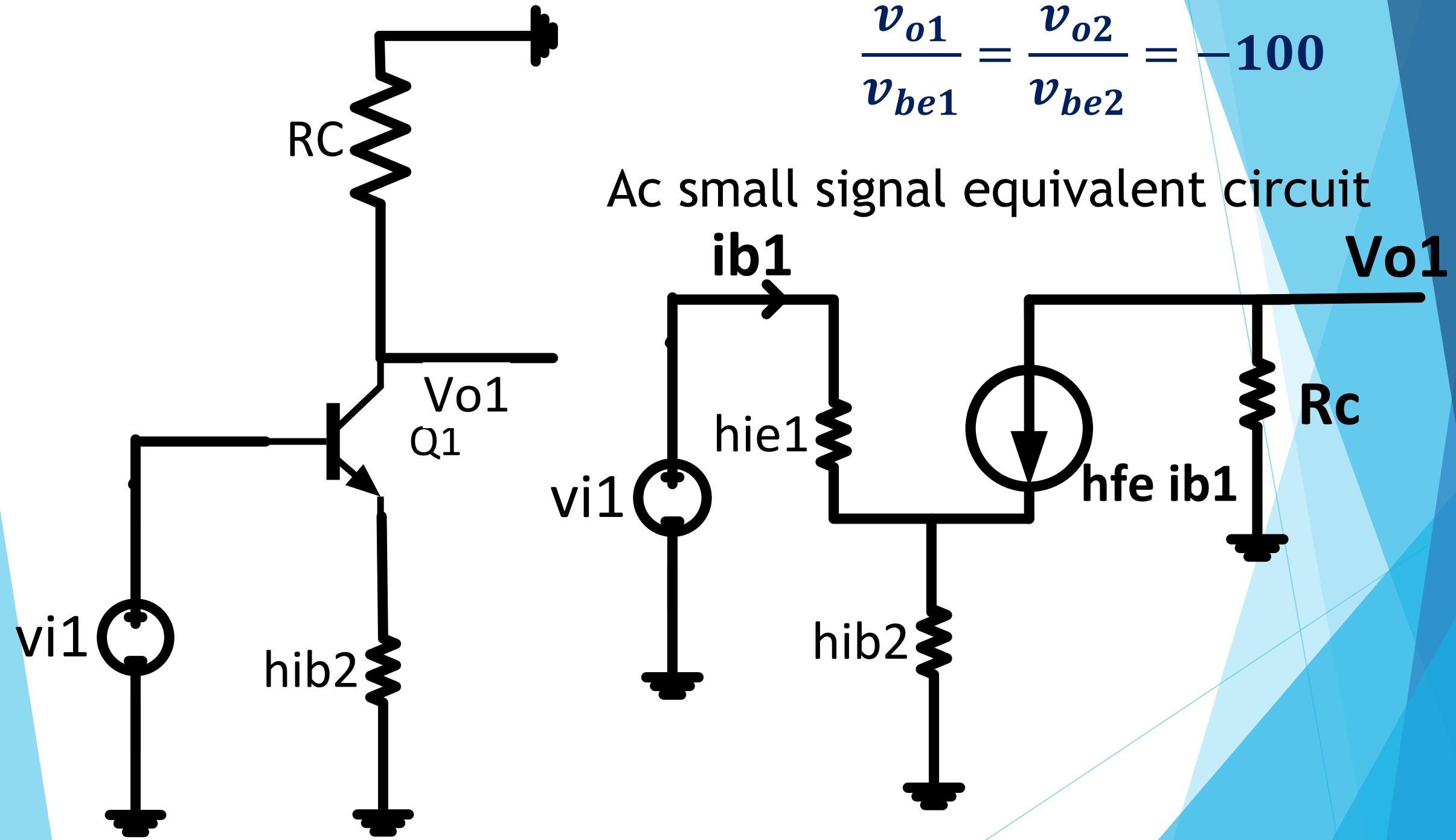

Differential Amplifiers


Simple Differential Amplifier

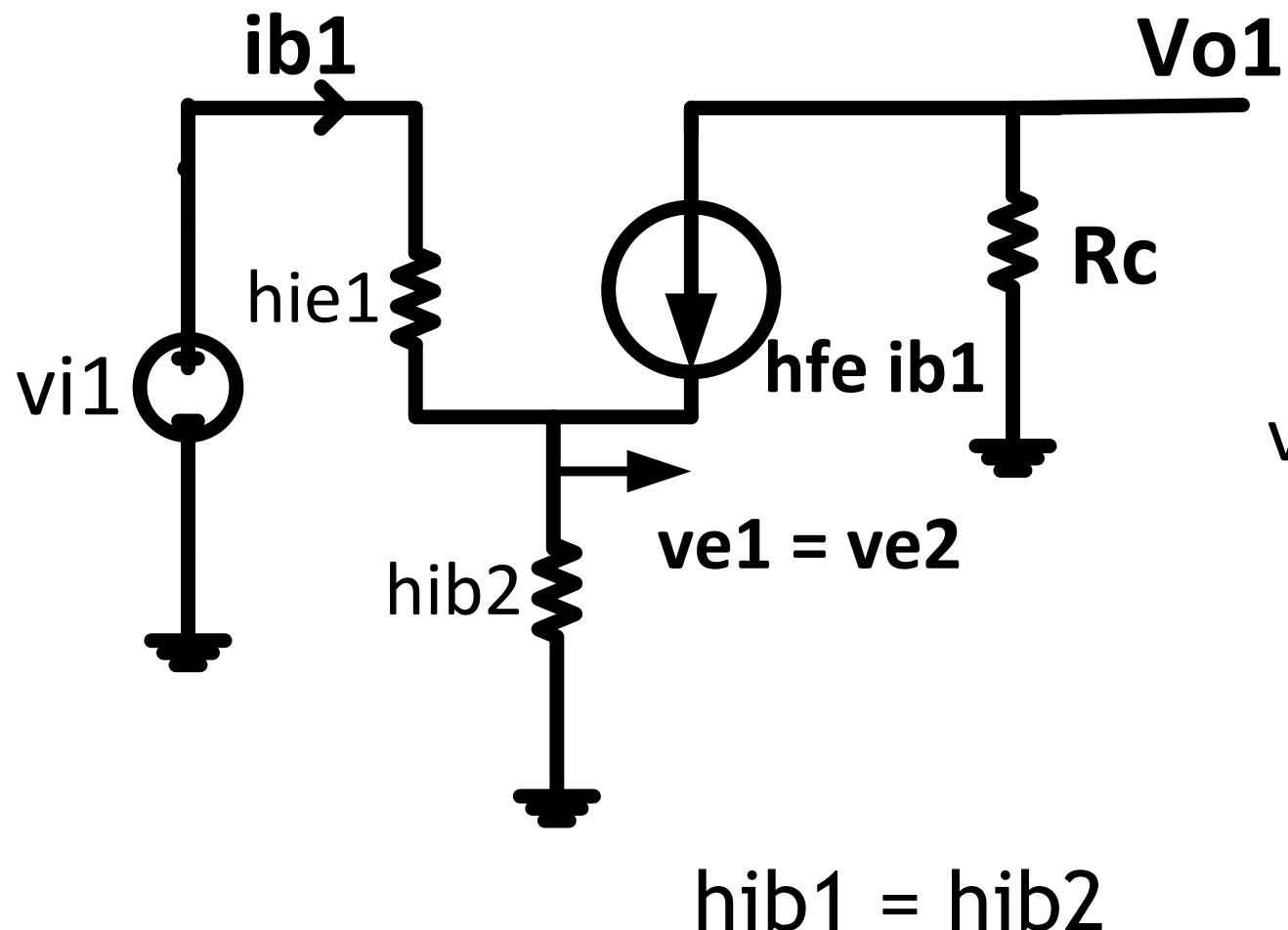

To find $v_{e1} = v_{e2}$



Emitter equivalent circuit

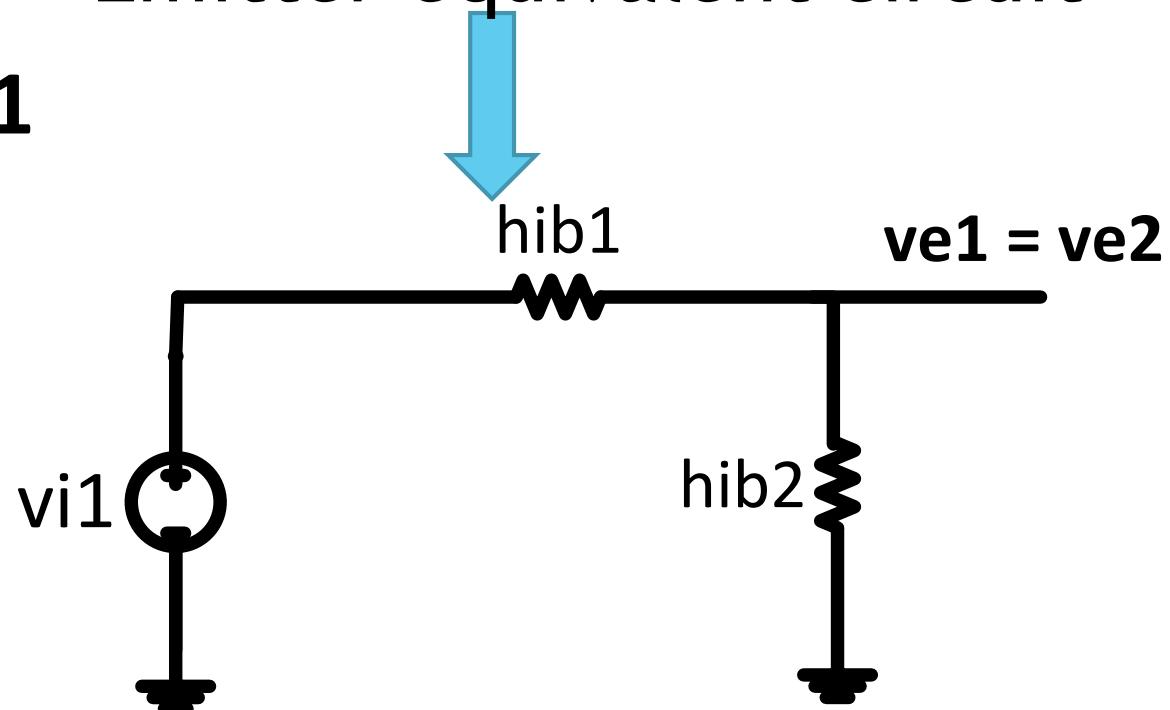

$$v_{e1} = \frac{1}{2} v_{i1} = 50 \text{ mV peak}$$

Differential Amplifiers

AC Small Signal Analysis:

$$v_{e1} = v_{e2} = \frac{1}{2} v_{i1} = 50 \text{ mV peak}$$

$$v_{be1} = v_{b1} - v_{e1}$$


$$v_{be1} = 100 \text{ mV peak} - 50 \text{ mV peak}$$

$$v_{be1} = 50 \text{ mV peak}$$


$$\therefore v_{c1} = v_{o1} = (-100)(50 \text{ mV peak})$$

$$\therefore v_{c1} = -5 \text{ V peak}$$

$$v_{o1} = -5 \text{ V peak}$$

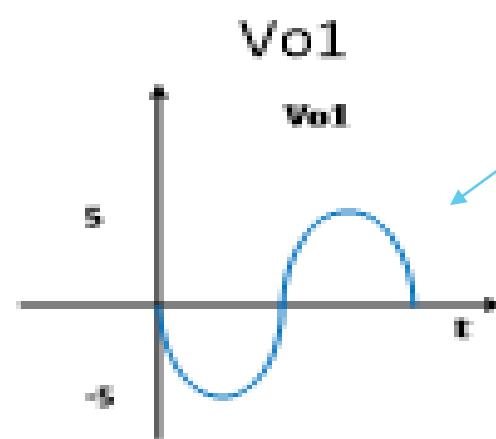

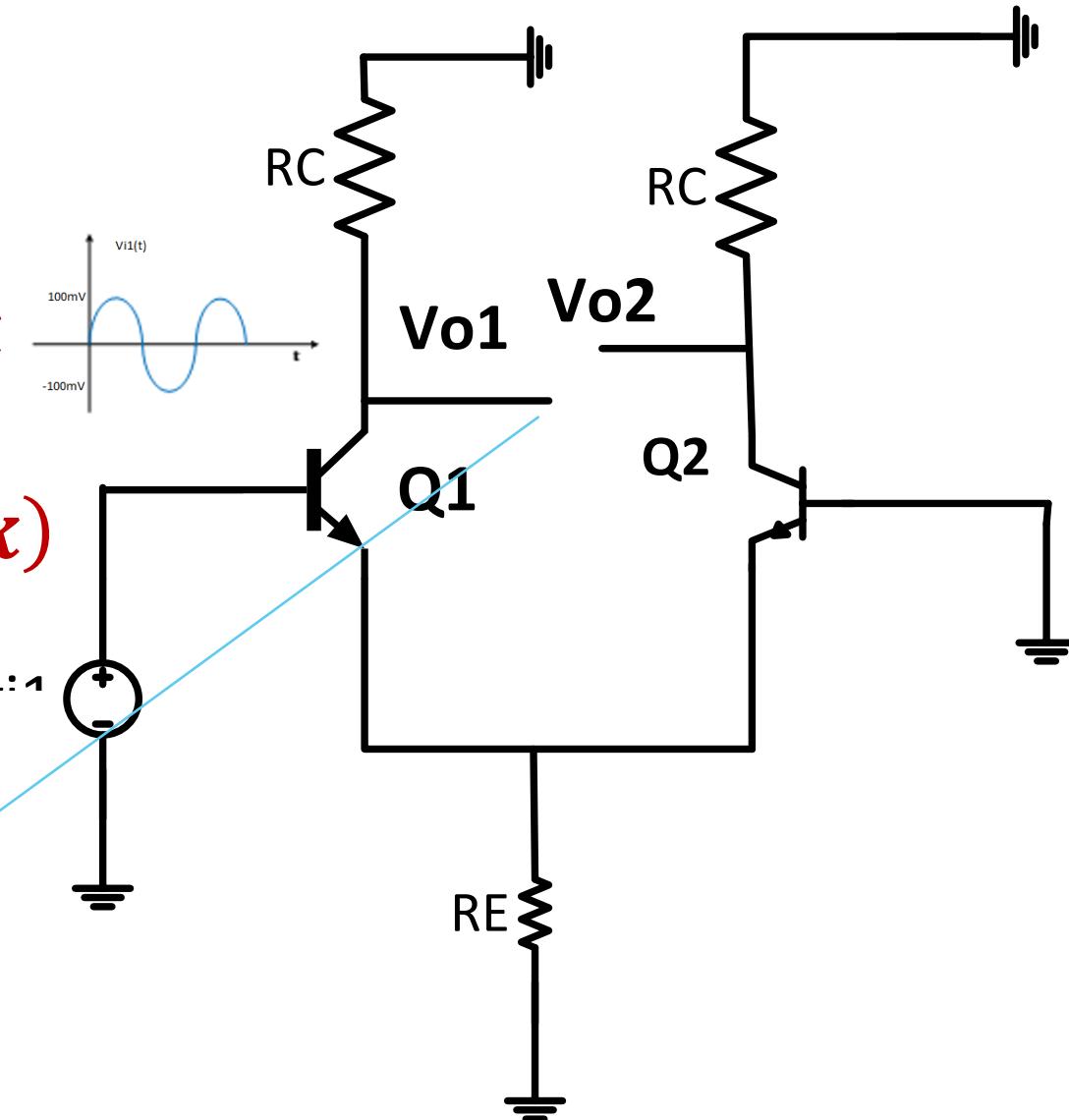
$$\frac{v_{o1}}{v_{be1}} = \frac{v_{o2}}{v_{be2}} = -100$$



$$\frac{v_{o2}}{v_{be2}} = -100$$

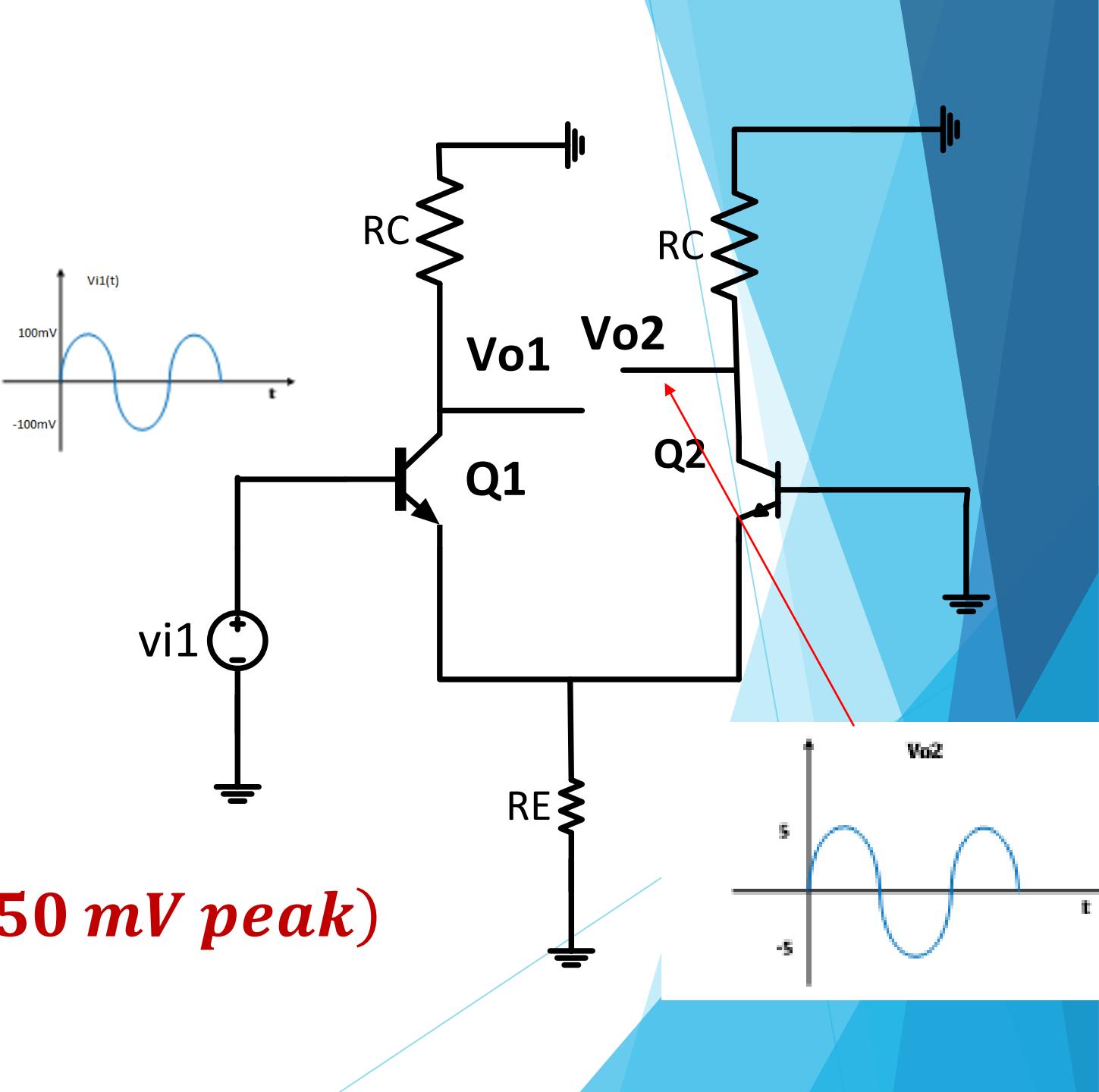- to find $v_{c2} = v_{o2}$,
- we need to find v_{be2}
- $v_{be2} = v_{b2} - v_{e2}$
- $= v_{b2} - v_{e2}$
- $v_{be2} = 0 - 50 \text{ mV peak}$
- $v_{be2} = -50 \text{ mV peak}$
- ∴ $v_{o2} = v_{c2} = (-100)(-50 \text{ mV peak})$
- $v_{o2} = +5 \text{ V peak}$




Differential Amplifiers

Simple Differential Amplifier

AC Small Signal Analysis:

$$v_{o1} = -5 \text{ V peak}$$

$$v_{o2} = +5 \text{ V peak}$$

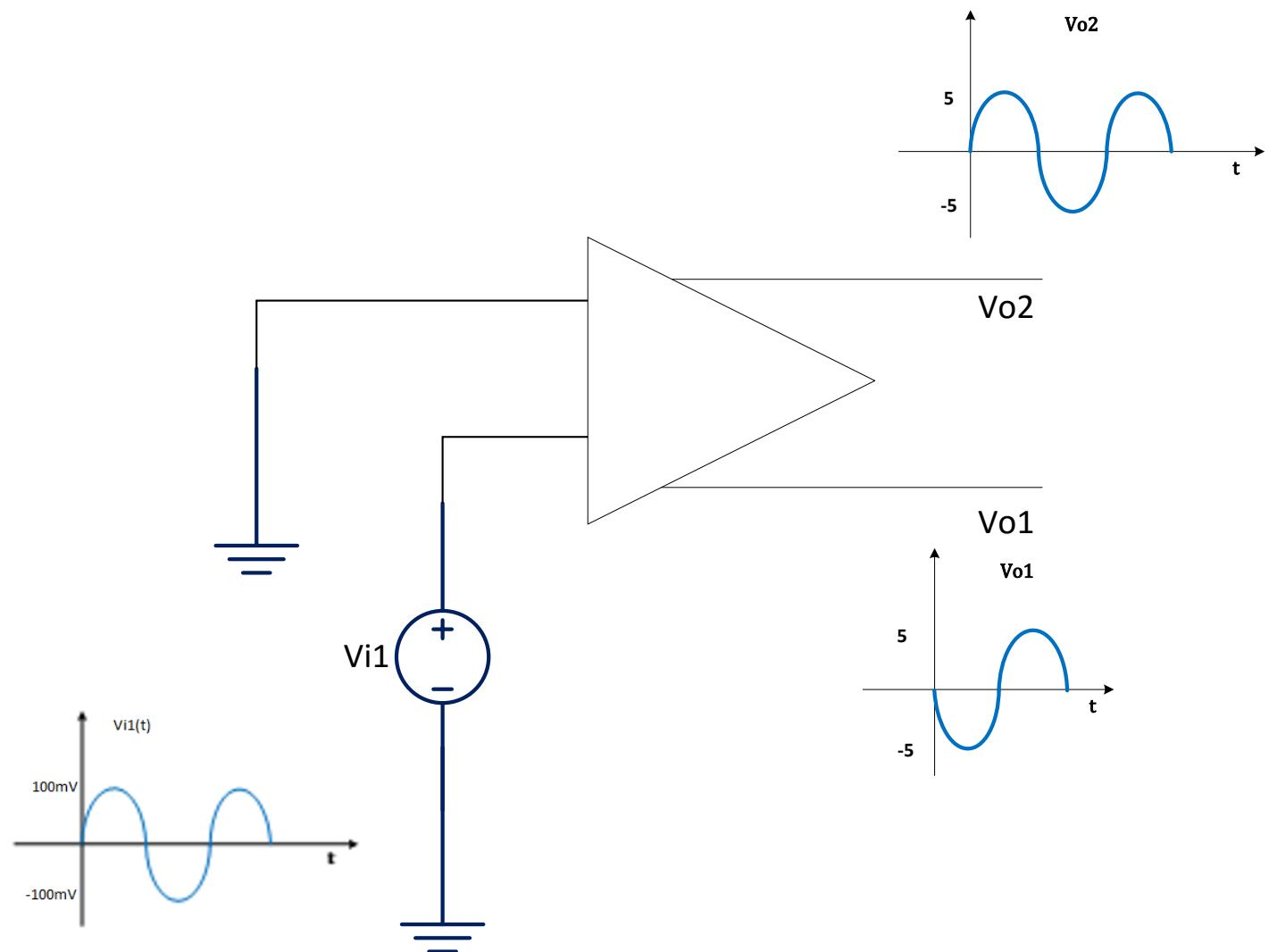

Differential Amplifiers

AC Small Signal Analysis:


Using same steps for

$$v_{i2} = 100 \text{ mV peak}$$

$$v_{i1} = 0$$

$$v_{o1} = +5 \text{ V peak}$$

$$v_{o2} = -5 \text{ V peak}$$

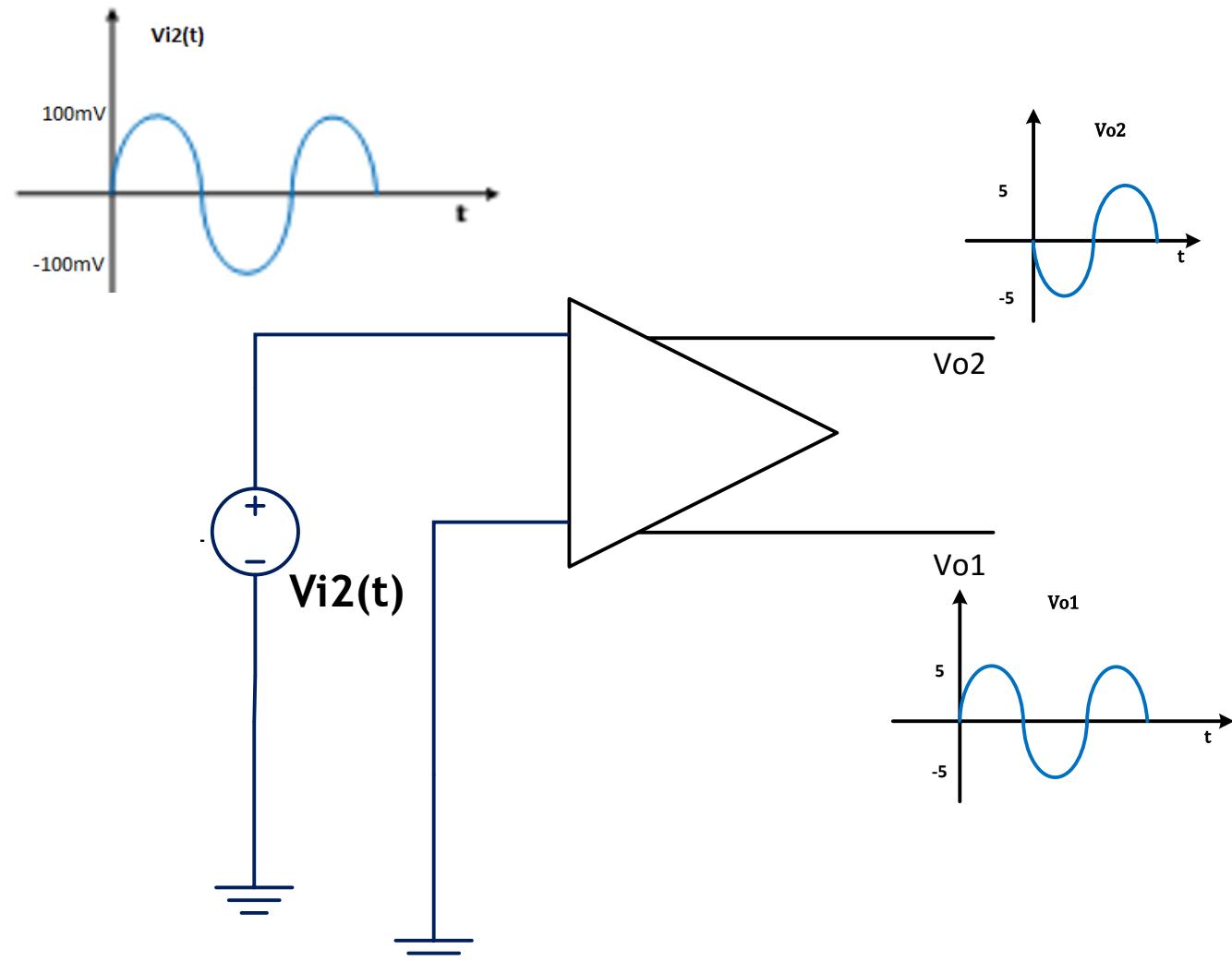

Differential Amplifiers








Simple Differential Amplifier

AC Small Signal Analysis:

now if $v_{i1} = v_{i2} = 100 \text{ mV peak}$

$$v_{o1} = 0$$

$$v_{o2} = 0$$

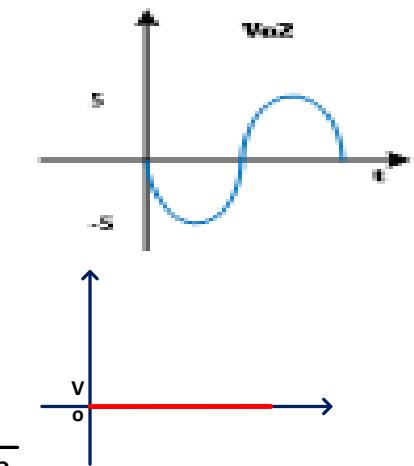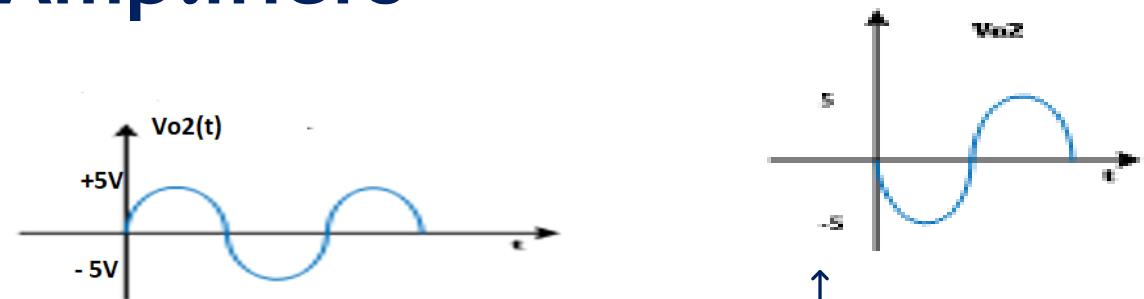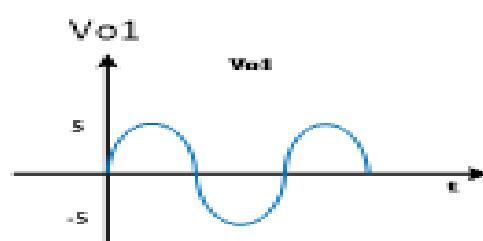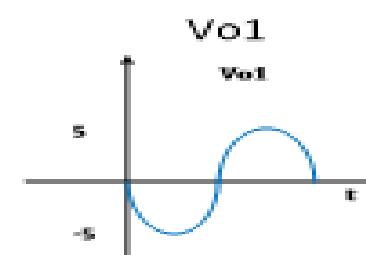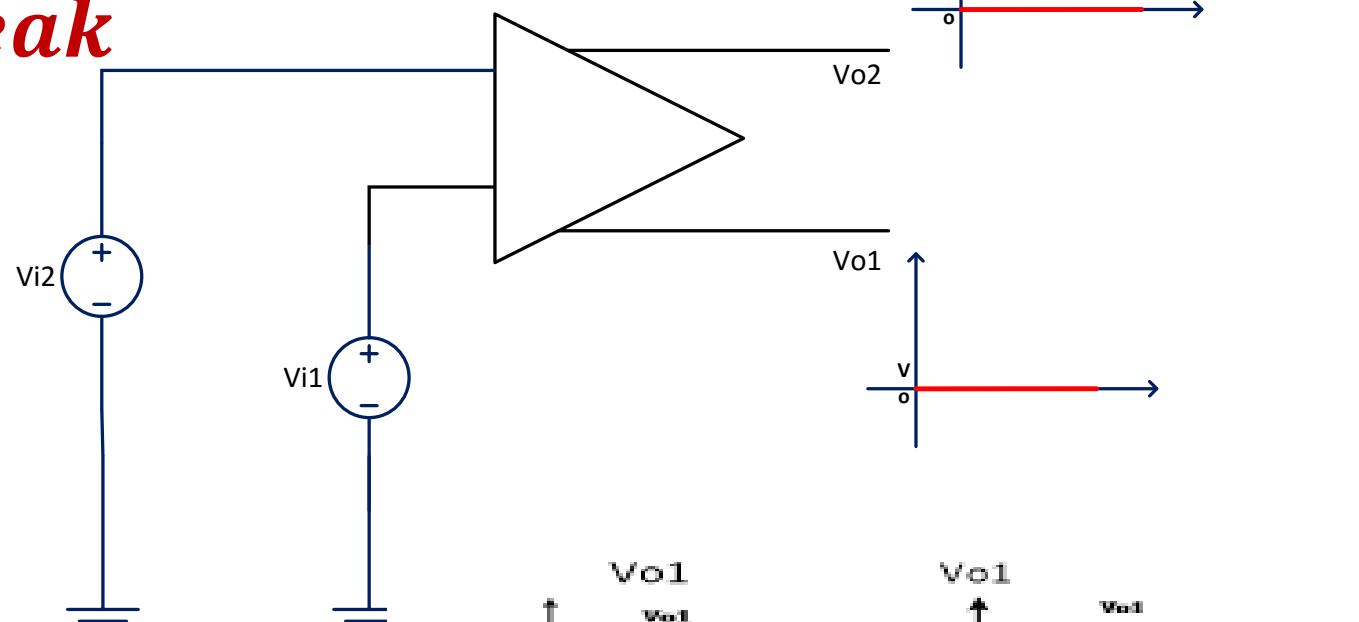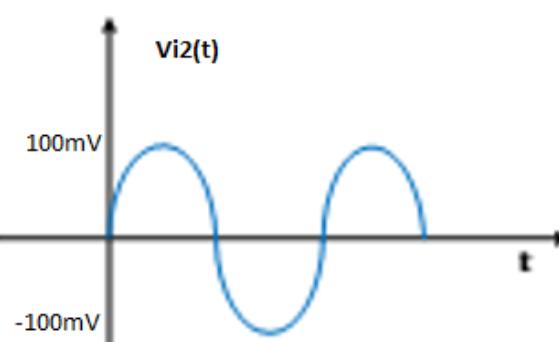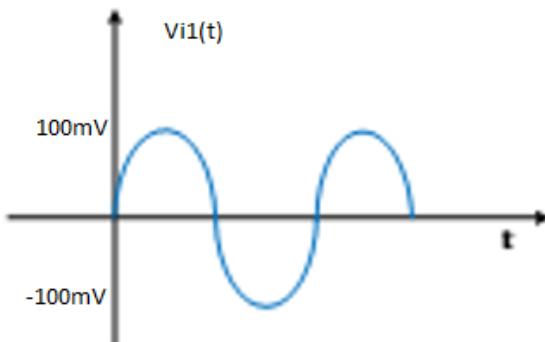

Differential Amplifiers

Simple Differential Amplifier

AC Small Signal Analysis:




Using same steps for

$$v_{i1} = 100 \text{ mV peak}$$

$$v_{i2} = -100 \text{ mV peak}$$

$$v_{o2} = +10 \text{ V peak}$$

$$v_{o1} = -10 \text{ V peak}$$

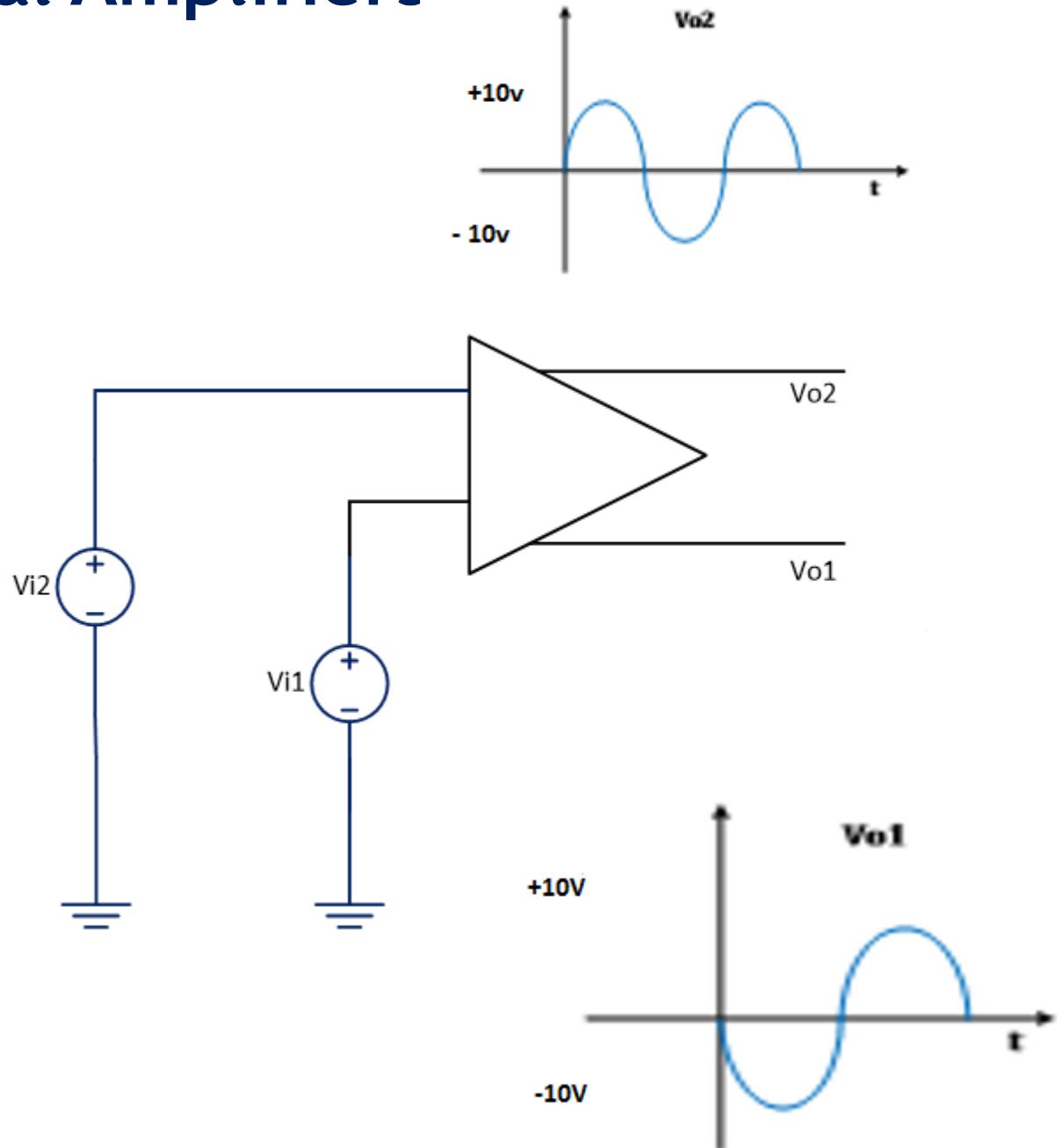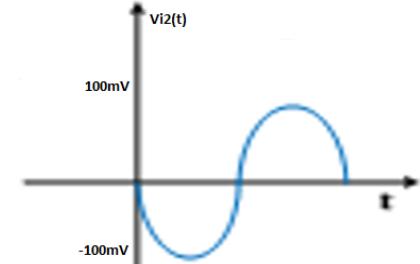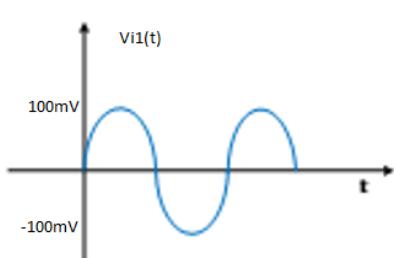

Differential Amplifier Circuit: Common Mode & Differential mode Signal

Since the differential amplifier is most often used to amplify the difference between two input signals.

$$\text{let } v_d = v_{i2} - v_{i1}$$

$v_d \equiv$ Differential mode input signal

$$\text{let } v_c = \frac{v_{i2} + v_{i1}}{2}$$

$v_c \equiv$ Common mode input signal

$$\therefore v_{i2} = v_c + \frac{v_d}{2}$$

$$v_{i1} = v_c - \frac{v_d}{2}$$

Differential Amplifiers

Differential Amplifier Circuit:

Common Mode & Differential mode Signal

Input voltage can be represented in terms of a common mode and differential mode input signals.

In the usual application of the differential amplifier , the differential mode input is desired and to be amplified , while the common mode input is to be rejected.

Differential Amplifier Circuit:

DC Analysis: $\rightarrow v_{i1} = v_{i2} = 0$


$$R_S I_{B1} + V_{BE1} + R_E I - 12 = 0$$

$$I = I_{E1} + I_{E2}$$

$$I_{E1} = I_{E2} \text{ [symmetry]}$$

$$\begin{aligned} I_{E1} &= I_{E2} = \frac{12 - 0.7}{\frac{1k}{41} + (2)(20k)} \\ &= 0.2825 \text{ mA} \end{aligned}$$

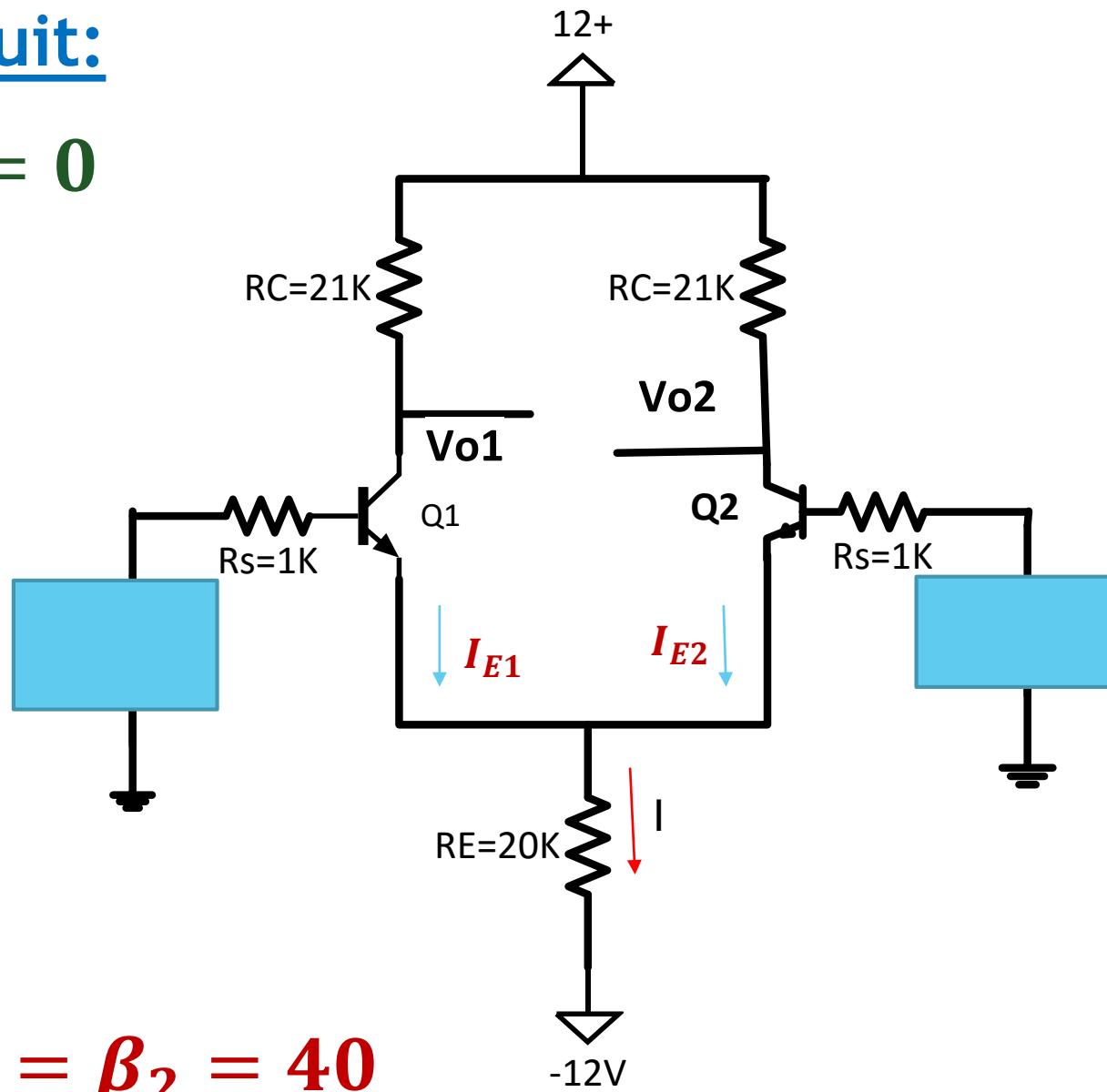$\beta_1 = \beta_2 = 40$
 Q_1 and Q_2 identical



Differential Amplifiers


Differential Amplifier Circuit:

AC Analysis:


since $I_{E1} = I_{E2}$ and $\beta_1 = \beta_2$

$$h_{ie1} = h_{ie2} = h_{ie}$$

$$h_{ib1} = h_{ib2} = h_{ib}$$

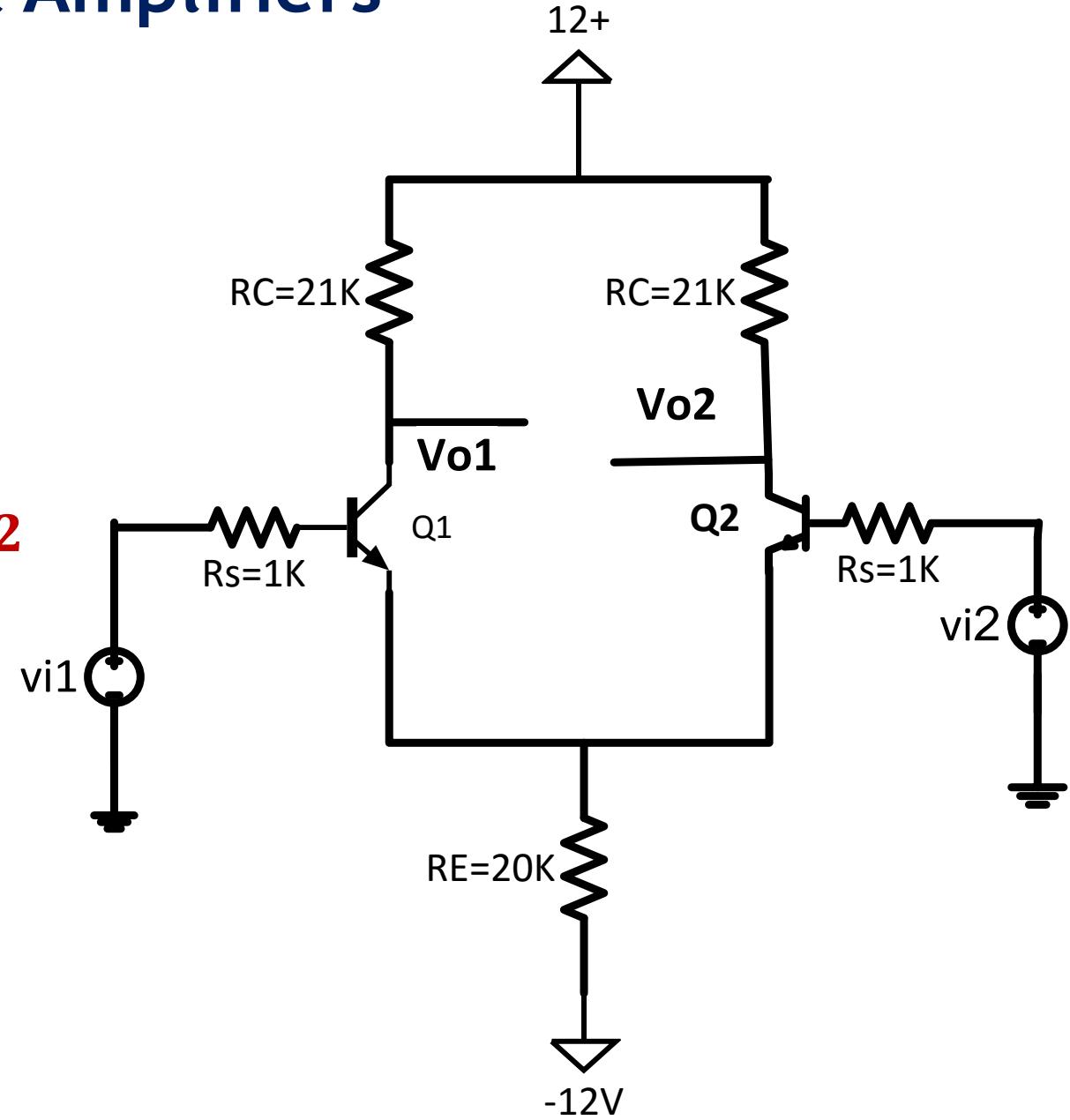


Ac small signal equivalent circuit

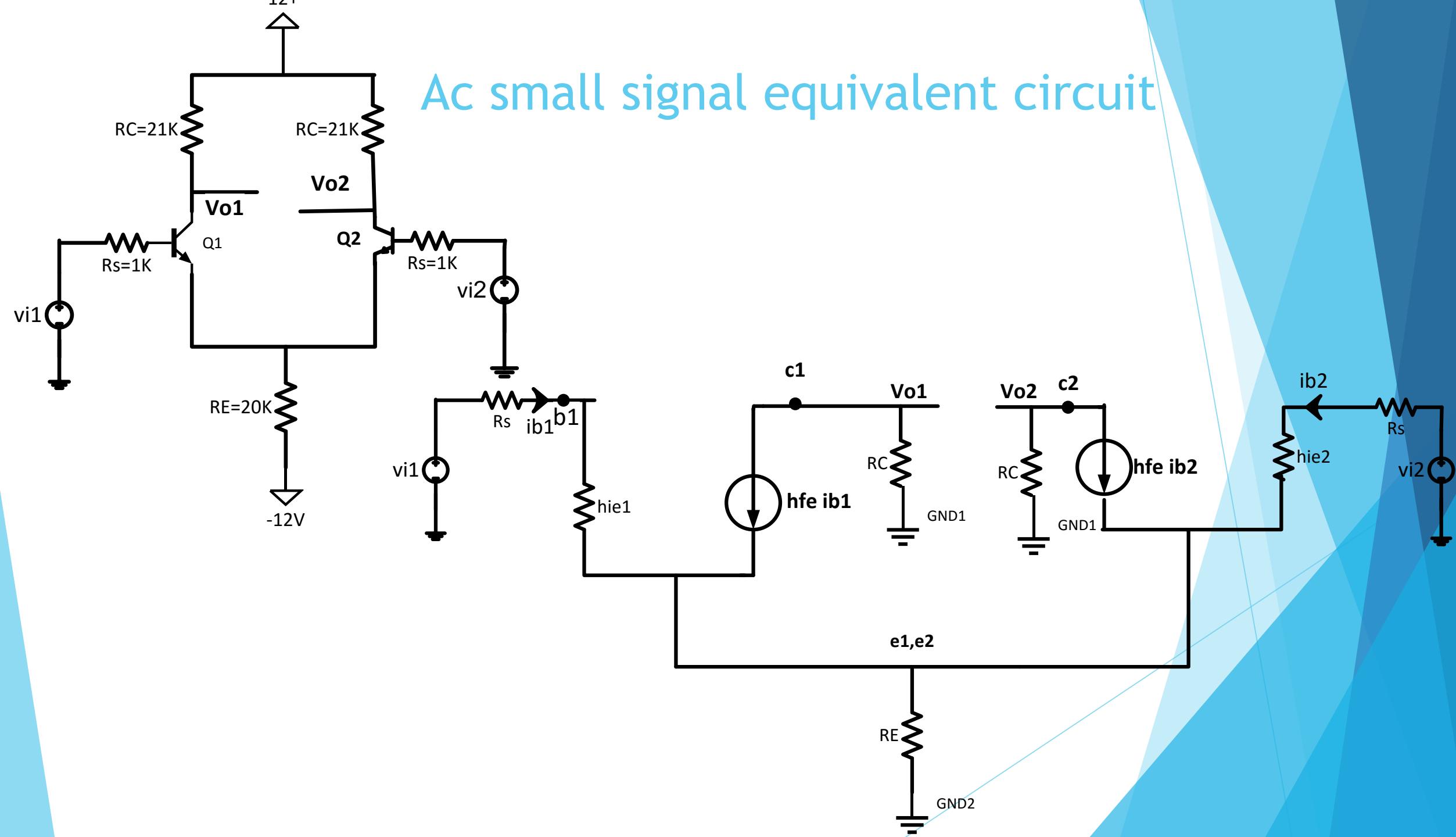

Differential Amplifiers

Differential Amplifier Circuit:


AC Analysis:

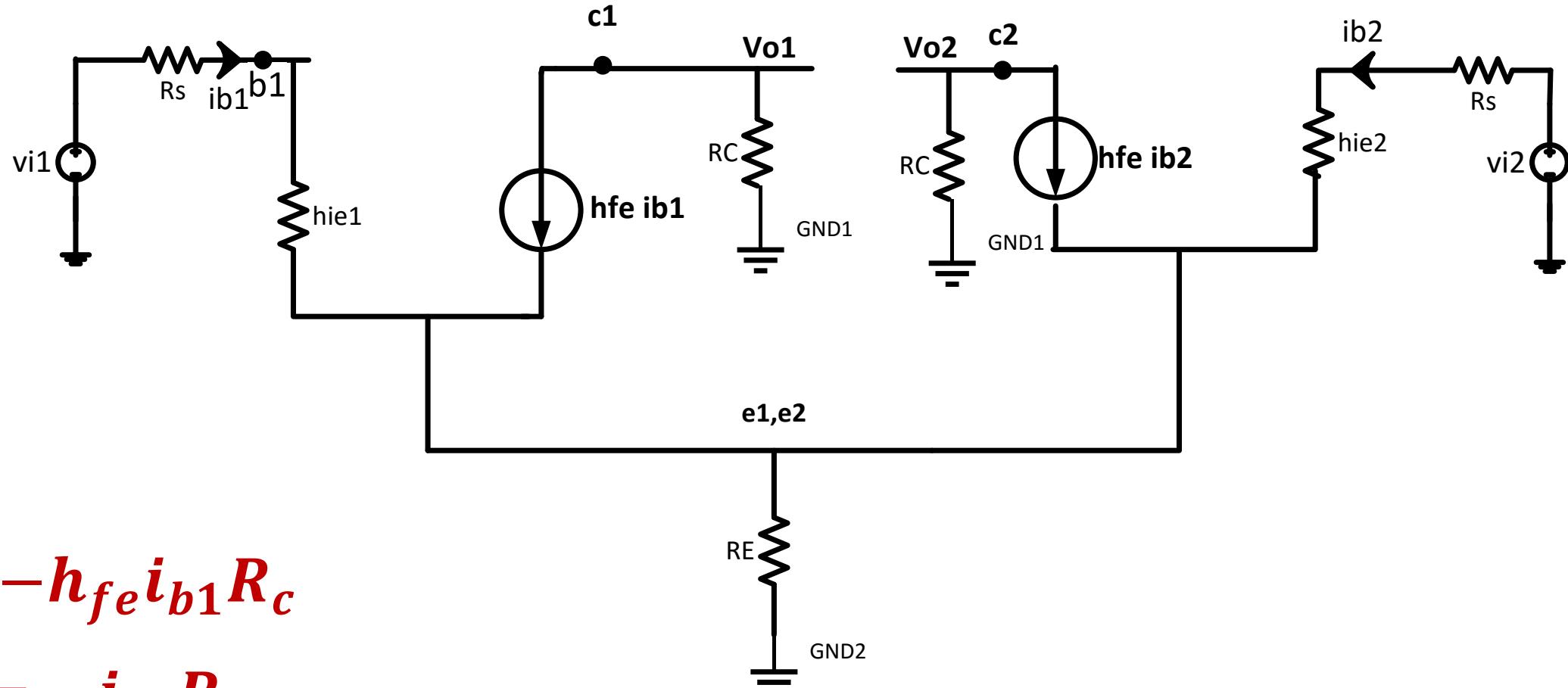

$$v_{o1} = -h_{fe} i_{b1} R_c$$

$$v_{o1} = -i_{c1} R_c$$


$$v_{o1} \approx -i_{e1} R_c$$

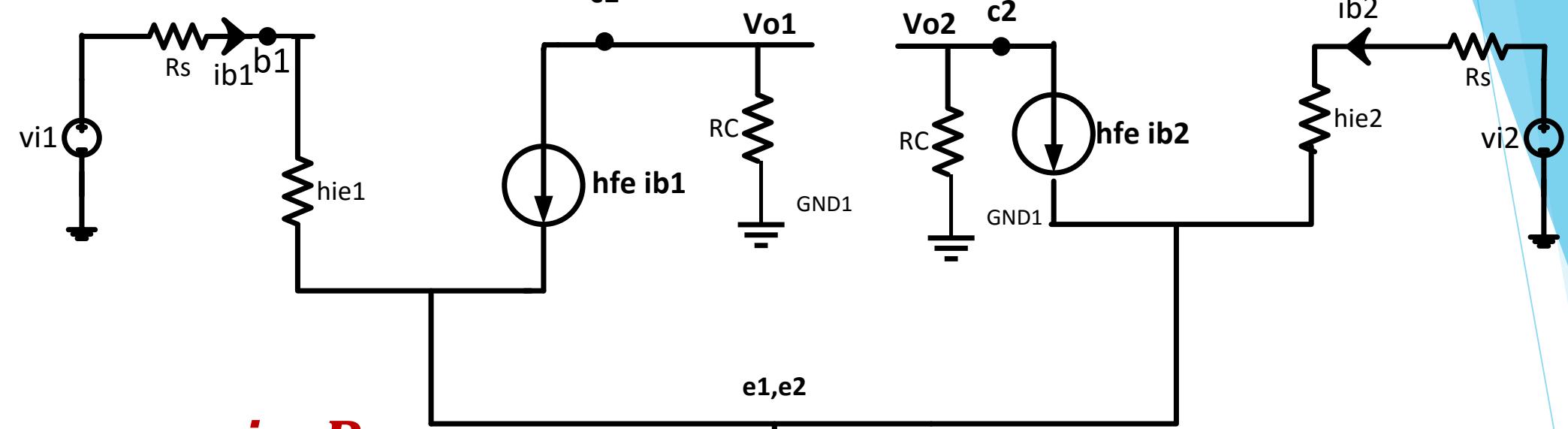

$$v_{o1} \approx -i_{e1} R_c$$

To find i_{e1}

Emitter equivalent circuit

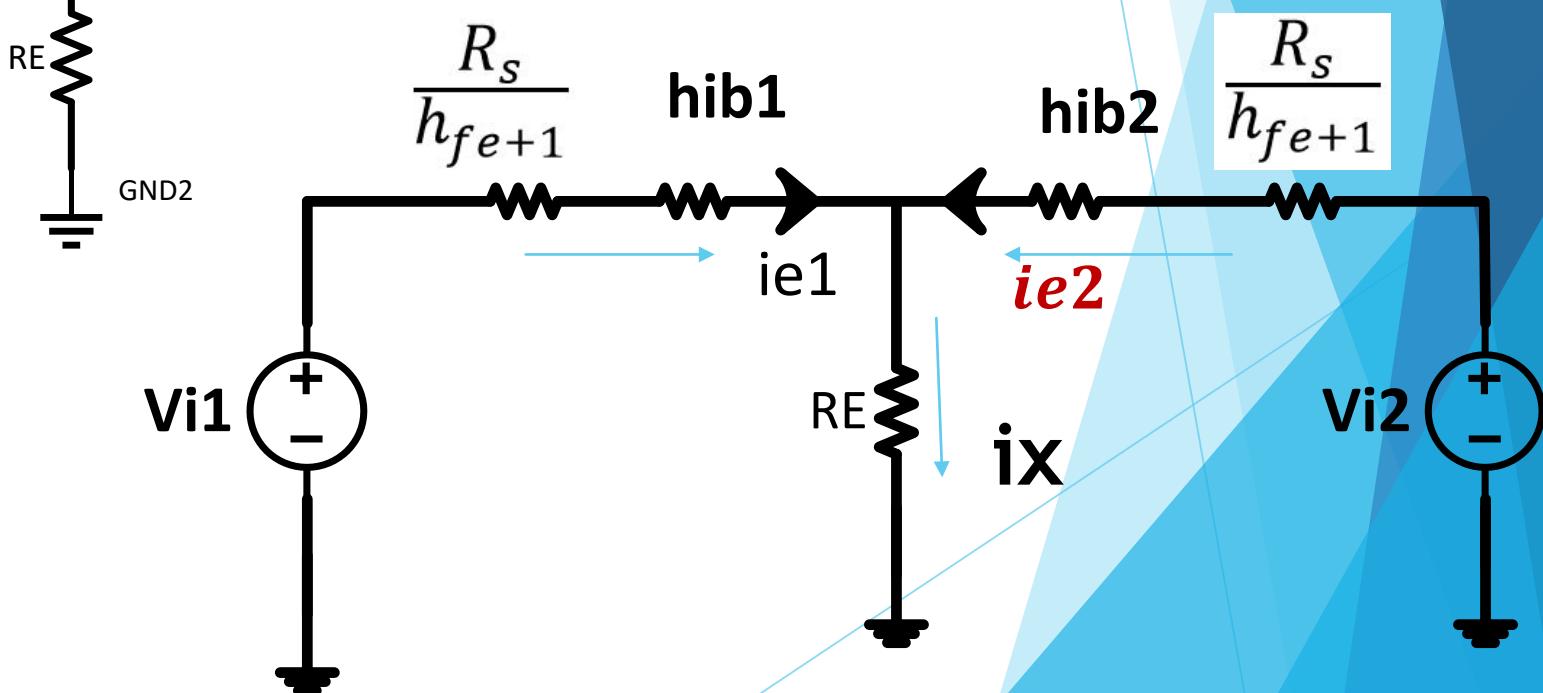

Differential Amplifiers

Differential Amplifier Circuit:

To find $ie1$ 


Small Signal Analysis

$$v_{i1} = v_c - \frac{v_d}{2}$$

$$v_{i2} = v_c + \frac{v_d}{2}$$

$$v_{o1} \approx -ie1 \cdot R_c$$

Using emitter equivalent ckt

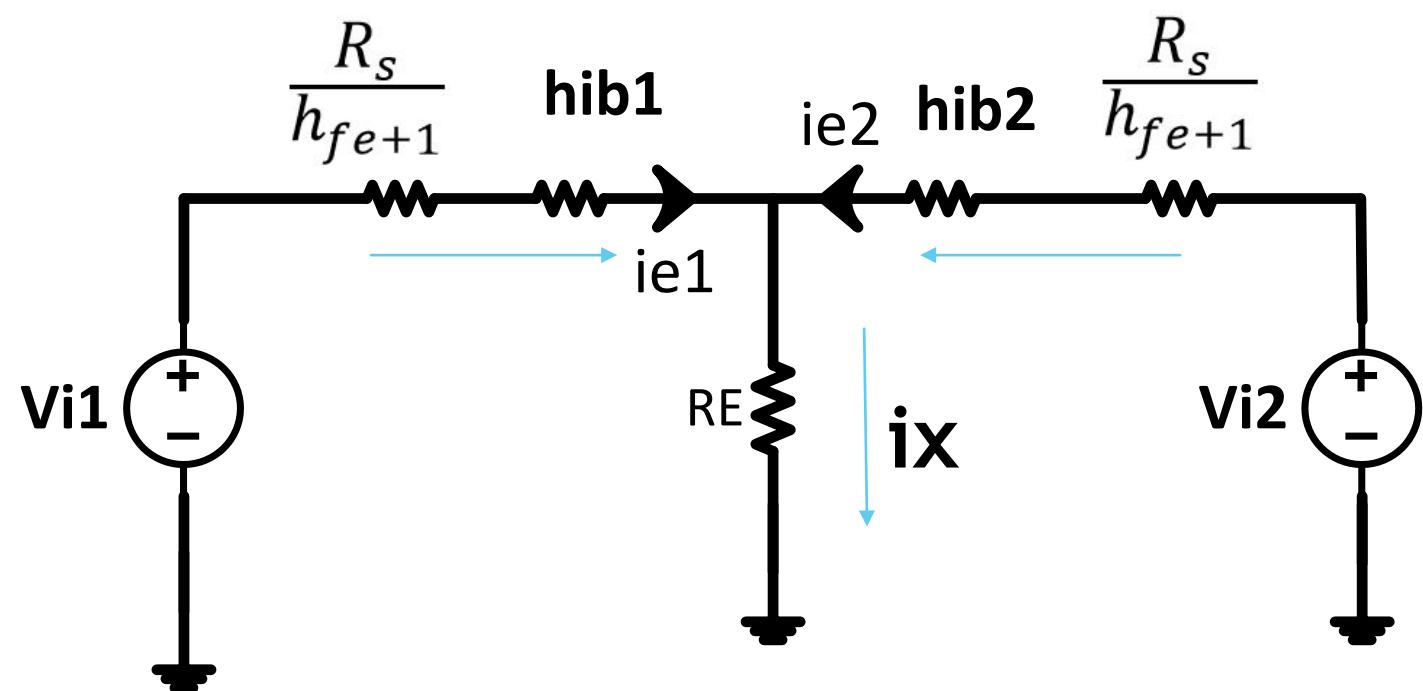

Differential Amplifiers

$$v_{o1} \approx -ie1 \cdot R_c$$


Using Superposition

$$ie1 = ie11 + ie12$$

To find $ie11$

$$\text{let } v_d = 0$$

$$v_{i1} = v_c ; v_{i2} = v_c$$

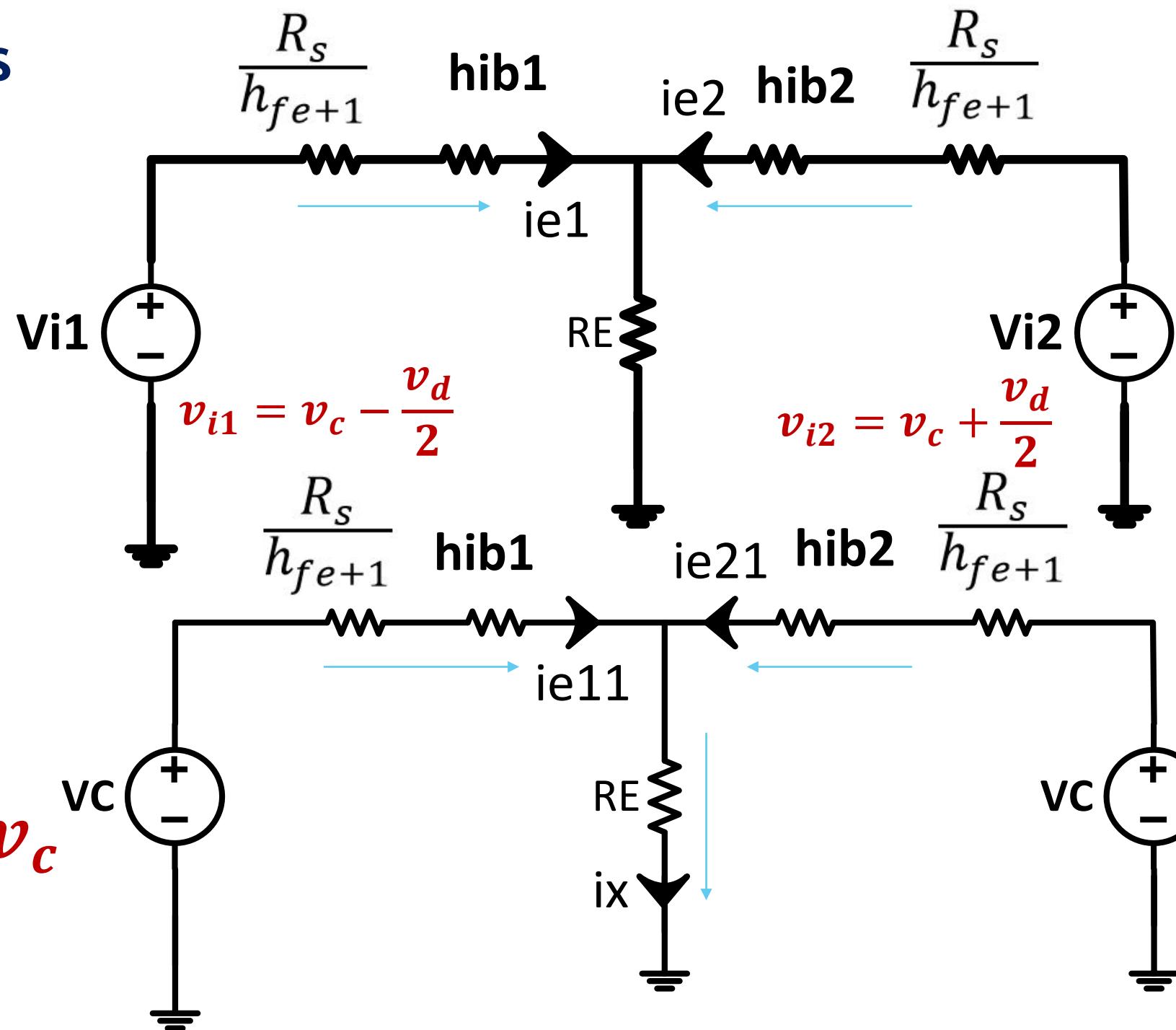

Differential Amplifiers

Small Signal Analysis

Using emitter equivalent ckt


$$v_{i1} = v_c ; v_{i2} = v_c$$

By Symmetry

$$i_{e11} = i_{e21} ; i_x = 2i_{e11}$$

$$i_{e11} = \frac{v_c}{h_{ib} + \frac{R_s}{h_{fe+1}} + 2R_E}$$
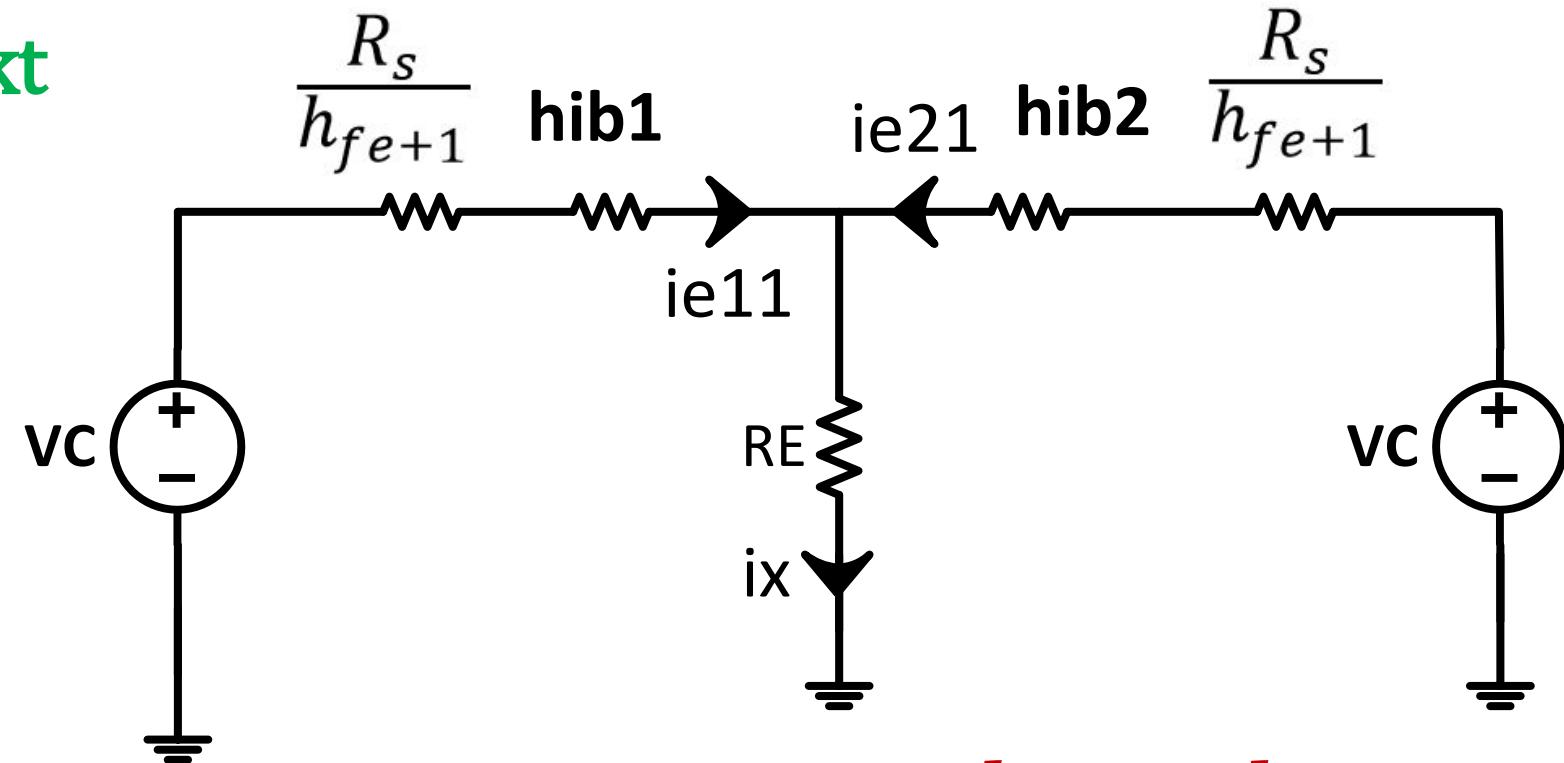
$$i_{e21} = \frac{v_c}{h_{ib} + \frac{R_s}{h_{fe+1}} + 2R_E}$$



$$h_{ib1} = h_{ib2}$$

Differential Amplifiers

2) let $v_c = 0$

$$v_1 = -\frac{v_d}{2}; \quad v_2 = \frac{v_d}{2}$$



(Using symmetry)

$$i_{e12} = -i_{e22}$$

$$ix = 0$$

$$i_{e12} = \frac{-v_d/2}{\frac{R_s}{h_{fe+1}} + h_{ib}}$$
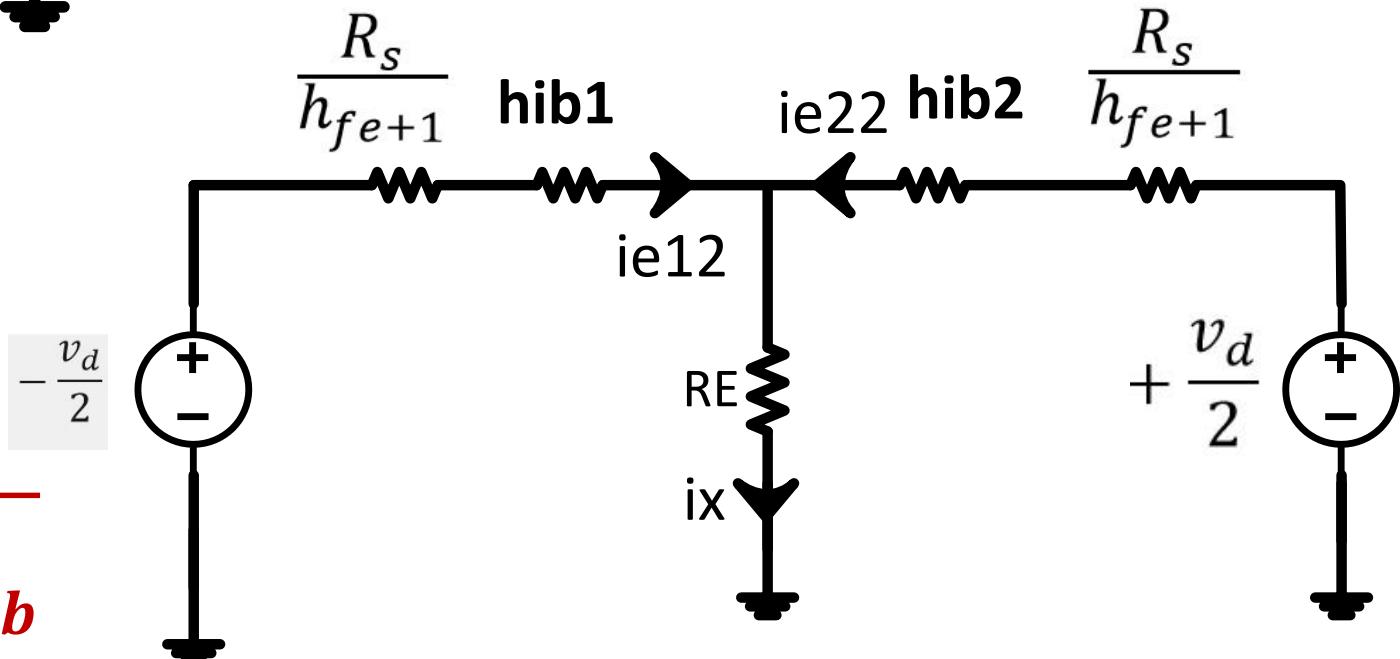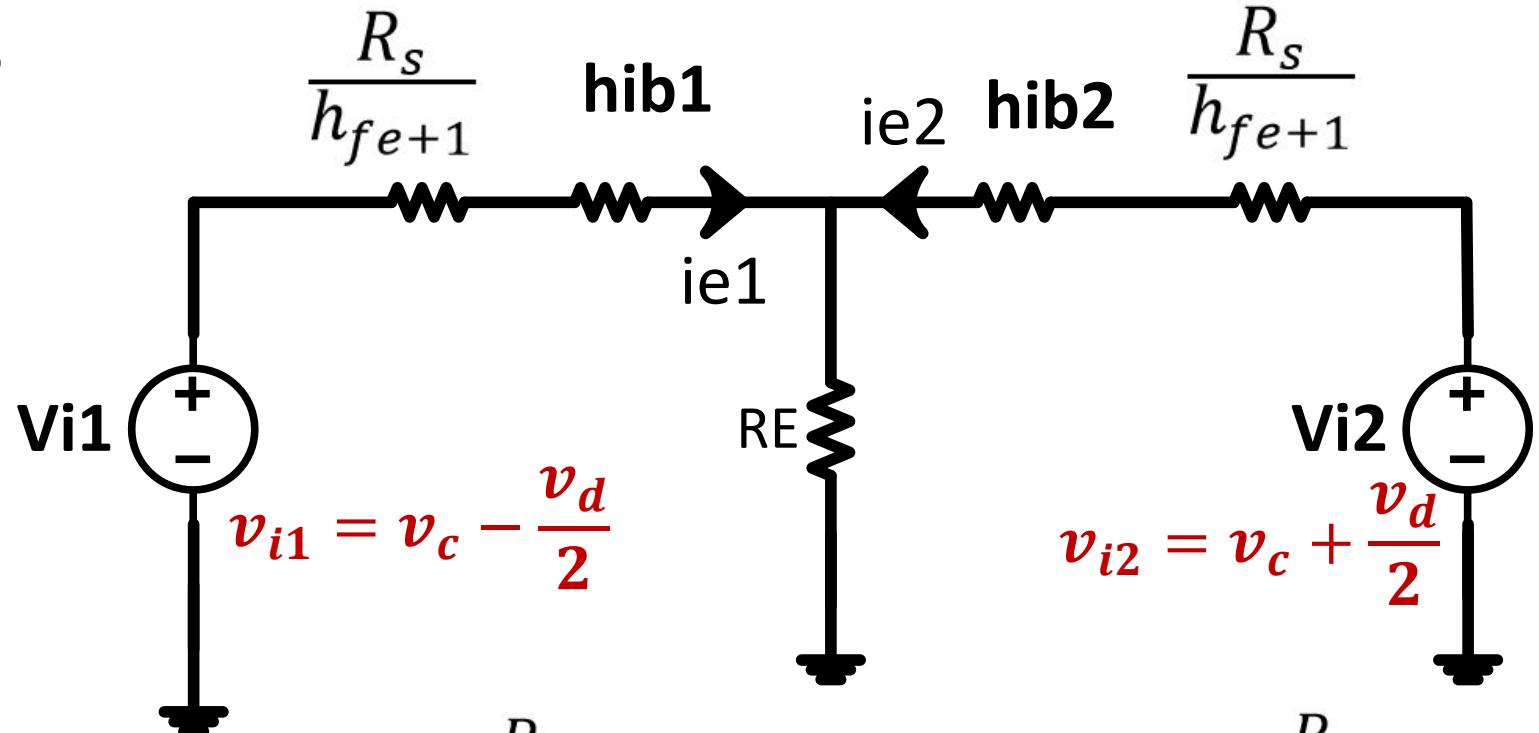
$$i_{e22} = \frac{v_d/2}{\frac{R_s}{h_{fe+1}} + h_{ib}}$$



Differential Amplifiers

Differential Amplifier Circuit:

Using Superposition

$$i_{e1} = \frac{v_c}{h_{ib} + \frac{R_s}{h_{fe+1}} + 2R_E} - \frac{v_d/2}{\frac{R_s}{h_{fe+1}} + h_{ib}}$$

$$i_{e2} = \frac{v_c}{h_{ib} + \frac{R_s}{h_{fe+1}} + 2R_E} + \frac{v_d/2}{\frac{R_s}{h_{fe+1}} + h_{ib}}$$

$$v_{o1} = + \frac{R_c v_d}{2 \left(h_{ib} + \frac{R_s}{h_{fe+1}} \right)} - \frac{R_c v_c}{h_{ib} + \frac{R_s}{h_{fe+1}} + 2R_E} \rightarrow$$

$$\triangleright v_{o2} = - \frac{R_c v_d}{2 \left(h_{ib} + \frac{R_s}{h_{fe+1}} \right)} - \frac{R_c v_c}{h_{ib} + \frac{R_s}{h_{fe+1}} + 2R_E}$$

$$v_{o1} - v_{o2} = \frac{R_c}{h_{ib} + \frac{R_s}{h_{fe+1}}} v_d$$

Differential Amplifiers

$$v_{o1} = + \frac{R_c v_d}{2 \left(h_{ib} + \frac{R_s}{h_{fe+1}} \right)} - \frac{R_c v_c}{h_{ib} + \frac{R_s}{h_{fe+1}} + 2R_E}$$

Ad \equiv Differential mode gain

$$Ad = \frac{v_o}{v_d} \Big|_{v_c=0}$$

let $v_o = v_{o1}$

$$Ad = \frac{v_{o1}}{v_d} \Big|_{v_c=0}$$

$$Ad = \frac{R_c}{2 \left(h_{ib} + \frac{R_s}{h_{fe+1}} \right)}$$

Differential Amplifiers

$$v_{o1} = + \frac{R_c v_d}{2 \left(h_{ib} + \frac{R_s}{h_{fe+1}} \right)} - \frac{R_c v_c}{h_{ib} + \frac{R_s}{h_{fe+1}} + 2R_E}$$

Ac ≡ Common mode gain

$$Ac = \frac{v_o}{v_c} \mid v_d=0$$

let $v_o = v_{o1}$

$$Ac = \frac{v_{o1}}{v_c} \mid v_d=0$$

$$Ac = \frac{-R_c}{2R_E + h_{ib} + \frac{R_s}{h_{fe+1}}}$$

Differential Amplifiers

CMRR ≡ Common Mode Rejection Ratio


$$CMRR = \left| \frac{Ad}{Ac} \right|$$

$$CMRR = \frac{2R_E + h_{ib} + \frac{R_s}{h_{fe+1}}}{2 \left(h_{ib} + \frac{R_s}{h_{fe+1}} \right)}$$

To increase CMRR we need to increase R_E

$$CMRR = \frac{2R_E + h_{ib} + \frac{R_s}{h_{fe+1}}}{2 \left(h_{ib} + \frac{R_s}{h_{fe+1}} \right)}$$

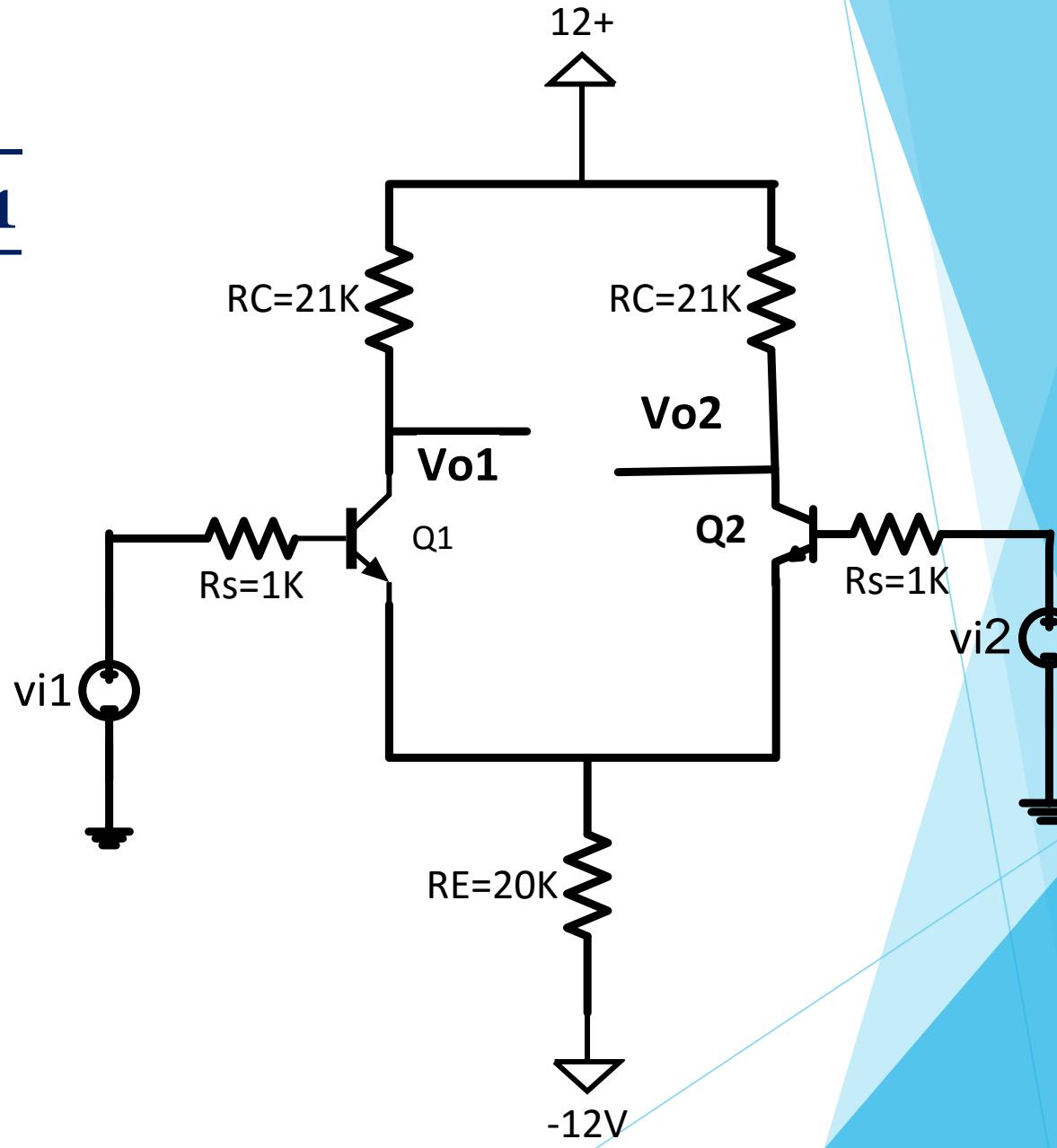
$$I_{E1} = I_{E2} = \frac{12 - 0.7}{\frac{R_s}{41} + 2R_E}$$



Differential Amplifier with constant current source:


$$R_{TH} = 5k \parallel 5k = 2.5k$$
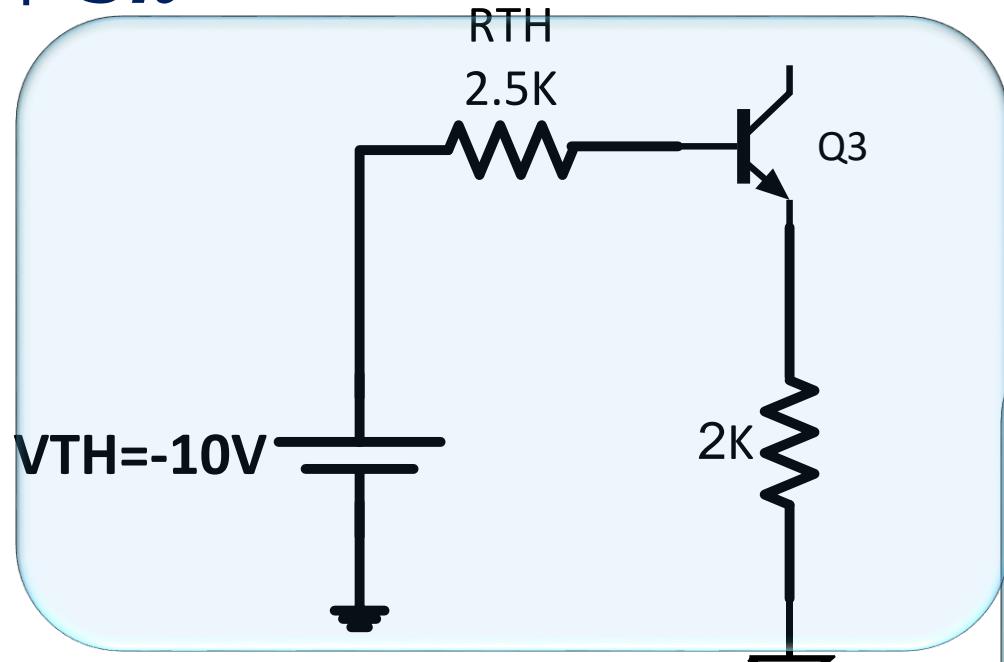
$$V_{TH} = \frac{5k}{5k + 5k} (-20) = -10 V$$



$$I_{E3} = \frac{10 - 0.7}{\frac{2.5k}{101} + 2k} = 4.65 mA$$

$$\beta = 100$$


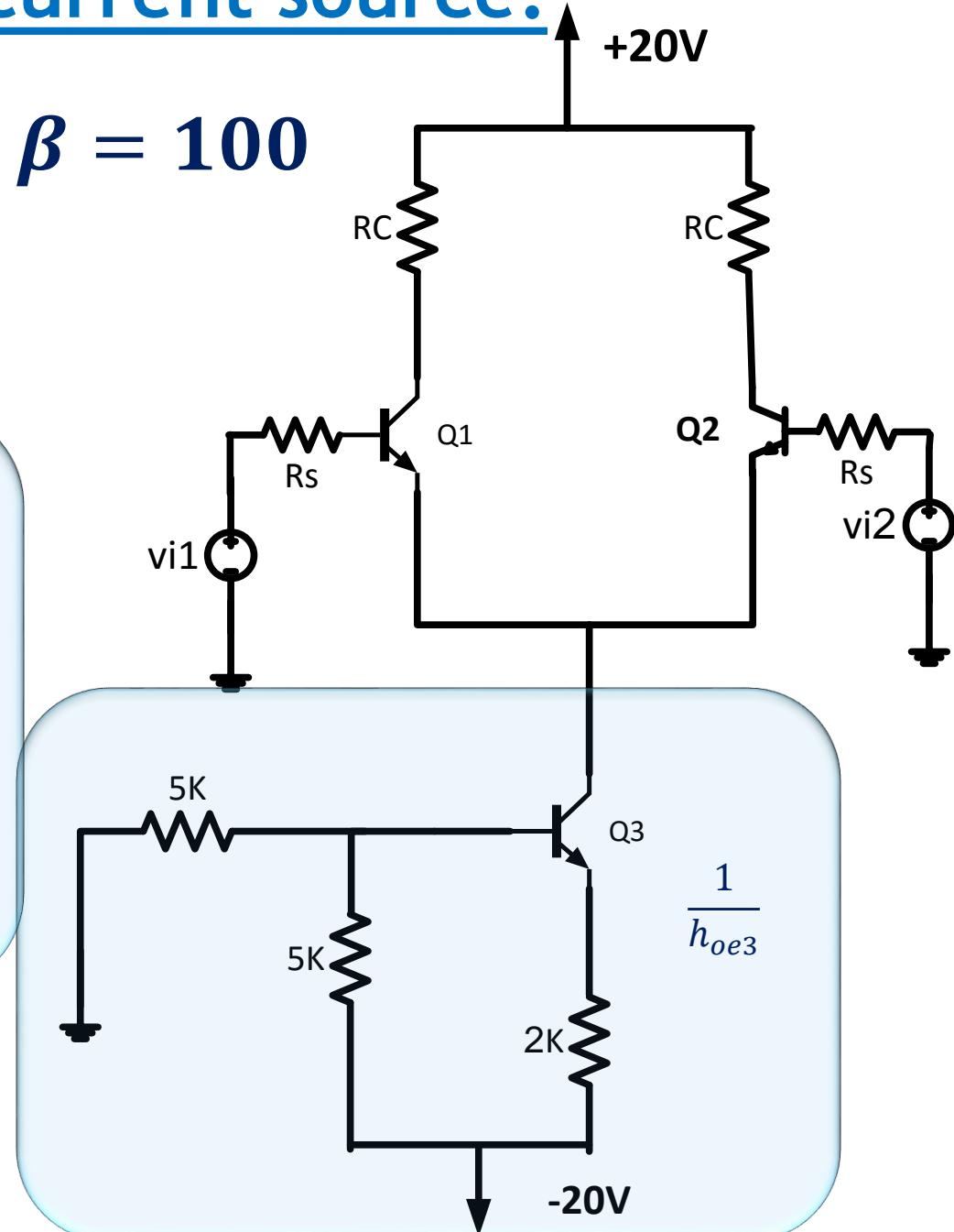


Differential Amplifiers

Differential Amplifier with constant current source:



$$I_{E3} = \frac{10 - 0.7}{\frac{2.5k}{101} + 2k} = 4.65 \text{ mA}$$
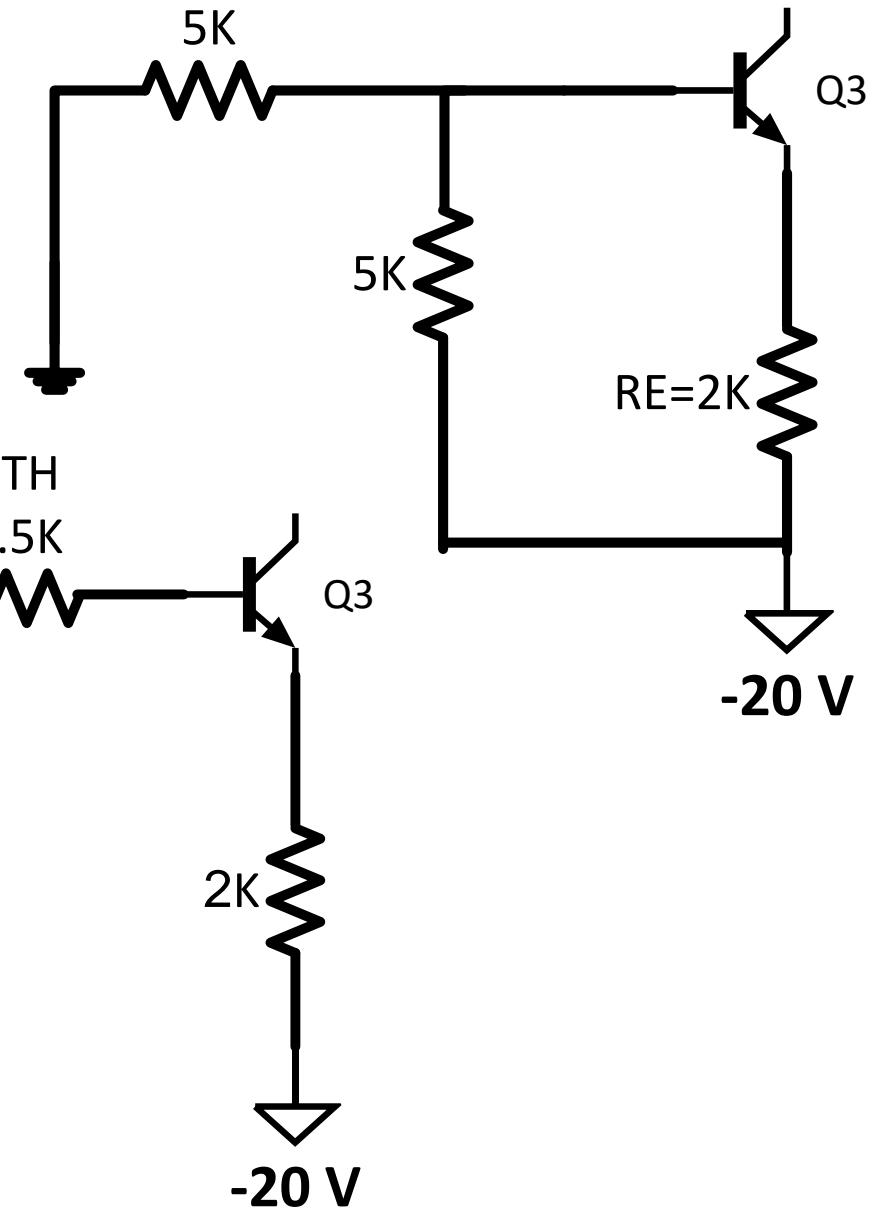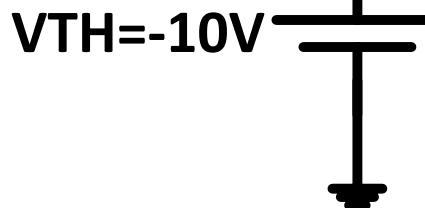
$$h_{ie3} = \beta \frac{V_T}{I_{CQ3}} = 0.559K$$



Differential Amplifiers

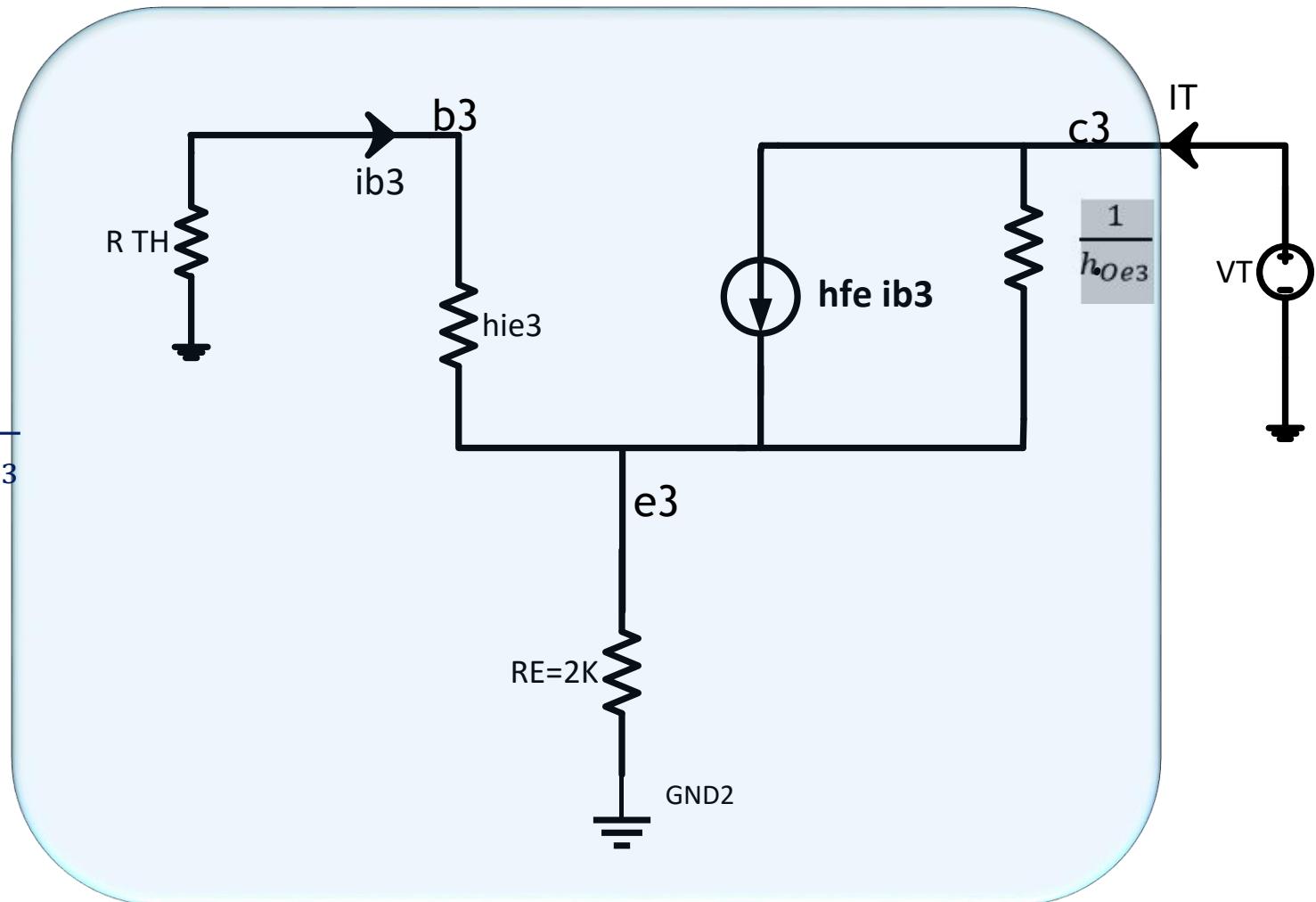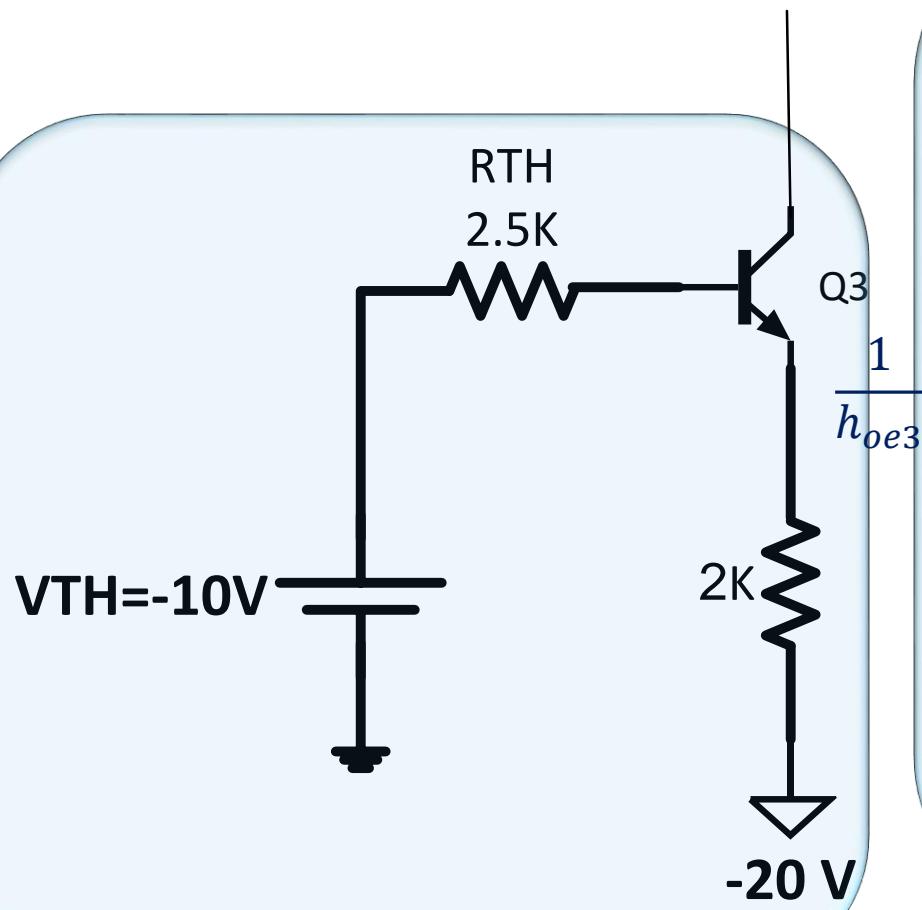Ac small signal equivalent circuit for the constant current source:




Differential Amplifiers

Ac small signal equivalent circuit for the constant current source:

$$V_T = \frac{1}{h_{oe3}} I_T - \frac{h_{fe}}{h_{oe3}} i_{b3} - (h_{ie3} + R_{TH}) i_{b3}$$
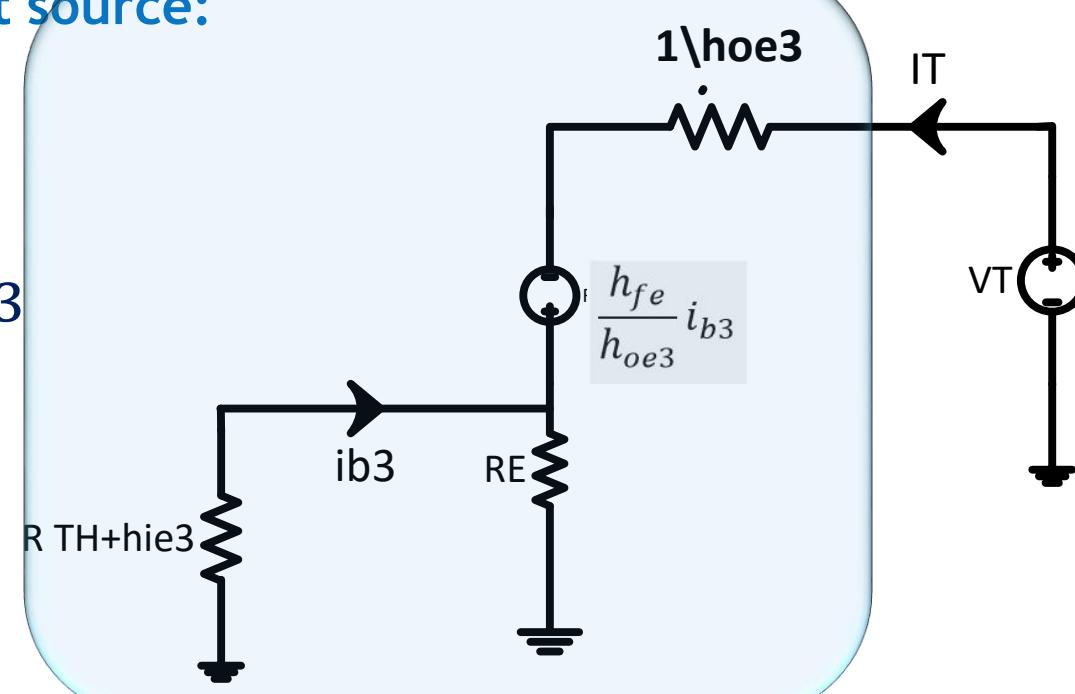
$$i_{b3} = -\frac{R_E}{R_E + h_{ie3} + R_{TH}} I_T$$



$$\therefore R_o = \frac{V_T}{I_T}$$

$$= \frac{1}{h_{oe3}} + \frac{h_{fe}}{h_{oe3}} \frac{R_E}{R_E + h_{ie3} + R_{TH}} + \frac{(h_{ie3} + R_{TH})}{R_E + h_{ie3} + R_{TH}} R_E$$


$$R_o \approx \frac{1}{h_{oe3}} + \frac{h_{fe}}{h_{oe3}} \frac{R_E}{R_E + h_{ie3} + R_{TH}}$$

$$R_o \approx \frac{1}{h_{oe3}} + \frac{h_{fe}}{h_{oe3}} \frac{R_E}{R_E + h_{ie3} + R_{TH}}$$

- ▶ let $\frac{1}{h_{oe}} = 80K$, $h_{ie} = 0.559k$
- ▶ $h_{fe} = 100$, $R_E = 2k$, $R_{TH} = 2.5k$
- ▶ $R_o = 3.25 M\Omega$

$$CMRR = \frac{2R_E + h_{ib} + \frac{R_s}{h_{fe+1}}}{2 \left(h_{ib} + \frac{R_s}{h_{fe+1}} \right)}$$

R_E → R_o

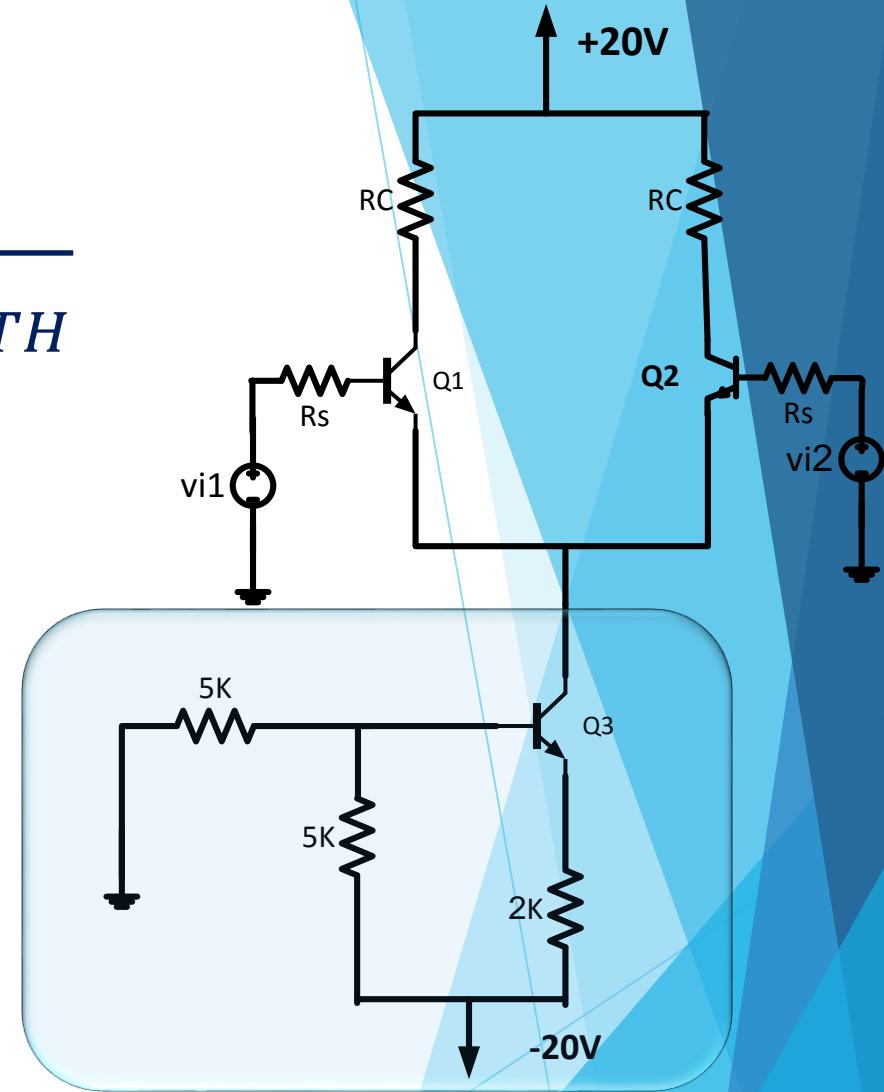

Differential Amplifiers

Bipolar transistor current sources:

Q1 and Q2 are In the active region

1. Current mirror : Simple


$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

If Q_1 is matched to Q_2

$$\beta_1 = \beta_2 ; I_{S1} = I_{S2} ; V_{T1} = V_{T2}$$


And since $V_{BE1} = V_{BE2}$

$$\therefore I_{C1} = I_{C2} = I_o$$

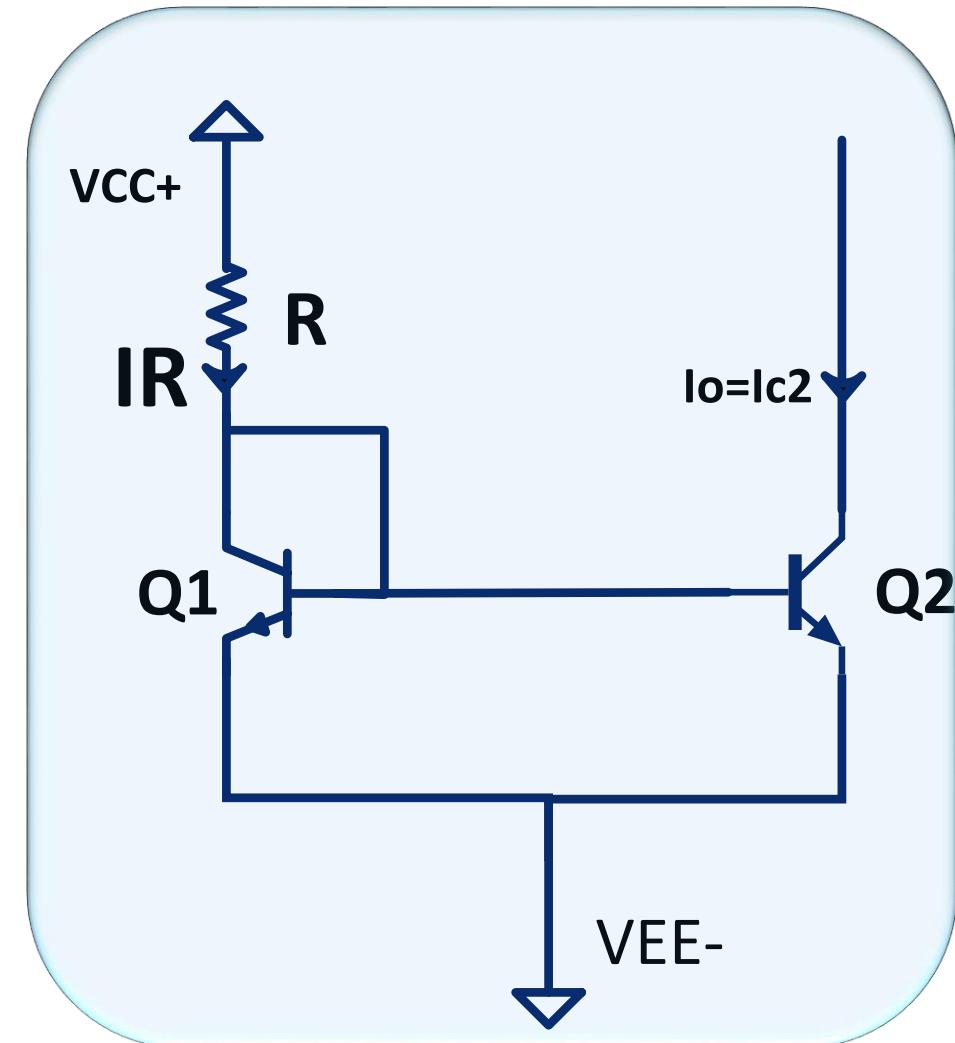

To find I_o in terms of I_R

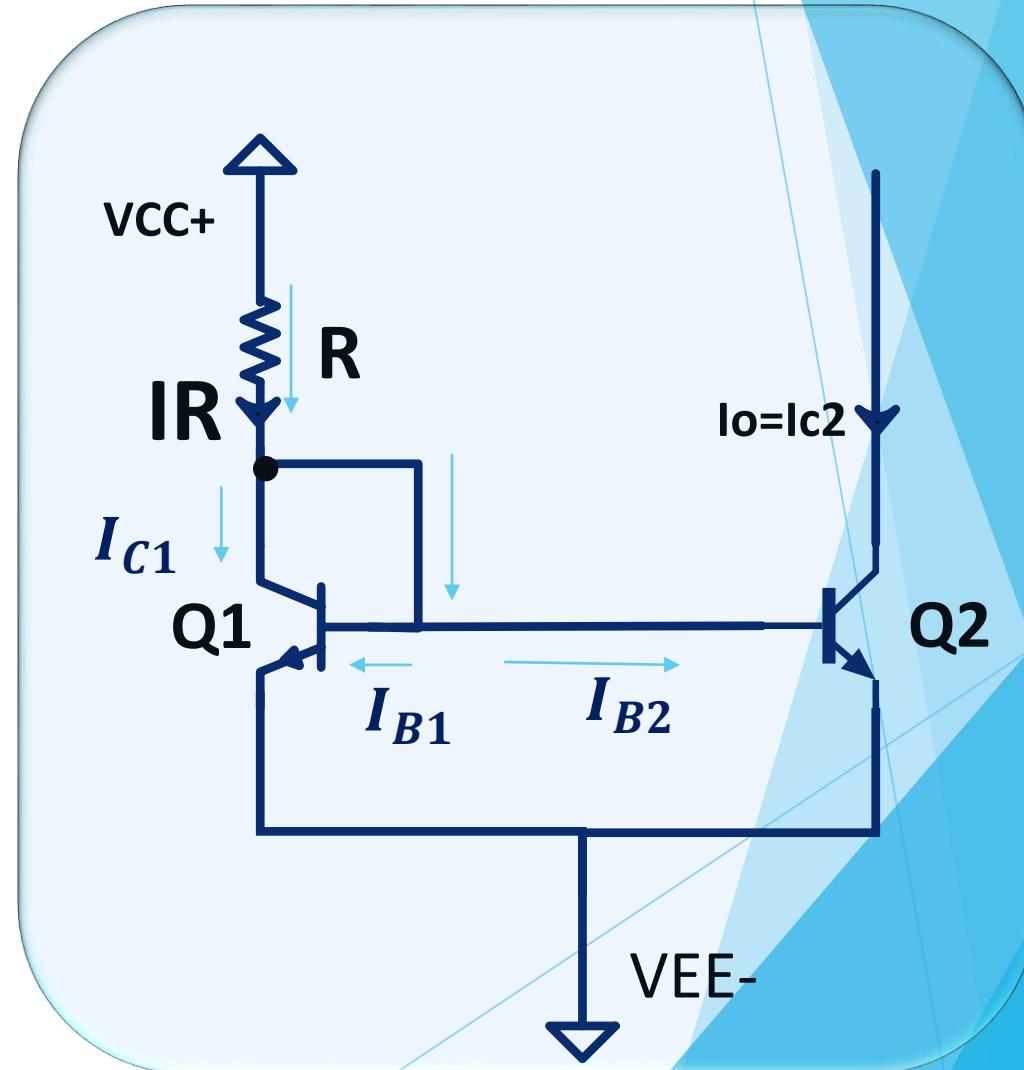- ▶ **KCL** $I_R = I_{C1} + I_{B1} + I_{B2}$
- ▶ $I_{C1} = I_{C2}$; $I_{B1} = I_{B2}$
- ▶ ∴ $I_o = I_{C2} = \frac{I_R}{1 + \frac{2}{\beta}}$



Differential Amplifiers

Bipolar transistor current sources:

1. Current mirror : Simple

1) if $\beta = \infty$

$$I_o = I_R$$



2) if $\beta = 100$

$$I_o = I_R ; \text{ } 2\% \text{ error}$$

To find I_R

$$KVL: V_{CC} = R I_R + V_{BE1} - V_{EE}$$
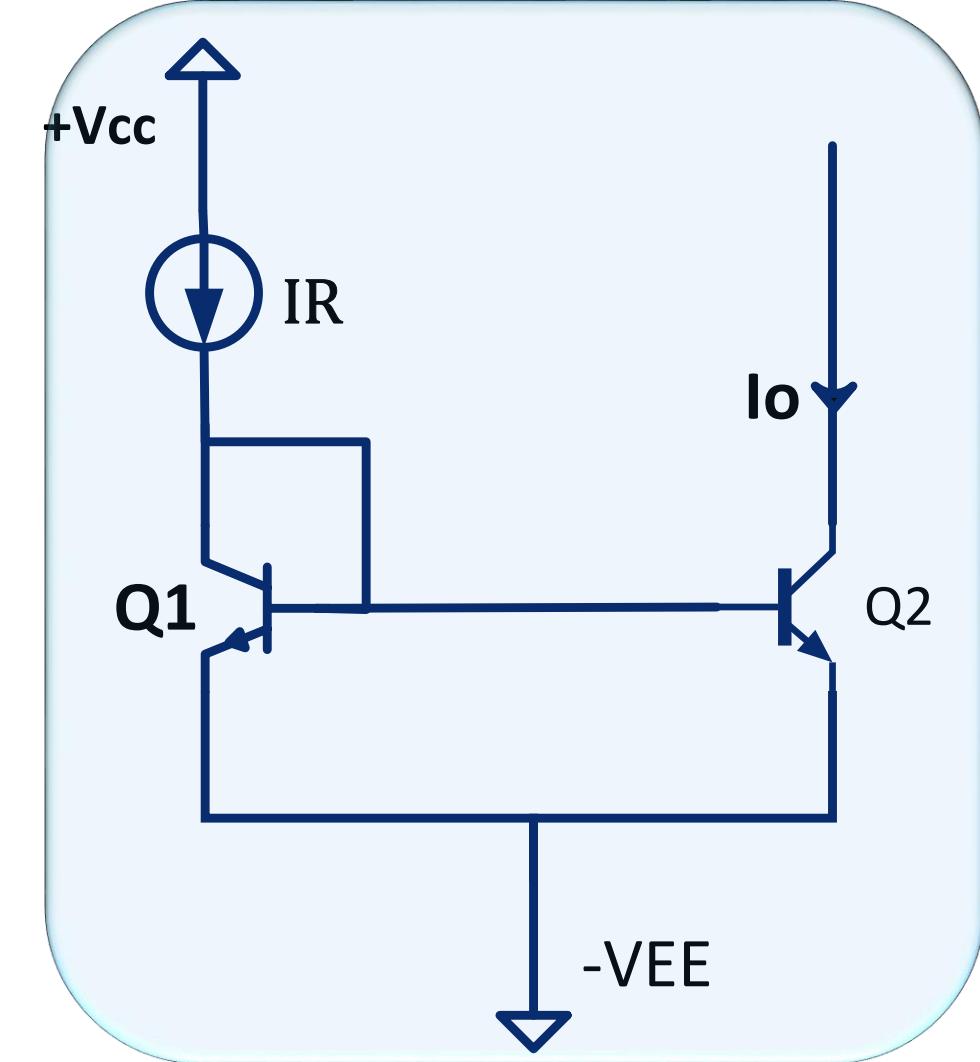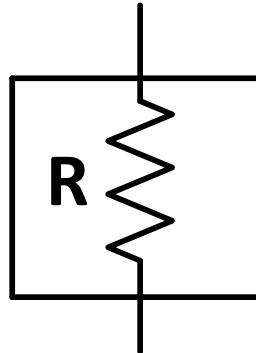
$$I_R = \frac{V_{CC} + V_{EE} - V_{BE}}{R}$$



$$I_o = I_{C2} = \frac{I_R}{1 + \frac{2}{\beta}}$$

Bipolar transistor current sources:

$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

1. Current mirror : Simple

If the area of the EB junction of Q2 is m times that of Q1


$$\therefore I_{S2} = mI_{S1}$$

And since $V_{BE1} = V_{BE2}$ and $\beta_1 = \beta_2$; $V_{T1} = V_{T2}$

$$\therefore I_{C2} = mI_{C1}$$

KCL: $I_R = I_{C1} + I_{B1} + I_{B2}$
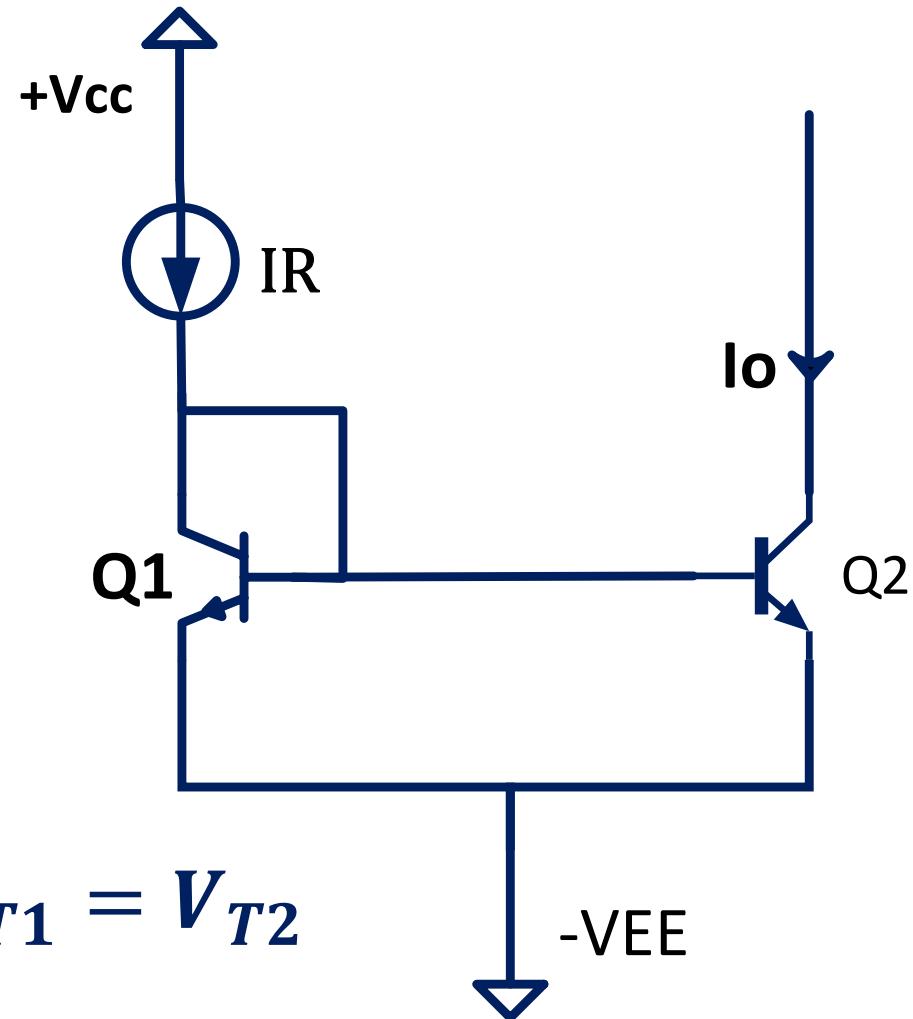
$$I_R = \frac{I_{C2}}{m} + \frac{I_{C2}}{\beta m} + I_{B2}$$




$$I_R = \frac{I_{C2}}{m} + \frac{I_{C2}}{\beta m} + I_{B2}$$

$$I_{C2} = m I_{C1}$$

$$\therefore I_{C2} = I_o = I_R \frac{m}{1 + \frac{m+1}{\beta}}$$

if $\beta = \infty$

$$I_o = I_{C2} = m I_R$$

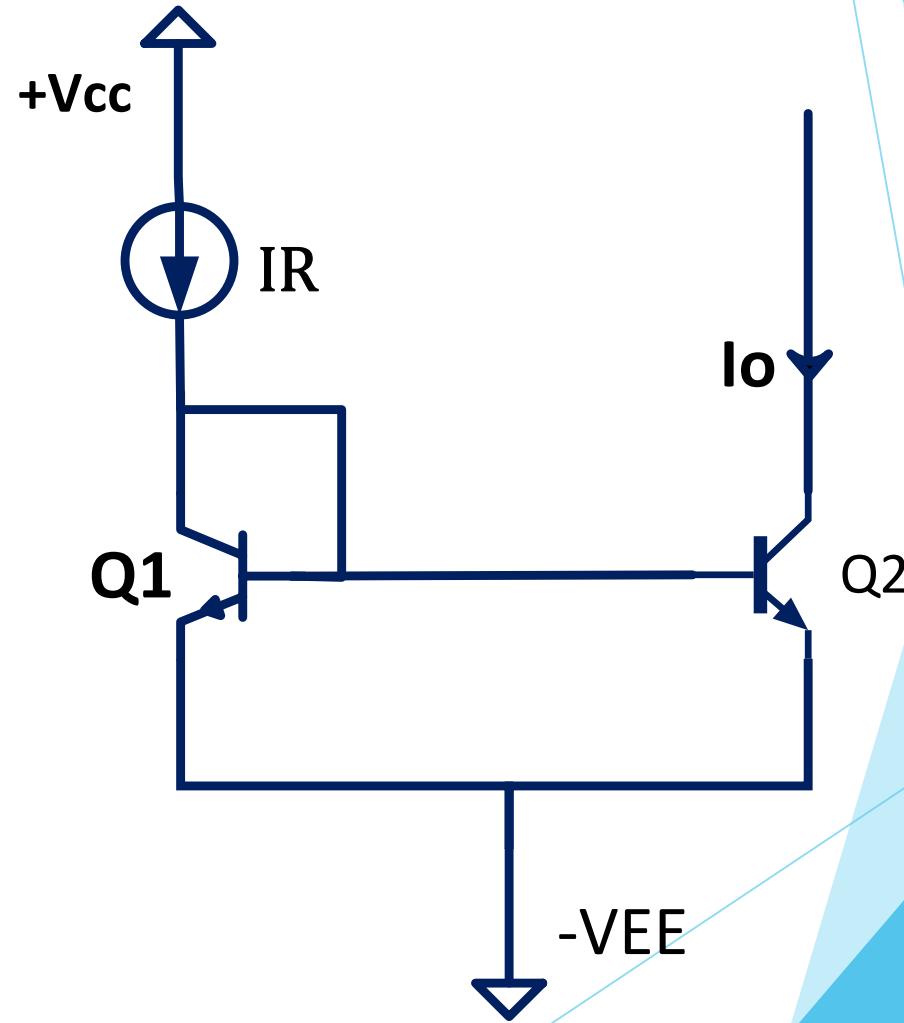


Bipolar transistor current sources:

Output - Impedance:

$$\text{To find } R_o = \frac{V_T}{I_T}$$

Ac small signal equivalent circuit

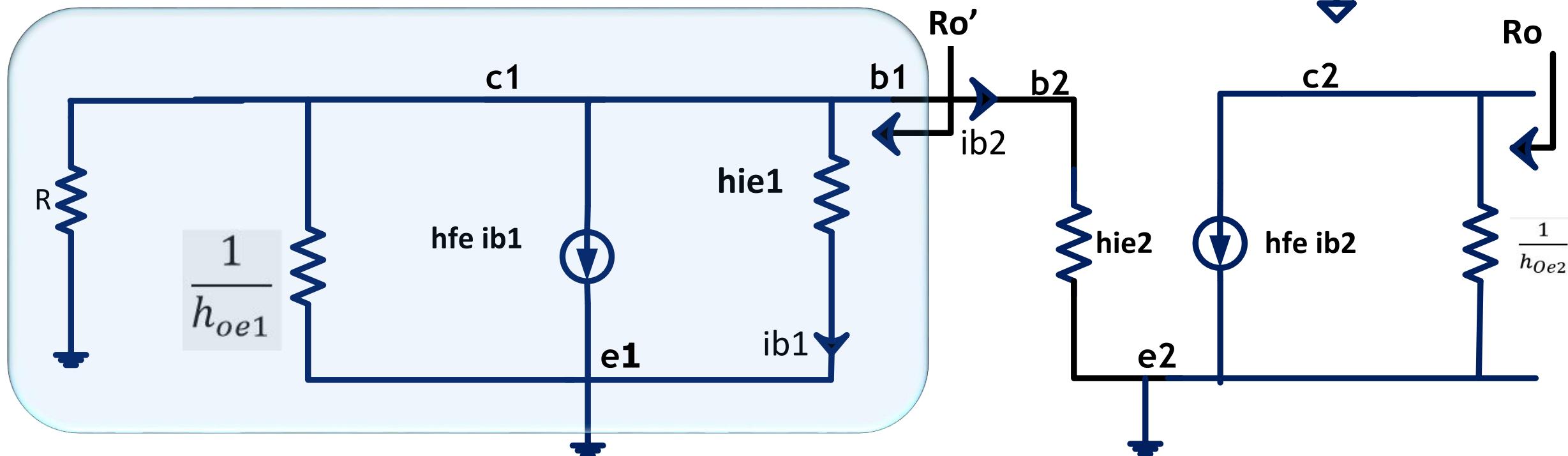


Differential Amplifiers

Bipolar transistor current sources:

Output - Impedance:


To find Ro'

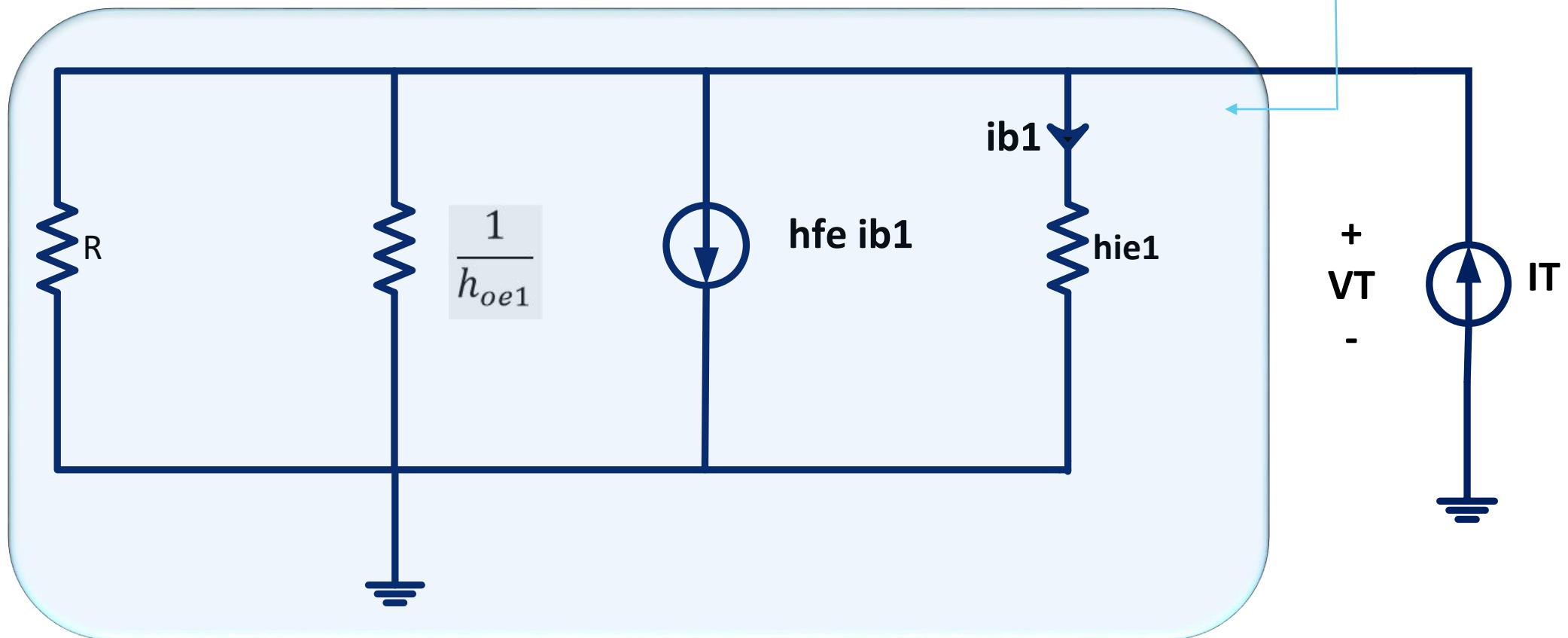

Bipolar transistor current sources:

To find $\text{Ro}' = \frac{V_T}{I_T}$

Output - Impedance:

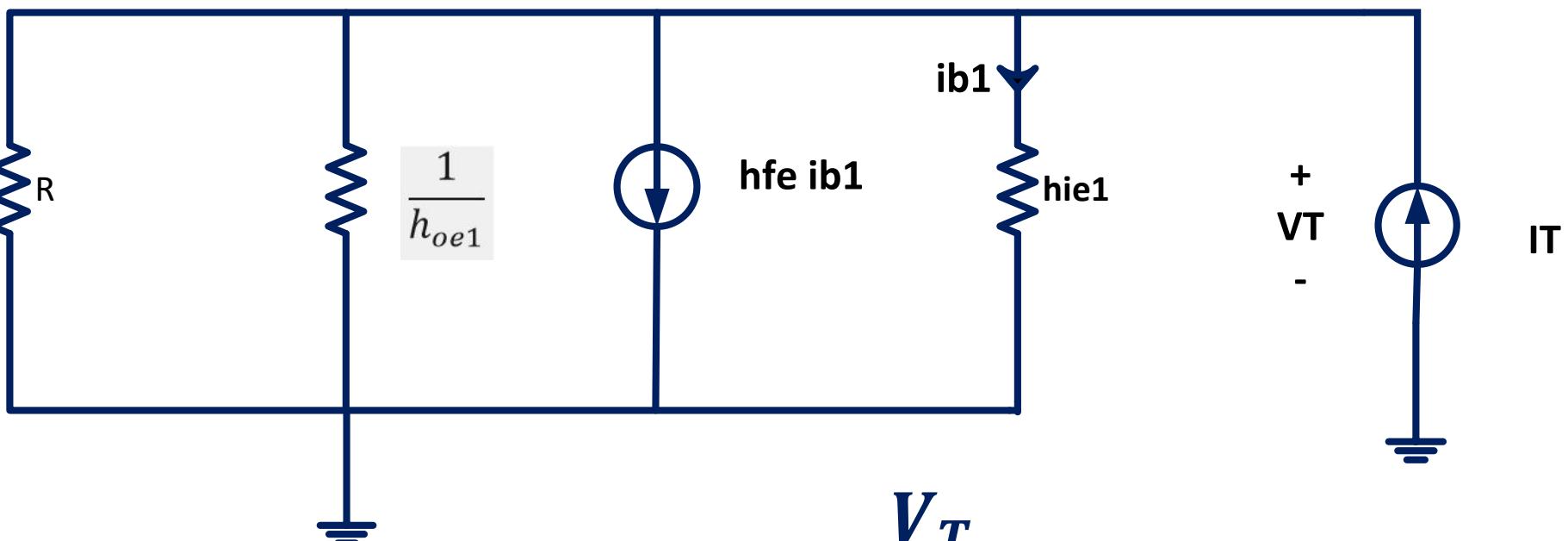

$$I_T = \frac{V_T}{R \parallel \frac{1}{h_{oe1}} \parallel h_{ie1}} + h_{fe} i_{b1}$$

$$I_T = \frac{h_{fe}}{h_{ie1}} V_T + \frac{V_T}{R \parallel h_{ie1} \parallel \frac{1}{h_{oe1}}}$$

$$i_{b1} = \frac{V_T}{h_{ie1}}$$

$$g_{m1} = \frac{h_{fe1}}{h_{ie1}}$$

$$\text{Ro}' = R \parallel h_{ie1} \parallel \frac{1}{h_{oe1}} \parallel \frac{1}{g_{m1}}$$

Differential Amplifiers

Bipolar transistor current sources:


Output - Impedance:

To find $R_o = \frac{V_T}{I_T}$

$$I_T = h_{fe} i_{b2} + \frac{V_T}{\frac{1}{h_{oe2}}}$$

$$i_{b2} = 0$$
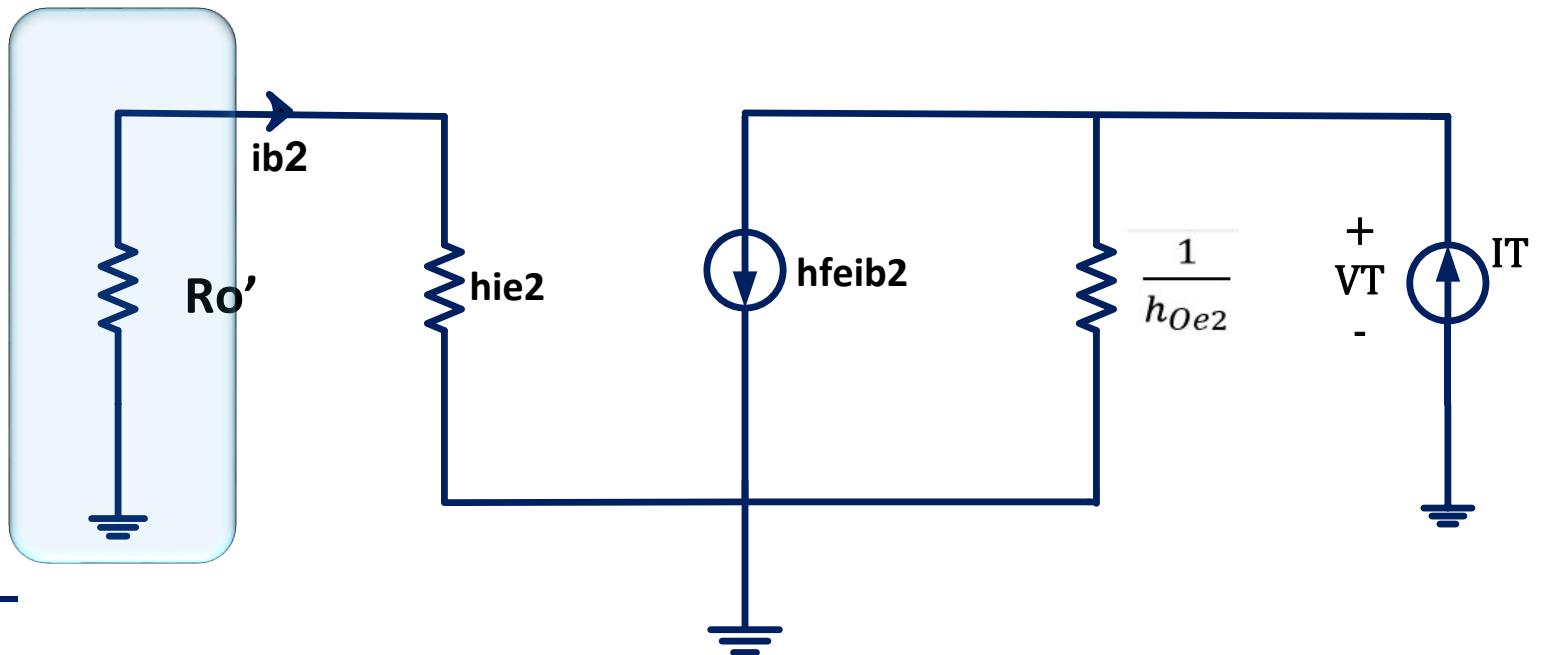
$$\therefore \frac{V_T}{I_T} = \frac{1}{h_{oe2}}$$



Bipolar transistor current sources:

2. Bipolar mirror with base-current compensation:



Q_1, Q_2 are matched

Reduce the B dependence

$$\beta_1 = \beta_2 ; I_{S1} = I_{S2} ; V_{T1} = V_{T2}$$

And since $V_{BE1} = V_{BE2}$


$$\therefore I_{C1} = I_{C2} = I_o$$

$$I_{B1} = I_{B2}$$

$$\therefore I_R = I_{C1} + I_{B3}$$

$$I_{B3} = \frac{I_{E3}}{\beta + 1}$$

$$I_{E3} = \frac{2I_C}{\beta}$$

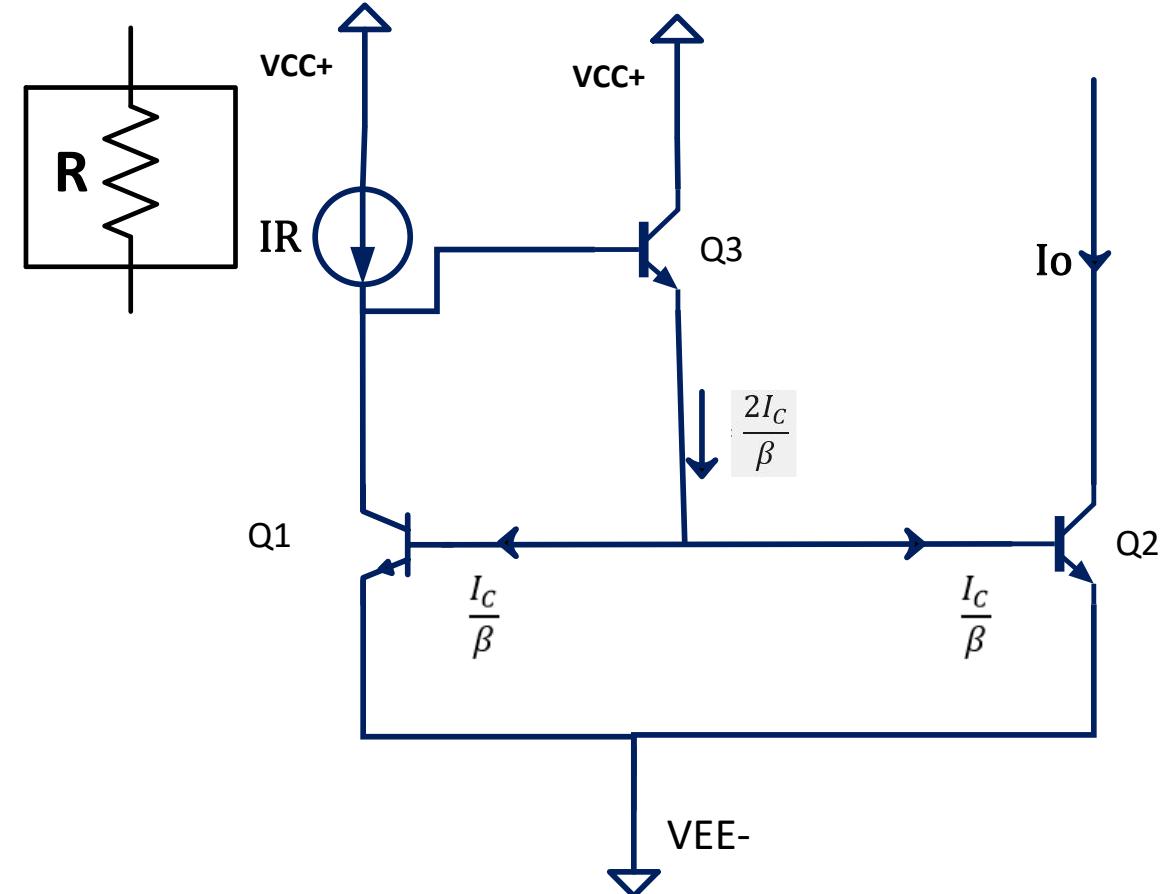


Bipolar transistor current sources:

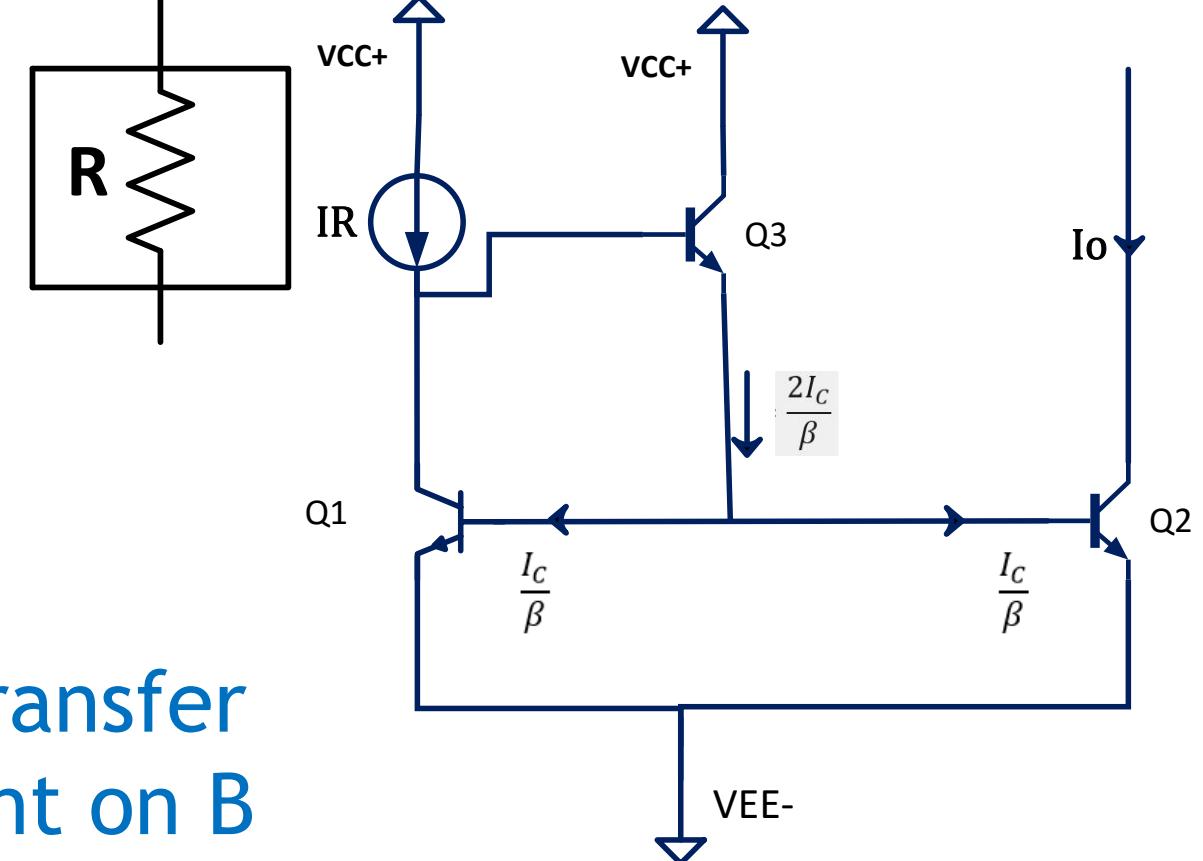2. Bipolar mirror with base-current compensation:

$$\therefore I_R = I_C + \frac{2I_C}{\beta(\beta + 1)}$$

$$\therefore I_o = I_R \cdot \frac{1}{1 + \frac{2}{\beta^2 + \beta}}$$



Current source with a current transfer ratio that is much less dependent on B than that of the simple current mirror.


Bipolar transistor current sources:

2. Bipolar mirror with base-current compensation:

Show that :

$$R_o = \frac{1}{h_{oe2}}$$
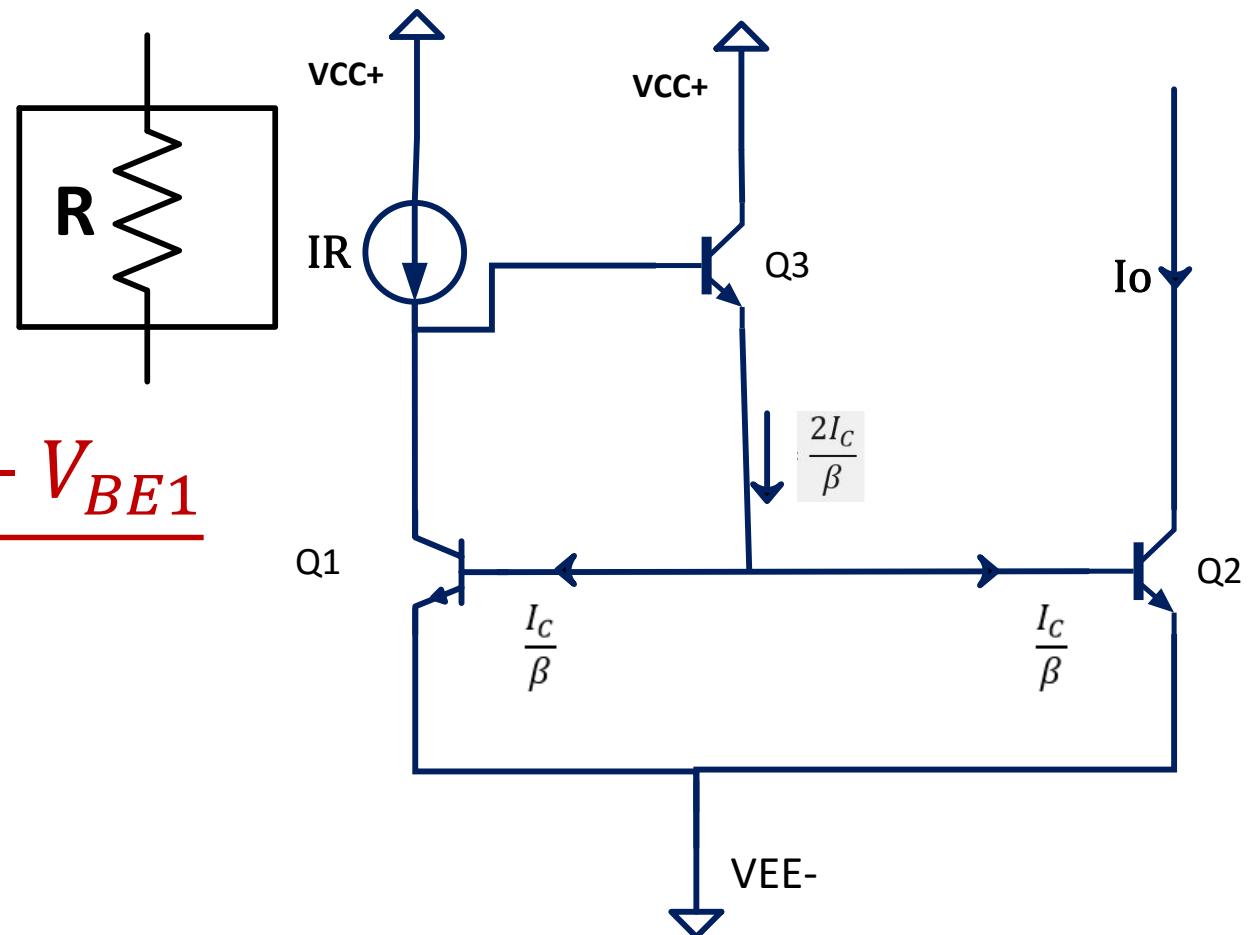
$$I_R = \frac{V_{CC} + V_{EE} - V_{BE3} - V_{BE1}}{R}$$



Bipolar transistor current sources:

3. The Wilson Current:


1) Reduce the B dependence

2) Increase $R_o = \frac{h_{fe}}{2} \frac{1}{h_{oe3}}$

Q_1, Q_2 are matched

$$I_{C1} = I_{C2} = I_C$$
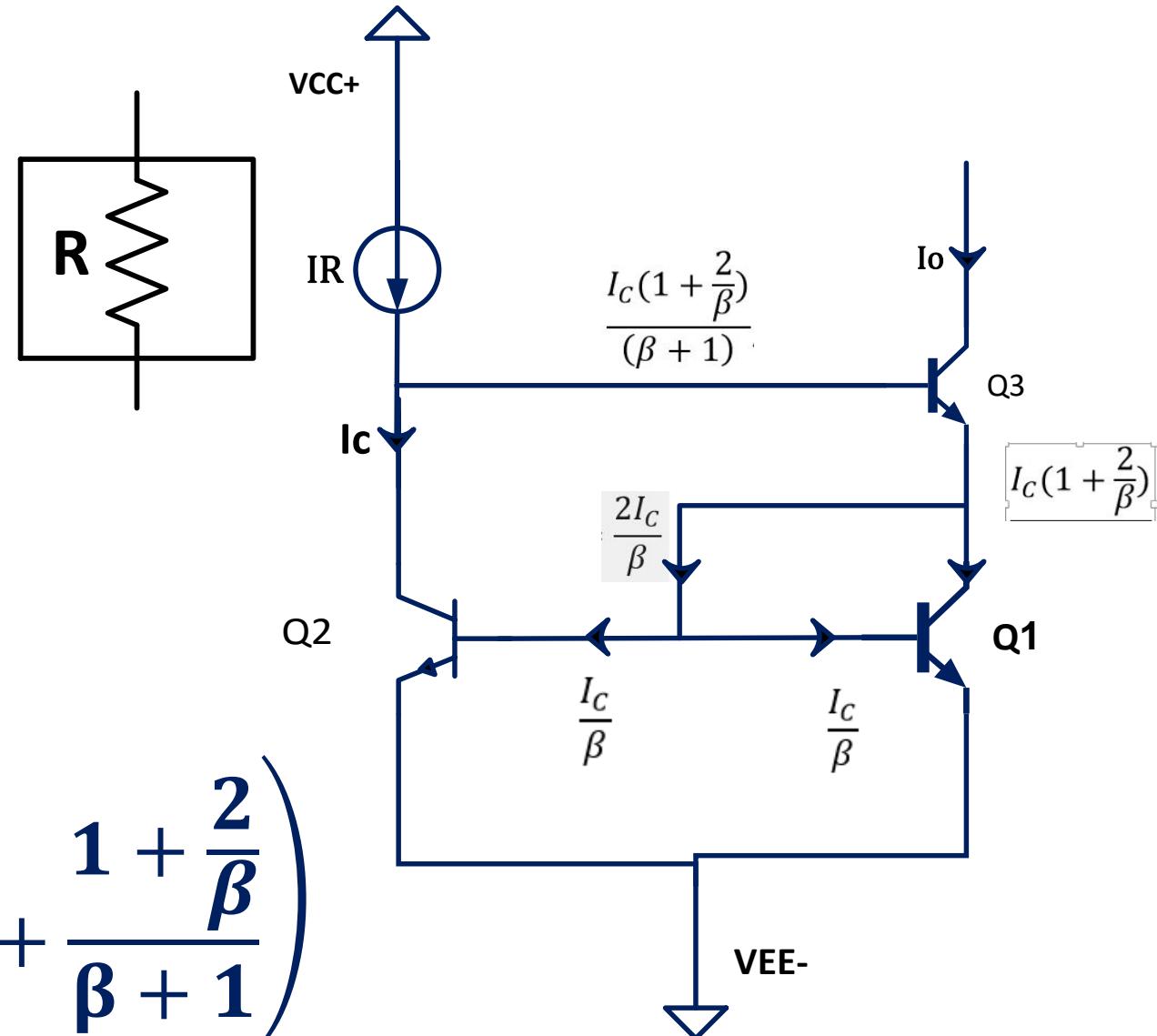
$$I_R = I_C + \frac{I_C \left(1 + \frac{2}{\beta}\right)}{\beta + 1} = I_C \left(1 + \frac{1 + \frac{2}{\beta}}{\beta + 1}\right)$$




Bipolar transistor current sources:

3. The Wilson Current:

$$I_o = I_{C3} = \frac{\beta}{\beta + 1} I_{E3} = \frac{\beta \left(1 + \frac{2}{\beta}\right)}{\beta + 1} I_c$$

$$\frac{I_o}{I_R} = \frac{I_c \left(1 + 2/\beta\right) (\beta/\beta + 1)}{I_c \left(1 + \frac{2}{\beta + 1}\right)}$$

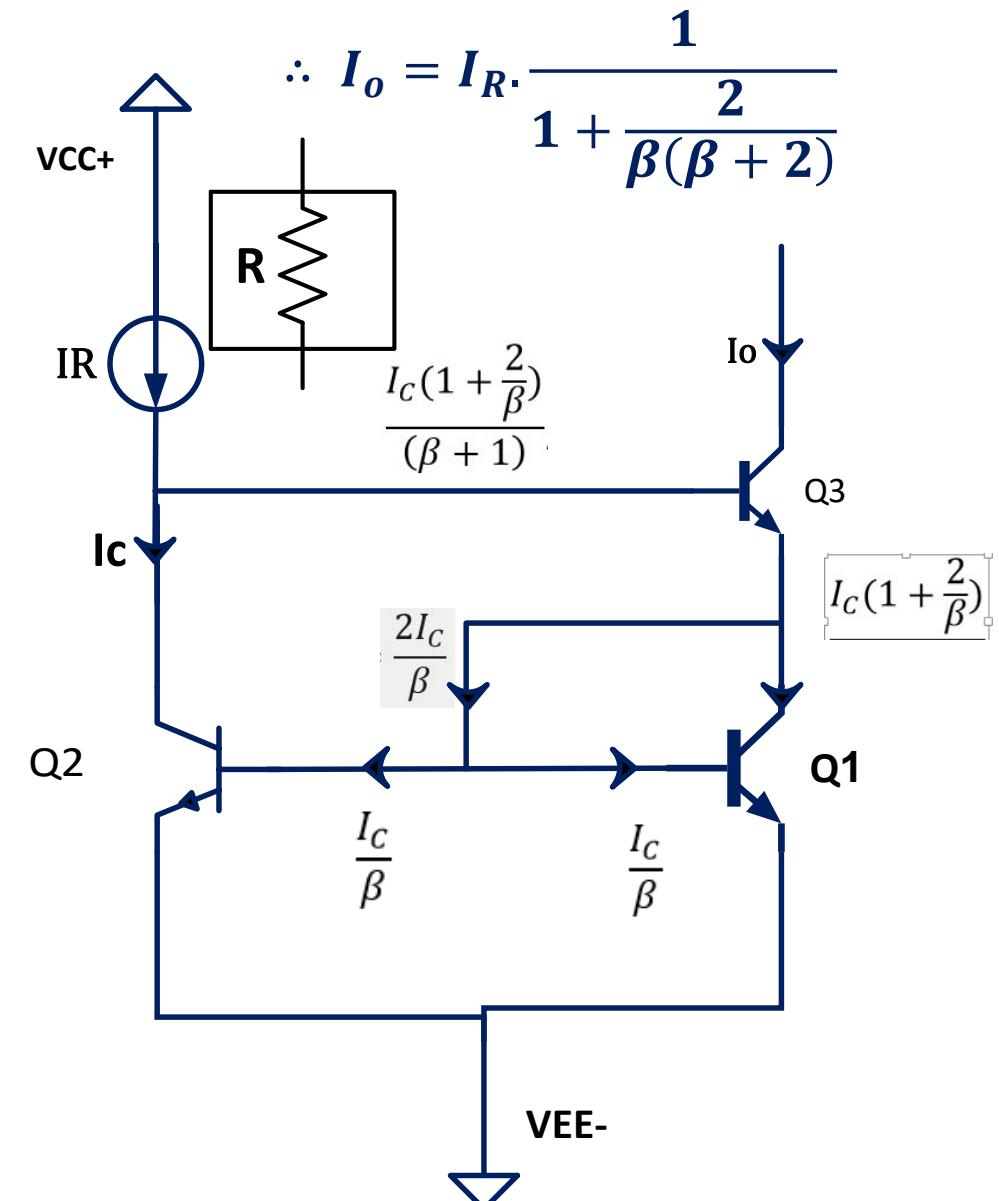
$$I_o = I_R \frac{1}{1 + \frac{2}{\beta(\beta + 2)}}$$



Differential Amplifiers


The Wilson current mirror

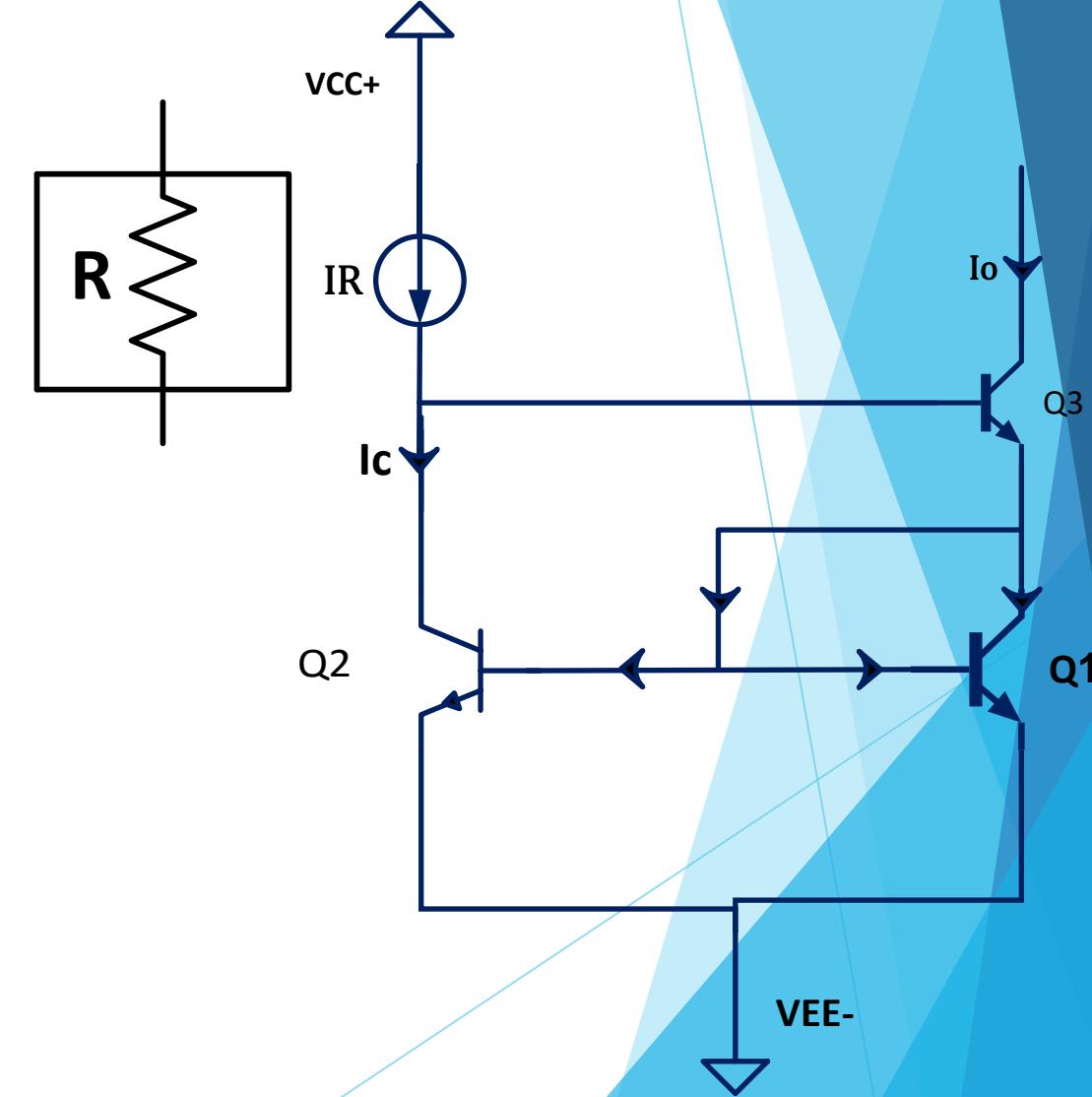To proof that $R_o \approx \frac{h_{fe}}{2} \frac{1}{h_{oe}}$



Bipolar transistor current sources:

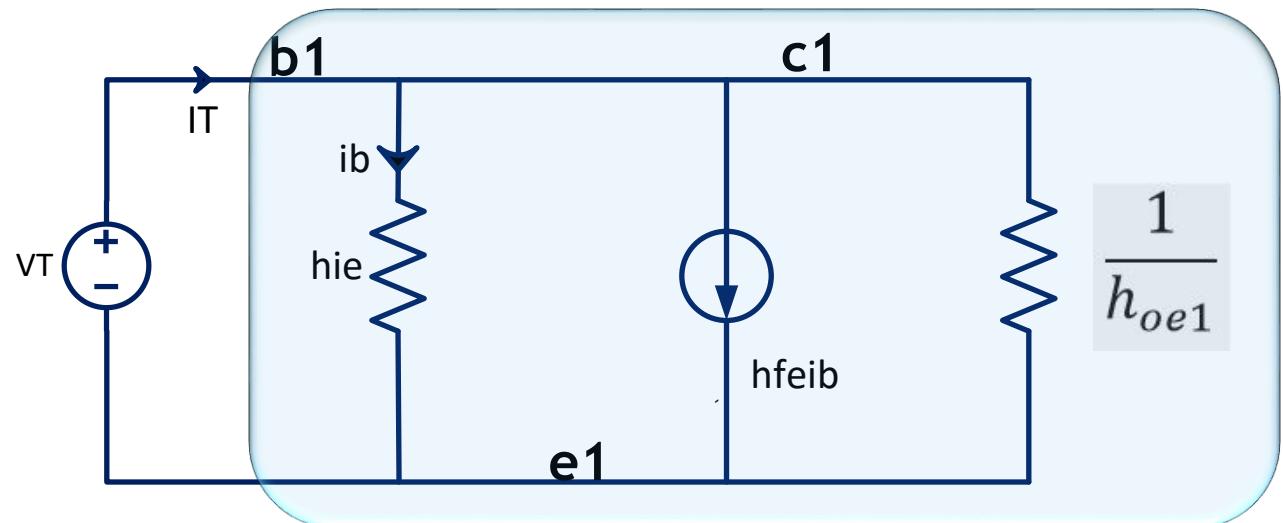The Equivalent circuit for a diode connected transistor




$$I_T = h_{fe1} i_{b1} + \frac{V_T}{h_{ie1} \parallel \frac{1}{h_{oe1}}}$$




$$\therefore \frac{V_T}{I_T} = \frac{1}{g_{m1}} \parallel h_{ie1} \parallel \frac{1}{h_{oe1}}$$

$$i_{b1} = \frac{V_T}{h_{ie1}}$$
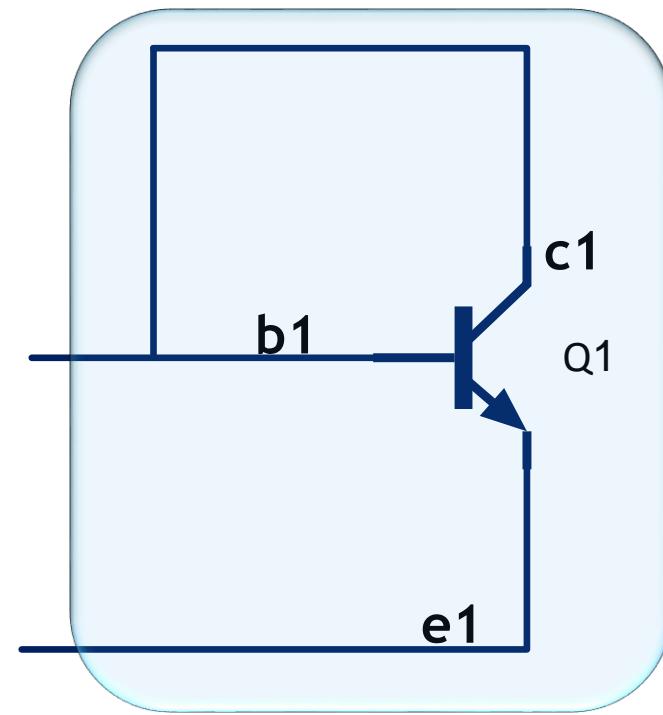
$$R_{TH} \approx \frac{1}{g_{m1}} \approx h_{ib1}$$




Two Port Model for the current mirror

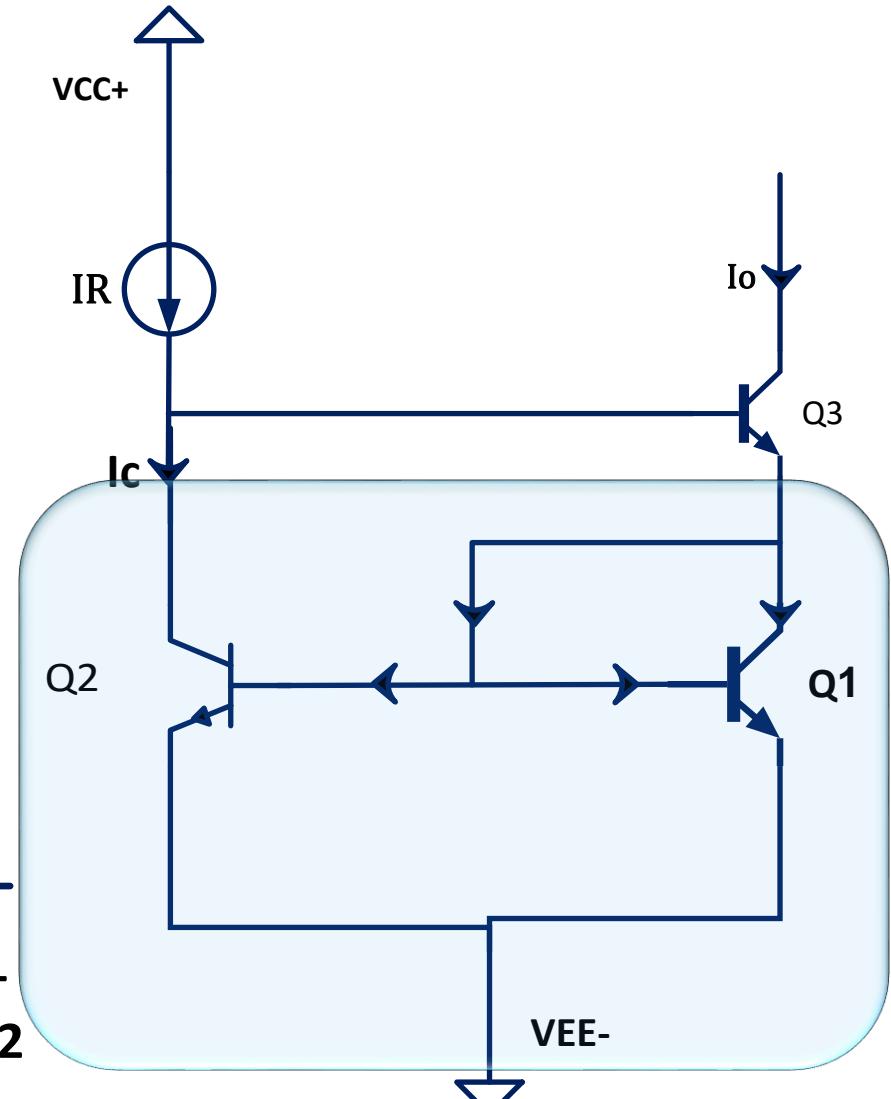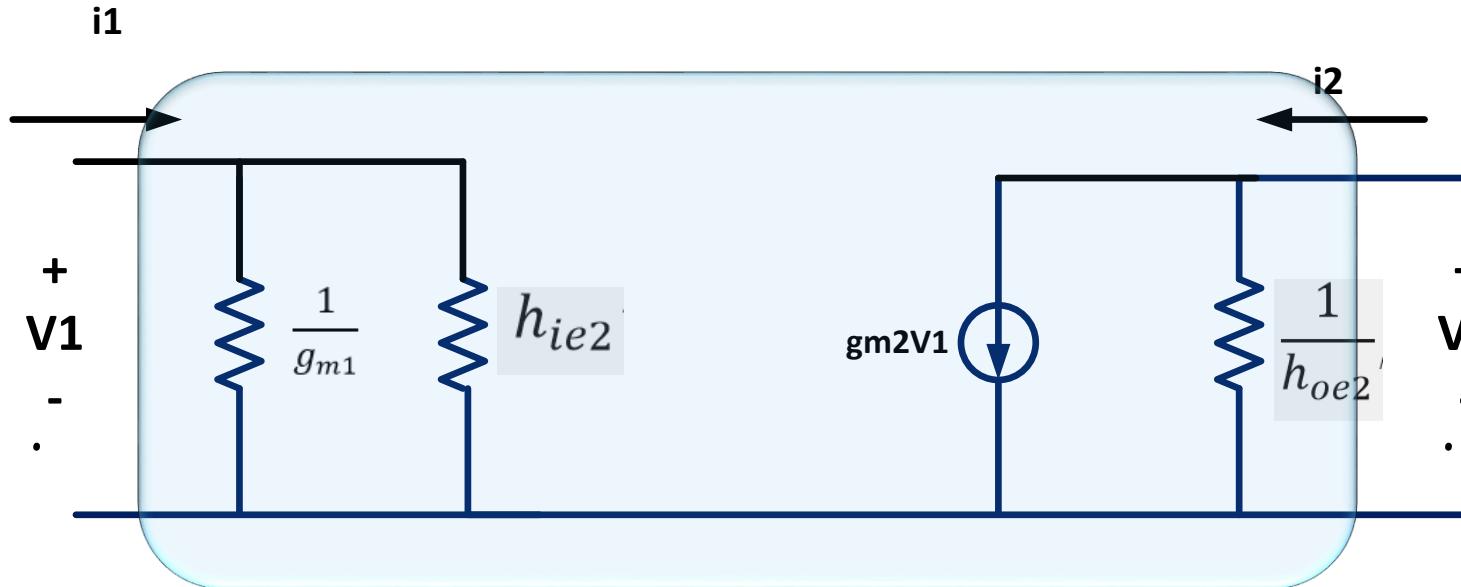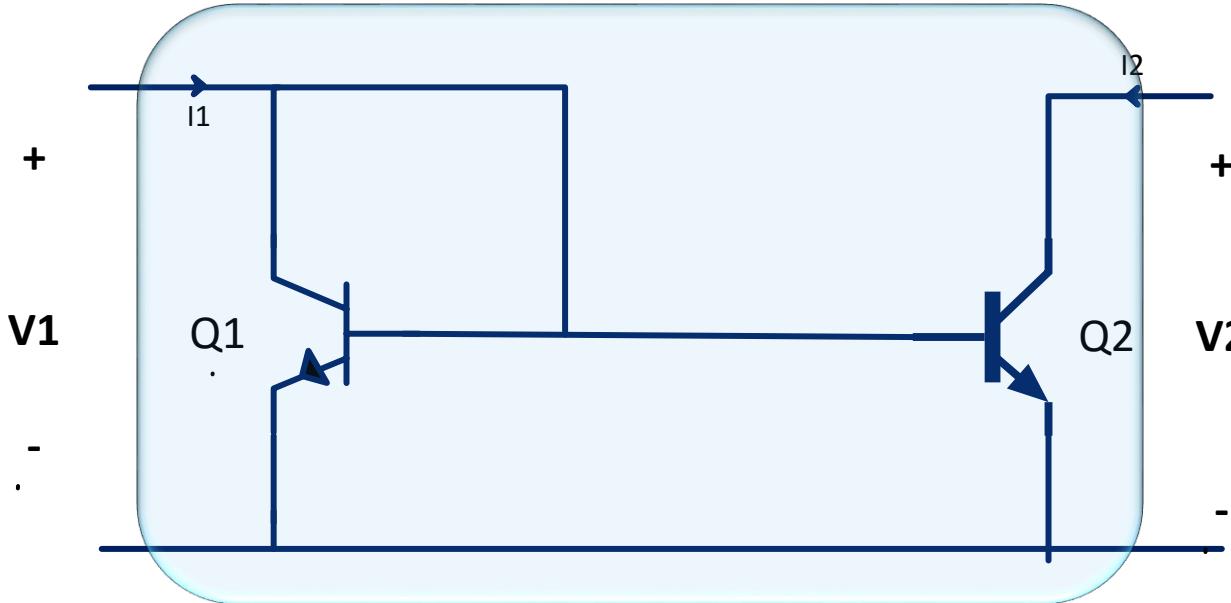

Two Port Model for the current mirror

$$V_1 = h_{11} i_1 + h_{12} V_2$$

$$i_2 = h_{21} i_1 + h_{22} V_2$$

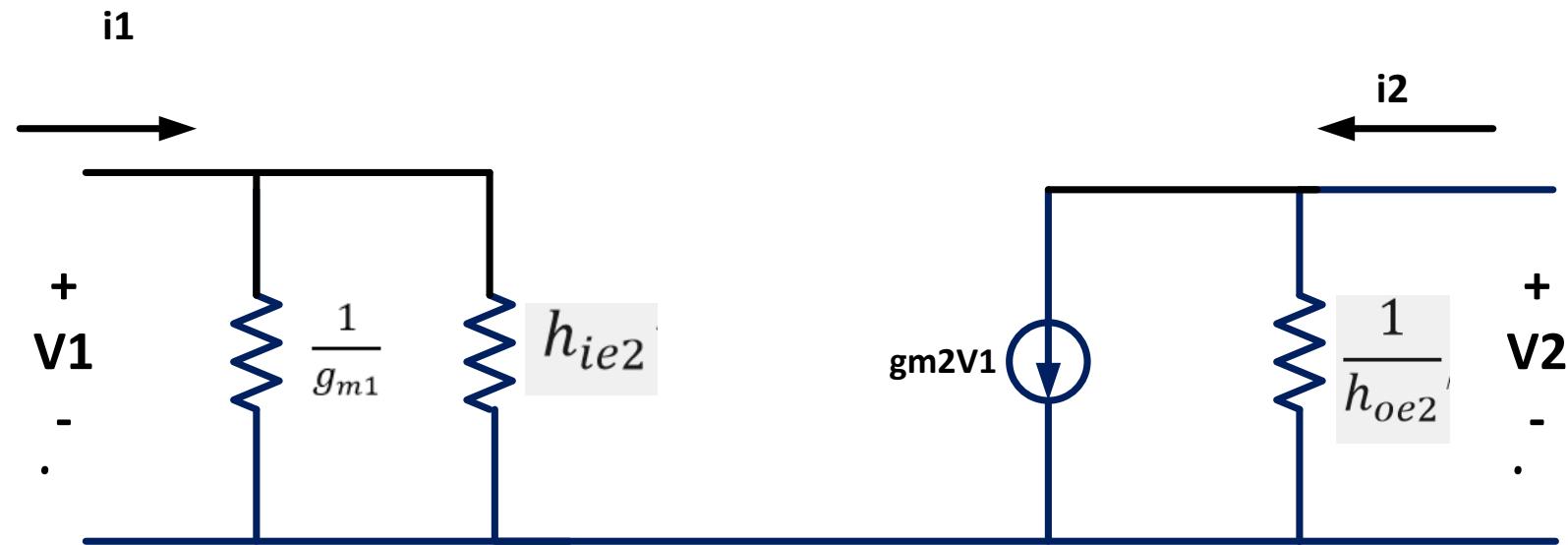




$$h_{11} = \frac{v_1}{i_1} \Big|_{v_2=0} = \frac{1}{g_{m1}} \parallel h_{ie2} \approx \frac{1}{g_{m1}}$$

$$h_{12} = \frac{v_1}{v_2} \Big|_{i_1=0} = 0$$

$$h_{21} = \frac{i_2}{i_1} \Big|_{v_2=0} = \frac{g_{m2} h_{ie2}}{1 + g_{m1} h_{ie1}} \approx \frac{g_{m2}}{g_{m1}} = 1$$

$$h_{22} = \frac{i_2}{v_2} \Big|_{i_1=0} = h_{oe2}$$

Two Port Model for the current mirror

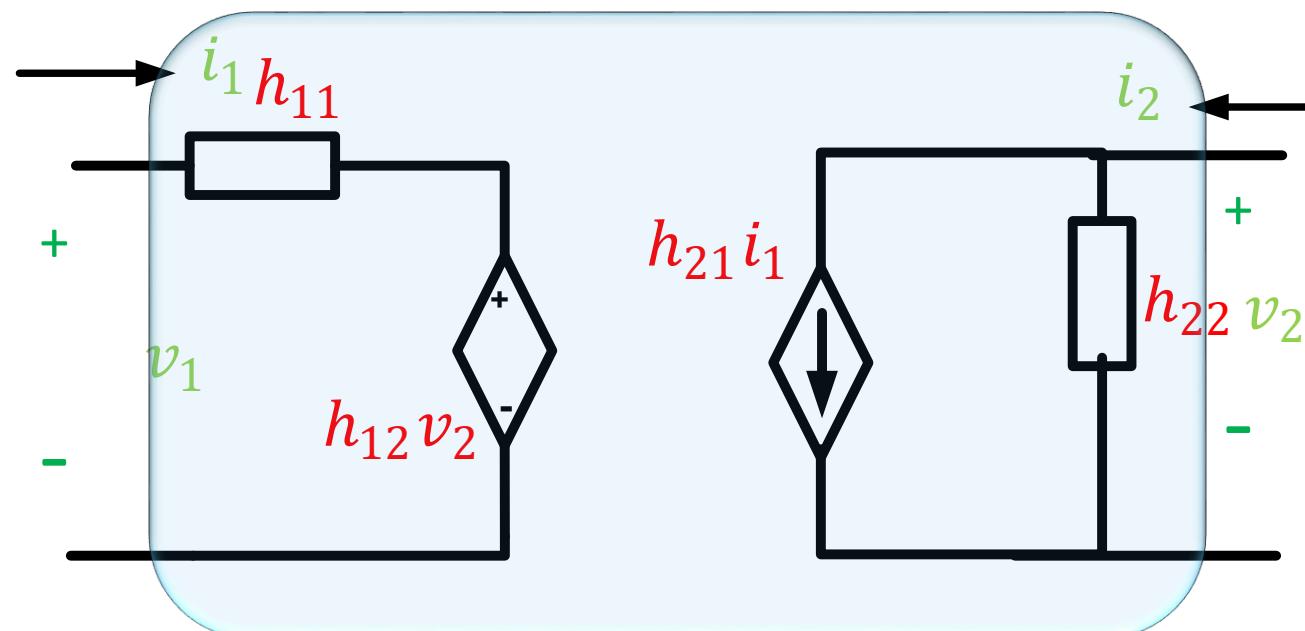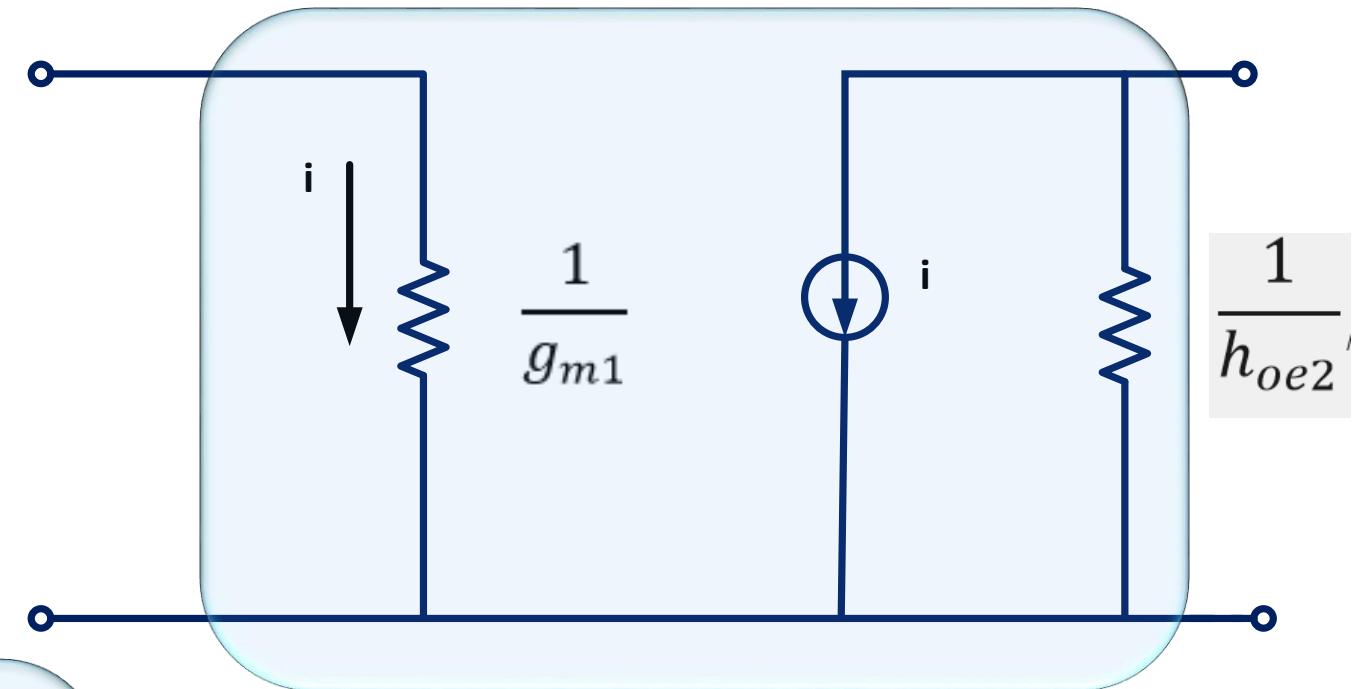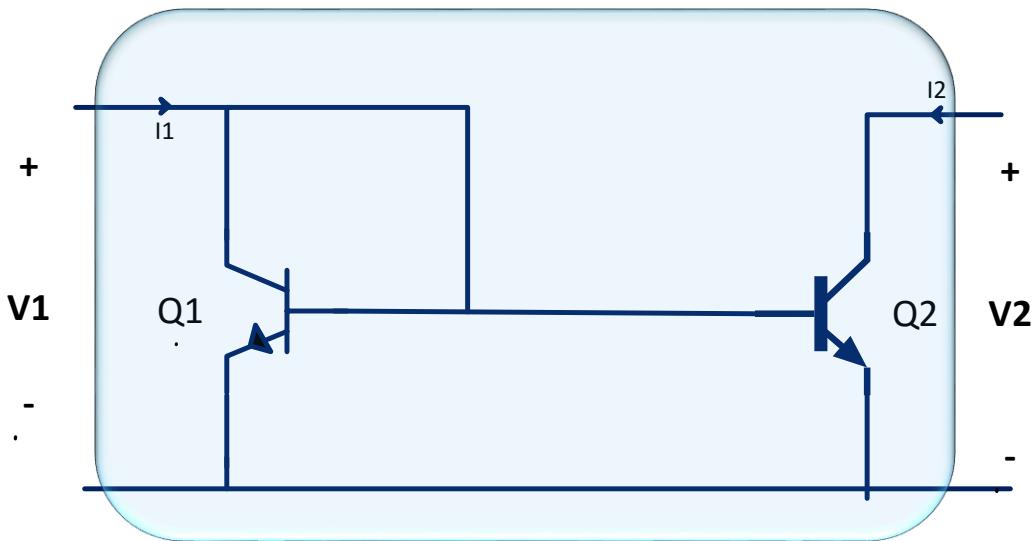

$$h_{11} = \frac{1}{g_{m1}}$$

$$h_{12} = 0$$


$$h_{21} = 1$$

$$h_{22} = h_{oe2}$$

Differential Amplifiers



The Wilson Current:

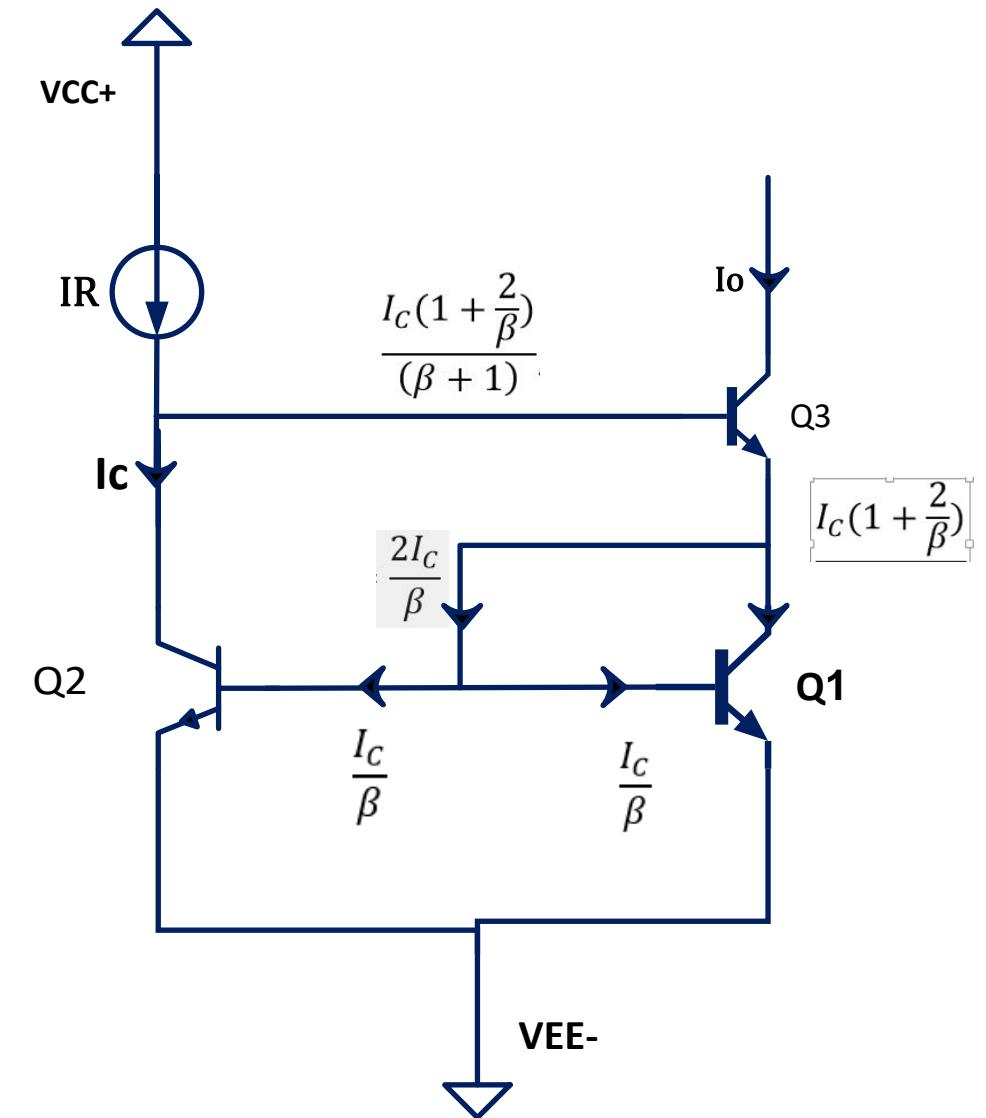
$$To \ proof \ R_o \cong \frac{h_{fe}}{2} \cdot \frac{1}{h_{oe3}}$$




Differential Amplifiers

The Wilson current mirror

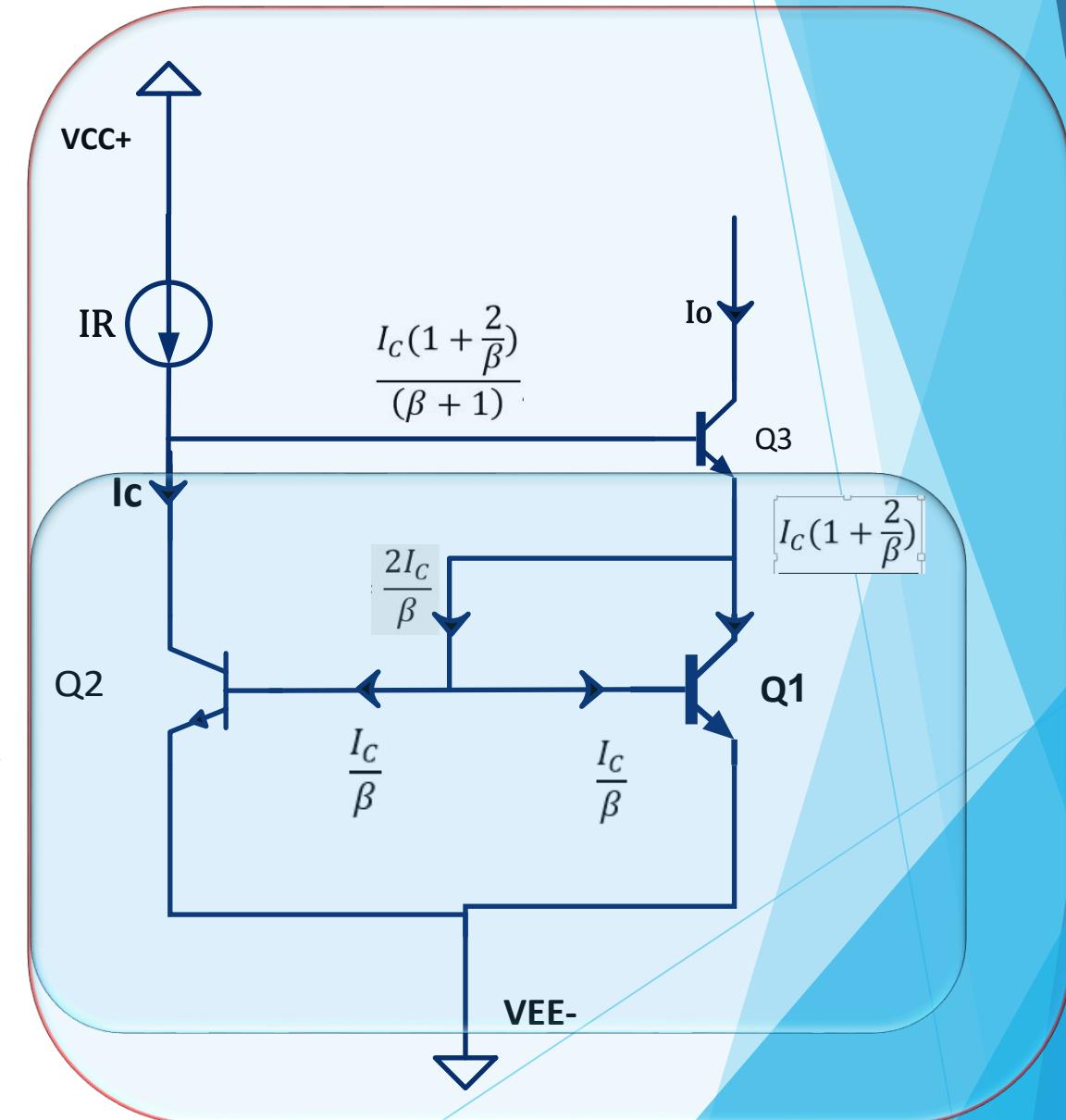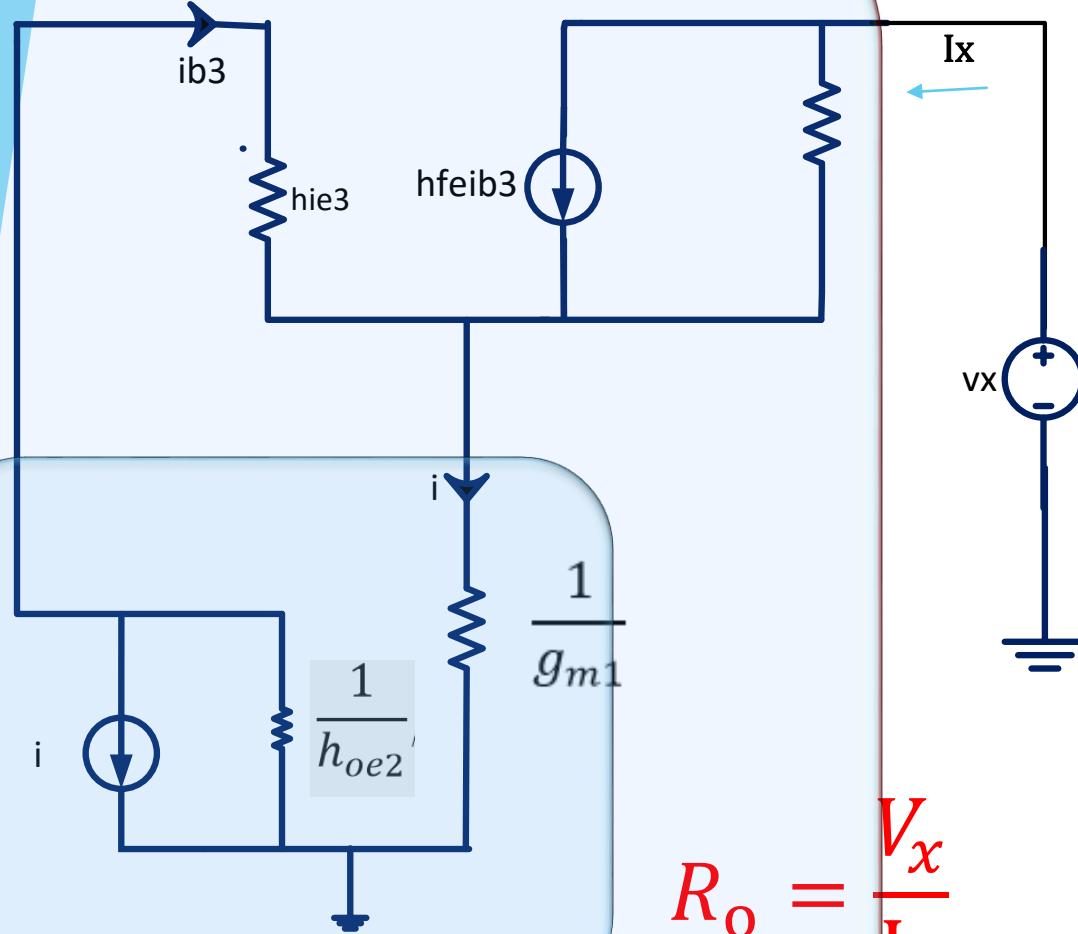

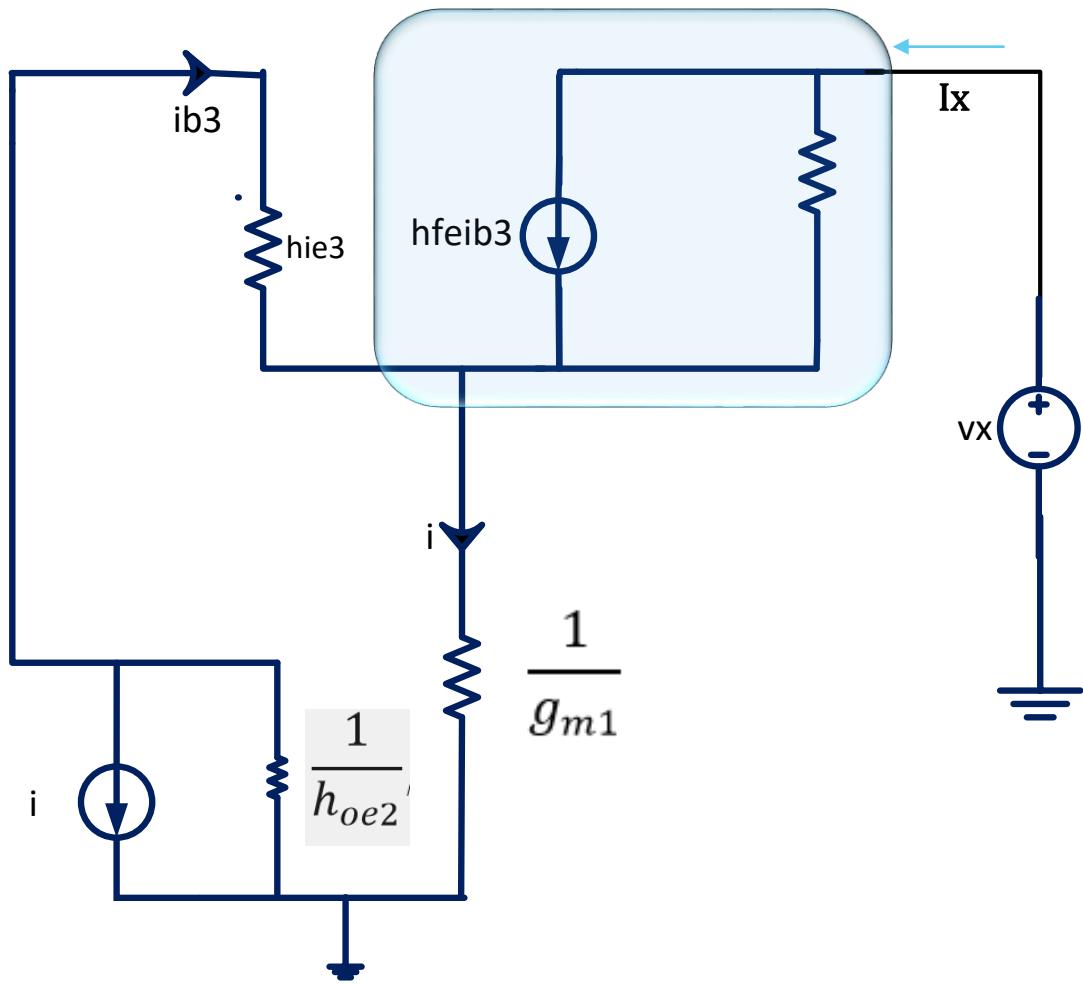

Source transformation

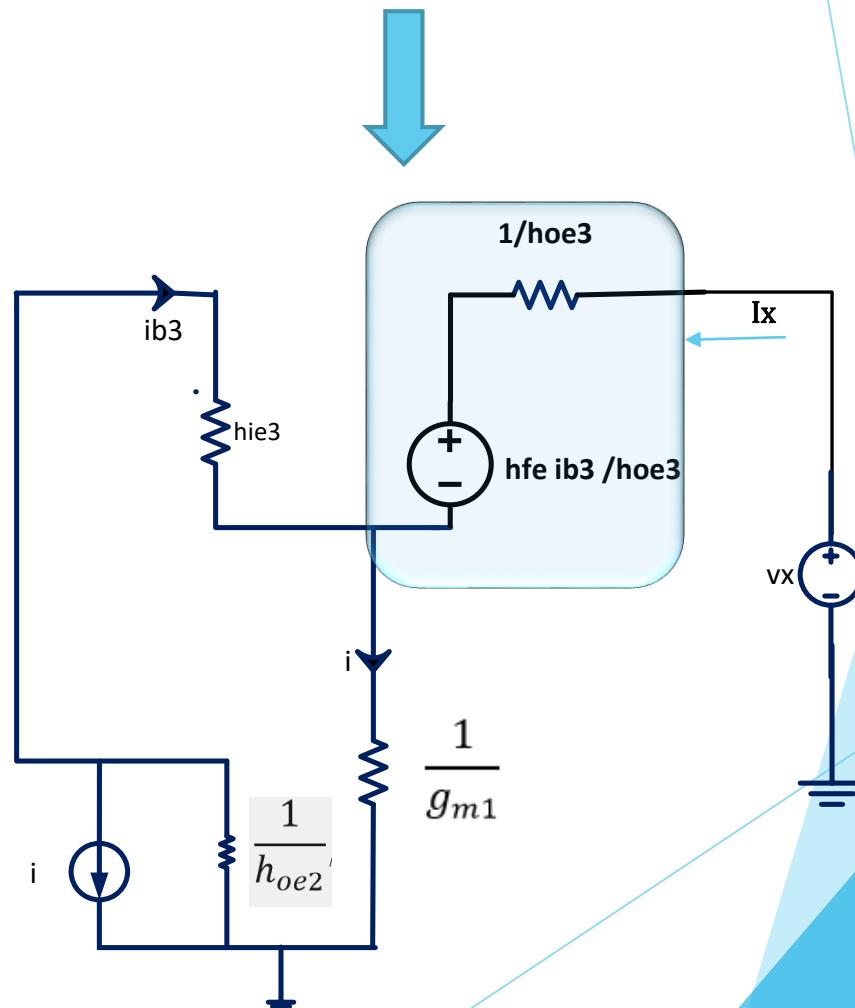

The Wilson current mirror

$$V_X + \frac{h_{fe}}{h_{oe3}} ib_3 = \left(\frac{1}{h_{oe3}} + \frac{1}{g_{m1}} \right) I_X + \frac{1}{g_{m1}} ib_3$$


$$V_X = \left(\frac{1}{h_{oe3}} + \frac{1}{g_{m1}} \right) I_X + \left(\frac{1}{g_{m1}} - \frac{h_{fe}}{h_{oe3}} \right) ib_3$$

since $\frac{1}{h_{oe3}} \gg \frac{1}{g_{m1}}$ and $\frac{h_{fe}}{h_{oe3}} \gg \frac{1}{g_{m1}}$

$$V_X = \frac{1}{h_{oe3}} I_X - \frac{h_{fe}}{h_{oe3}} ib_3 \rightarrow (1)$$

$$-\frac{i}{h_{oe2}} = \frac{1}{g_{m1}} I_X + \left(h_{ie3} + \frac{1}{g_{m1}} + \frac{1}{h_{oe2}} \right) ib_3 \rightarrow (2)$$

$$i = ib_3 + I_X \rightarrow (3)$$

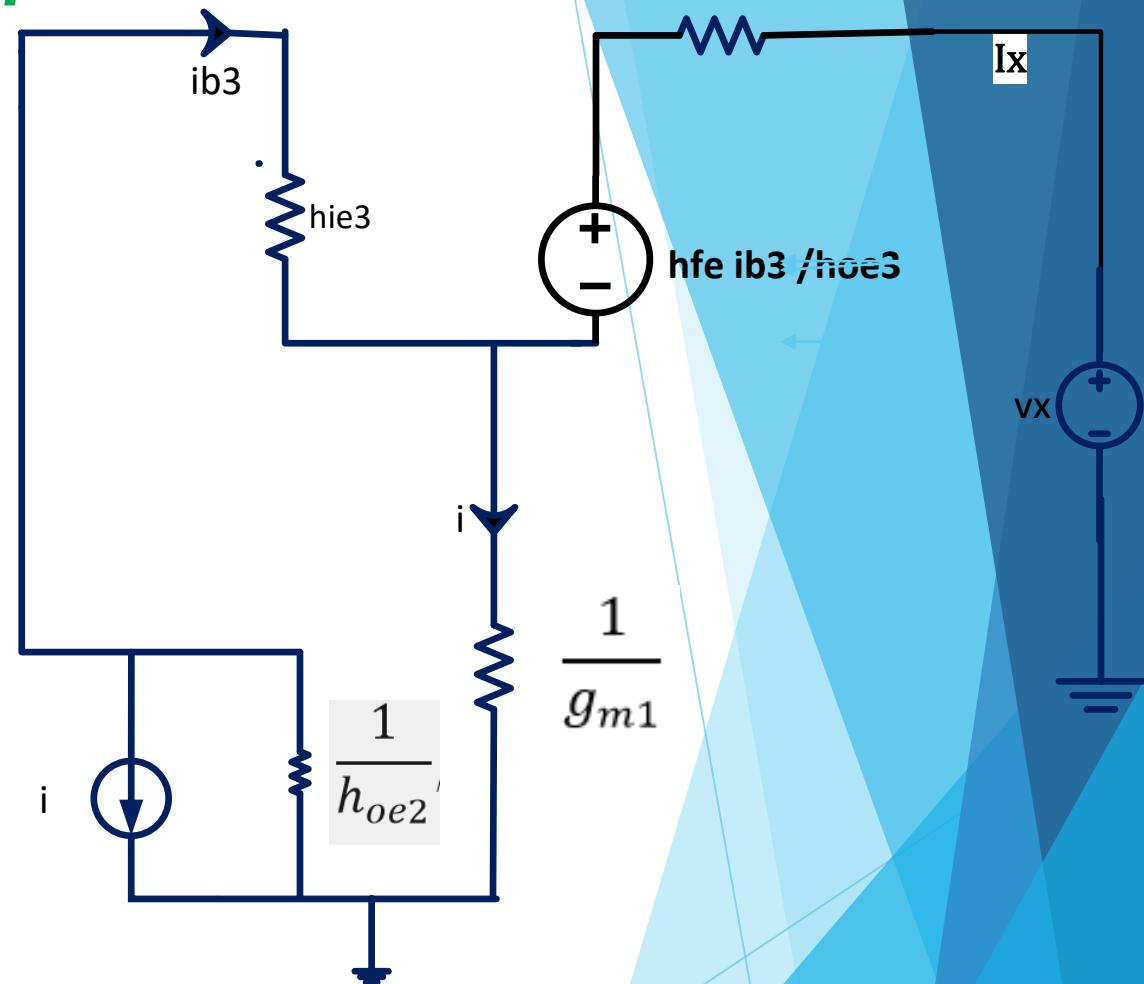


sub (3) into (2) ►

$$0 = \left(\frac{1}{h_{oe2}} + \frac{1}{g_{m1}} \right) I_X + \left(\frac{1}{g_{m1}} + h_{ie3} + \frac{2}{h_{oe2}} \right) i b_3 ►$$

since $\frac{1}{h_{oe2}} \gg \frac{1}{g_{m1}}$ and $\frac{2}{h_{oe2}} \gg \frac{1}{g_{m1}} + h_{ie3}$ ►
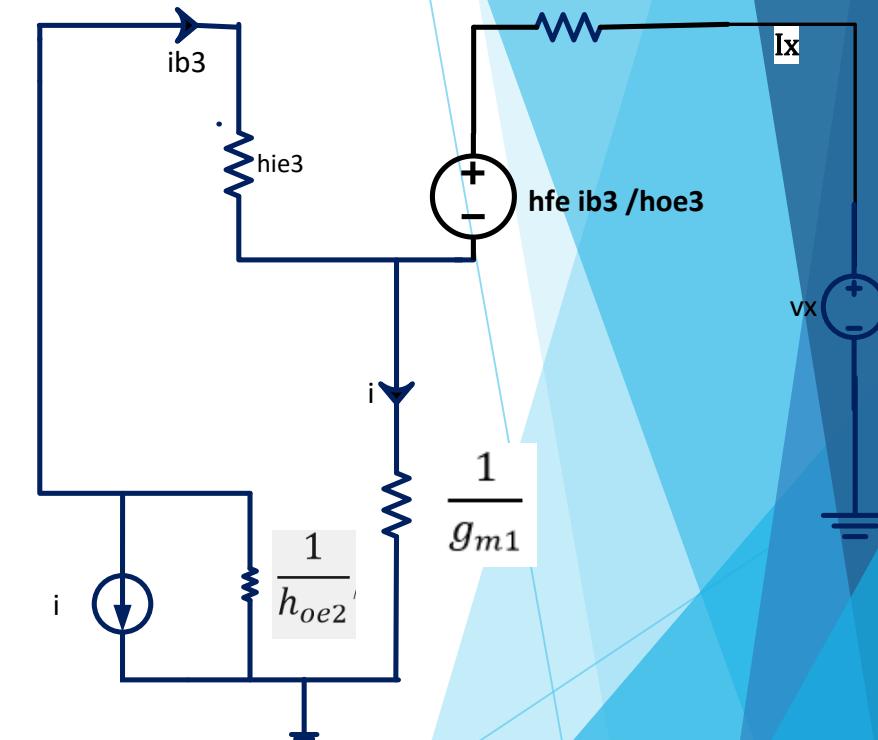
$$0 = \frac{1}{h_{oe2}} I_X + \frac{2}{h_{oe2}} i b_3 \rightarrow (4) ►$$



The Wilson current mirror


$$V_X = \frac{1}{h_{oe3}} I_X - \frac{h_{fe}}{h_{oe3}} i_{b3} \rightarrow (1)$$

using (4) we get $i_{b3} = -\frac{I_X}{2}$

$$\therefore V_X = \frac{1}{h_{oe3}} I_X + \frac{h_{fe}}{2} \frac{1}{h_{oe3}} I_X$$

$$\therefore \frac{V_X}{I_X} = \left(\frac{h_{fe}}{2} + 1 \right) \frac{1}{h_{oe3}}$$
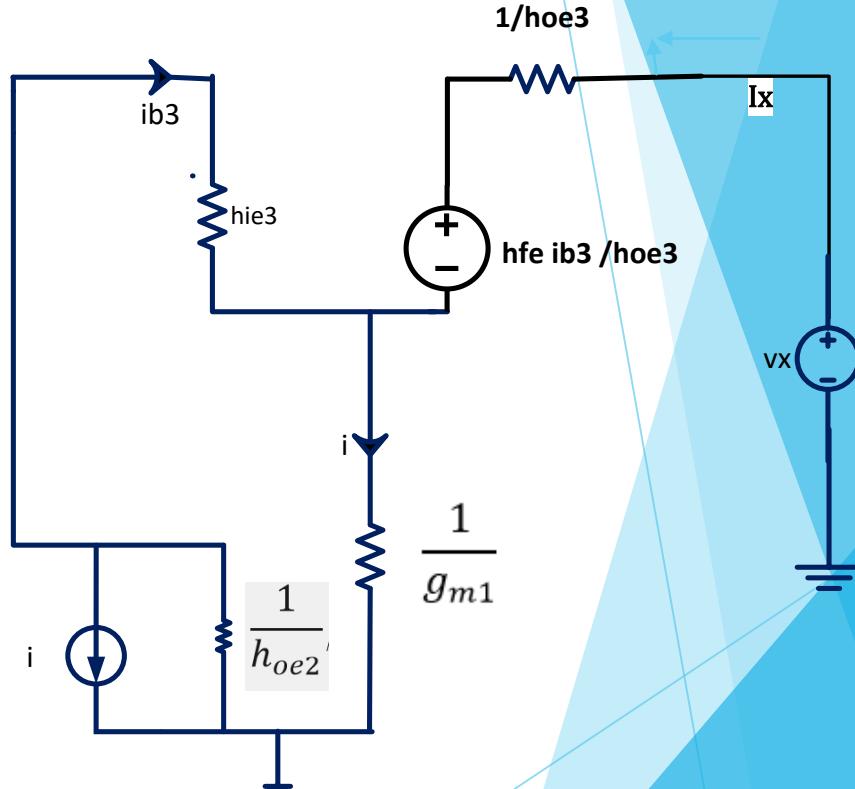
$$\therefore R_o = \frac{V_X}{I_X} \approx \frac{h_{fe}}{2} \frac{1}{h_{oe3}}$$



4. Widlar Current Source:


- To Produce Very small I_o
- To increase R_o

$$KVL : V_{BE1} = V_{BE2} + R_E I_{E2}$$

$$V_T \ln \frac{I_{C1}}{I_{S1}} = V_T \ln \frac{I_{C2}}{I_{S2}} + R_E I_{E2}$$

$$V_T \ln \frac{I_{C1}}{I_{S1}} - V_T \ln \frac{I_{C2}}{I_{S2}} = R_E I_{E2}$$

if Q_1 and Q_2 are matched

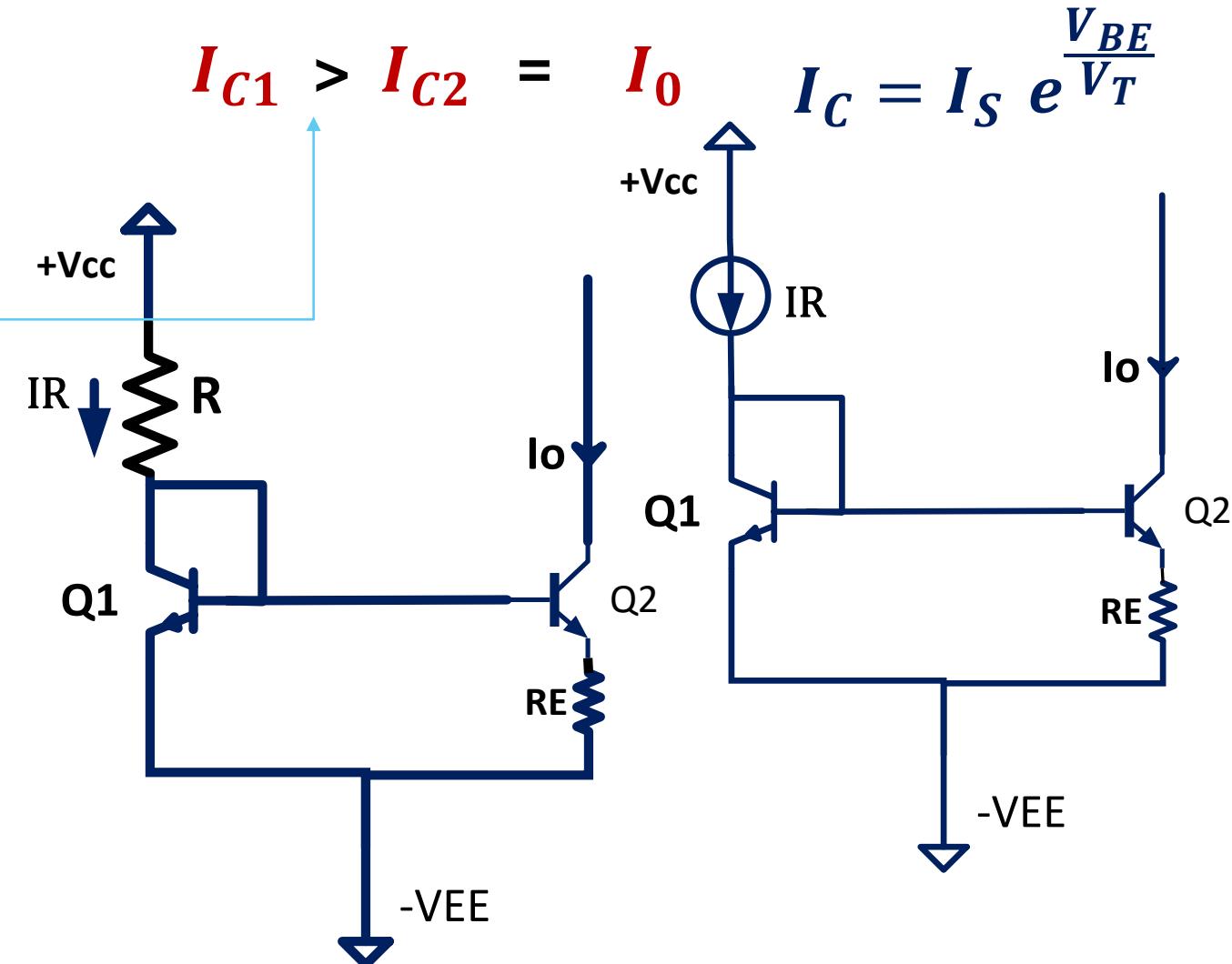


$$V_T \ln \frac{I_{C1}}{I_{C2}} = R_E I_{E2}$$

$$V_T \ln \frac{I_{C1}}{I_{C2}} = R_E I_{E2}$$

if $\beta = \infty$



$$V_T \ln \frac{I_R}{I_0} = R_E I_O$$
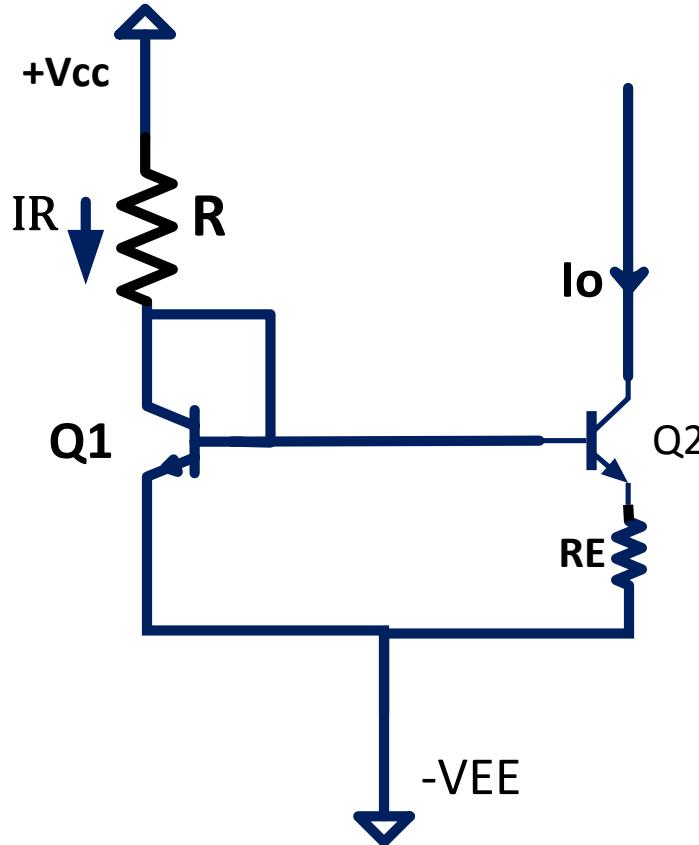
$$I_R = \frac{V_{CC} + V_{EE} - V_{BE1}}{R}$$



4. Widlar Current Source:

- To Find R_o :

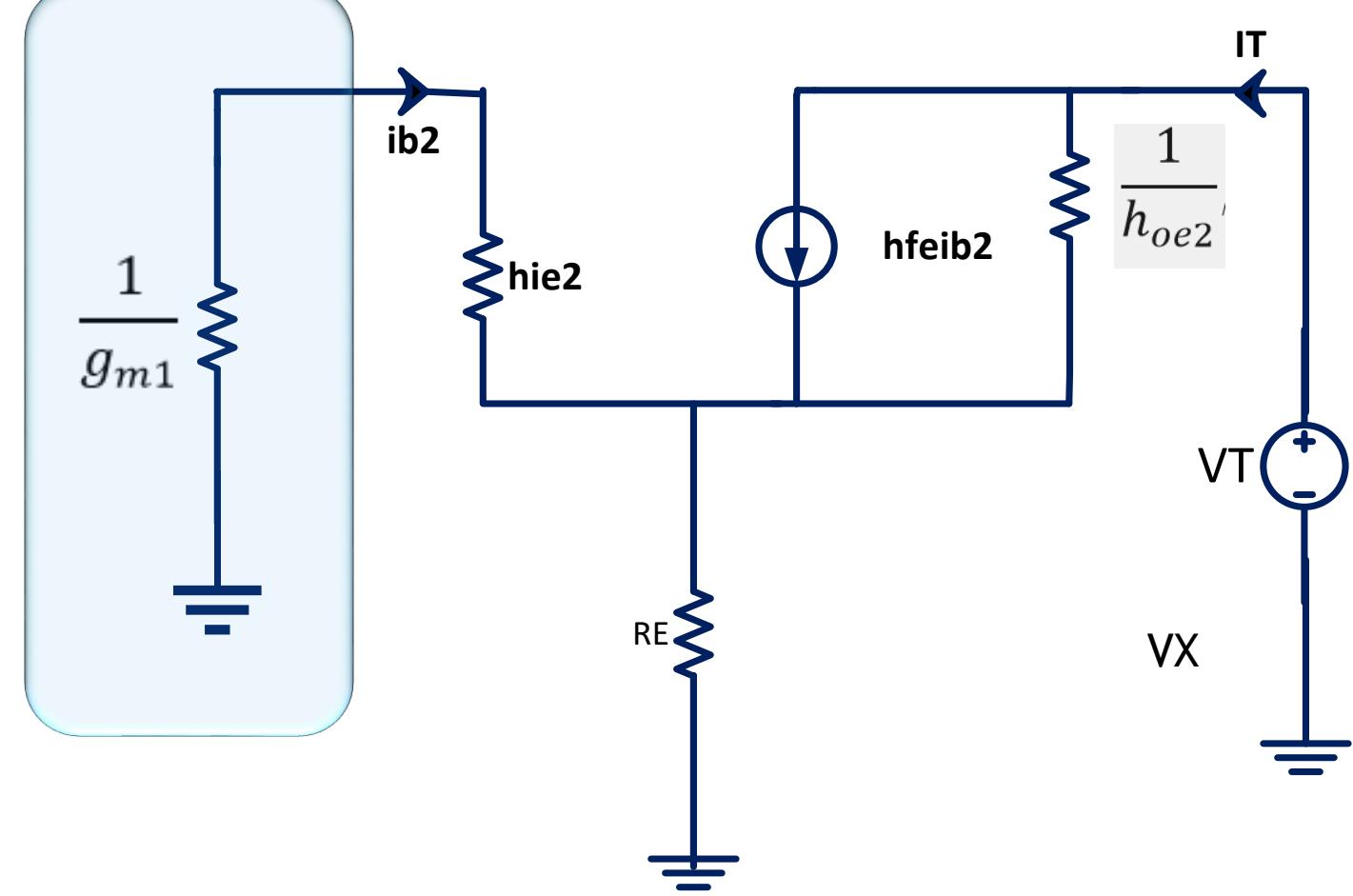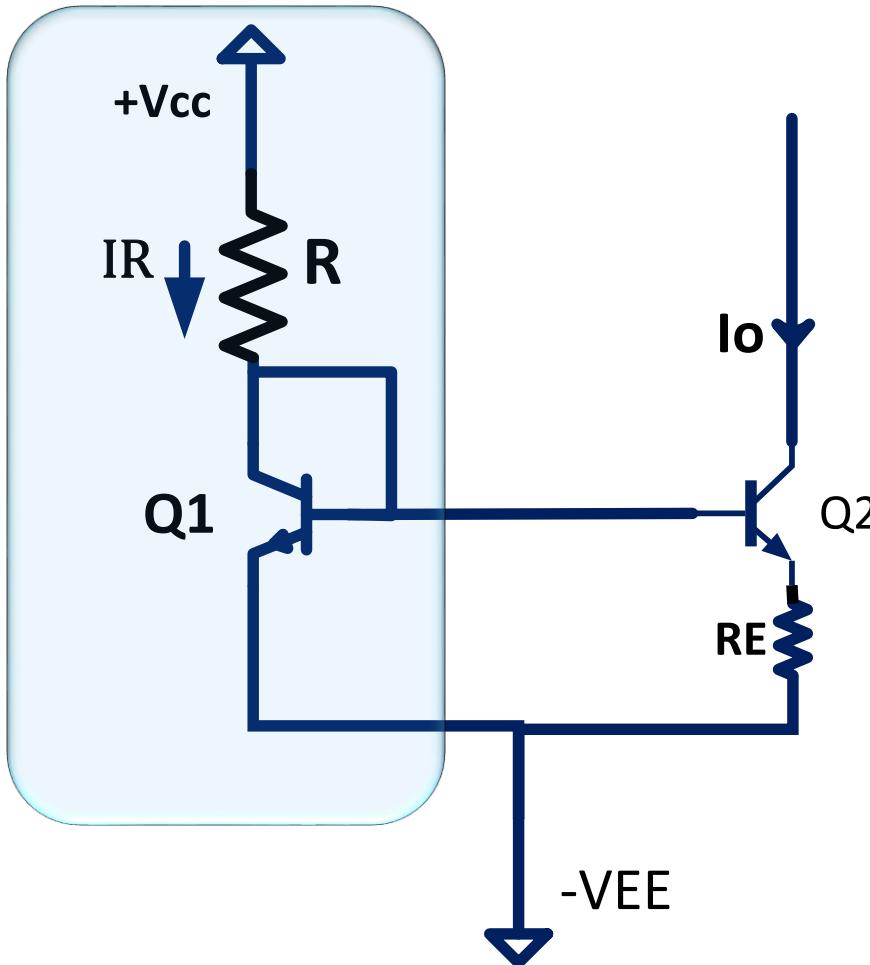

$$R_o \approx \frac{1}{h_{oe2}} + \frac{h_{fe}}{h_{oe2}} \frac{R_E}{R_E + h_{ie2} + \frac{1}{gm1}}$$

Design a simple current mirror to generate $I_o = 10\mu A$
given that $V_{BE} = 0.7 V @ 1mA$

Assume $B = \infty$, $V_{CC} = 10V$ and $V_{EE} = 0V$


We need to find the value of V_{BE} @ $10\mu A$

$$V_{BE} = V_T \ln \frac{I_C}{I_S}$$

$$V_{BE2} - V_{BE1} = V_T \ln \frac{I_{C2}}{I_{C1}}$$

$$V_{BE2} = V_{BE1} + V_T \ln \frac{I_{C2}}{I_{C1}}$$
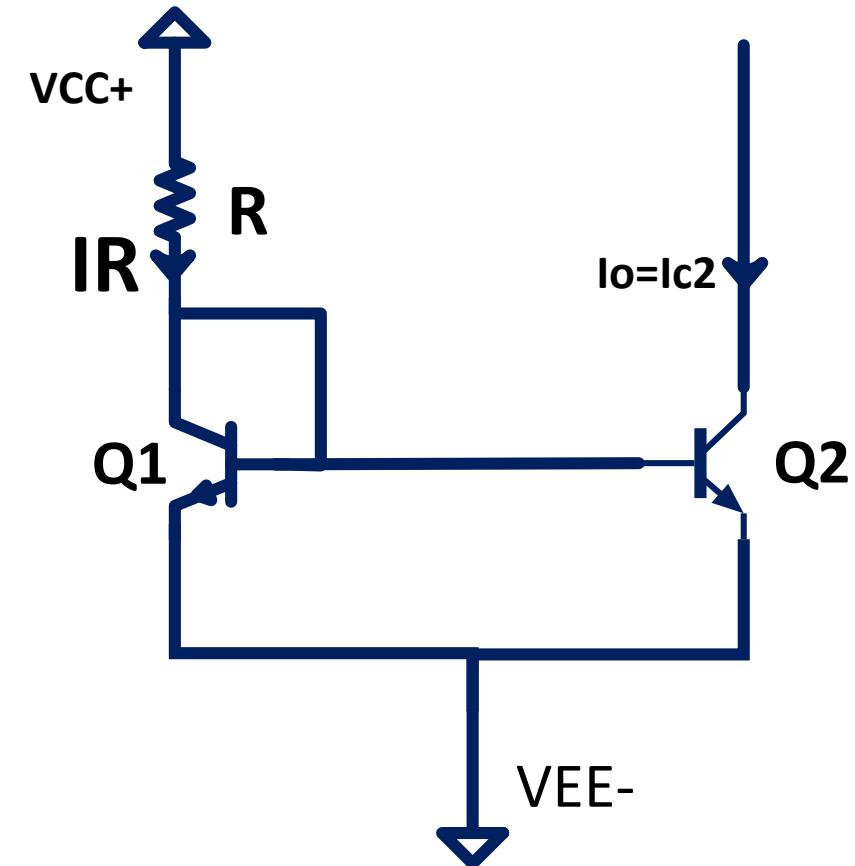
$$= 0.7 + V_T \ln \frac{10HA}{1mA}$$
$$= 0.58 V$$



Differential Amplifiers

Design a simple current mirror to generate $I_o = 10\mu A$ given that $V_{BE} = 0.7 V @ 1mA$

Assume $B = \infty$, $V_{CC} = 10V$ and $V_{EE} = 0V$

$$V_{BE} = 0.7 V @ I_C = 1mA$$


$$V_{BE} = 0.58 V @ I_C = 10\mu A$$

$$KVL : V_{CC} = R I_R + V_{BE}$$

since $\beta = \infty$

$$I_R = I_o = 10\mu A$$

$$\therefore R = 942K$$

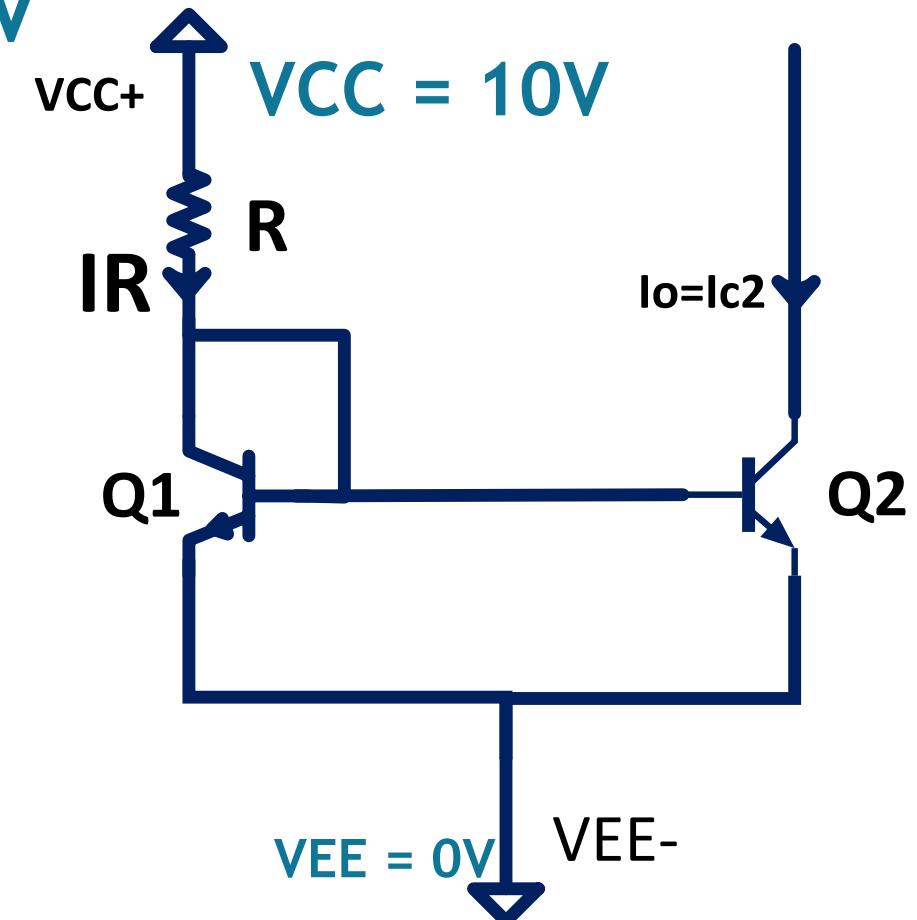

Too Large , Not Practical

Design a Wedlar current source to generate $I_o = 10\mu A$

given that $V_{BE} = 0.7 V @ I_c=1mA$

Assume $B=\infty$, $V_{CC} = 10V$ and $V_{EE} = 0V$


Assume that $I_R = 1mA$

$$\therefore V_{BE1} = 0.7 V$$

$$R = \frac{V_{CC} - V_{BE1}}{I_R} = 9.3k$$

$$I_o R_E = V_T \ln \frac{I_R}{I_o}$$


$$\therefore R_E = 11.5k$$

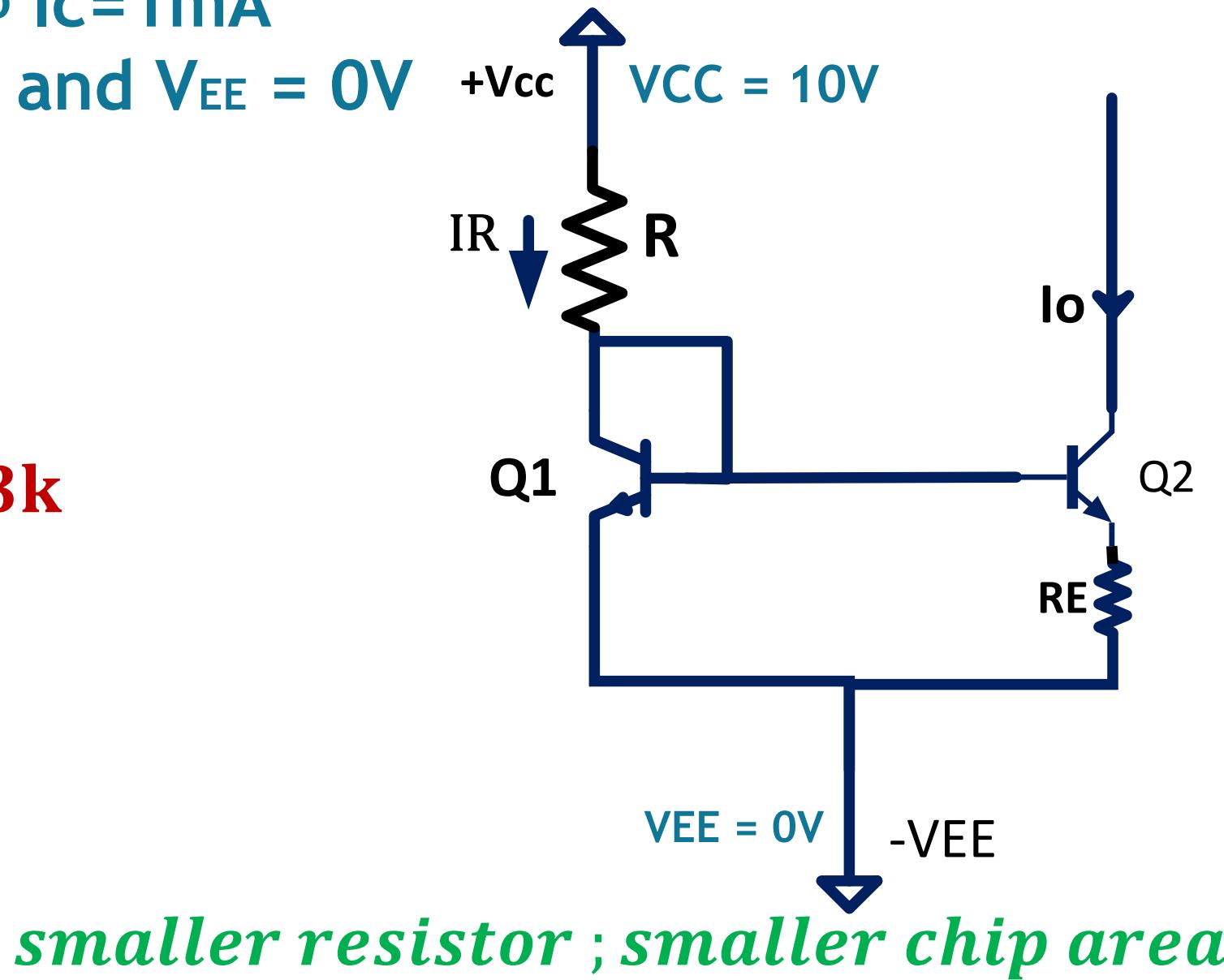

Multitransistor Current Mirror

If β is finite and all the transistors are matched:
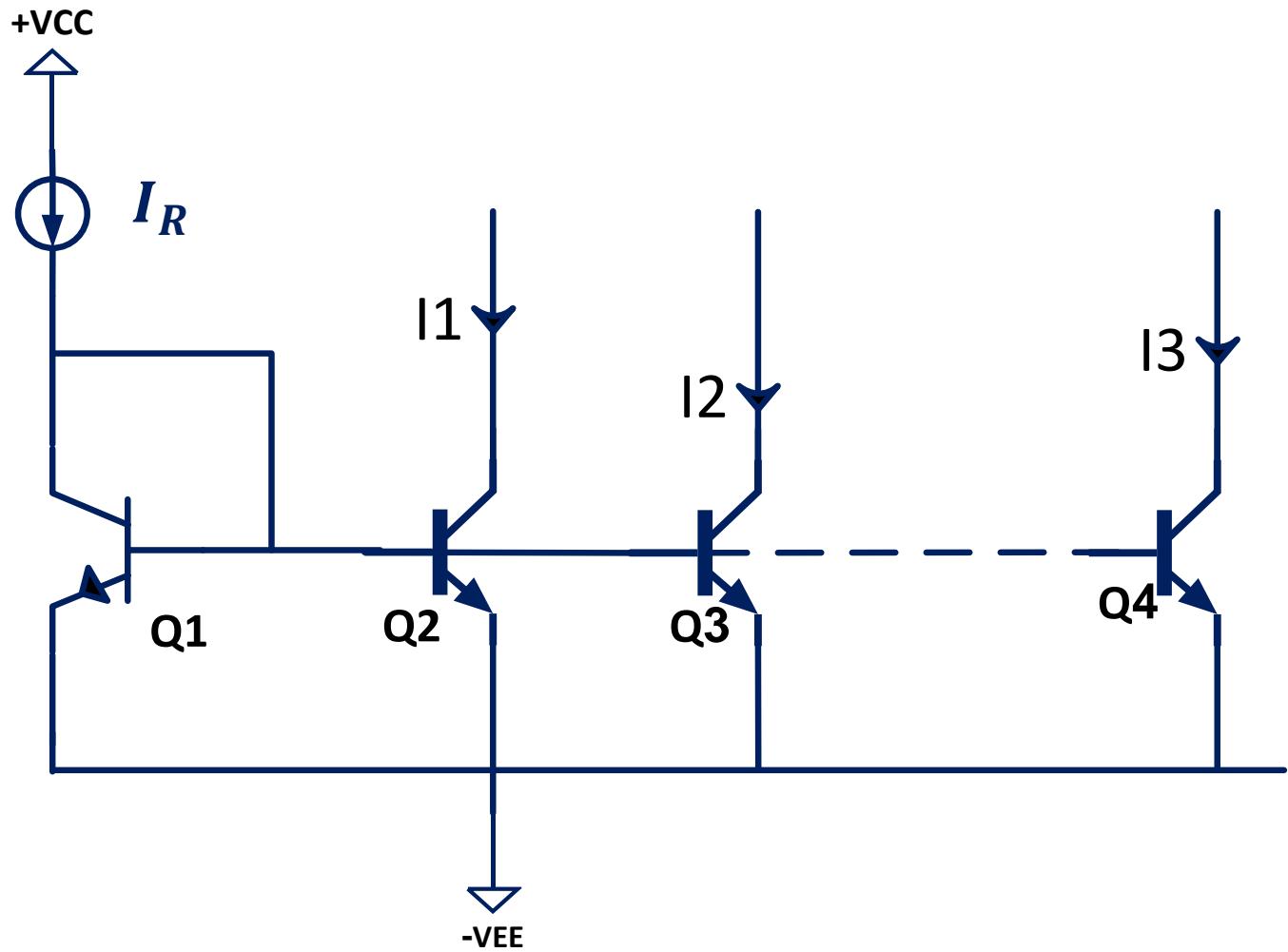
$$I_1 = I_2 = I_3 = \frac{I_R}{1 + \frac{(N + 1)}{\beta}}$$



Generalized Current Mirror


To Generate bias currents for different amplifier stages in an IC

$$I_R = \frac{V_{CC} + V_{EE} - V_{EB1} - V_{BE2}}{R}$$

if $\beta \rightarrow \infty$

Since $|VBE|$ For all the transistors are equal

$$I_1 = I_R ; I_2 = 2I_R ; I_4 = 3I_R$$

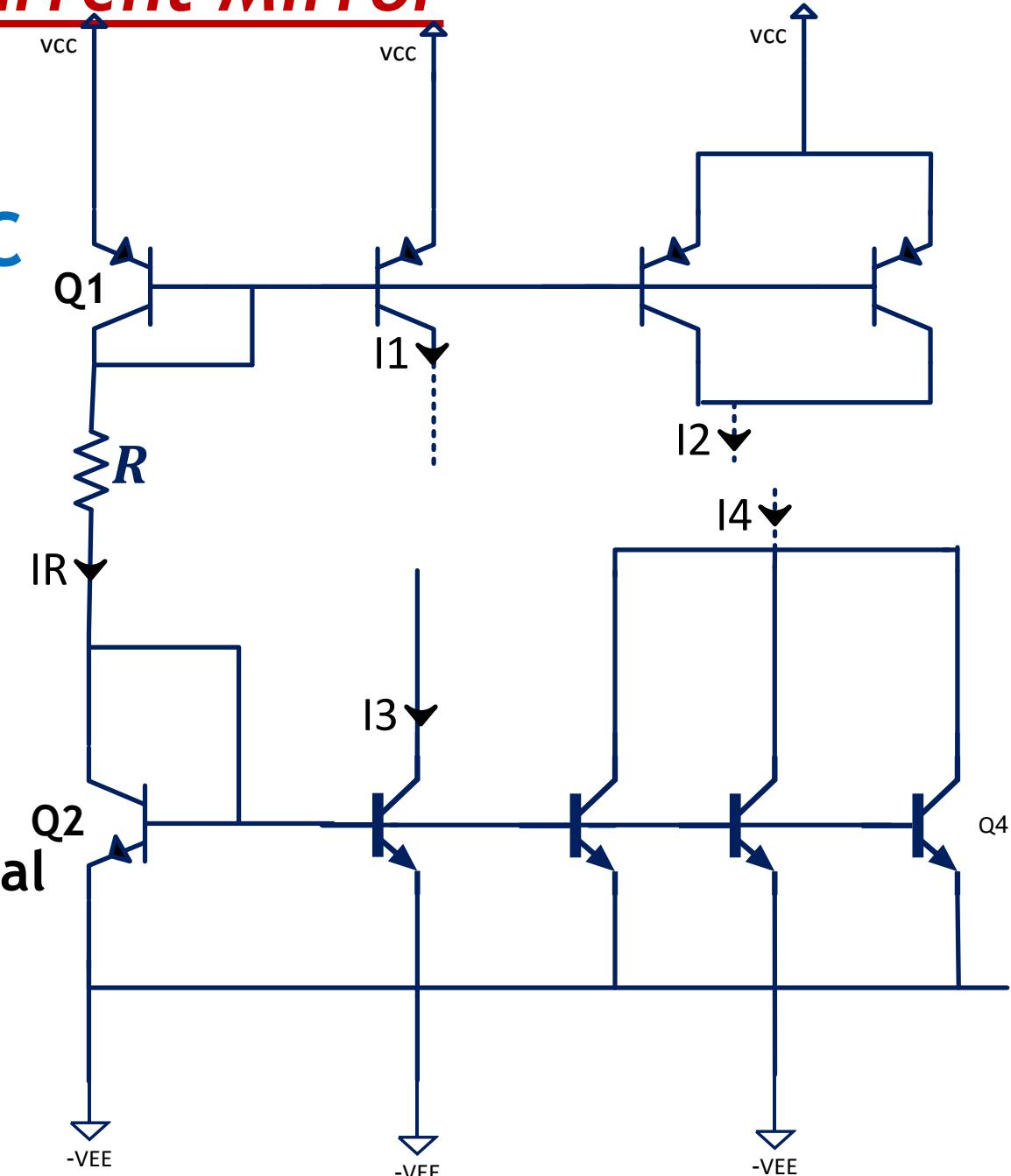

Mosfet Current Sources:

The Basic mosfet Current Source


Since $V_{G1} = V_{D1}$ and $V_{GS} = V_D$ so
 $|V_{DS}| > |V_{GS} - V_T|$

$\therefore Q1$ is operated in the pinch off region

$$I_{DS1} = \frac{1}{2} \bar{K}_{n1} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_T)^2$$

$$I_o = I_{DS2} = \frac{1}{2} \bar{K}_{n2} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_T)^2$$
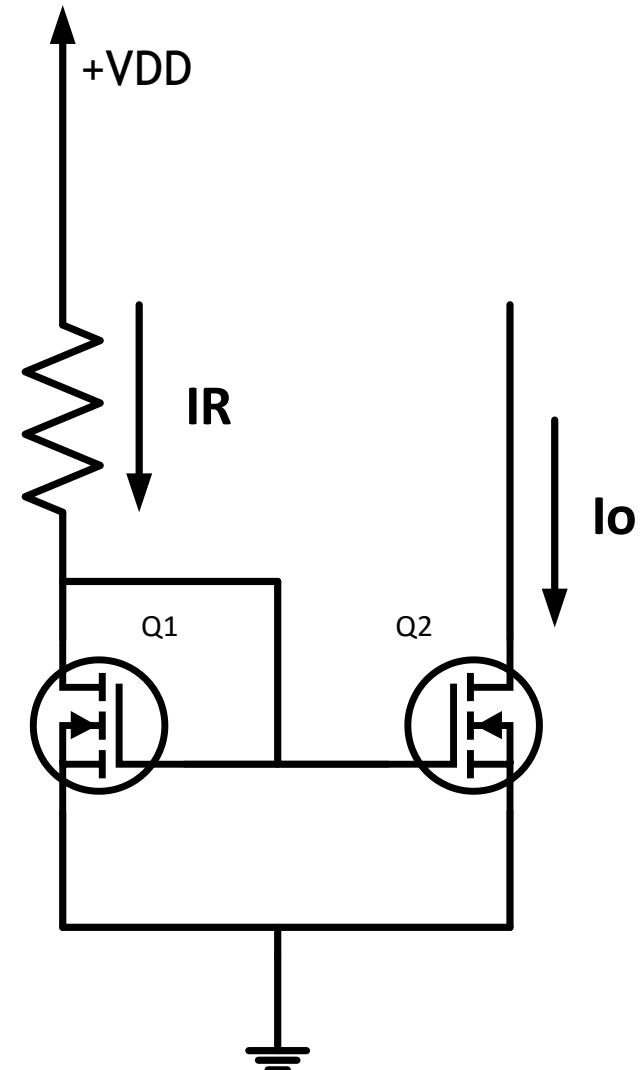
$$I_R = I_{DS1} + I_{G1} + I_{G2} = I_{DS1}$$




$$I_R = I_{DS1} = \frac{1}{2} \bar{K}_{n1} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_T)^2$$

$$I_o = I_{DS2} = \frac{1}{2} \bar{K}_{n2} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_T)^2$$

*Since $V_{GS1} = V_{GS2}$
and $V_{T1} = V_{T2}$, and $\bar{K}_{n1} = \bar{K}_{n2}$*
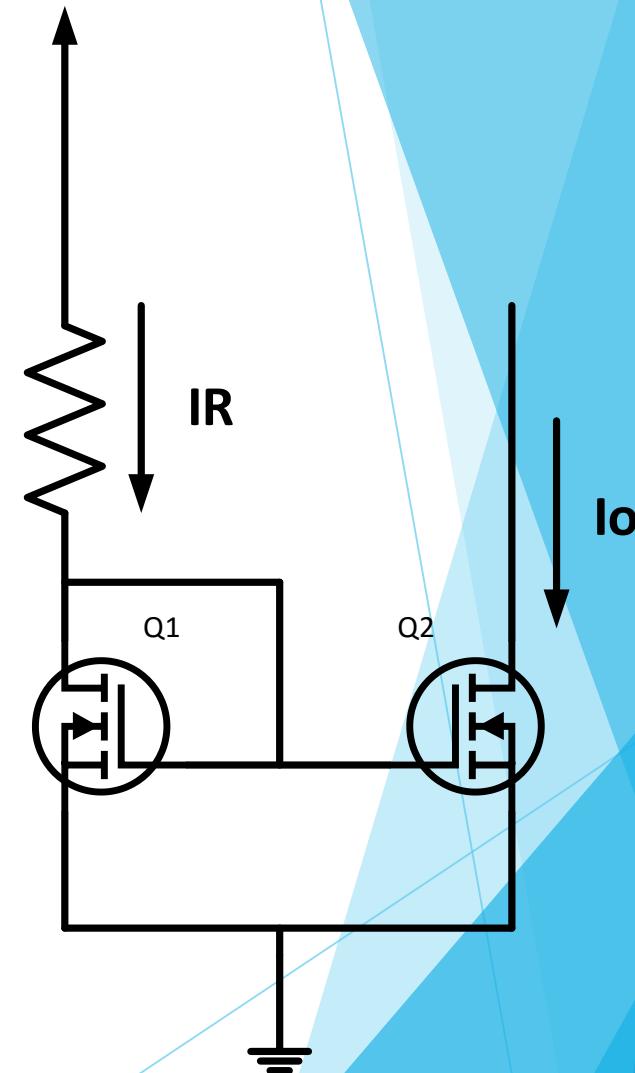
$$\therefore \frac{I_o}{I_R} = \frac{\left(\frac{W}{L} \right)_2}{\left(\frac{W}{L} \right)_1} \equiv \text{current gain}$$




Mosfet Current Sources:

The Basic mosfet Current Source





If we have matched Transistors

$$\frac{I_o}{I_R} = 1$$

$I_o = I_R$ current mirror

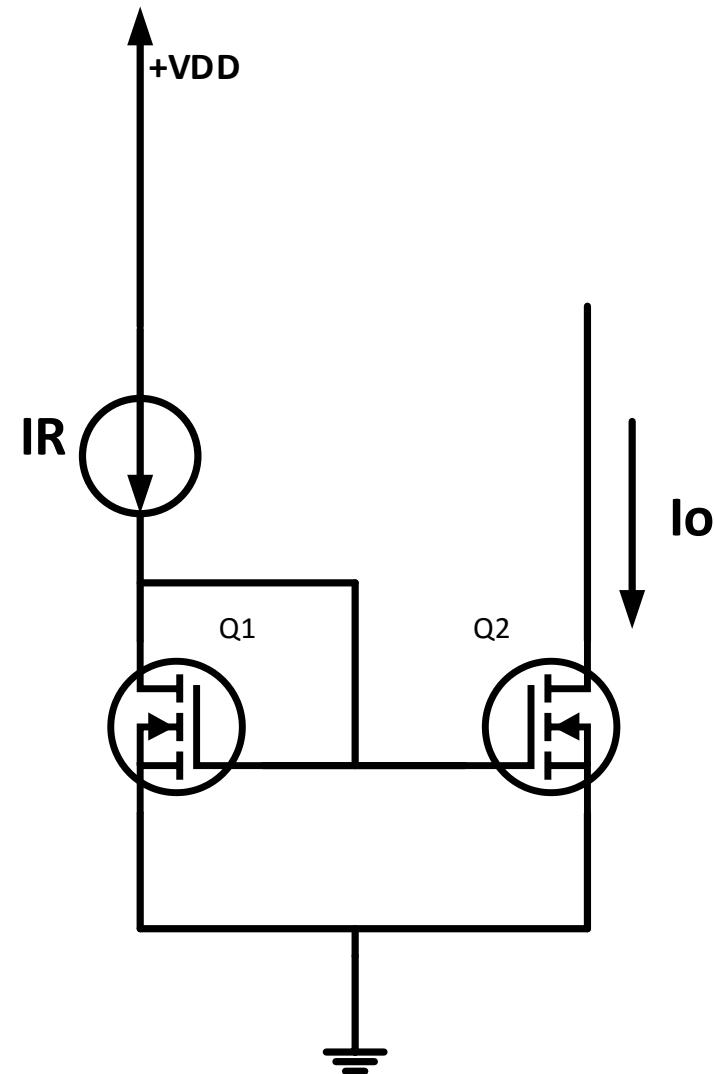


Mosfet Current Sources:

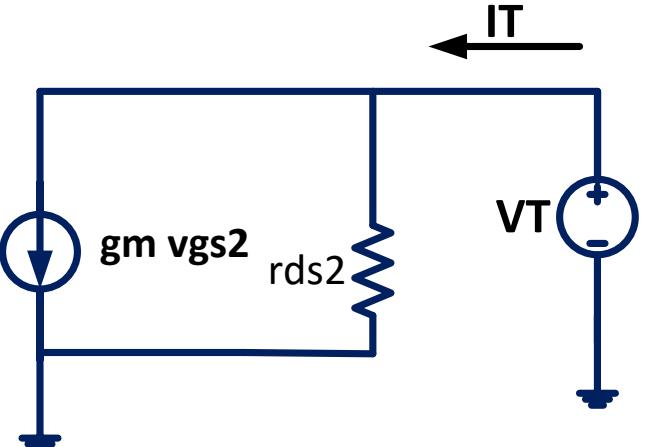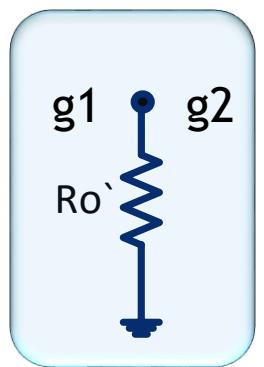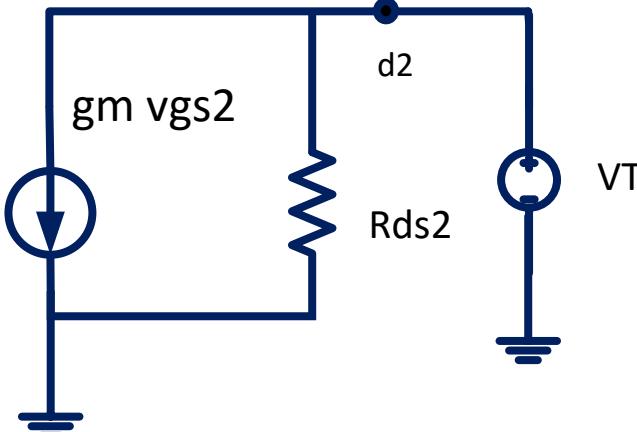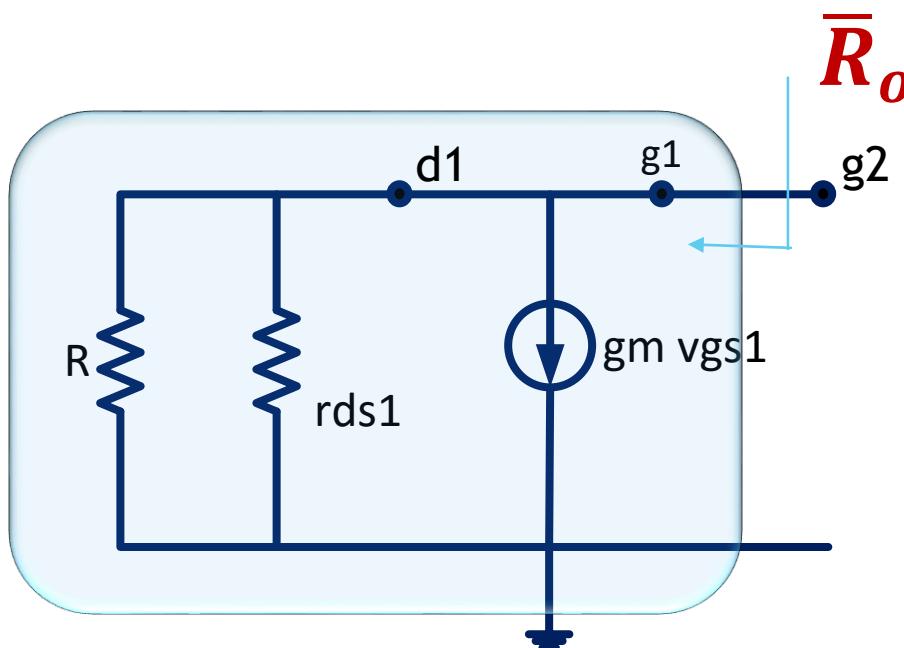

$$\bar{R}_o = \frac{1}{g_{m1}} \parallel R \parallel r_{ds1}$$

$$R_o = \frac{V_T}{I_T} = r_{ds2}$$

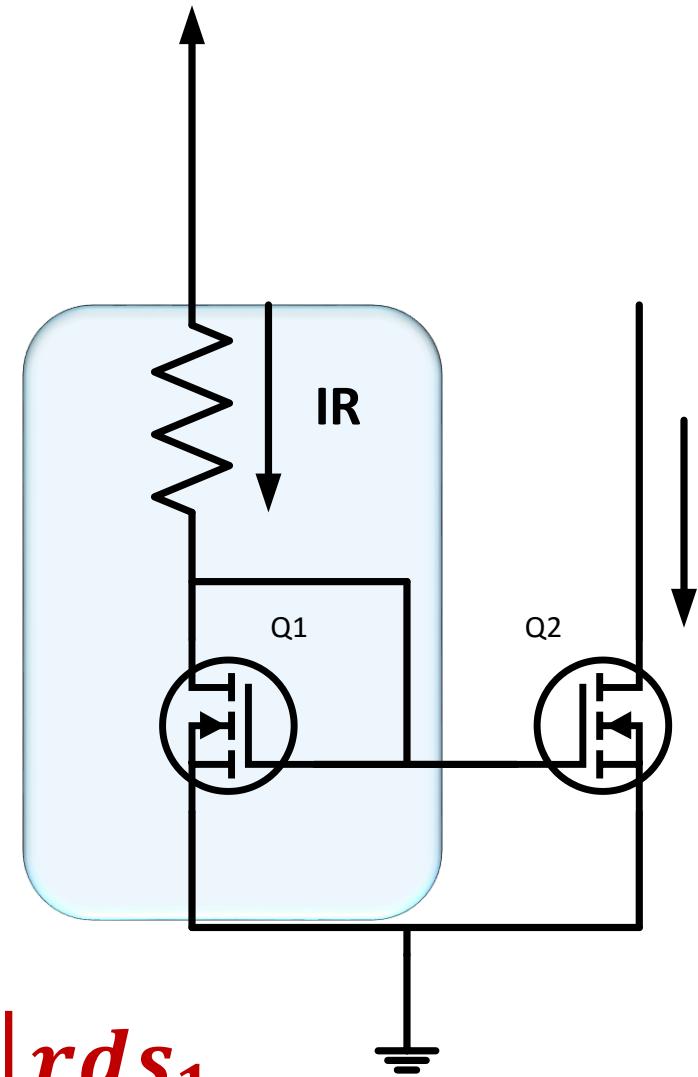


Mosfet Current Sources:

The Wilson mosfet current mirror

Q_1, Q_2 are matched




$$\therefore I_o = I_R$$

$$R_o \cong gm_3 r_{ds3} r_{ds2}$$

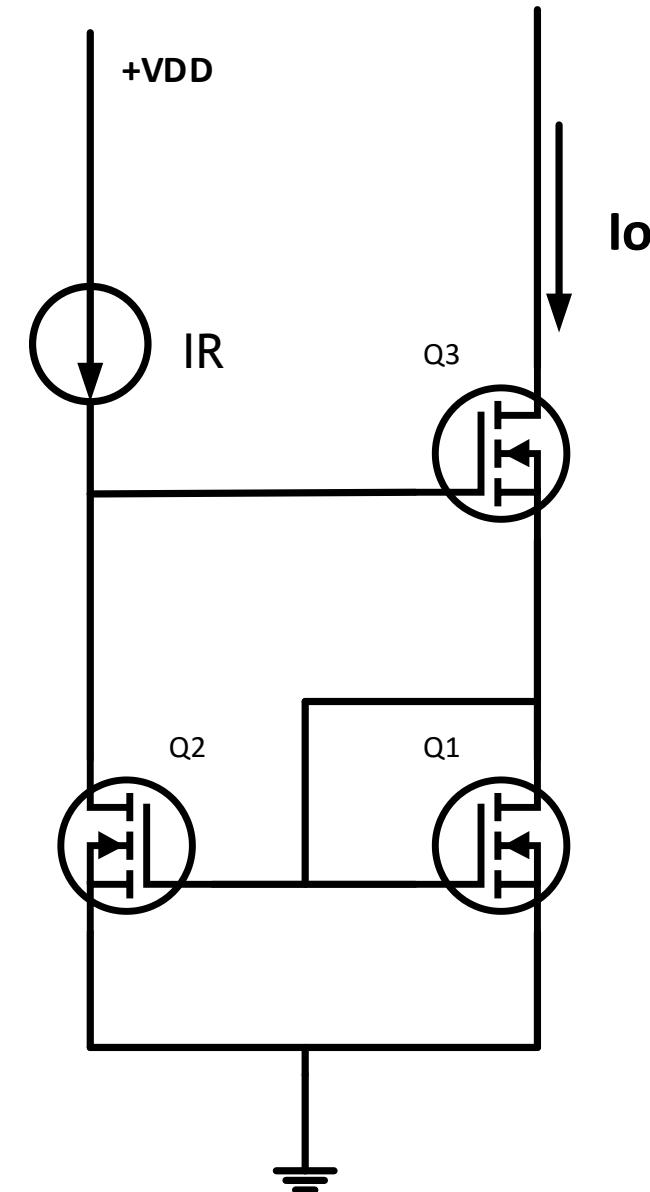

Mosfet Current Sources:

Two Port Model for Mosfet Current Mirror

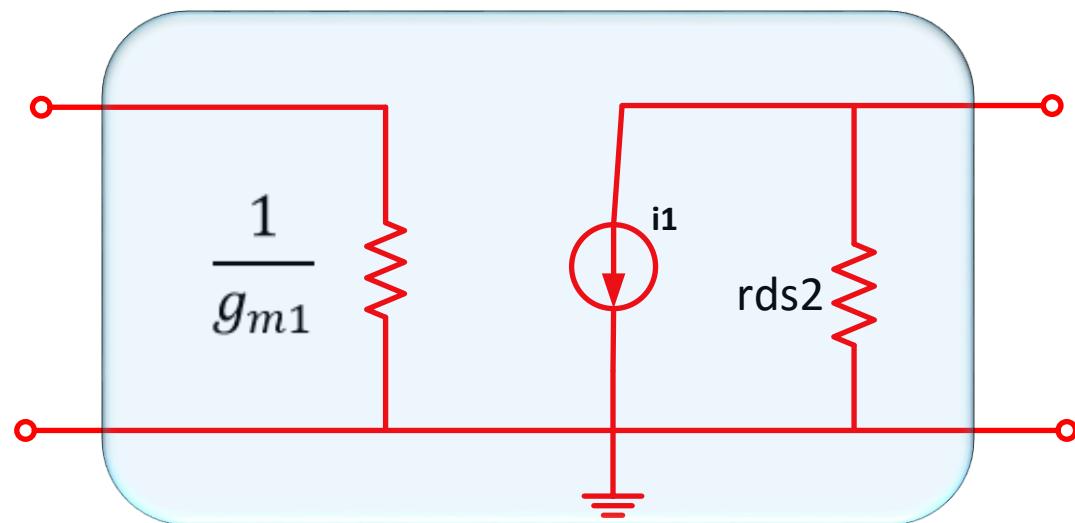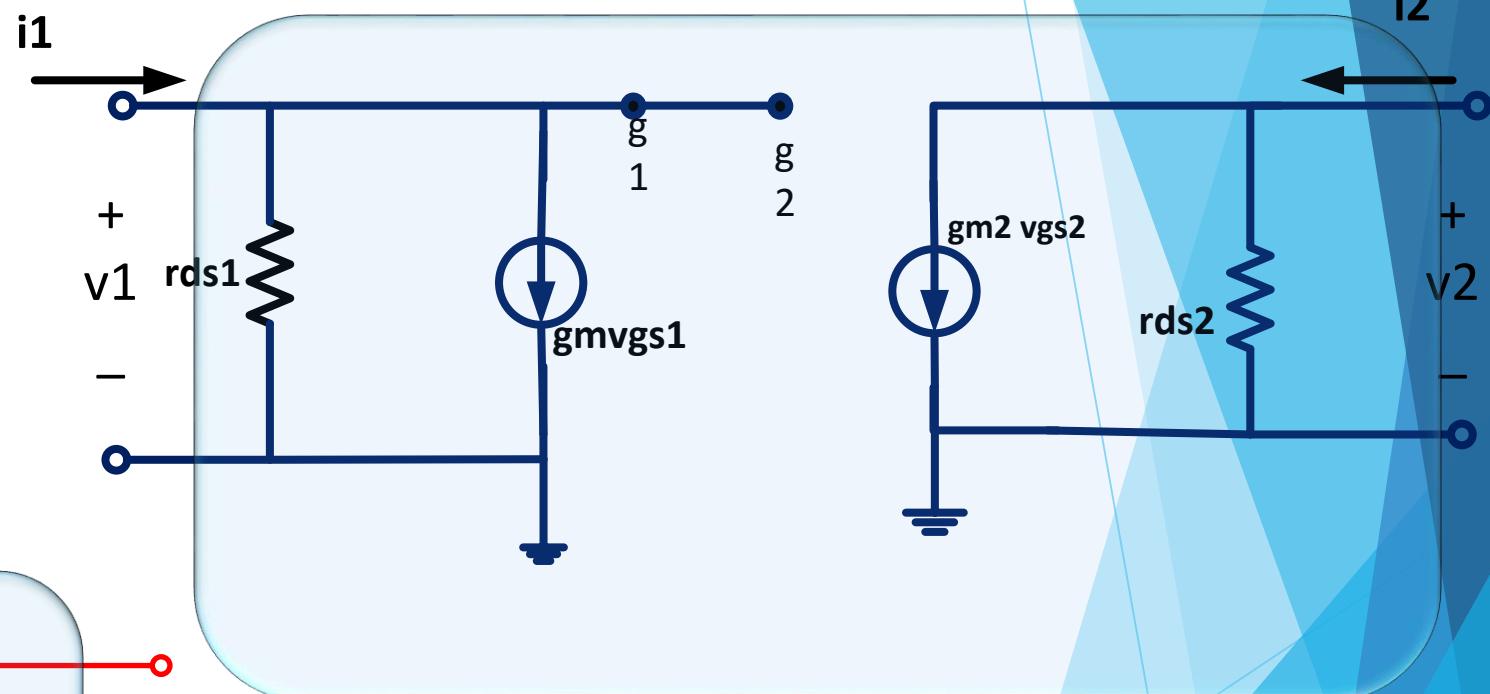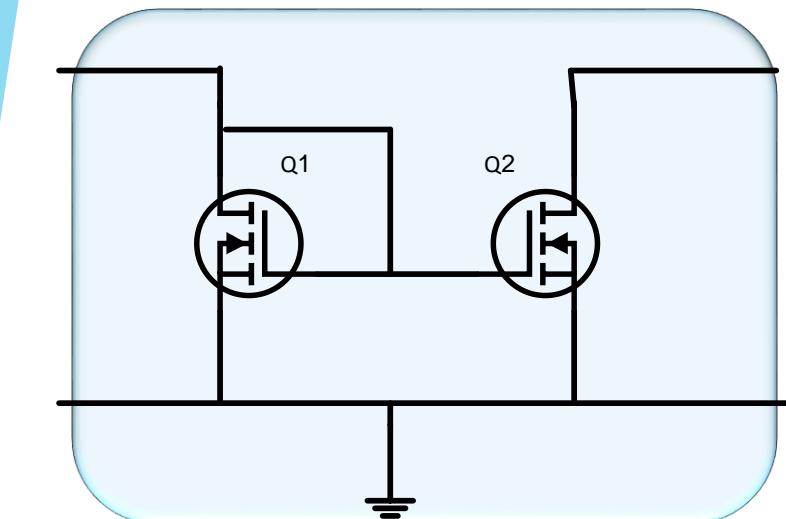


Mosfet Current Sources:

Cascode mosfet current mirror

$$I_{DS1} = \frac{1}{2} \bar{K}_n (V_{GS1} - V_T)^2 \left(\frac{W}{L} \right)_1 = I_R$$


$$I_{DS2} = \frac{1}{2} \bar{K}_n (V_{GS2} - V_T)^2 \left(\frac{W}{L} \right)_2 = I_o$$
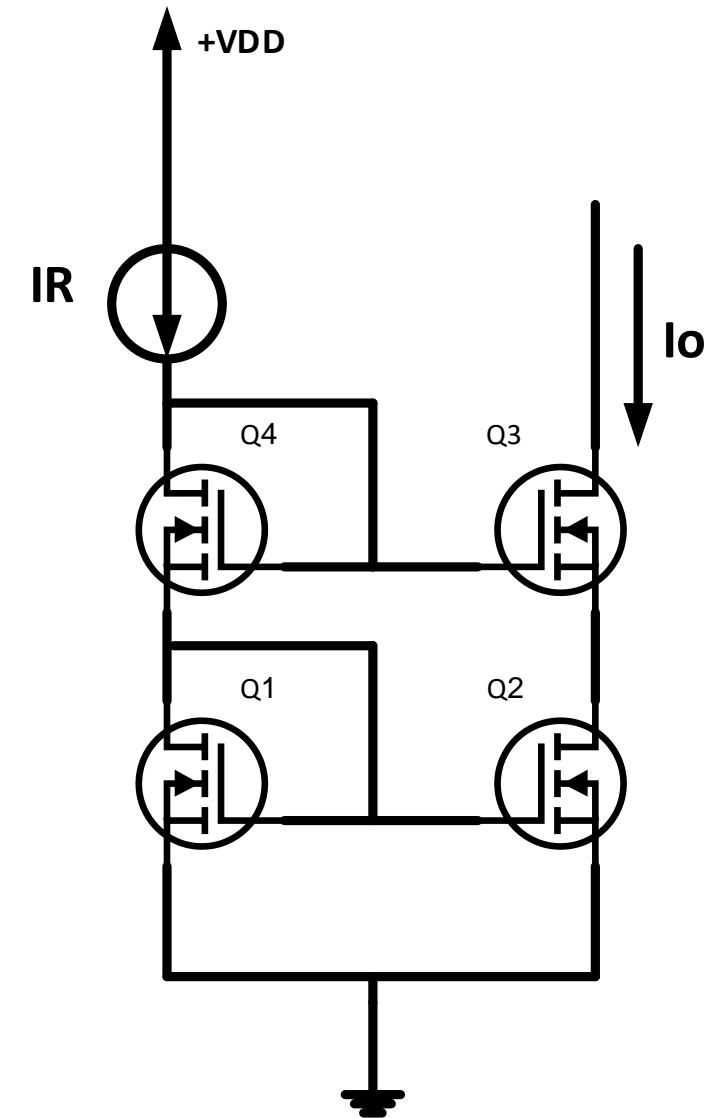
$$\frac{I_o}{I_R} = \frac{\left(\frac{W}{L} \right)_2}{\left(\frac{W}{L} \right)_1}$$



► $R_o = rds_3 + rds_2(1 + gm rds_3)$

$R_o \approx rds_2 rds_3 gm$

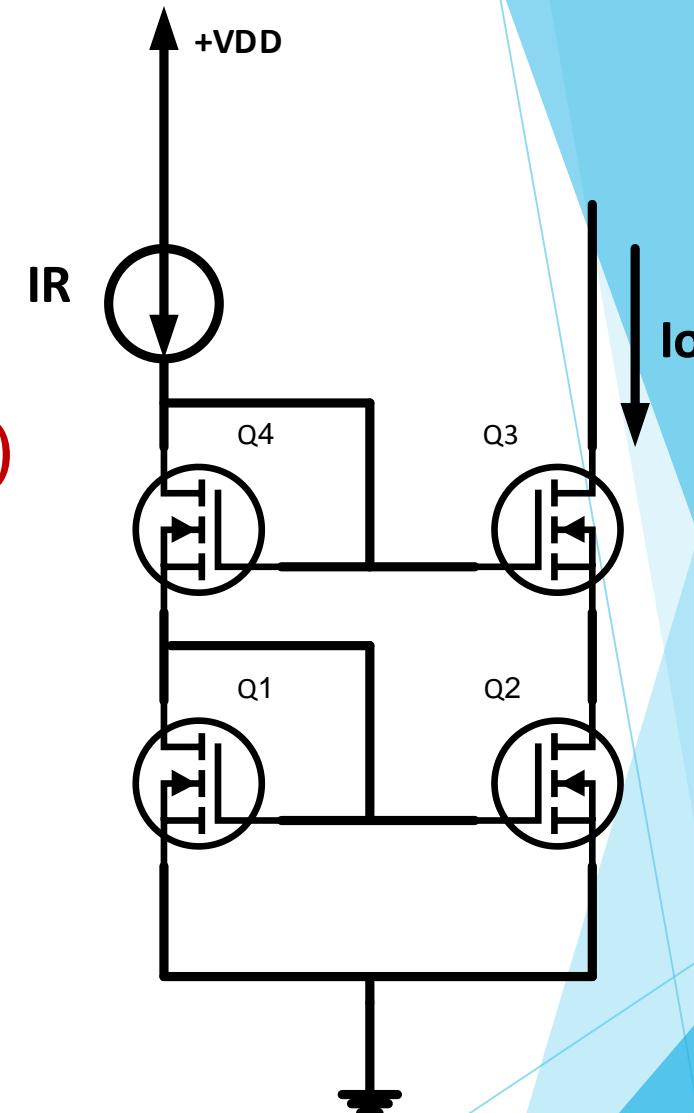

Circuits With Active Load


Find $A_v = \frac{V_o}{V_i}$


Let $R_C = 5k$,

$I_{CQ} = 1mA$,


and $\frac{1}{h_{oe}} = 120k$

$R_L = 10k$

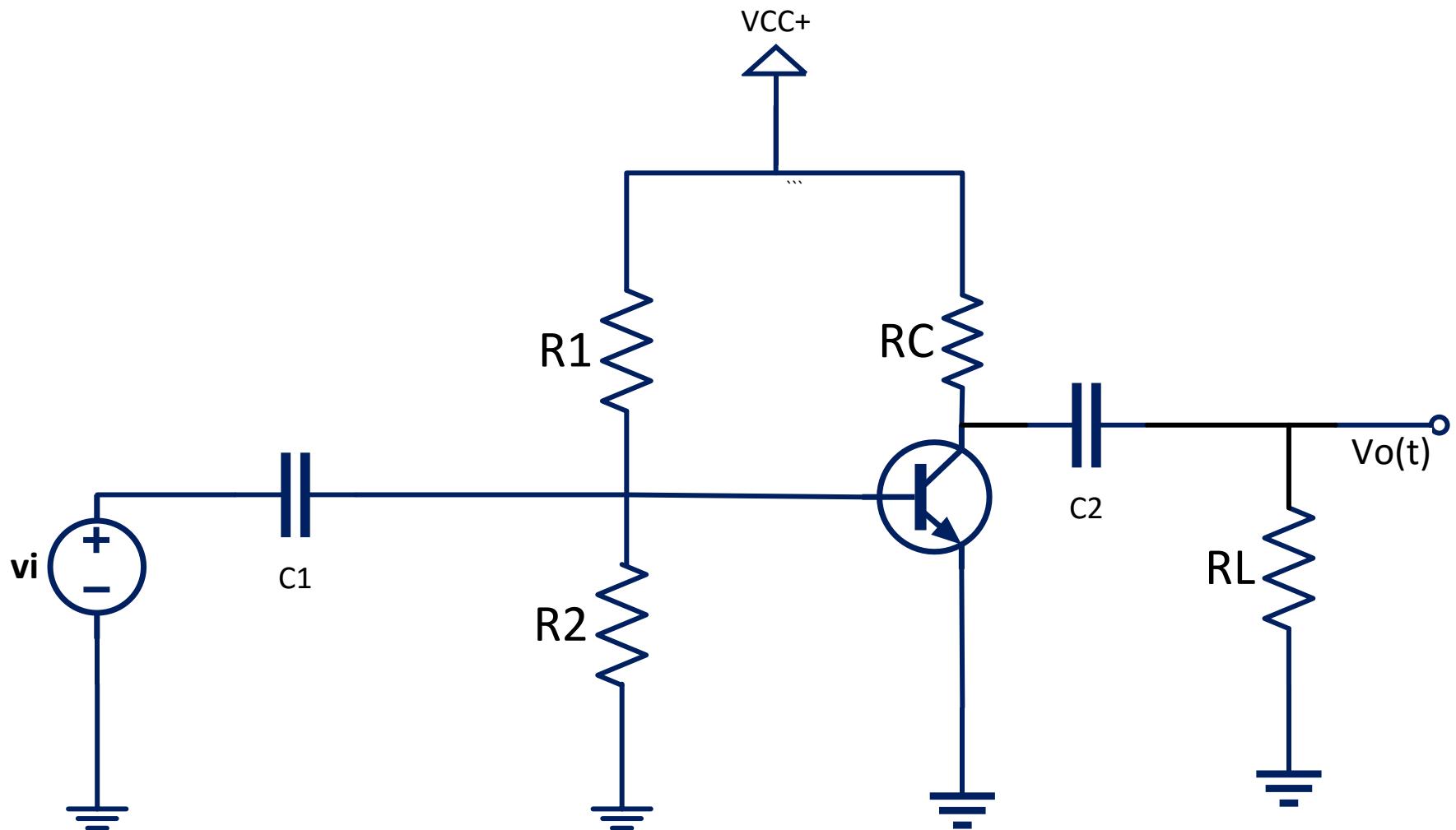


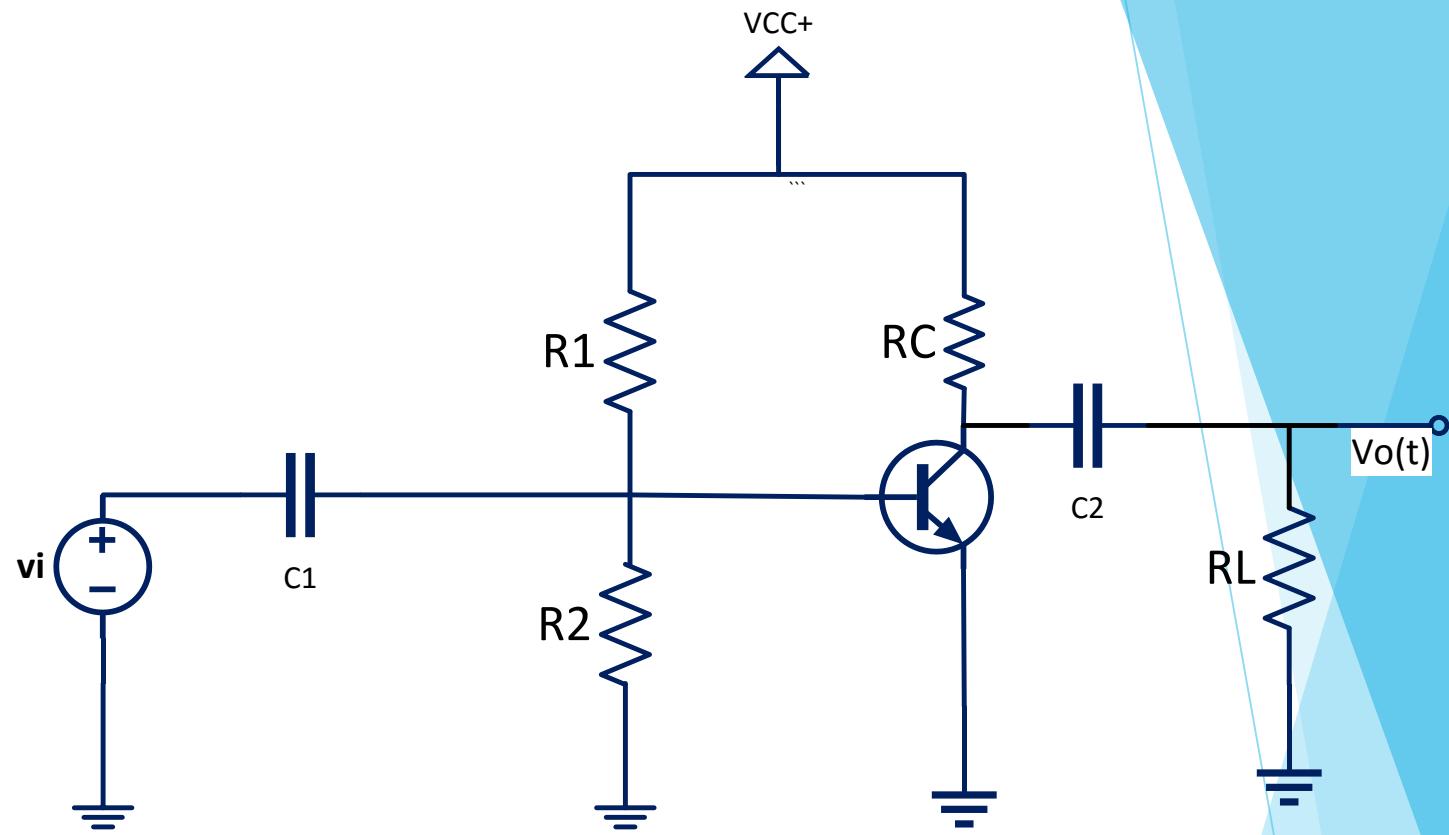

Ac Small signal equivalent Circuit

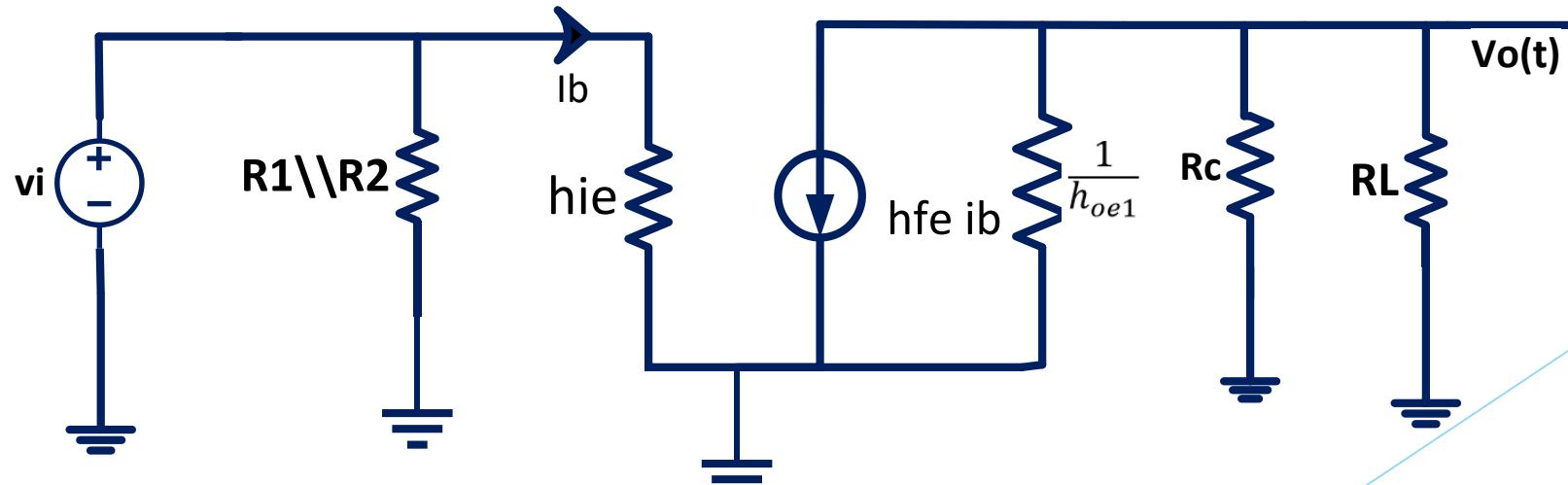

Circuits With Active Load

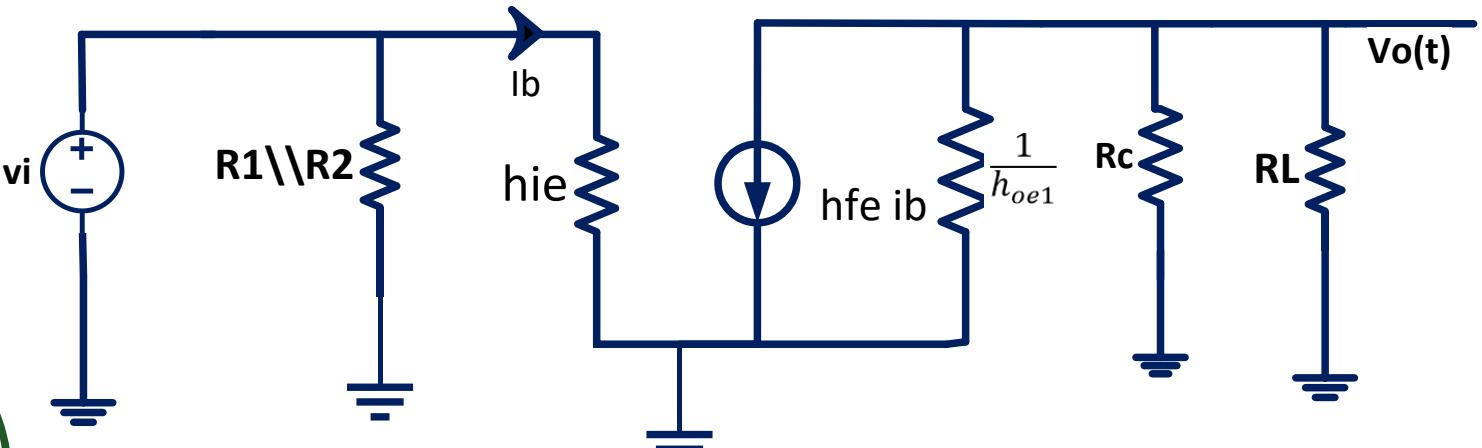

$$V_o = -h_{fe} i_b \left(R_C \parallel R_L \parallel \frac{1}{h_{oe}} \right)$$

$$i_b = \frac{v_i}{h_{ie}}$$

To increase $|Av|$, $R_C \uparrow, V_{CE} \downarrow$
→ Transistor enters saturation



$$\therefore Av = -\frac{h_{fe}}{h_{ie}} \left(R_C \parallel R_L \parallel \frac{1}{h_{oe}} \right)$$

$$Av = -gm \left(R_C \parallel R_L \parallel \frac{1}{h_{oe}} \right) = -125$$

$$V_{CE} = V_{CC} - R_C I_{CQ}$$

Amplifier With an Active Load

Ac Small signal equivalent Circuit

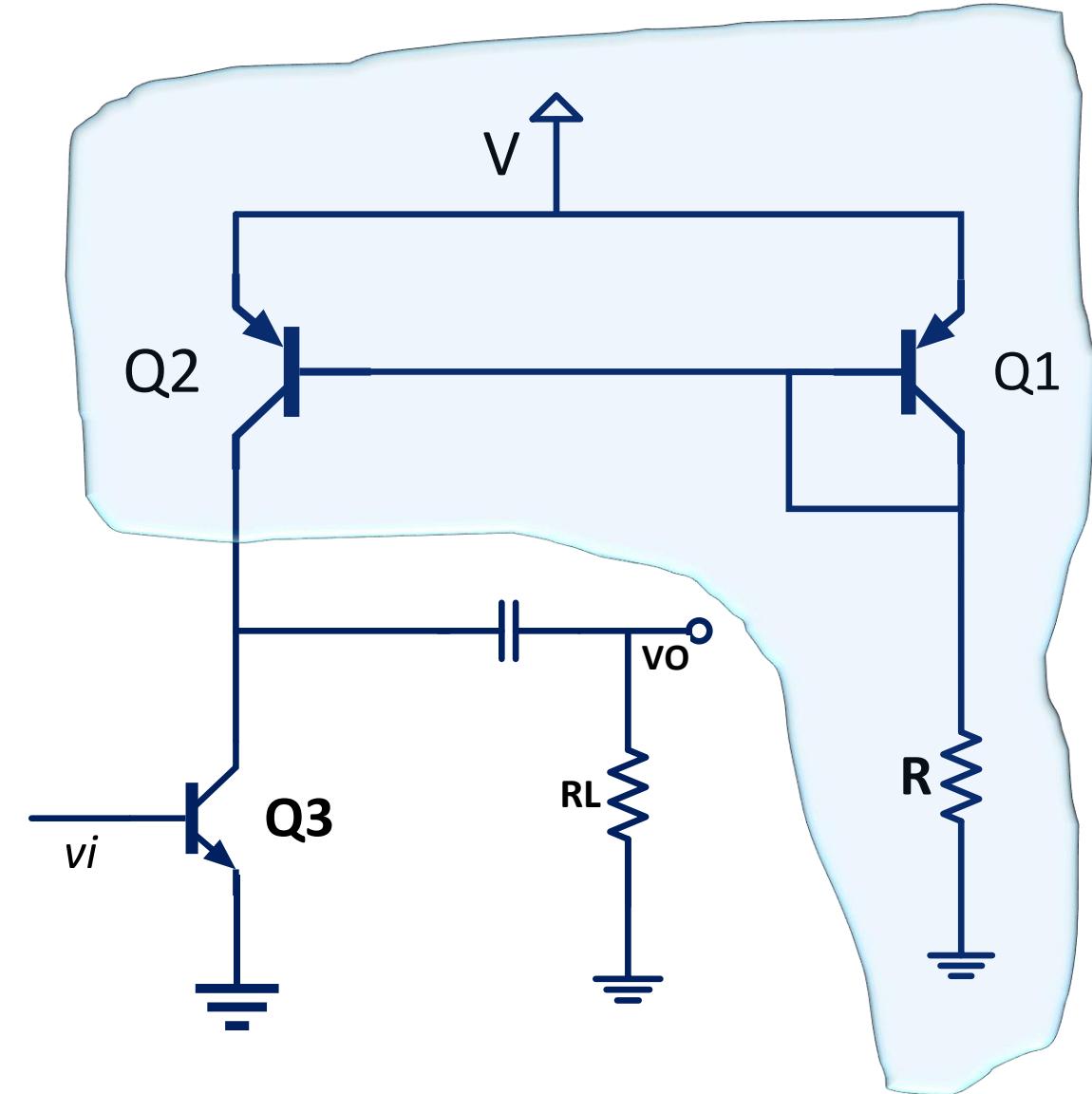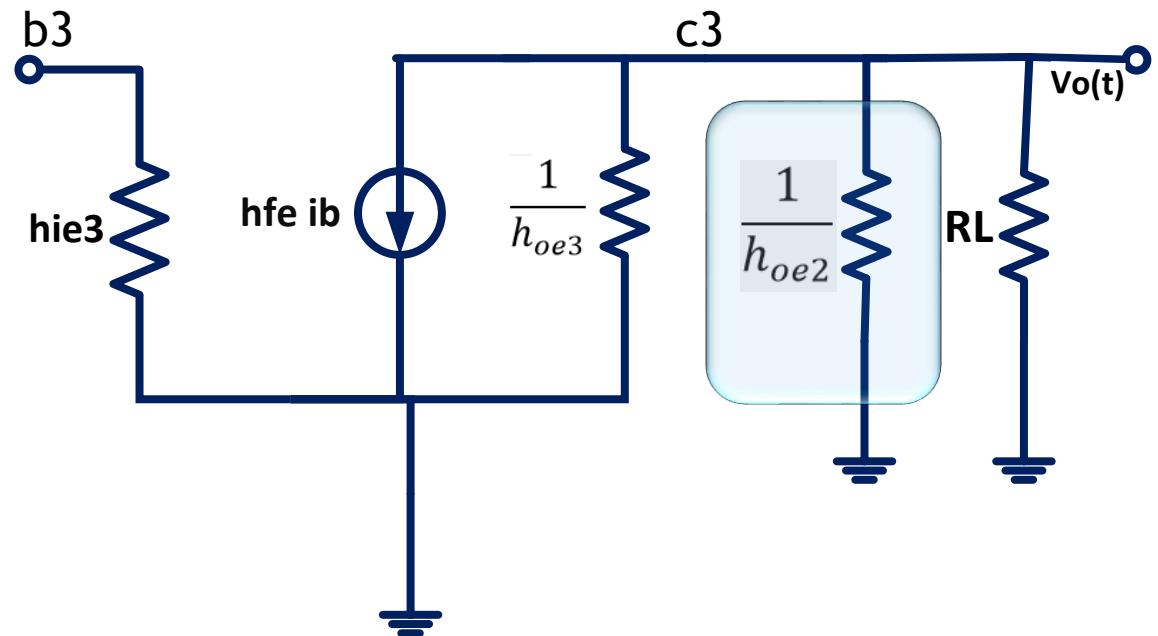

Amplifier With an Active Load


$$Av = -gm \left(\frac{1}{h_{oe3}} \parallel \frac{1}{h_{oe3}} \parallel R_L \right)$$

let $\frac{1}{h_{oe3}} = 120k$

$$\frac{1}{h_{oe2}} = 80k$$

$$, I_{CQ} = 1mA$$
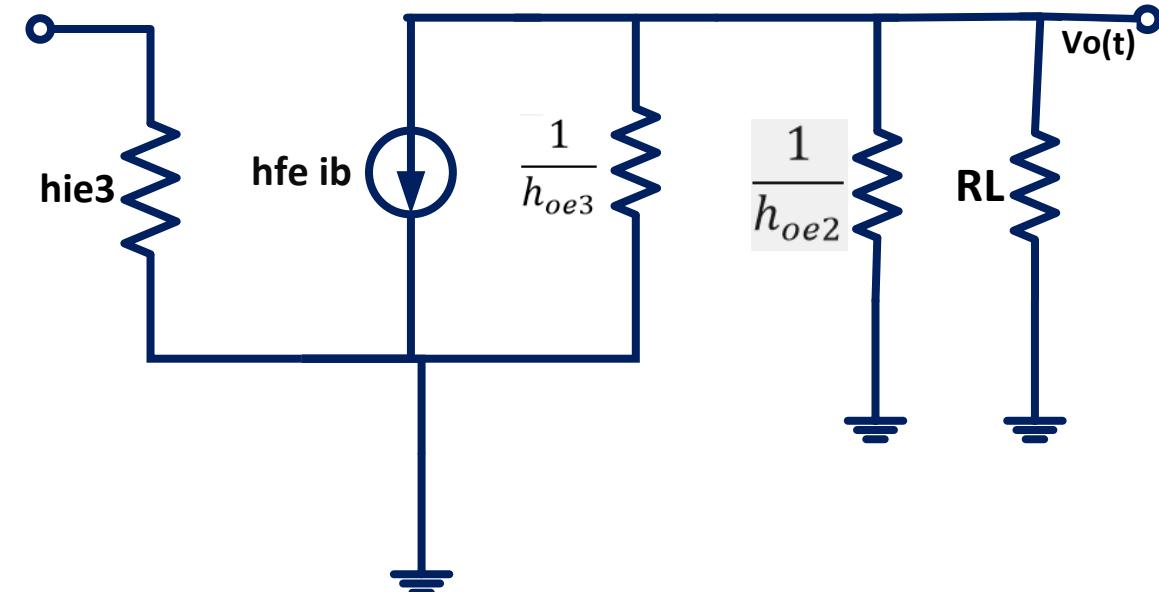
$$\therefore gm = \frac{h_{fe3}}{h_{ie3}} = \frac{I_{CQ}}{V_T} = 38.46 \Omega$$



$$V_o = \begin{cases} -1846 v_i ; R_L = \infty \\ -1247 v_i ; R_L = 100k \\ -318 v_i ; R_L = 10k \end{cases}$$


Differential Amplifiers


AC Analysis: Input Impedance

since $I_{E1} = I_{E2}$ and $\beta_1 = \beta_2$


$$h_{ie1} = h_{ie2} = h_{ie}$$

$$h_{ib1} = h_{ib2} = h_{ib}$$

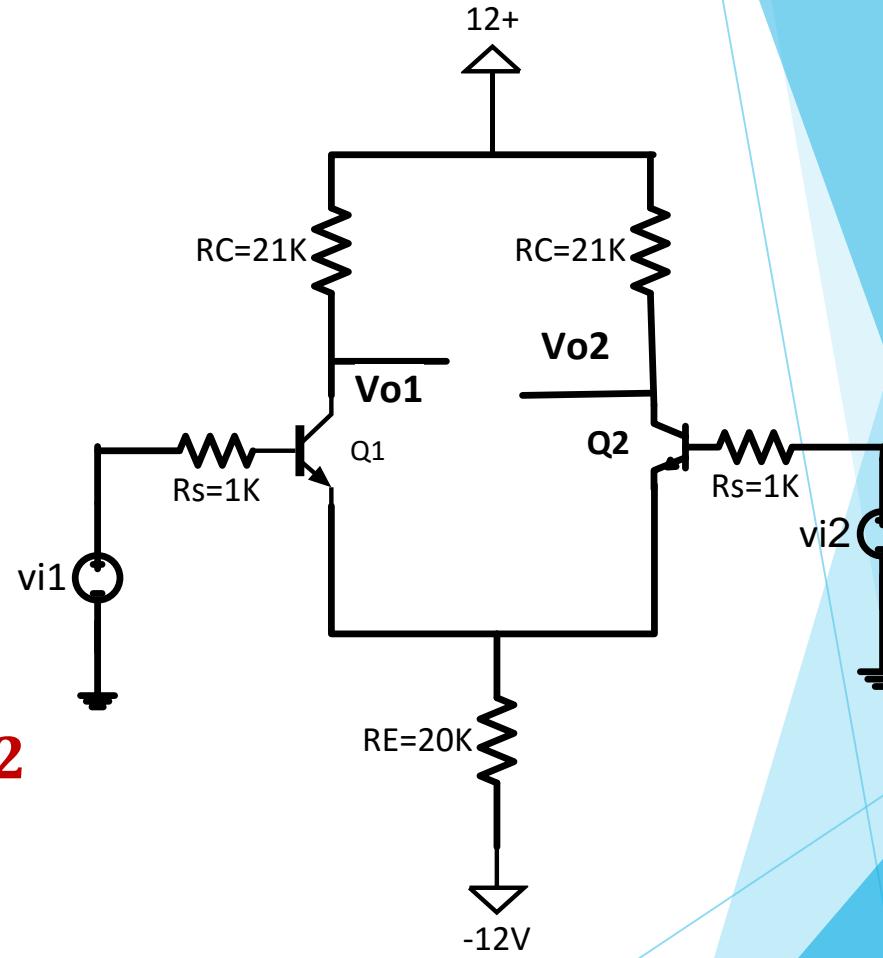


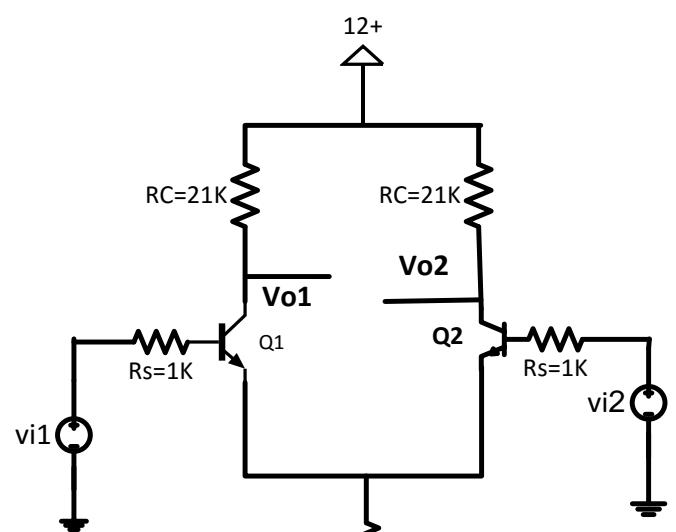


Ac small signal equivalent circuit

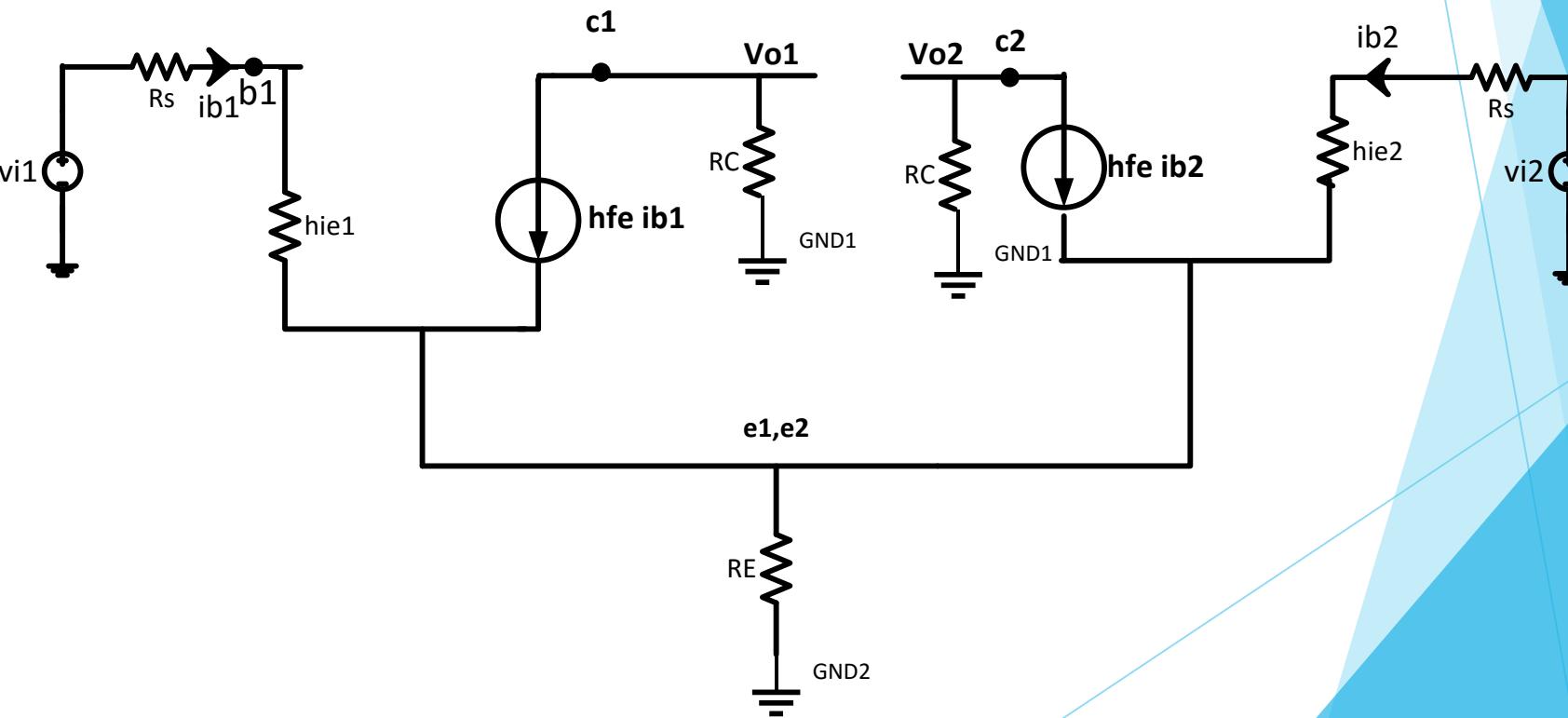

To find the input impedance

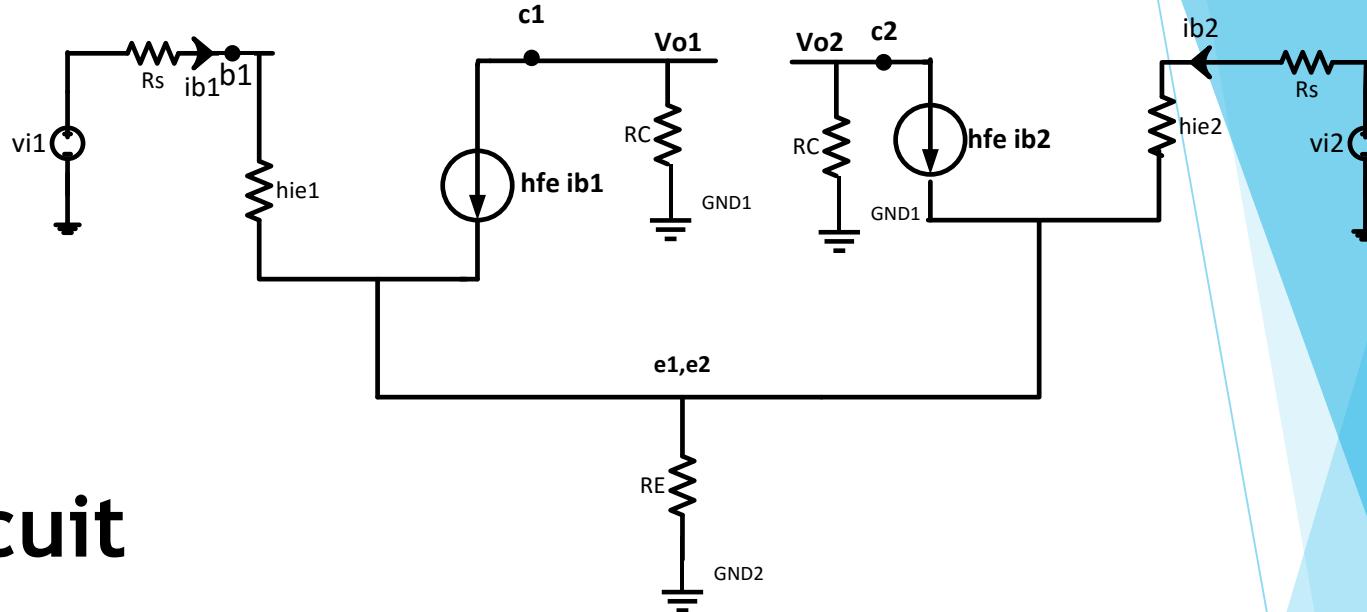

Base equivalent circuit

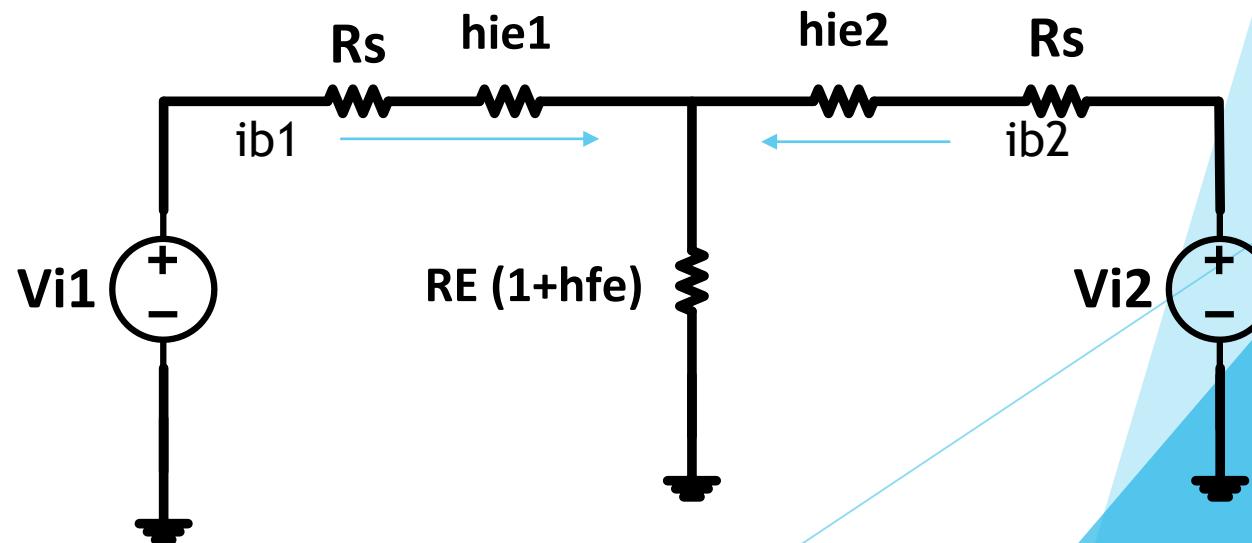

Input Impedance:

Base equivalent circuit

Differential mode input impedance $\equiv Z_{id}$

$$Z_{id} = \left. \frac{v_d}{i_b} \right|_{v_c=0}$$

Common mode input impedance $\equiv Z_{ic}$

$$Z_{ic} = \left. \frac{v_c}{i_b} \right|_{v_d=0}$$

Input impedance

$$Z_{id} = \frac{v_d}{i_b} \Big|_{v_c=0}$$



$$v_{i1} = -\frac{v_d}{2}; v_{i2} = \frac{v_d}{2}$$

$$Z_{id} = 2(R_s + h_{ie})$$

$$Z_{ic} = \frac{v_c}{i_b} \Big|_{v_d=0}$$

$$v_{i1} = v_c ; v_{i2} = v_c$$
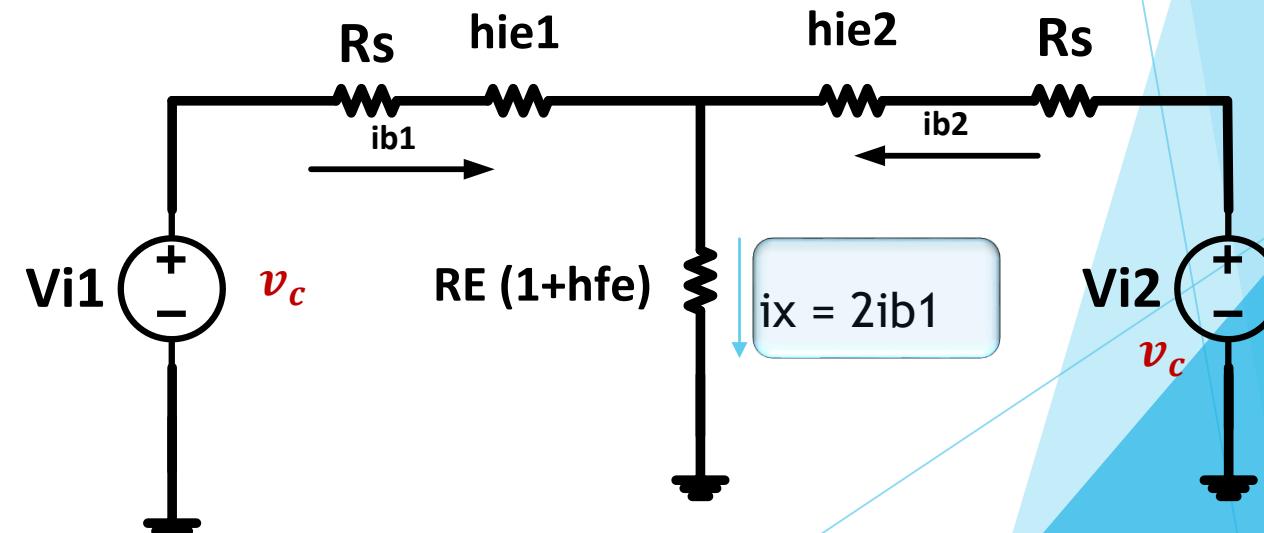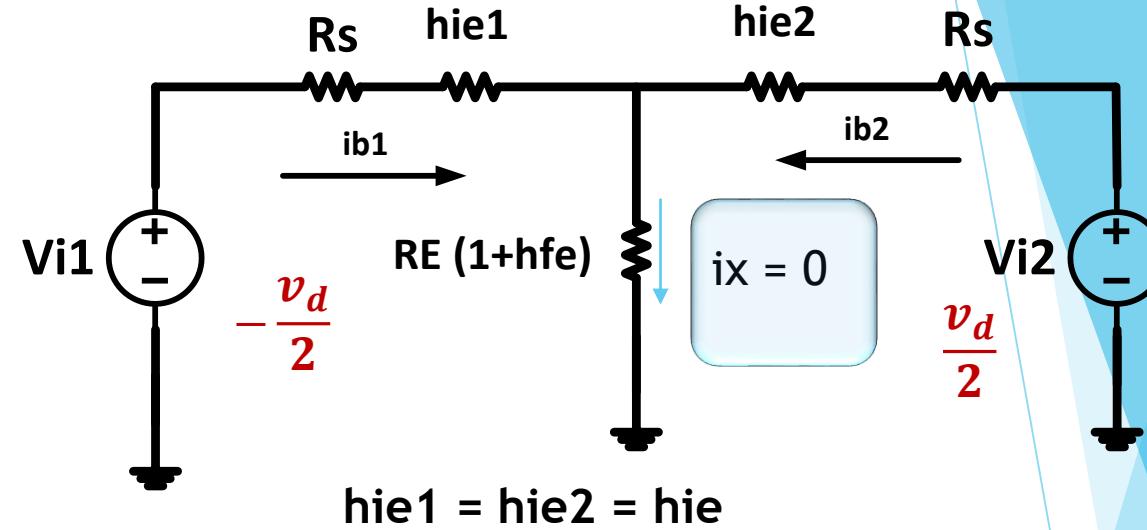
$$Z_{ic} = R_s + h_{ie} + 2(1 + h_{fe})RE$$





Differential Amplifiers Using Darlington and FET

Differential Amplifiers Using Darlington

To find A_c & A_d :

Emitter equivalent circuit

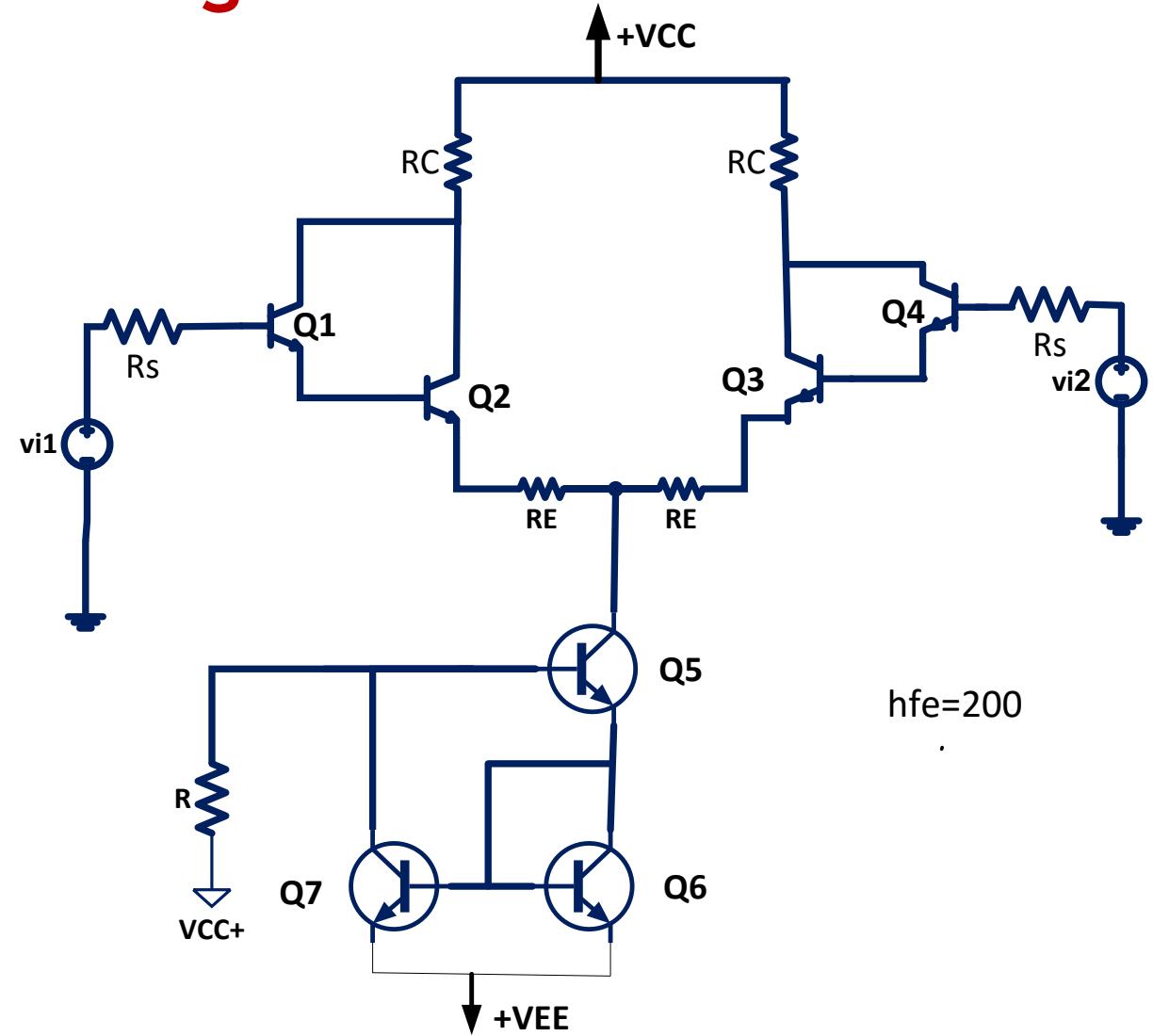
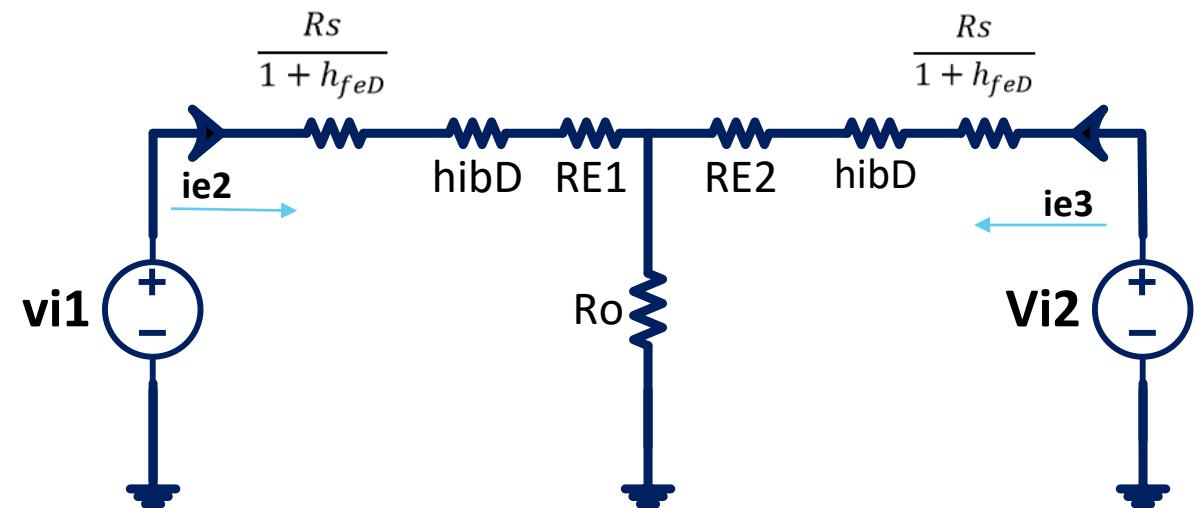


Differential Amplifiers Using Darlington and FET

Differential Amplifiers Using Darlington

To find Zid:

Base equivalent circuit

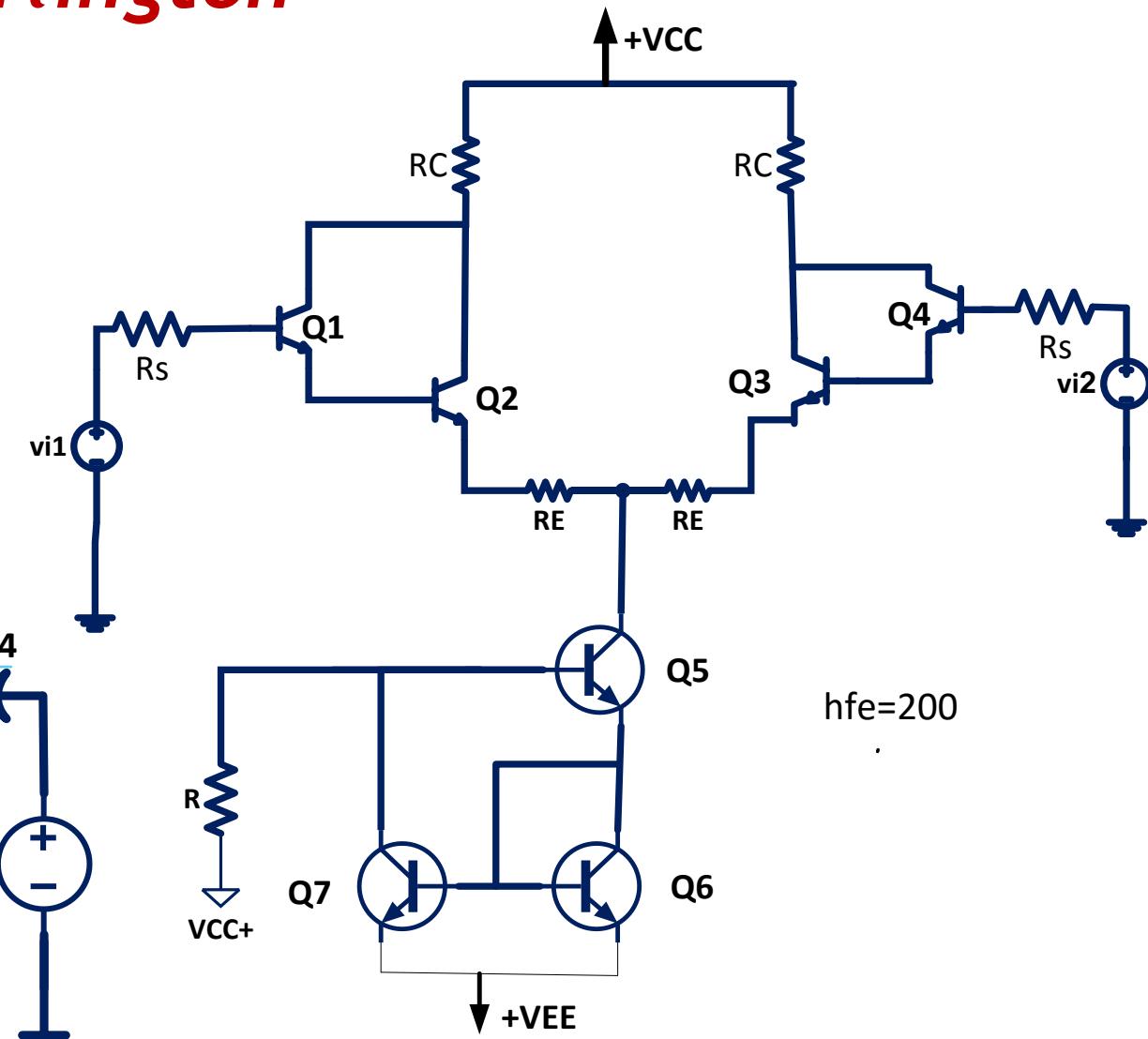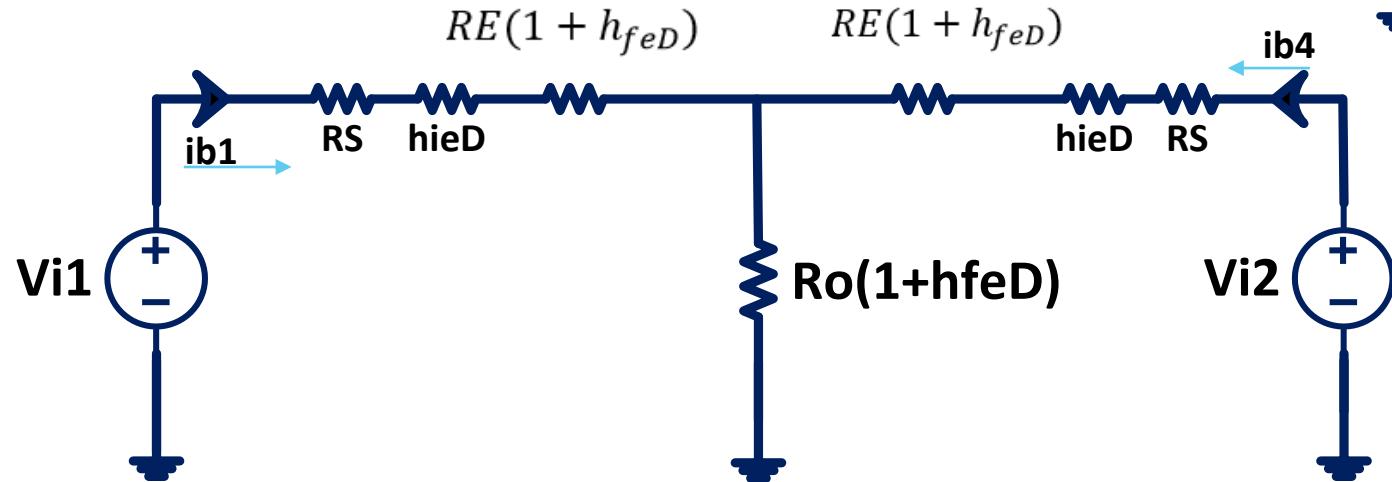


Input Impedance:

Base equivalent circuit

$$Z_{id} = \frac{v_d}{i_{b1}} \Big|_{v_c=0}$$
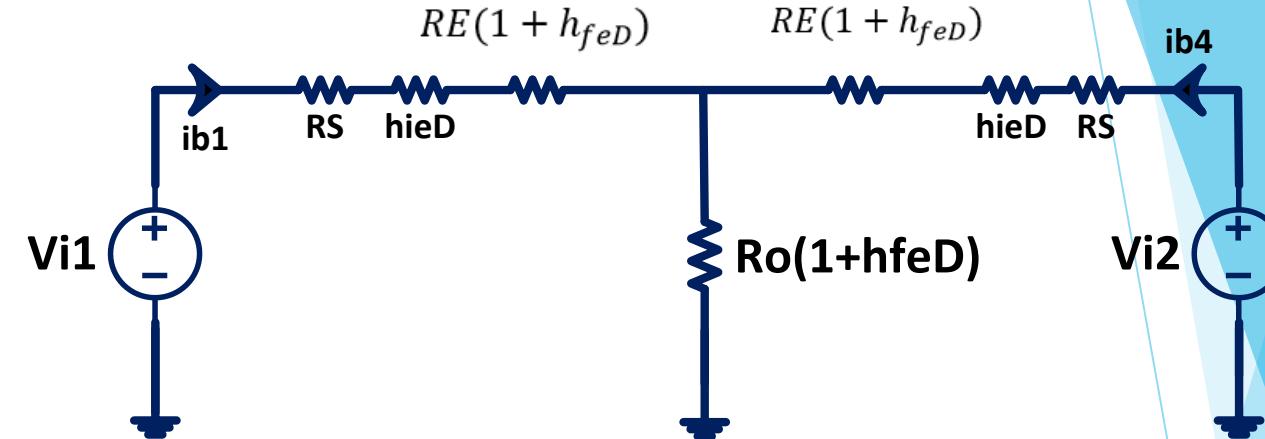
$$v_{i1} = -\frac{v_d}{2}; v_{i2} = \frac{v_d}{2}$$



$$Z_{id} = 2 \left(R_S + h_{ieD} + R_E (1 + h_{feD}) \right)$$

$$Z_{ic} = \frac{v_c}{i_b} \Big|_{v_d=0}$$



$$v_{i1} = v_c; v_{i2} = v_c$$

$$Z_{ic} = R_S + h_{ieD} + R_E (1 + h_{feD}) + 2R_o (1 + h_{feD})$$


Differential Amplifiers Using Darlington and FET

Differential Amplifiers Using FET




Ac Small signal equivalent Circuit:

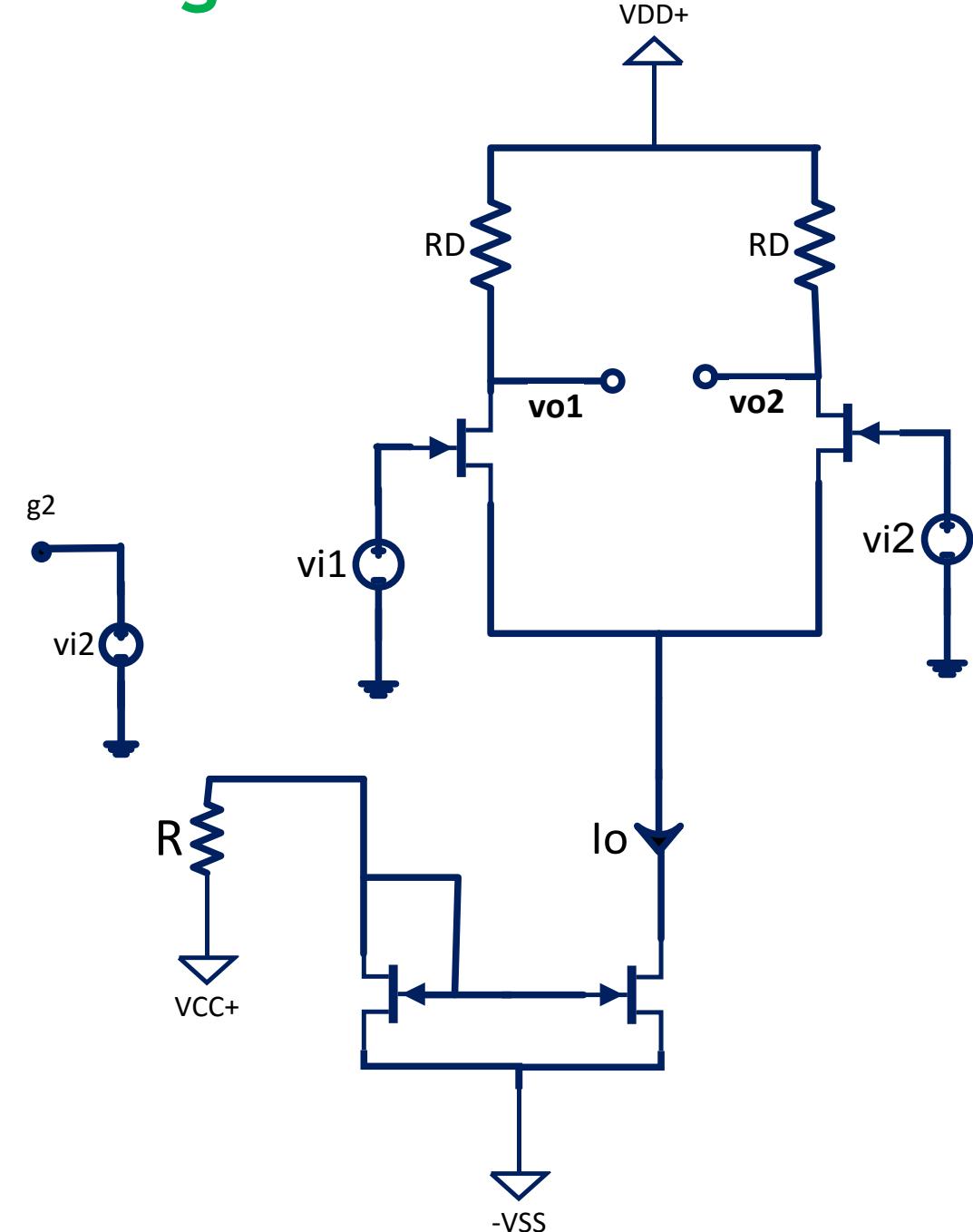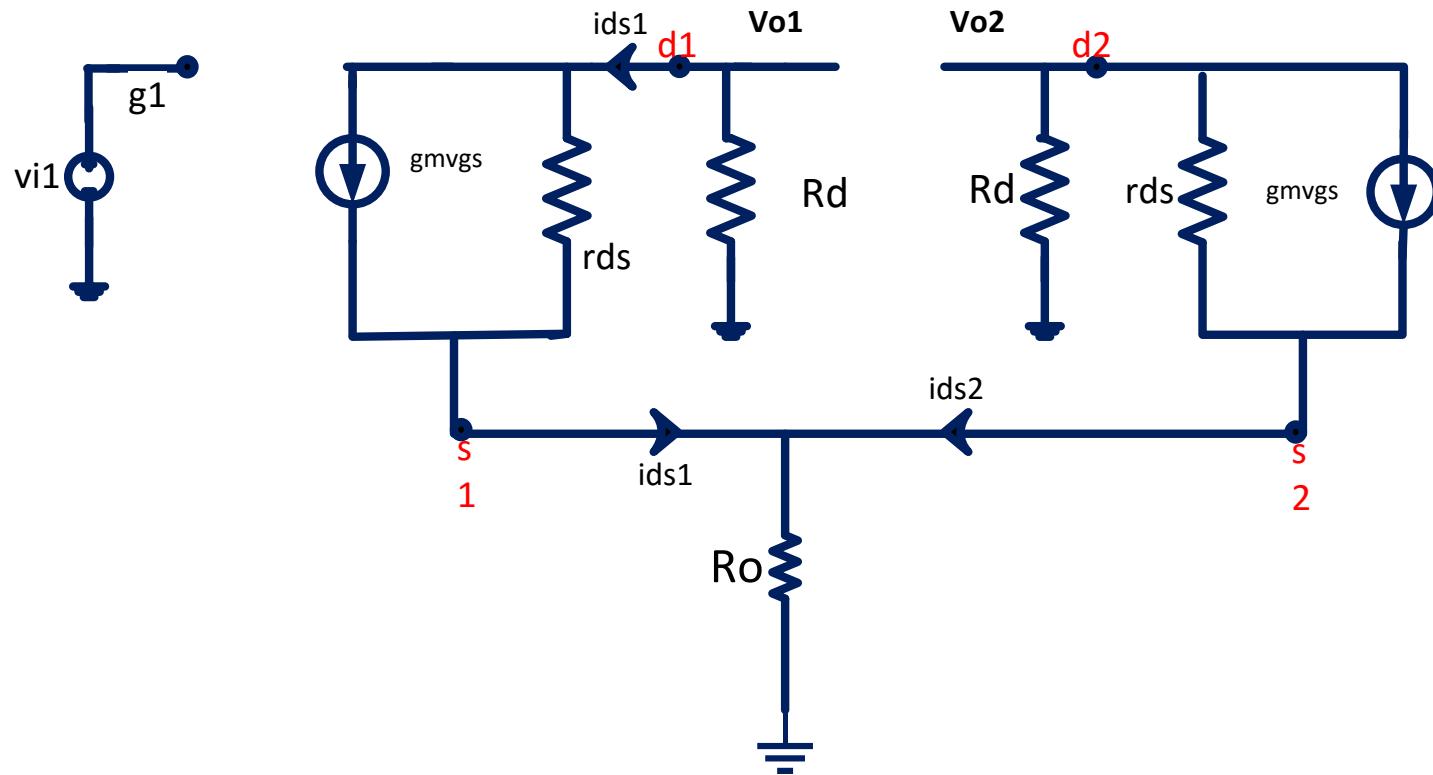

Differential Amplifiers Using FET

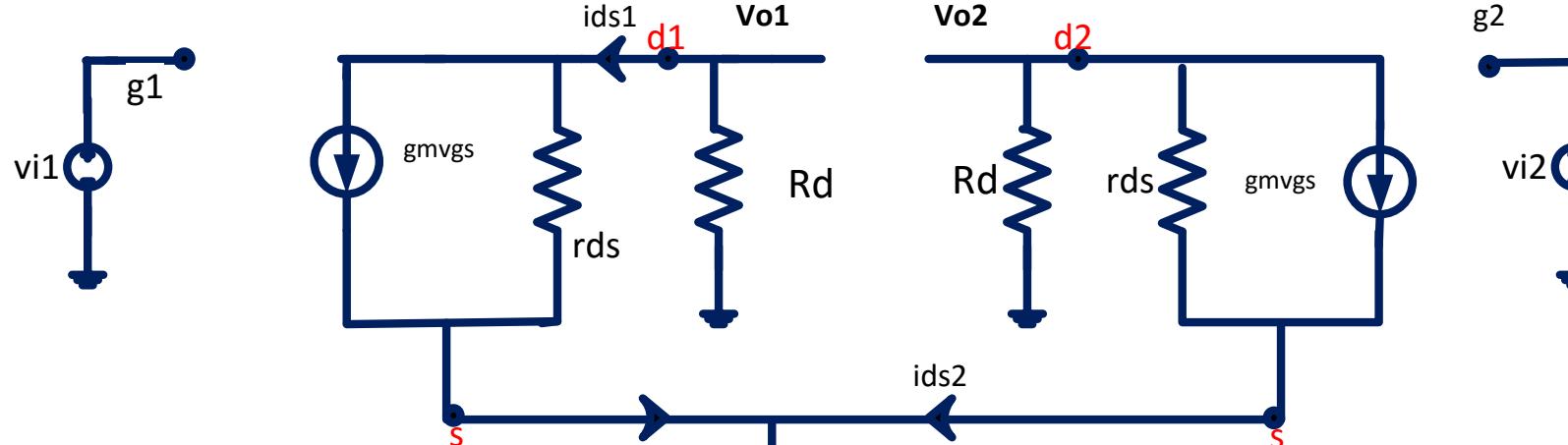

$$Vo_1 = -ids_1 \cdot R_d$$

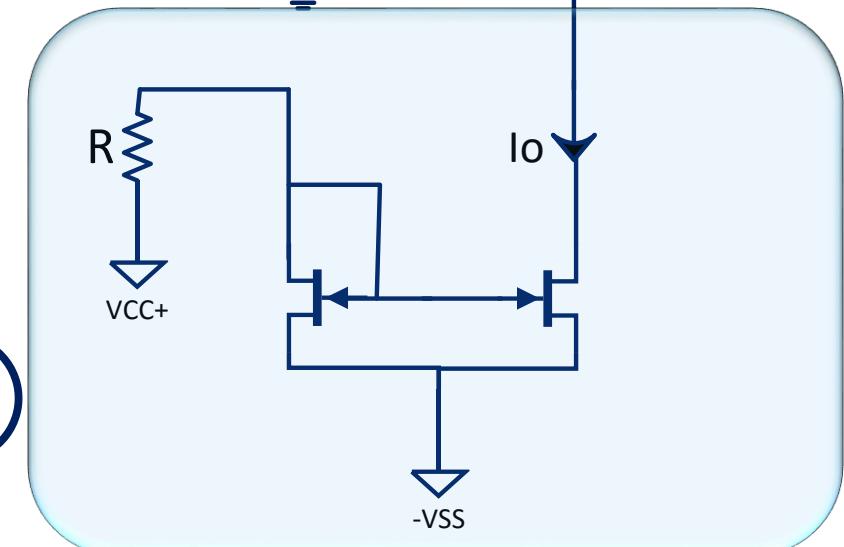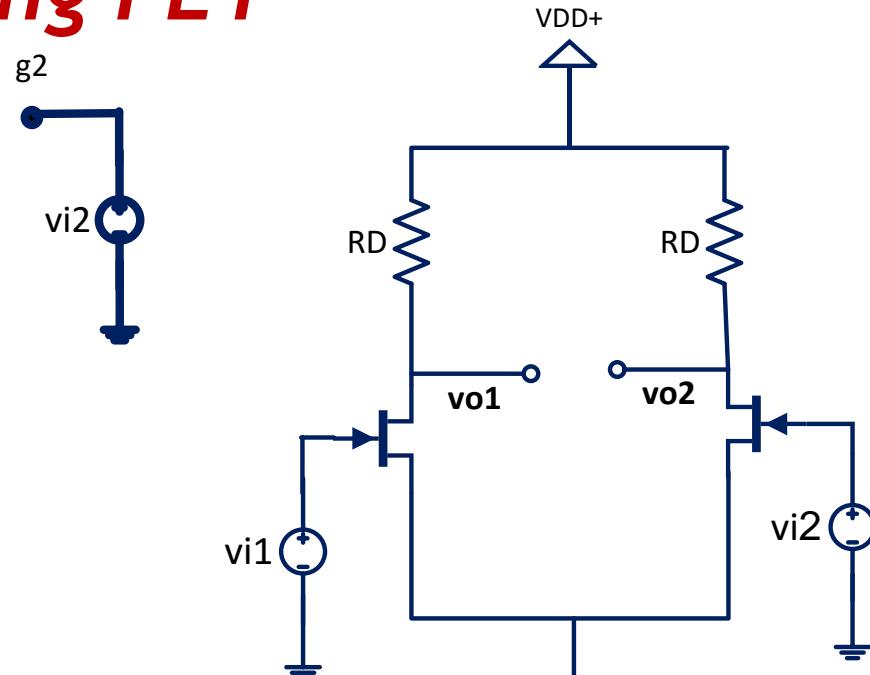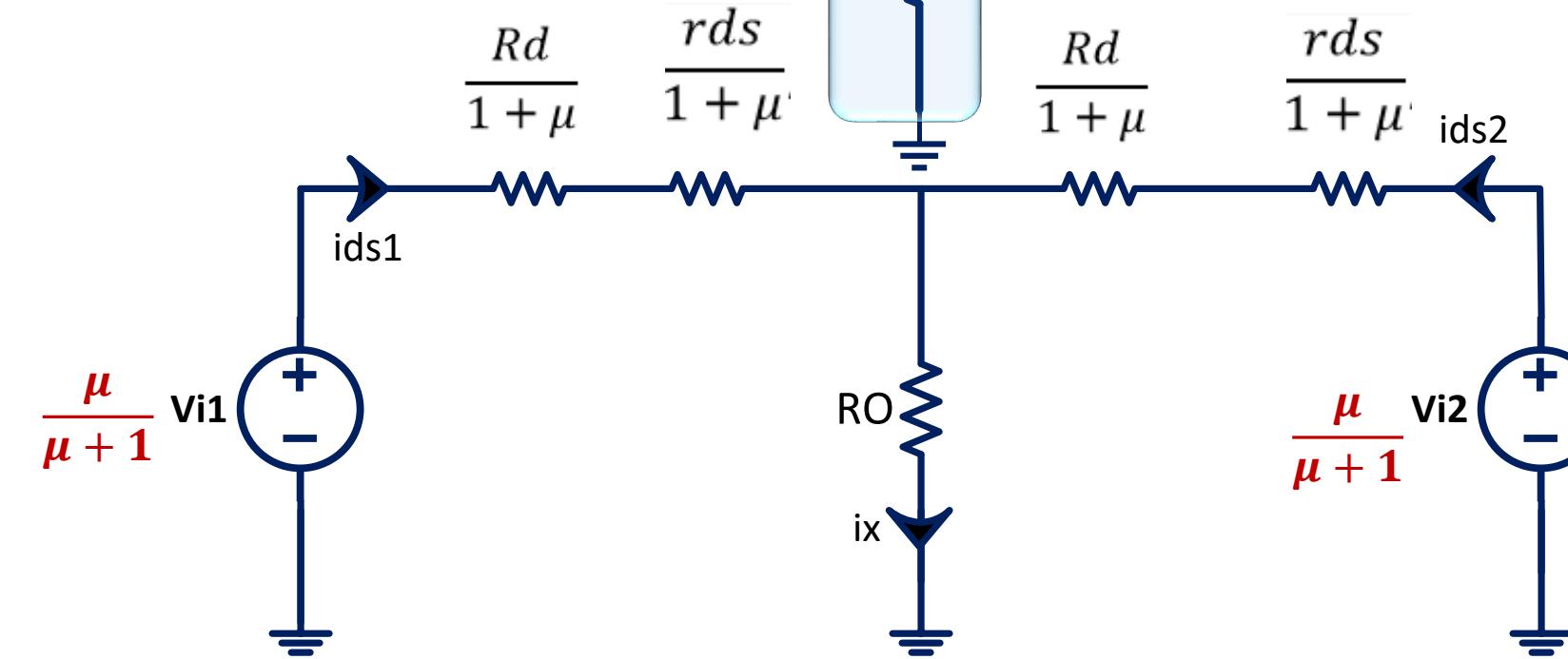


Differential Amplifiers Using FET

Source equivalent Circuit:

$$v_{i1} = v_c - \frac{v_d}{2}$$

$$v_{i2} = v_c + \frac{v_d}{2}$$

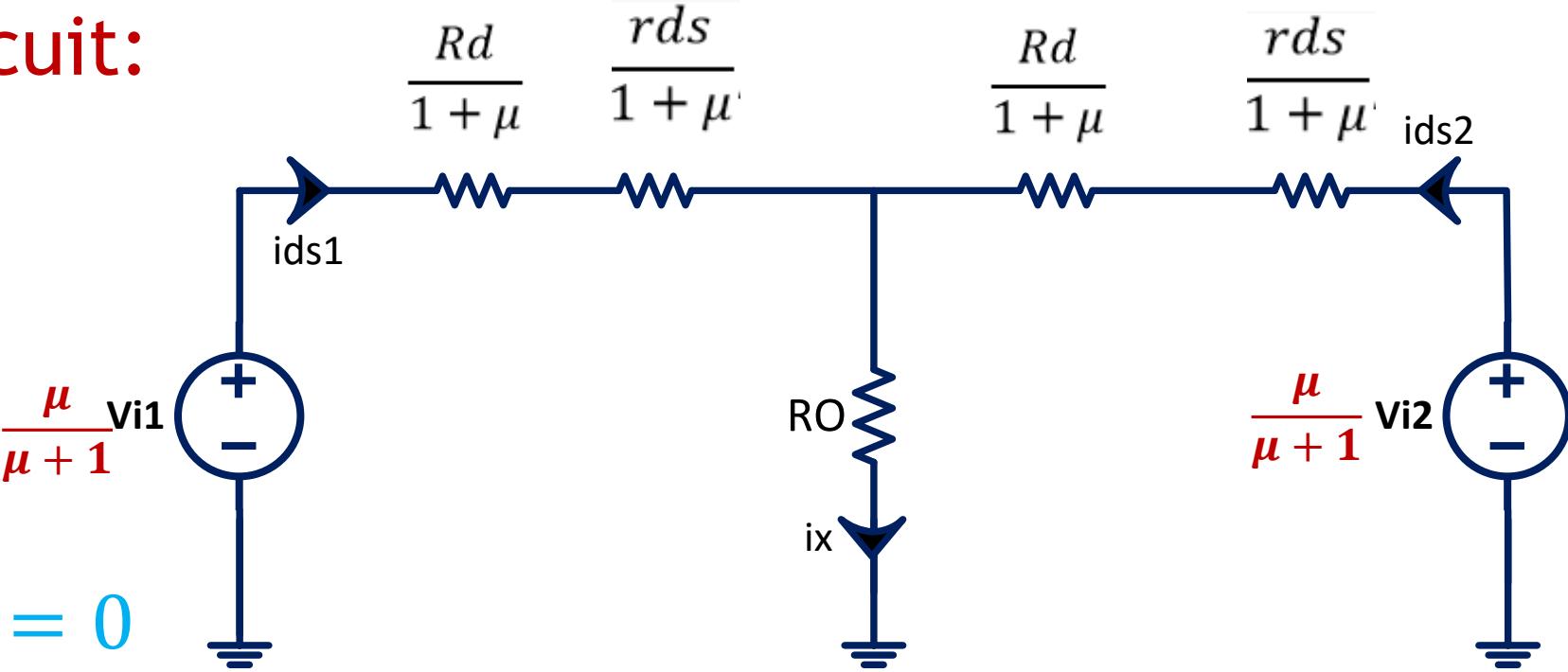

1) To find A_d ; set $v_c = 0$

$$v_{i1} = -\frac{v_d}{2}$$

$$v_{i2} = \frac{v_d}{2}$$

$i_x = 0$ symmetry

$$ids_1 = -ids_2$$

$$ids_1 = \frac{\mu}{\mu+1} \left(-\frac{v_d}{2} \right)$$

$$\frac{R_d + rds}{\mu+1}$$

$$v_{o1} = \frac{R_d \frac{\mu}{\mu+1} v_d}{2 \left(\frac{R_d + rds}{\mu+1} \right)}$$

$$v_{o1} = \frac{R_d \frac{\mu}{\mu+1} v_d}{2 \left(\frac{R_d + rds}{\mu+1} \right)}$$

$$A_d = \frac{v_{o1}}{v_d} \Big|_{v_c=0}$$

$$A_d = \frac{R_d \frac{\mu}{\mu+1}}{2 \left(\frac{R_d + rds}{\mu+1} \right)}$$

Differential Amplifiers Using FET

Ac Small signal equivalent Circuit:


$$2) \text{ To find } A_c = \frac{v_{o1}}{v_c} \Big|_{v_d=0}$$

$$vi_1 = v_c$$

$$vi_2 = v_c$$

$$ids_1 = ids_2$$

$$i_x = 2ids_1$$

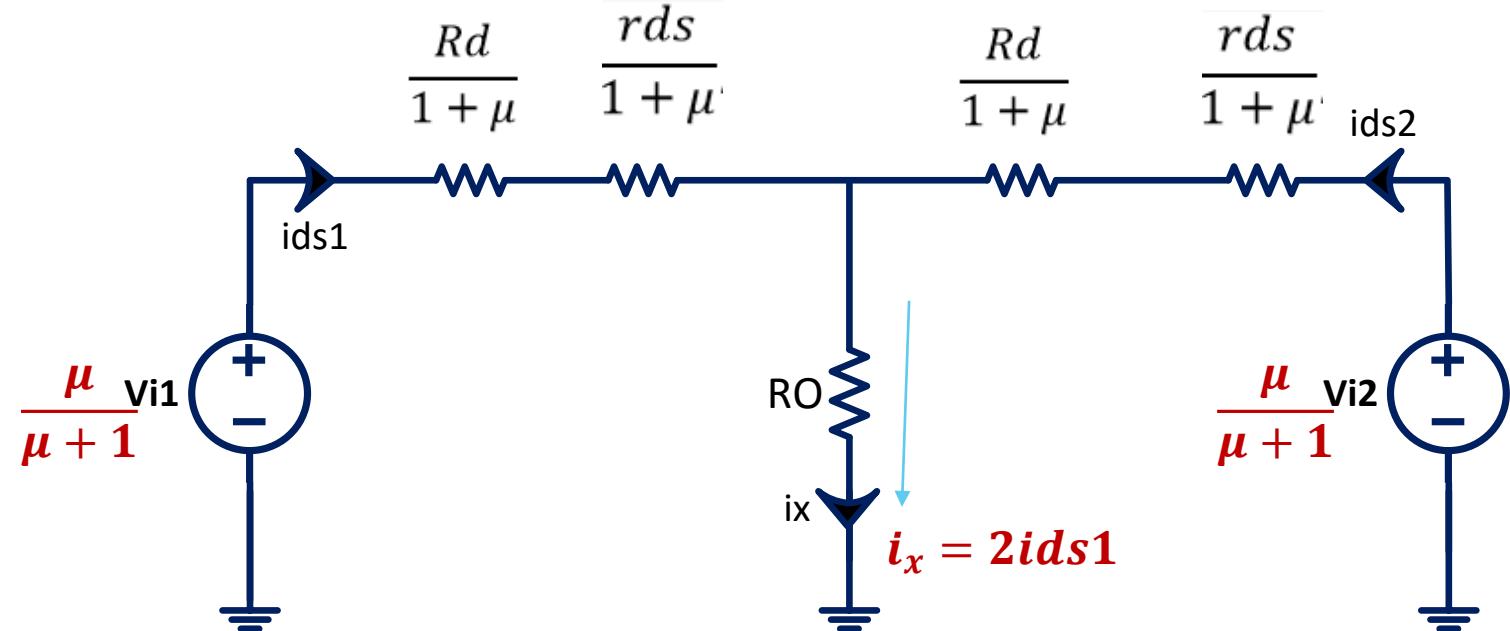


$$i_{ds1} = \frac{v_c \frac{\mu}{\mu + 1}}{\left(\frac{R_d + rds}{\mu + 1} \right) + 2R_o}$$

$$v_{o1} = \frac{-R_d \frac{\mu}{\mu + 1}}{\left(\frac{R_d + rds}{\mu + 1}\right) + 2R_o} v_c$$

$$\therefore A_c = \frac{R_d \frac{\mu}{\mu + 1}}{\left(\frac{R_d + rds}{\mu + 1}\right) + 2R_o}$$

$$CMRR = \left| \frac{A_d}{A_c} \right| = \frac{rds + R_d + 2R_o(\mu + 1)}{2(R_d + rds)}$$

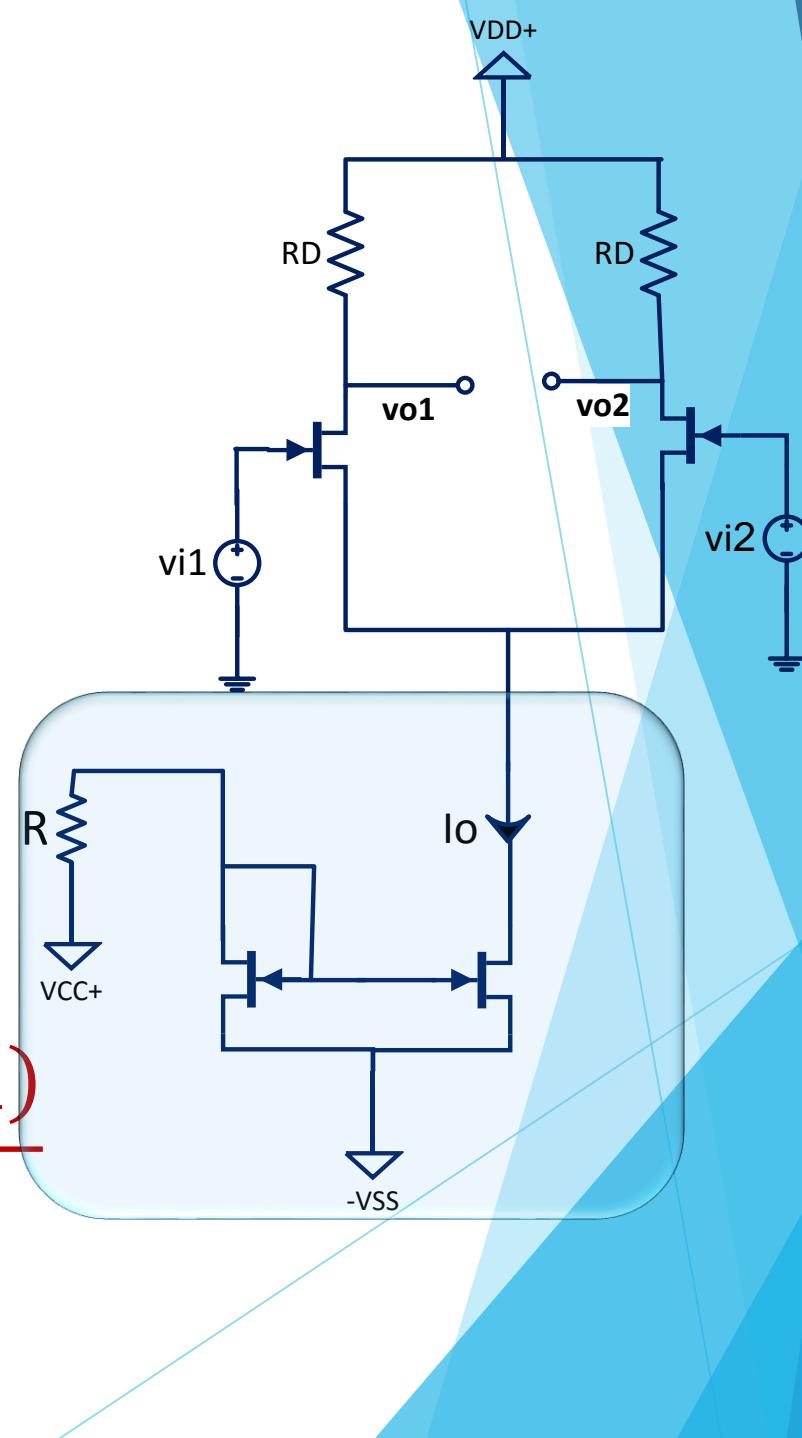


The Operational Amplifier

Very high voltage gain ; 200,000

Very High input impedance ; 10M ohm

Very small output impedance ; 75ohm

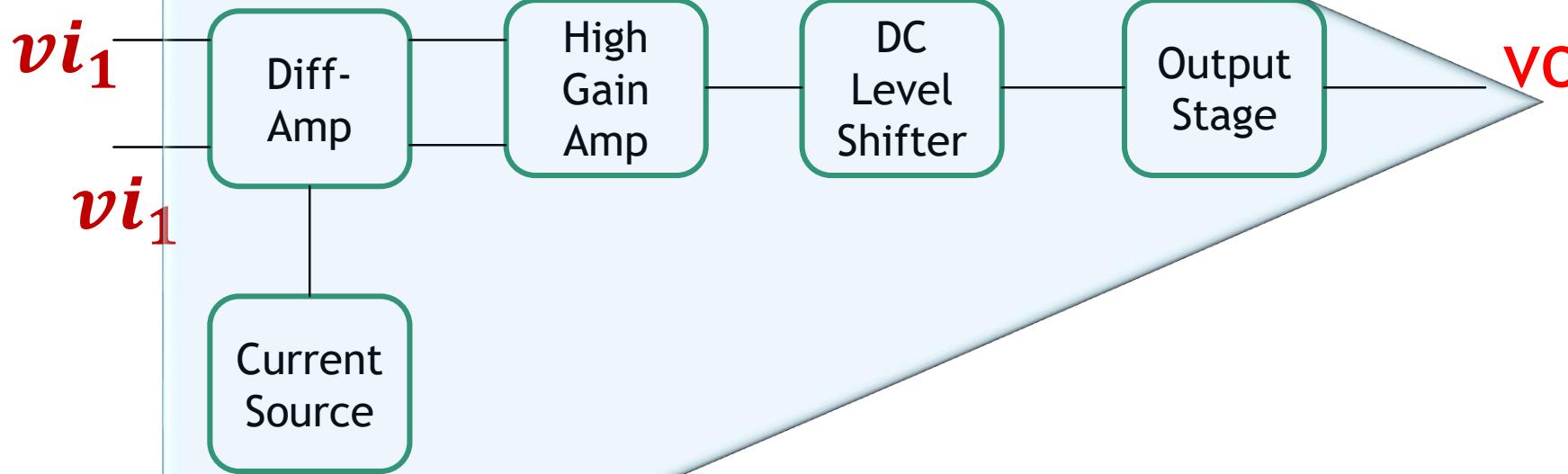Designed to do mathematical operations such as addition , subtraction



The Operational Amplifier

DC Level Shifter

To make $v_o = 0$, when

$$v_{i1} = v_{i2} = 0$$


$$R_C = \text{?????}$$

$$R_{TH} = 2.3k \parallel 3.7k = 1.418\text{ k}\Omega$$

$$V_{TH} = \frac{2.3k}{2.3k + 3.7k}(-6) = -2.2\text{ V}$$

$$I_{E2} = \frac{V_{TH} - 0.7 + 6}{3k + \frac{R_{TH}}{\beta + 1}}$$


$$I_{E2} = 1.0285\text{ mA}$$

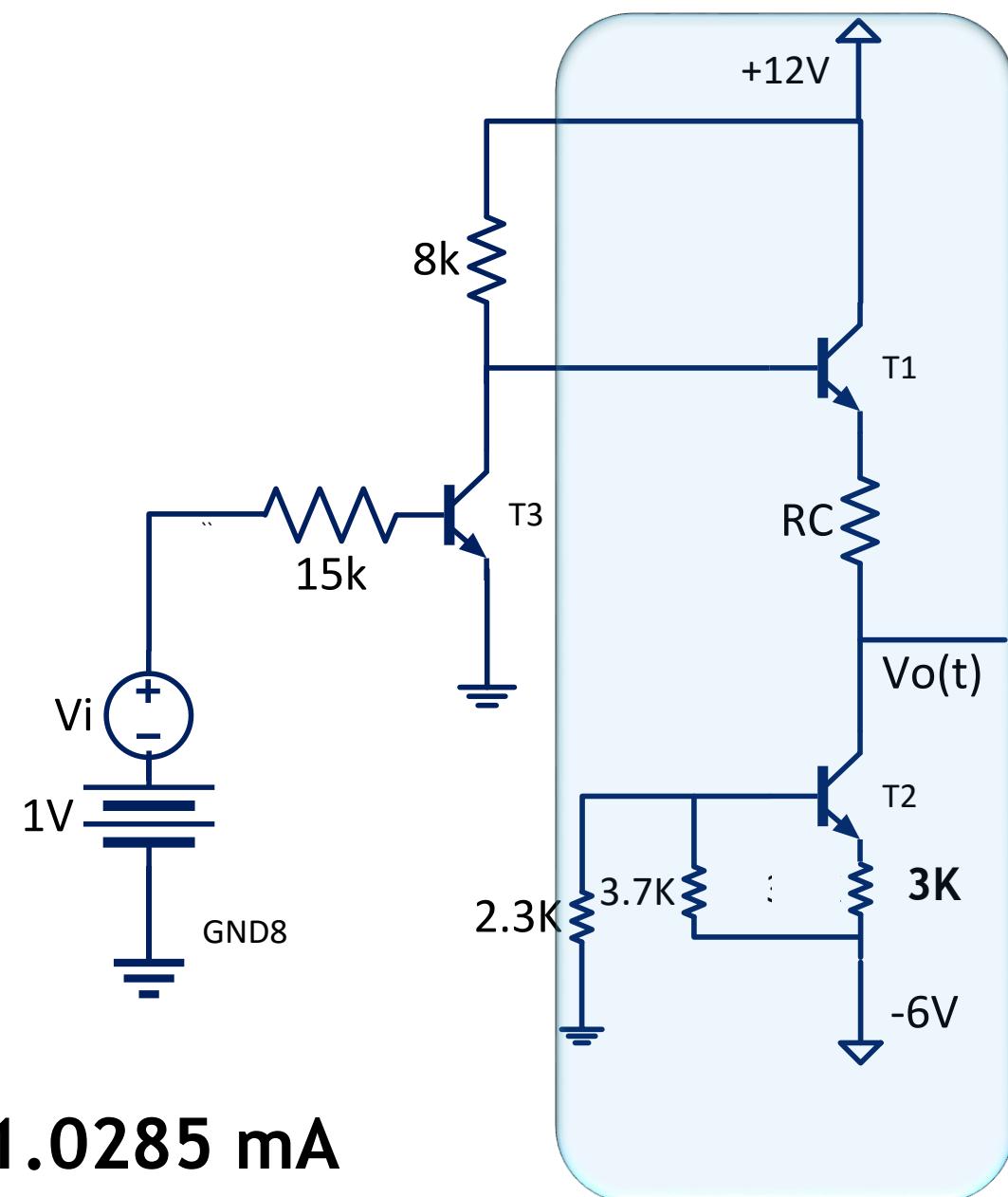

$$I_{B3} = \frac{1-0.7}{15k} = 0.02\text{mA} \blacktriangleright$$

$$I_{C3} = 1\text{mA}$$

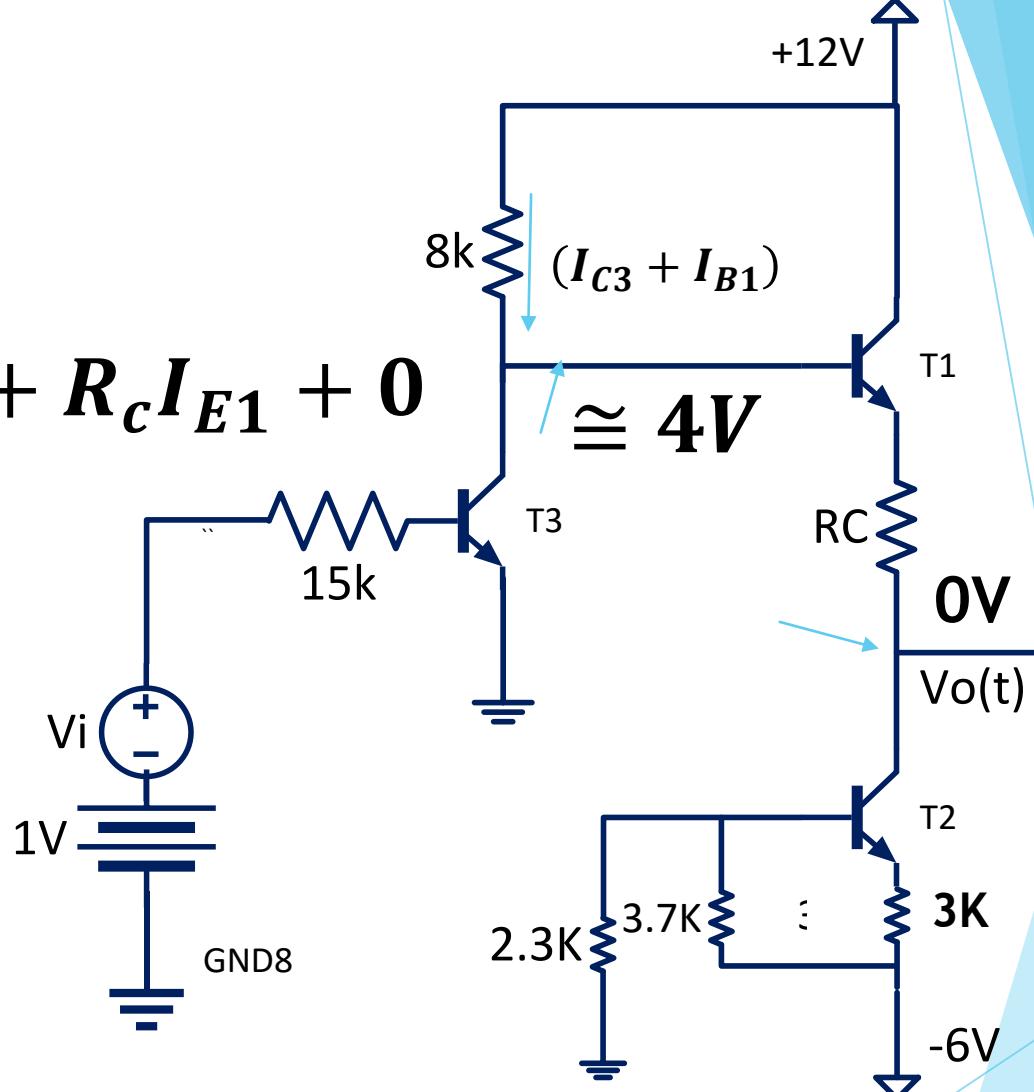
$$12 = 8k(I_{C3} + I_{B1}) + 0.7 + R_c I_{E1} + 0 \\ \therefore R_c \approx 3.3k$$




THE FUNCTION OF THE CAPACITOR

The Operational Amplifier

Ac Small signal equivalent Circuit:

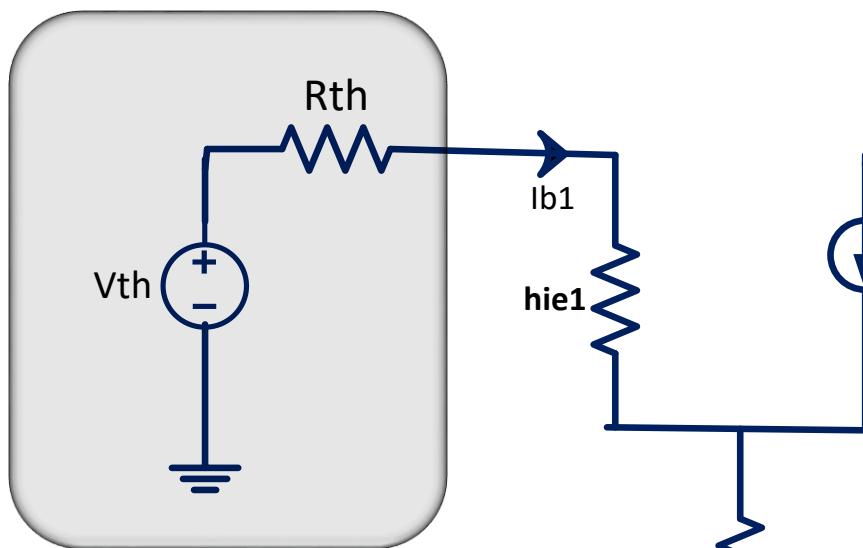


Emitter equivalent circuit

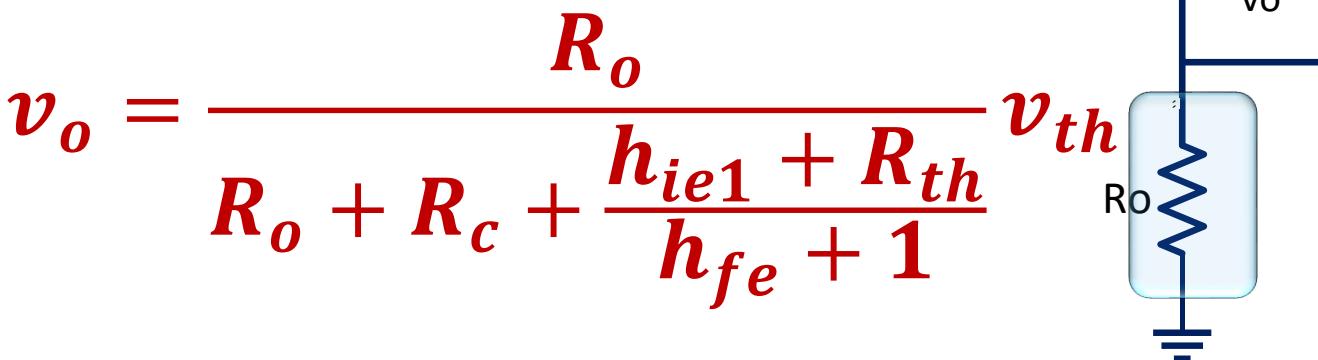


$$v_o = \frac{R_o}{R_o + R_c + \frac{h_{ie1} + R_{th}}{h_{fe} + 1}} v_{th}$$

$$v_o \approx v_{th}$$

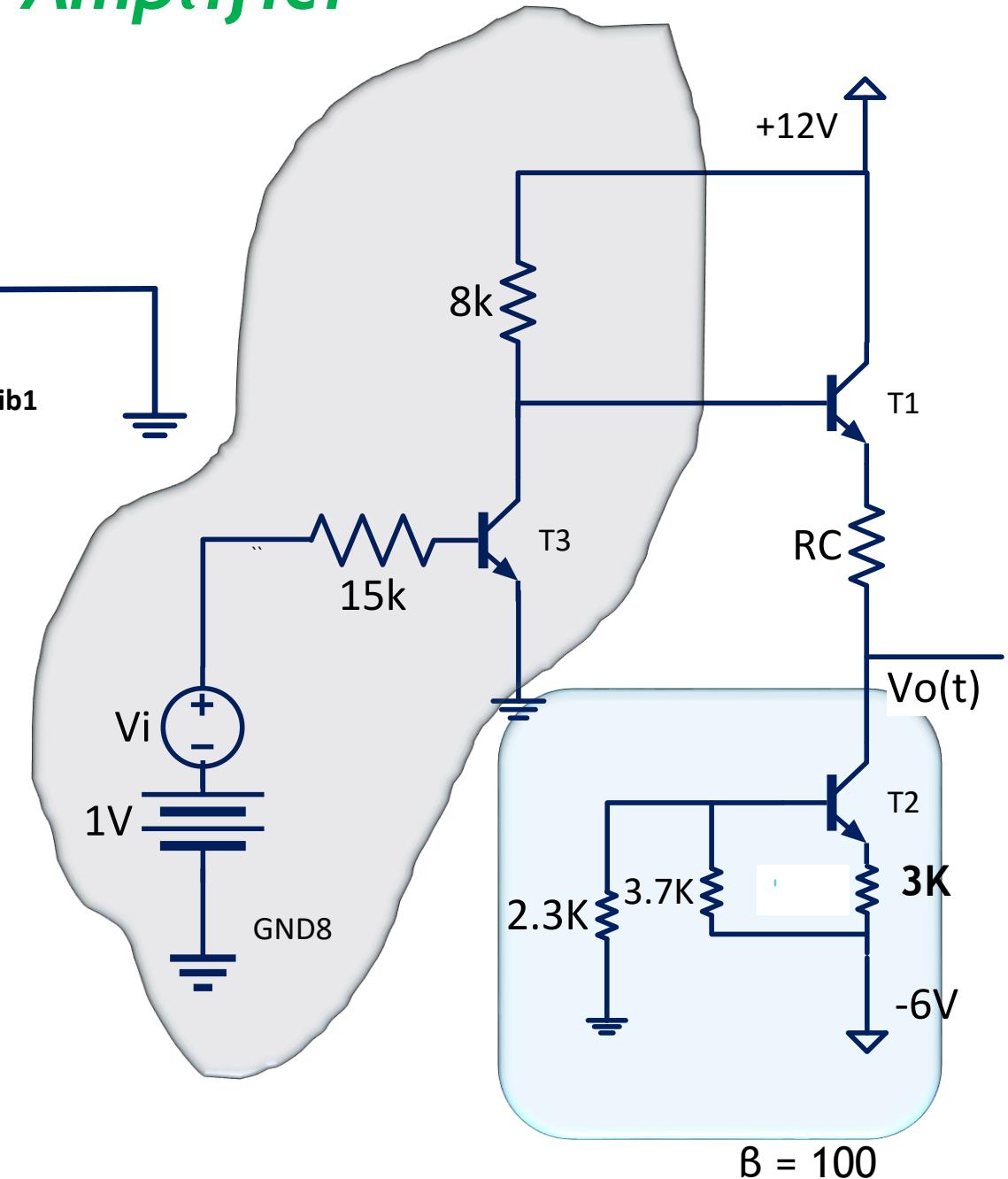

Complete Operational Amplifier

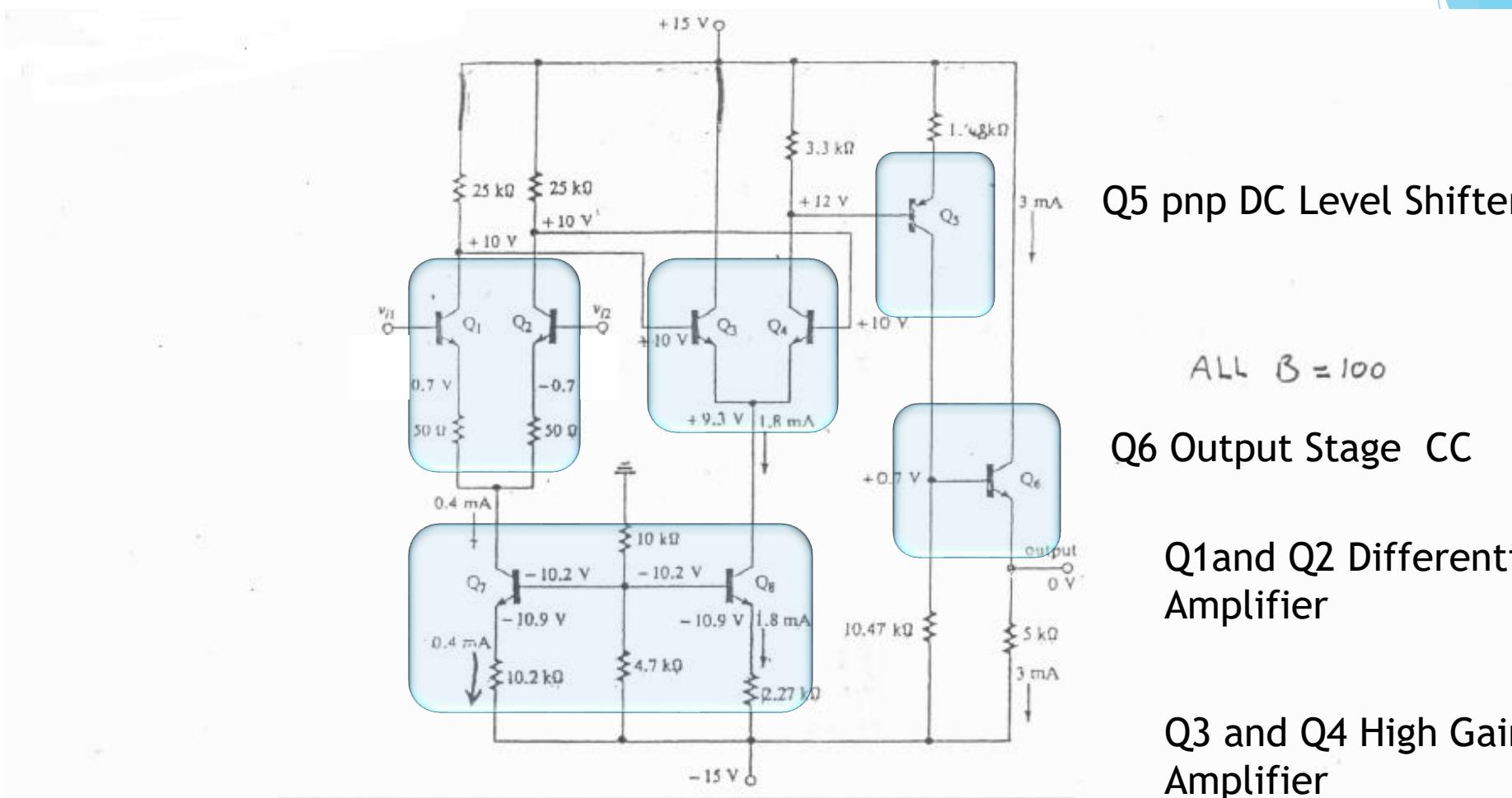

Q5 pnp DC Level Shifter


ALL $\beta = 100$

Q6 Output Stage CC

Q1 and Q2 Differential Amplifier

Q3 and Q4 High Gain Amplifier


Q7 and Q8 Current Source

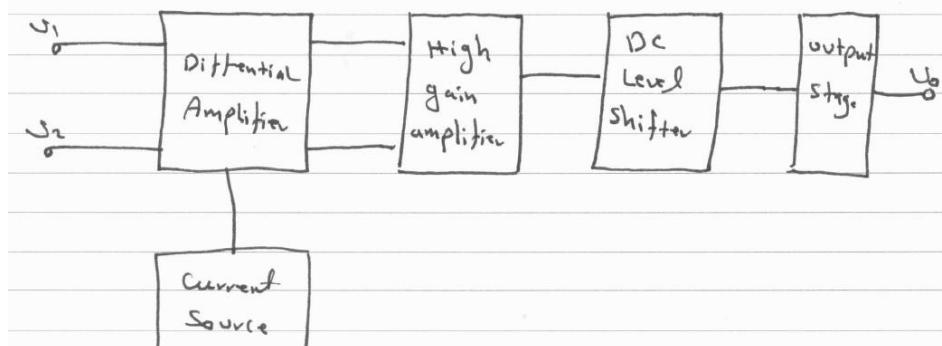

Complete Operational Amplifier :

DC Analysis :

$$V_{i2} = V_{i1} = 0$$

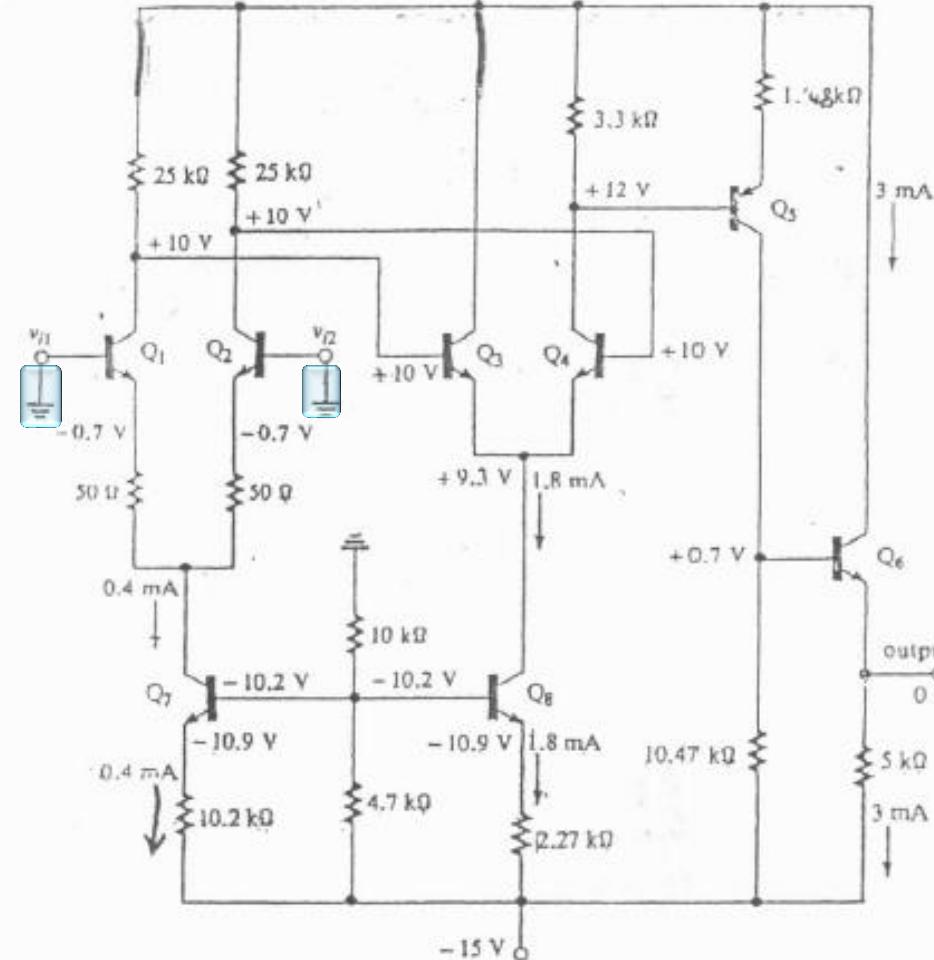

All $\beta = 100$

ALL $\beta = 100$

$$V_{B7} = V_{B8} = (10K) \cdot (-15V) / (10K + 4.7K) = -10.2V$$

$$V_{E7} = V_{E8} = -10.2V - 0.7V = -10.9V$$

$$I_{E7} = (+15 - 10.9) / R_{E7} = 0.4mA$$

$$I_{E8} = (+15 - 10.9) / R_{E8} = 1.8mA$$

$$ICQ1 = ICQ2 = 0.5 IE7 = 0.2mA$$

$$ICQ3 = ICQ4 = 0.5 IE8 = 0.9mA$$


$$0 = 3.3K (IC4-IB5) + VBE5 - 1.48K IE5$$

$$IE5 = 1.53 mA$$

$$VBE6+5K IE6 - 10.47K (IC5-IB6) = 0$$


$$IE6 = 3mA$$
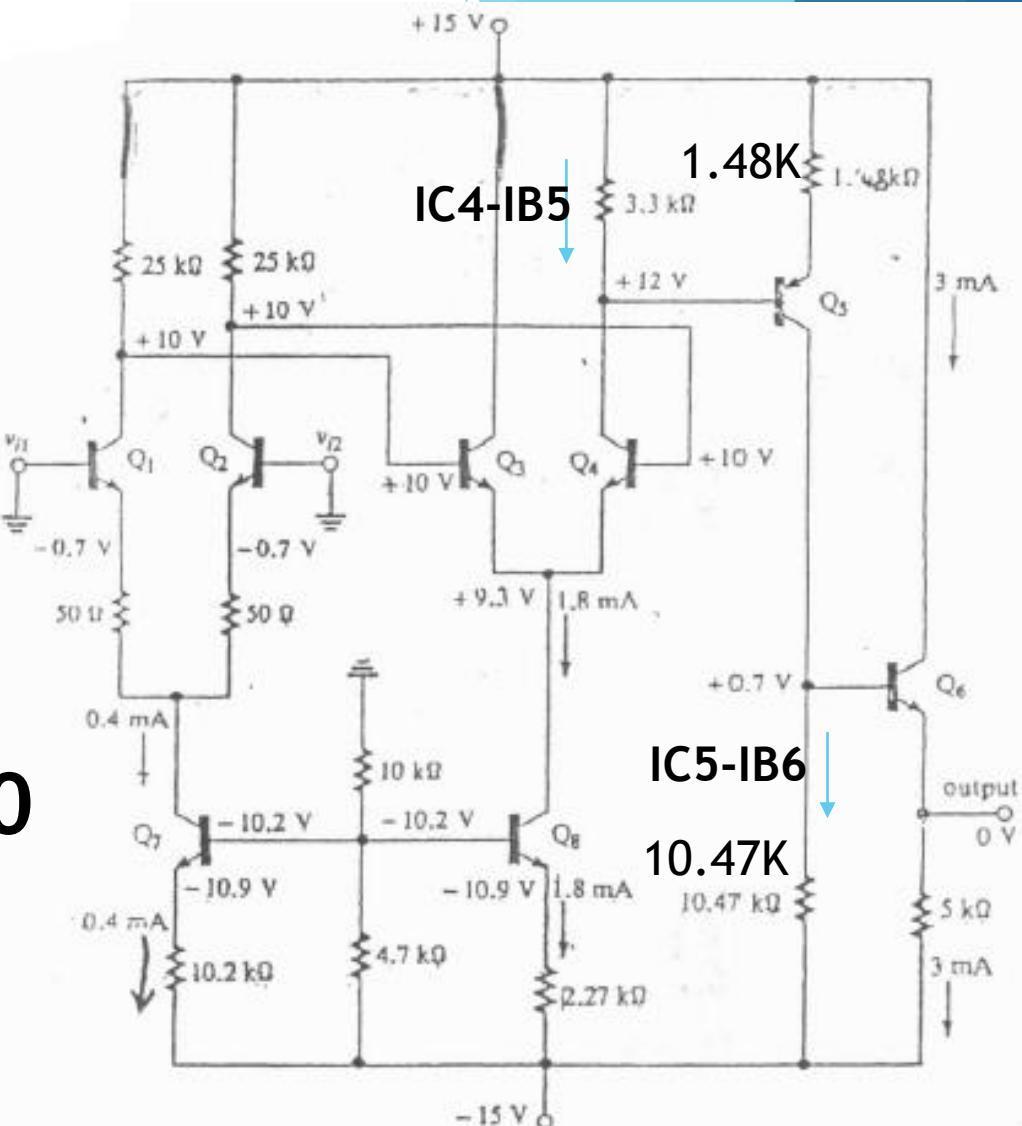
$$\text{Or } IE6 = \frac{0 - (-15)}{5K} = 3mA$$



Review

Ac Analysis : Differential Mode Analysis

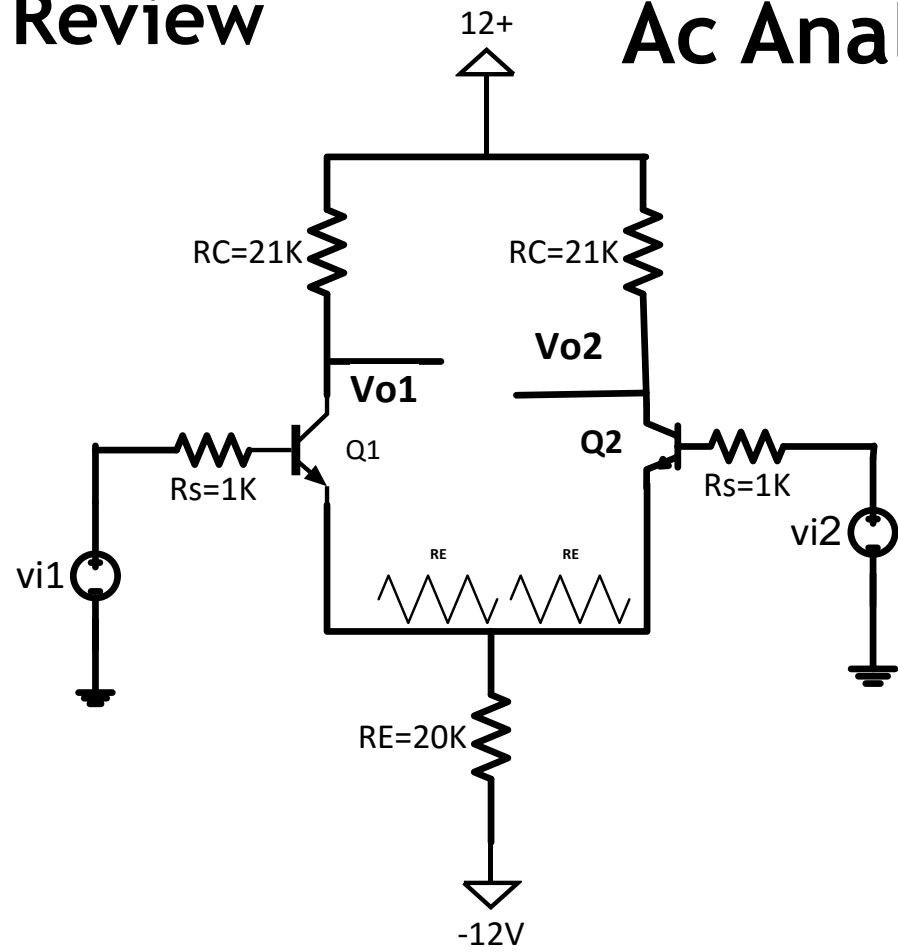


$$v_{o1} = \frac{R_c v_d}{2 \left(h_{ib} + \frac{R_s}{h_{fe+1}} \right)}$$

If we have $RE1 = RE2$


$$v_{o1} = \frac{R_c v_d}{2 \left(h_{ib} + RE1 + \frac{R_s}{h_{fe+1}} \right)}$$



$$v_{o2} = - \frac{R_c v_d}{2 \left(h_{ib} + RE1 + \frac{R_s}{h_{fe+1}} \right)}$$
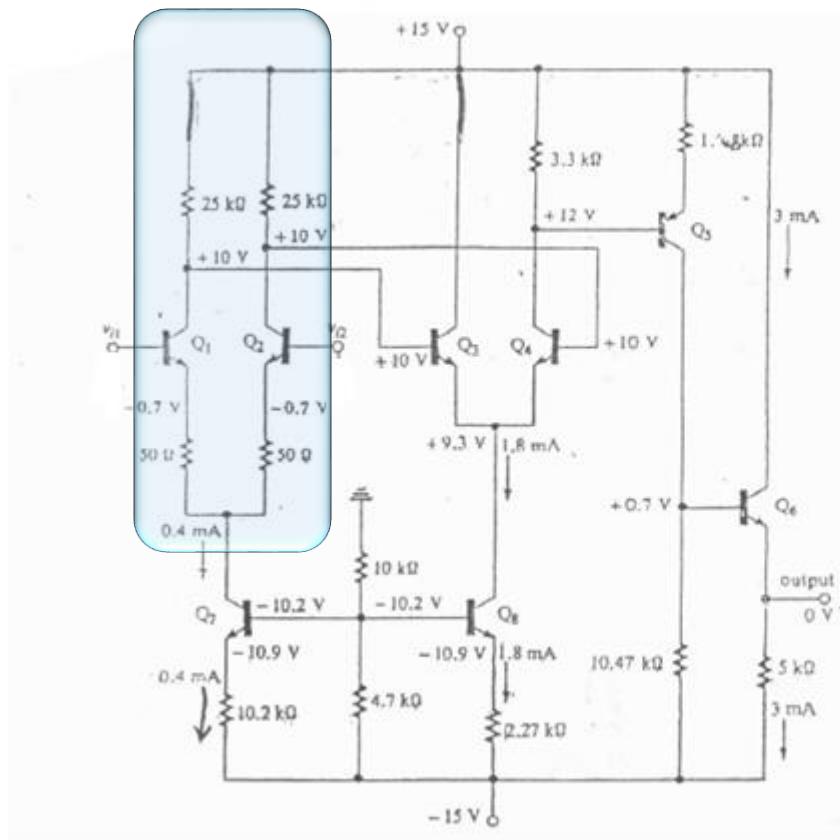
$$v_{o2} = - \frac{R_c v_d}{2 \left(h_{ib} + \frac{R_s}{h_{fe+1}} \right)}$$



All $\beta = 100$

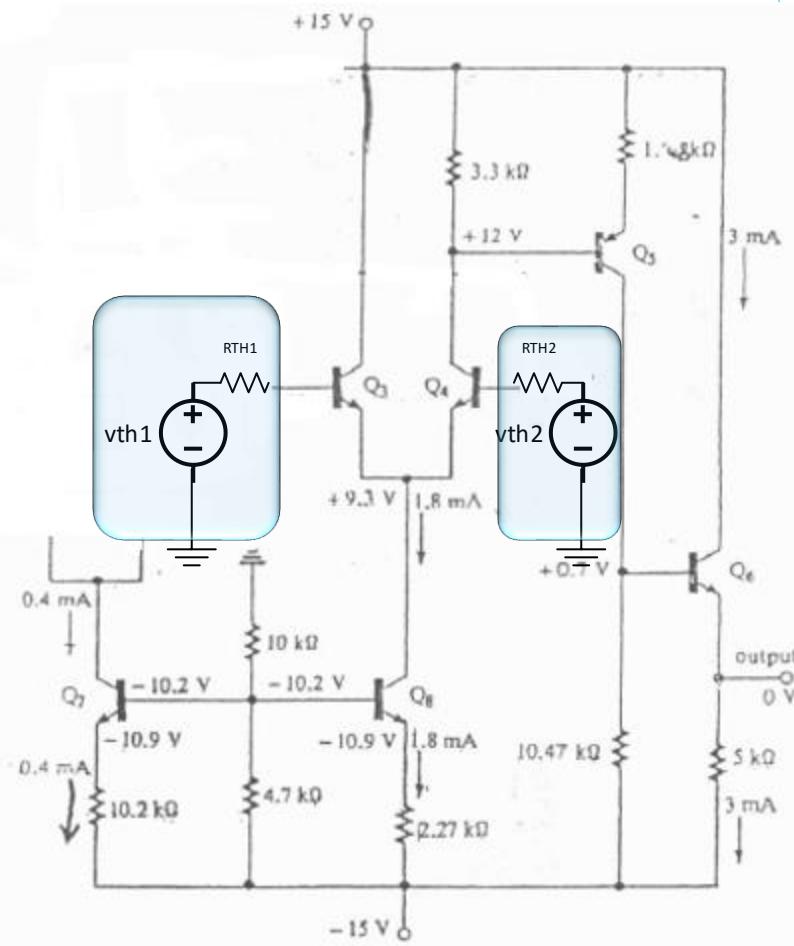

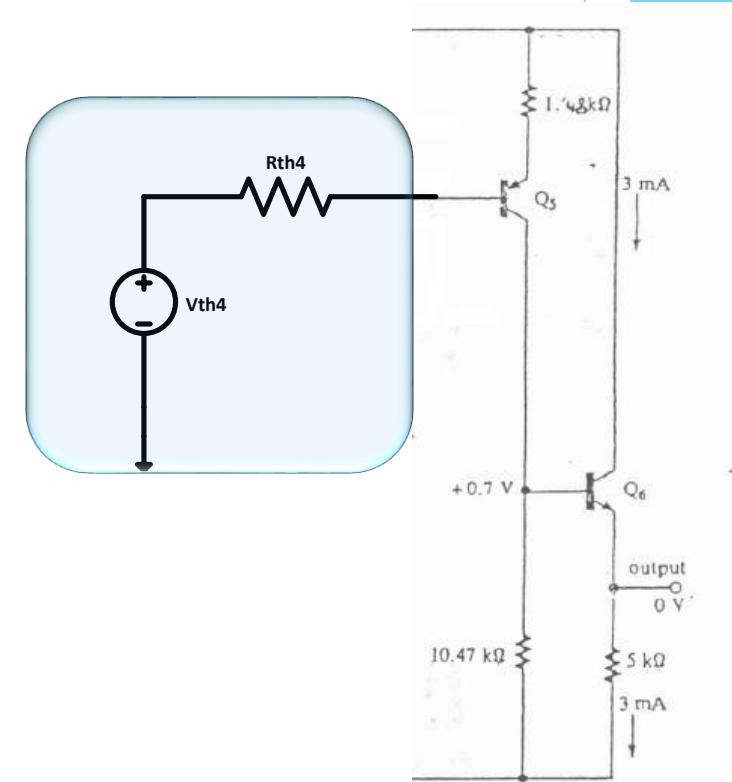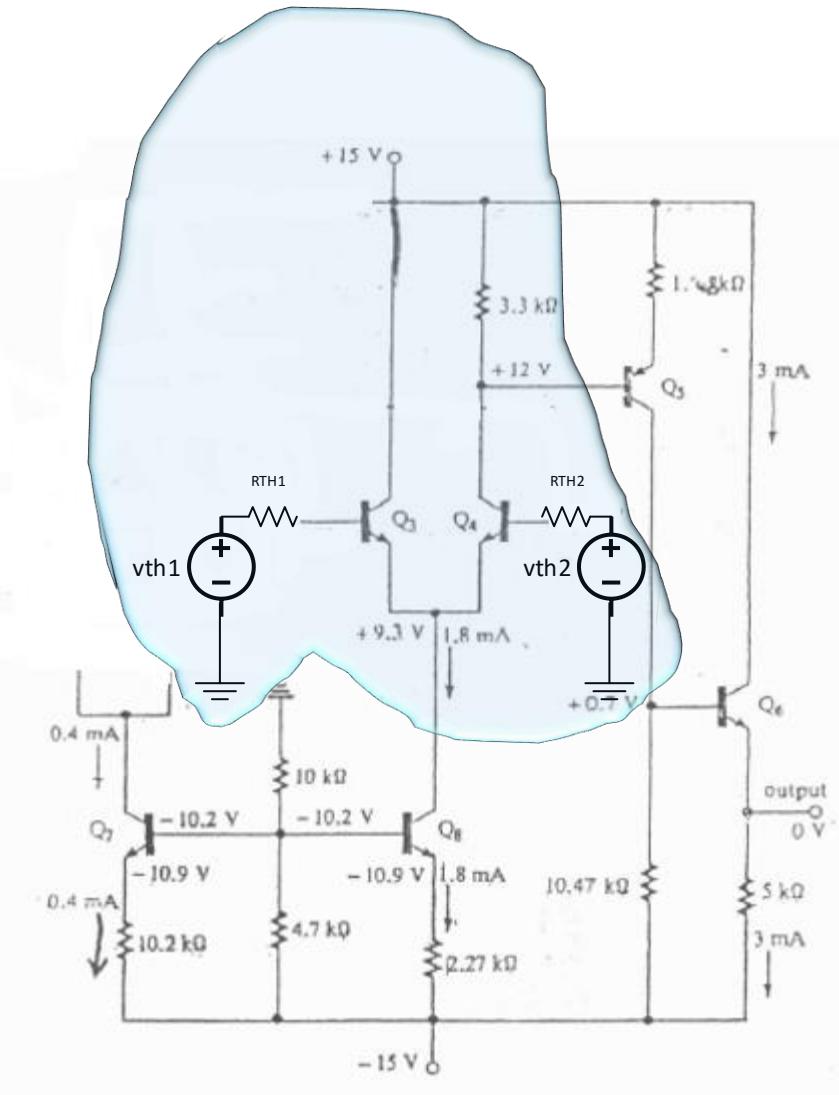

All $\beta = 100$

Ac Small signal Analysis

$$hie1 = 13k\Omega$$

$$hie2 = 13k\Omega$$

$$hie3 = 2.89k\Omega$$

$$hie4 = 2.89k\Omega$$

$$hie5 = 1.7k\Omega$$

$$hie6 = 0.87k\Omega$$

$$V_{th1} = \frac{\left(+\frac{v_{d1}}{2} \right) R_{c1}}{R_{e1} + h_{ib1} + R_s1 / (h_{fe} + 1)}$$



$$R_s1 = 0 \quad v_{d1} = V_{i2} - V_{i1}$$


$$V_{th1} = 69.4 V_{d1} \quad R_{th1} = R_{c1} = 25K$$

$$V_{th2} = -V_{th1} = \frac{-\left(+\frac{v_{d1}}{2} \right) R_{c1}}{R_{e1} + h_{ib1} + R_s1 / (h_{fe} + 1)}$$

$$V_{th2} = -69.4 V_{d1}$$

$$R_{th2} = 25K$$

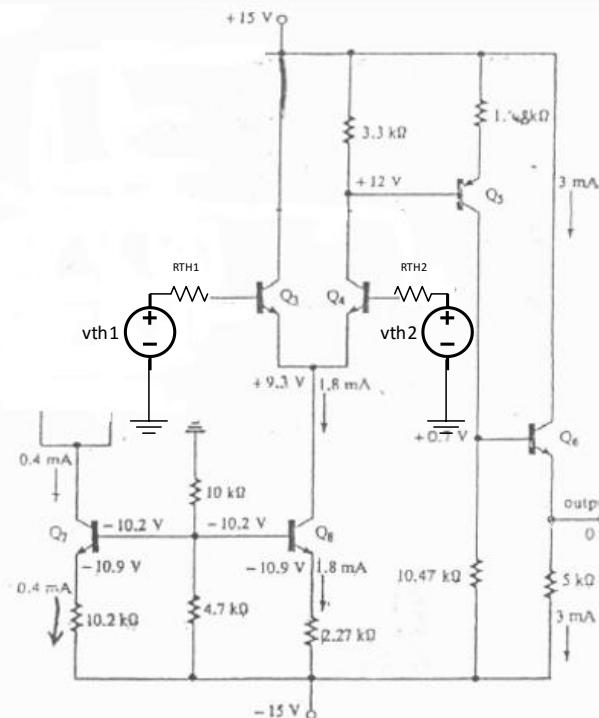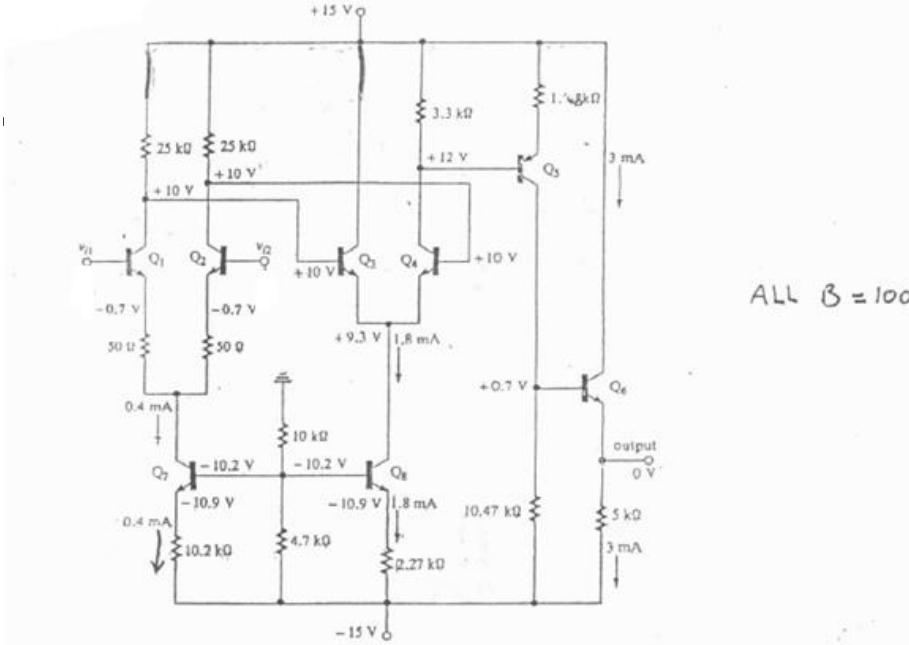

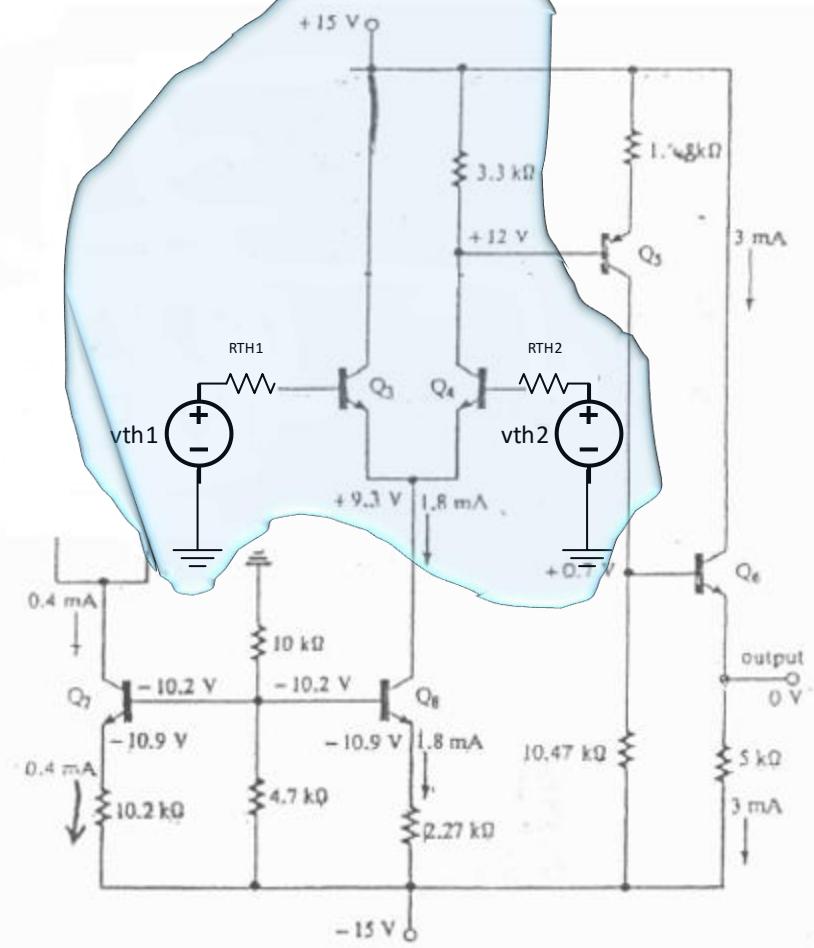


$$V_{th4} = \frac{-\left(\frac{vd4}{2}\right)RC4}{Re4+hib4+Rs4/(hfe+1)} = 829 Vd4$$

$$\text{Re4} = 0$$


$$Rs4 = 25K$$

$$V_{d4} = (V_{th2} - V_{th1})$$

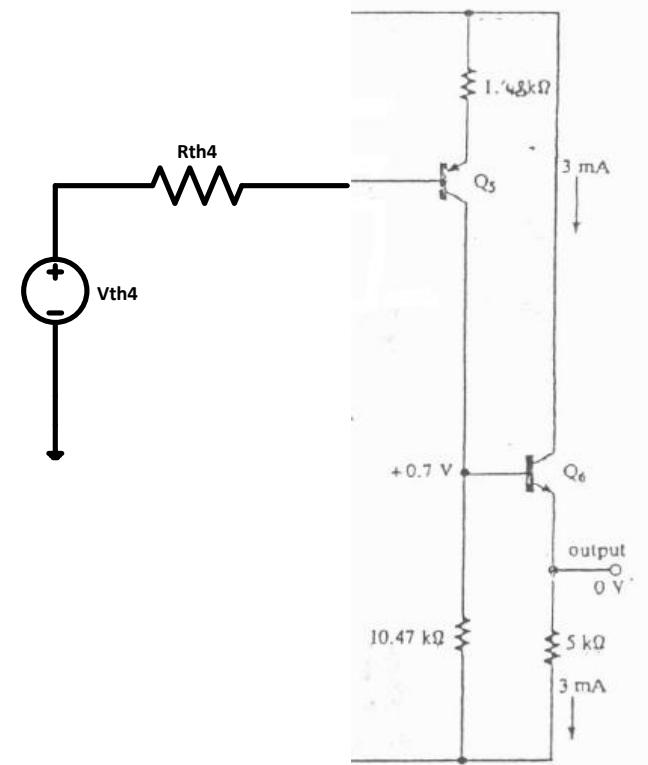

$$R_{th4} = 3.3k$$

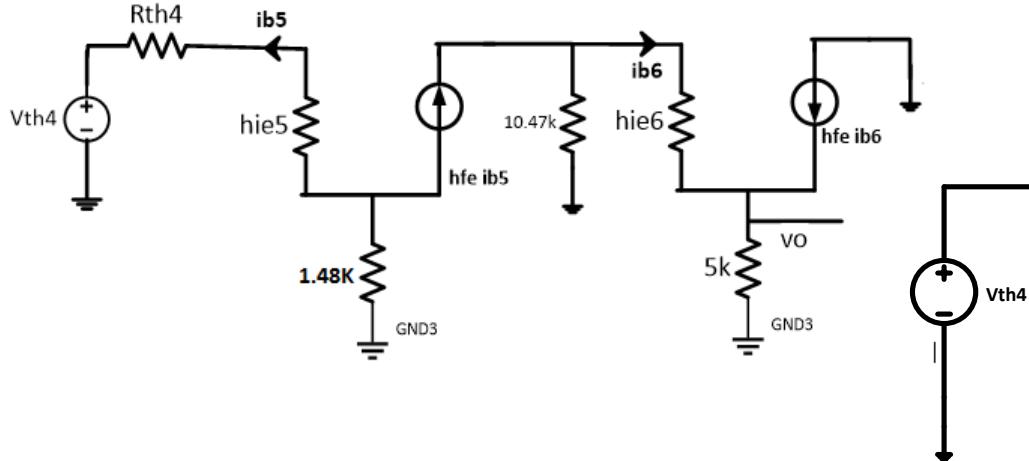Ac Small Signal Equivalent Circuit Of the DC Level Shifter and the Output Stages :





$$V_o = 5k i_{e6} ; i_{e6} = (1+hfe) i_{b6}$$

$$i_{b6} = \frac{10.47k \cdot hfe i_{b5}}{10.47k + hie6 + 5k(1+hfe)}$$



$$i_{b5} = \frac{-v_{th4}}{R_{th4} + hie5 + 1.48k(1+hfe)}$$
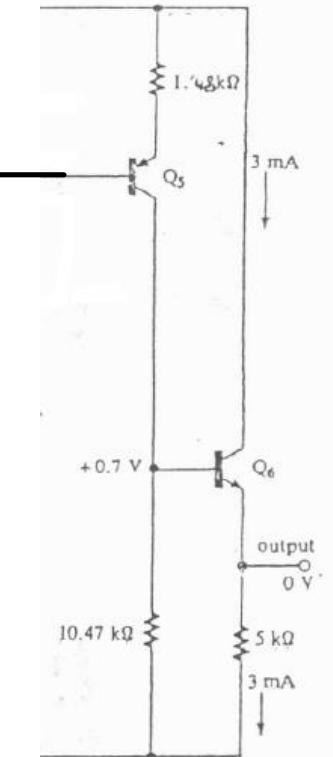
$$V_o = -5540 v_{d1} = +5540 (v_i1 - v_i2)$$



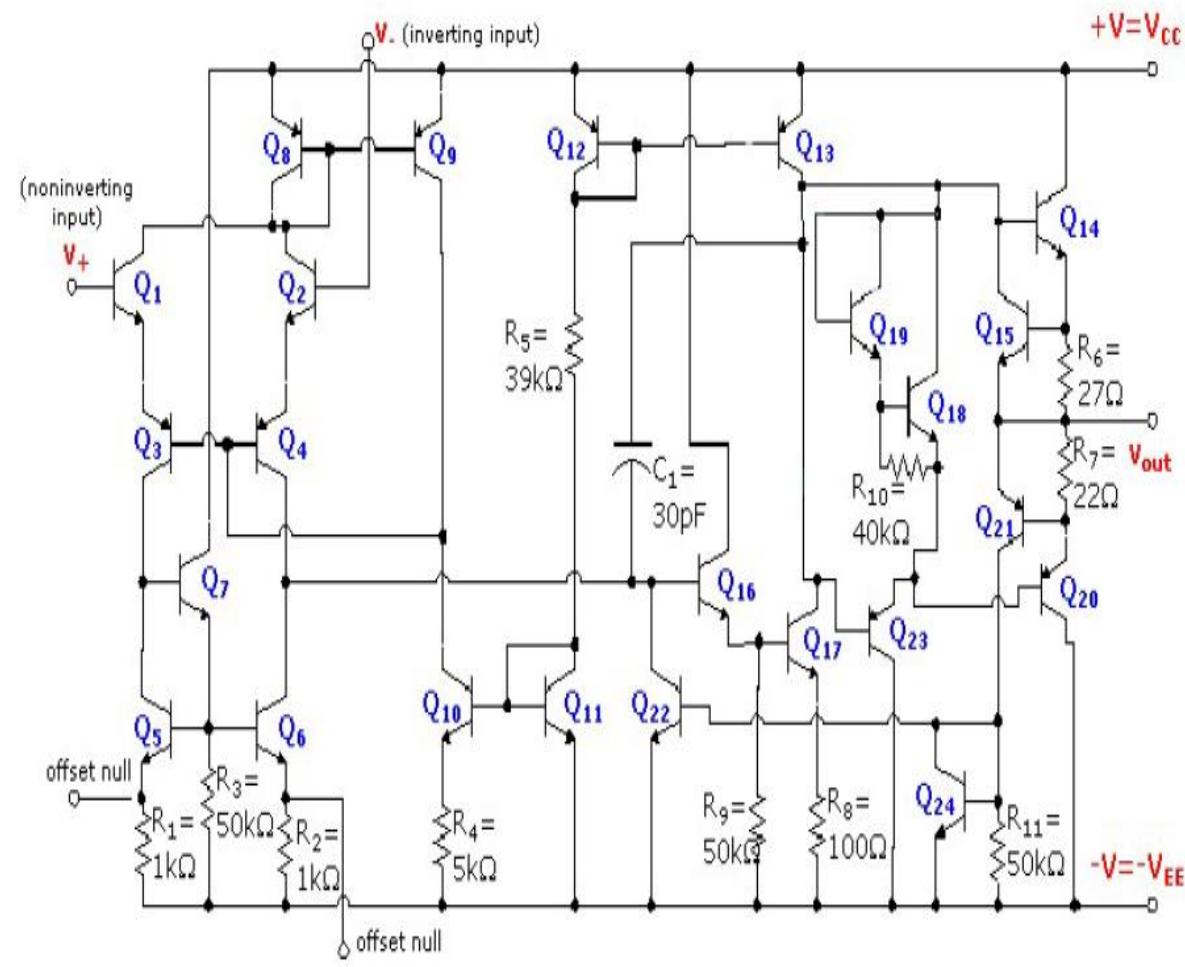

Operational Amplifier

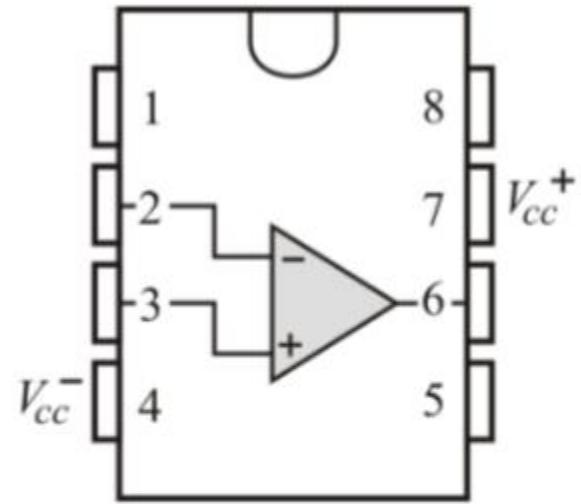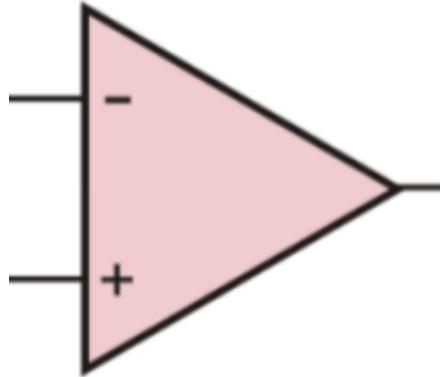

741 Op-Amp Pin out