

# Negative Feedback

## Negative Feedback

### Advantages

- 1-Stabilizes the gain of the amplifier against parameters changes in the active devices due to temperature .
- 2- Modifies the input and output impedance in any desired fashion.
- 3- Increases the Bandwidth .

### Disadvantages

- 1- Decreases the gain .
- 2- Oscillation .

## Negative Feedback

### General Feedback equation

$$S_o = AS_\epsilon$$


$$S_\epsilon = S_i - S_{fb}$$

$$A_f = \frac{S_o}{S_i} = \frac{A}{1+A\beta}$$

$A \beta \equiv \text{Loop gain}$

If  $A \beta \gg 1$

$$\therefore A_f = \frac{1}{\beta}$$

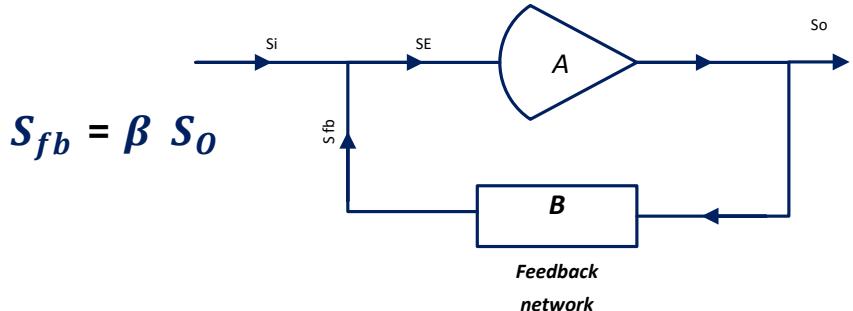

## Negative Feedback

### General Feedback equation

$$S_\epsilon = S_i - S_{fb}$$


$$S_\epsilon = S_i - \beta S_o$$

$$S_\epsilon = S_i - \beta \frac{A}{1+AB} S_i$$

$$S_\epsilon = S_i \left(1 - \frac{A\beta}{1+A\beta}\right)$$

If  $A \beta \gg 1$
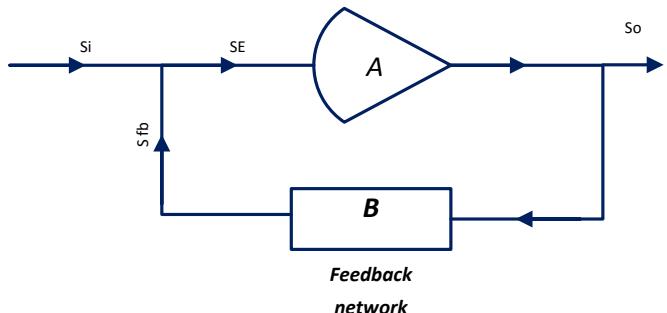
$$S_\epsilon \approx S_i \left(1 - \frac{A\beta}{A\beta}\right) \approx 0$$



## Negative Feedback


### Gain stabilization

$$\text{let } A = 10,000$$

$$\beta = 0.01$$

$$\therefore A\beta = 100$$

$$Af = \frac{A}{1 + A\beta} = 99$$

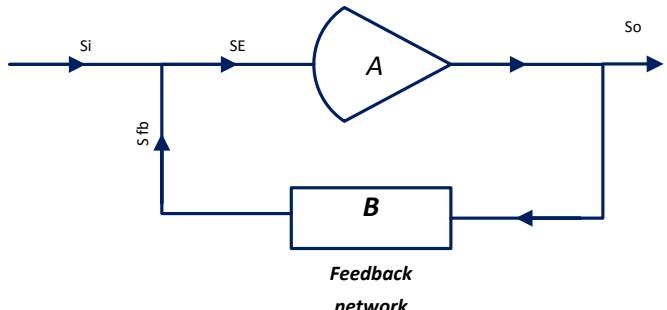

$$\text{let } A = 9000$$

$$\beta = 0.01$$

$$\therefore A\beta = 90$$

$$Af = \frac{A}{1 + A\beta} = 98.9$$

Change in  $A \rightarrow$  change in  $Af$

$$10\% \rightarrow 0.1\%$$

## Negative Feedback

### Increasing the Bandwidth.

#### At high frequency

$$A(jw) = \frac{A_m}{1 + \frac{jw}{w_2}}$$

$$\therefore wH = w2$$

#### With Negative Feedback

$$Af(jw) = \frac{A(jw)}{1 + A(jw)\beta}$$



$$Af(jw) = \frac{A_m}{1 + A_m\beta} \cdot \frac{1}{1 + \frac{jw}{w2(1 + A_m\beta)}}$$

$$\therefore wH = w2(1 + A_m\beta)$$

## Oscillators

### The Oscillation Problem

1) At mid band

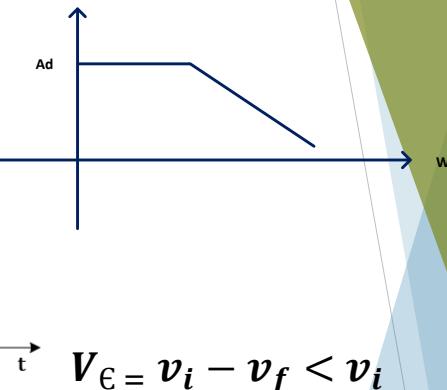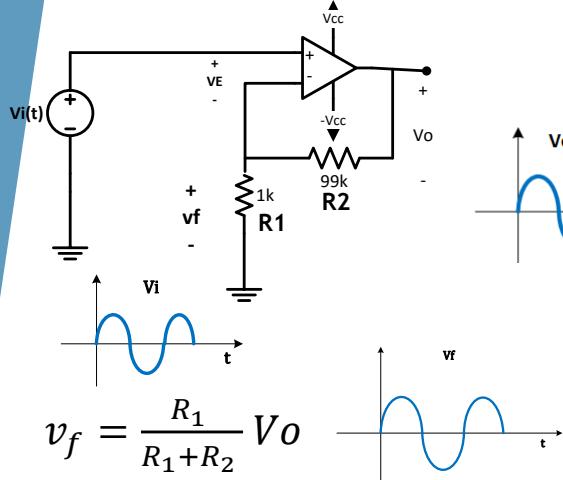


Negative Feedback

$v_f$  Opposes  $v_i$

### The Oscillation Problem

## Oscillators

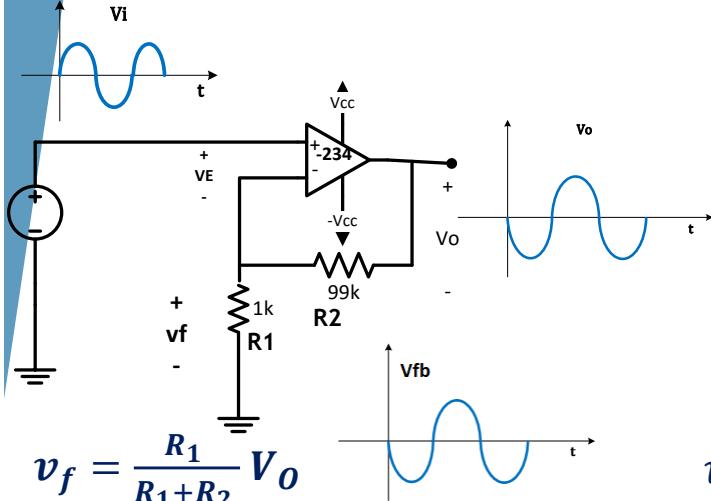2) At High-frequency (phase = 180) at  $w_0$



Positive Feedback

$v_{fb}$  adds to  $v_i$

## Oscillators


### The Oscillation Problem

Now let  $v_i = 0$

$$\therefore V_E = -v_{fb}$$

$$V_o = AV_E$$
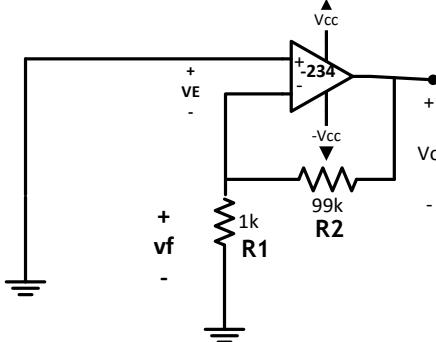
$$v_{fb} = \frac{R_1}{R_1+R_2} V_o = \frac{1}{100} V_o$$



## Oscillators

### The Oscillation Problem

1. Let  $V_{E1} = 1\text{mV peak}$

$$V_{o1} = -234\text{mV peak}$$


$$V_{fb1} = -2.34\text{mV peak}$$

2.  $V_{E2} = -v_{fb1} = 2.34\text{mV peak}$

$$V_{o2} = -548\text{ mV peak}$$

$$V_{fb2} = -5.48\text{ mV peak}$$

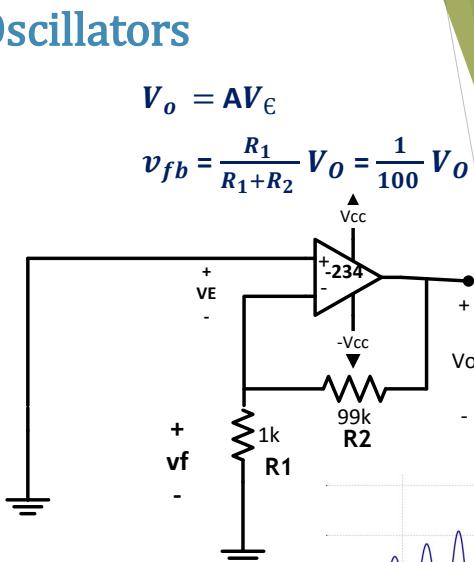3.  $V_{E3} = -V_{fb2} = 5.48\text{mV peak}$



## Oscillators

### The Oscillation Problem


**Building up voltage**

$$|V_{fb1}| > |V_{\epsilon 1}|$$

$$|\beta V_{o1}| > |V_{\epsilon 1}|$$

$$|A\beta V_{\epsilon}| > |V_{\epsilon 1}|$$

$$\therefore |A\beta| > 1$$

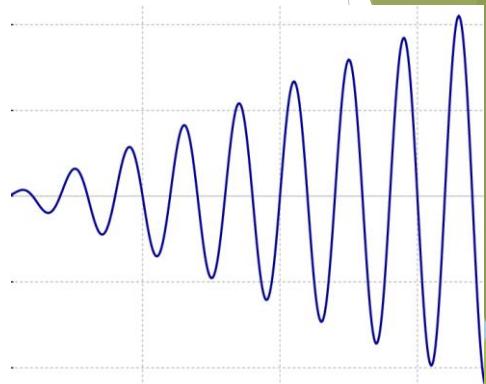

### The Oscillation Problem

**1. Let  $A = -100$**

$$V_{\epsilon 1} = 100 \text{ mV peak}$$

$$\therefore V_{o1} = -10 \text{ V peak}$$

$$V_{fb1} = -100 \text{ mV peak}$$

**2.  $V_{\epsilon 2} = -V_{fb} = 100 \text{ mV peak}$**

$$V_{o2} = -10 \text{ V peak}$$



$$V_{fb2} = -100 \text{ mV peak}$$

**The output signal is sustained**

$$|V_{fb1}| = |V_{\epsilon 1}|$$

$$|A\beta| = 1$$

## Oscillators

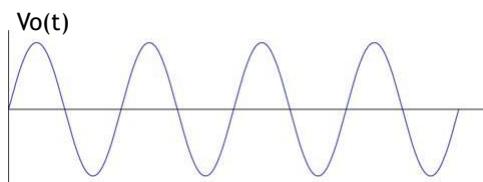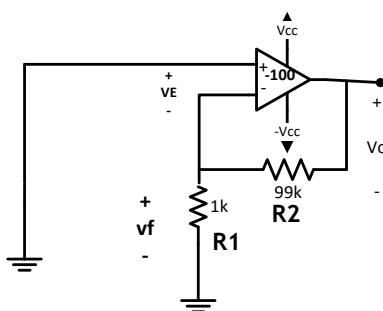

## Oscillators

### The Oscillation Problem

Now let change  $R_2 = 299K$

$$\therefore \beta = \frac{1}{300}$$

$$A = -234$$


$$1. V_{\epsilon 1} = 1 \text{ mV peak}$$

$$V_{o1} = -234 \text{ mV peak}$$

$$v_{fb1} = -0.78 \text{ mV peak}$$

$$2. V_{\epsilon 2} = -v_{fb1} = 2.34 \text{ mV peak}$$

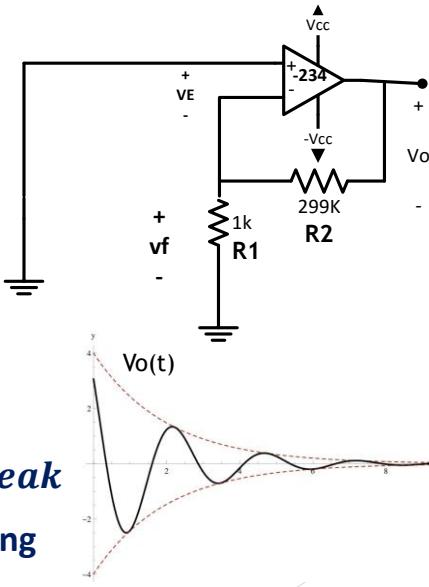$\therefore V_{\epsilon}, V_o, v_{fb}$  are decreasing down



## Oscillators

### The Oscillation Problem

#### White noise

-All active and passive devices will generate small levels (typically, nano volts or less ) of white noise.

-White noise are random generation of electrical signal that encompass the frequency spectrum from dc (0Hz) to extremely high (many giga hertz frequencies).

-Thermal energy will produce a random motion in free electrons . this random electrons motion serves to produce a random current . If this random current exists in a resistor , a random (noise) voltage will be developed a cross the resistor.