

- **Abstract:**

The aim of this assignment is to simulate a chopper circuit supplying a highly inductive and a purely resistive load with an IGBT as a switch. Using PSpice to show the turn-on and turn-off transitions for the voltage, current and power loss in the IGBT. And by calculations the conduction and the switching power losses will be obtained.

- **Theory:**

A chopper is basically a dc to dc converter whose main function/usage is to create adjustable dc voltage from fixed dc voltage sources through the use of semiconductors. In other words, a chopper is a high speed switch which connects and disconnects the load from source at a high rate to get variable or chopped voltage at the output.

The Insulated Gate Bipolar Transistor (IGBT), is a power semiconductor device basically used as a switch, IGBT combines between a Bipolar Junction Transistor (BJT), and a Field Effect Transistor (MOSFET), and it has a simple gate-drive characteristics as MOSFETs with a high-current and low-saturation-voltage capability as BJT. To sum up, an IGBT combines an isolated-gate FET for the control input and a bipolar power transistor as a switch in a single device.

-The average switching power loss in the switch with highly inductive load is:

$$P_s = 0.5 * f_s * V_d * I_o * (t_c(\text{on}) + t_c(\text{off}))$$

-Total average switching power loss with resistive load is:

$$P_s = 1/6 * f_s * V_d * I_o * (t_c(\text{on}) + t_c(\text{off}))$$

-The average power loss dissipation during conduction is:

$$P_{on} = V_{on} * I_o * t_{on} * f_s$$

- **Calculations and Simulations:**

First part (Highly Inductive Load):

A chopper circuit supplying a highly inductive load and having an **IGBT** as a switch, has the following parameters: $I_o=25A$, $V_d=400V$, $f_s=15kHz$, $L_s=700nH$ and $t_{on}=30\mu s$. Assume linear voltage and current falls and rises during switching:

I. Calculate The conduction and the switching power losses if $t_{c(on)}=400ns$, $t_{c(off)}=600ns$, assuming that $V_{on}=2.5V$ using the appropriate derived formulas.

$$P_{switching} = (1/2) * f_s * V_d * I_o * (t_{c,on} + t_{c,off})$$

$$= (1/2) * (15k) * (400) * (25) * (1000n)$$

$$= 75 \text{ Watt}$$

$$P_{on,conduction} = f_s * V_{on} * I_o * t_{on}$$


$$= (15k) * (2.5) * (25) * (30 * 10^{-6})$$





$$= 28.125 \text{ Watt}$$

III. The total average power losses in the IGBT:

$$P_{Total} = P_{switching} + P_{on,conduction} = 103.125 \text{ Watt}$$

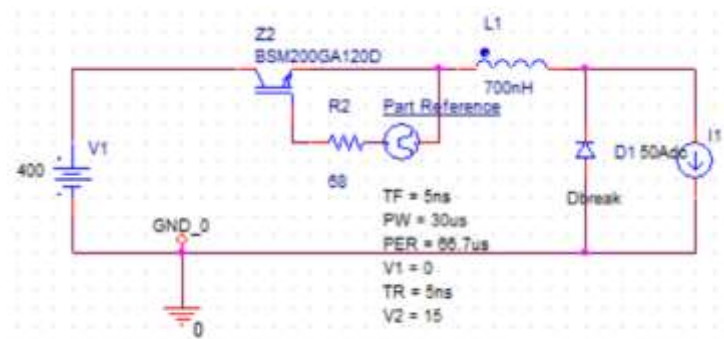II. In ORCAD/PSPICE, simulate a chopper circuit implementing an IGBT (BSM150GB50D) as a switch to supply a highly inductive load which has the following parameters: $I_o=25A$, $V_d=400V$, $f_s=15kHz$, $L_s=700nH$ and $t_{on}=30\mu s$. In the results, show the turn-on and turn-off transitions (magnified) for the voltage, current and power losses in the IGBT.



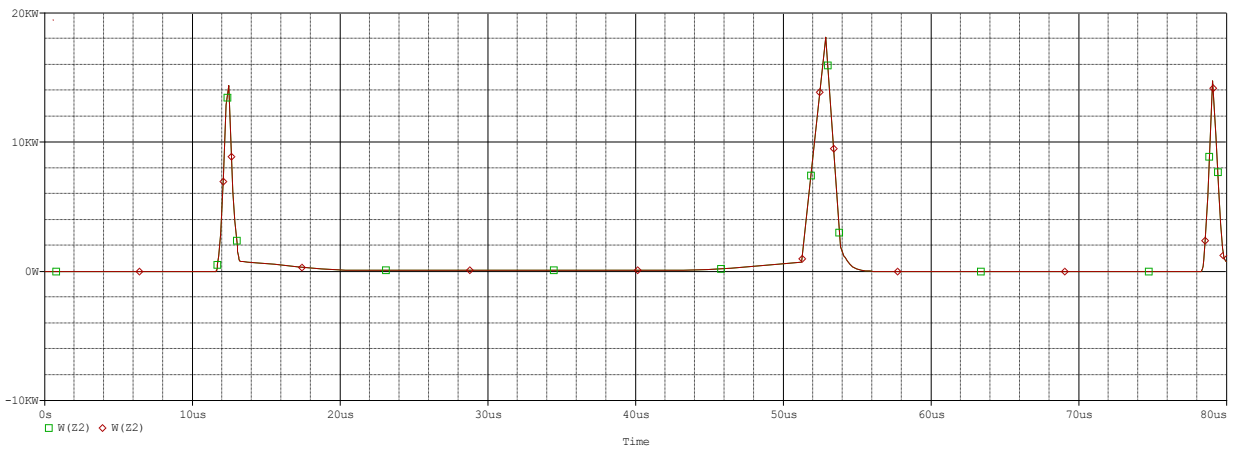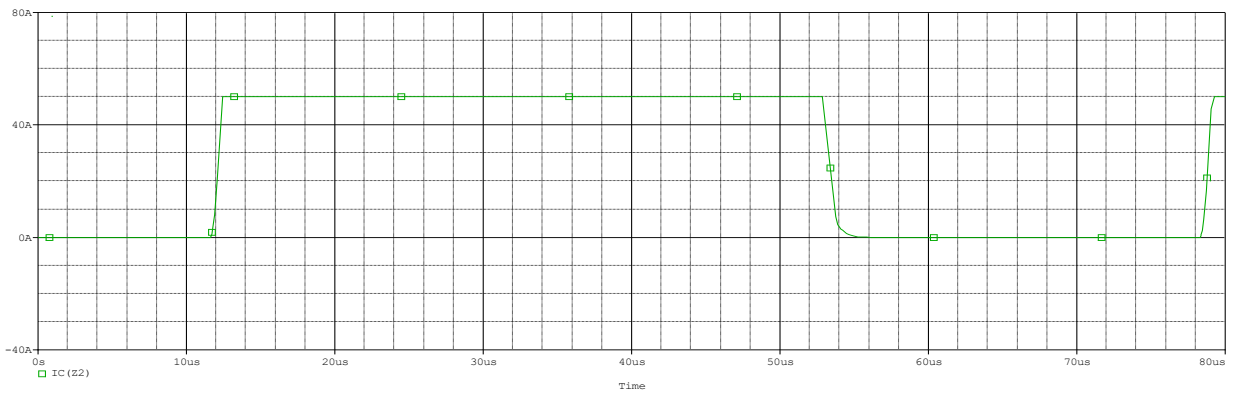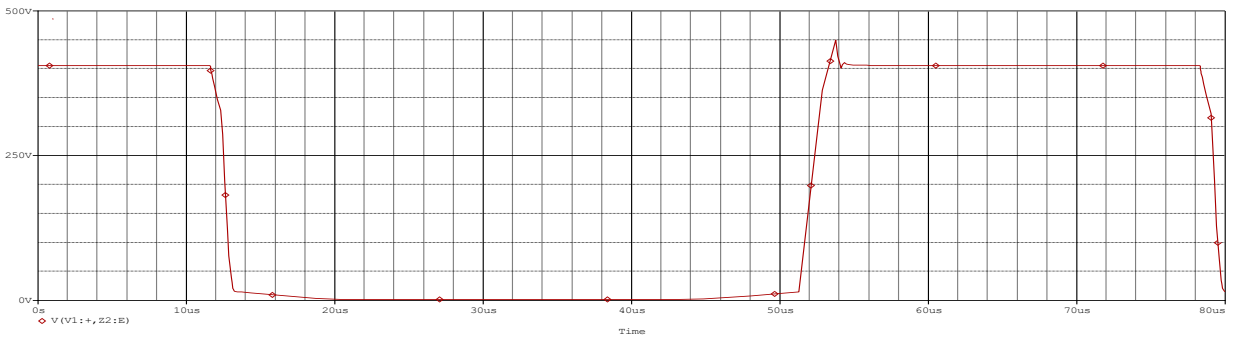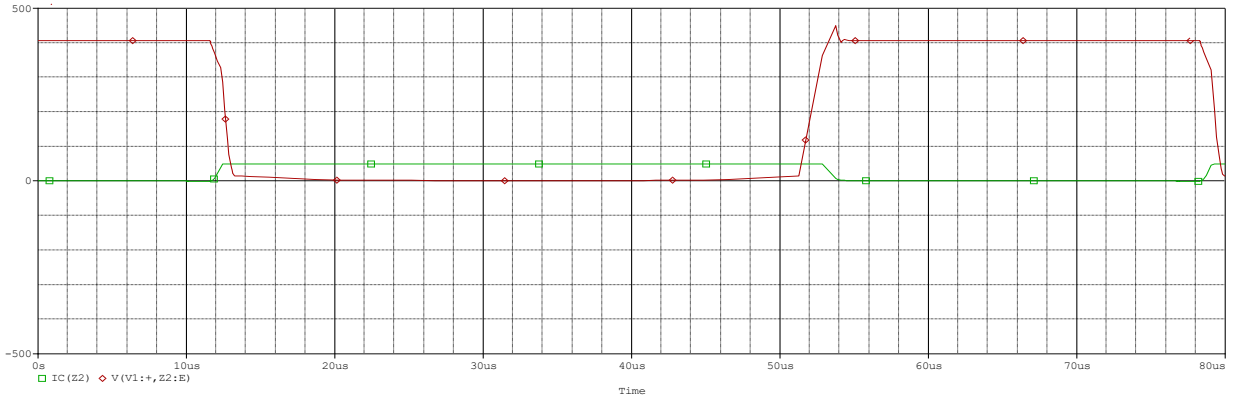

Second Part (Resistive Load):

If the chopper circuit is now supplying a purely resistive load of 15 Ohms (no parallel diode) and implementing the IGBT model. Assume linear voltage and current falls and rises during switching to:

- a) Calculate the conduction and the switching power losses if $V_d=400V$, $f_s=15kHz$, $t_{on}=30\mu s$, $t_{c(on)}=400ns$, $t_{c(off)}=600ns$, $L_s=700nH$ and $V_{on}=2.5V$ using the appropriate derived formulas.


$$\begin{aligned} P_{\text{switching}} &= \left(\frac{1}{6}\right) * f_s * V_d * I_o * (t_{c,on} + t_{c,off}) \\ &= \left(\frac{1}{6}\right) * (15k) * (400) * (25) * (1000n) \\ &= 25 \text{ Watt} \end{aligned}$$





$$\begin{aligned} P_{\text{on,conduction}} &= f_s * V_{on} * I_o * t_{on} \\ &= (15k) * (2.5) * (25) * (30n) \\ &= 28.125 \text{ Watt} \end{aligned}$$

- c) calculate the average power losses in the IGBT

$$P_{\text{Total}} = P_{\text{switching}} + P_{\text{on,conduction}} = 53.125 \text{ Watt}$$

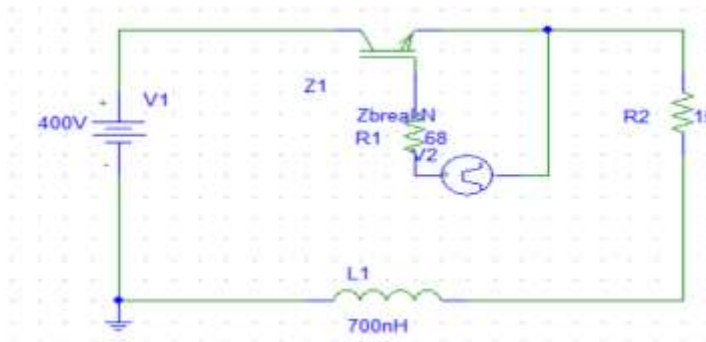- b) simulate the circuit in 2) using ORCAD/PSPICE and plot the magnified turn-on and turn off transitions of the voltage, current and power loss in the IGBT.



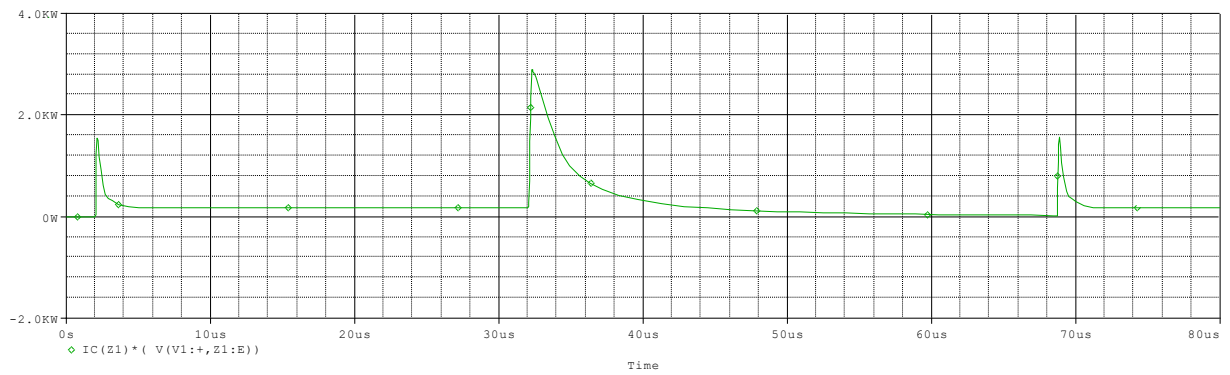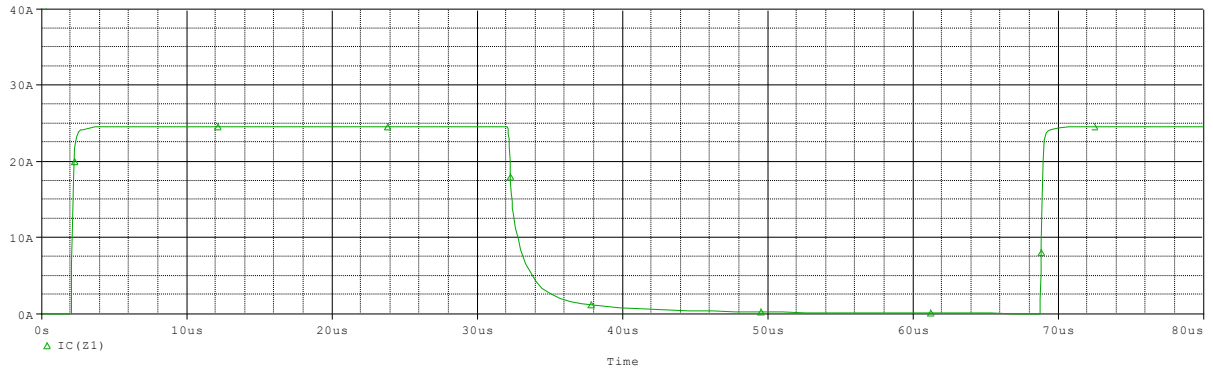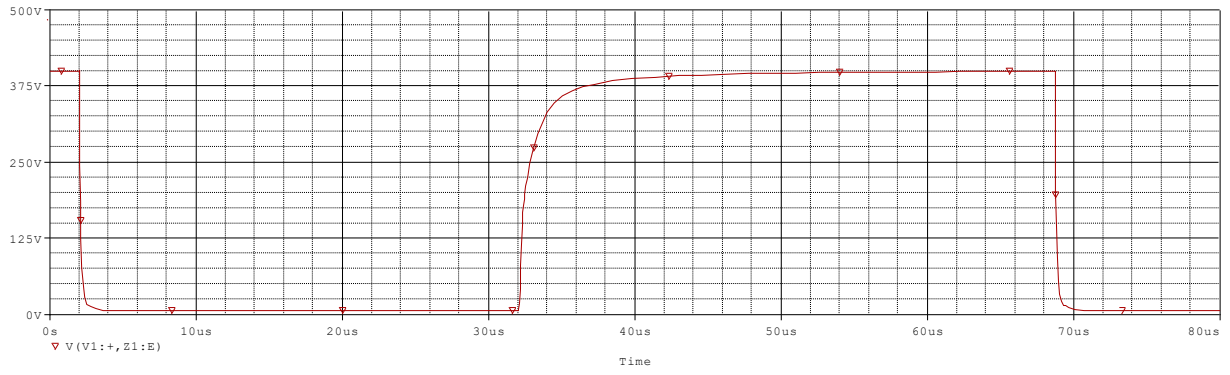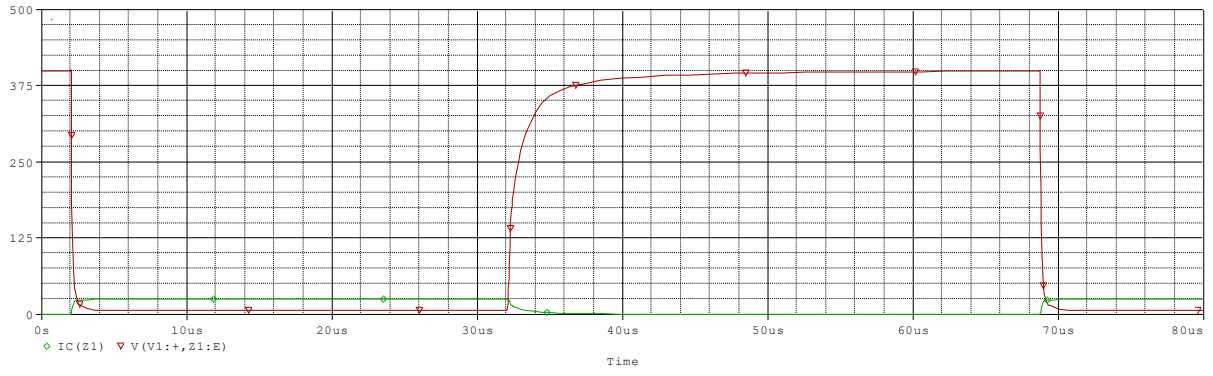

- **Conclusion:**

The results obtained from the simulations and calculations show that the power loss in case of a purely resistive load is less than the power loss in case of an inductive load.

By the end of this assignment, a full understanding of chopper circuits was achieved.