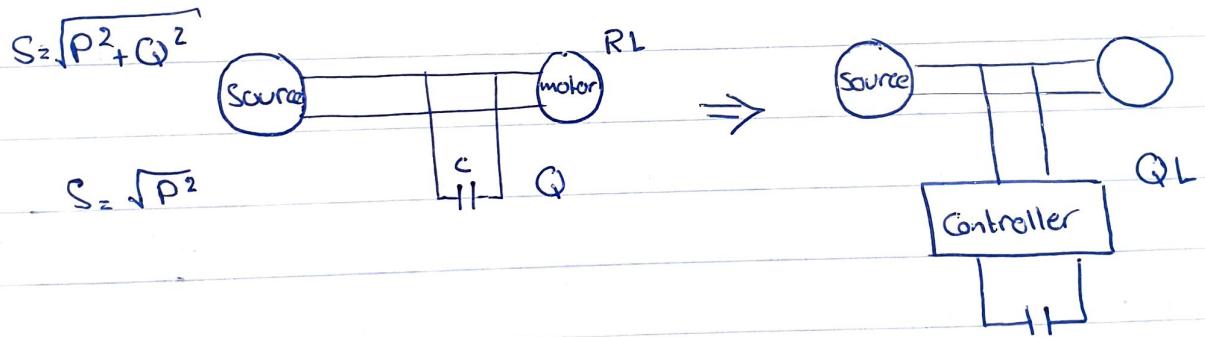


Introduction.

Definition of electronics; It is application of solid-state power devices and circuits for the control and conversion of electric energy from one to another form suitable for the load.

- Applications:

- Motor or Machine Control.
- Heat Control.
- Power Supply.
- High voltage DC transmission system(HVDC).
- light Control
- Charging & battery cells.
- Electric Vehicles.
- Flexible AC transmission(FACT)



- Solid-State Devices.

1. Power Diodes.
2. Silicon Control Rectifier (SCR).
3. Metal-Oxide Field effect transistor (MOSFET).
4. Insulated Gate Bipolar transistor (IGBT).
5. Bipolar Junction Transistor (BJT).


- Types of Power electronic Circuits.

1. Diode rectifiers $AC \rightarrow DC$ uncontrolled rectifier.
2. AC - DC Converters (Controlled rectifier).
3. DC - DC (DC choppers) stepup or stepdown
(Boost Converters or Buck Converters).
4. DC - AC Converters (Inverters); Variable Voltage Variable Frequency.
5. AC - AC Converters (AC voltage controller).

- Conversion types and symbols.

Conversion From / To	Conversion Name	Conversion Function	Conversion Symbol
1. AC / DC	Rectifier	AC to Unipolar "controller or uncontrolled" DC Current.	
2. DC / DC	Chopper	Constant DC to Constant or variable DC.	
3. DC / AC	Inverter	Fixed DC to AC of desired voltage & frequency.	
4. AC / AC	AC Voltage regulator or Controller	AC of desired voltage and/or frequency from line AC Supply.	

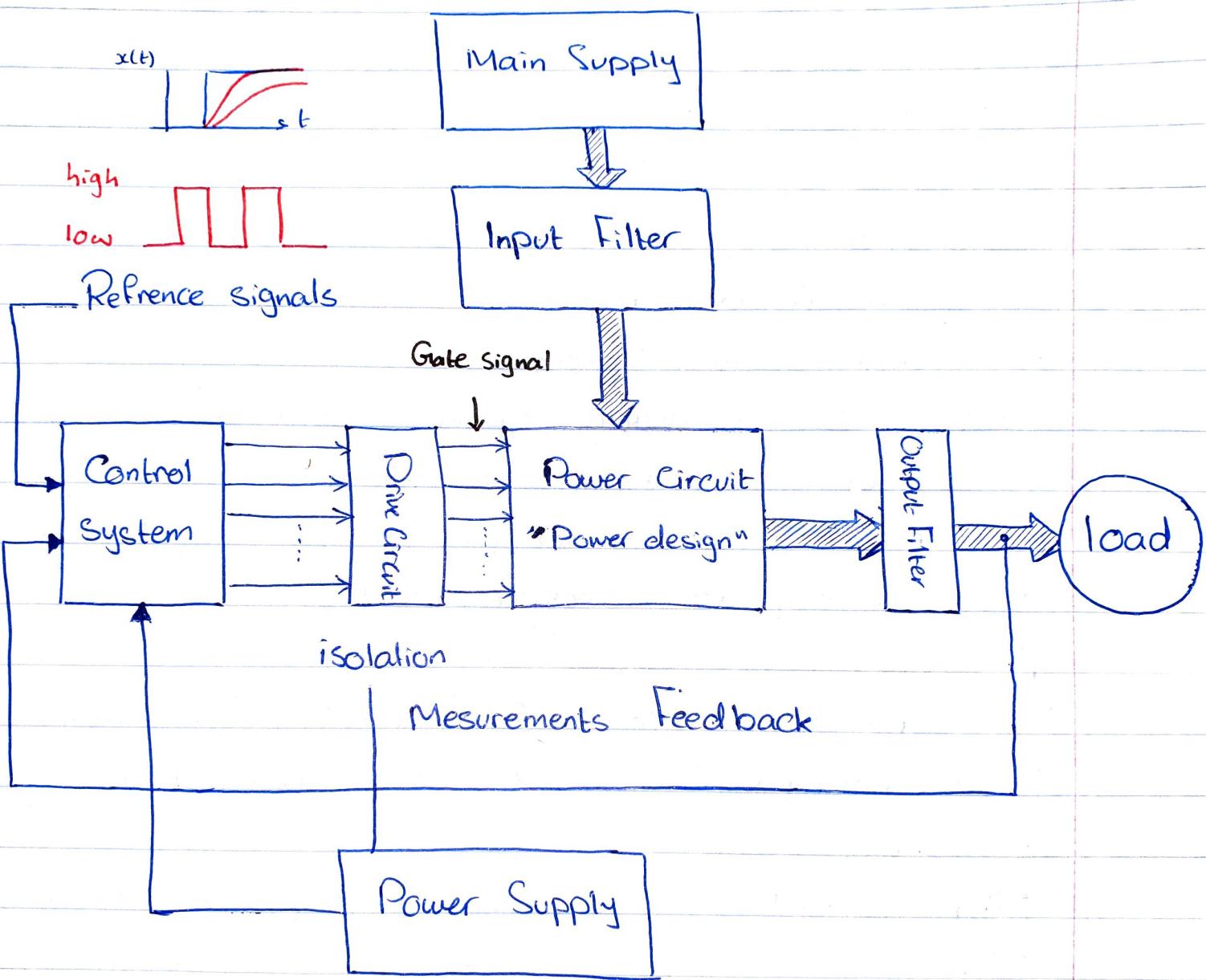- A typical Block Diagram of Power Conversion System.



- "Main Components"

1. Power Circuit: It is the power electronic converter which consists of solid-state devices and some passive elements.
(AC/DC, DC/DC, DC/AC, AC/AC).

2. Control System: It matches the power converter with the load to meet the load requirements.

- Inputs of the Control System:

- Reference current, voltage, speed or torque.
- Measure of current, voltage, speed or torque.
- Gain of the PI-Controller Proportional-Integral Controller.

- Measured temperature, pressure, torque for monitoring purposes.

- The Output of Controller is the final gating signal, which are issued directly to the base/gate of power or devices.

- Example:


- Micro Controller

- Digital Signal Processor DSP


- Micro Processor

- Field programmable Gate Array FPGa

3. Loads:

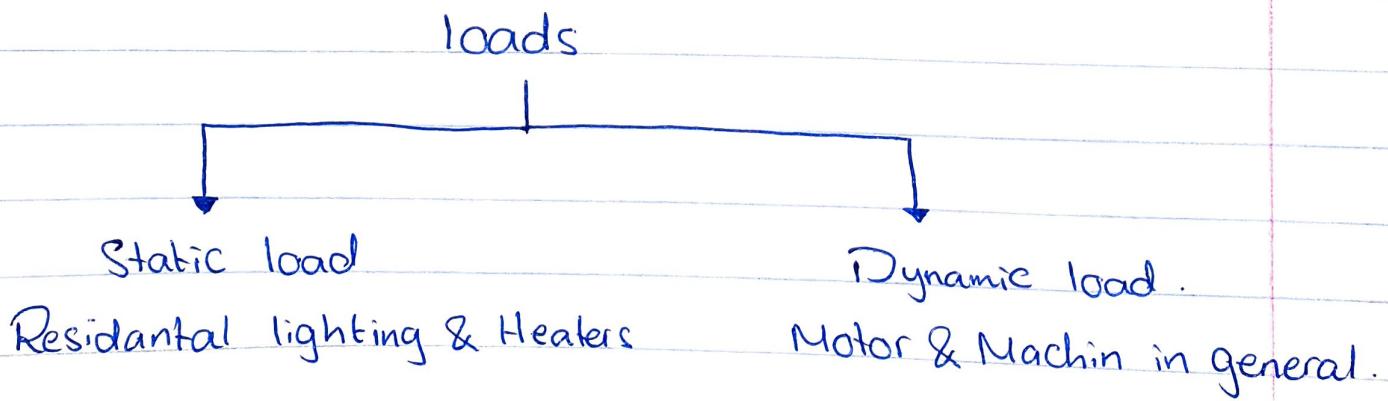

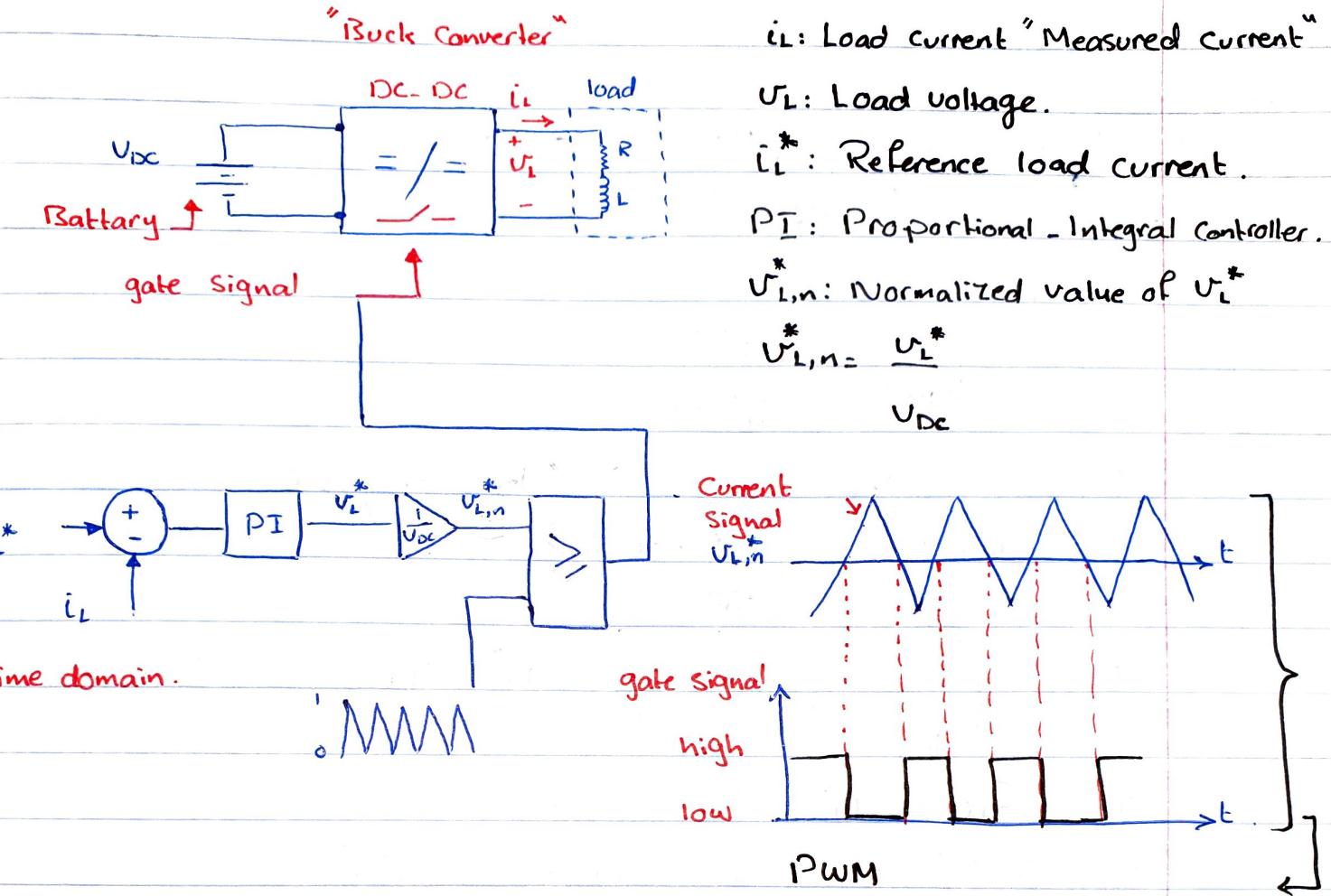- Current Controller in DC-DC Converts with static RL-load.



- PI Controller:

$$V_L^* = k_p e + k_i \int e dt.$$

k_p : Proportional gain of the PI.

k_i : integral gain of the PI. $e(t)$ is the error signal.

- Design of PI current controller:



KVL in the power circuit.

$$V_L = R i_L + L \frac{di_L}{dt}; \quad 1^{st} \text{ order differential equation.}$$

t-domain, Linear & time invariant.

$$V_L(s) = R I_L(s) + L s I_L(s).$$
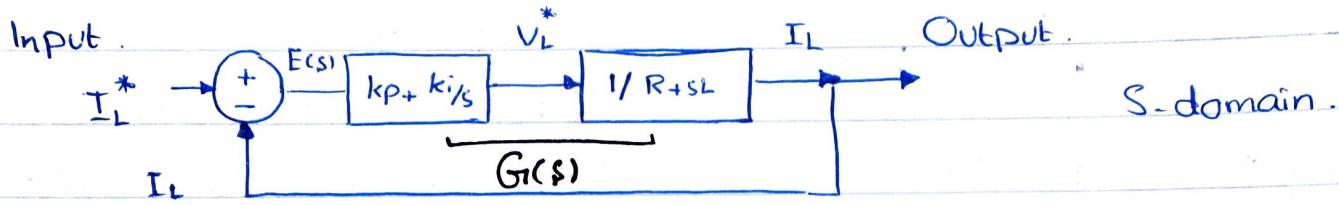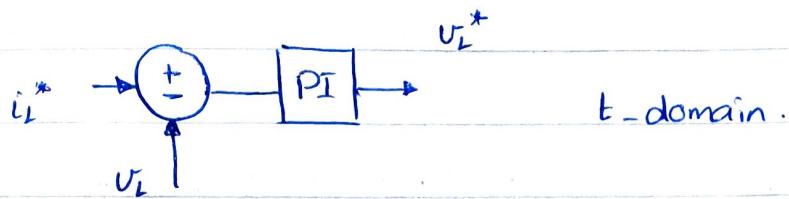
$$V_L(s) = (R + sL) I_L(s) \quad S\text{-domain.}$$



Transfer function:

$$T(s) = \frac{\text{Output}}{\text{Input}} = \frac{I_L(s)}{I_L^*(s)}$$

$$I_L = \frac{1}{R+SL} \quad V_L = \left(\frac{1}{R+SL} \right) \left(k_p + \frac{k_i}{s} \right) E(s).$$

$$I_L(s) = \underbrace{\left(\frac{1}{R+SL} \right)}_{G(s)} \left(k_p + \frac{k_i}{s} \right) (I_L^* - I_L).$$

$$I_L = G(s)(I_L^* - I_L)$$

$$I_L = G_I I_L^* - G_I I_L \Rightarrow (1+G_I) I_L = G_I I_L^*$$

$$\frac{I_L}{I_L^*} = \frac{G_I}{1+G_I}$$

$$\frac{I_L}{I_L^*} = \frac{(1/R+SL)(k_p s + k_i/s)}{1 + (1/R+SL)(k_p s + k_i/s)}$$


$$\frac{I_L}{I_L^*} = \frac{k_p s + k_i}{s(R+SL) + k_p s + k_i}$$

$$\frac{I_L}{I_L^*} = \frac{k_p s + k_i}{s^2 L + s(R+k_p) + k_i}$$

$$= \left(\frac{k_p}{L} \right) \frac{s + (k_i/k_p)}{s^2 + \left(\frac{k_p + R}{L} \right) s + \left(\frac{k_i}{L} \right)}$$

- The steady-state value of i_L .
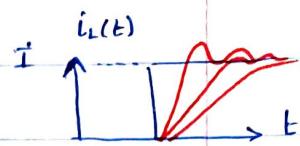
$$i_{L,ss} = \lim_{t \rightarrow \infty} i_L(t) = \lim_{s \rightarrow 0} s I_L(s),$$




$$i_{L,ss} = \lim_{s \rightarrow 0} \frac{\frac{k_p}{L}}{s^2 + \left(\frac{k_p+R}{L}\right)s + \frac{k_i}{L}} \cdot \underbrace{I_L(s) \cdot s}_{I} = \frac{I}{s}$$

$$i_{L,ss} = \frac{k_p}{L} \cdot \frac{\frac{(k_i/k_p)}{(k_i/L)}}{1} = I$$

- The general transfer function of 2nd Order Closed-loop Control System is given by:


$$T(s) = k \frac{s+a}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad (2)$$

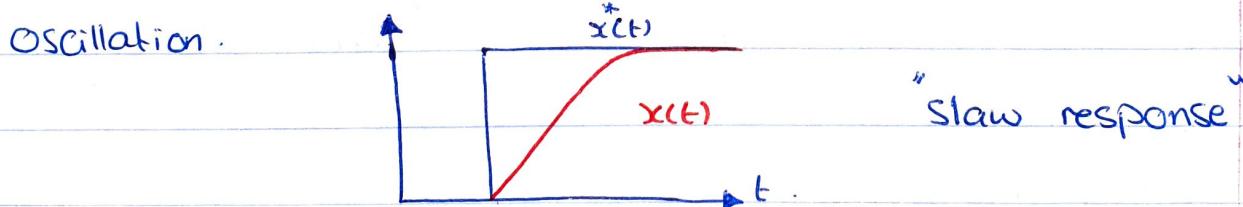- ζ is called the damping ratio $\zeta > 1 \Rightarrow$ Over damped response.
the actual value will reach its Steady-state value without oscillation.




- $\zeta < 1 \Rightarrow$ Under damped response.

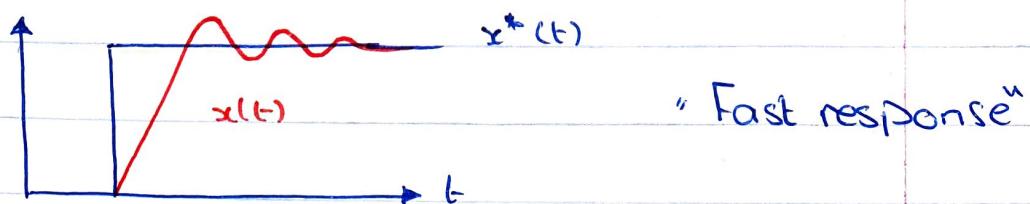The actual value will oscillate about its final value.




- $\zeta = 1 \Rightarrow$ Critically damped.

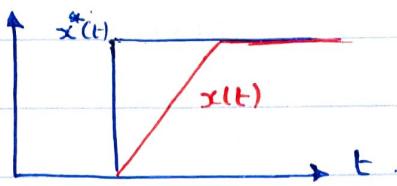The actual value is on the edge of oscillation.



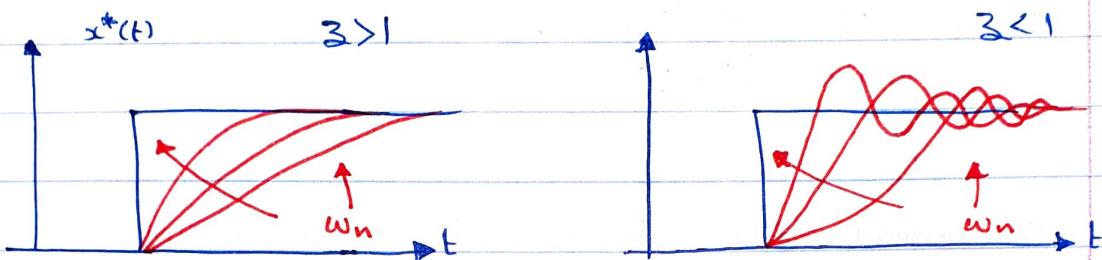- ω_n is called the natural Frequency of the controller.



By equating the equations (11) & (12), we get

$$k_i = \omega_n^2 L$$

$$k_p = 2\zeta \omega_n L - R$$

- AC-DC Uncontrolled Converters "Rectifier".

- Power diodes.


Fid. 18.14

The diode acts as a switch to perform various function such as switching in rectifiers, free wheeling in switching regulators, energy transfer between components, and energy feedback from load to source.

- Basic Semiconductor Physics

- * The most commonly used semiconductors are silicon and germanium. The silicon material is cheaper and allows the diode to operate at higher temperature, therefore, the germanium diodes are rarely used.

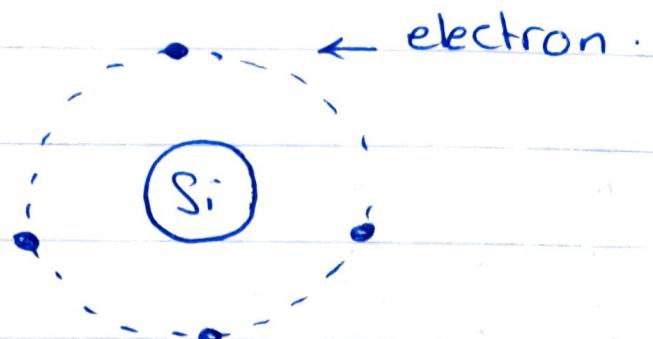
* The Silicon(Si) has 4 electrons in its Outer orbit and lies in the group IV of the periodic table.



* The array or crystal of Semiconductor material is composed of Si atoms. Each atom is bonded to the nearest 4 atoms by Covalent bonds. Each bond is composed of shared electrons between the two adjacent atoms.

- Semiconductor material

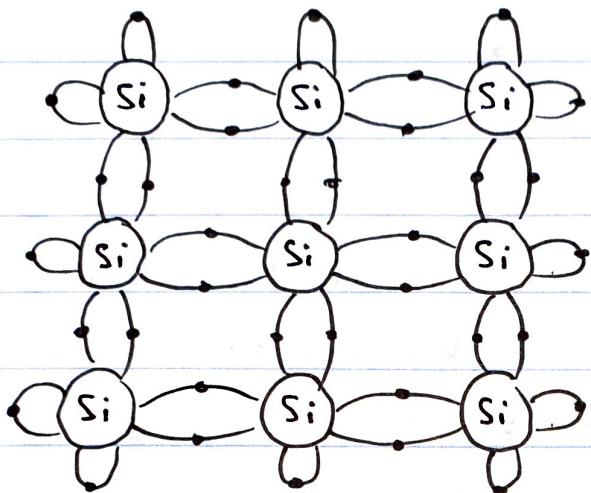It is formed by using elements in group IV of periodic table such as silicon (Si) and germanium (Ge).




Array of Si atoms.

- * At temperature beyond absolute zero, some of covalent bonds will be broken due to thermal ionization, which creates positive charges + electrons.



A; neutral atom. kT; Thermal energy.

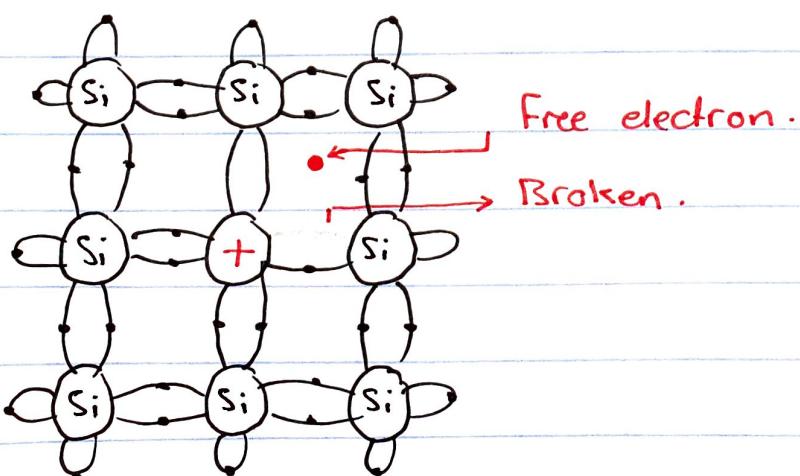

- Doped Semiconductor.


S *o* *l* *g* *o*

Doping process: It is the process of adding impurities to the semiconductor material to form the n-type & p-type material.

Impurities.

- Elements in group III of Periodic table.
- They have 3 electrons in their outer shell.
- Example: Boron.
- Elements in group II of Periodic table.
- They have 5 electrons in their outer shell.
- Example: Phosphorous.

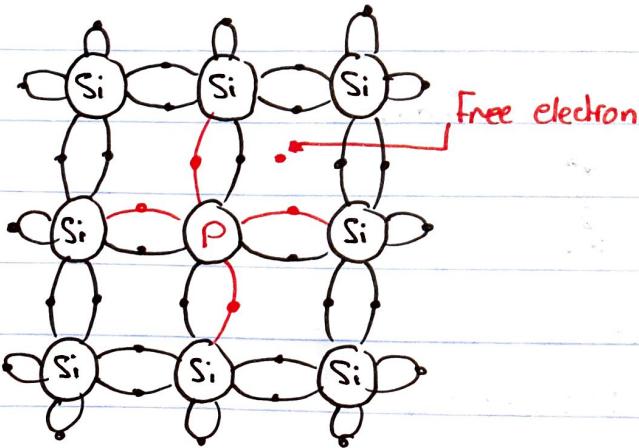
- n-type: The semiconductor (Si) is doped with some elements in group II (P) → Free electrons available.
- P-type: The semiconductor (Si) is doped with elements in group III (B) → Free holes.



n-type material

Majority Charge Carriers → electrons.

Minority Carriers → holes.

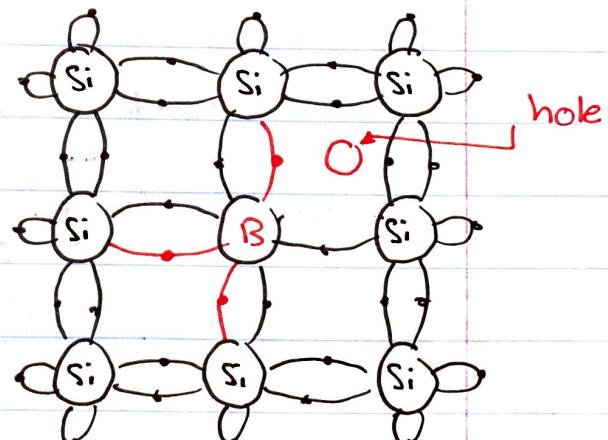


p-type material.

Majority Charge Carriers → holes.

Minority Charge Carriers → electrons.


- Pn-junction.

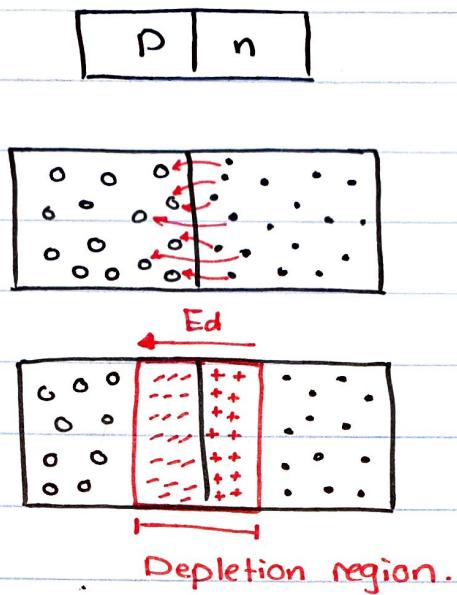It is formed by connecting the P-type material with the n-type material.





E_d : Depletion electric Field.

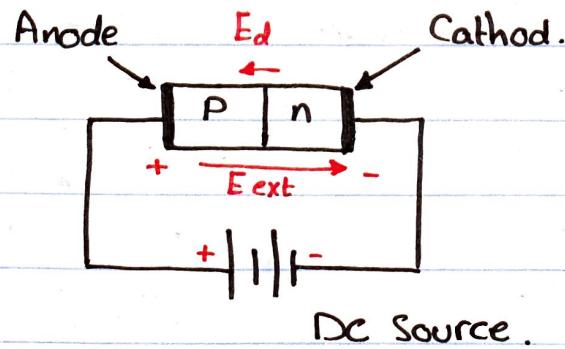- The electrons near the junction will diffuse over it to fill ~~surrounding~~ all the holes in the P-type material. As a result, positive and negative space charges are formed in a region called the depletion region.
- Pn junction "Conducting".




- . The negative terminal of the DC Source is connected to the n-type (Cathode) and the positive terminal is connected to the P-type (Anode).



- Since $E_{ext} \gg E_d$, the electrons will move to the left and the depletion region will become smaller.
- Any of electrons close to the depletion region will jump over it and other electrons will keep moving to the left.
- New electrons will be generated from the Cathode by the negative terminal of the DC source. These electrons will replace that have been ^{now} pushed to the left, resulting in a steady flow of electrons.
- At the same time, the holes will diffuse over the depletion region, resulting in a steady flow of positive charge carriers.
- By definition of Current, we have current flowing.

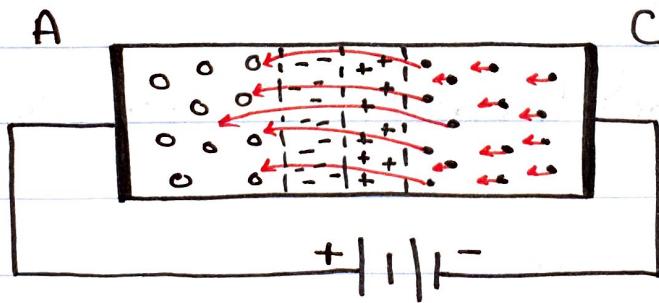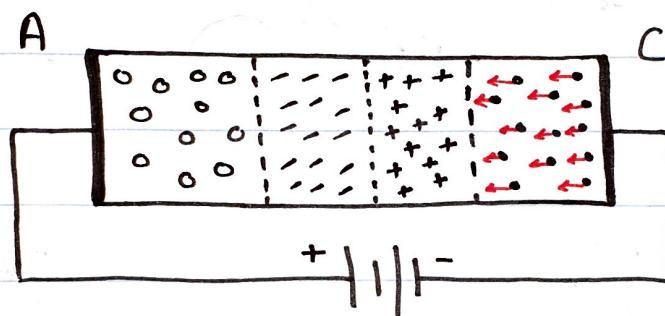


- Pn junction "Non-Conducting"

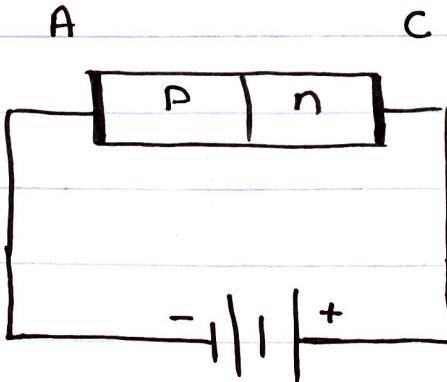

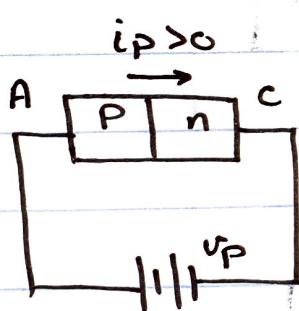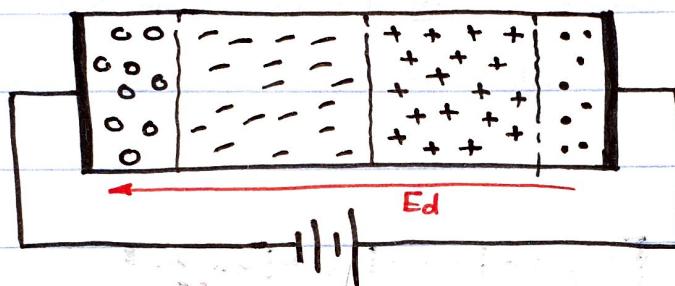- The positive terminal is connected to the Cathode and the negative terminal is connected to the anode.
- The electrons are attracted by the anode and the holes are attracted by the cathode.
- The depletion region is exploited. (expands).
- It becomes very difficult for the electrons to move from n-type material to the anode.
- The current is blocked.




Conducting ; Forward biased

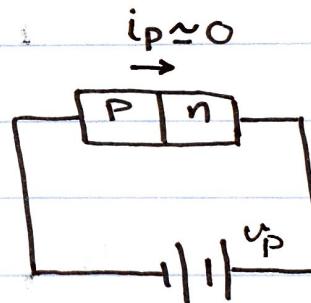


Non-Conducting ; Reversed biased

- Diode characteristic.

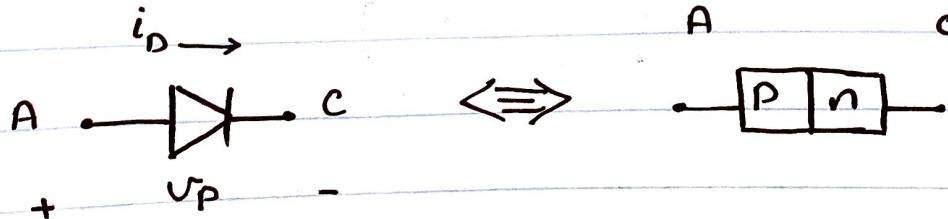- The diode is a two terminal Pn-junction device.
- Symbol of diode



i-v characteristic of diode.

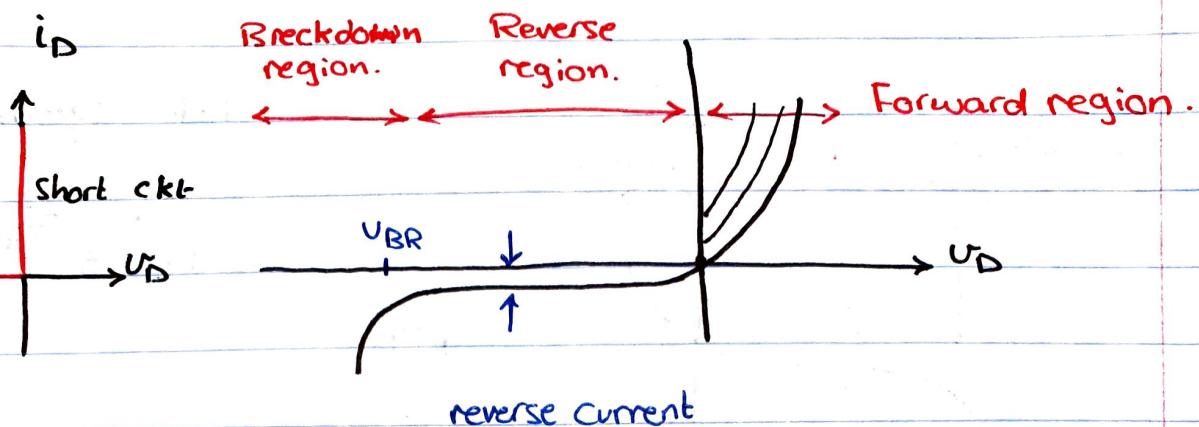

- Diode equation.

$$i_D = I_S [e^{(V_D / (nV_T))} - 1] \quad \leftarrow \text{empirical equation.}$$

i_D : Diode current.

V_D : Diode voltage.

I_S : Reverse leakage current; $(10^{-6} - 10^{-15})$ A.

n : Empirical Constant or ideality Factor.

$n = 1 - 2$.

V_T : Terminal voltage.


$$V_T = \frac{kT}{q}, \quad k = 1.38 \times 10^{-23} \text{ J/K.}$$

$$q = 1.6 \times 10^{-19}$$

- Junction temperature of 25°C .

$$V_T = \frac{1.38 \times 10^{-23} \times (25 \times 273)}{1.6 \times 10^{-19}} = 25.7 \text{ mV.}$$

- Region of Diode characteristic.

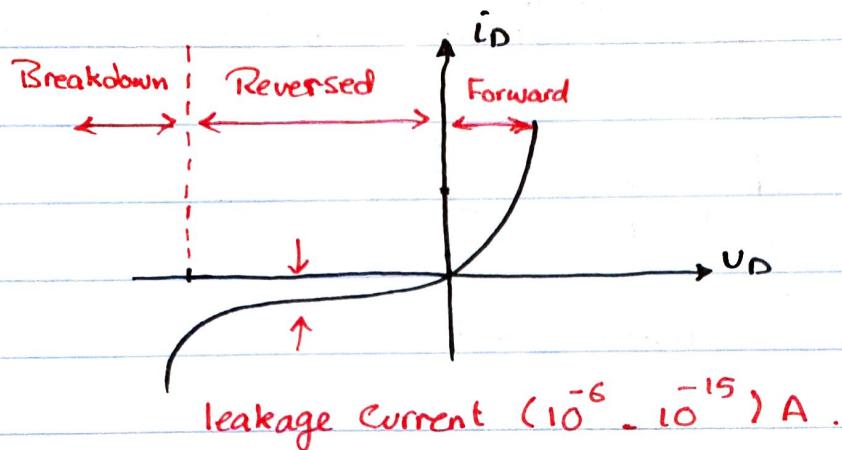

Diode equation:

$$i_D = I_s \left[e^{\frac{u_D}{nV_T}} - 1 \right]$$

1. Forward-biased region:

- In this region, the diode is conducting as long as $u_D > V_{TD}$. Where V_{TD} is called threshold or turn-on voltage of diode, which is around 0.7 V.
- When the diode is conducting, a small forward voltage will appear across its terminals. This voltage depends on the manufacturing process and the junction temperature.
- The diod current in this region can be approximately given by: $i_D \approx I_s e^{(u_D/(nV_T))}$

2. Reversed-biased region:

In this region the diode is consider to be non-conducting.

- To turn-off the diode,
- $V_{BR} < u_D < 0$; V_{BR} : Breakdown voltage.
- $u_D \gg V_T$.
- The diode current in this region is given by:


$$i_D = I_s \left[e^{\frac{u_D}{nV_T}} - 1 \right] \approx -I_s$$

3. Breakdown region.


VBR or reverse voltage \Rightarrow القيمة المعاكسة

- The diode goes to this region when $V_D < -V_{BR}$, where V_{BR} is the breakdown voltage (typically 1kV).
- Since V_{BR} is usually high voltage, it is necessary to limit the reverse current to limit the power dissipation within a permissible value.
- The reverse current decrease rapidly.

- Reverse Recovery Characteristic.

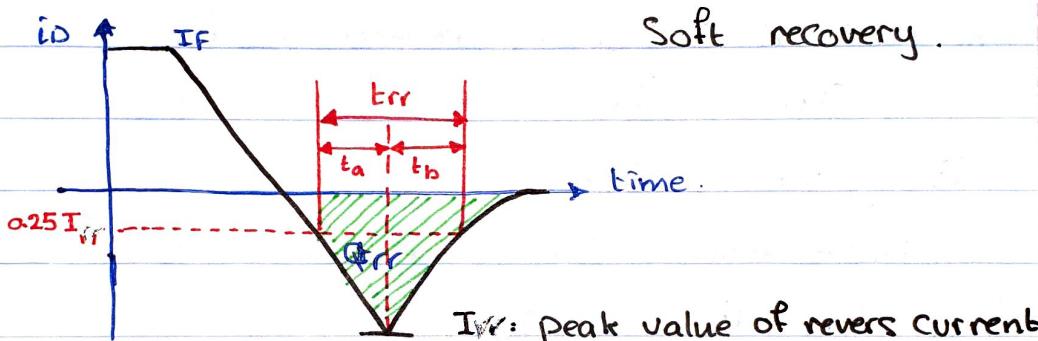

I_{rr} : peak value of reverse current

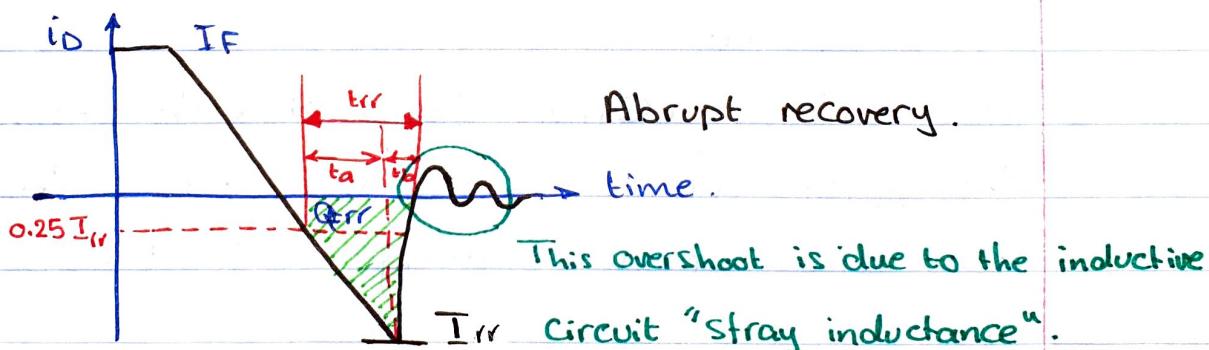

This overshoot is due to the inductive

I_{rr} circuit "stray inductance".

القيمة المعاكسة تؤدي إلى ازدواج في الارجاع

- Reverse recovery time (t_{rr}): It is the time between the instant when the diode Current passes through Zero and the moment when the peak reverse current (I_{rr}) has decayed to 25% of its value.

Positive ions \rightarrow C_1, C_2, \dots will be released

- » This time is required to recombine the minority charge carriers with their opposite charge.

Thermal ionization

$$t_{rr} = t_a + t_b.$$

t_a : due to the charge stored in the depletion region.

t_b : due to the charge stored in the bulk semiconductor material

In reality, $t_a \gg t_b$.

» Soft Factor (SF):

$$SF = \frac{t_a}{t_b}$$

$SF \downarrow \Rightarrow$ Over voltage \uparrow

- The rate of change of reverse current is given by:

$$\frac{di}{dt} = \frac{I_{rr}}{t_a} \approx \frac{I_{rr}}{t_{rr}}$$

- The Peak reverse Current is given by::

$$I_{rr} = t_{rr} \frac{di}{dt} \quad (1)$$

- Reverse recovery charge (Q_{rr}): It is the charge that flows in the opposite direction in the diode due to the charge over from forward mode to reverse mode. It can be calculated as: when it makes a check over forward to revers.

$$Q_{rr} \approx \frac{1}{2} t_{rr} I_{rr} \quad (2)$$

$$(1) \rightarrow (2) \Rightarrow Q_{rr} = \frac{1}{2} t_{rr} (t_{rr} \frac{di}{dt})$$

$$Q_{rr} = \frac{1}{2} t_{rr}^2 \frac{di}{dt}$$

$$\Rightarrow t_{rr} = \sqrt{\frac{2Q_{rr}}{(di/dt)}}$$

• Note:

Q_{rr} , t_{rr} , I_{rr} & SF ; are usually given in the datasheet of the diode.

- Example: The recovery reverse time of diode is 3 μ sec, the rate of fall of the diode current is 30 A/ μ sec.

1. Determine the peak reverse current.

2. Determine the storage current.

$$1. t_{rr} = 3 \mu\text{sec} = 3 \times 10^{-6}$$

$$\frac{di}{dt} = 30 \text{ A}/\mu\text{sec} = 30 \times 10^6$$


$$\frac{di}{dt} = \frac{I_{rr}}{t_{rr}} \Rightarrow I_{rr} = \frac{di}{dt} \cdot t_{rr} = 90 \text{ A}$$

$$2. Q_{rr} = \frac{1}{2} t_{rr} \cdot I_{rr}$$

$$= \frac{1}{2} (3 \times 10^{-6}) (90) = 135 \text{ MC}$$

- Diode Rectifier:

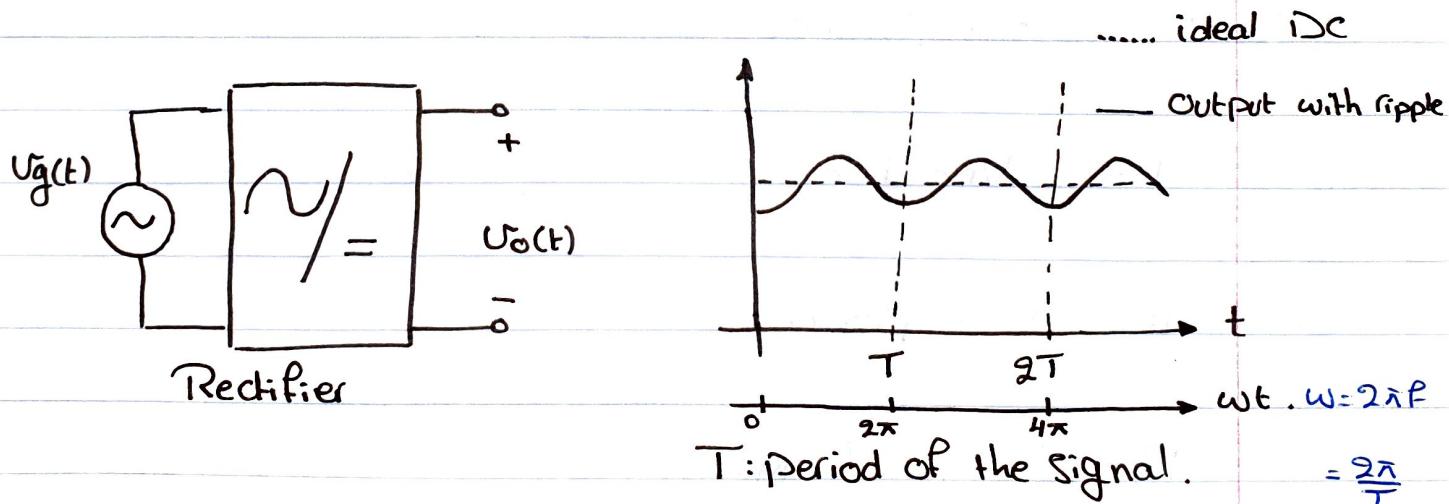A rectifier is a circuit that converts the AC signal into a unidirectional signal.



- Performance Parameters:

1. Average Value of Output (load) Voltage.

$$\text{average } \Rightarrow V_{DC} = \frac{1}{T} \int_0^T U_o(t) dt = \frac{1}{2\pi} \int_0^{2\pi} U_o(t) d(\omega t)$$

2- Average Value of Output Current.

$$I_{DC} = \frac{1}{T} \int_0^T i_o(t) dt = \frac{1}{2\pi} \int_0^{2\pi} i_o(t) d(\omega t)$$

3- RMS value of output voltage.

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v_o^2(t) dt} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_o^2(t) d(\omega t)}$$

4- RMS value of load current.

$$I_{RMS} = \sqrt{\frac{1}{T} \int_0^T i_o^2(t) dt} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i_o^2(t) d(\omega t)}$$

5- DC output Power:

$$P_{DC} = V_{DC} I_{DC}$$



6- AC output Power:

$$P_{AC} = V_{RMS} \cdot I_{RMS}$$

7- Efficiency or rectification ratio.

$\eta = \frac{P_{DC}}{P_{AC}}$; This is not a power efficiency. This is a conversion efficiency that measures the quality of output waveform.

- Rectifier Circuit.

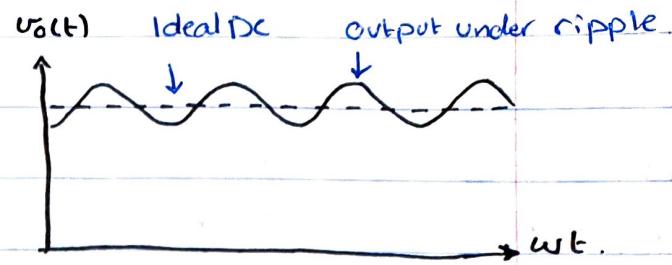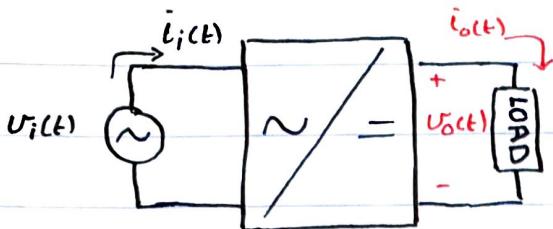

- Performance parameters.

1. Average value of output voltage.

$$V_{DC} = \frac{1}{2\pi} \int_0^{2\pi} U_o(t) d(\omega t)$$

2. Average value of Output current.

$$I_{DC} = \frac{1}{2\pi} \int_0^{2\pi} i_o(t) d(\omega t)$$

3. RMS value of $U_o(t)$.

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} U_o^2(t) d(\omega t)}$$

4. RMS value of $i_o(t)$.

$$I_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i_o^2(t) d(\omega t)}$$

5. DC output power.

$$P_{DC} = V_{DC} I_{DC}$$

6. AC output power.

$$P_{AC} = V_{RMS} I_{RMS}$$

7. Rectification


$$\eta = \frac{P_{DC}}{P_{AC}}$$

8. Effective RMS value of the AC component of $v_o(t)$.

$$v_o(t) = V_{DC} + v_{AC}(t).$$

RMS value $\rightarrow V_{DC} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_{AC}(t) d(\omega t)}$
of $v_{AC}(t)$.

$$= \sqrt{V_{RMS}^2 - V_{AC}^2}$$

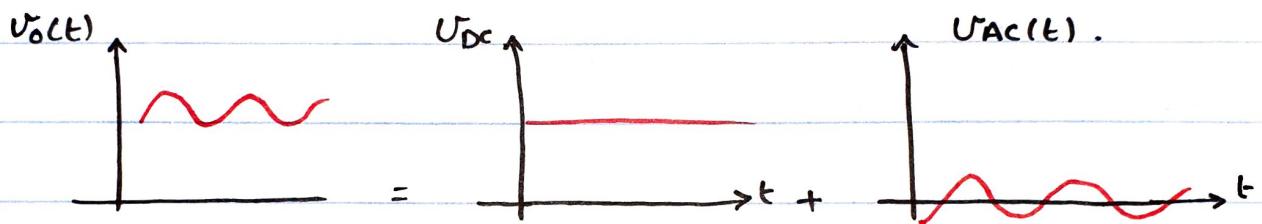

- Recall the RMS value of $v_o(t)$.

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_o^2(t) d(\omega t)}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_{DC} + v_{AC}(t))^2 d(\omega t)}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_{AC}^2(t) d(\omega t) + \frac{1}{2\pi} \int_0^{2\pi} 2V_{DC} v_{AC}(t) d(\omega t) + \frac{1}{2\pi} \int_0^{2\pi} V_{DC}^2 d(\omega t)}$$

$$V_{RMS} = \sqrt{V_{AC}^2 + V_{DC}^2}$$

9. Ripple Factor (RF) : It is measure of ripple content in the Output waveform.

$$RF = \frac{V_{AC}}{V_{DC}}, \text{ For ideal rectifier } \rightarrow RF = 0\%.$$

10. Form Factor (FF) : It is a measure of the shape of output waveform.

$$FF = \frac{V_{RMS}}{V_{DC}} = \sqrt{\frac{V_{AC}^2 + V_{PC}^2}{V_{DC}}} = \sqrt{\left(\frac{V_{AC}}{V_{DC}}\right)^2 + 1}$$

$$FF = \sqrt{(RF)^2 + 1}, \text{ For ideal rectifier } FF = 100\%.$$

11. Transformation utilization factor (TUF).

$$TUF = \frac{P_{DC}}{V_s I_s}$$

where, V_s is the rms value of input voltage.

I_s is the rms value of input current.

12. Total harmonic distortion (THD) or harmonic Factor (HF) of input current.

$$THD = \sqrt{\frac{I_s^2 - I_1^2}{I_1^2}}, \text{ Ideally } THD = 0\%.$$

$$I_s = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i_s^2(t) d(\omega t)}$$

I_1 : It is RMS value of the Fundamental component of $i_s(t)$.

13. Crest Factor (CF).


$CF = \frac{I_{s \text{ Peak}}}{I_s}$, It is used to determine the rated peak current of power device.

121- Input Power Factor.

$$PF = \frac{I_1}{I_s} \cos \phi$$

$\frac{I_1}{I_s}$: distortion factor , $\cos \phi$: displacement factor.

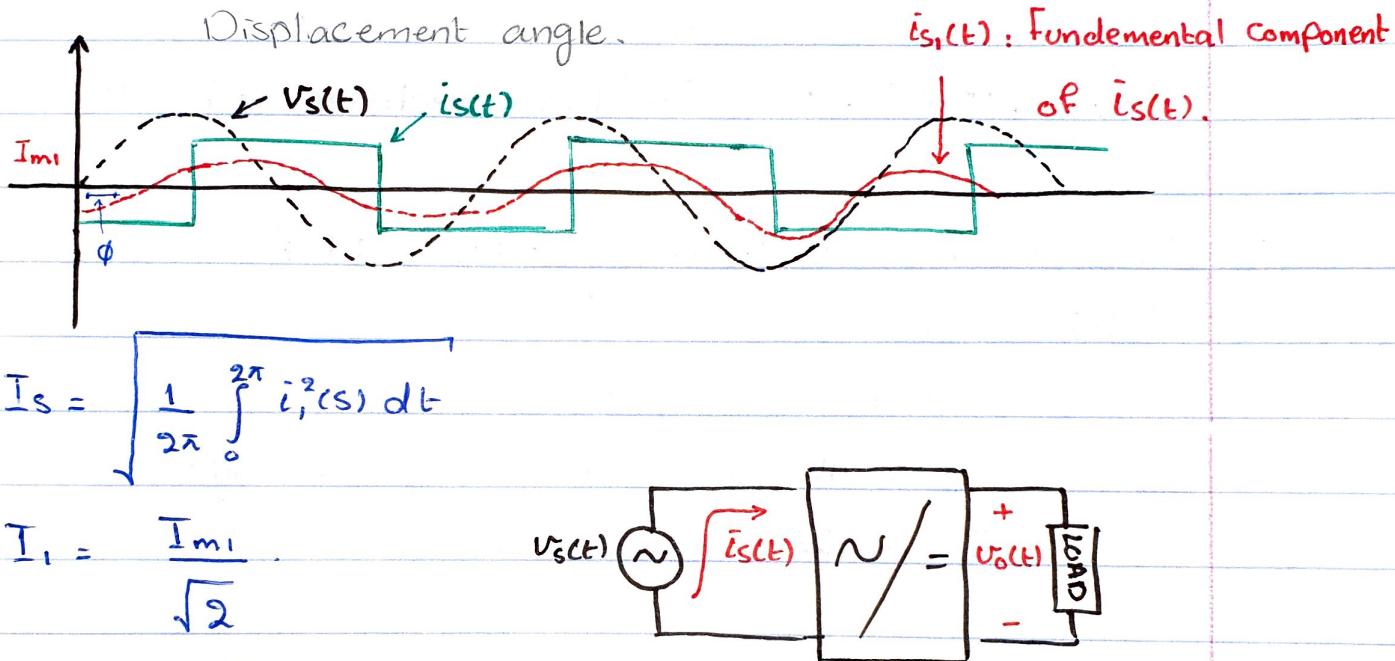ϕ : Phase difference between the fundamental components of input voltage and current.



Distortion Factor = I_1 / I_s

Displacement Factor = $\cos \phi$

- Fourier Series.

It is used to represent any periodic signal by a discrete sum of sinusoidal functions with average value.


$$x(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos(nwt) + \sum_{n=1}^{\infty} b_n \sin(nwt).$$

$$a_0 = \frac{1}{T} \int_0^T x(t) dt = \frac{1}{2\pi} \int_0^{2\pi} x(t) d(wt).$$

$$a_n = \frac{2}{T} \int_0^T x(t) \cos(nwt) dt = \frac{1}{\pi} \int_0^{2\pi} x(t) \cos(nwt) dwt$$

$$b_n = \frac{2}{T} \int_0^T x(t) \sin(n\omega t) dt = \frac{1}{\pi} \int_0^{2\pi} x(t) \sin(n\omega t) d(\omega t).$$


$$5 \cos(\omega t) + 3 \sin(10t).$$

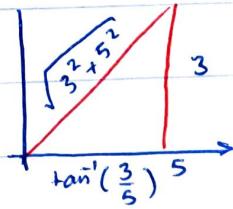

$$x(t) = a_0 + \sum_{n=1}^{\infty} C_n (\cos(n\omega t + \phi_n))$$

$$C_n = \sqrt{a_n^2 + b_n^2}$$
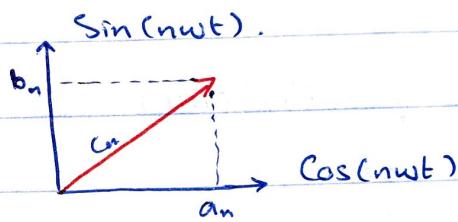
$$\phi_n = \tan^{-1} \left(\frac{b_n}{a_n} \right)$$




$$x(t) = a_0 + \underbrace{c_1 \cos(\omega t + \phi_1)}_{\text{DC Component}} + \underbrace{c_2 \cos(2\omega t + \phi_2)}_{\text{Fundamental}} + \underbrace{c_3 \cos(3\omega t + \phi_3)}_{\text{Harmonics}} + \dots$$


or main component.

magnitude.

Frequency spectrum.

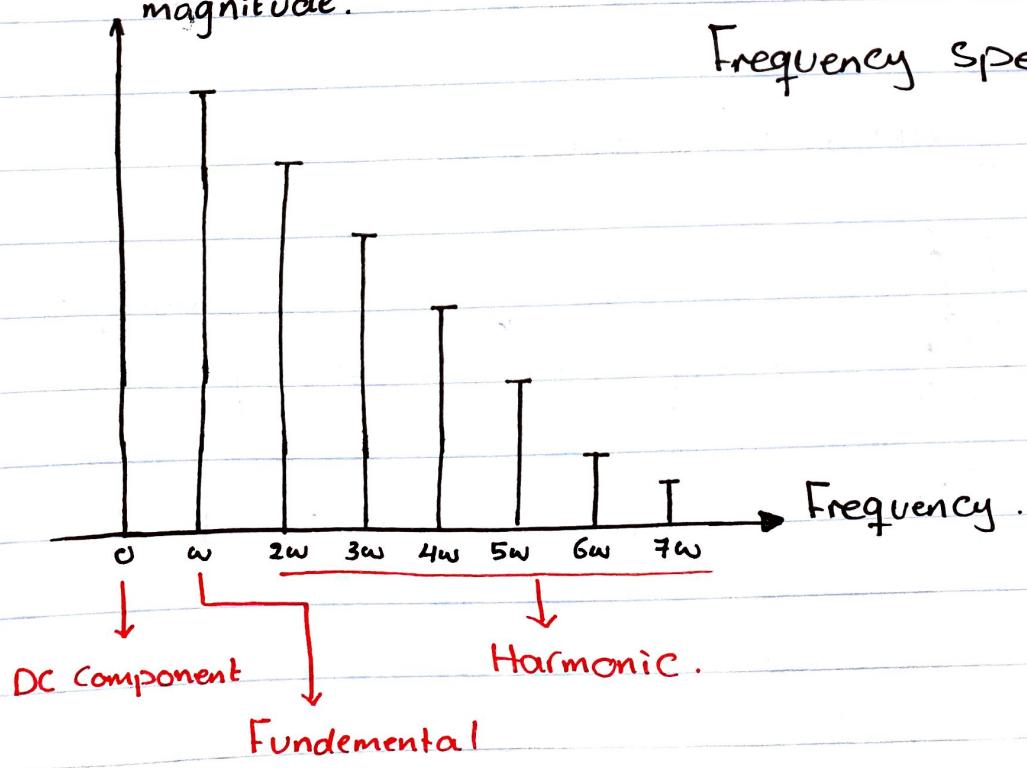

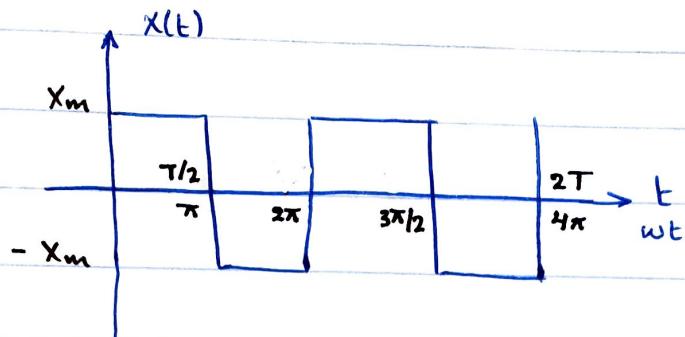- Example: Fourier Series For square wave.



Solution:

$$x(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos(nwt) + \sum_{n=1}^{\infty} b_n \sin(nwt).$$

$$a_0 = \frac{1}{2\pi} \int_0^{2\pi} x(t) d(wt) = 0, \text{ NO DC component.}$$

$$\begin{aligned} a_n &= \frac{1}{\pi} \int_0^{2\pi} x(t) \cos(nwt) d(wt), \\ &= \frac{1}{\pi} \left[\int_0^{\pi} X_m \cos(nwt) dwt - \int_{\pi}^{2\pi} X_m \cos(nwt) dwt \right] \\ a_n &= \frac{X_m}{\pi} \left[\frac{1}{n} \sin(nwt) \Big|_0^{\pi} - \frac{1}{n} \sin(nwt) \Big|_{\pi}^{2\pi} \right] \end{aligned}$$


$$a_n = 0. \quad \text{symmetric about } x\text{-axis (odd Function)}$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} x(t) \sin(nwt) dwt.$$

$$\begin{aligned} b_n &= \frac{1}{\pi} \left[\int_0^{\pi} X_m \sin(nwt) dwt - \int_{\pi}^{2\pi} X_m \sin(nwt) dwt \right] \\ &= \frac{X_m}{\pi} \left[\frac{1}{n} \cos(nwt) \Big|_0^{\pi} + \frac{1}{n} \cos(nwt) \Big|_{\pi}^{2\pi} \right] \\ &= \frac{X_m}{n\pi} \left[(1 - \cos(n\pi)) + (\cos(2n\pi) - \cos(n\pi)) \right] \end{aligned}$$

$$= \frac{2X_m}{m\pi} (1 - \cos(m\pi)) = \begin{cases} 0 & , n \text{ is even} \\ \frac{4X_m}{n\pi} & , m \text{ is odd.} \end{cases}$$

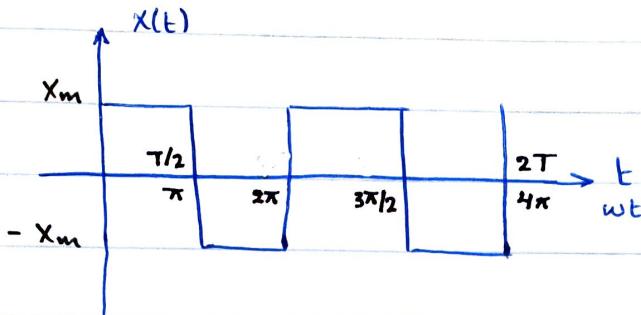- Example: Fourier Series For Square Wave.



Solution:

$$x(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos(nwt) + \sum_{n=1}^{\infty} b_n \sin(nwt).$$

$$a_0 = \frac{1}{2\pi} \int_0^{2\pi} x(t) d(wt) = 0, \text{ NO DC component.}$$

$$\begin{aligned} a_n &= \frac{1}{\pi} \int_0^{2\pi} x(t) \cos(nwt) d(wt) \\ &= \frac{1}{\pi} \left[\int_0^{\pi} x_m \cos(nwt) dwt - \int_{\pi}^{2\pi} x_m \cos(nwt) dwt \right] \\ a_n &= \frac{x_m}{\pi} \left[\frac{1}{n} \sin(nwt) \Big|_0^{\pi} - \frac{1}{n} \sin(nwt) \Big|_{\pi}^{2\pi} \right] \end{aligned}$$


$a_n = 0$. Symmetric about x-axis (odd Function)

$$b_n = \frac{1}{\pi} \int_0^{2\pi} x(t) \sin(nwt) dwt$$

$$\begin{aligned} b_n &= \frac{1}{\pi} \left[\int_0^{\pi} x_m \sin(nwt) dwt - \int_{\pi}^{2\pi} x_m \sin(nwt) dwt \right] \\ &= \frac{x_m}{\pi} \left[\frac{1}{n} \cos(nwt) \Big|_0^{\pi} + \frac{1}{n} \cos(nwt) \Big|_{\pi}^{2\pi} \right] \\ &= \frac{x_m}{n\pi} \left[(1 - \cos(n\pi)) + (\cos(2n\pi) - \cos(n\pi)) \right] \end{aligned}$$


$$= \frac{2x_m}{n\pi} (1 - \cos(m\pi)) = \begin{cases} 0 & , n \text{ is even} \\ \frac{4x_m}{n\pi} & , m \text{ is odd.} \end{cases}$$
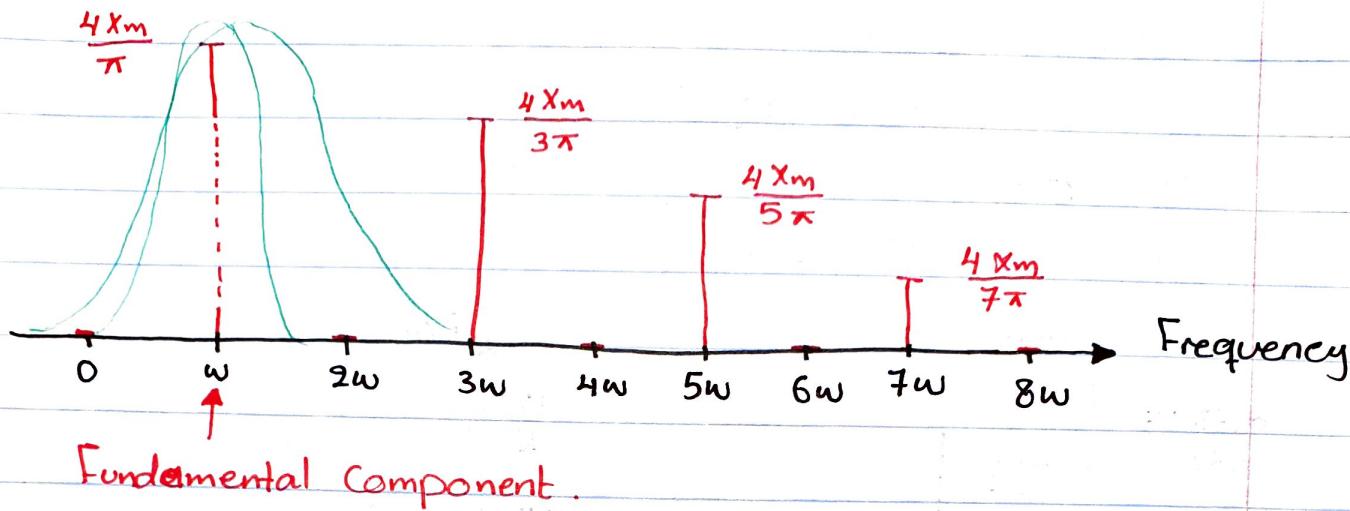
$$x(t) = \sum_{m=1}^{\infty} \frac{4X_m}{n\pi} \sin(n\omega t)$$



- Diode Circuits and Rectifier.

1. Diode Circuit with RC load.

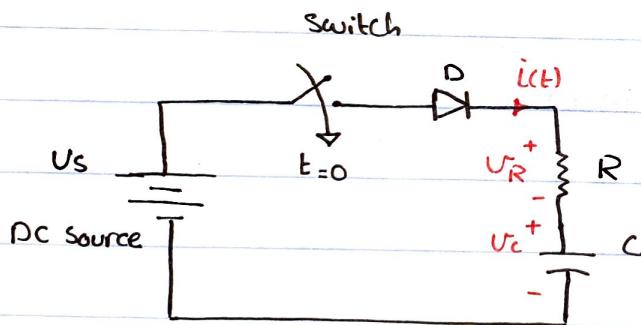

Assume that the switch is closed at $t=0$.

KVL in the loop:

$$U_s = R i(t) + U_c(t)$$

$$i(t) = C \frac{dU_c}{dt}$$

$$U_s = RC \frac{dU_c(t)}{dt} + U_c(t). \quad X(t) = X_f + (X_i - X_f) e^{-\frac{(t-t_0)}{\tau}}$$

The solution is given by:

$$U_c(t) = U_c(\infty) + [U_c(0) - U_c(\infty)] e^{-\frac{t}{\tau}}. \quad X_f = X(\infty) = \text{Final value}$$

τ : time constant.

$$\tau = RC$$

- Assume that the capacitor is initially fully discharged $\Rightarrow U_C(0) = 0$.

When $t \rightarrow \infty \Rightarrow C$ is open circuit.



$$U_C(\infty) = U_S$$

$$U_C(t) = U_S + (0 - U_S) e^{-t/\tau}$$

$$U_C(t) = U_S (1 - e^{-t/\tau}), t \geq 0$$

$$i(t) = C \frac{dU_C(t)}{dt} = C U_S \left(\frac{1}{\tau} e^{-t/\tau} \right)$$

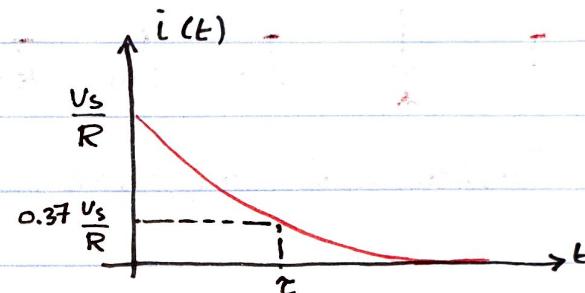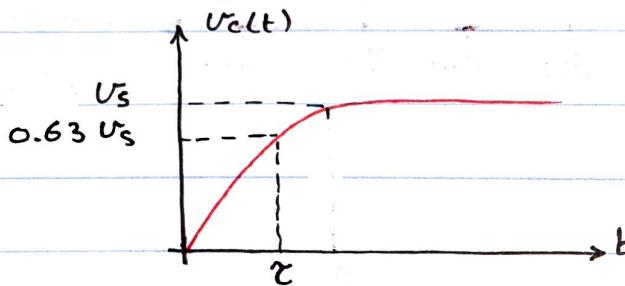
$$i(t) = \frac{U_S}{R} e^{-t/\tau}, t \geq 0$$



- The energy stored in the capacitor under steady state

$$\text{Condition } (t \rightarrow \infty); E_C = \frac{1}{2} C U_S^2$$

2. Diode circuit with RL load.

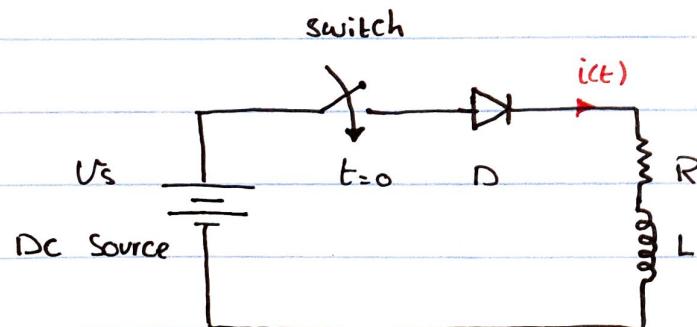

Assume that the switch is closed at $t=0$. By applying KVL in the loop:

$$U_S = R i(t) + L \frac{di(t)}{dt}$$

The solution is given by:

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

τ : time Constant.

$$\tau = L/R$$

Assume that the inductor is initially Fully discharged $\Rightarrow i(0) = 0$.



At $t \rightarrow \infty \Rightarrow L$ is short circuit.

$$i(\infty) = \frac{V_s}{R}; \quad i(\infty): \text{Steady state conductor current.}$$

$$i(t) = \frac{V_s}{R} + (0 - \frac{V_s}{R}) e^{-t/\tau}$$

$$i(t) = \frac{V_s}{R} (1 - e^{-t/\tau}); \quad t \geq 0.$$
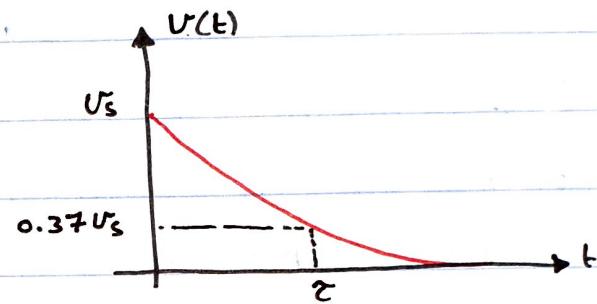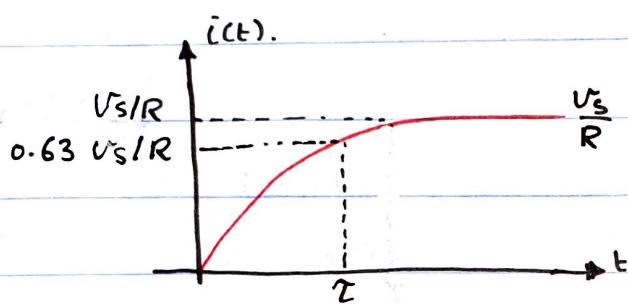
$$U_L(t) = L \frac{di(t)}{dt} = L \frac{V_s}{R} \frac{1}{\tau} e^{-t/\tau} = V_s e^{-t/\tau}, \quad t \geq 0.$$



The energy stored in the inductor under Steady state condition is:

$$E_L = \frac{1}{2} L I^2; \quad I = \frac{V_s}{R}$$

Freewheeling diode with RL load.


The Steady state current in the inductor is given by:

$$I_{ss} = I = \frac{V_s}{R}; \quad I_{ss}: \text{Steady state current.}$$

An attempt to open the switch will result in transferring the energy stored in the inductor ($\frac{1}{2} L I^2$) into a high voltage across the diode and switch. The energy will be dissipated in the form of spark that may damage the circuit component.


To overcome this problem, a **Freewheeling diode** is connected across the RL load to provide an alternative path for the current when the switch is opened.

لوجستي وظيفة
Z(t) = Z₀ / (1 + e^{-t/T})

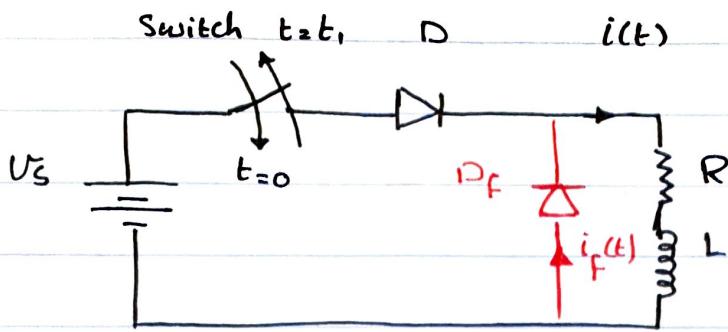

D_f : Free wheeling diode.

Modes of operation

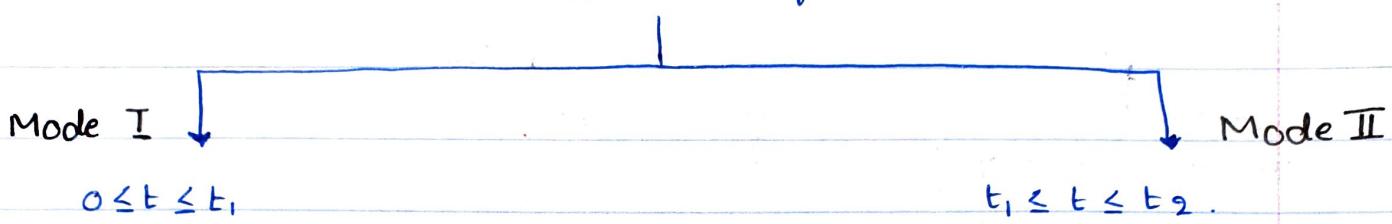


$$0 \leq t \leq t_1$$

The switch is ON "closed".

D is Conducting.

D_f is reversed-biased.

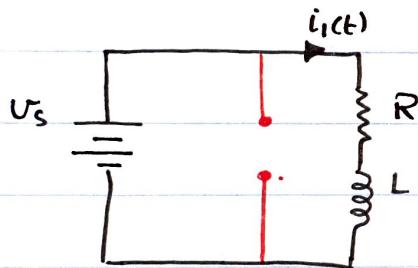


$$i_1(t) = \frac{V_s}{R} \left(1 - e^{-\frac{t-t_1}{\tau}}\right)$$

Step response.

The switch is OFF "Open".

D_f is Conducting.

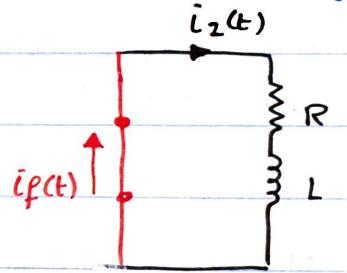


$$i_2(t) = I e^{-(t-t_1)/\tau}$$

where I is the initial current of

$$i_2(t) \Rightarrow i_2(t_1) = i_1(t_1).$$


$$i(t) = \begin{cases} i_1(t), & 0 \leq t \leq t_1, \\ i_2(t), & t_1 \leq t \leq t_2. \end{cases}$$

Natural Response.

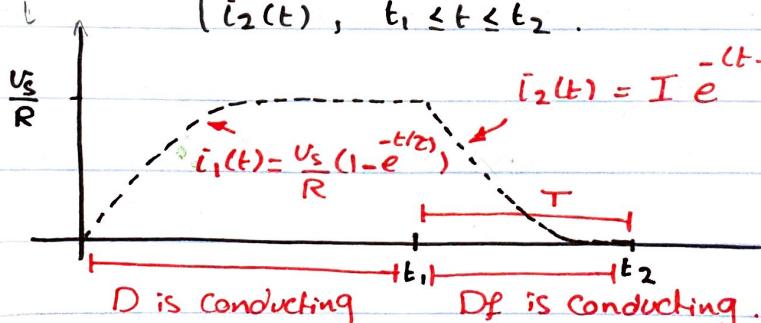


$$i_2(t) = I e^{-\frac{(t-t_1)}{\tau}}$$

$$\tau \gg \tau = \frac{L}{R}$$




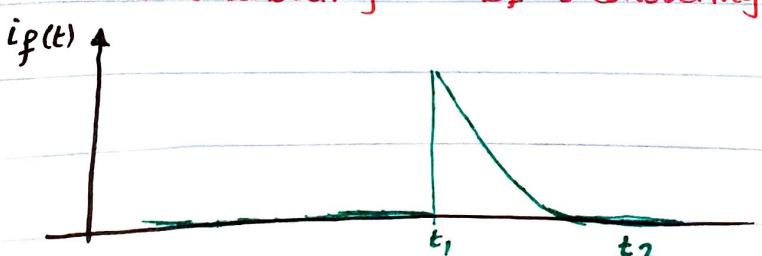


- Rectifiers:

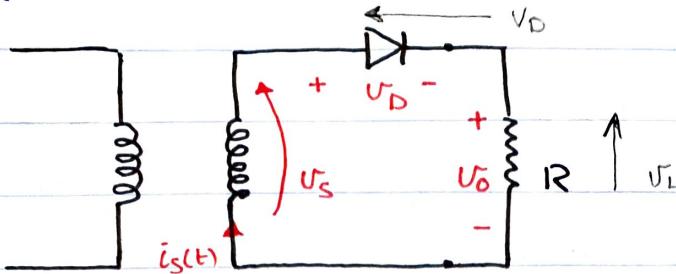1. Single-phase ($1-\phi$) Half-wave Rectifiers.



$$U_S = V_m \sin(\omega t)$$

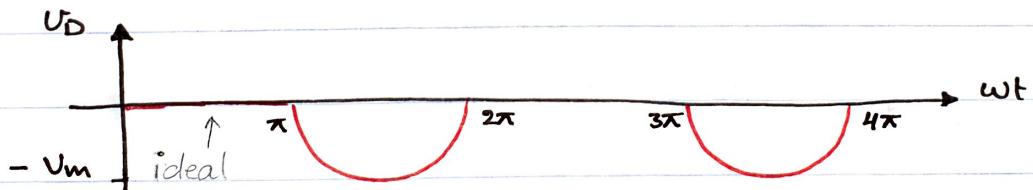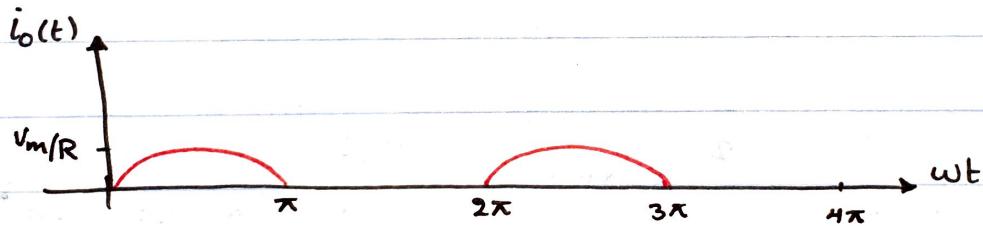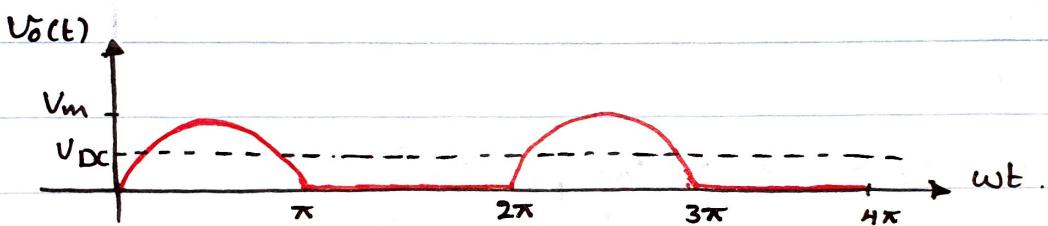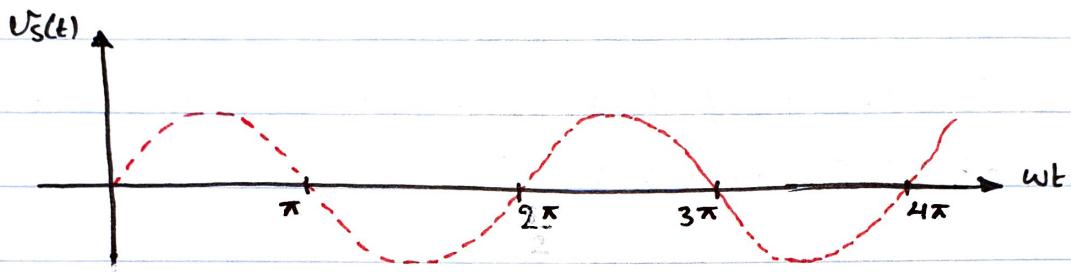

- The average value of output voltage.

$$\begin{aligned}
 U_{DC} &= \frac{1}{2\pi} \int_0^{2\pi} U_O(t) d(\omega t) \\
 &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega t) d(\omega t) \\
 &= \frac{V_m}{2\pi} \left[\cos(\omega t) \right]_0^{2\pi} = \frac{V_m}{2\pi} [\cos(0) - \cos(\pi)] \\
 U_{DC} &= \frac{V_m}{2\pi} (1 - (-1)) = \frac{V_m}{\pi}
 \end{aligned}$$

- The average Output Current is:

$$I_{DC} = \frac{V_{DC}}{R} = \frac{V_m}{\pi R}$$

- Peak inverse voltage (PIV):

It is the maximum reverse voltage across the diode when the diode is in blocking state.

$$PIV = V_m$$


- Example: For the 1-Ø half-wave rectifier with resistive load, Find η , FF, RF, TUF & CF?

$$1. \quad \eta = \frac{P_{DC}}{P_{AC}}$$

$$P_{DC} = V_{DC} I_{DC} = \left(\frac{V_m}{\pi}\right) \left(\frac{V_m}{\pi R}\right) = \frac{V_m^2}{\pi^2 R}$$

$$P_{AC} = V_{RMS} I_{RMS}$$
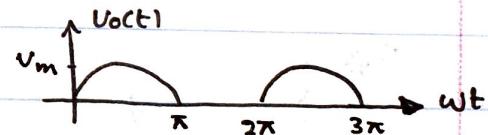
$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^\pi V_m^2 \sin^2(\omega t) d\omega t}$$



$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^\pi \frac{V_m^2}{2} (1 - \cos(2\omega t)) d\omega t}$$

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^\pi \frac{V_m^2}{2} d\omega t} = \frac{V_m}{2}$$

$$I_{RMS} = \frac{V_{RMS}}{R} = \frac{V_m}{2R}$$

$$P_{AC} = \left(\frac{V_m}{2}\right) \left(\frac{V_m}{2R}\right) = \frac{V_m^2}{4R}$$

$$\eta = \frac{V_m^2 / \pi^2 R}{V_m^2 / 4R} = \frac{4}{\pi^2} \approx 40.5\%$$

$$2. \text{ FF} = \frac{V_{\text{RMS}}}{V_{\text{DC}}} = \frac{V_m/2}{V_m/\pi} = \frac{\pi}{2} = 157\%.$$

$$3. \text{ RF} = \sqrt{\text{FF}^2 - 1} \\ = \sqrt{(1.57)^2 - 1} \approx 121\% = 1.21.$$

$$4. \text{ TUF} = \frac{P_{\text{DC}}}{V_s I_s} = \frac{V_{\text{DC}} I_{\text{DC}}}{V_s I_s}$$

$$P_{\text{DC}} = \frac{V_m^2}{\pi^2 R}, \quad V_{\text{DC}} = \frac{V_m}{\pi}, \quad I_{\text{DC}} = \frac{V_m}{\pi R}.$$


$$V_s = \frac{V_m}{\sqrt{2}}, \quad I_s = \frac{V_m}{2R}$$

$$\text{TUF} = \frac{V_m^2}{\pi^2 R} \cdot \frac{2\sqrt{2} R}{V_m^2} = \frac{2\sqrt{2}}{\pi^2} \approx 28\%.$$

$$\frac{1}{\text{TUF}} \approx 3.5.$$

- The transformer has to be around 3.5 times larger than it is needed to deliver the same power when it is supplied by a pure AC sinusoidal source.

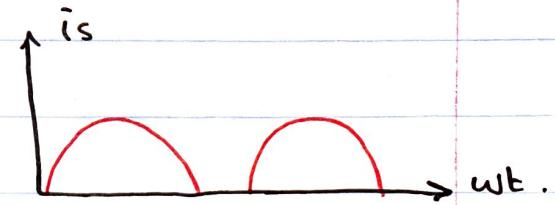- The transformer carries a DC current saturation problem in the transformer core.




$$I_s(\text{peak}) = \frac{V_m}{R}, \quad I_s = \frac{V_m}{2R}$$

$$\text{CF} = \frac{I_s(\text{Peak})}{I_s} = \frac{V_m/R}{V_m/2R} = 2.$$

CF (Creast Factor).

- 1-∅ Half-wave rectifier with RL load.

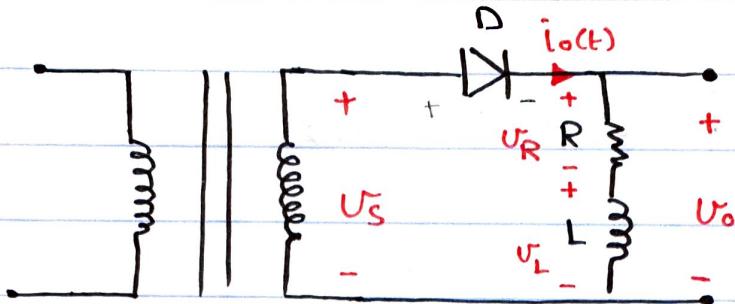

$$U_s(t) = V_m \sin(\omega t).$$

- Due to the inductive load, the condition period of the diode will extend beyond π until the current becomes zero at $\omega t = \pi + \theta$
- The average value of $U_L(t)$ is zero, since i_o is periodic.

$$\bar{U}_L = \frac{1}{T} \int_0^T U_L(t) dt = 0$$

• Proof:

$$U_L = L \frac{di_o}{dt}$$

$$U_L dt = L di_o.$$

$$\frac{1}{T} \int_0^T U_L dt = \frac{1}{T} \int_0^T L di_o.$$

$$\frac{1}{T} \int_0^T U_L dt = \frac{L}{T} [i_o(T) - i_o(0)].$$

$$\bar{U}_L = \frac{L}{T} [i_o(T) - i_o(0)]$$

$$\bar{U}_L = 0$$

• Apply KVL:


$$-U_s + R i_o + L \frac{di_o}{dt} = 0 \Rightarrow V_m \sin(\omega t) = R i_o(t) + L \frac{di_o}{dt}$$

$$i_o(t) = \frac{V_m}{Z} \sin \beta e^{-\frac{t}{\tau}} + \frac{V_m}{Z} \sin(\omega t - \beta), \quad 0 \leq \omega t \leq \pi + \theta$$

$$Z = \sqrt{R^2 + (WL)^2}$$

$$\tau = L/R$$

$$\beta = \tan^{-1}(\frac{WL}{R})$$

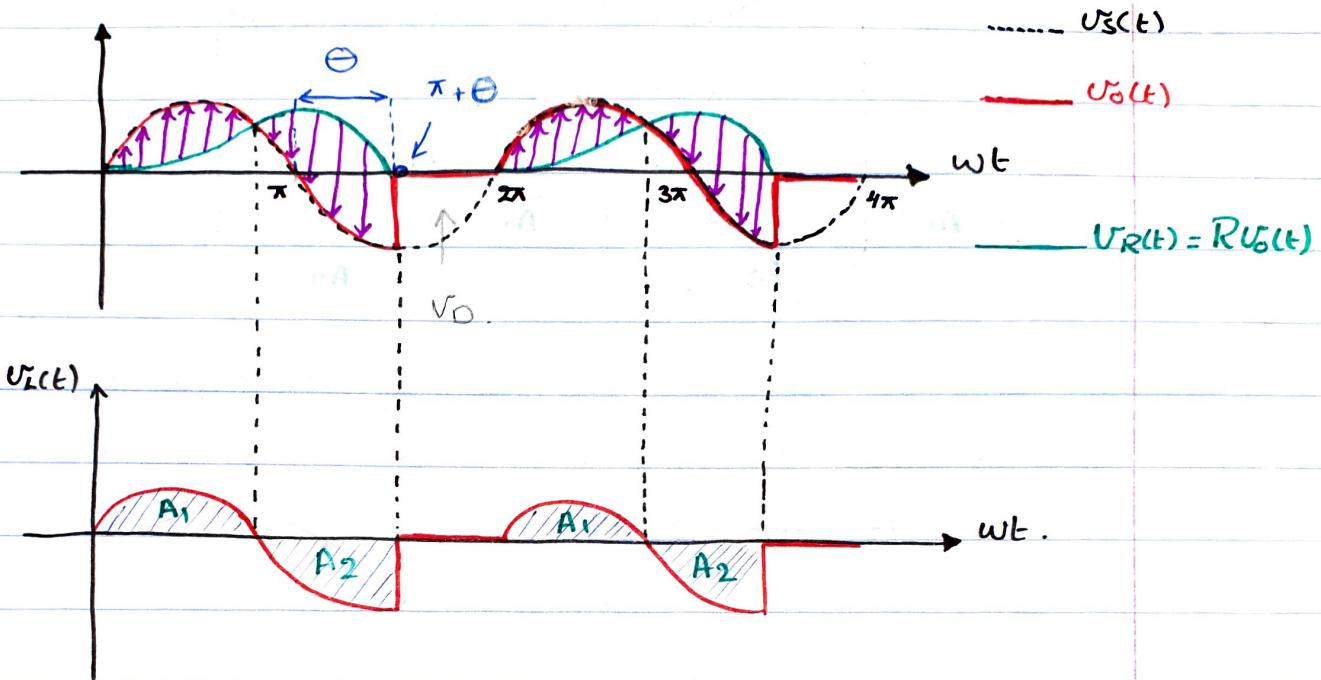


The average output voltage is

$$U_{O_DC} = \frac{1}{2\pi} \int_0^{2\pi} U_O(t) d(\omega t) = \frac{1}{2\pi} \int_0^{\pi+\theta} U_m \sin(\omega t) d(\omega t) = \frac{U_m}{2\pi} [\cos(\omega t)]_0^{\pi+\theta}$$

$$U_{O_DC} = \frac{U_m}{2\pi} (1 - \cos(\pi + \theta)) = \frac{U_m}{2\pi} (1 + \cos\theta) < \frac{U_m}{\pi}$$


$$\cos(a+b) = \cos A \cos B - \sin A \sin B$$

Addition of freewheeling diode.

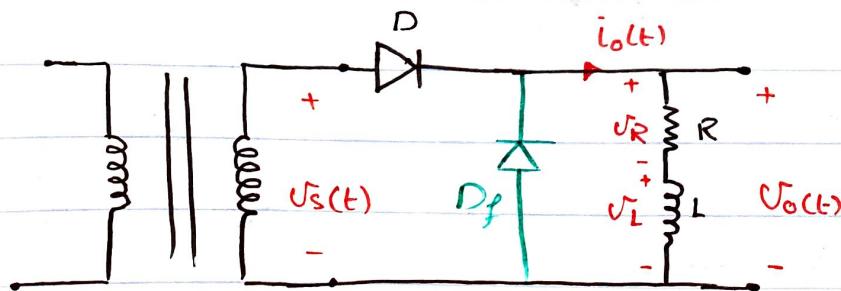

$$U_S(t) = U_m \sin(\omega t)$$

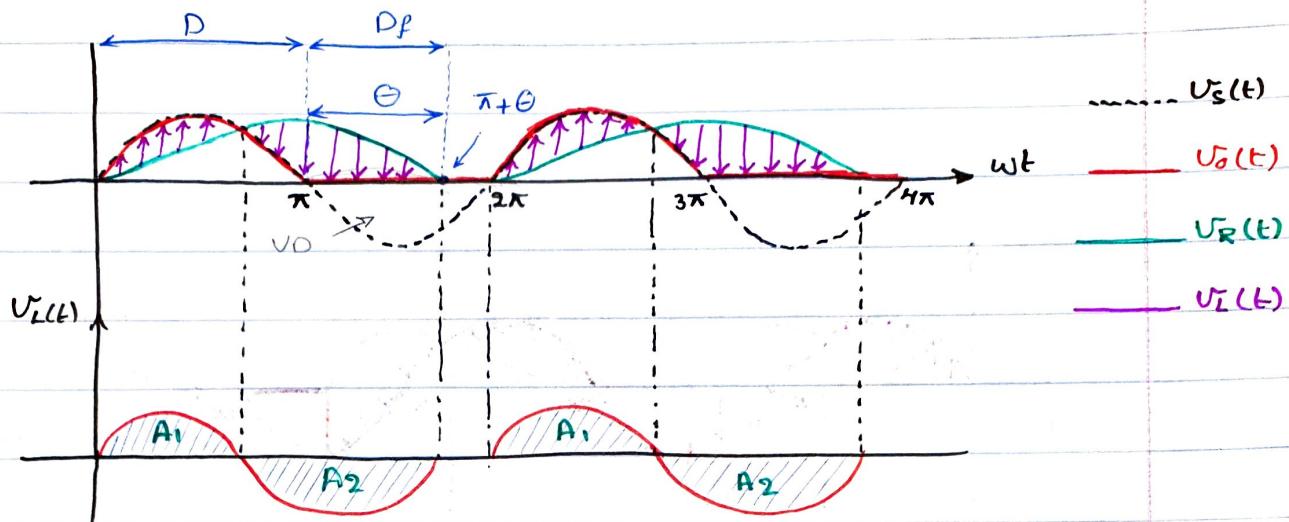
$$U_S(t) = V_m \sin [\int w(t) dt + \theta_0]$$



- The diode prevents the negative voltage to appear across the load $\rightarrow U_{dc}$ increases and becomes similar to U_{dc} in case of purely resistive load.

$(\theta \rightarrow \pi + \theta)$ without freewheeling diode, $(\theta \rightarrow \pi)$ with freewheeling diode.



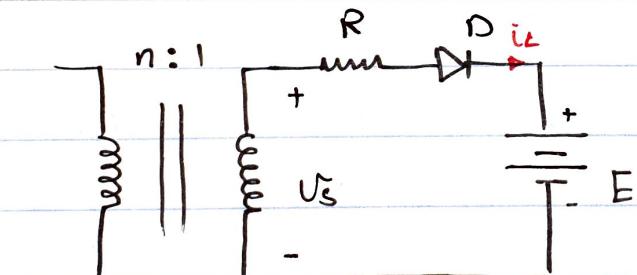
- 1-Φ Half-wave rectifiers (Battery Charger).




i_c : charging current.

The diode conducts when $U_S(t) > E$.

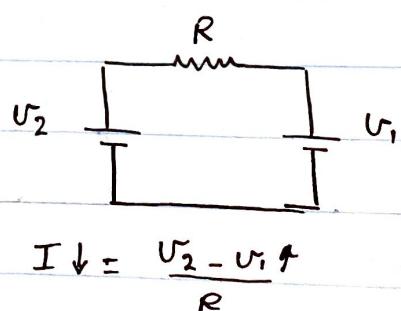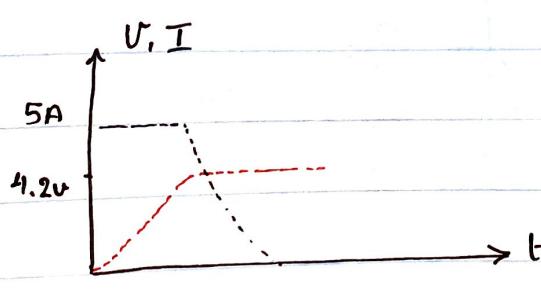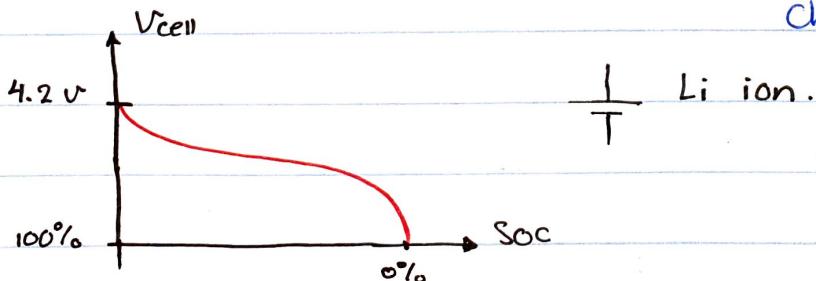R: It is used to limit the charging resistor.



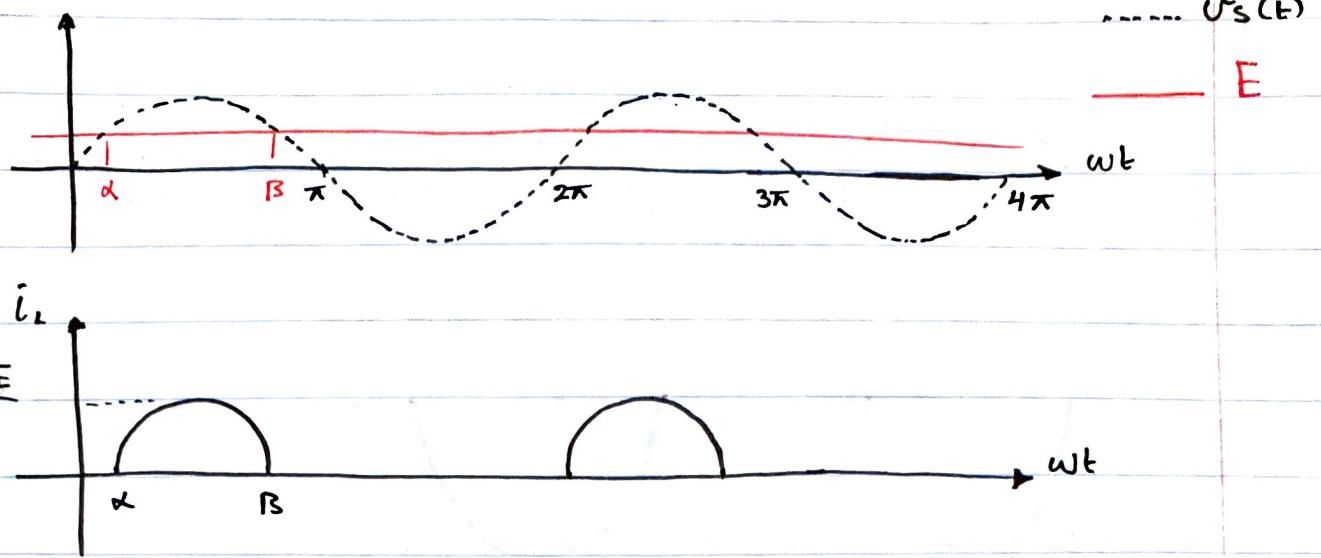

α & β are found from:

$$U_s(t) = E \Rightarrow V_m \sin(\alpha) = E$$


$$\omega t = \alpha, \quad \alpha = \sin^{-1}\left(\frac{E}{V_m}\right), \quad \beta = \pi - \alpha.$$



Charging current is given by:

$$i_L = \frac{U_s(t) - E}{R} = \frac{V_m \sin \omega t - E}{R}$$

2. Full-wave Rectifiers.

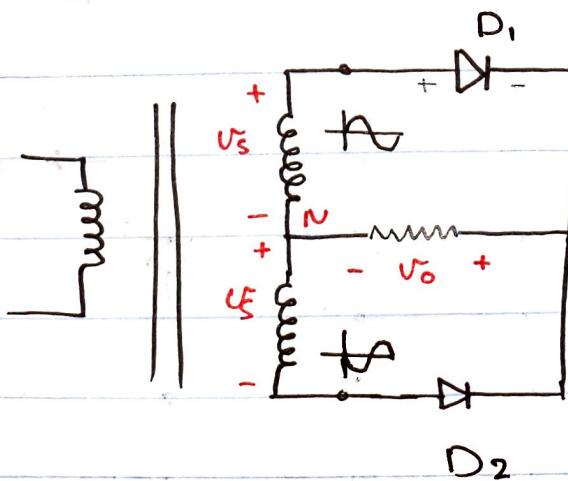2.1 Full-wave rectifier with center-tapped transformer.



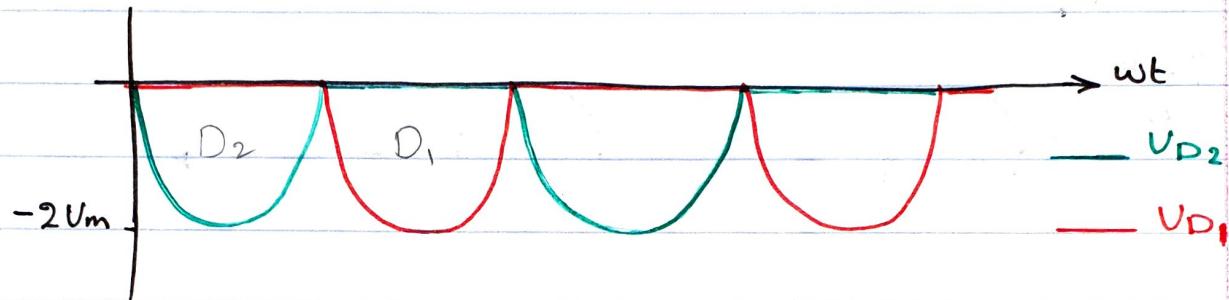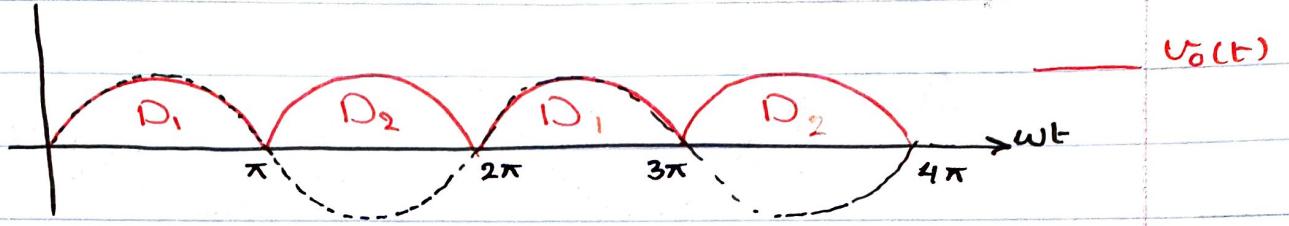

$$U_{DC} = \frac{2Vm}{\pi}$$

Rectifiers.

1. 1-Φ Half-wave.


2. 1-Φ Full-wave.

2.1) 1-Φ Full wave with Center-Tapped Transformer.


2.2) 1-Φ Full-wave bridge rectifier.

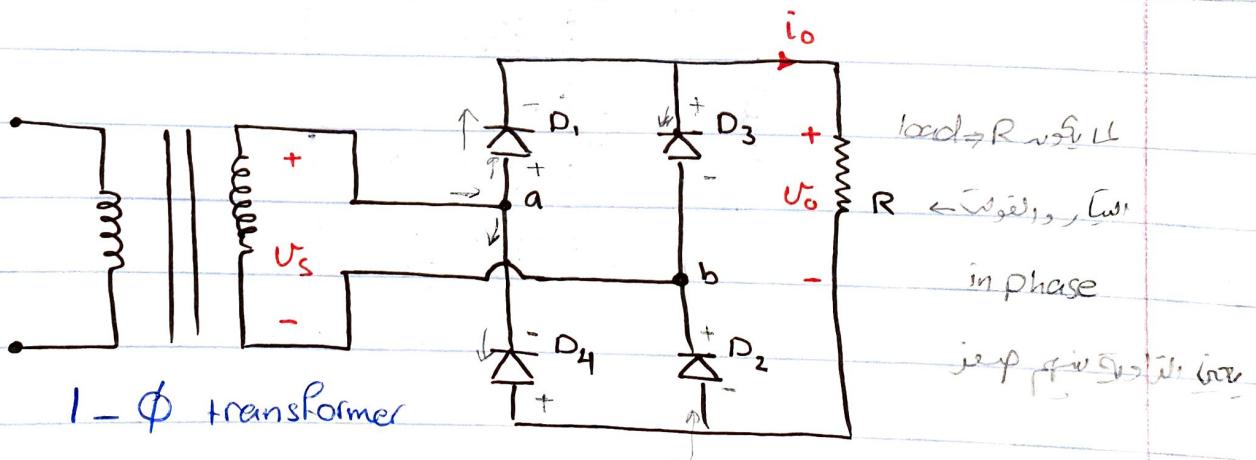2.2) 1-Φ Full-wave bridge rectifier.

It is commonly used for industrial application.



$$U_s = V_m \sin(\omega t)$$

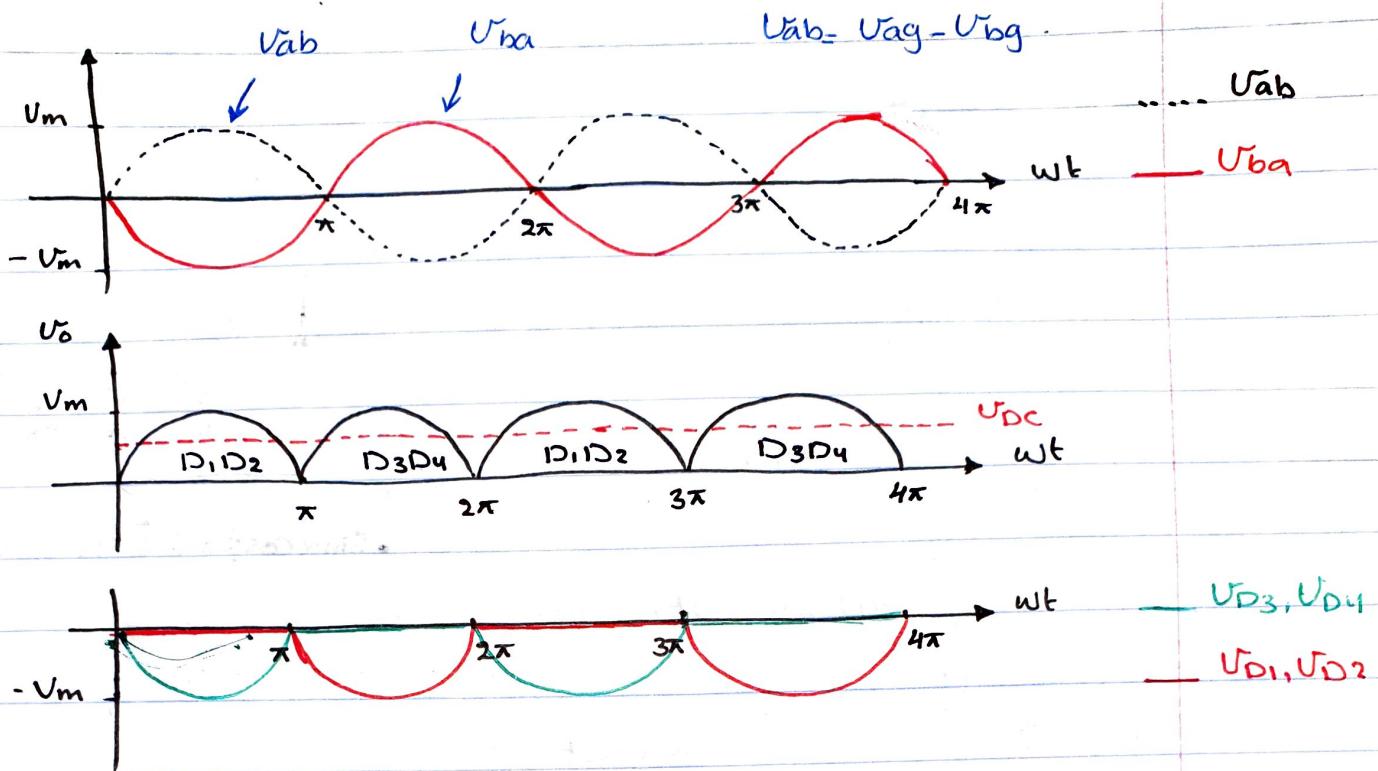

The average Output voltage :

$$U_{DC} = \frac{1}{2\pi} \int_0^{2\pi} U_0(t) d(\omega t)$$

$$U_{DC} = \frac{1}{\pi} \int_0^{\pi} V_m \sin(\omega t) d(\omega t)$$

$$U_{DC} = \frac{V_m}{\pi} \left[\cos(\omega t) \Big|_0^\pi \right] = \frac{V_m}{\pi} [1 - (-1)] = \frac{2V_m}{\pi}$$

- Note: Two diodes are conducting at once and the Forward voltage could be a problem for low voltage application (5 V power supply).
- Note: The transformer current does not carry DC current \rightarrow No DC saturation problem in the transformer core.


2, 3, 4, 9, 10, 11, 12, 13, 14, 15, 16, 17, 20, 22, 23

24, 27

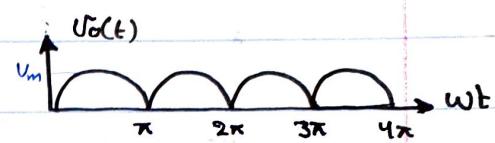- Example: Find the Fourier series for output voltage from the 1-Φ Full-wave rectifier?

Solution:

$$\tilde{U_o}(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos(nwt) + \sum_{n=1}^{\infty} b_n \sin(nwt)$$



$$a_0 = \frac{1}{2\pi} \int_0^{2\pi} \tilde{U_o}(t) dt = \frac{2U_m}{\pi}$$

$$\sin \alpha \cos \beta = \frac{1}{2} [\sin(\alpha+\beta) + \sin(\alpha-\beta)]$$

$$a_n = \frac{1}{\pi} \int_0^{\pi} \tilde{U_o}(t) \cos(nwt) dt$$

$$a_n = \frac{2}{\pi} \int_0^{\pi} U_m \sin(wt) \cos(nwt) dt$$

$$a_n = \frac{U_m}{\pi} \int_0^{\pi} \sin((n+1)wt) dt - \int_0^{\pi} \sin((n-1)wt) dt$$

$$a_n = \frac{U_m}{\pi} \left[\frac{1}{n+1} \cos((n+1)\pi) \Big|_0^\pi + \frac{1}{n-1} \cos((n-1)\pi) \Big|_0^\pi \right]$$

$$a_n = \frac{U_m}{\pi} \left[\frac{1}{n+1} (1 - \cos((n+1)\pi)) + \frac{1}{n-1} (\cos((n-1)\pi) - 1) \right]$$

When n is odd $\rightarrow a_n = 0$.

$$a_n = \frac{U_m}{\pi} \left[\frac{2}{n+1} - \frac{2}{n-1} \right] = \frac{2U_m}{\pi} \left(\frac{2n-2-2n-2}{n^2-1} \right)$$

$$a_n = -\frac{4U_m}{\pi(n^2-1)} \quad \text{when } n \text{ is even.}$$

$$b_n = \frac{1}{\pi} \int_0^{2\pi} \tilde{U_o}(t) \sin(nwt) dt$$

$$\sin \alpha \sin \beta = \frac{1}{2} [\cos(\alpha+\beta) - \cos(\alpha-\beta)]$$

$$b_n = \frac{2}{\pi} \int_0^{\pi} U_m \sin(wt) \sin(nwt) dt$$

$$b_n = \frac{V_m}{\pi} \left[\int_0^{\pi} \cos(n+1)wt \, d(wt) - \int_0^{\pi} \cos(n-1)wt \, d(wt) \right]$$


$$b_n = \frac{V_m}{\pi} \left[\frac{1}{n+1} \sin(n+1)wt \Big|_0^{\pi} - \left(\frac{1}{n-1} \right) \sin(n-1)wt \Big|_0^{\pi} \right]$$

$$b_n = 0.$$

$$\tilde{V_o}(t) = \frac{2V_m}{\pi} - \frac{-4V_m}{3\pi} \cos(2wt) \cos(4wt) - \frac{4V_m}{5\pi} \cos(6wt) -$$

$$\frac{4V_m}{35\pi} \cos(8wt) - \dots$$

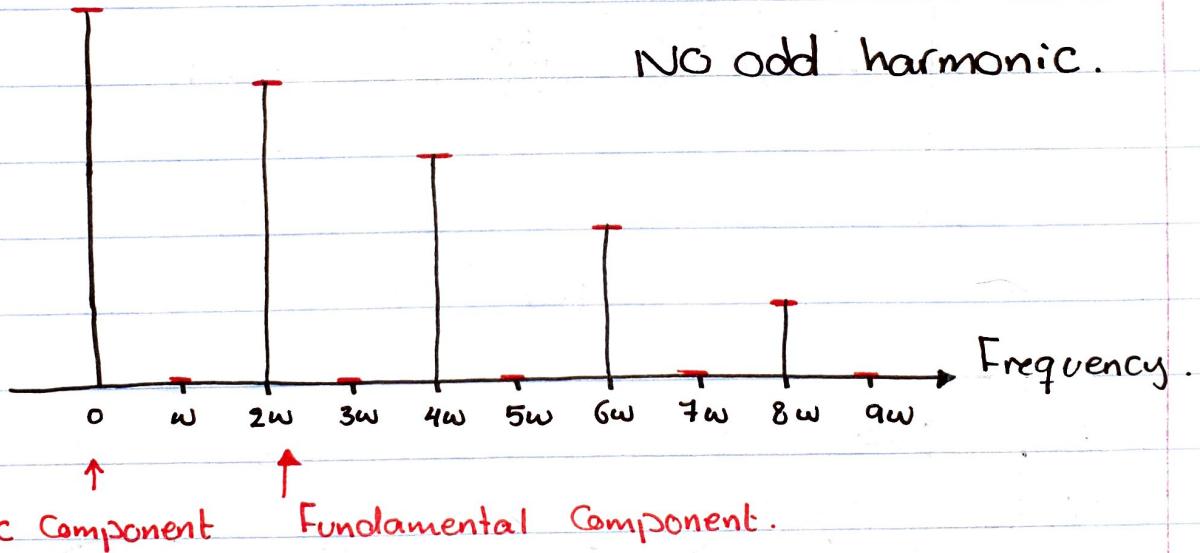
$$\tilde{V_o}(t) = \frac{2V_m}{\pi} + \sum_{\substack{n=2, \\ 4, 6, \dots}}^{\infty} \frac{4V_m}{(n^2-1)\pi} \cos(nwt - \pi)$$



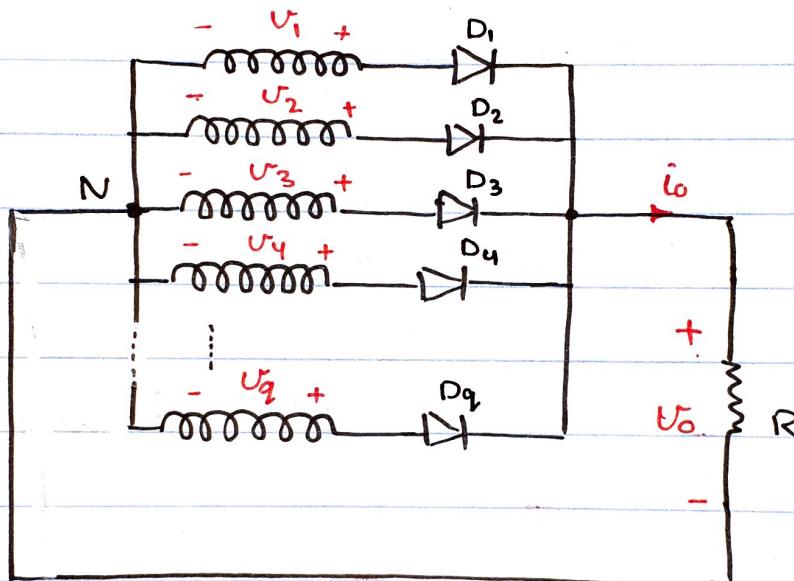3. Multi-Phase Star Rectifiers.

- The 1-Φ Full-wave rectifier is usually used in application up to 5 kw.
- The Fundamental Frequency of 1-Φ Full wave rectifier is $2w$ where w is the source frequency.

- A Filter is used to remove the harmonics. The size of the filter decreases with the increase in the Frequency of harmonic.
- For higher powers, multi-phase rectifiers are usually used to produce a fundamental component at Frequency of $q\omega$ where q is the number of phases.
- The other harmonics at frequencies $nq\omega$, $n=2, 3, \dots$




$$U_1 = U_m \sin(\omega t)$$

$$U_2 = U_m \sin(\omega t - 90^\circ)$$

$$U_3 = U_m \sin(\omega t - 180^\circ)$$

$$U_4 = U_m \sin(\omega t - 270^\circ)$$

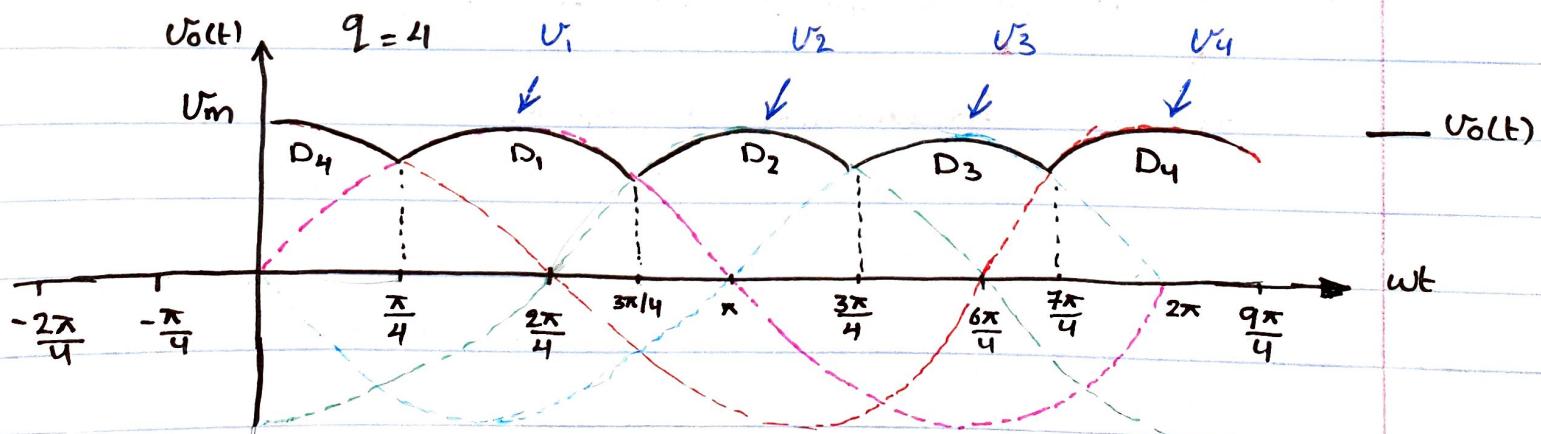
U_1, U_2, \dots, U_q are shifted from each other by $\frac{2\pi}{q}$.



- Each diode conducts for $\frac{2\pi}{q}$

- The average output voltage:

$$V_{DC} = \frac{4}{2\pi} \int_{\frac{\pi}{4}}^{\frac{3\pi}{4}} V_m \sin(\omega t) d(\omega t) = \frac{4}{2\pi} \int_{-\frac{\pi}{4}}^{\frac{\pi}{4}} V_m \cos(\omega t) d(\omega t).$$
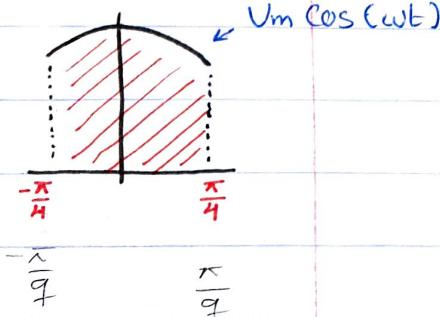
$$\begin{aligned} V_{DC} &= \frac{4 \times 2}{2\pi} \int_0^{\frac{\pi}{q}} V_m \cos(\omega t) d\omega t = \frac{2q}{2\pi}, \quad q = 4 \Rightarrow \text{Pulses} \\ &= \frac{2q}{2\pi} \int_0^{\frac{\pi}{q}} V_m \cos(\omega t) d\omega t \\ &= \frac{q}{\pi} \sin\left(\frac{\pi}{q}\right), \quad \text{valid } q > 2. \\ &= \frac{q}{\pi} V_m \sin\left(\frac{\pi}{q}\right). \end{aligned}$$


- The rms value of the output voltage:

$$V_{RMS} = \sqrt{\frac{2q}{2\pi} \int_0^{\frac{\pi}{q}} V_m^2 \cos^2(\omega t) d\omega t}, \quad \cos^2 x = \frac{1}{2}(1 + \cos 2x).$$

$$V_{RMS} = \sqrt{\frac{q}{2\pi} \int_0^{\frac{\pi}{q}} V_m^2 (1 + \cos 2\omega t) d\omega t}$$

$$= \sqrt{\frac{q}{2\pi} \left[\frac{\pi}{q} + \frac{1}{2} \sin\left(\frac{2\pi}{q}\right) \right]} \cdot V_m$$

$$V_{RMS} = V_m \sqrt{\frac{q}{2\pi} \left(\frac{\pi}{q} - \frac{1}{2} \sin\left(\frac{2\pi}{q}\right) \right)}$$

- The rms value of the transformer secondary current.

$$I_S = \sqrt{\frac{1 \times 2}{2\pi} \int_0^{\frac{\pi}{q}} I_m^2 \cos^2 \omega t d(\omega t)} ; \quad I_m = \frac{V_m}{R}$$

Single phase

- Example: A 3- ϕ star rectifier has a purely resistive load with R ohms. Determine:

- a- Efficiency . b- FF c- RF. d- TUF e- PIV
- F. Peak current through a diode if the rectifier deliver.

$I_{DC} = 30 \text{ A}$ at an output voltage of $V_{DC} = 140 \text{ V}$.

$VI \Rightarrow \text{RMS value}$

. Solution:

$$\text{a- } \eta = \frac{P_{DC}}{P_{AC}} = \frac{V_{DC} I_{DC}}{V_{RMS} I_{RMS}}$$

$$V_{DC} = \frac{3 \times 2}{2\pi} \int_0^{\pi/3} U_m \cos(\omega t) dt$$

$$V_{DC} = \frac{3}{\pi} U_m \sin\left(\frac{\pi}{3}\right) = \frac{3\sqrt{3}}{2\pi} U_m \quad U_m = 0.827 U_{Vm}$$

$$I_{DC} = \frac{V_{DC}}{R} = 0.827 \frac{U_m}{R}$$

$$V_{RMS} = \sqrt{\frac{3 \times 2}{2\pi} \int_0^{\pi/3} U_m^2 \cos^2(\omega t) dt}$$

$$V_{RMS} = \sqrt{\frac{3}{2\pi} U_m^2 \int_0^{\pi/3} (1 + \cos(2\omega t)) dt}$$

$$V_{RMS} = \sqrt{\frac{3}{2\pi} U_m^2 \left(\frac{\pi}{2} + \frac{1}{2} \sin\left(\frac{2\pi}{3}\right) \right)}$$

$$V_{RMS} = 0.841 U_m ; I_{RMS} = \frac{V_{RMS}}{R} = 0.841 \frac{U_m}{R}$$

$$\eta = \frac{(0.827)^2 (U_m^2 / R)}{(0.841)^2 (U_m^2 / R)} = 96.77 \%$$

V_{DC} \leftarrow
at
diode off

$$b. \text{ FF} = \frac{V_{RMS}}{V_{DC}} = \frac{0.841 V_m}{0.827 V_m} = 101.65\%$$

$$c. \text{ RF} = \sqrt{\text{FF}^2 - 1} = \sqrt{(1.0165)^2 - 1} = 18.94\%$$

$$d. \text{TUF} = \frac{V_{DC} I_{DC}}{V_s I_s}$$

$$3-\phi \rightarrow 3 V_s I_s$$

$$V_s = V_m / \sqrt{2}, \quad I_s = \frac{V_m}{2R}$$

$$I_s = \sqrt{\frac{1 \times 2}{2\pi} \int_0^{\pi/3} I_m^2 \cos^2(\omega t) d(\omega t)}$$

$$I_s = \sqrt{\frac{1}{2\pi} I_m^2 \left(\frac{\pi}{3} + \frac{1}{2} \sin \frac{\pi}{3} \right)} = 0.4854 \frac{V_m}{R}$$

$$\text{TUF} = \frac{(0.827)^2 V_m^2 / R}{3 \left(\frac{1}{\sqrt{2}} \right) (0.4854) \frac{V_m^2}{R}} = 66.43\%$$

$$e. \text{ PIV} = \sqrt{3} V_m$$

$$f. \text{ I}_{\text{diode, peak}} = \frac{V_m}{R} = I_m$$

$$R = \frac{V_{DC}}{I_{DC}} = \frac{140}{30} \Omega$$

$$V_m = \frac{V_{DC}}{0.827} = \frac{140}{0.827}$$

$$\text{I}_{\text{diode, peak}} = \frac{120}{0.827} \cdot \frac{30}{140}$$

$$= 36.27 \text{ A.}$$

$$I_d = I_m \cdot \frac{1}{\pi} \sin \frac{\pi}{q}$$


$$I_d = 0.2757 I_m$$

$$I_d = 30 / 0.2757$$

$$I_m = 10 / 0.2757$$

$$= 36.27 \text{ A}$$

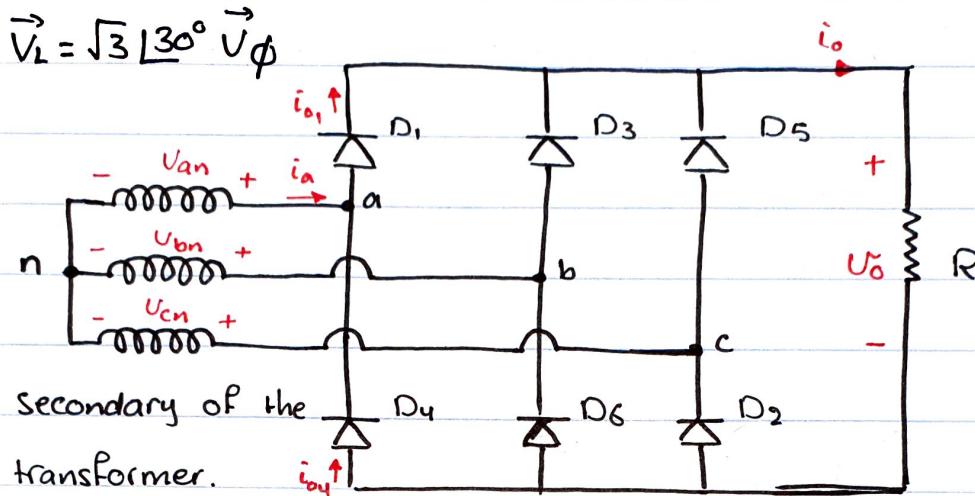4- Three-Phase Full-Wave Bridge Rectifier.



$$U_{an} = U_m \sin(\omega t - 30^\circ)$$


$$\bar{U}_{ab} = \sqrt{3} U_m \sin(\omega t).$$

$$U_{bn} = U_m \sin(\omega t - 150^\circ)$$


$$\bar{U}_{bc} = \sqrt{3} U_m \sin(\omega t - 120^\circ)$$

$$U_{cn} = U_m \sin(\omega t + 90^\circ)$$
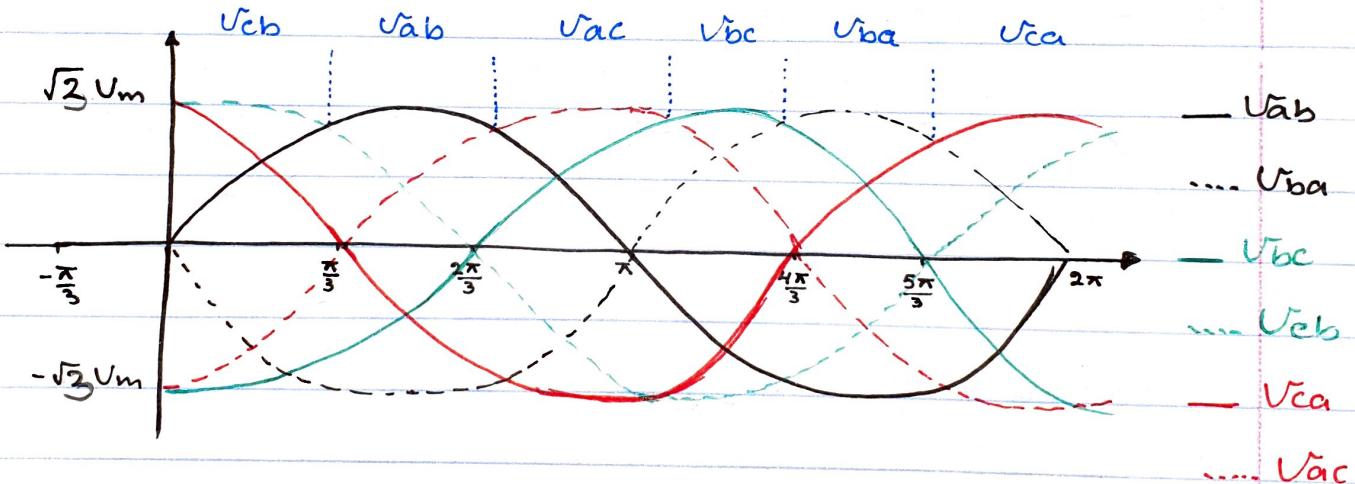
$$\bar{U}_{ca} = \sqrt{3} U_m \sin(\omega t + 120^\circ).$$



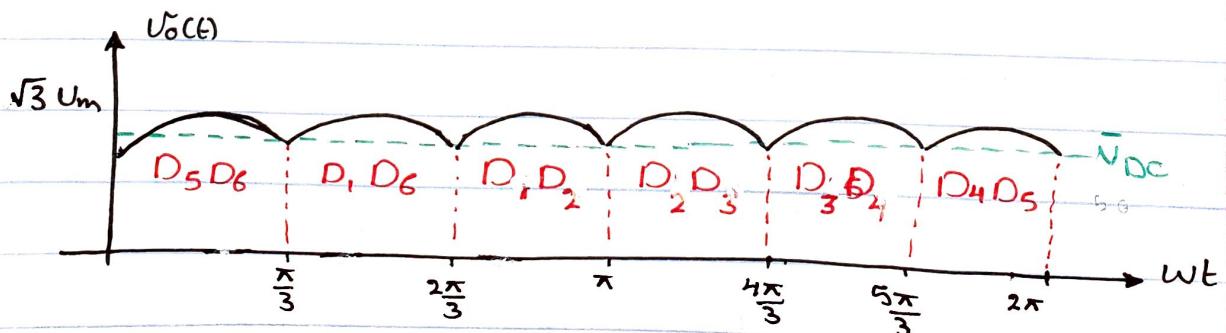
$$\bar{U}_{cb} = \bar{U}_{cg} - \bar{U}_{bg}.$$




- Each diode conducts for $\frac{2\pi}{3}$.

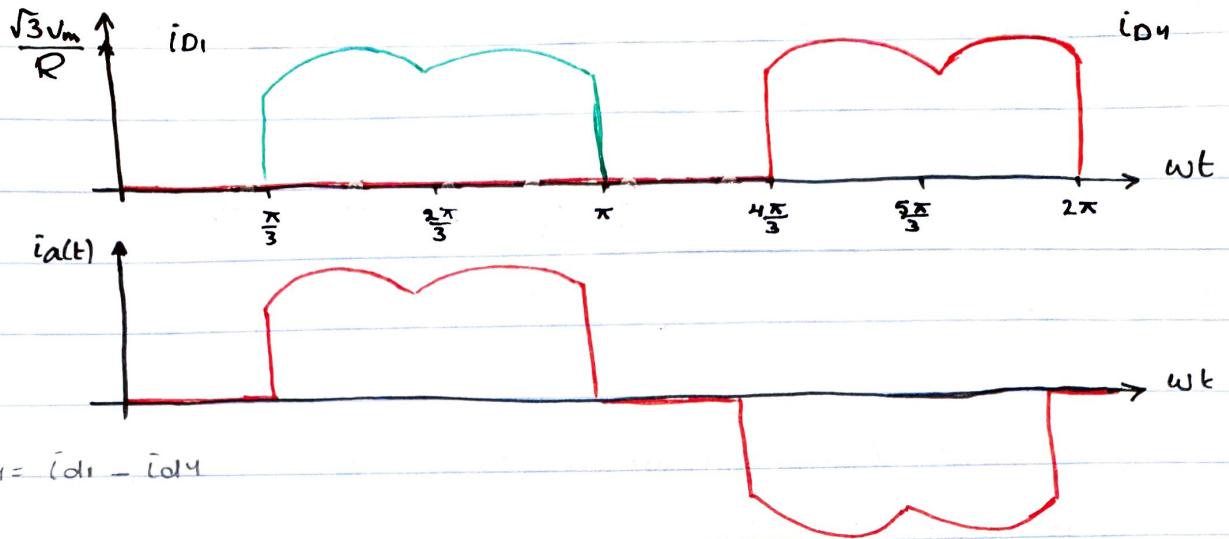- Conduction sequence of diodes: D₁D₂, D₂D₃, D₃D₄, D₄D₅, D₅D₆, D₆D₁, ...



- The average output voltage :
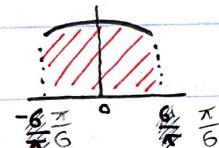
$$V_{DC} = \frac{1}{2\pi} \int_0^{2\pi} V_o(t) d(\omega t)$$



$$V_{DC} = \frac{6}{2\pi} \int_0^{\pi/3} V_{cb} d(\omega t) = \frac{6}{2\pi} \int_0^{\pi/3} \sqrt{3} V_m \sin(\omega t - 120^\circ) d(\omega t)$$

$$V_{DC} = -\frac{6}{2\pi} \int_{-\pi/6}^{\pi/6} \sqrt{3} V_m \sin(\omega t - 90^\circ) d(\omega t)$$

$$V_{DC} = \frac{6 \times 2}{2\pi} \int_0^{\pi/6} \sqrt{3} V_m \cos(\omega t) d(\omega t)$$

$$V_{DC} = \frac{6}{\pi} \sqrt{3} V_m \sin\left(\frac{\pi}{6}\right) = \frac{3\sqrt{3}}{\pi} V_m$$

- The rms value of the output voltage :

$$V_{RMS} = \sqrt{\frac{6 \times 2}{2\pi} \int_0^{\pi/6} (\sqrt{3} V_m \cos(\omega t))^2 d(\omega t)}$$

$$V_{RMS} = \sqrt{\frac{9}{\pi} \int_0^{\pi/6} (1 + \cos(2\omega t)) d(\omega t)} \cdot V_m$$

$$V_{RMS} = \sqrt{\frac{9}{\pi} \left[\frac{\pi}{6} + \frac{1}{2} \cdot \frac{\sqrt{3}}{2} \right]} \cdot V_m = 1.6554 V_m$$

- The rms value of the transformer secondary current.

$$I_s = \sqrt{\frac{4 \times 2}{2\pi} \int_0^{\pi/6} I_m^2 \cos^2(\omega t) d(\omega t)} \quad ; \quad I_m = \frac{\sqrt{3}}{R} V_m$$

$$I_s = \sqrt{\frac{2}{\pi} \left[\frac{\pi}{6} + \frac{1}{2} \cdot \frac{\sqrt{3}}{2} \right]} \cdot I_m \rightarrow I_s = 0.7804 I_m$$

- Example: A 3-Φ Full-wave bridge rectifier, supplying a purely resistive load of R.

1. Draw the circuit.
2. Plot the output voltage and the input current - i_a, i_b, i_c
3. Determine:
 - η
 - FF
 - RF
 - TUF
 - PIV
- f. Peak current of the diode.

The rectifier delivers $I_{DC} = 60$ A at output voltage of $V_{DC} = 280.7$ V and Frequency of 60 Hz.

$$a. \eta = \frac{P_{DC}}{P_{AC}} = \frac{N_{PC} I_{DC}}{V_{RMS} I_{RMS}}$$

$$V_{DC} = \frac{6 \times 2}{2\pi} \int_0^{\pi/6} \sqrt{3} V_m \cos(\omega t) d(\omega t) = \frac{3\sqrt{3}}{\pi} V_m$$

$$V_{DC} = 1.6542 V_m, \quad I_{DC} = \frac{1.6542}{R} V_m$$

$$V_{RMS} = \sqrt{\frac{6 \times 2}{2\pi} \int_0^{\pi/6} (\sqrt{3} V_m \cos(\omega t))^2 d(\omega t)}$$

$$V_{RMS} = \sqrt{\frac{9}{\pi} \left[\frac{\pi}{6} + \frac{1}{2} \cdot \frac{\sqrt{3}}{2} \right]} \cdot V_m = 1.6554 V_m$$

$$I_{RMS} = \frac{1.6554}{R} V_m, \quad \eta = \frac{(1.6542)^2}{(1.6554)^2} = 99.86\%$$

$$b. \text{ FF} = \frac{V_{\text{RMS}}}{V_{\text{DC}}} = \frac{1.6554}{1.6542} = 1.0007 = 100.07\%.$$

$$c. \text{ RF} = \sqrt{\text{FF}^2 - 1} = \sqrt{(1.0007)^2 - 1} = 3.74\%.$$

$$d. \overline{\text{TUF}} = \frac{V_{\text{DC}} I_{\text{DC}}}{\sqrt{3} V_s I_s}, \quad V_s (\text{line to line RMS}). \quad \frac{\sqrt{3} V_m}{\sqrt{2}}$$

$$V_s = \frac{\sqrt{3} V_m}{\sqrt{2}}, \quad I_s = \sqrt{\frac{4 \times 2}{2\pi} \int_0^{\pi/6} I_m^2 \cos^2(\omega t) d(\omega t)}$$

$$= \sqrt{\frac{2}{\pi} \left(\frac{6}{\pi} + \frac{1}{2} \cdot \frac{\sqrt{3}}{2} \right)} I_m = 0.7804 I_m.$$

$$\overline{\text{TUF}} = \frac{(1.6542)^2 (V_m^2 / R)}{\sqrt{3} \left(\frac{\sqrt{3}}{\sqrt{2}} V_m \right) \left(0.7804 \cdot \frac{\sqrt{3} V_m}{R} \right)} = 0.9545.$$

$$e. \text{ PIV} = \sqrt{3} V_m.$$

$$f. I_{D, \text{peak}} = \frac{\sqrt{3} V_m}{R} = \frac{\sqrt{3} (V_{\text{DC}} / 1.6542)}{(V_{\text{DC}} / I_{\text{DC}})}$$


$$I_{D, \text{peak}} = \frac{\sqrt{3} (60)}{1.6542} \approx 62 \text{ A}.$$

$$I_d = I_m \frac{1}{\pi} \sin \frac{\pi}{q}$$




$$I_d = \frac{60}{3} = 20.$$



- The effect of load and source inductances.

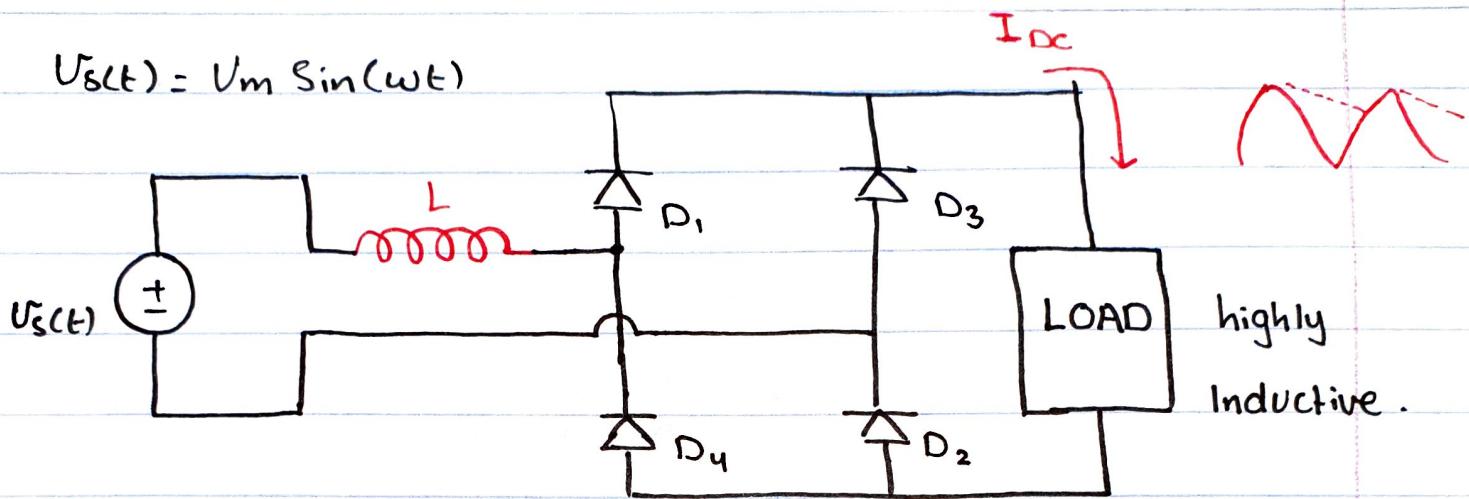Consider a 1-Φ full-wave bridge rectifier supplying a highly inductive load.



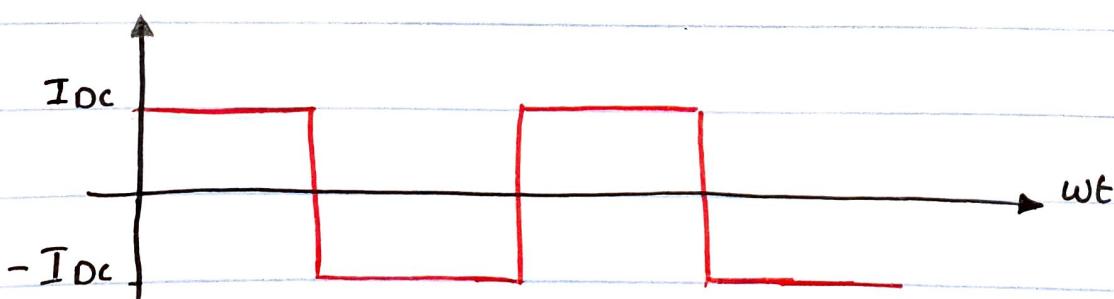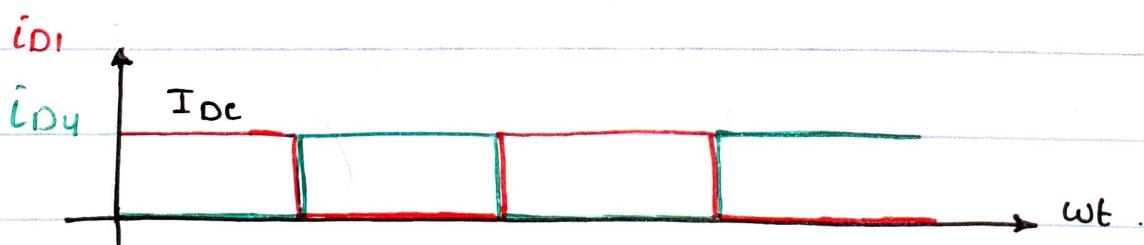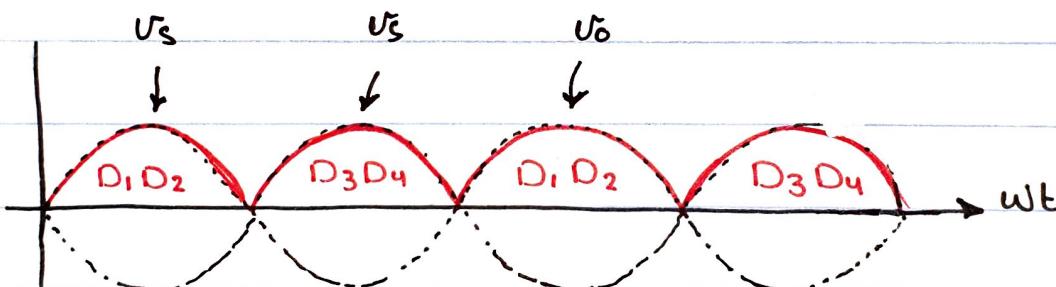- The highly inductive load Causes the load current to be continuous and free ripple - (constant).



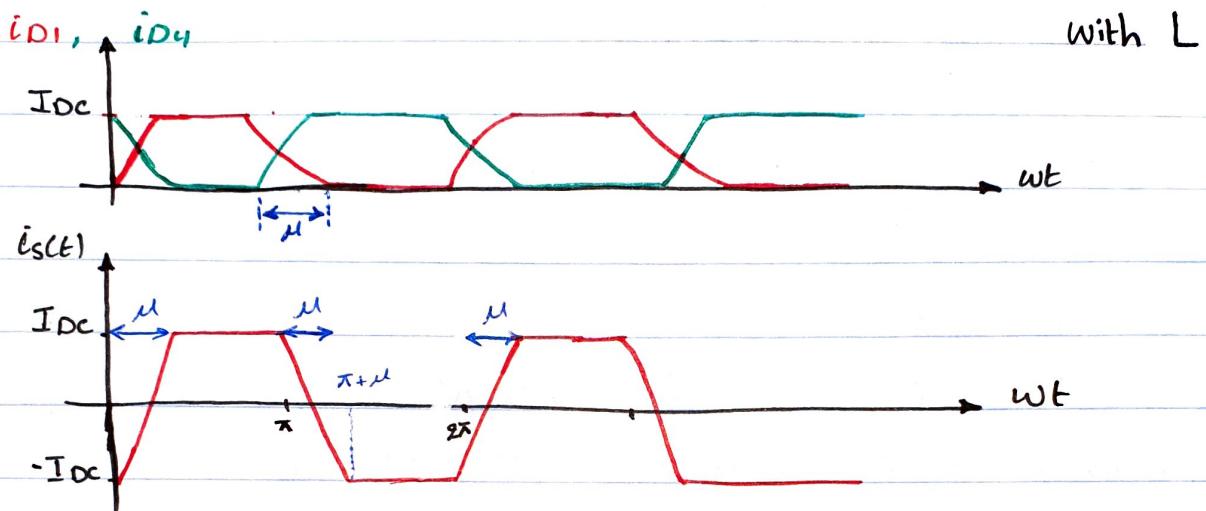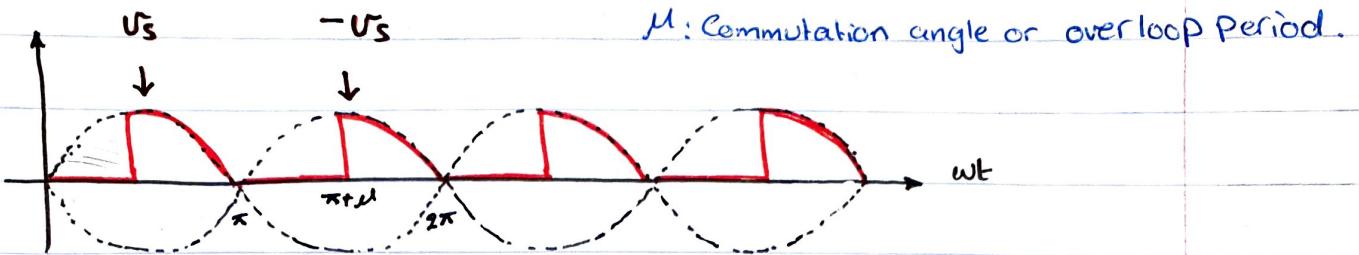


- Equivalent Circuit during overloop period.

$$U_S(t) = L \frac{di_s(t)}{dt} = V_m \sin(\omega t)$$

$$\int_{i_s(\pi)}^{i_s(\pi+\mu)} wL di_s(t) = \int_{\pi}^{\pi+\mu} V_m \sin(\omega t) d\omega t$$

$\pi \leq \omega t \leq \pi + \mu$

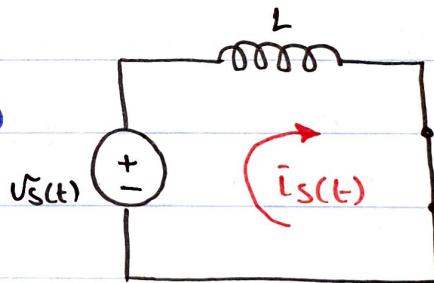

$$wL(i_s(\pi+\mu) - i_s(\pi)) = V_m (\cos \pi - \cos(\pi + \mu))$$

$$-2wL I_{DC} = V_m (-1 + \cos \mu)$$

$$\cos \mu = 1 - \frac{2wL I_{DC}}{V_m}$$

- The average voltage reduction, V_x , due to commutation is:

$$V_x = V_{DC} - V_{DC}$$

V_{DC} : without L .

V_{DC} : with L .

$$V_x = \frac{2V_m}{\pi} - \frac{2}{2\pi} \int_{-\pi}^{\pi} V_m \sin(\omega t) d(\omega t)$$

$$V_x = \frac{2V_m}{\pi} + \frac{V_m}{\pi} [\cos(\pi) - \cos(\pi)]$$

$$V_x = \frac{V_m}{\pi} [1 - \cos \pi]$$

$$V_x = \frac{V_m}{\pi} \left(\frac{2\omega L I_{DC}}{V_m} \right) = \frac{2\omega L I_{DC}}{\pi}$$

$\rightarrow V_x = 4PL I_{DC}$. single phase

where; F is the source frequency.

The average output voltage is given by:

$V_{DC} = \frac{2V_m}{\pi} - V_x$.

- For 3-Φ Full-wave bridge rectifier:

$$V_x = 6PL I_{DC}$$

$$V_{DC} = \frac{3\sqrt{3}V_m}{\pi} - V_x$$

- Example: A 3-Φ bridge rectifier is supplied from Y-connected $208\text{ V}_{L-L, rms}$ source. The load current is 60 A, and has ignored ripple. Calculate the percentage reduction of the output voltage due to commutation, and then calculate the average output voltage if the line inductance per phase is 0.5 mH.

Solution:

$$V_x = 6PL I_{DC}$$

$$= 6(60)(0.5)(10^{-3})(60)$$

$$= 10.8 \text{ V}$$

$$V_{DC} = \frac{3\sqrt{3} V_m}{\pi} - U_x$$

$$= \frac{3\sqrt{3} (\sqrt{2}/\sqrt{3})(208)}{\pi} = 280.7$$

$$\% = \frac{10.8}{280.7} = 3.85\% \quad \frac{U_x}{V_{DC}}$$


$$V_{DC} = 280.7 - 10.8 \quad V_{DC} - U_x$$

$$V_{DC} = 266.9 \text{ V}$$

- Rectifier Circuit Design.

- The output of all rectifiers contains harmonics (DC Pulse AC ripple). Therefore, Low pass DC Filter are used to reduce the ripple (harmonics).
- Types of DC Filters.
 - C-type Capacitor smoothing.
 - L-type Inductor smoothing.
 - LC-type.
- The input current also contains harmonics, due to rectification process.
- Low pass AC Filters are needed to reduce the harmonics from the grid.


LC-filter.

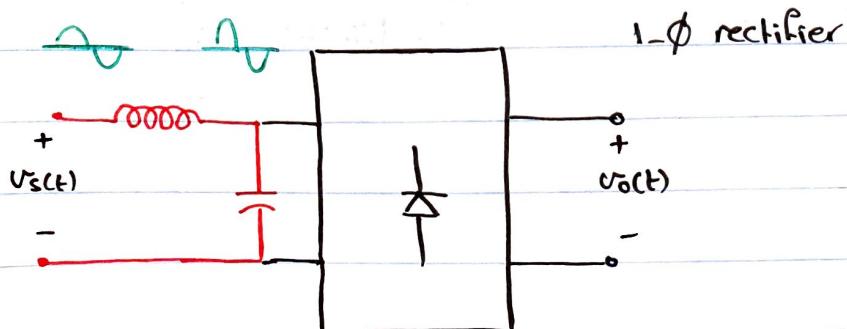


1. C-type Filter.

3-Φ AC Source



"Grid"


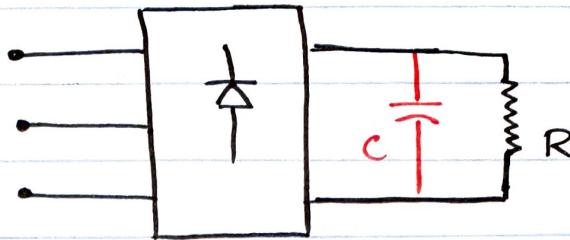


- Consider a 1-Φ Full-wave rectifier.

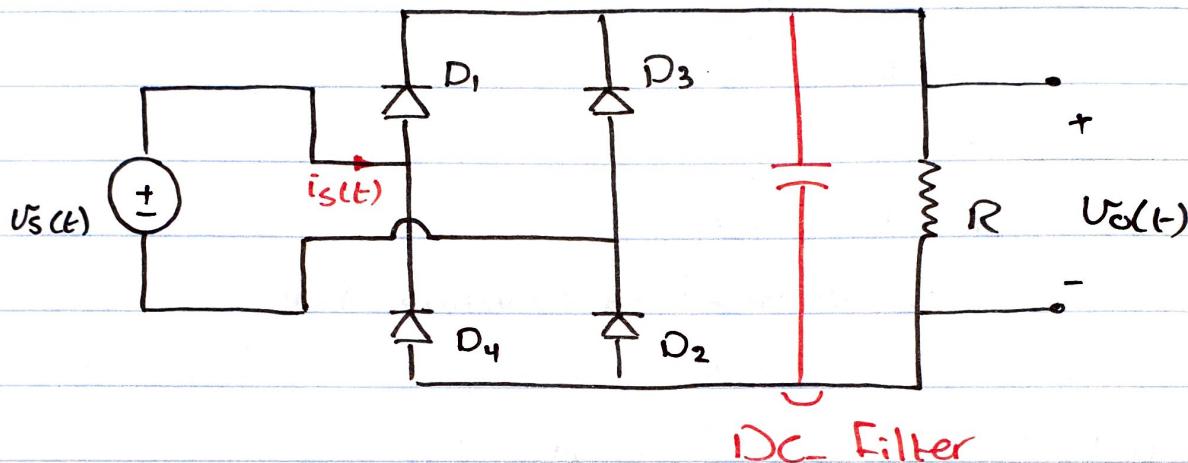

- Circuit model.

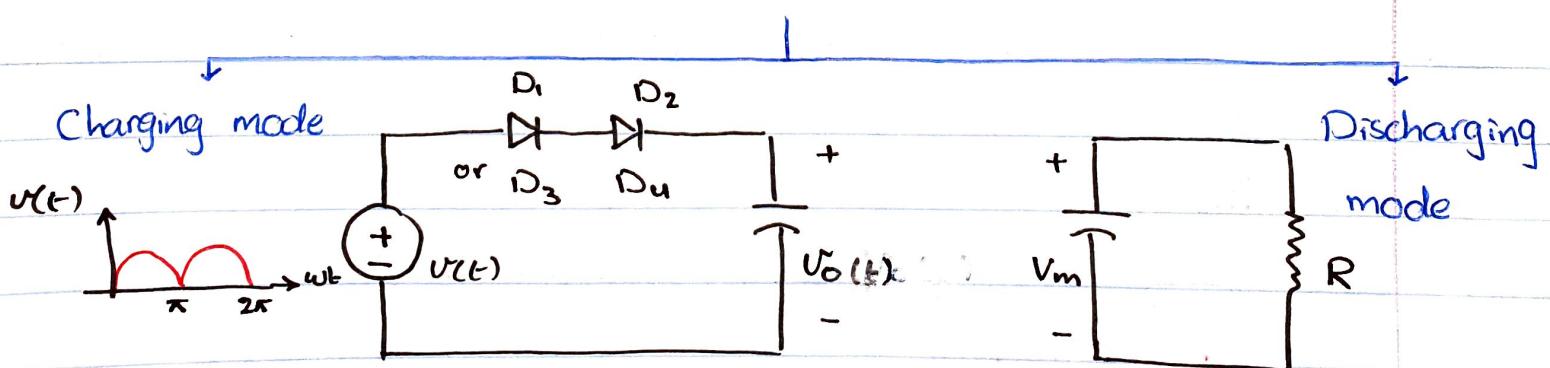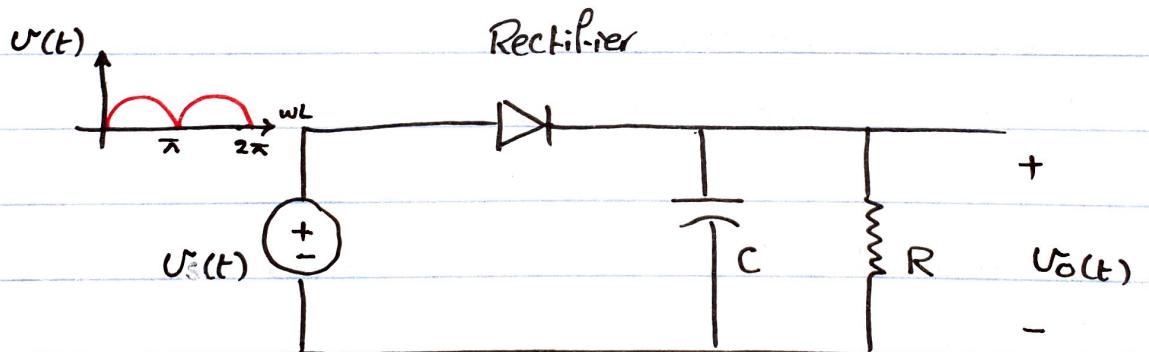

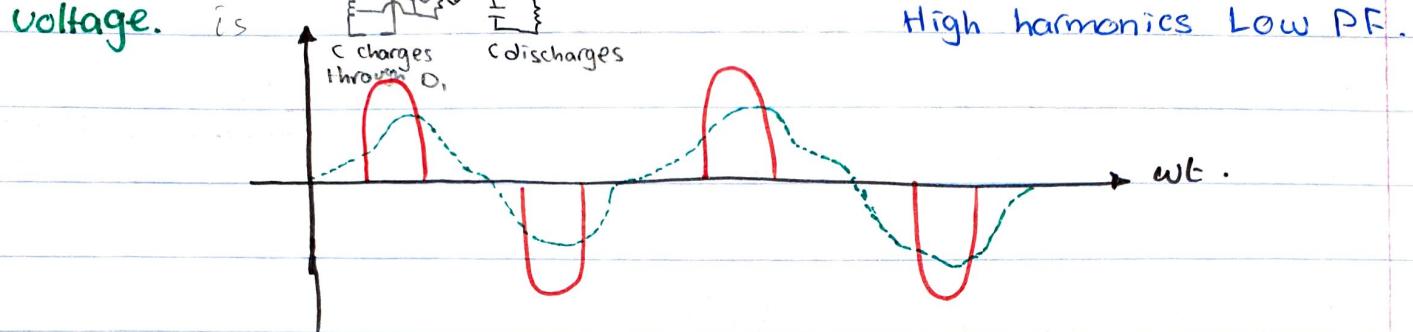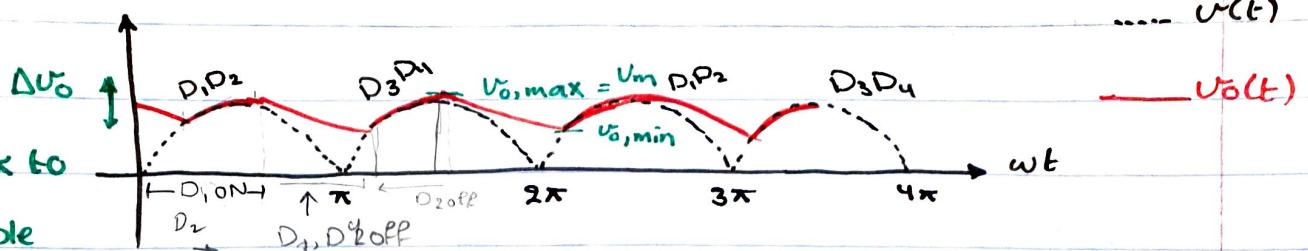


- The diode current is given by:

$$i_D = i_C + i_R = C \frac{dV_o}{dt} + \frac{V_o}{R} = WC V_m \cos(\omega t) + \frac{V_m \sin(\omega t)}{R}$$

- The Output voltage across the capacitor during the discharging mode is:

$$V_o(t) = V_m e^{-\frac{t}{\tau}}, \tau = RC.$$
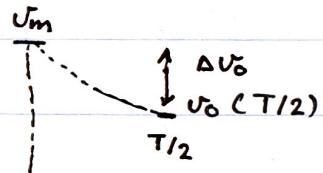
$$\tau \gg \frac{T}{2}; T: \text{is the period } T = 1/f.$$



Using Taylor expansion:

$$e^{-x} \approx 1 - x \text{ if } x \text{ is small.}$$

$$V_o(t) \approx V_m \left(1 - \frac{t}{\tau}\right).$$

$$\Delta V_o = V_{o,\max} - V_{o,\min}.$$

$$V_{o,\max} = V_m.$$

$$V_{o,\min} = V_o(T/2) = V_m \left(1 - \frac{T}{2\tau}\right).$$

$$\Delta V_o = V_m - V_m \left(1 - \frac{T}{2\tau}\right).$$

$$\Delta V_o = \frac{V_m T}{2\tau}.$$

$$\Delta V_o = \frac{V_m}{2fRC}$$

- In general ;


$$\Delta V_o = \frac{V_{max}}{f_r R C}$$

where; V_{max} is the maximum value of $v_o(t)$.

f_r is called the ripple frequency.

The average Output voltage is ; V_{DC} .
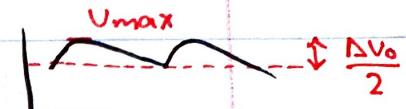
$$V_{DC} = V_{max} - \frac{\Delta V_o}{2} = V_{max} \left(1 - \frac{1}{2f_r R C} \right)$$



Type of rectifier.

V_{max}

f_r

1-Φ half-wave.

V_m

f

1-Φ full-wave.

V_m

$2f$

2-Phase Star

V_m

$2f$

3-Phase bridge

$\sqrt{3} V_m$

$6f$

- IF ΔV_o is small , the load current is approximated as

$$I_{DC} = \frac{V_{max}}{R}$$



$$\Delta V_o = \frac{I}{f_r C} . \quad I \uparrow \Rightarrow \Delta V_o \uparrow \Rightarrow V_{DC} \downarrow$$

Rectifier Circuit Design.

1. C-type Filter

3-Φ AC-Source

1-Φ AC-Source.

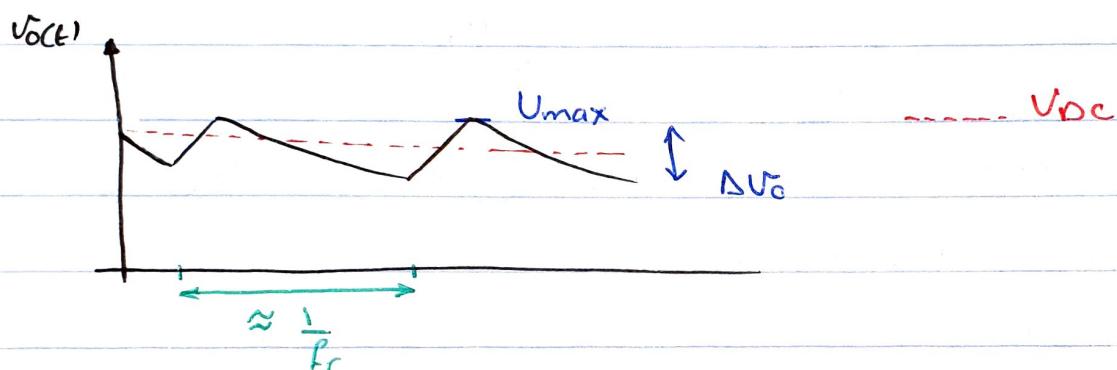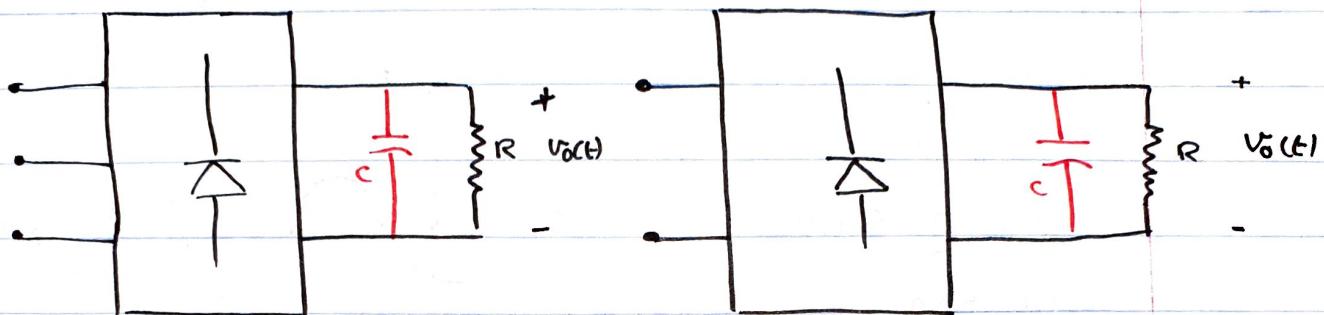

Peak to Peak ripple voltage.

$$\Delta V_o = \frac{U_{max}}{f_r R C}$$

The average Output voltage

$$V_{DC} = U_{max} - \frac{\Delta V_o}{2} = U_{max} \left(1 - \frac{1}{2 f_r R C} \right)$$

Since ΔV_o is small, the average load current is approximated as:

$$I_{DC} = \frac{U_{max}}{R}$$

$$\Delta V_o = \frac{I_{DC}}{f_r C}$$

$$V_{DC} = U_{max} - \frac{I_{DC}}{2 f_r C}$$


- Ripple factor:

$$RF = \frac{V_{AC}}{V_{DC}}$$

Where; V_{AC} is RMS value of the AC component (ripple).

$$V_{AC} = \frac{\Delta U_0}{2\sqrt{2}}, \text{ by}$$


assuming sinusoidal wave form.

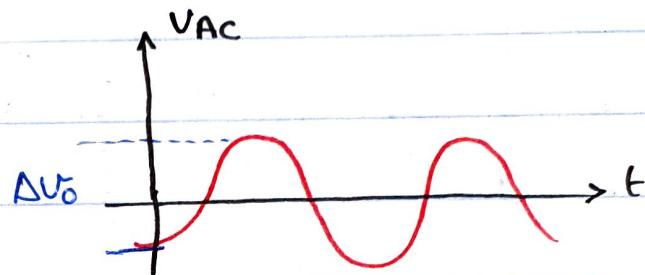

OR:

$$V_{AC} = \frac{\Delta U_0}{2\sqrt{3}}, \text{ by}$$

assuming triangular waveform.

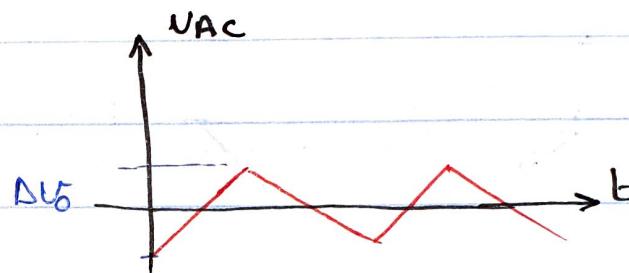

$V_{AC} = \frac{\Delta U_0}{2\sqrt{2}}$; It gives more margin for safety.

$$RF = V_{AC} / V_{DC}.$$

$$V_{AC} = \frac{\Delta U_0}{2\sqrt{2}} = \frac{U_{max}}{2\sqrt{2} f_r R C}$$

$$V_{DC} = U_{max} \left(1 - \frac{1}{2f_r R C}\right)$$


$$RF = \frac{1}{2\sqrt{2} f_r R C} \cdot \frac{1}{\left(1 - \frac{1}{2f_r R C}\right)}$$

$$RF = \frac{1}{\sqrt{2}} \cdot \frac{1}{(2f_r R C - 1)}$$



2. L-type Filter.

3-Φ AC Source.

1-Φ AC Source.

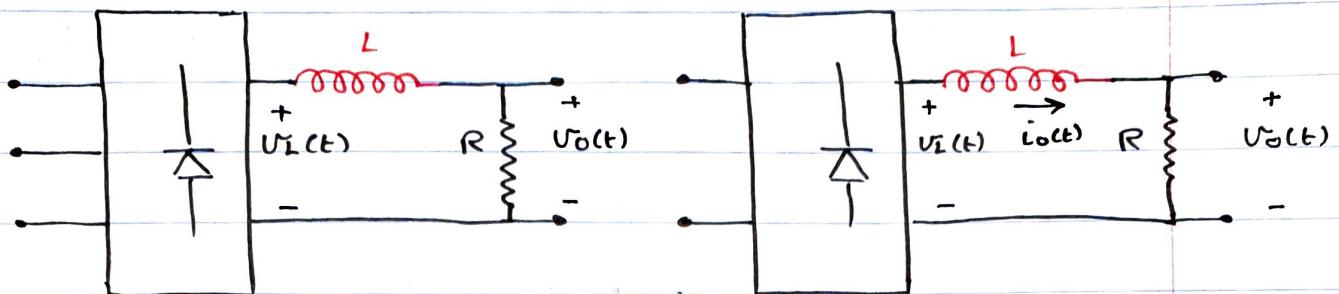

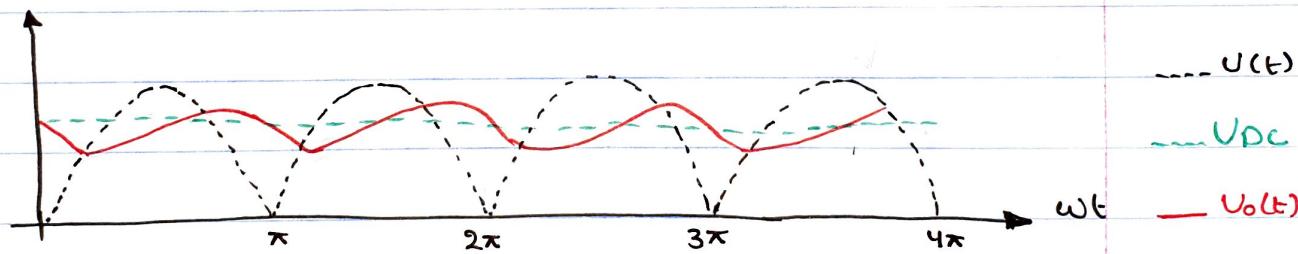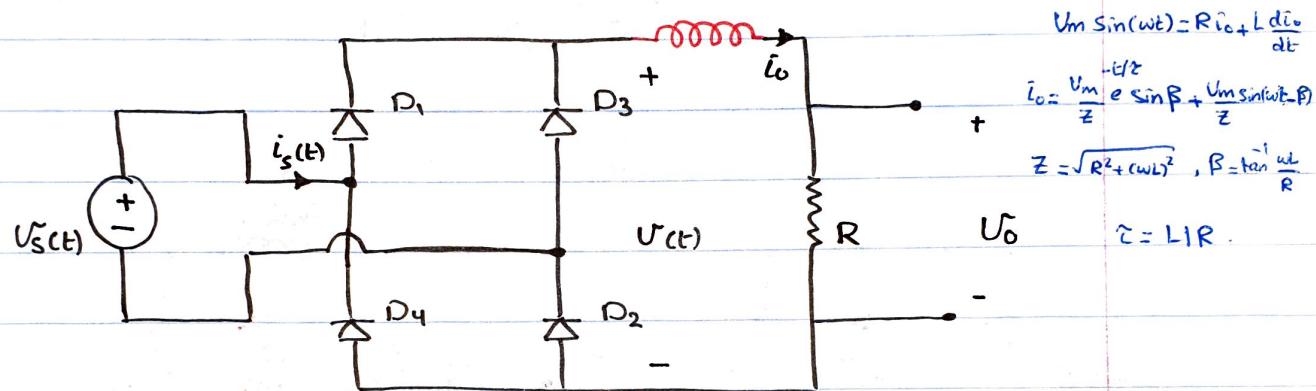Consider a 1-Φ Full-wave bridge rectifier:




$$U_o(t) = R \dot{i}_o(t)$$

$$-\dot{i}_o(t)$$


$$-\dot{i}_s(t)$$

$$wt \quad L \rightarrow \infty$$

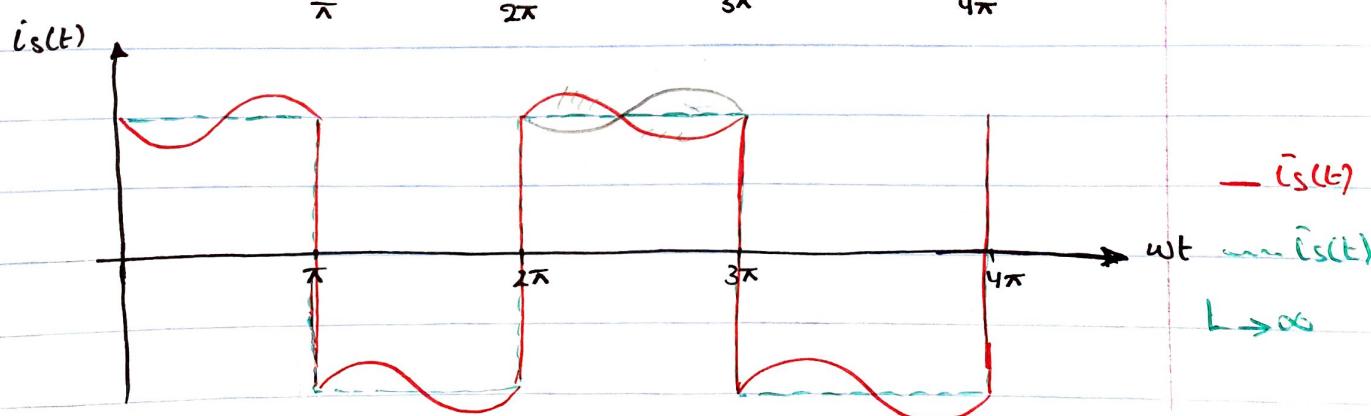


Fourier Series.
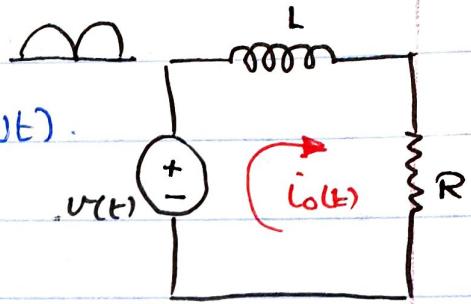
$$V(t) = \frac{2V_m}{\pi} - \sum_{n=2,4,\dots}^{\infty} \frac{4V_m}{\pi(n^2-1)} \cos(nwt)$$




Equivalent circuit for DC component:

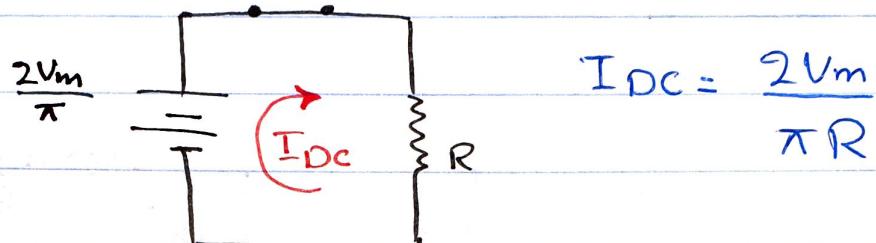

$$I_{DC} = \frac{2V_m}{\pi R}$$

Equivalent circuit for nth harmonic:

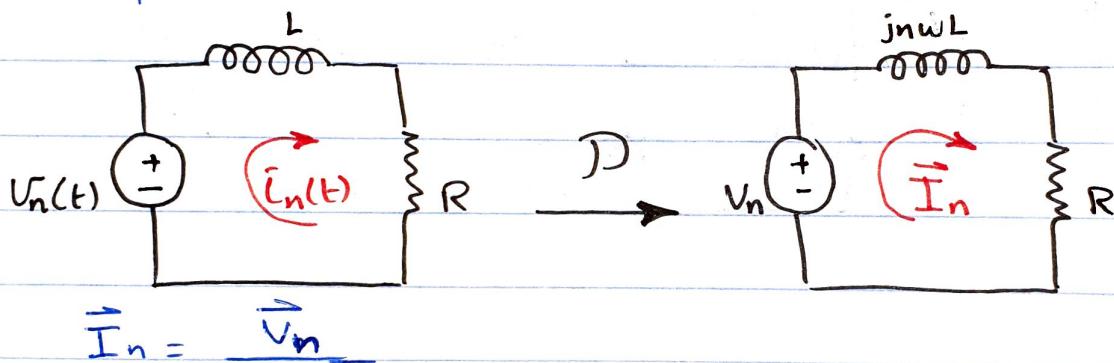

$$R + jnwL$$

$$\tilde{V}_n = \frac{4V_m}{\pi(n^2-1)} \angle 180^\circ = V_n \angle 180^\circ$$

$$\tilde{I}_n = \frac{V_n \angle 180^\circ}{\sqrt{R^2 + (nwL)^2} \left| \tan^{-1}(nwL/R) \right|}$$

$$\tilde{I}_n = \frac{V_n}{\sqrt{R^2 + (nwL)^2}} \angle 180 - \tan^{-1}(nwL/R)$$

$\downarrow P^{-1}$

$$\hat{i}_n(t) = \frac{-V_n}{\sqrt{R^2 + (nwL)^2}} \cos(nwt - \Theta_n)$$

$$\Theta_n = \tan^{-1} \left(\frac{nwL}{R} \right)$$

$$i_o(t) = I_{DC} + i_2(t) + \underbrace{i_4(t) + i_6(t) + \dots}_{\text{These harmonic are ignored, since they are attenuated compared with } i_2}$$

$$i_o(t) = I_{DC} - \frac{4V_m}{3\pi} \cdot \frac{1}{\sqrt{R^2 + (2\omega L)^2}} \cos(2\omega t), \quad I_{DC} = \frac{2V_m}{\pi R}$$

$$= I_{DC} + \hat{i}_2 \cos(2\omega t - 180^\circ)$$

The RMS value of AC Component (ripple) is;

$$I_{AC} = \frac{\hat{i}_2}{\sqrt{2}}$$

$$I_{DC} = \frac{2V_m}{\pi R}$$


Ripple Factor.

$$RF = \frac{I_{AC}}{I_{DC}} = \frac{\sqrt{2}}{3} \cdot \frac{1}{\sqrt{R^2 + (2\omega L)^2}} \cdot R$$


$$\hat{i}_2 = \frac{4V_m}{3\pi} \left(\frac{1}{2\omega L_f} \right)$$

3. LC-type.

3-Φ AC Source.

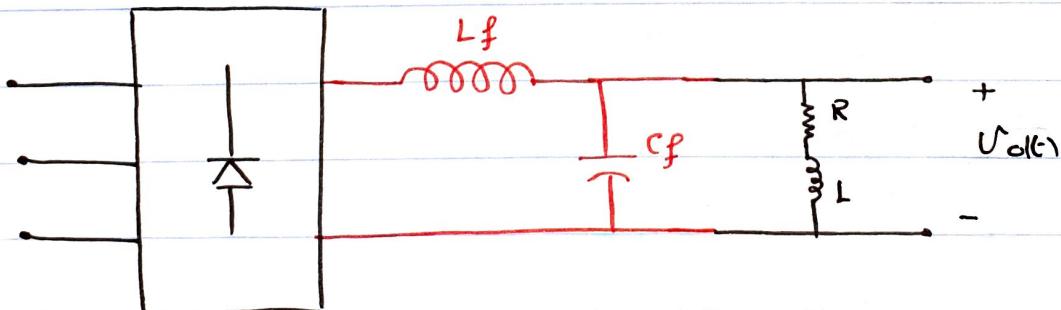

1-Φ AC Source.

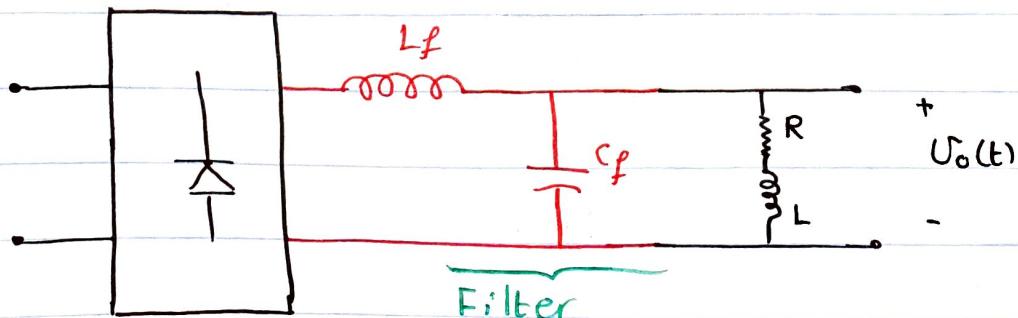


- The Following Condition must be satisfied to pass the n^{th} harmonic Current through the Capacitor.

$$\sqrt{R^2 + (nwL)^2} \gg \frac{1}{nwC_f}$$

$$\sqrt{R^2 + (nwL)^2} = \frac{10}{nwC_f} \Rightarrow C_f = \frac{10}{nw\sqrt{R^2 + (nwL)^2}}$$

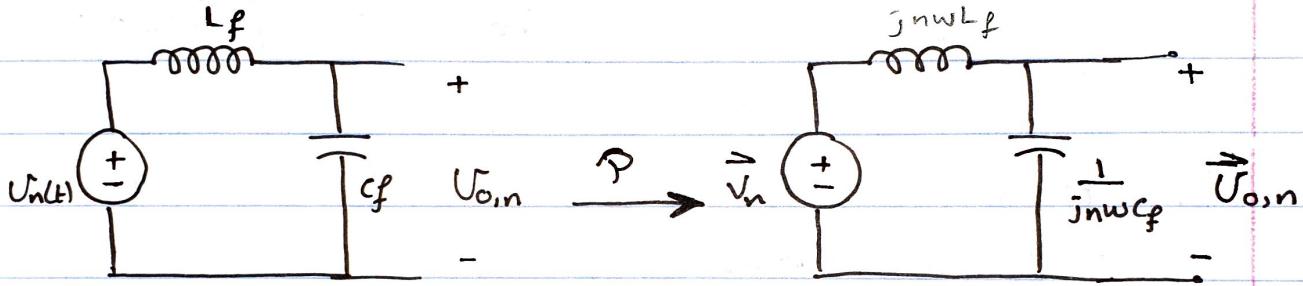- Applying Superposition, the equivalent circuit for the n^{th} harmonic is :



$$\vec{U}_{0,n} = \frac{1/jnwC_f}{\frac{1}{jnwC_f} + jnwL_f} \cdot \vec{V}_n$$

$$\vec{V}_{0,n} = \frac{1}{1 - (nw)^2 C_f L_f} \vec{V}_n$$

Consider a 1-Φ Full-wave rectifier.

$$U(t) = \frac{2V_m}{\pi} - \sum_{n=2,4,6}^{\infty} \frac{4V_m}{\pi(n^2-1)} \cos(nwt).$$

$$U(t) = V_{DC} + V_2 + V_4 + V_6 + \underbrace{V_8 + \dots}_{\text{ignored.}}$$

$$U(t) = \underbrace{\frac{2V_m}{V_{DC}}}_{\pi} - \frac{4V_m}{3\pi} \cos(2wt).$$

$$\vec{V}_2 = -\frac{4V_m}{3\pi} \vec{L}_0$$

$$V_{0,2} = \frac{4Vm}{3\pi} \cdot \frac{1}{(2\omega)^2 L_f C_f - 1}$$

$$\Rightarrow V_{AC} = \frac{V_{0,2}}{\sqrt{2}}$$

$$V_{DC} = \frac{2Vm}{\pi}$$


$$RF = \frac{\sqrt{2}}{3} \cdot \frac{1}{(2\omega)^2 L_f C_f - 1}$$

- Example:

A LC Filter is used to reduce the ripple Content of the output voltage for a 1-φ Full-wave rectifier. The load resistance, $R = 40\Omega$, load inductance, $L = 10\text{ mH}$, and the source frequency is 60 Hz.

Determine the values of L_f & C_f so that the ripple Factor of the output voltage is 10% ?
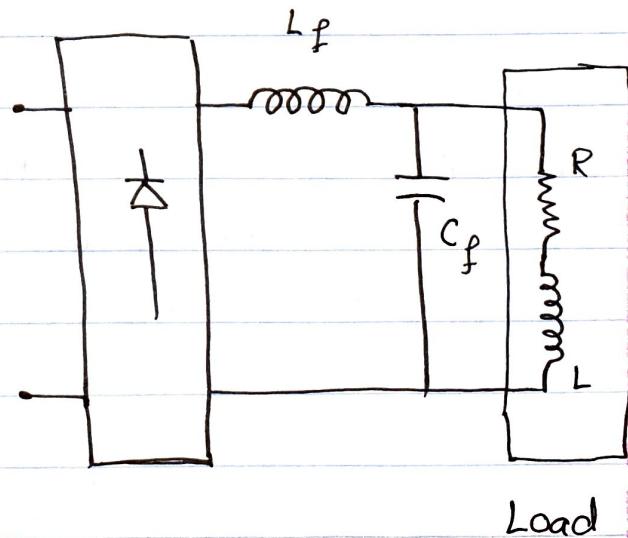
$$\sqrt{R^2 + (n\omega L)^2} = \frac{10}{n\omega C_f}$$



- Consider the domain harmonic ($n=2$) .

$$\sqrt{40^2 + (2(2\pi \times 60))(10 \times 10^{-3})} = \frac{10}{2(2\pi)(60)C_f}$$

Solve for C_f ;

$$C_f = 426 \mu F$$

$$\vec{V}_{o2} = \frac{1/j\omega C_F}{1/j\omega C_F + j\omega L_F} \cdot \left(-\frac{4V_m}{3\pi} \right) 10$$

$$V_{o2} = \frac{4V_m}{3\pi} \left(\frac{1}{(2\omega)^2 L_F (\varphi - 1)} \right)$$

$$V_{AC} = \frac{4V_m}{\sqrt{2}(3\pi)} \frac{1}{4\omega^2 L_F (\varphi - 1)}$$

$$RF = \frac{V_{AC}}{V_{DC}} ; V_{DC} = \frac{2V_m}{\pi}$$

$$RF = \frac{2}{\sqrt{2}(3)} \frac{1}{(4\omega^2 L_F (\varphi - 1))} = 0.1 ; \omega^2 = (2\pi f_0)^2$$

$$C_F = 4.26 \times 10^{-6}$$

$$L_F = 30.83 \text{ mH.}$$

$$RF = \frac{1}{\sqrt{2}(2Rf_r C_F - 1)} ; f_r = 2 \times 60$$


$$R = 40.$$

$$C_F = 840.7 \mu F.$$

- Example:

An output of 5V at 1A is required, the regulator type is LM317 M and is supplied through a 1-Φ Full wave bridge rectifier Fed from 10V rms @ 50 Hz transformer, secondary. The voltage drop across the regulator must be at least 1.8V. Assuming the diode's voltage drop is 1V.

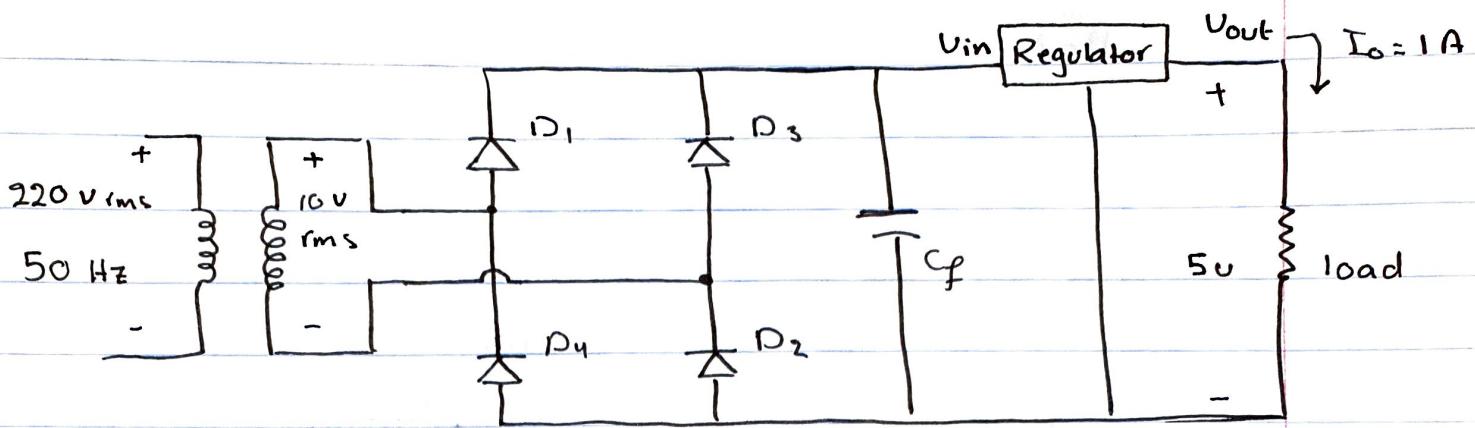1. What size of smoothing capacitor is required.



$$\Delta V_{in} = V_{max} - V_{min}$$

$$V_{max} = 10\sqrt{2} - 2 = 12.14 \text{ V}$$

Voltage drop across two conducting diode.

$$V_{min} = 5 + 1.8 = 6.8 \text{ V}$$

$$\Delta V_{in} = 12.14 - 6.8 = 5.34 \text{ V}$$

$$\Delta V_{in} = \frac{I}{F_C C_F}$$

$$5.34 = \frac{1}{2(50)C_F} \Rightarrow C_F = 1.873 \text{ mF}$$

$$2 \quad P_{loss} = P_{in} - P_{out}$$

$$= \bar{V}_{in}I - \bar{V}_{out}I$$

$$\bar{V}_{in} = V_{max} - \frac{\Delta V_{in}}{2} = 12.14 - \frac{5.34}{2}$$

$$\bar{V}_{in} = 9.47 \text{ V}$$

$$P_{loss} = 9.47(1) - 5(1) = 4.47 \text{ W}$$

3- IF the RRR is 65 dB, then calculate the ripple of the output voltage.

$$20 \log_{10} * = \text{dB}$$

$$\frac{(dB/20)}{10} = x$$


$$RRR = 65 = 20 \log \frac{\Delta V_{in}}{\Delta V_{out}}, \Delta V_{in} = 5.34$$

$$\Delta V_{out} = 3 \text{ mV}$$


- Controlled AC-DC Converters (Controlled Rectifiers).

Silicon Controlled Rectifiers (SCRs)

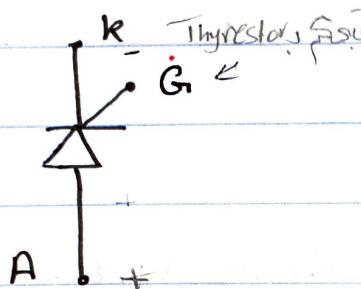A thyristor is a 4 layer semiconductor device of PNPN structure with 3 Pn-junctions.



Symbol of thyristor.

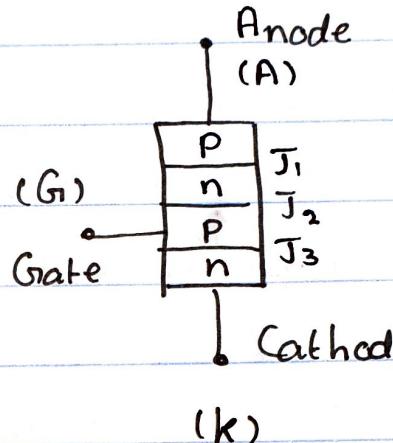


- When V_{AK} is positive $\rightarrow J_1, J_3$ are forward biased.
& J_2 is reversed biased.
 \rightarrow Small leakage current flows.
 \rightarrow Forward blocking or off-state.
- When $V_{AK} > V_{FB}$, where V_{FB} is the forward breakdown voltage. $\rightarrow J_2$ breaks.
 \rightarrow large forward anode current, I_A flows.
 \rightarrow Conducting mode or on-state.

• Note:



- The forward current is limited by an external resistance or impedance.
- In the conducting mode, there will be a small voltage drop due to the ohmic drop of the layers (typically 1V).

i-v characteristic
of thyristor.

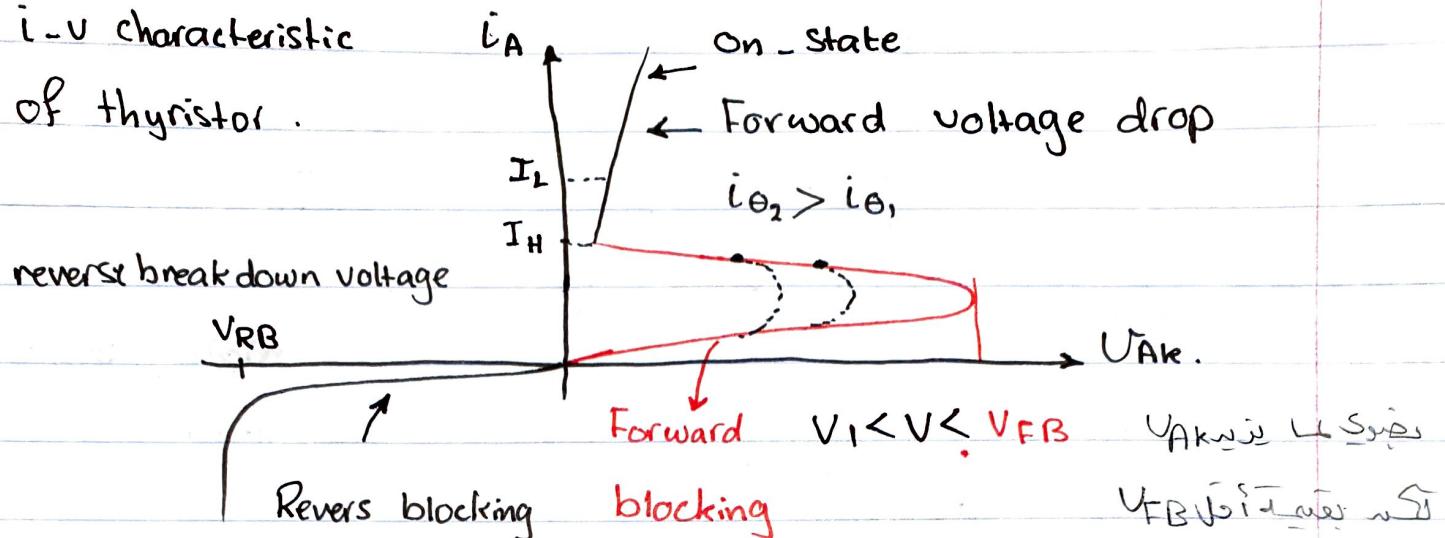


- Turn-On.
- The thyristor can be turned on by increasing U_{Ak} beyond V_{FB} , such a turn on may damage the thyristor.
- In practice, the thyristor is turned on by applying a positive voltage between the gate and cathode.
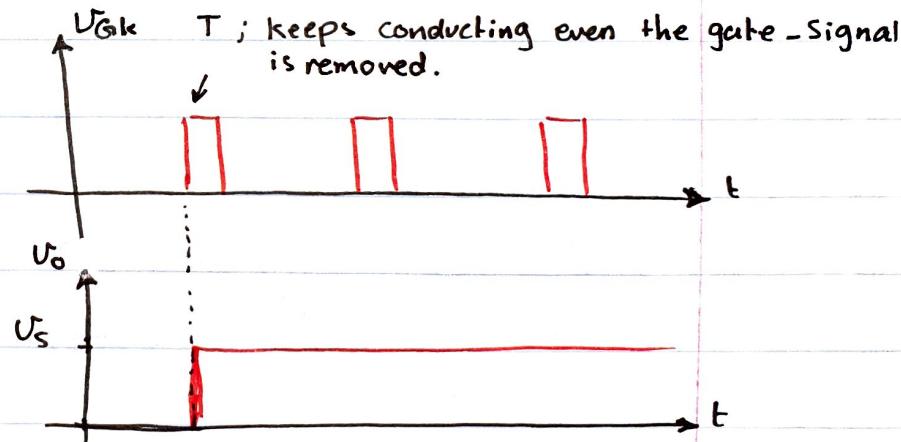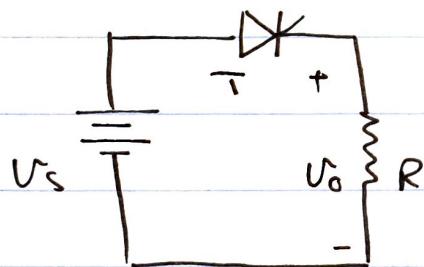
$$U_{Gk} \approx 3-5 \text{ @ } 0.1-0.3 \text{ A for } 6 \text{ kA device.}$$



- Turn off.
- The thyristor can not be turned off via its gate signal.
- To turn it off, I_A has to fall below I_H .
- In AC Circuits, the thyristor is turned off by self-commutation (self-turned-off).
- In the rectifiers & inverters, the thyristors are turned off by line or load commutations.

Resonant Commutation Circuit.

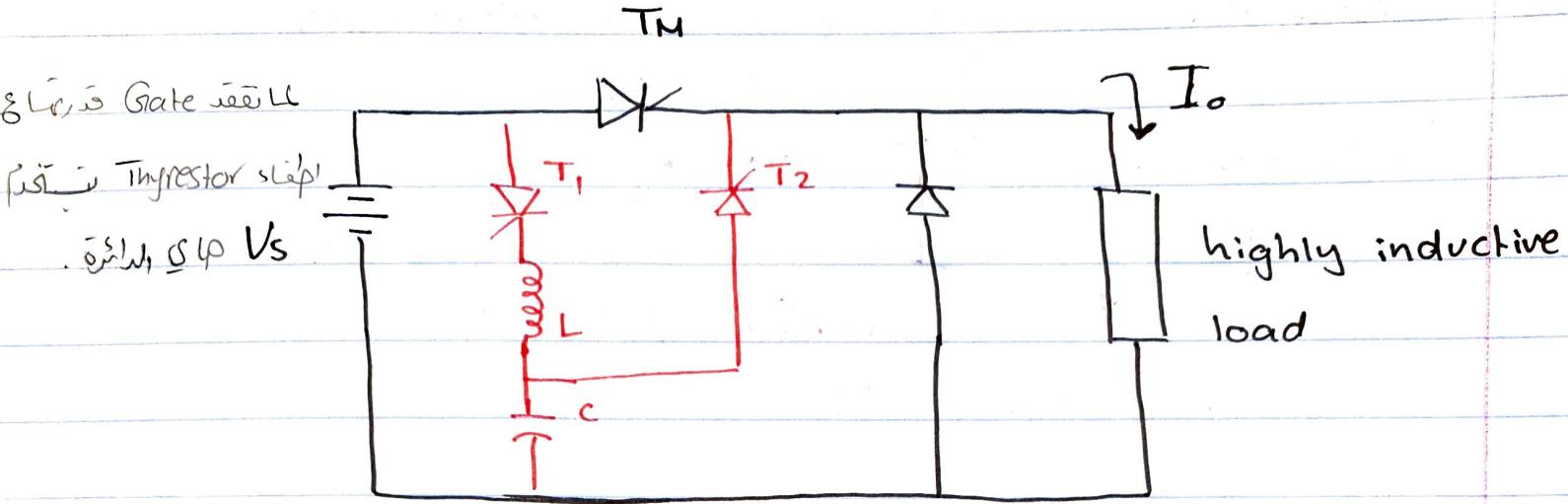

- Assume T_M is triggered at $t = t_1$.
- When T_1 is turned on at $t = t_2 > t_1$, a resonant circuit is formed.
- Applying KVL.

$$V_s = L \frac{di}{dt} + \frac{1}{C} \int i dt \Rightarrow \frac{d^2i}{dt^2} + \frac{1}{LC} i = 0.$$

$$i(t) = A \sin(\omega_0(t - t_2)) + B \cos \omega_0 (t - t_2)$$

$$i(t_2) = B = 0.$$

$$i(t) = A \sin (\omega_0 (t - t_2))$$

$$\frac{di(t_2)}{dt} = \frac{1}{L} (V_s - V_c(t_2)) = \omega_0 A.$$

$$A = \frac{V_s}{\omega_0 L}$$


$$i(t) = \frac{V_s}{\omega_0 L} \sin (\omega_0 (t - t_2)).$$

$$V_c = V_s - L \frac{di(t)}{dt}$$

$$V_c = V_s (1 - \cos \omega_0 (t - t_2))$$

- Resonant Commutation Circuit.

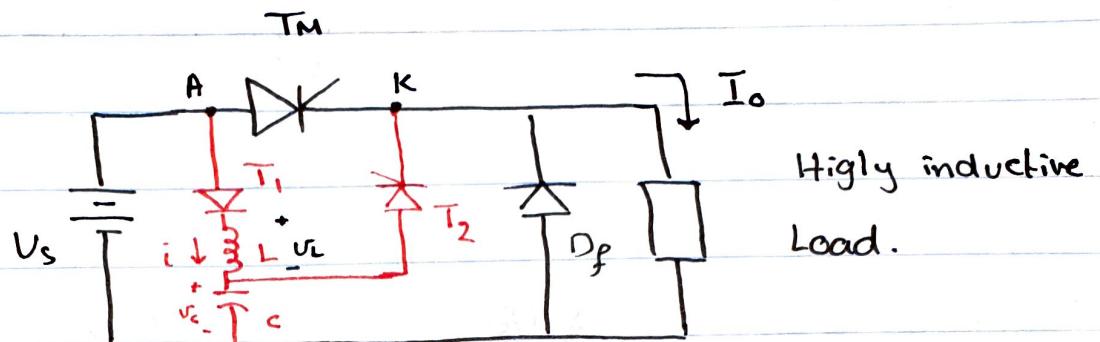It is used to turn off the Thyristor DC circuit.



- Assume that T_M is triggered at $t = t_1$.
- When T_1 is turned on at $t = t_2 > t_1$, a resonant circuit is formed.
- KVL in the circuit.

$$\text{माना } U_s = L \frac{di}{dt} + \frac{1}{C} \int i dt \Rightarrow \frac{d^2i}{dt^2} + \frac{1}{LC} i = 0. \quad \downarrow \text{लेखा करने पर}$$

$t = t_2$ तक

$$i(t) = A \sin(\omega_0(t - t_2)) + B \cos(\omega_0(t - t_2)).$$

$$i(t_2) = 0$$

$$\frac{di(t_2)}{dt} = \frac{1}{L} (U_s - V_c(t_2)) = \frac{U_s}{L} = \omega_0 A \Rightarrow A = \frac{U_s}{\omega_0 L}.$$

$$i(t) = \frac{U_s}{\omega_0 L} \sin(\omega_0(t - t_2)).$$

- When; $t = t_2 + \frac{\pi}{\omega_0} \Rightarrow i = 0 \Rightarrow T_1$ is turned off.

$$V_c = U_s - L \frac{di}{dt} = U_s (1 - \cos(\omega_0(t - t_2))).$$


- When; $t = t_2 + \frac{\pi}{\omega_0} \Rightarrow V_c = 2U_s$.

The Thyristor T_M is turned off when T_2 is turned on at $t = t_2$.

$$V_A = U_s, V_K = 2U_s \Rightarrow V_{AK} = -U_s \Rightarrow T_M \text{ is off.}$$

- The capacitor is selected according to:



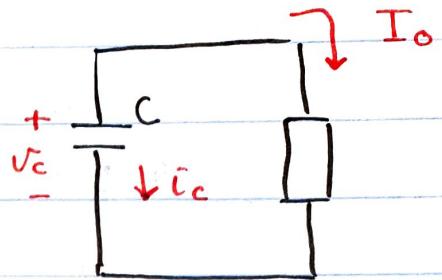
$$i_c = C \frac{\Delta U_c}{\Delta t} = -I_0$$



$\Delta t \geq t_q$ (turn-off time of the thyristor T_M).



$$|\Delta U_c| = C U_s - U_{k, \text{final}}, U_{k, \text{final}} \geq U_s, |\Delta U_c| \leq U_s.$$

$U_{gk, TH}$

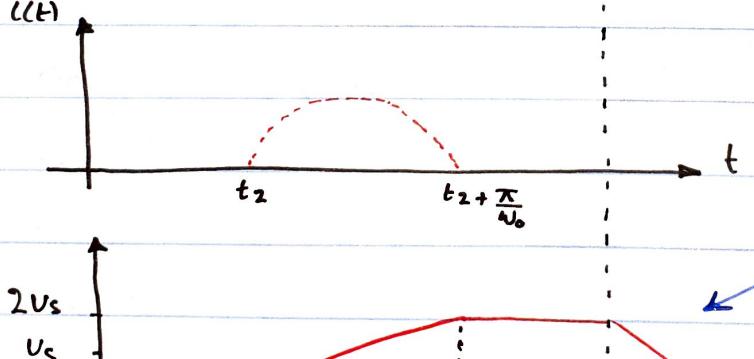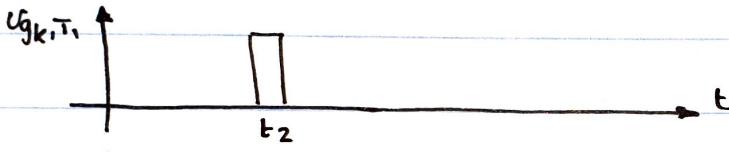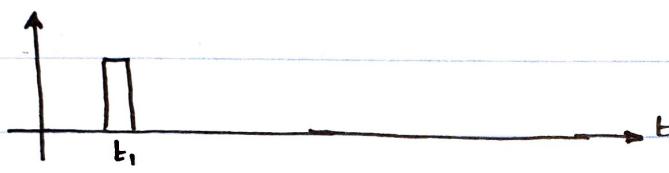


$$\begin{aligned} -I_0 &= C \frac{dU}{dt} \\ -\frac{I_0}{C} \int_{t_3}^t dt &= \int dU_c \\ \frac{U_c}{2U_s} &= \frac{t - t_3}{C} \end{aligned}$$

$$U_c = 2U_s - \frac{I_0}{C}(t - t_3)$$

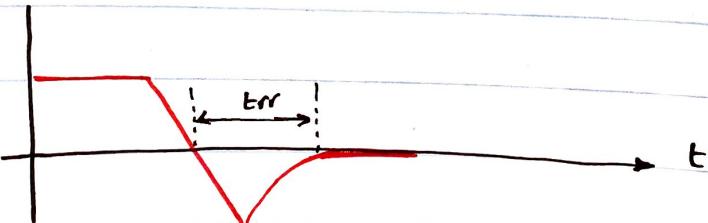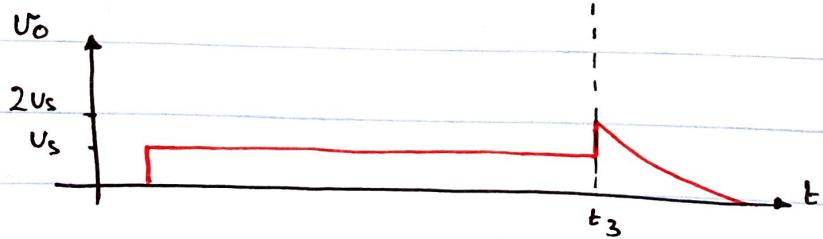


Controlled Rectifiers.

1. 1-Φ Half-wave Controlled Rectifier.

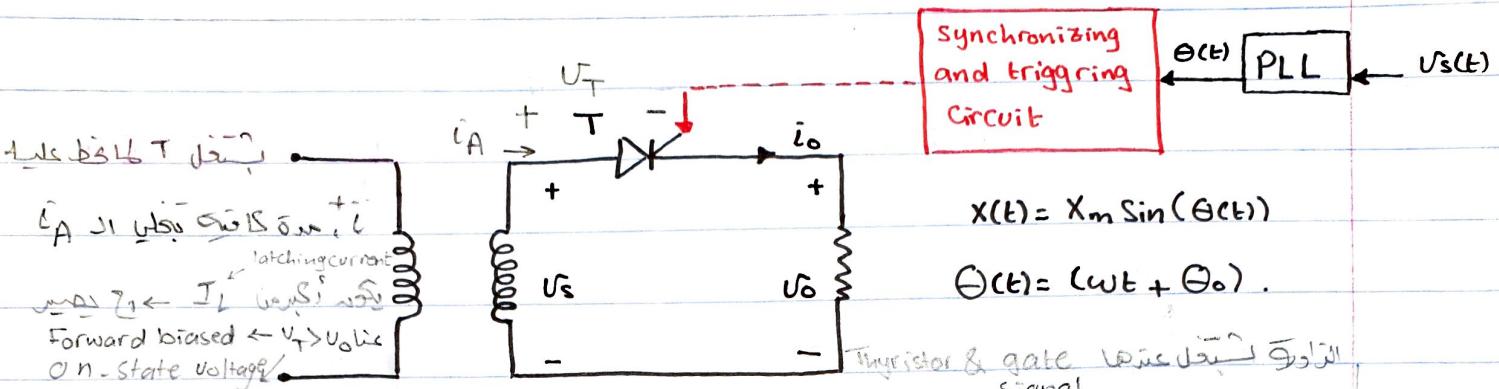

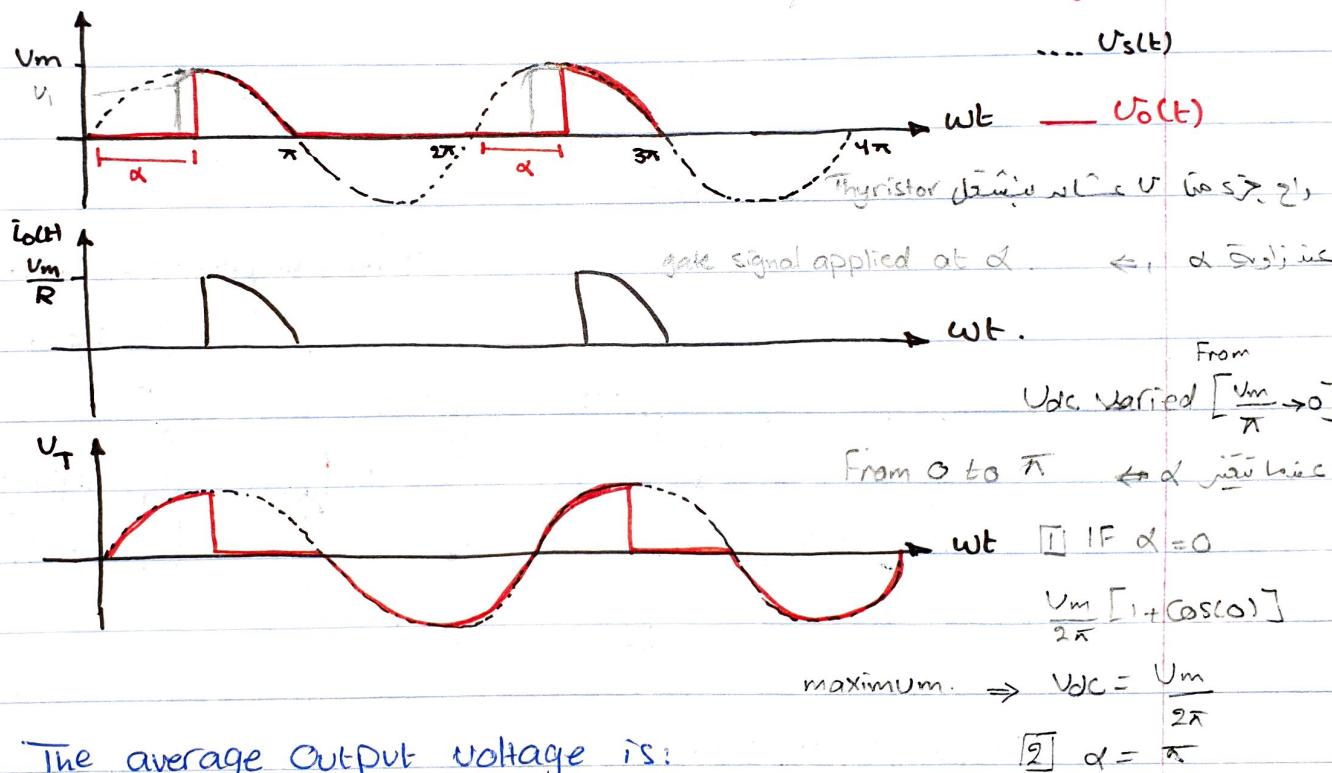Assume that $V_S(t) = V_m \sin(\omega t)$.



The average Output Voltage is:

$$U_{DC} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d(\omega t), \quad 0 \leq \alpha \leq \pi$$

$$U_{DC} = \frac{V_m}{2\pi} \left[\cos(\omega t) \right]_{\alpha}^{\pi}$$

$$U_{DC} = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

- Normalized Output Voltage

$$U_n = \frac{U_{DC}}{V_m} = 0.5(1 + \cos \alpha)$$

$$- i_{DC} = \frac{U_{DC}}{R}$$

$$- PIV = V_m$$

- The RMS value of $V_o(t)$

$$V_{\text{RMS}} = \sqrt{\frac{1}{2\pi} \int_{-\alpha}^{\pi} V_m^2 \sin^2(\omega t) d(\omega t)}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_{-\alpha}^{\pi} \frac{1}{2} (1 - \cos(2\omega t)) d\omega t} = \frac{V_m}{2} \sqrt{\frac{1}{\pi} (\pi - \alpha + \frac{\sin 2\alpha}{2})}$$

I_{DC}

$0 < \alpha < \pi$


This Converter has only one

quadrant of operation.

Output voltage & current have One polarity.


2- 1-Φ Semi-Convarstor.

It used to produce the conduction losses

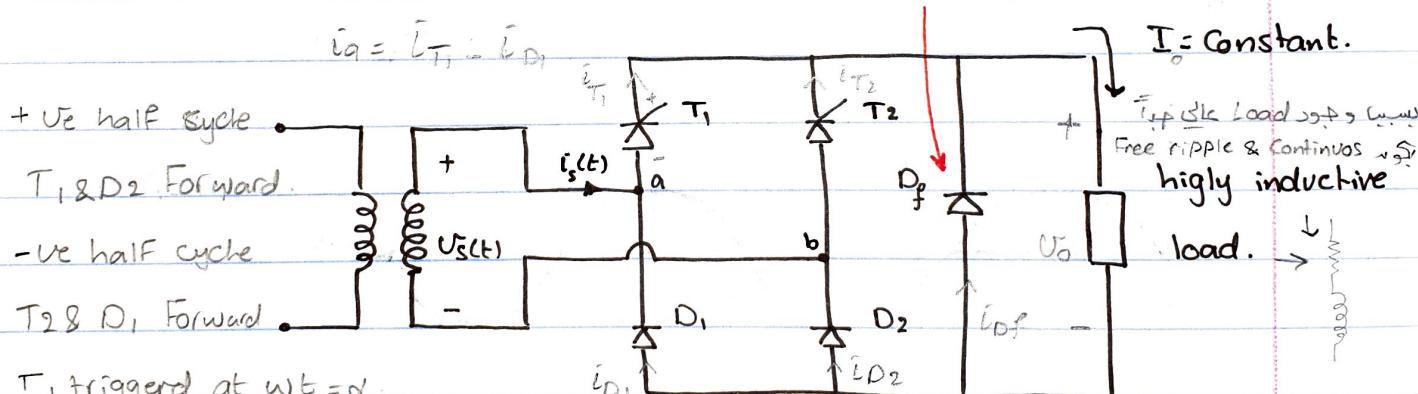

$$\alpha < \omega t < \pi \quad U_s(t) = V_m \sin(\omega t) \quad 0 \text{ to } \alpha \text{ & } \pi \text{ to } \pi + \alpha \approx \text{constant}$$

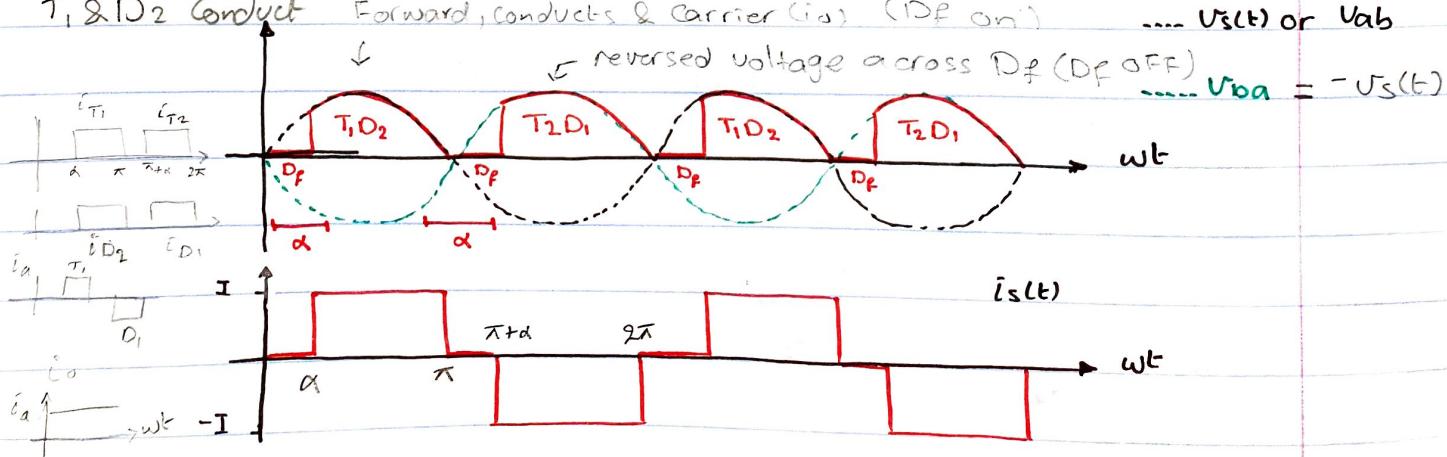T₁ & D₂ Conduct Forward, conducts & carrier (i_s) (D_f on) ---- U_{s(t)} or U_{ab}



- The average output voltage is:

$$V_{DC} = \frac{2}{2\pi} \int_0^{\pi} V_m \sin(\omega t) d(\omega t)$$

$$V_{DC} = \frac{V_m}{\pi} (1 + \cos \alpha); \quad 0 \leq \alpha \leq \pi.$$

- The RMS value of $V_o(t)$:


$$V_{RMS} = \sqrt{\frac{2}{2\pi} \int_0^{\pi} V_m^2 \sin^2(\omega t) d(\omega t)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} (\pi - \alpha + \frac{\sin 2\alpha}{2})}$$

- The Converter has 1-quadrant of operation.




$$\text{Normalized } V_o \Rightarrow V_n = \frac{U_{DC}}{V_m} = 0.5(1 + \cos \alpha).$$

3- 1-Φ Full wave Converter.

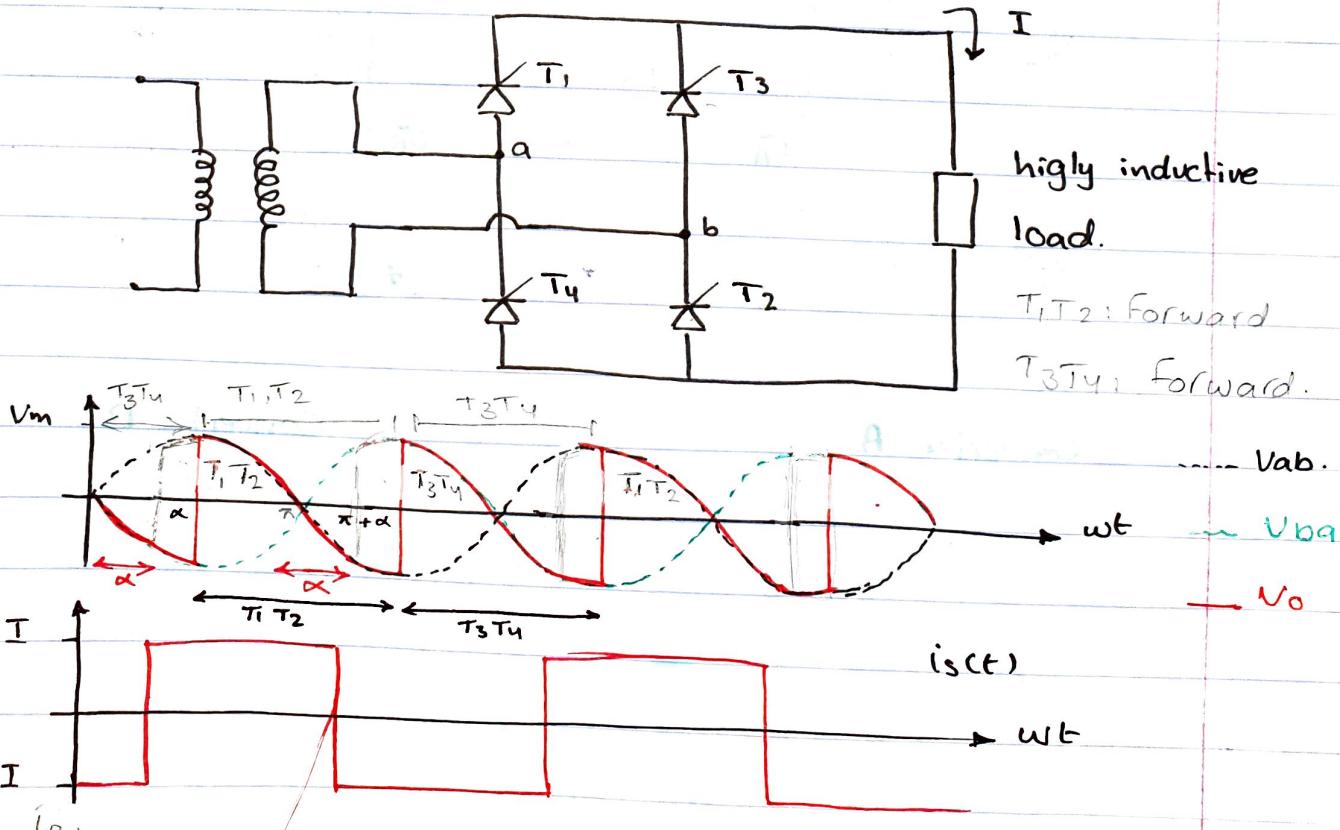

- The average Output Voltage is:
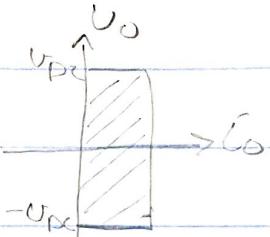
$$V_{DC} = \frac{2}{2\pi} \int_{-\alpha}^{\pi+\alpha} U_m \sin(\omega t) d(\omega t)$$



U_o both polarity + U_C & - U_C

$$U_{DC} = \frac{U_m}{\pi} |\cos \omega t| = \frac{U_m}{\pi} (\cos \alpha - \cos(\pi + \alpha)) \quad 2 \text{ quadrants}$$

$$U_{DC} = \frac{2U_m}{\pi} \cos \alpha. \quad 0 < \alpha < \pi$$


- The average RMS value of U_{AC} :

→ $T_1, T_2 \rightarrow$ still conducting beyond $\omega t = \pi$

$U_{RMS} = \frac{U_m}{\sqrt{2}}$, even though the input voltage is negative
because their anode current are higher

than the holding current.

4- 1-Φ Dual Converter.

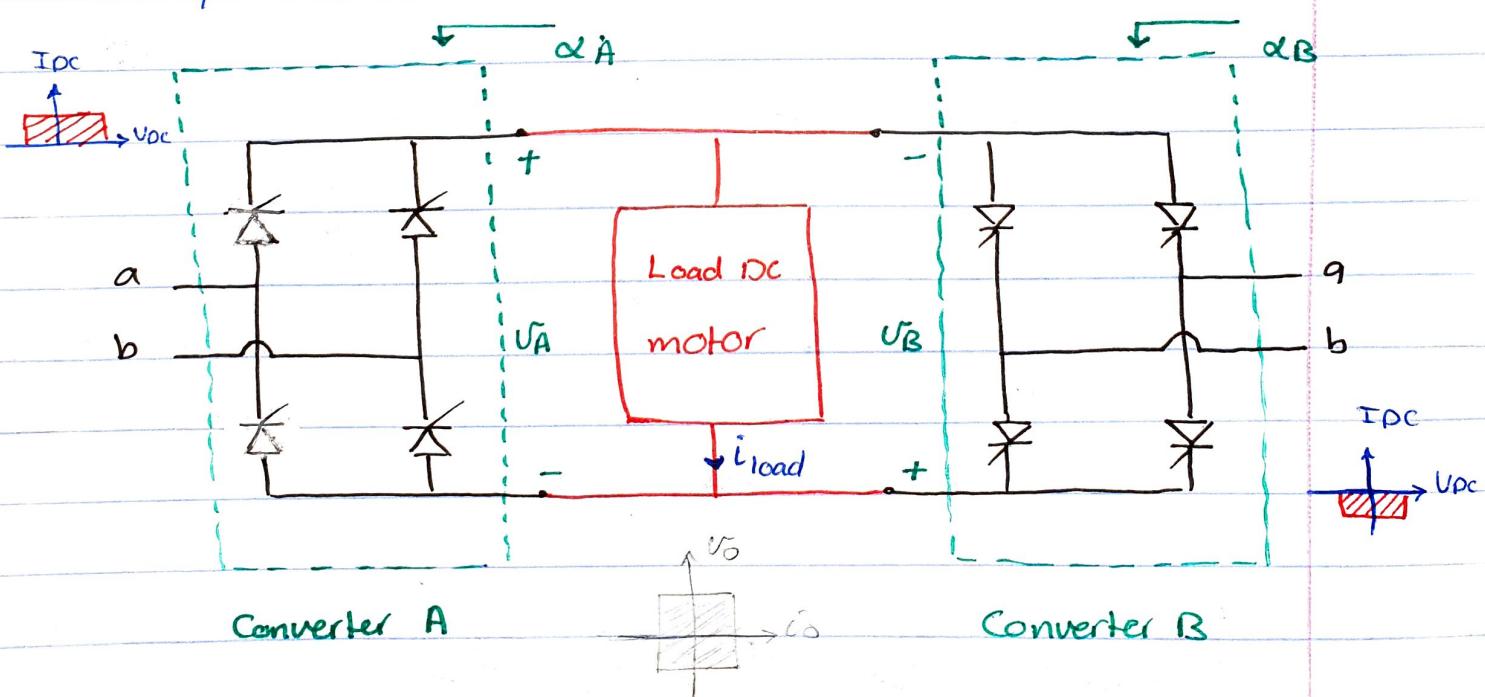

- Two full-wave Converters connected in back-to-back or in Outi-parallel to obtain the 4 quadrant operation.
- The Converter is Controlled Using the Change-Over logic.

$i_{load} > 0$ $v_{load} > 0$ Converter A Converter B $Q \leftarrow \text{مخرج}$


Yes	Yes	ON	OFF	I
Yes	No	ON	OFF	II
No	Yes	OFF	ON	IV
No	No	OFF	ON	III

KVL :

$$V_{A,DC} + V_{B,DC} = 0$$

$$V_{A,DC} = -V_{B,DC}$$

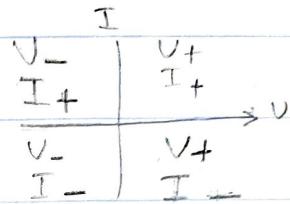
$$\frac{2V_m}{\pi} \cos \alpha_A = - \frac{2V_m}{\pi} \cos \alpha_B$$




$$\cos \alpha_A = -\cos \alpha_B = \cos(\pi - \alpha_B)$$

$$\alpha_A + \alpha_B = \pi$$

5- 3-Φ Half-wave Converter.

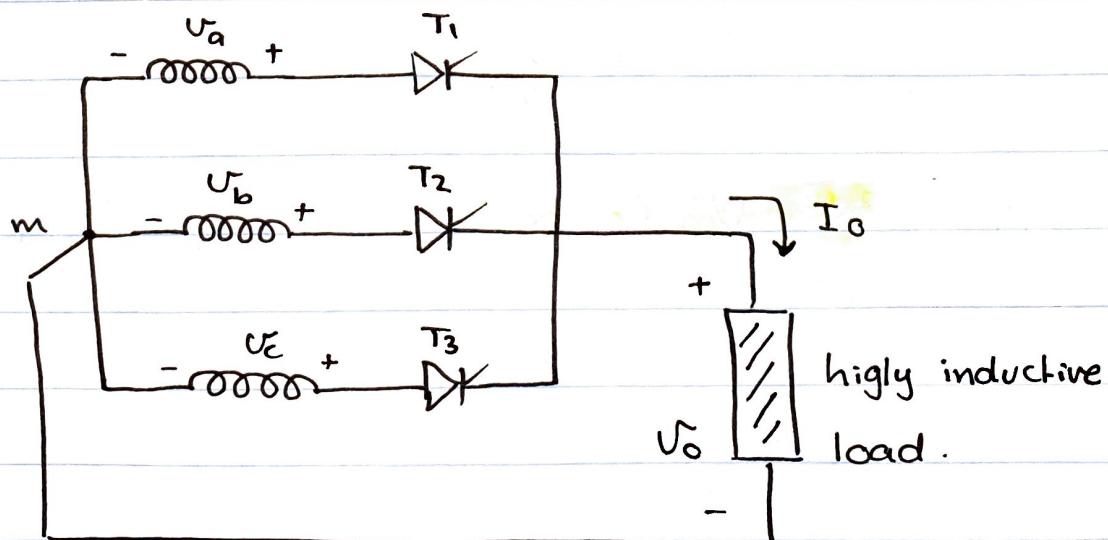

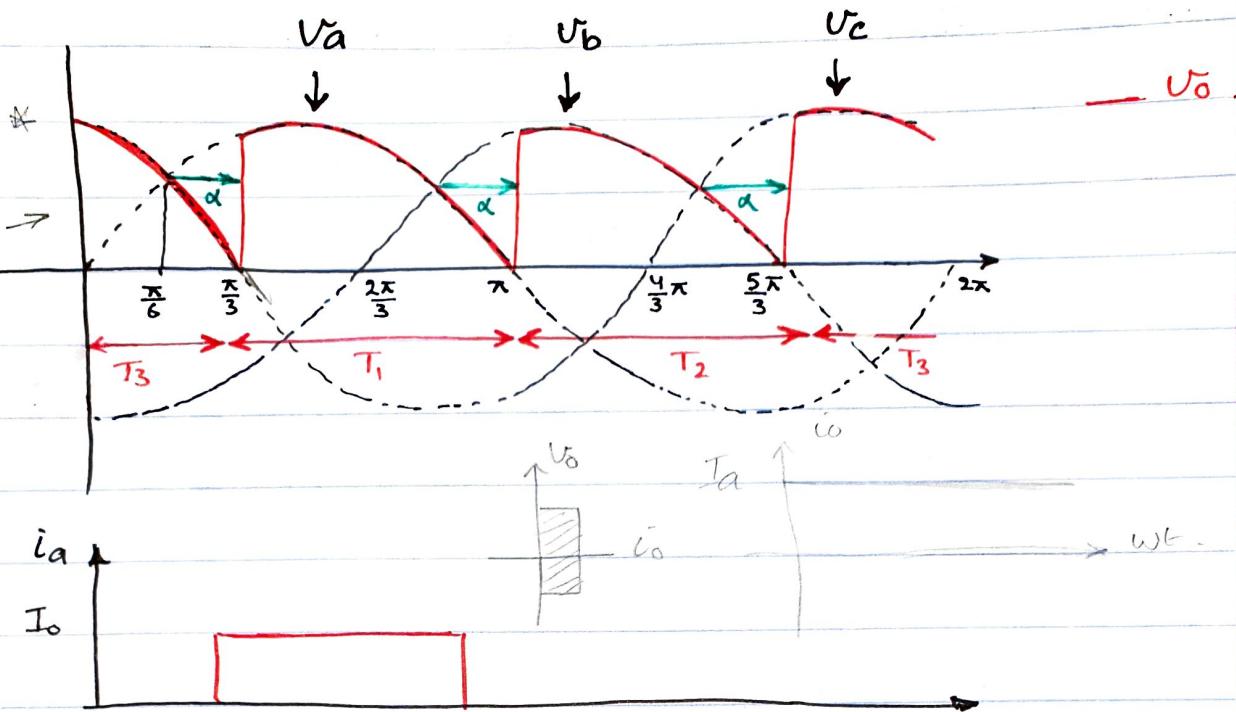

- The average output voltage.

$$V_{DC} = \frac{3}{2\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha} V_m \sin(\omega t) d\omega t$$

$$V_{DC} = \frac{q}{n} V_m \sin\left(\frac{\pi}{q}\right)$$

with $\Rightarrow q = 3$!

$$\begin{aligned} V_{DC} &= \frac{3V_m}{2\pi} \left[\cos\left(\frac{\pi}{6} + \alpha\right) - \cos\left(\frac{5\pi}{6} + \alpha\right) \right] \\ &= \frac{3V_m}{2\pi} \left[\frac{\sqrt{3}}{2} \cos\alpha - \frac{1}{2} \sin\alpha - \left(\frac{\sqrt{3}}{2} \cos\alpha - \frac{1}{2} \sin\alpha \right) \right] \end{aligned}$$

$$V_{DC} = \frac{3\sqrt{3}}{2\pi} V_m \cos\alpha ; \quad 0 \leq \alpha \leq \pi, \text{ highly inductive}$$

$$0 \leq \alpha \leq \frac{\pi}{6}, \text{ purely resistive.}$$

- The RMS value of output voltage.


$$V_{RMS} = \sqrt{\frac{3}{2\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha} V_m^2 \sin^2(\omega t) d(\omega t)} , \quad \sin^2 x = \frac{1}{2} [1 - \cos 2x].$$

$$V_o(\max) \text{ at } \alpha = 0 \Rightarrow V_{dm} = \frac{3\sqrt{3}}{2\pi} V_m$$

$$V_n = \frac{V_{dc}}{V_{dm}} = \cos\alpha.$$

$$V_{rms} = \sqrt{3} V_m \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha}$$

Purely resistive

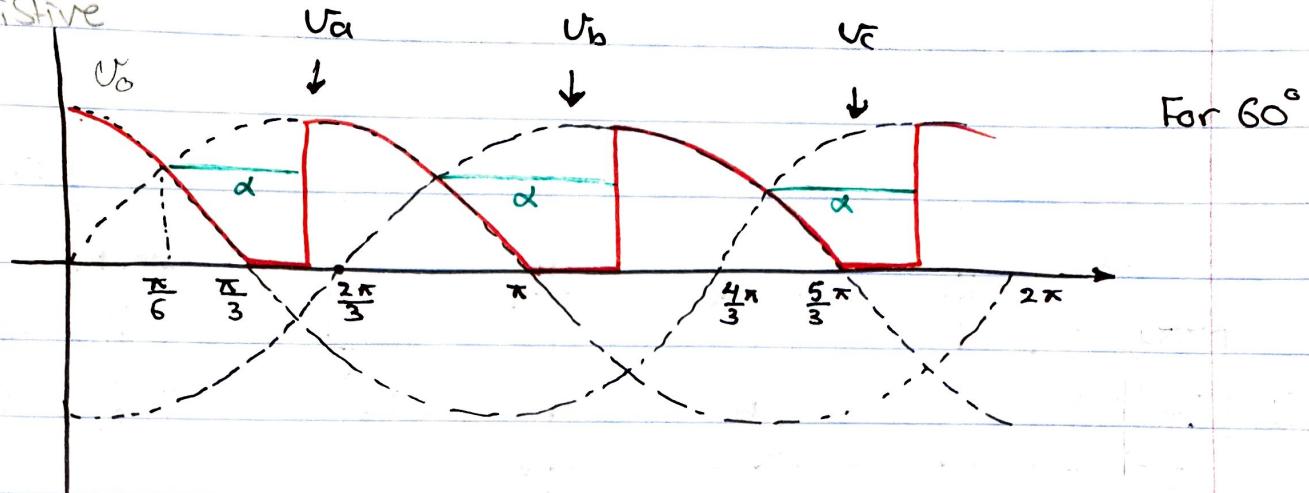

- The average output voltage.

$$U_{DC} = \frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\pi} U_m \sin(\omega t) d\omega t = \frac{3U_m}{2\pi} [\cos(\frac{\pi}{6} + \alpha) + 1]$$

Purely resistive load, $\frac{\pi}{6} \leq \alpha \leq \pi$

- The RMS value of $U_o(t)$.

$$U_{RMS} = \sqrt{\frac{3}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\pi} U_m^2 \sin^2(\omega t) d\omega t} = \sqrt{3} U_m \sqrt{\frac{5}{24} - \frac{\alpha}{4\pi} + \frac{1}{8\pi} \sin(\frac{\pi}{3} + 2\alpha)}$$

- Note:

When the load is purely resistive, and $\alpha \geq \frac{\pi}{6}$, $U_o(t)$ can never have negative parts.

6. 3-Φ Semi-Converter



$$V_{an} = V_m \sin \omega t$$

$$V_{en} = V_m \sin(\omega t + \frac{2\pi}{3})$$

I_{DC}


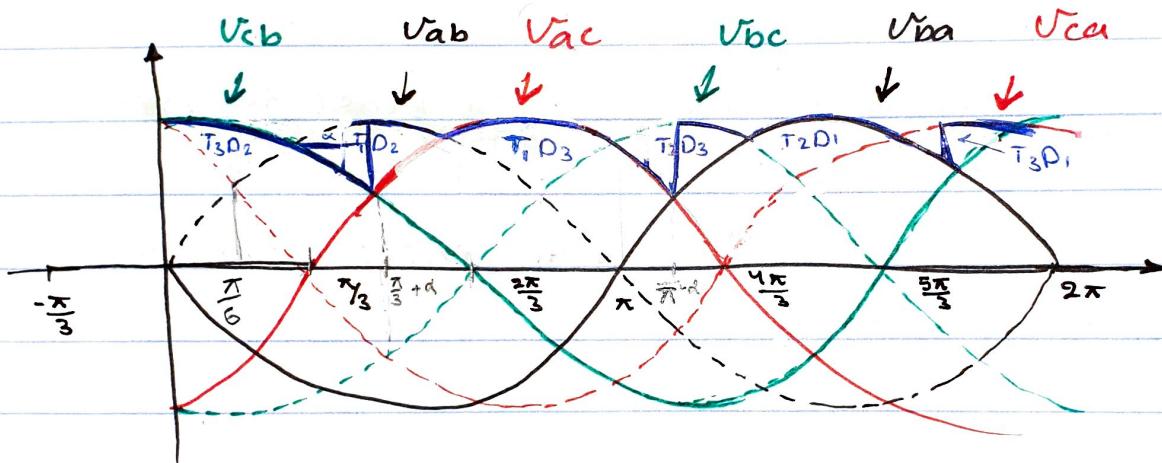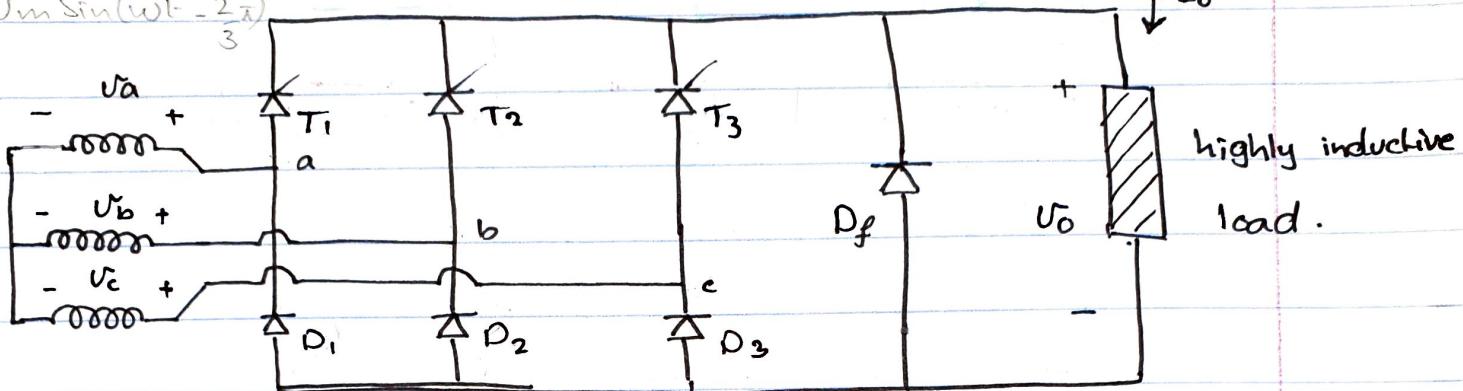
$$V_{bn} = V_m \sin(\omega t - \frac{2\pi}{3})$$



Mode (I)

$$0 \leq \alpha \leq \frac{\pi}{3} \quad V_{DC} = \frac{3}{2\pi} \left[\int_{\frac{\pi}{3}+\alpha}^{\frac{2\pi}{3}} V_{ab} d(\omega t) + \int_{\frac{2\pi}{3}}^{\pi+\alpha} V_{ac} d(\omega t) \right]$$


$$V_{ab} = \sqrt{3} V_m \sin(\omega t)$$

$$V_{ac} = -\sqrt{3} V_m \sin(\omega t + 120^\circ)$$

$$V_{DC} = \frac{3\sqrt{2}}{2\pi} V_m (1 + \cos \alpha)$$

$$VRMS = \sqrt{\frac{3}{2\pi} \int_{\frac{\pi}{3}+\alpha}^{\frac{2\pi}{3}} (V_{ab})^2 d(\omega t) + \int_{\frac{2\pi}{3}}^{\pi+\alpha} (V_{ac})^2 d(\omega t)}$$
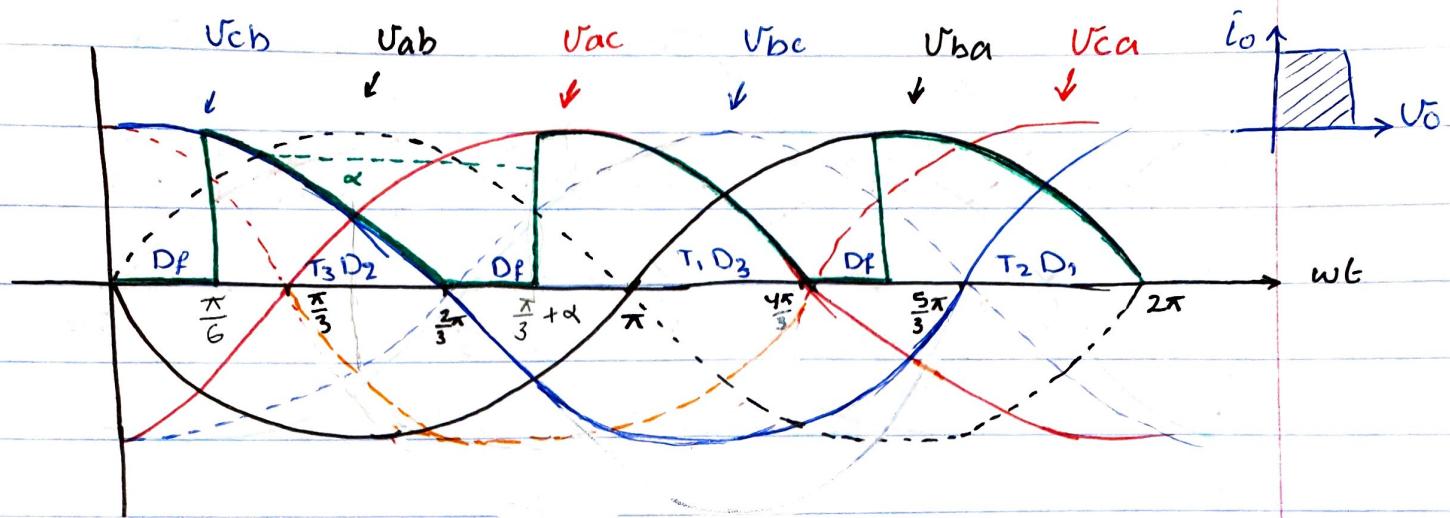
$$VRMS = \sqrt{3} V_m \sqrt{\frac{3}{4\pi} \left(\frac{2\pi}{3} + \sqrt{3} (\cos \alpha)^2 \right)}$$





Mode (II) : $\frac{\pi}{3} \leq \alpha \leq \pi$.

$$U_{DC} = \frac{3}{2\pi} \int_{\frac{\pi}{3}+\alpha}^{\frac{4\pi}{3}} V_{ac} d(wt) = \frac{3\sqrt{3}}{2\pi} (1 + \cos \alpha) = U_{DC}_{(I)}$$

$$V_{RMS} = \sqrt{\frac{3}{2\pi} \int_{\frac{\pi}{3}+\alpha}^{\frac{4\pi}{3}} (V_{ac})^2 d(wt)}$$

7. 3-Φ Full Converter.

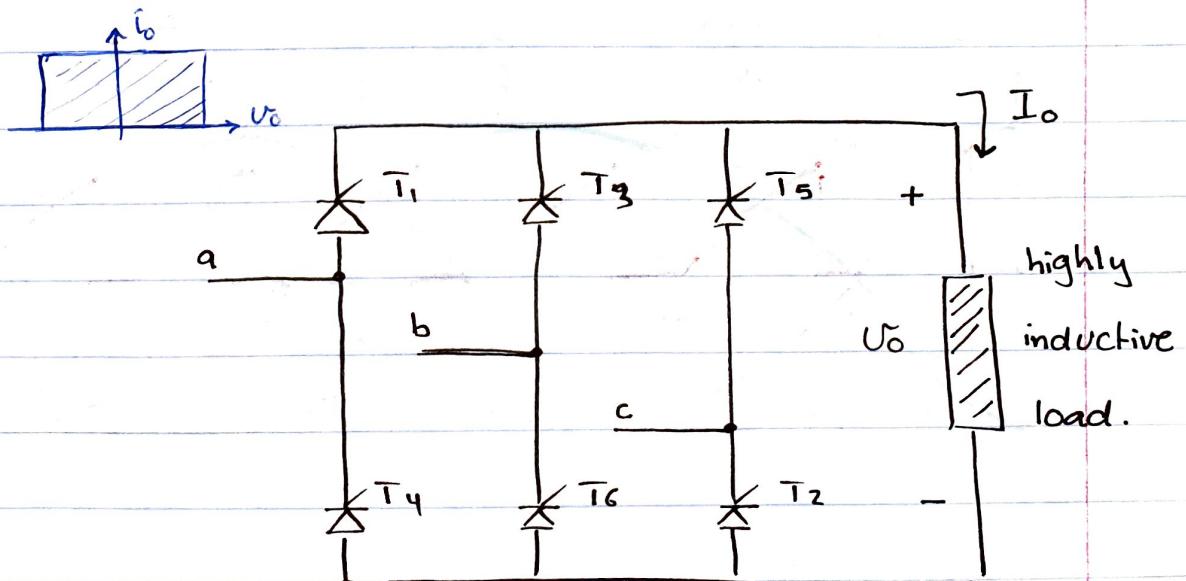

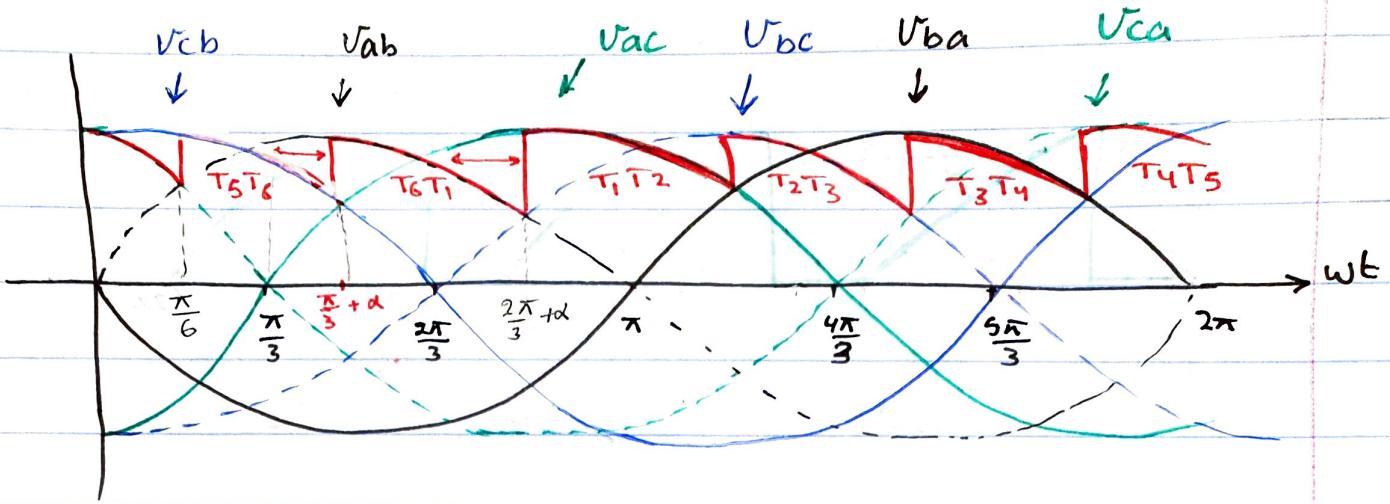


$$V_{DC} = \frac{6}{2\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} V_{ab} d(wt), \quad V_{ab} = \sqrt{3} V_m \sin(wt).$$


$$V_{DC} = \frac{3\sqrt{3}}{\pi} V_m \cos \alpha.$$

$$V_{RMS} = \sqrt{\frac{6}{2\pi} \int_{\frac{\pi}{3} + \alpha}^{\frac{2\pi}{3} + \alpha} (V_{ab})^2 d(wt)} = \sqrt{3} V_m \sqrt{\left(\frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos 2\alpha\right)}$$

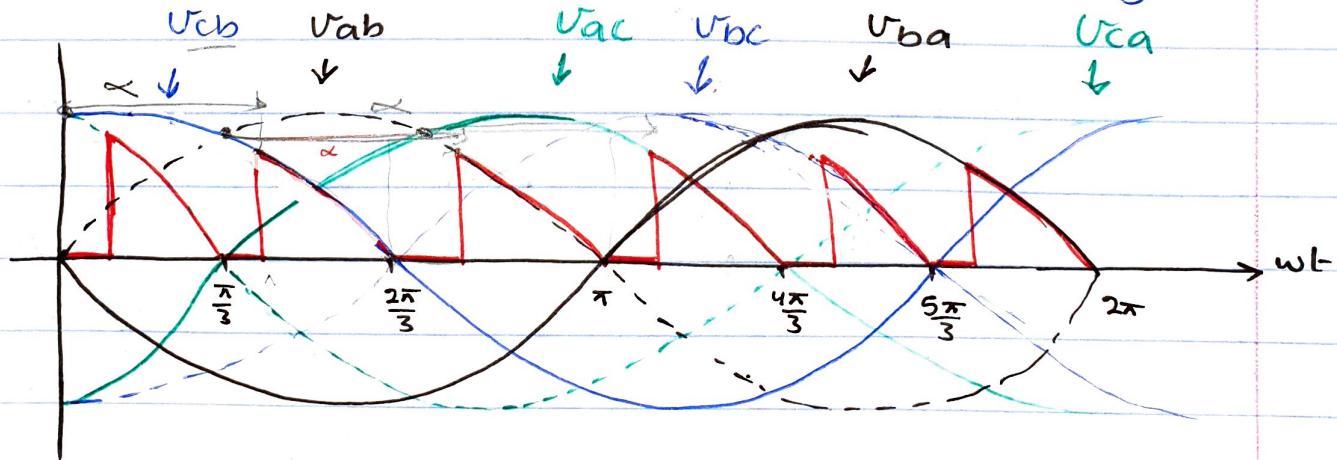
? Special Case : IF the load is resistor & $\alpha \geq \frac{\pi}{3}$


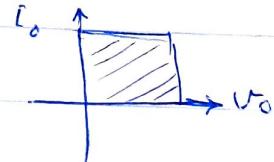
$$V_{DC} = \frac{6}{3\pi} \int_{\frac{\pi}{3} + \alpha}^{\pi} V_{ab} d(wt) = \frac{3\sqrt{3}}{\pi} V_m \left(\cos\left(\frac{\pi}{3} + \alpha\right) + 1 \right).$$




8. 3-Φ Dual Converter.

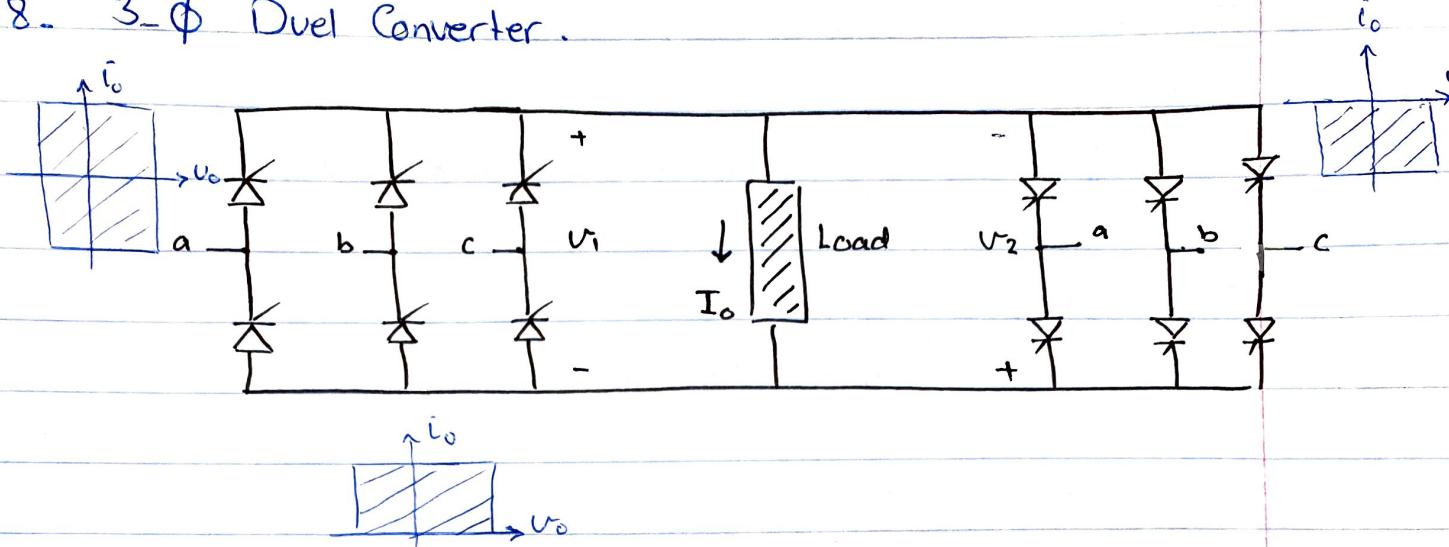

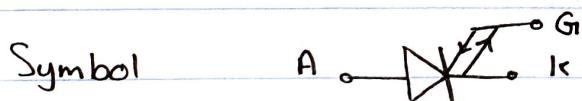
8.11

- Gate Turn-off Thyristors (GTOs).

- It is a special thyristor that can be turned off via its gate. It is self-turned off, but it has higher on-state voltage than normal thyristor.
(e.g., 3.4 V for 1.2 kV @ 0.5 kA device).



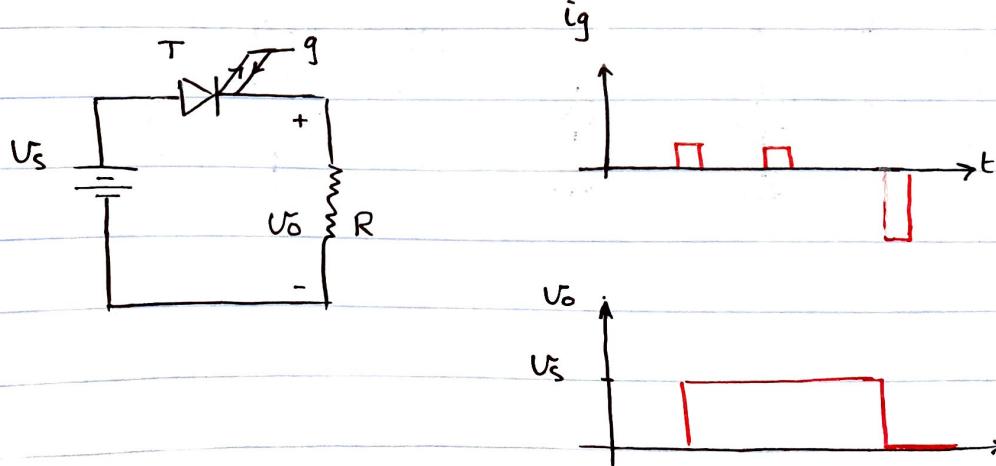- It has the same layers structure of thyristor, but it is modified by adding n^+ (heavy doped n-type) at the anode to operate as a sink to holes at turn off.



- Turn on \rightarrow short pulse of small positive current applied to the gate.
- Turn off \rightarrow short pulse of large negative current applied to the gate.

$$I_g \approx \left(\frac{1}{5} - \frac{1}{3} \right) \underbrace{I_A}_{\text{Anode Current.}}$$

- Power Factor Connection (PFC)

The idea is to improve the PF of the controlled rectifiers or to use the controlled rectifiers as PFC equipment.

- Control Strategies.


1. Extinction Angle Control (EAC)

1.1 EAC for 1- ϕ semi-Converter.


1.2 EAC for 1- ϕ Full-Converter.

2. Symmetrical Angle Control.


1.1 EAC - 1- ϕ Semi Converter.

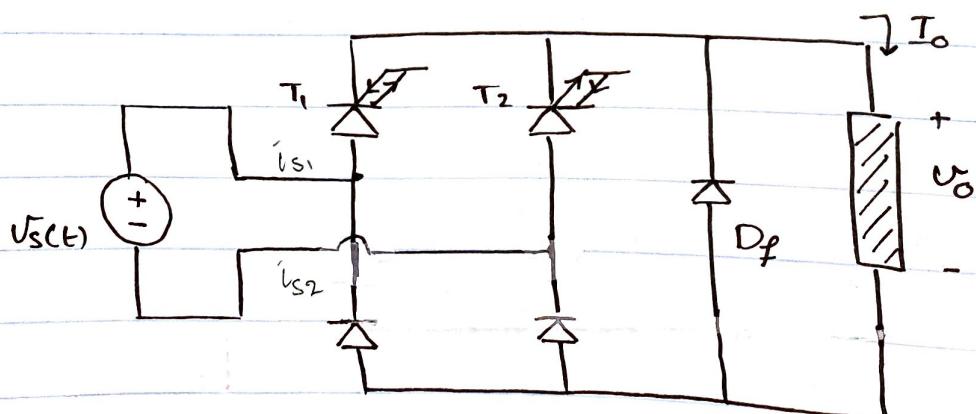

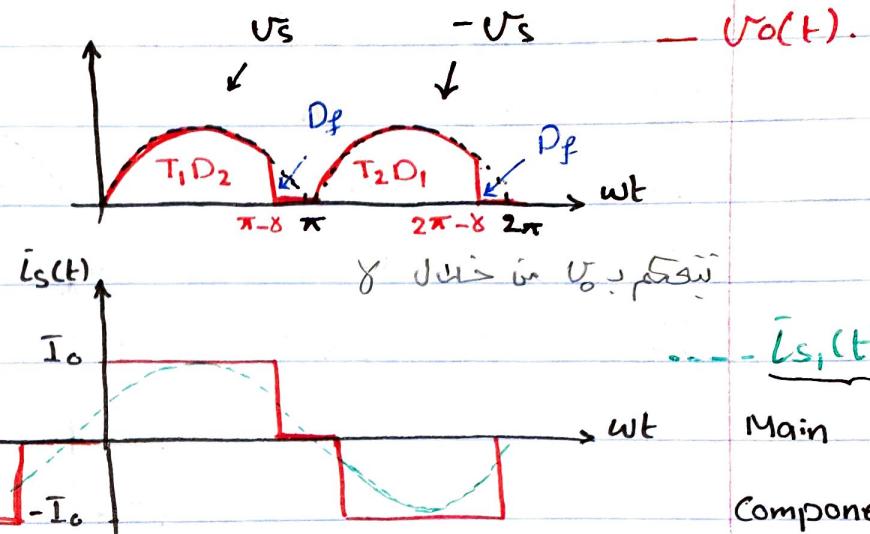ON OFF
 T_1 0 $\pi - \gamma$
 T_2 π $2\pi - \gamma$



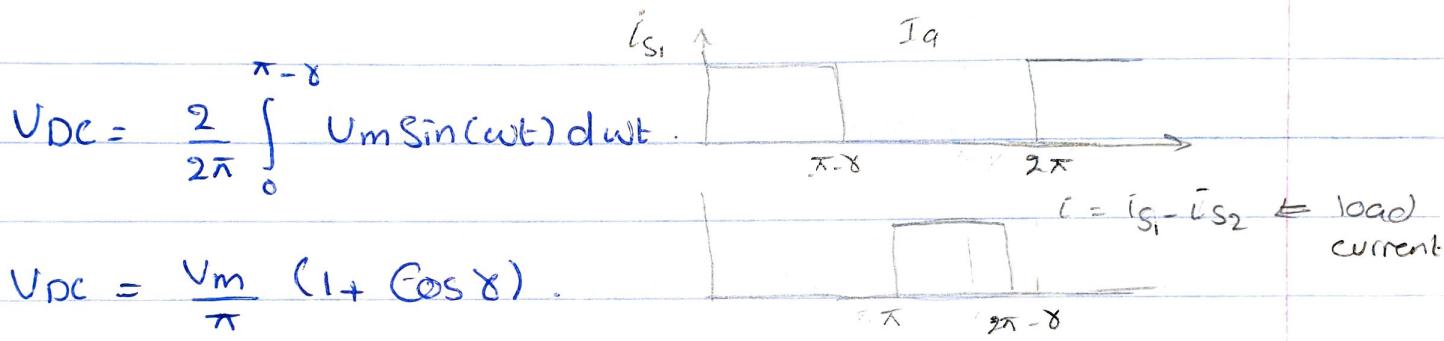$i_{S_1}(t)$ leads $U_s(t)$ \rightarrow Generation of reactive power.





$$V_{DC} = \frac{2}{2\pi} \int_0^{\pi - \gamma} U_m \sin(wt) dwt$$

$$V_{DC} = \frac{V_m}{\pi} (1 + \cos \gamma)$$

$$V_{RMS} = \sqrt{\frac{2}{2\pi} \int_0^{\pi - \gamma} V_m^2 \sin^2(wt) d(wt)}$$

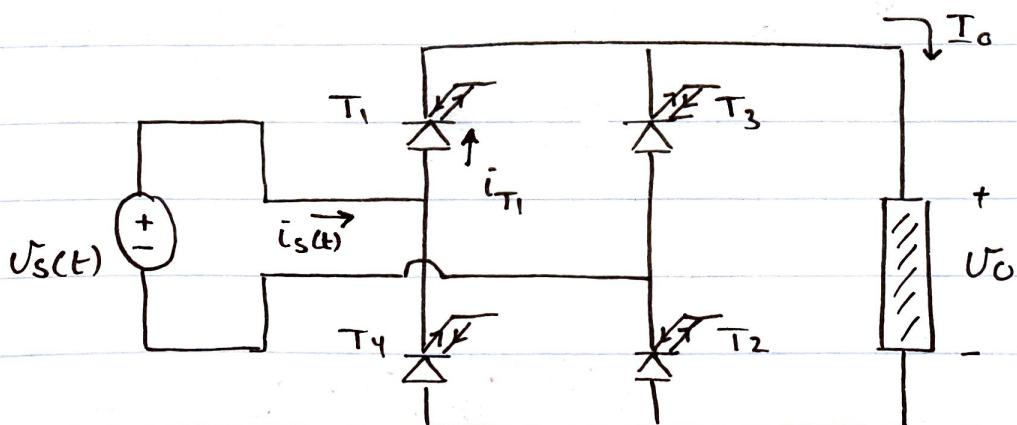1.2. EAC - 1-Φ Full Converter. (Static VAR Compensator).



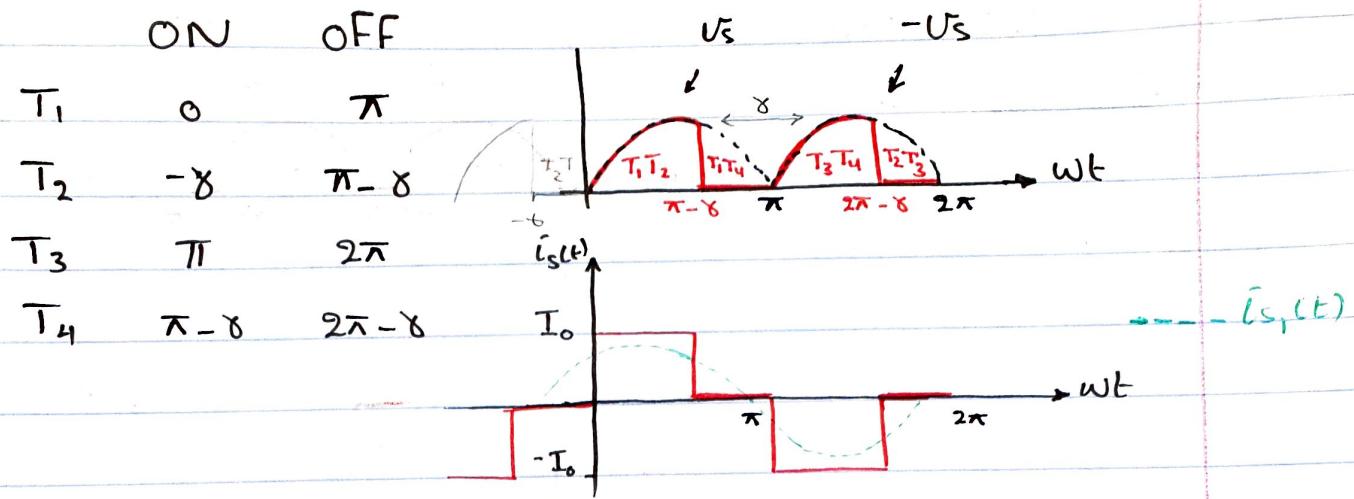


$i_{S1}(t)$ leads $U_S(t)$ \rightarrow Generation of reactive power.

$$V_{DC} = \frac{U_m}{\pi} (1 + \cos \gamma).$$


$$V_{RMS} = \sqrt{\frac{2}{2\pi} \int_{-\gamma}^{\pi-\gamma} U_m^2 \sin^2(\omega t) d\omega t}.$$

2- Symmetrical Angle Control.

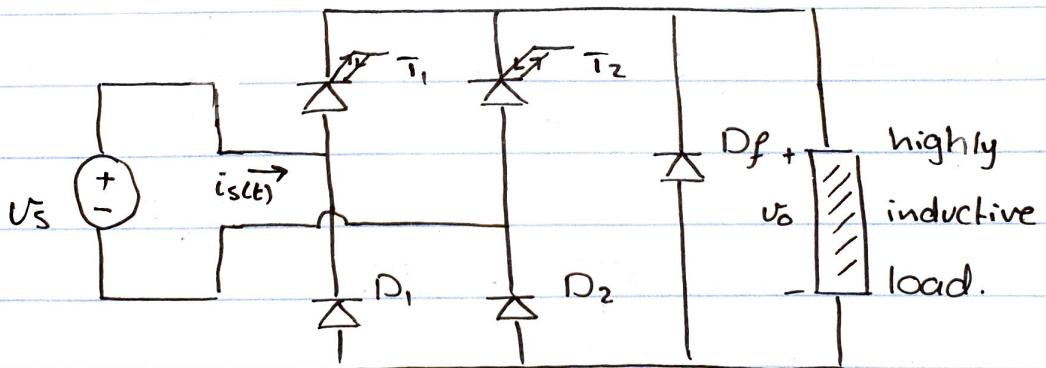

	ON	OFF
T_1	$\frac{\pi - \beta}{2}$	$\frac{\pi + \beta}{2}$
T_2	$\frac{3\pi - \beta}{2}$	$\frac{3\pi + \beta}{2}$

β : Conduction angle.

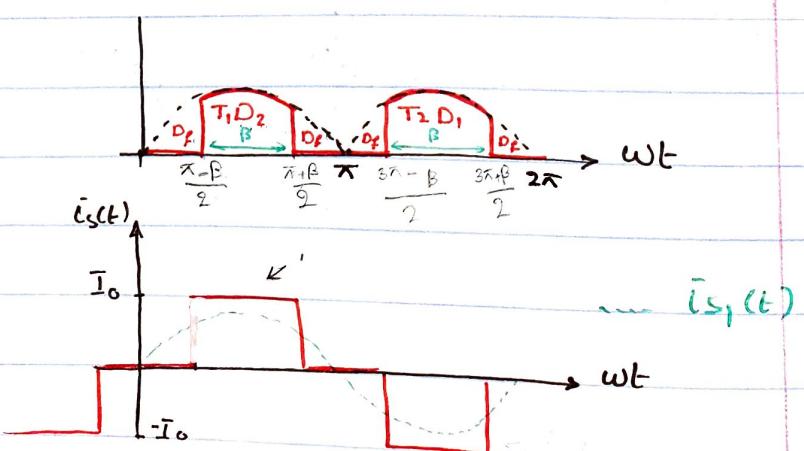


$i_{s_1}(t)$ is in phase with $u_s(t)$.

→ Displacement Factor = $\cos(\Theta_{u_s} / \Theta_{i_{s_1}}) = 1$

$$\Rightarrow PF = \frac{I_{s_1}}{I_1} \times \cos(\Theta_{u_s} / \Theta_{i_{s_1}})$$

i_{T_1}

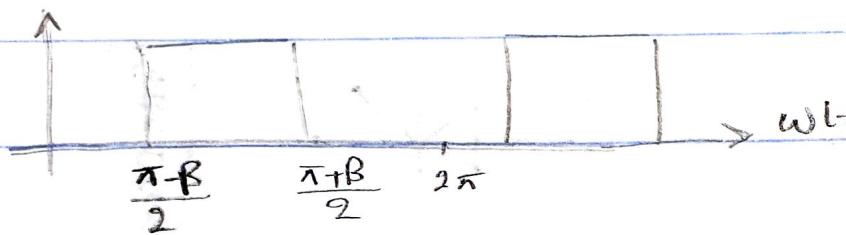

i_{T_2}

$$\frac{3\pi - \beta}{2} \quad \frac{3\pi + \beta}{2}$$


i_{E_0}




- Chapter 4: AC Voltage Controller.

TRIAC \rightarrow Triode for Alternating Current.

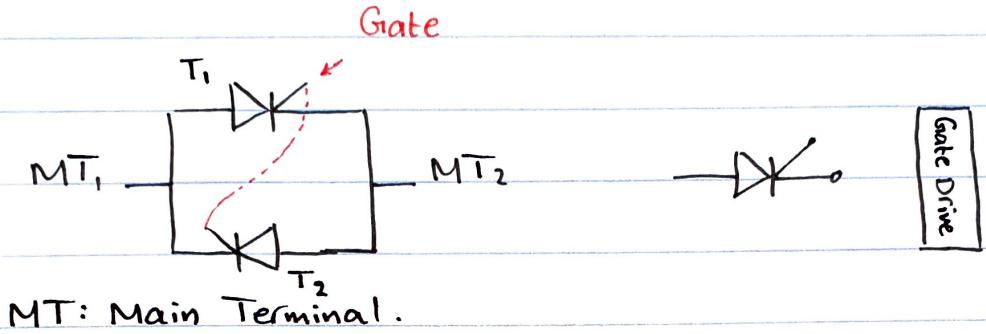
It is equivalent to two anti-parallel thyristors.



- Symbol ;

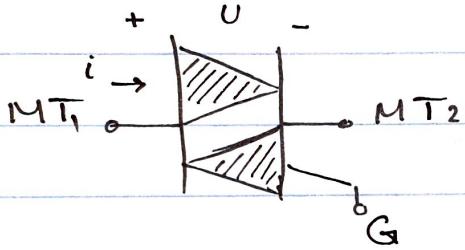

i - U characteristic

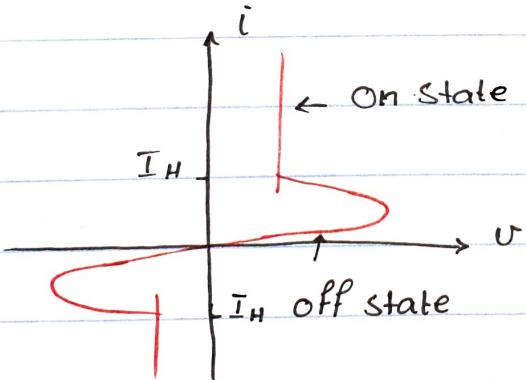

- Types of AC Controller

- 1- ϕ Controllers.
- 3- ϕ Controllers.





- Control Methods

• ON-OFF Control

• Phase angle Control \rightarrow Undirectional Half-wave
 \downarrow Bidirectional Full-wave.

AC Voltage Controllers.

1. On-OFF Control

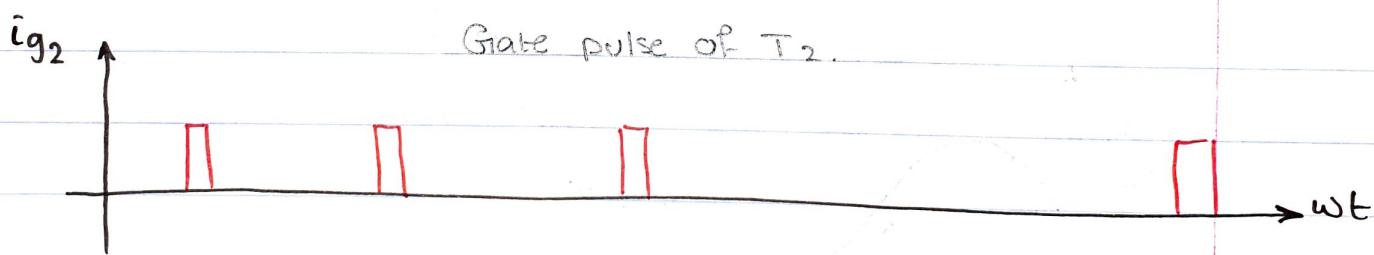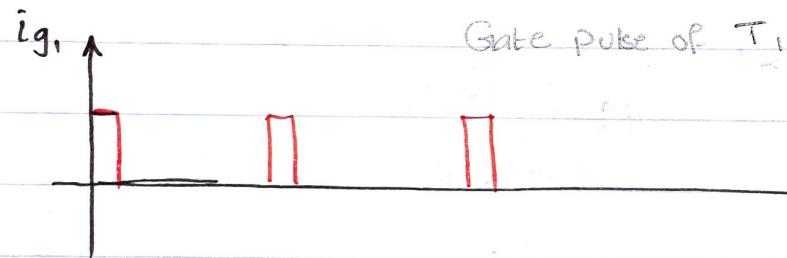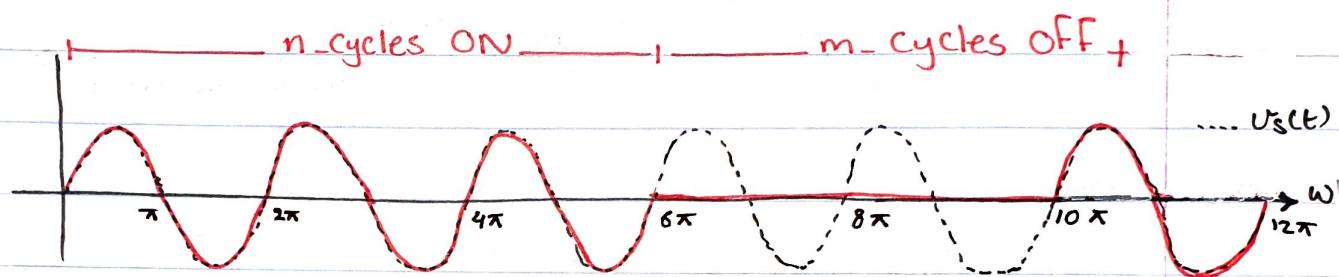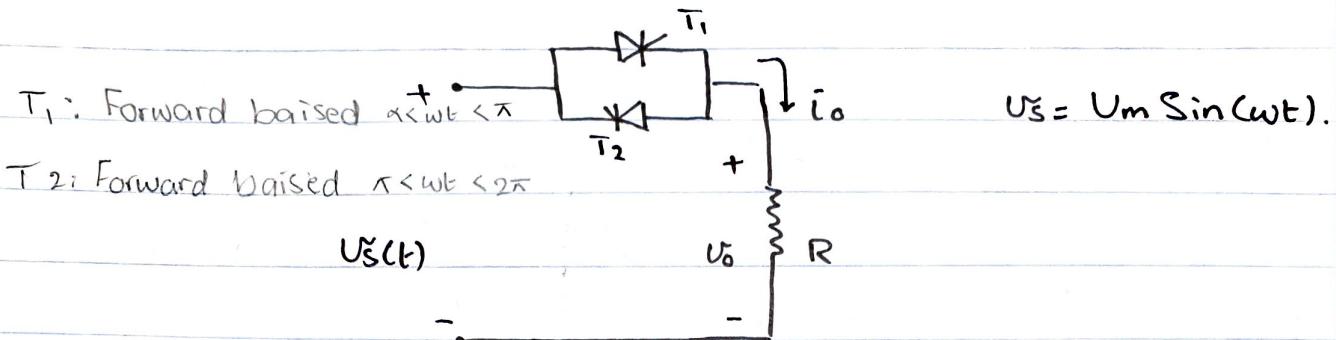

$$V_{RMS} = \sqrt{\frac{n}{(m+n)(2\pi)} \int_0^{2\pi} U_m^2 \sin^2(\omega t) d(\omega t)} = \sqrt{\frac{n}{n+m} \frac{U_m}{\sqrt{2}}}$$

$$V_{RMS} = \sqrt{k} U_S \text{, where ; } U_S \text{ is the RMS value of } U_S(t) \\ k \text{ is the duty cycle } k = \frac{n}{n+m}$$

n : number of "On-Cycle".

m : number of "OFF-Cycle".

- Input Power Factor.

$$PF = \frac{P_s}{S_s}$$


$$S_s$$

$$P_s = \frac{V_{\text{RMS}}^2}{R} \quad \text{"lossless Converter"}$$

$$S_s = V_s I_s, \quad I_s = \frac{V_{\text{RMS}}}{R}$$




$$PF = \frac{(V_{\text{RMS}}^2 / R)}{\left(\frac{V_{\text{RMS}}^2}{\sqrt{k}} / R\right)} = \sqrt{k}$$

(lagging)

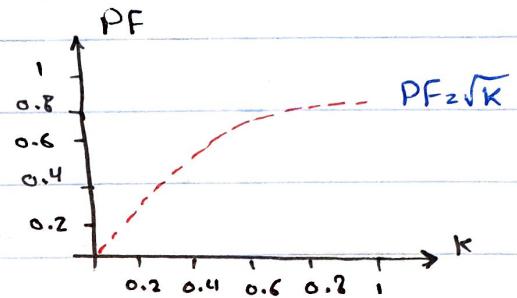

2- Phases Angle Control.

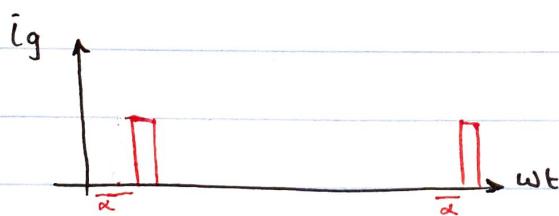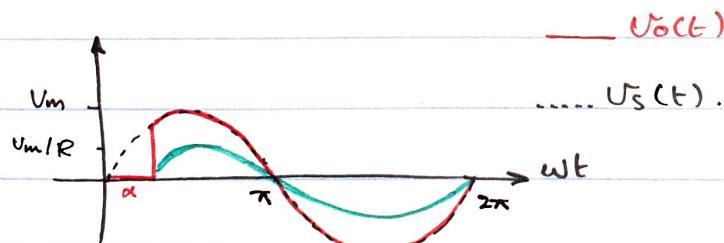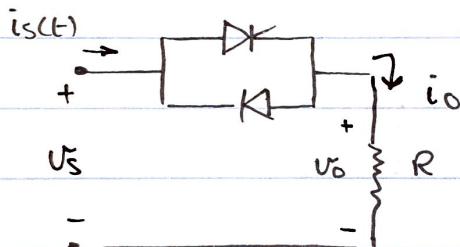2-1 1-Φ half-wave (unidirectional) control.



$$V_{\text{RMS}} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{2\pi} V_m^2 \sin^2(wt) d(wt)}$$

$$V_{\text{RMS}} = \sqrt{\frac{V_m^2}{4\pi} \int_{\alpha}^{2\pi} (1 - \cos(2wt)) d(wt)}$$

$$\sin^2 x = \frac{1}{2}(1 - \cos 2x)$$

$$V_{RMS} = \sqrt{\frac{U_m^2}{4\pi} \left[(2\pi - \alpha) - \frac{1}{2} \sin(2\omega t) \right]_0^{2\pi}}$$

$$V_{RMS} = \sqrt{\frac{U_m^2}{4\pi} \left[2\pi - \alpha + \frac{\sin(2\alpha)}{2} \right]}$$


$$= V_s \sqrt{\frac{1}{2\pi} \left(2\pi - \alpha + \frac{\sin 2\alpha}{2} \right)} ; V_s = \frac{U_m}{\sqrt{2}}$$

$$V_{DC} = \frac{1}{2\pi} \int_0^{2\pi} U_m \sin(\omega t) d(\omega t) = \frac{U_m}{2\pi} (\cos \alpha - 1) , V_m = \sqrt{2} V_s$$

The DC component may cause a saturation problem in the transformer core.

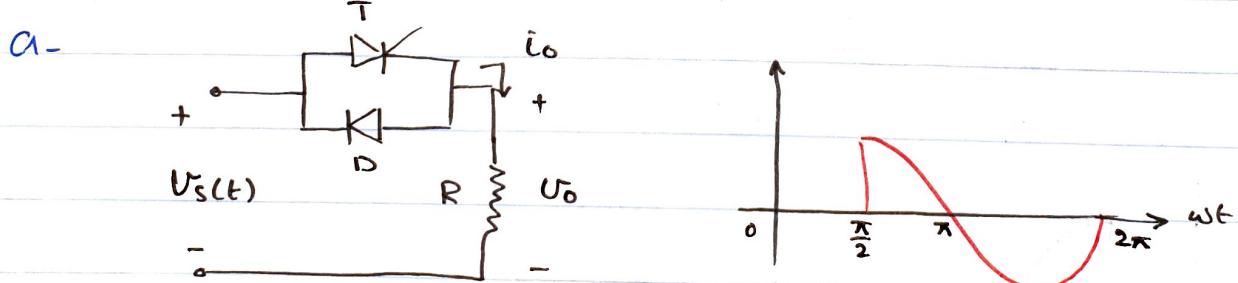- Example: A 1-Φ AC voltage controller (Half-wave controller) has a resistive load of $R = 10 \Omega$, and input voltage is $V_s = 120 \text{ V}$, 60 Hz. The delay angle of the thyristor is $\frac{\pi}{2}$. Determine;

a- V_{RMS} , b- Average input current, c- input PF.



$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_{\pi/2}^{2\pi} U_m^2 \sin^2(\omega t) d\omega t}$$

$$V_{RMS} = \sqrt{\frac{U_m^2}{4\pi} \left[\frac{3\pi}{2} + \frac{\sin(2\pi/2)}{2} \right]} = \sqrt{\frac{3}{8}} (120\sqrt{2})$$

$$= 103.92 \text{ V.}$$

$$b. I_{DC,S} = \frac{1}{2\pi} \int_{\pi/2}^{2\pi} \frac{U_m}{R} \sin(\omega t) d(\omega t)$$

$$I_{DC,S} = \frac{U_m}{2\pi R} \left[\cos \frac{\pi}{2} - \cos(2\pi) \right] = -\frac{120\sqrt{2}}{2\pi(10)} A$$

$$c. PF = \frac{P_s}{S_s}$$




$$P_s = \frac{U_{RMS}^2}{R} = \frac{(103.92)^2}{10} = 1079.94 \text{ W}$$

$$S_s = U_s I_s = 120 \left(\frac{U_{RMS}}{10} \right) = 12(103.92)$$

$$S_s = 1247.04 \text{ VA}$$


$$PF = \frac{1079.94}{1247.04} = 0.866 \text{ lagging}$$

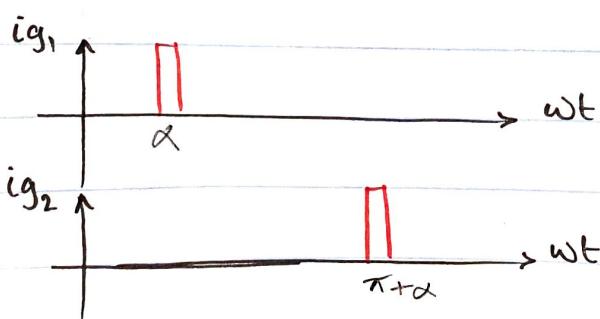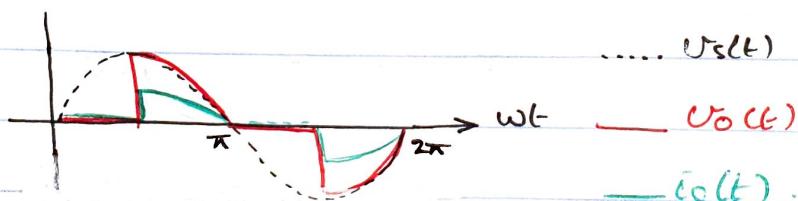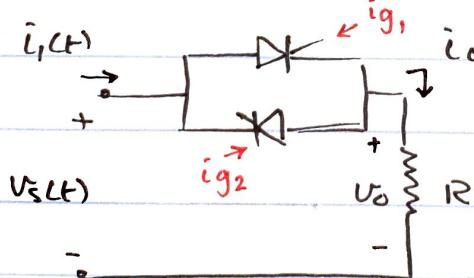2-2 1-Φ Full wave (Bidirectional) control.




- The RMS Value of Output Voltage:

$$\begin{aligned}
 V_{RMS} &= \sqrt{\frac{2}{2\pi} \int_{-\alpha}^{\pi} U_m^2 \sin^2(\omega t) d(\omega t)} \\
 &= \sqrt{\frac{U_m^2}{2\pi} \int_{-\alpha}^{\pi} (1 - \cos(2\omega t)) d(\omega t)} \\
 &= \frac{U_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \left[\pi - \alpha - \frac{\sin(2\omega t)}{2} \right]_{-\alpha}^{\pi}} \\
 &= V_S \sqrt{\frac{1}{\pi} \left[\pi - \alpha + \frac{\sin 2\alpha}{2} \right]}
 \end{aligned}$$

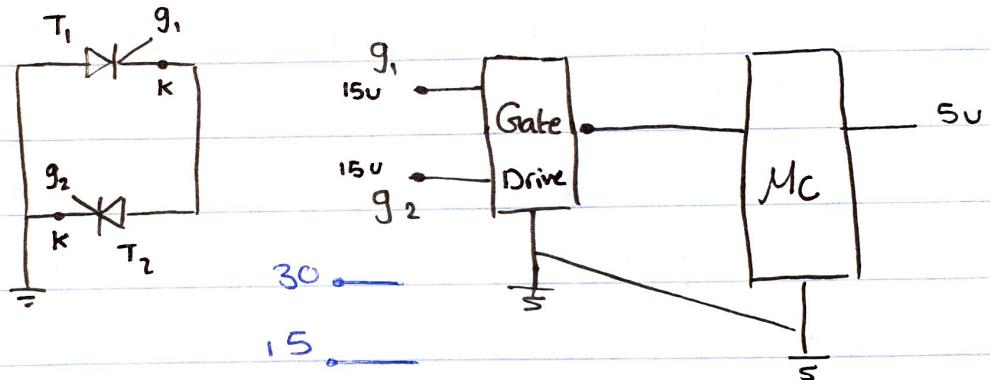

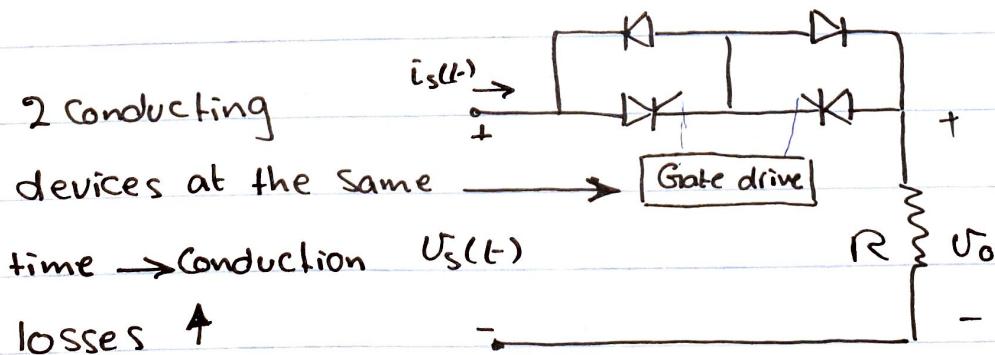The gate drive circuits must be isolated using pulse transformers or auto couplers.



This circuit is used to solve the issue of isolation.

- Example: A 1- ϕ Full-wave AC voltage controller has a resistive load of $R = 10\Omega$, and the input voltage is 120 V, 60 Hz. The delay angle of thyristors T_1 & T_2 are $\frac{\pi}{2}$ & $\frac{3\pi}{2}$. Determine;


- a- V_{RMS} . b- Average current of thyristors.
- c- RMS current of thyristors. d- Input PF.

Solution. π

$$I_{av} = \frac{1}{2\pi} \int_{\frac{\pi}{2}}^{\pi} I_m \sin(\omega t) dt = 2.7 \text{ A.}, I_m = \frac{120\sqrt{2}}{10}$$

$$I_{RMS} = \sqrt{\frac{1}{2\pi} \int_{\frac{\pi}{2}}^{\pi} I_m^2 \sin^2(\omega t) dt} = 6 \text{ A.}$$
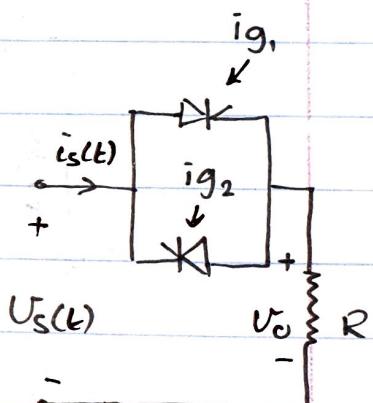
$$V_{RMS} = \sqrt{\frac{2}{2\pi} \int_{\frac{\pi}{2}}^{\pi} V_m^2 \cdot \sin^2(\omega t) d\omega t}$$



$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\pi/2}^{\pi} (1 - \cos 2\omega t) d\omega t}$$


$$= V_s \sqrt{\frac{1}{\pi} \left[\pi - \frac{\pi}{2} + \frac{\sin \pi}{2} \right]} = 84.85 \text{ V.}$$

$$PF = \frac{P_S}{S_S}, P_S = \frac{V_{RMS}^2}{R} = \frac{(84.85)^2}{10} = 720 \text{ W.}$$

$$S_S = V_s I_s = 120 \cdot \frac{84.85}{10} = 8.485 \text{ W}$$

$$PF = \frac{720}{8.485} = 84.86.$$

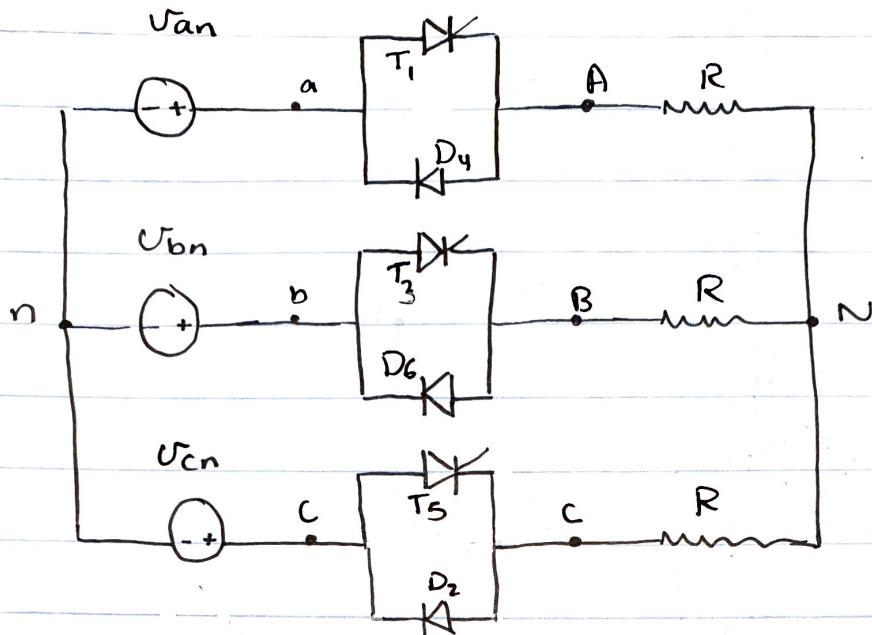2-3 3-Φ Half-wave (Unidirectional) AC controller.




(Look up table)


- Modes of operations.
- Mode I $0 \leq \alpha \leq 60^\circ$

Possible Combinations of conduction's devices.

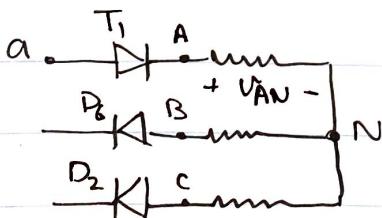- 1- 2 Thyristors & 1 diode.
 - 2- 1 Thyristor & 2 diodes.
 - 3- 1 Thyristor & 1 diode.
- Mode II $60^\circ \leq \alpha \leq 120^\circ$
 - 1- 1 Thyristor & 2 diodes.
 - 2- 1 Thyristor & 1 diode.
- Mode III $180^\circ \leq \alpha \leq 210^\circ$
 - 1- 1 Thyristor & 1 diode.




$$U_{AN} = U_{an}$$

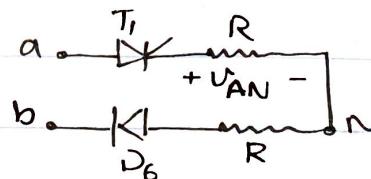


$$U_{AN} = \frac{U_{ab}}{2}$$

$$U_{bn} = U_{BN}, U_{an} = U_{CN}$$

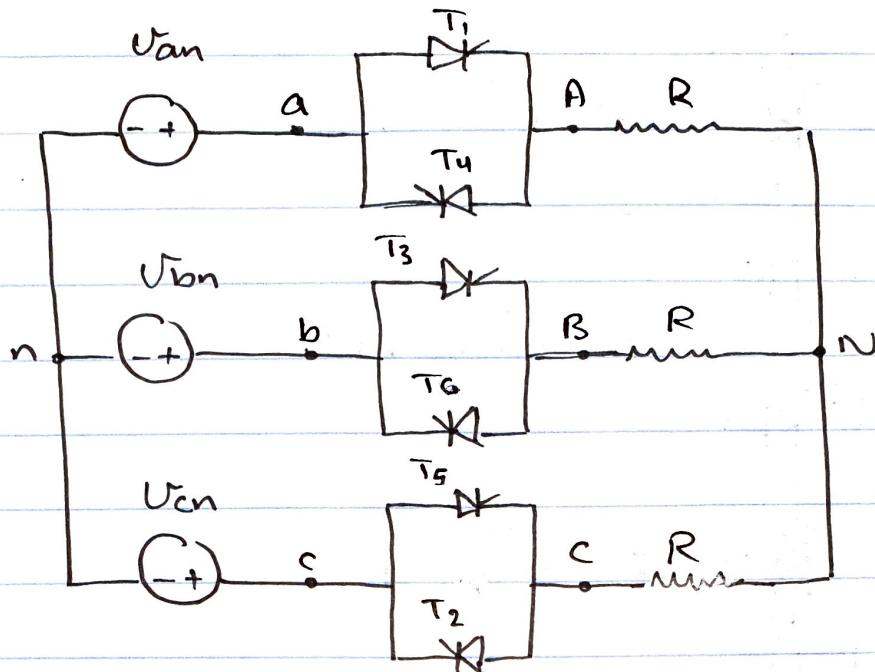
2.4 - 3-Φ Full-wave (Bidirectional) AC Controller.



The input current has high harmonics.

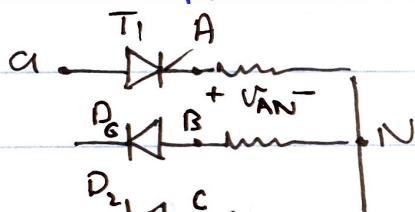

$$\bar{V}_{AN} = U_{an}$$

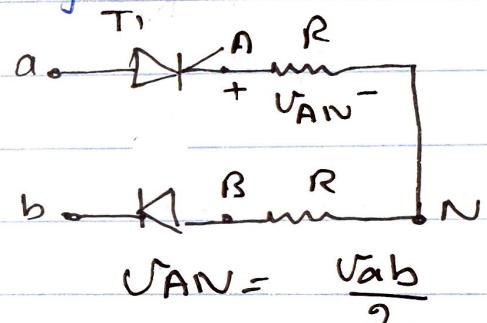

$$\bar{V}_{AN} = \frac{\bar{V}_{ab}}{2}$$

- This input current has DC Component & high harmonics.

- Modes of Operations.

- Mode I $0^\circ \leq \alpha \leq 60^\circ$

1- 3 Thyristors.

2- 2 Thyristors.

- Mode II $60^\circ \leq \alpha \leq 90^\circ$

1- 2 Thyristors.

2- 1 Thyristor

- Mode III $90^\circ \leq \alpha \leq 150^\circ$

1- 1 Thyristor On.

- Cycle Converters.

1- ϕ , 3- ϕ

(AC Power)

Fixed voltage

Fixed Frequency







1- ϕ , 3- ϕ



(AC Power)

Variable voltage, variable frequency (VVVF).

$f_o = \text{Fraction of input Freq. } \approx < \frac{1}{3} f_i$

1- 1- ϕ / 1- ϕ Cycle converter .

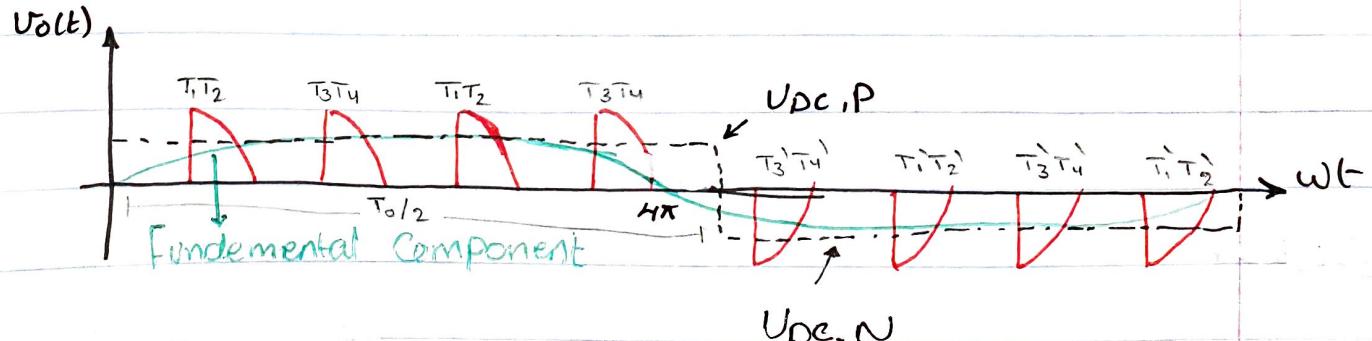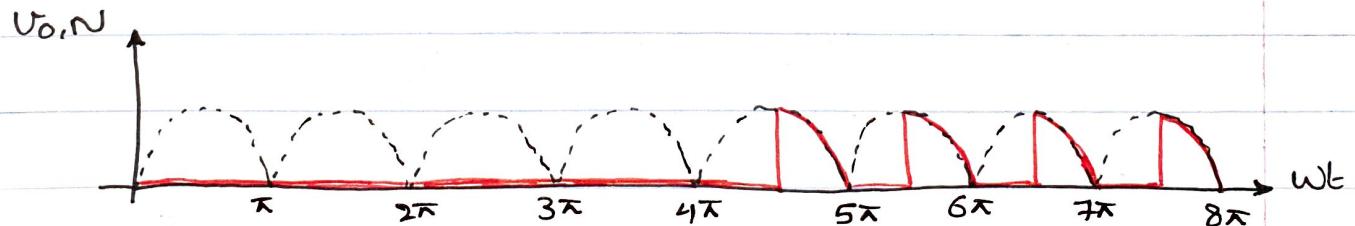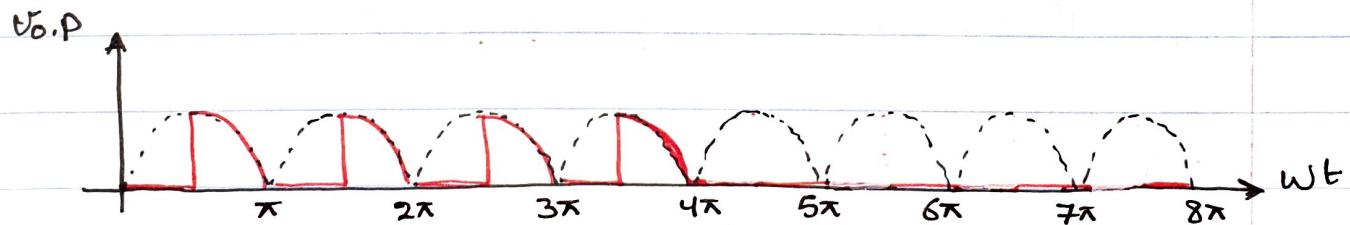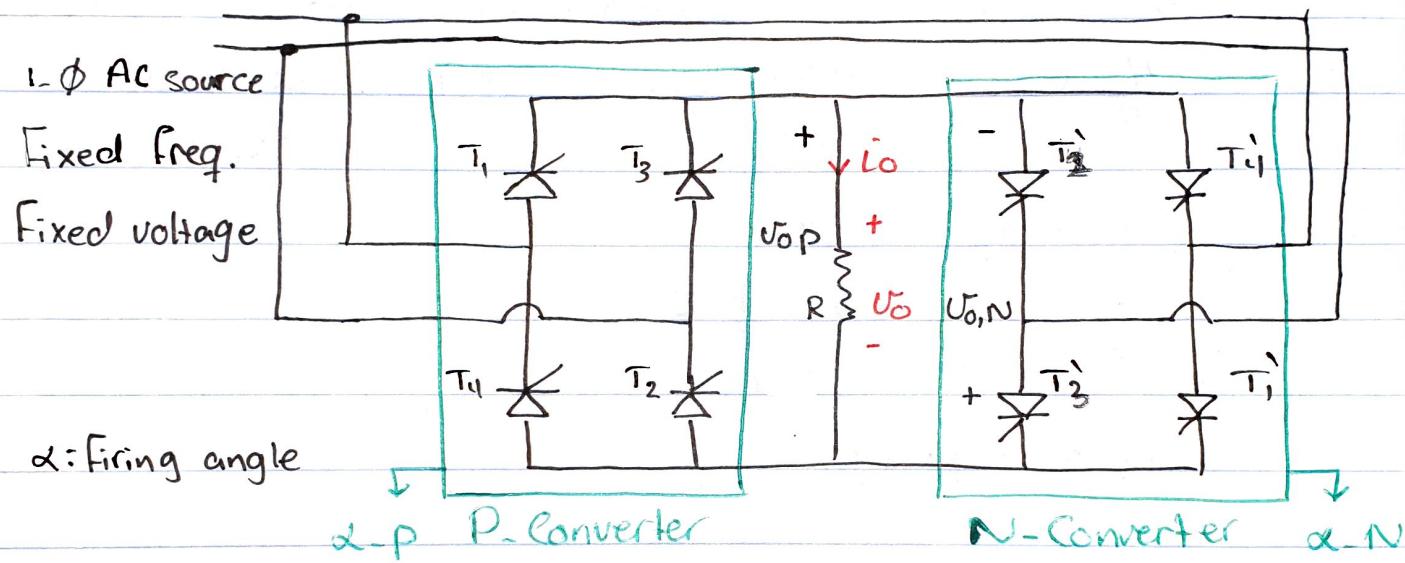

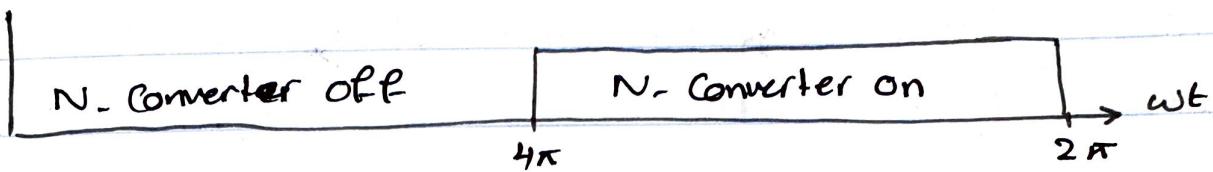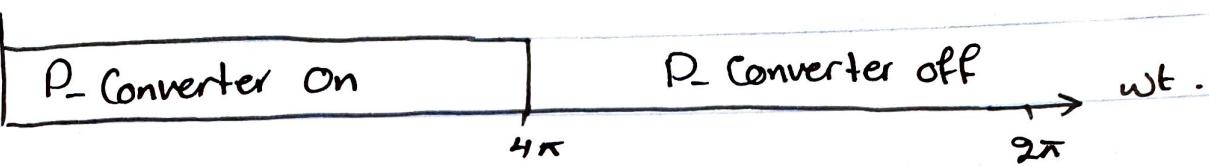

$$V_{DC,P} = |V_{DC,N}| = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$U_o(t) = U_{o,1}(t) + \text{Harmonics}$$

* $U_{o,1} = \hat{U}_o \cdot \sin(\omega_0 t) \Rightarrow \text{Fundamental Component of } U_o(t)$

* $\hat{U}_{o,1} = \frac{4}{\pi} \cdot V_{DC} = \frac{4V_m}{\pi^2} (1 + \cos 2\alpha) \Rightarrow \text{Peak value of } U_{o,1}(t)$.


- The Output Frequency is:

$$f_o = \frac{1}{T_o} f = \frac{2\pi}{8\pi} (f) = \frac{1}{4} f.$$

Input Frequency.


- Note: IF the load highly inductive;
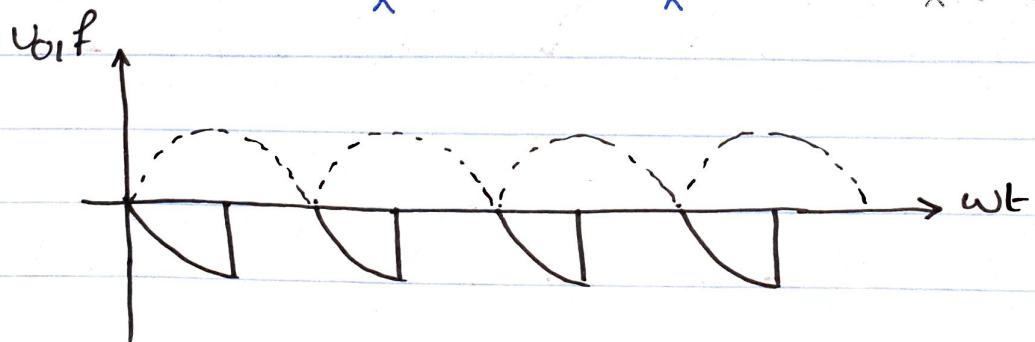
$$\hat{U}_{o,1} = \frac{2V_m}{\pi} \cos \alpha \left(\frac{4}{\pi} \right) \quad \hat{U}_{o,f} = \frac{4}{\pi} \left(\frac{2V_m}{\pi} \cos \alpha \right)$$



- IF a low Filter was used at the output, then the load will have only the Fundamental Component applied across it.

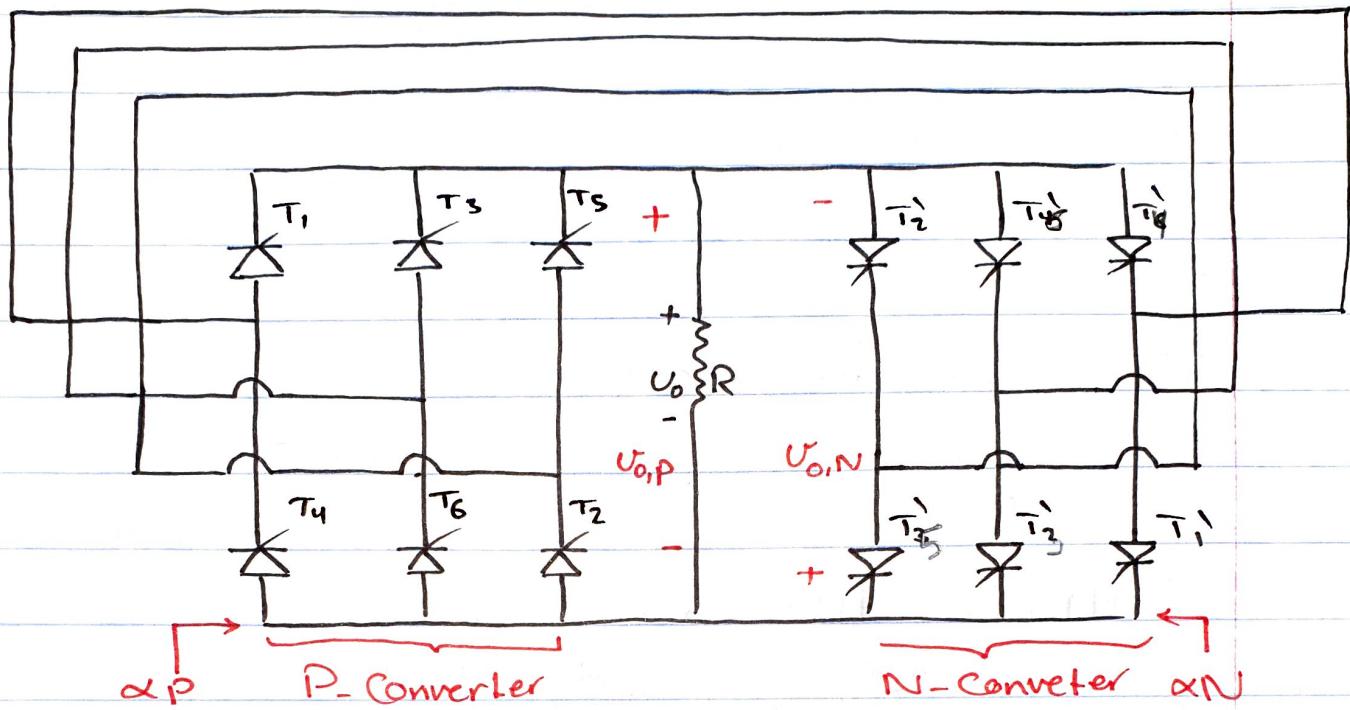2- 3-Φ / 1-Φ Cyclo Converters. It used in higher power applications.



$$\alpha_P = \alpha_N = \alpha$$




$$f_o = 6\pi$$

$$V_{o,P} = |V_{DC,P}| = V_{DC}$$

$$\alpha = \pi/3$$

harmonic distortion $\sqrt{5}$ \leftarrow Pulses are sinusoidal

$$f_o = \frac{1}{3} f_i$$

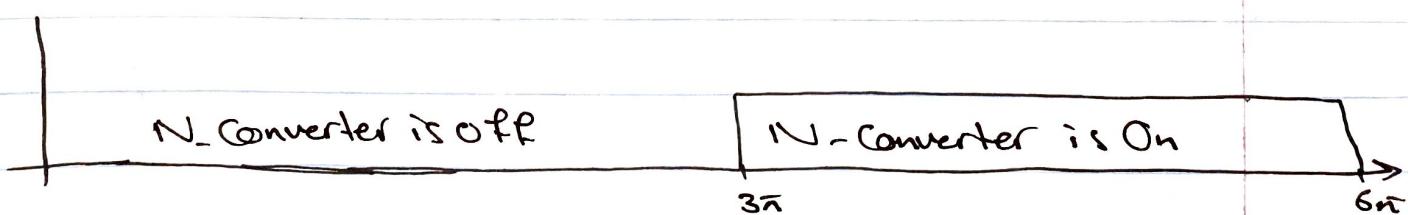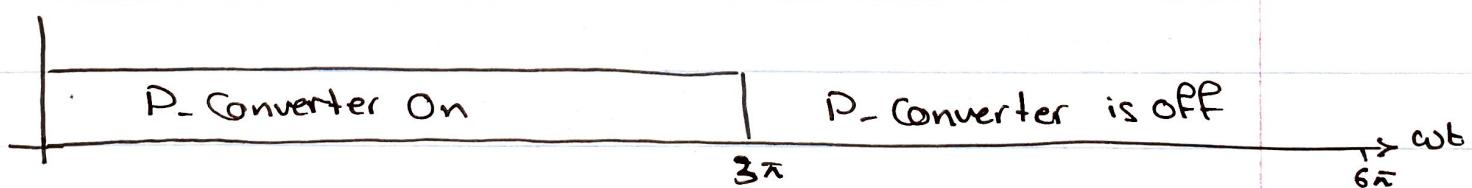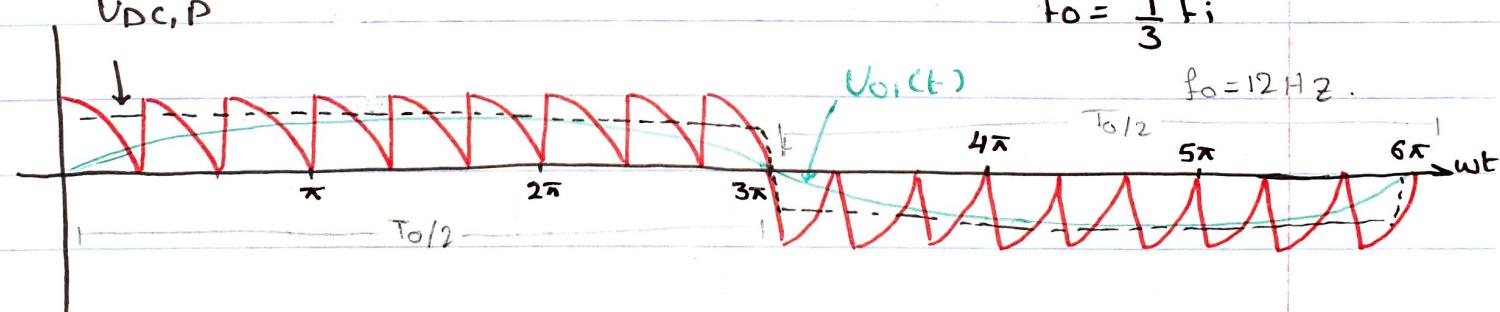

$$V_{DC} = V_{DC,P} = |V_{DC,N}| = \begin{cases} \frac{3\sqrt{3}}{\pi} V_m \cos \alpha, & 0 \leq \alpha \leq \frac{\pi}{3} \\ \frac{3\sqrt{3}}{\pi} V_m (1 + \cos(\alpha + \frac{\pi}{3})), & \alpha \geq \frac{\pi}{3} \end{cases}$$

$V_o(t) = V_{o1}(t) + \text{Harmonics}$. - IF the load highly inductive.

$$V_{o1}(t) = \hat{V}_{o1} \sin(\omega t)$$

$$\hat{V}_{o1} = \frac{4}{\pi} \left(\frac{3\sqrt{3}}{\pi} \cos \alpha \right) \quad 0 \leq \alpha \leq \pi$$

$$\hat{V}_{o1} = \frac{4}{\pi} V_{DC}$$

- The Output frequency:

$$f_0 = \frac{T}{T_0} f = \frac{2\pi}{6\pi} f = \frac{1}{3} f, \quad T = 2\pi$$

T_0 = variable.




THD > THD > THD

1-Φ / 1-Φ 2-Φ / 1-Φ 2-Φ / 1-Φ


Half wave Full wave.

3- 3-Φ / 3-Φ cycloconverters. (36 CSR's are needed).

3.1- 3-Φ Full-wave 1 3-Φ CycloConverter.

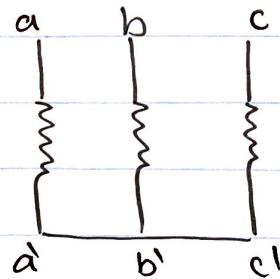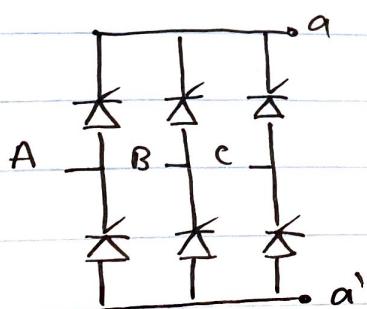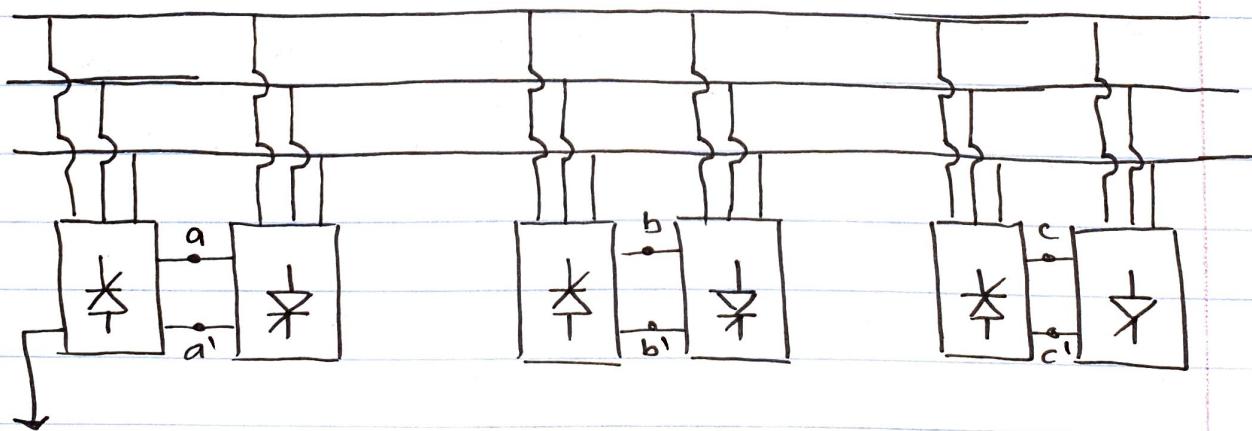


Y-Connected Load

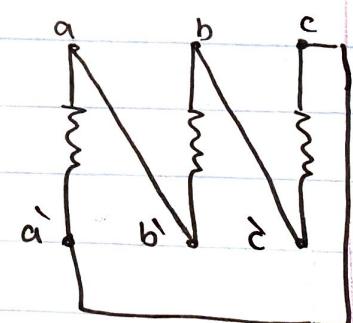


Delta-Connected Load

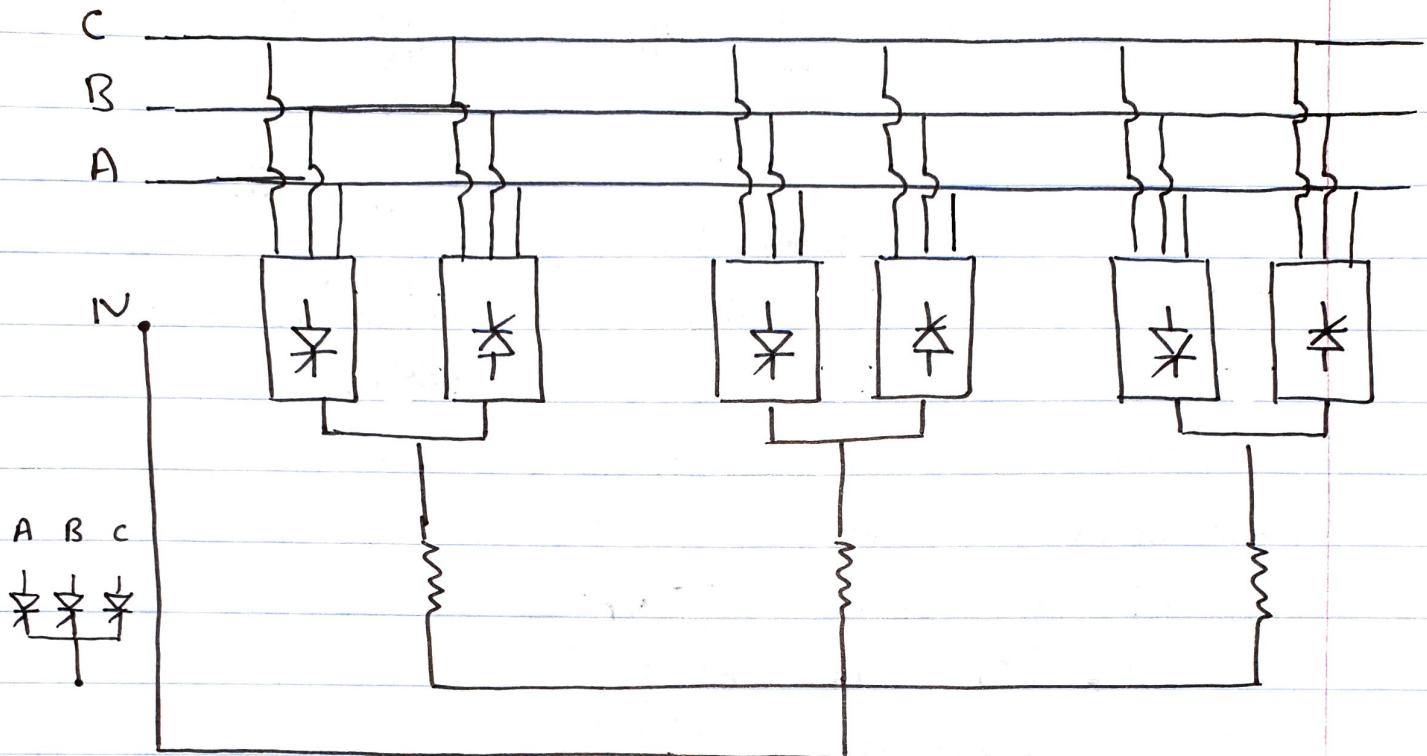
3.9. 3- ϕ half wave / 3- ϕ Cyclo Converter.




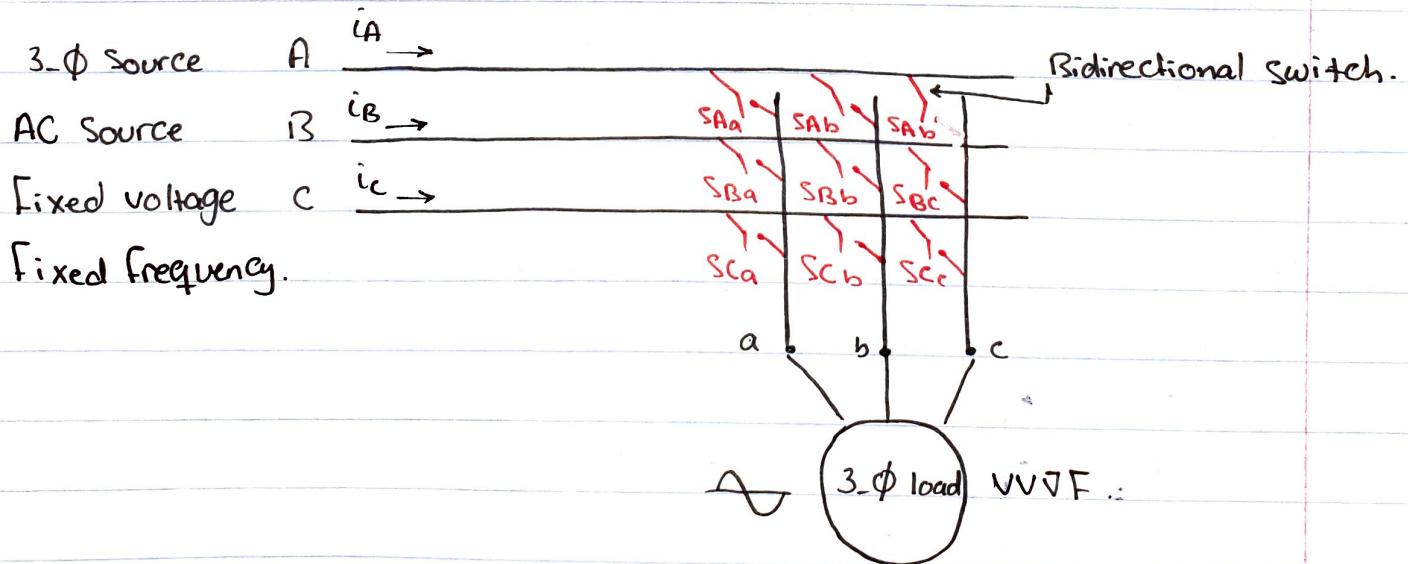- Matrix Converter. "AC voltage Regulator". 9 bidirectional switch



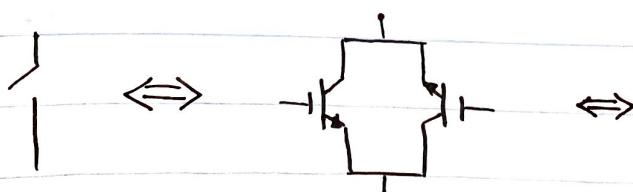- The switch must be able to support a voltage of either polarity and must be able to conduct the current in either direction.



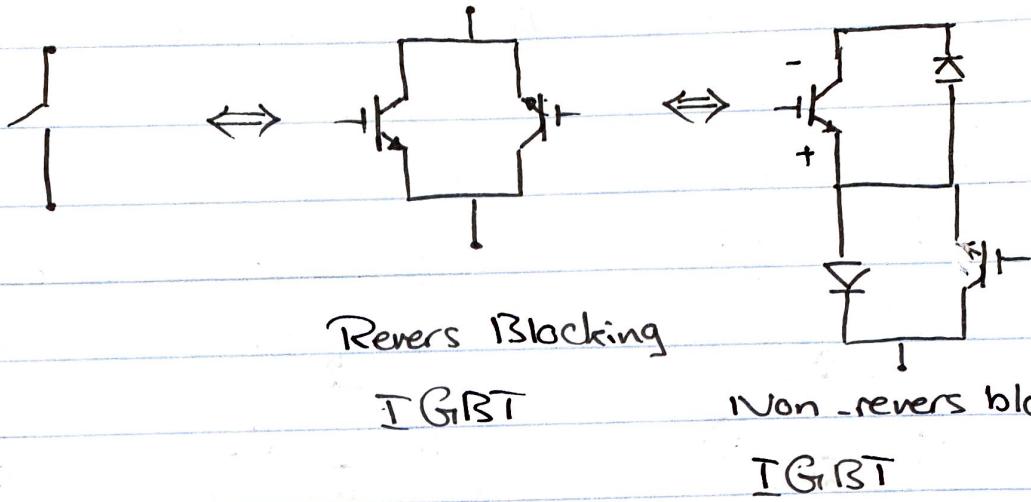

The relationship between the output voltages & input phase voltages is determined by the states of a switches.

$$\begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} S_{AA} & S_{BA} & S_{CA} \\ S_{AB} & S_{BB} & S_{CB} \\ S_{AC} & S_{BC} & S_{CC} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix}$$

To keep line-to-line voltage
at zero voltage.
On \rightarrow

$$V_{abc} = V_{ABC}$$

- Note: To avoid applying short circuit between the lines of input phases, only one switch in each row of the matrix S is ON.
- The relation between the input Current & output currents is determined by the states of switches.

$$\begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} S_{AA} & S_{BA} & S_{CA} \\ S_{AB} & S_{BB} & S_{CB} \\ S_{AC} & S_{BC} & S_{CC} \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix}$$


The Converter must be Controlled in away to avoid discontinuous load current.

- The Converter is controlled using SPWM technique to produce VVVF.
- $THD \ll THD_{\text{cycloconverter}}$.


- Chapter 5: DC-DC Converters (chopper Circuit). Switch Mode Converters.

- Applications.
- Switch Mode Power Supplies.
- DC Machine Drives . DC motor

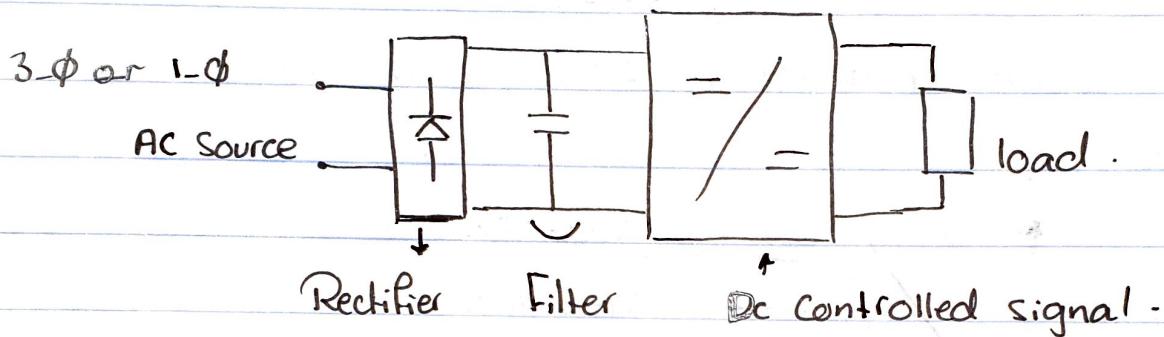1. Rectified AC signal via Uncontrolled rectifiers.



2. DC Battery "Electrics Cars".

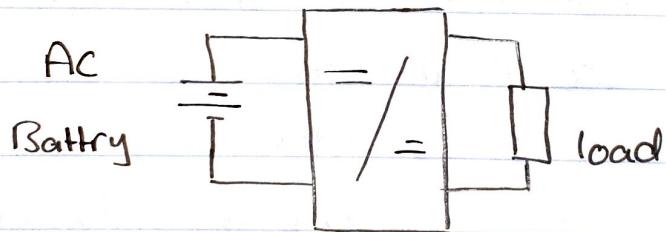


- Types of DC-DC converters.
- 1. Step-down (Buck) Converter.
- 2. Step-up (Boost) Converter.
- 3. Step-up/down (Buck-boost) Converter.
- 4. Half bridge chopper cell .
- 5. Full-bridge chopper cell.

دوائر كهربائية تتحكم في تدفق الجهد
اللائق (DC) عبر المكونات تردد
النطح على مسافت ثابت
 Thyristor ١٠ kHz - ١٠٠ kHz
 وTransistor ١٠ kHz - ١٠ MHz Power transistor


- MOSFET .

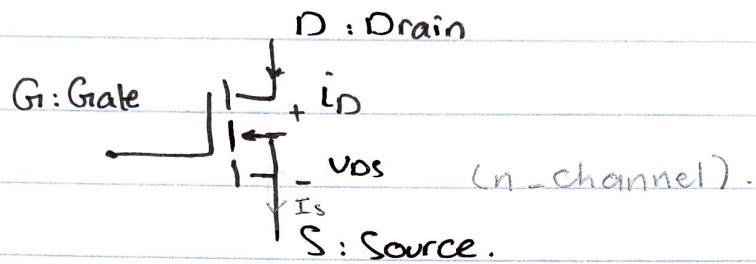- Metal Oxide Semiconductor Field Effect Transistor.
- It is a Voltage Controlled device .
- Fast switching device (0 kHz - 1 MHz).
- Symbol



- We need low gate voltage to turn on the device.

- I-V Curve.

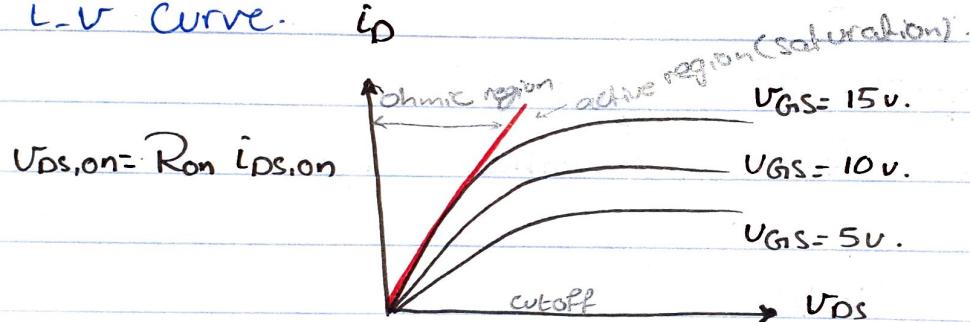

- It operates like resistor when it's conducting.

- It is available at 100 A @ 100 - 200 V.

10 A @ 1 kV .

- It has no reverse blocking capability . Therefore , it comes with built in anti-parallel diode .

مکانیکی - IGBT

- Insulated Gate Bipolar Transistor .
- It is voltage controlled device .
- It combines the best feature of MOSFET & BJT .



MOSFET

- Fast switching . $\leq 20 \text{ kHz}$
- low V_{GE} turn it on
- small gate control power .

BJT


- low voltage drop .
 - High current density .
- 1.2 kV - 600 A , 600 V - 1.2 kA
- low on-state voltage drop .

- Symbol:

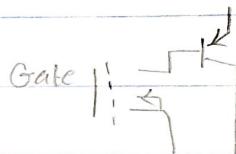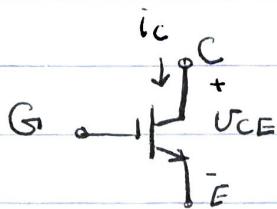

emitter

- I-U curve.

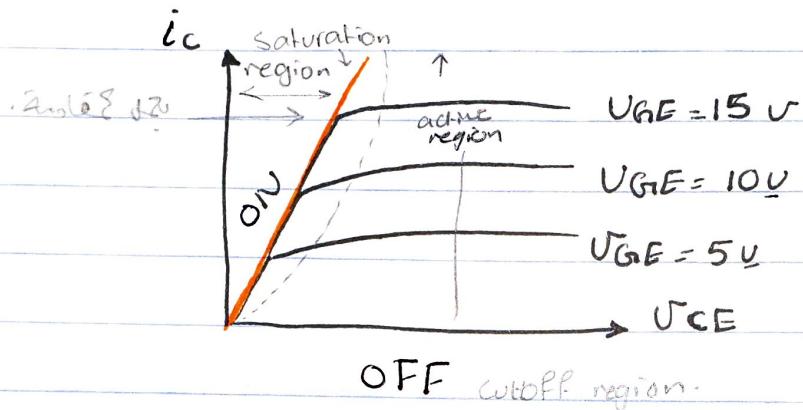


1. Step-down (Buck) Converter.

When T_s On \Rightarrow (U_s) applied


(R) \downarrow i_a \uparrow

When T_s OFF \Rightarrow U_s gate signal

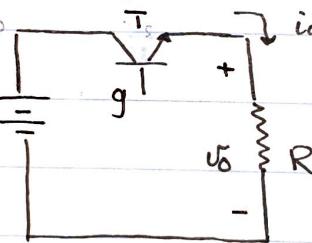


- T_s : Switching time (period)

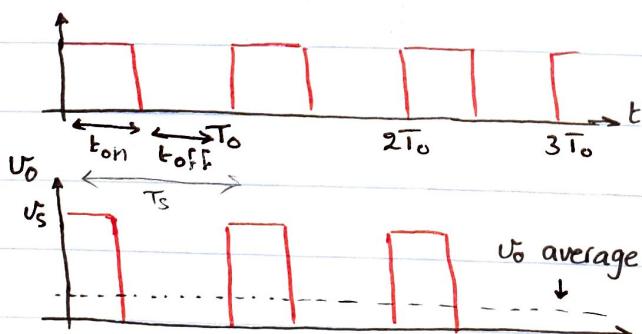- $f_s = \frac{1}{T_s}$: switching frequency
chopping freq.
or carrier freq.



- A few kHz $\leq f_s \leq$ A few hundred kHz.

$\frac{U_o}{U_s} = \frac{t_{on}}{T_s}$

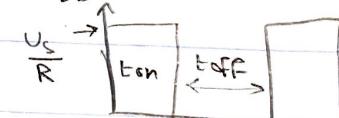

- The average output voltage:

$$\frac{T_s}{t_{on}}$$

$$U_o = \frac{1}{T_s} \int U_o(t) dt = \frac{t_{on}}{T_s} U_s \Rightarrow U_o = \sum U_s$$

$$I_o = \frac{\sum U_s}{R}$$

$\delta = \frac{t_{on}}{T_s}$ "duty cycle", $0 \leq \delta \leq 1$

$$0 \leq U_o \leq U_s$$

Transfer Function:

$$T = \frac{V_o}{V_s} = 8$$

The rms value of $V_o(t)$ is.

$$V_{RMS} = \sqrt{\frac{1}{T_s} \int_0^{T_s} V_o^2 dt} = \sqrt{\frac{1}{T_s} \int_0^{T_s} V_s^2}$$

$$V_{RMS} = \sqrt{\frac{t_{on}}{T_s} V_s^2} = \sqrt{8} V_s$$

Effective Resistor (Source). $\rightarrow P_{out} = P_{in}$.


Assume a loss less chopper, $P_{out} = P_{in} = i_{in} V_{in}$.

$$P_{out} = \frac{1}{T_s} \int_0^{T_s} \frac{V_s^2}{R} dt = 8 \frac{V_s^2}{R}$$

$$P_{in} = \frac{V_s^2}{R_{eq}} = P_{out} = \frac{V_s^2}{R/8}$$

$$R_{eq} = \frac{R}{8}, P_{in} = 8 \frac{V_s^2}{R_{eq}}$$

$P_o(t)$

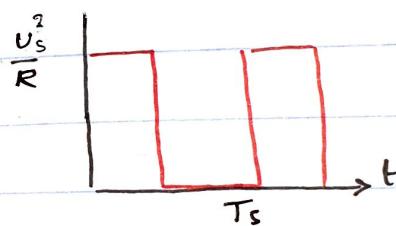



$$V_s = \frac{1}{R_{eq}}$$

Duty cycle control. t_{on}, t_{off}

$T_s : \text{PWM} \rightarrow t_{on}$ Impulse width

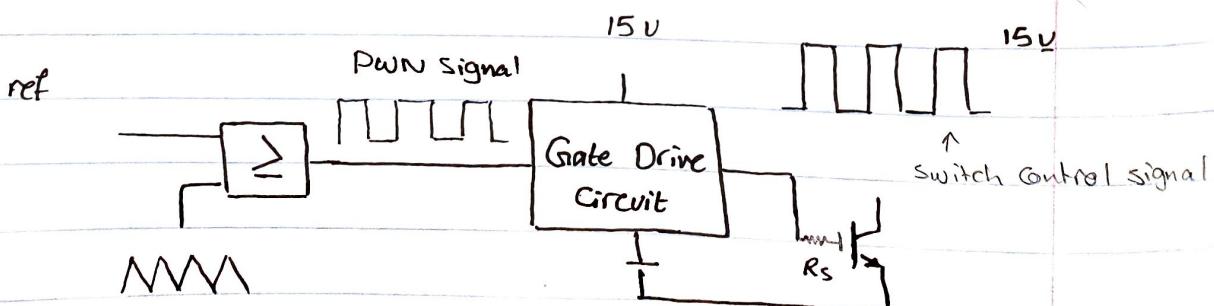
The duty cycle is controlled using pulse width modulation scheme, which is achieved by comparing constant voltage [reference voltage or reference 8] with carrier signal [sawtooth or triangular].



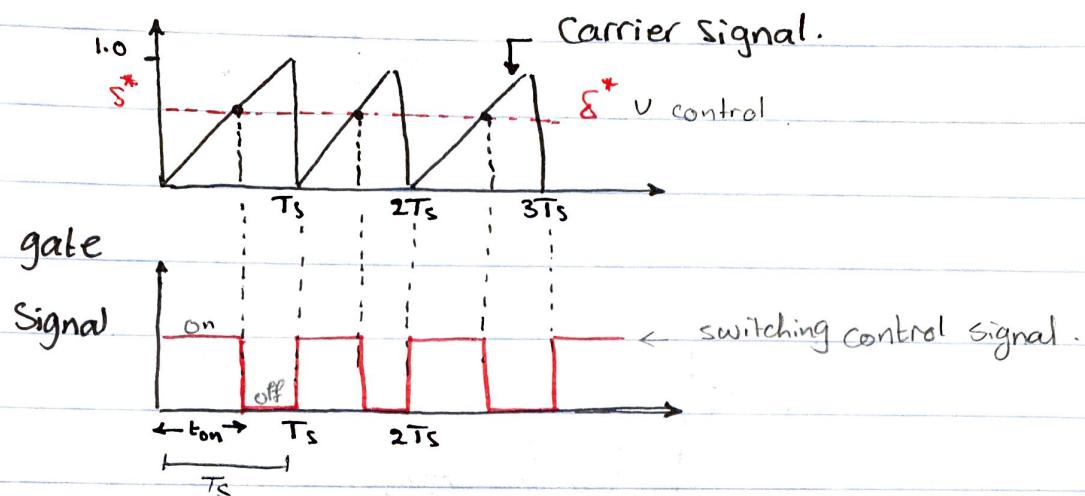

From symmetrical triangles.
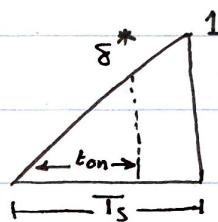
$$\frac{\delta^*}{1} = \frac{t_{on}}{T_s} \Rightarrow \delta^* = \frac{t_{on}}{T_s}$$



Example: DC chopper (Buck) has a resistive load of $10\ \Omega$ & the input voltage is $220\ V$. When the switch is On, its voltage is $\frac{V_{ch}}{2}\ V$, & the chopping frequency is 11cHz . If the duty cycle is 50% , determine the;

- a- Average output voltage. b- RMS output voltage.
- c- Chopper efficiency. d- effective input resistive.

a- $U_{oAV} = \delta(V_s)$ where ; $V_s' = 220 - 2 = 218$.

$$U_o = (0.5)(218) = 109\ V.$$

b- $U_{o,rms} = \sqrt{\delta} \times V_s'$
 $= \sqrt{0.5} (220 - 2) = 154.15\ V.$


c- $P_{out} = \frac{V_s'^2}{R} \cdot \delta = \frac{218^2}{10} \times 0.5 = 2376.2\ W$. $\eta = \frac{P_{out}}{P_{in}} = 99.09\%$

$P_{in} = \frac{V_s}{R_{eq}} \cdot I_{load} \delta = V_s I_o = \frac{220 (220 - 2)}{10} (0.5)$
 $= 2398\ W$

$$d) R_{eq} = \frac{R}{\delta} = \frac{10}{0.5} = 20 \Omega.$$




Step-down Chopper with RL Load. (Buck)

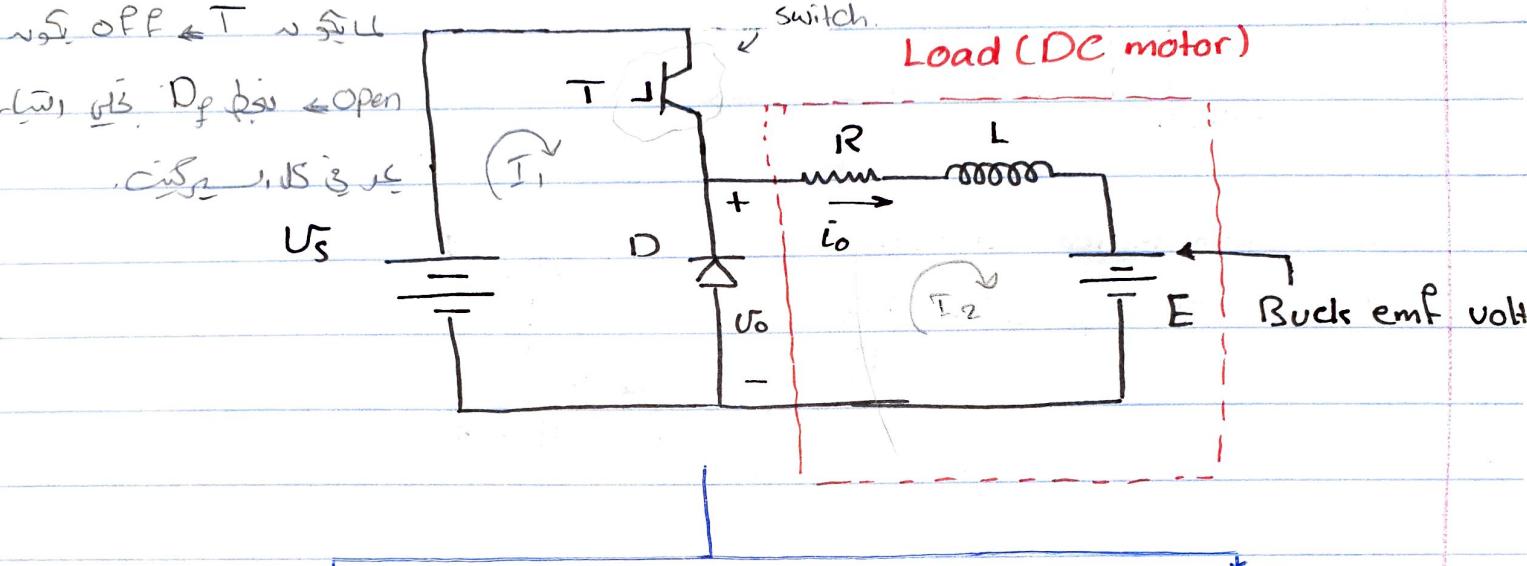




Mode I

T is ON & L is charged

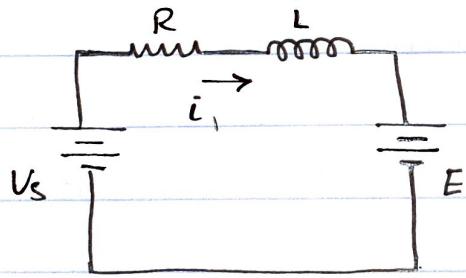

Mode II

T is OFF & L is discha

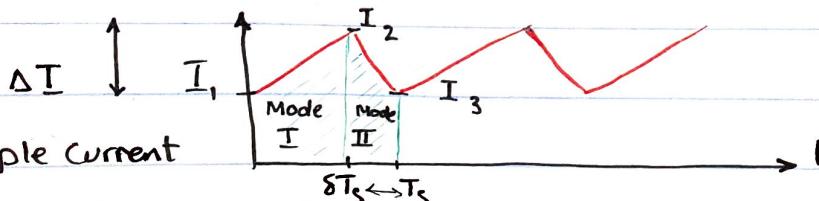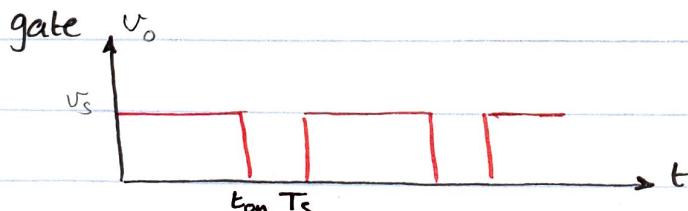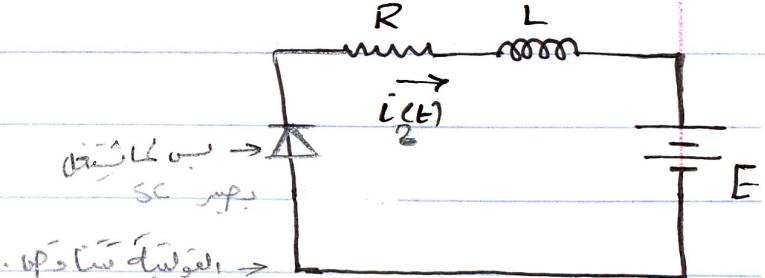

Peak-to-Peak Current. $(1-\delta)T_s$

Mode I: $0 \leq t \leq \delta T_s$

$$-U_s + RI + L \frac{di}{dt} + E = 0.$$

$$\Delta I = I_2 - I_1$$

Peak-to-Peak current

L-Short

$$i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-\frac{t}{LC}}$$

$$i(t) = \frac{V_s - E}{R} + \left(I_1 - \left(\frac{V_s - E}{R} \right) \right) e^{-t/\zeta}; \quad \zeta = \frac{L}{R}$$

$$I_2 = i(8T_s) = \frac{V_s - E}{R} + \left(I_1 - \left(\frac{V_s - E}{R} \right) \right) e^{-8T_s/\zeta}$$

- Mode II: $8T_s \leq t \leq T_s$.

$$RI + L \frac{di}{dt} + E = 0.$$

$$i(t) = -\frac{E}{R} + \left(I_s - \left(\frac{-E}{R} \right) \right) e^{-(t-8T_s)/\zeta}$$

$$I_1 = I_s = i(T_s) = -\frac{E}{R} + \left(I_1 + \frac{E}{R} \right) e^{-\frac{(t-8T_s)}{\zeta}}$$

$$\Delta I = I_2 - I_1 = \frac{V_s}{R} \begin{bmatrix} 1 + e^{-T_s/\zeta} & -e^{-8T_s/\zeta} & -e^{-(t-8T_s)/\zeta} \\ -e^{-T_s/\zeta} & 1 - e^{-8T_s/\zeta} & -e^{-(t-8T_s)/\zeta} \\ -e^{-8T_s/\zeta} & -e^{-(t-8T_s)/\zeta} & 1 \end{bmatrix}$$

Maximum ΔI

$$\frac{\partial \Delta I}{\partial \delta} = 0 \Rightarrow \frac{T_s}{\zeta} e^{-\frac{8T_s}{\zeta}} - \frac{T_s}{\zeta} e^{-\frac{(t-8T_s)}{\zeta}} = 0.$$

$$\delta = 0.5$$

$$\Delta I_{max} = \Delta I \Big|_{\delta=0.5} = \tanh\left(\frac{T_s}{4\zeta}\right) \cdot \frac{V_s}{R} \quad \tanh x = \frac{e^x - \bar{e}^x}{e^x + \bar{e}^x}$$

$$\Delta I_{max} = \frac{V_s}{R} \tanh\left(\frac{T_s}{4\zeta}\right)$$


For highly inductive load. $\tanh(x) \approx x$.

$$\Delta I_{max} = \frac{V_s}{R} \left(\frac{T_s}{4\zeta} \right) \quad \text{where } x \text{ is small}$$

$$\Delta I_{max} = \frac{V_s T_s}{4L}$$

$$\Delta I_{max} = \frac{V_s}{4f_s L} \quad (*)$$

Buck Converter

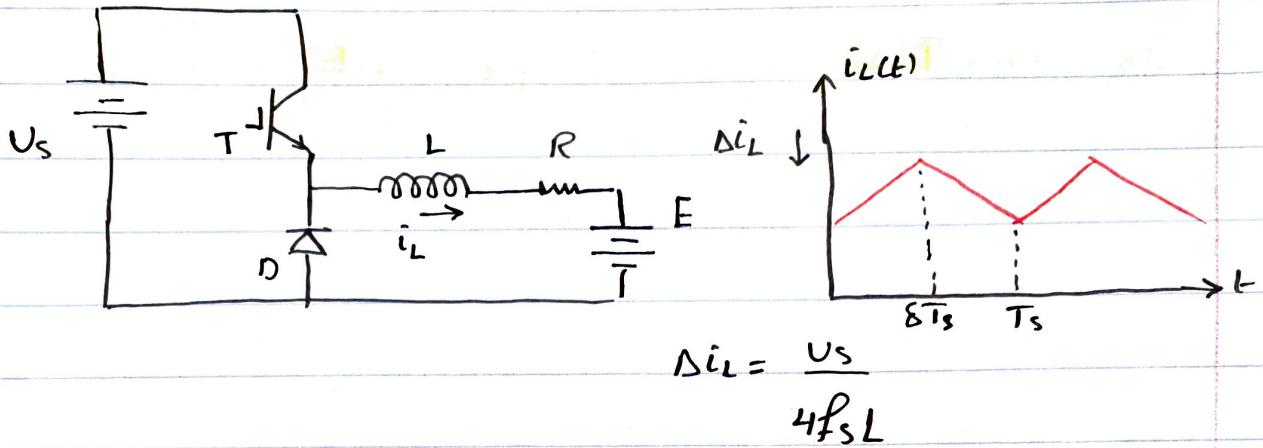

Discontinuous inductor (load) current.

- Mode I ; $0 \leq t \leq 8T_s$

$$V_s = L \frac{di}{dt} + Ri + E$$

$$i(t) = \frac{V_s - E}{R} + \left(0 - \frac{V_s - E}{R}\right) e^{-\frac{t}{L}}$$

$$i(t) = \frac{V_s - E}{R} \left(1 - e^{-\frac{t}{L}}\right)$$

$$I_2 = i(8T_s) = \left(\frac{V_s - E}{R}\right) \left(1 - e^{-\frac{8T_s}{L}}\right)$$

- Mode II ;

$$L \frac{di}{dt} + Ri + E = 0$$

$$-\frac{(t - 8T_s)}{L}$$

$$i(t) = -\frac{E}{R} + \left(I_2 + \frac{E}{R}\right) e^{-\frac{t - 8T_s}{L}}$$

$$i(t) = 0 = -\frac{E}{R} + \left(I_2 + \frac{E}{R}\right) e^{-\frac{t - 8T_s}{L}}$$

$$\frac{E}{R} = \left(I_2 + \frac{E}{R}\right) e^{-\frac{t_2 - 8T_s}{L}}$$

$$e^{\frac{t_2 - 8T_s}{L}} = \left(\frac{RI_2}{E} + 1\right), t_2 = \underbrace{L}_{\text{of mode II}} \ln \left[\frac{RI_2}{E} + 1 \right]$$



To make the current discontinuous ; $t_2 \leq (1 - \epsilon) T_s$.

Since the current is discontinuous,

then the current is zero at the end


$\Rightarrow I_3 = I_1 = 0$

2 Step-up (Boost) Converter.

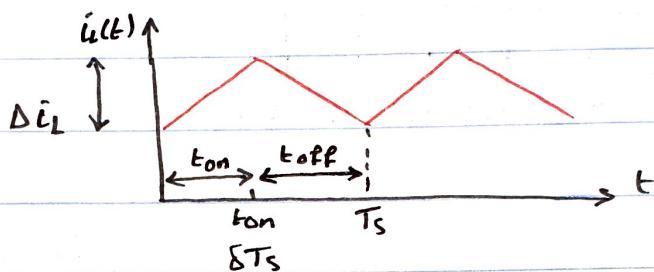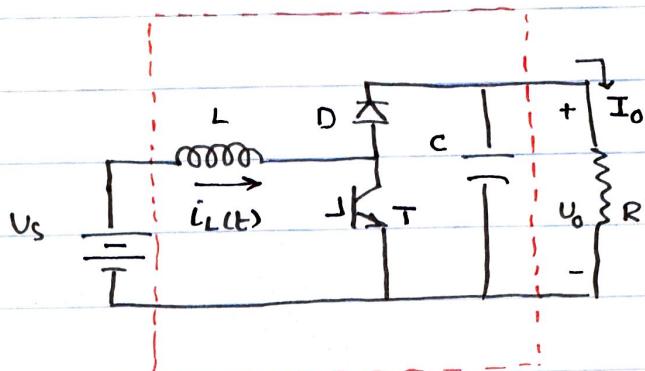

- When T is ON & D is OFF
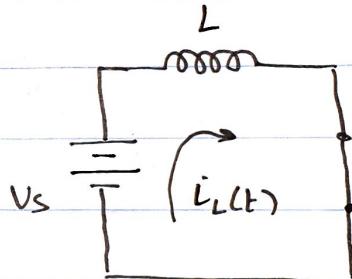
$$V_s = L \frac{di_L}{dt} = L \frac{\Delta i_L}{\Delta t}$$




$$L \Delta i_L = t_{on} V_s \quad \dots \dots (1)$$

- When T is off & D is on

$$V_s = L \frac{di_L}{dt} + U_o$$
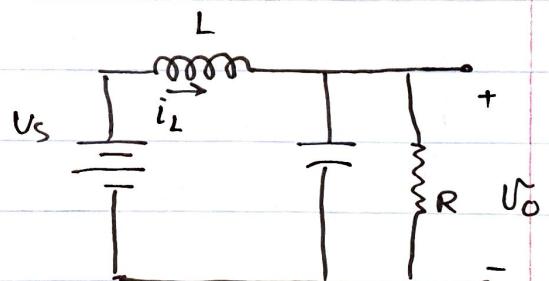
$$V_s = -L \frac{\Delta i_L}{t_{off}} + U_o$$



$$L \Delta i_L = (U_o - V_s) t_{off} \quad \dots \dots (2)$$


$$t_{on} V_s = (U_o - V_s) t_{off} \quad (1) = (2)$$

$$(t_{off} + t_{on}) V_s = t_{off} U_o$$


$$T_s V_s = t_{off} U_o$$

$$\frac{U_o}{U_s} = \frac{T_s}{T_{off}} = \frac{T_s}{T_s - t_{on}}$$
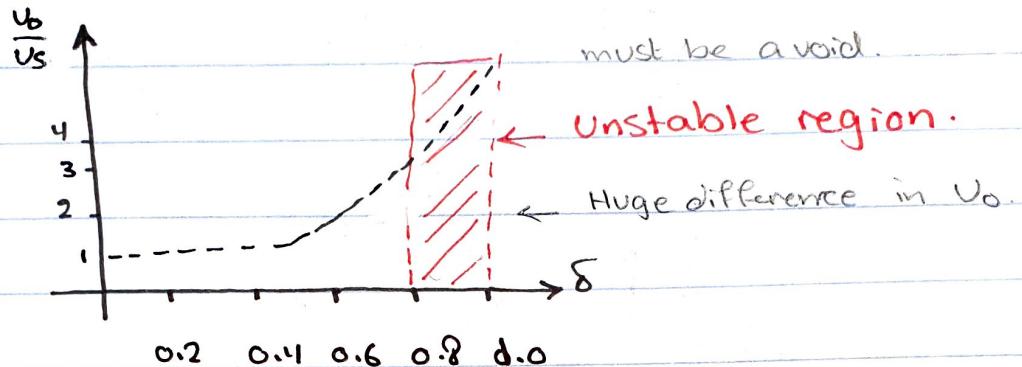
$$\frac{U_o}{U_s} = \frac{1}{1-\delta}; 0 < \delta = \frac{t_{on}}{T_s} < 1$$



Battery Charger Using Boost Converter

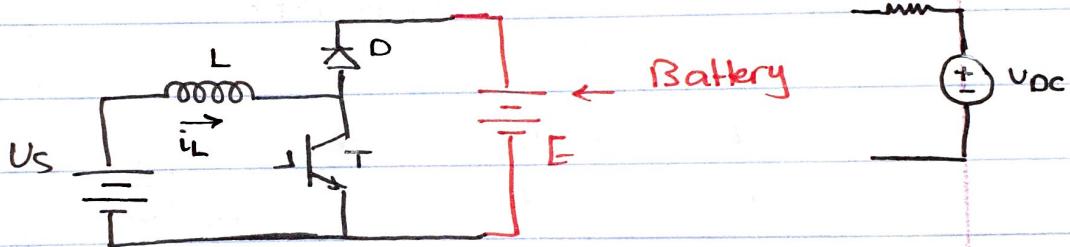


Mode I (T is ON).

$$V_s = L \frac{di_L}{dt} \Rightarrow i_L = \frac{V_s}{L} t + I_1$$

$$\frac{di_L}{dt} > 0 \Rightarrow V_s > 0$$

$$i_L(t) = \frac{V_s}{L} t + I_1$$

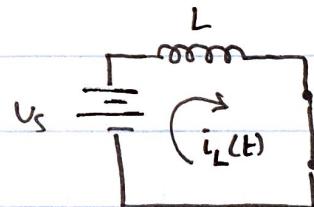

S → closed, D → off
L → charged.


Mode II (T is OFF).

$$V_s = L \frac{di_L}{dt} + E$$

$$\frac{V_s - E}{L} = \frac{di}{dt} < 0$$

$$i_2(t) = \frac{V_s - E}{L} t + I_2$$

$$V_s < 0$$

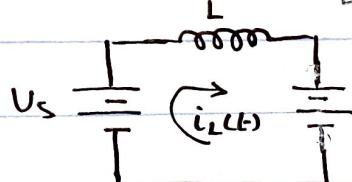

S → open, D → on


L → discharged.

Combined Condition

$$0 < V_s < E$$

Boost Converter δ, Si SW $\Leftrightarrow E > V_s$ up to up

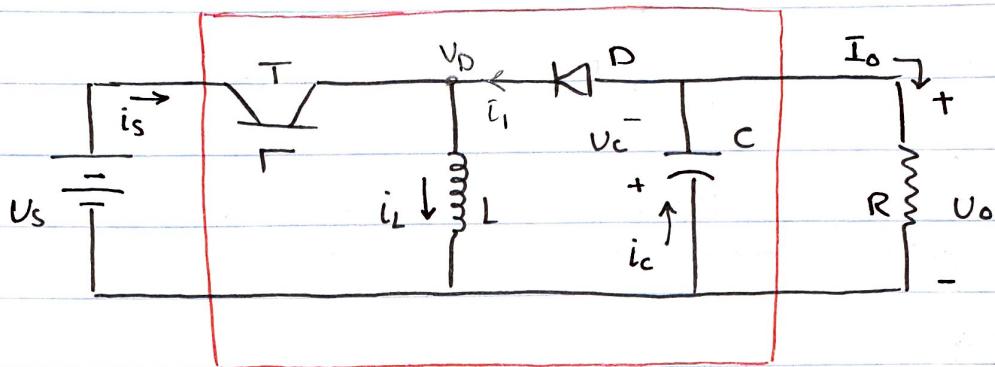3- Step up down (Buck-Boost) DC-DC Converter.




Buck-Boost

Mode I

T is On, D is OFF \leftarrow open

L is charged.

C is discharged.

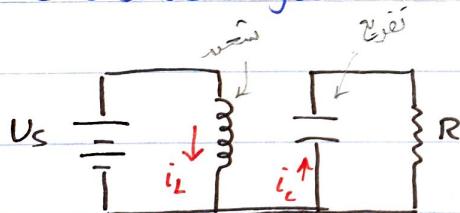

$$Us = L \frac{\Delta i_L}{t_{on}} \leftarrow I_2 - I_1$$

$$L \Delta i_L = Us \frac{t_{on}}{t_{off}} \dots (1)$$

$$\Delta i_L = \frac{Us}{L} t_{on}$$

$$(1) = (2) \Rightarrow -t_{off} V_o = t_{on} Us$$

$$\frac{V_o}{Us} = -\frac{t_{on}}{t_{off}} = \frac{-t_{on}}{T_S - t_{on}} = \frac{-\delta}{1-\delta} \quad V_D = Us \text{ (Mode I)}$$

$$\frac{V_o}{Us} = -\frac{\delta}{1-\delta}$$

$\delta < 0.5, |V_o| < Us$ (Buck).

$\delta > 0.5, |V_o| > Us$ (Boost).


$\delta = 0.5, V_o = -Us$ (Inversion).

Mode II

T is off, D is on \leftarrow closed

L is discharged.


C is charged.

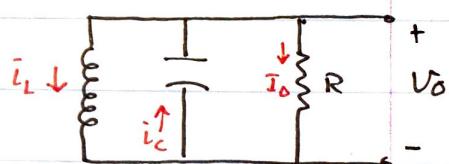

$$V_o = L \frac{\Delta i_L}{t_{off}}$$

$$L \Delta i_L = -t_{off} V_o \dots (2)$$

$$\Delta i_L = -V_o \frac{t_{off}}{L}$$

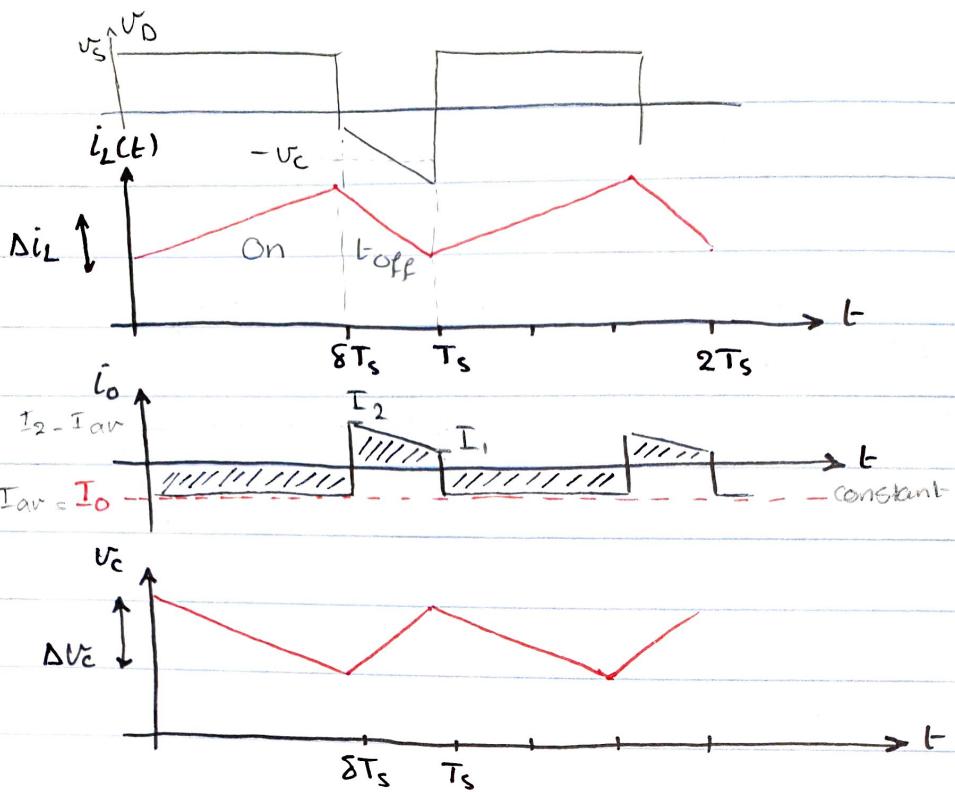

- Input / Output Currents relationship.

Assuming lossless converter.

$$P_{out} = P_{in} \quad P_{in}$$

$$V_o I_o = V_s I_s ; \quad I_s : \text{average input current.}$$

$$\frac{I_s}{I_o} = \frac{V_o}{V_s} = \frac{-\delta}{1-\delta} = \frac{\delta}{1-\delta}$$

- Peak - to - peak ripple current Δi_L :

- Mode I ; (inductor current ripple)

$$V_s = \frac{L \Delta i_L}{t_{on}} \Rightarrow \Delta i_L = \frac{t_{on}}{L} V_s ; \quad t_{on} : 8T_s$$

$$\Delta i_L = \frac{8T_s}{L} V_s$$

$$\Delta i_L = \frac{\delta V_s}{f_s L} \Leftarrow$$

- Capacitor voltage ripple.

$$C_c = C \frac{\Delta v_C}{t_{on}} = I_o$$

$$\Delta v_C = \frac{t_{on}}{C} I_o ; \quad t_{on} : 8T_s$$

$$\Delta v_C = \frac{\delta I_o}{f_s C} \Leftarrow$$

- Example: A buck-boost has an input voltage of $U_S = 12V$.
 The duty cycle, $\delta = 0.25$ & the switching frequency is 25 kHz .
 The inductance, $L = 150\text{ mH}$, and filter capacitance,
 $C = 220\text{ nF}$. The average load current, $I_O = 1.25\text{ A}$.


Determine :

- Average Output Voltage.
- Peak-to-Peak Output Voltage ripple.
- Peak-to-Peak inductor ripple current.
- Peak Current of switch.

$$a - \frac{U_O}{U_S} = \frac{-\delta}{1-\delta} = \frac{-0.25}{1-0.25} \Rightarrow U_O = -\frac{0.25}{1-0.25} \cdot U_S = -4V \text{ (Buck)}$$

$$b - \Delta U_C = \frac{\delta I_O}{f_S C} = \frac{0.25(1.25)}{25 \times 10^3 (220) \times 10^{-9}} = 56.8\text{ mV.}$$
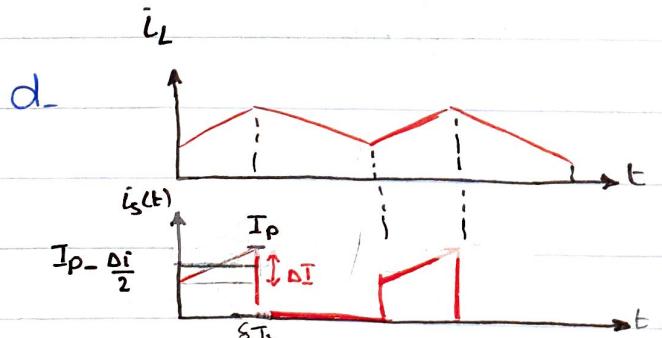
$$c - \Delta i_L = \frac{\delta U_S}{f_S L} = \frac{0.25(12)}{25 \times 10^3 (150) \times 10^{-6}} = 0.8\text{ A.}$$




$$I_S = \delta(I_P - \frac{\Delta i}{2}) \Rightarrow I_P = \frac{I_S}{\delta} + \frac{\Delta i}{2}$$

$$I_S = \frac{+8}{1-0.25} I_O$$


$$= \frac{0.4167}{0.25} + 0.4$$

$$= \frac{0.25}{0.75} (1.25)$$

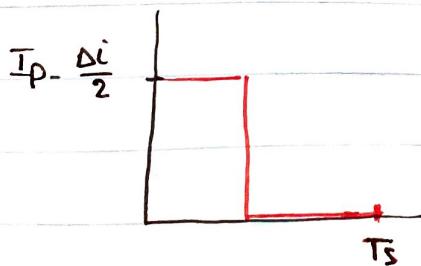


$$I_P = 2.067\text{ A.}$$

$$= 0.4167\text{ A.}$$

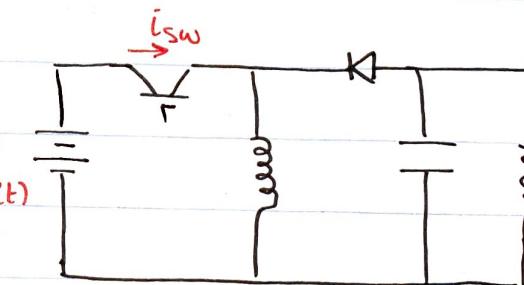

4 | Full-bridge DC/DC converter.

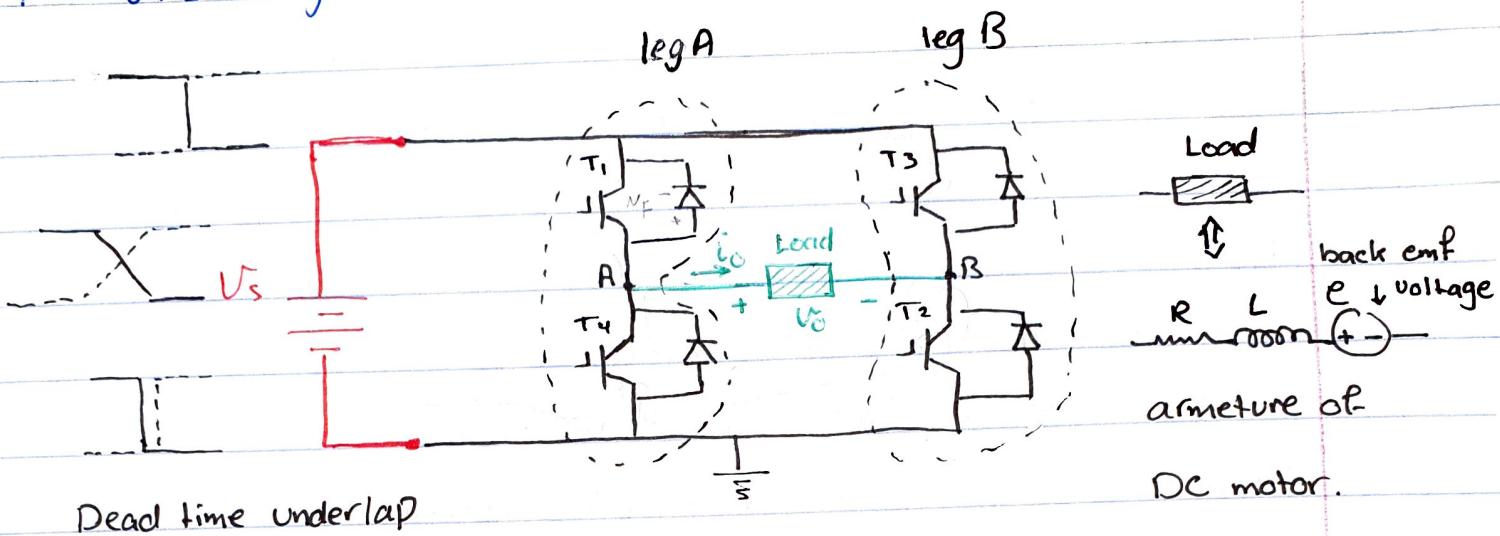


period (1-5) μsec

(Switching time, switches turn on and off time)

Note: A dead time (Underlap period) must be applied for each leg to avoid shorting the DC link.

DC motor & short circuit figure see [GP](#)

$$i_o > 0$$

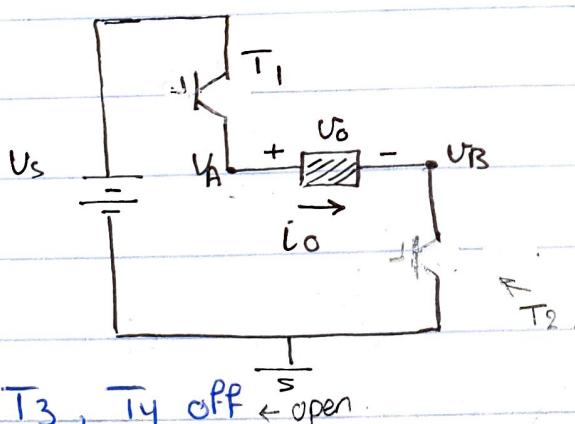


$T_1, T_2 \text{ ON}$.

$D_1, D_2, D_3, D_4 \text{ OFF}$.

$$V_A = V_s, V_B = 0$$

$$U_o = V_A - V_B = V_s$$

i_o builds up

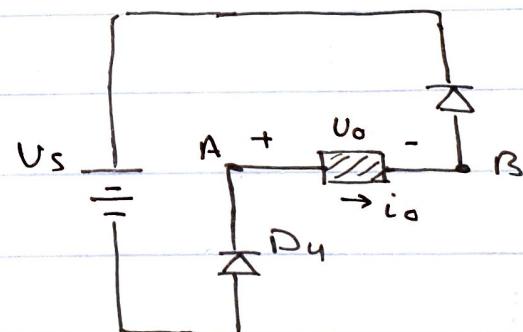

$D_1, D_3 \text{ OFF}$


$T_1, T_2, T_3, T_4 \text{ OFF}$

$$V_A = 0, V_B = V_s$$

$$U_o = -V_s$$

i_o decays.

$i_o < 0$.

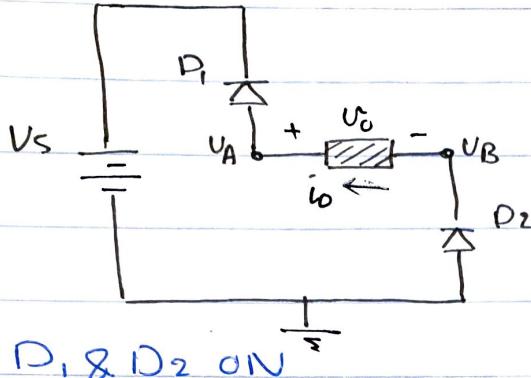

D₁ & D₂ ON


D₃ & D₄ OFF

T₁, T₂, T₃, T₄ OFF

$$u_A = u_s, u_B = 0.$$

$$u_o = u_A - u_B = u_s.$$

i_o decays.

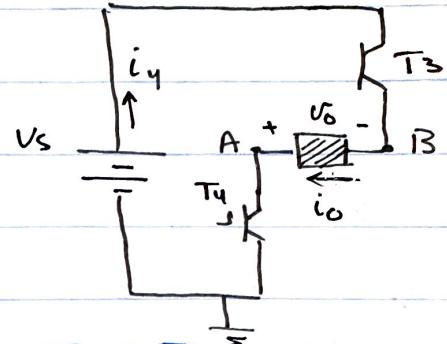

T₃ & T₄ ON

T₁ & T₂ OFF

D₁, D₂, D₃, D₄ OFF

$$u_A = 0, u_B = u_s$$

$$u_o = -u_s$$

i_o builds up.

Possible switching states.

$\frac{u_-}{I_+}$	$\frac{u_+}{I_+}$
$\frac{u_-}{I_-}$	$\frac{u_+}{I_-}$

Quadrant. i_o u_o T₁ T₂ T₃ T₄ D₁ D₂ D₃ D₄

I	+ +	1 1 0 0 0 0 0 0 0	I
	+ 0 _{SC}	1 0 0 0 0 0 0 1 0	
	+ 0	0 1 0 0 0 0 0 0 1	
	- +	0 0 0 0 1 1 0 0 0	

IV	- 0	0 0 0 1 0 1 0 0 0	IV
	- 0	0 0 1 0 1 0 0 0	
	- -	0 0 1 1 0 0 0 0	

III	- 0	0 0 0 1 0 1 0 0 0	III
	- 0	0 0 1 0 1 0 0 0	
	+ -	0 0 0 0 0 0 1 1	

II	+ 0	1 0 0 0 0 0 1 0	II
	+ 0	0 1 0 0 0 0 0 1	

- The average value of U_A is V_A

$$V_A = S_A U_s$$

where S_A is the duty cycle of leg A or T_1

The average value of U_B is V_B

$$V_B = S_B U_s$$

↳ duty cycle of leg B or T_3

Switching strategies :


1. PWM with bipolar switching

$(T_1 \& T_2)$ & $(T_3 \& T_4)$ are related as pairs

2. PWM with unipolar switching

Each leg is operated independently.

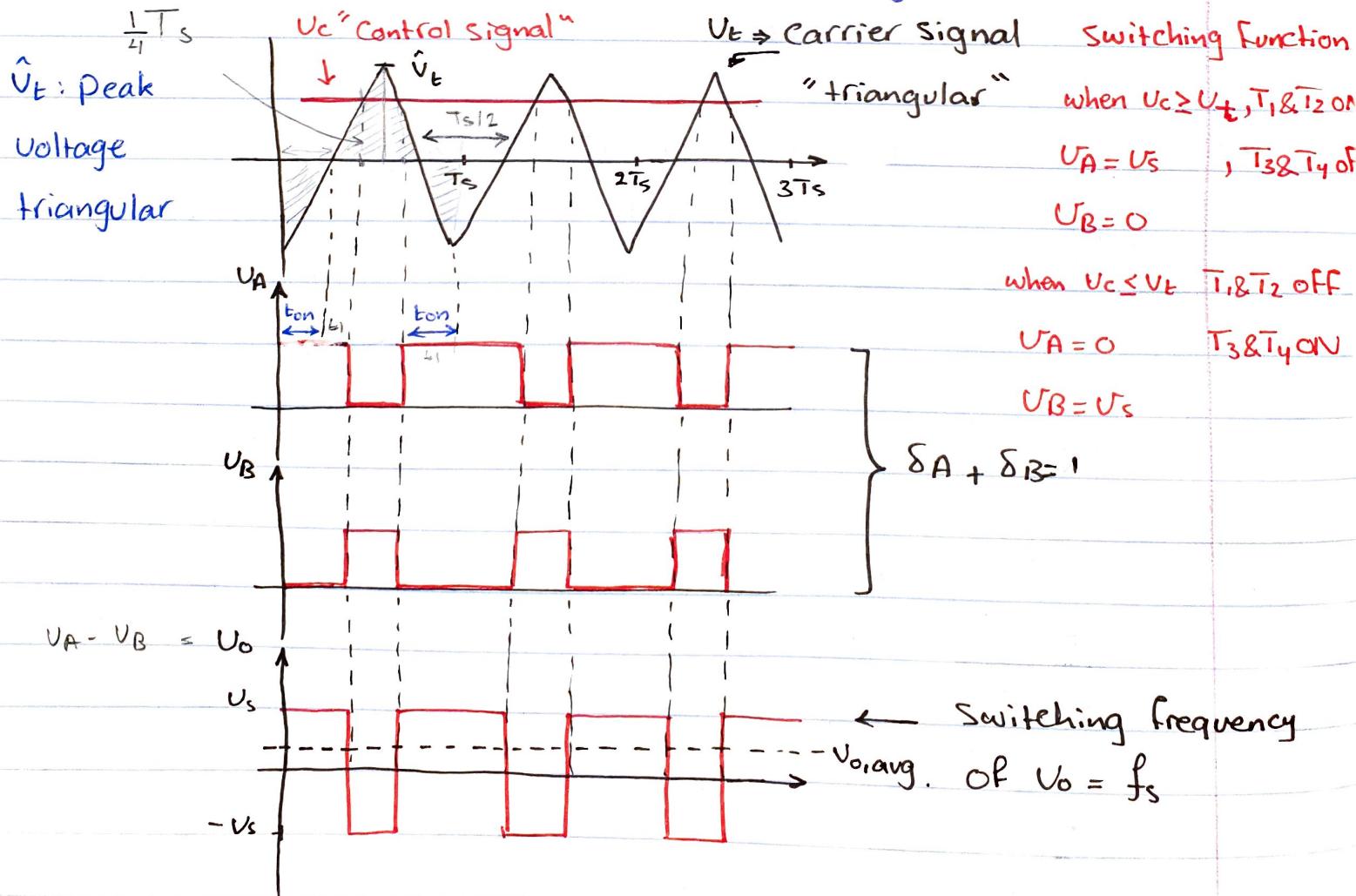1. Output voltage with bipolar switching .



$$V_o = U_A - U_B$$

$$V_o = (\delta A - \delta B) V_s \quad \delta A + \delta B = 1$$

$$V_o = (\delta A - (1 - \delta A)) V_s$$

$$V_o = (2\delta A - 1) V_s$$

$$0 \leq \delta A \leq 1 \Rightarrow -V_s \leq V_o \leq V_s$$

- Note: when $\delta A = 0.5 \Rightarrow V_o = 0$.

$\Rightarrow V_o$ square wave.

\Rightarrow The converter operates as 1- ϕ inverter in square-wave mode.

$\frac{1}{4} T_s$ from the Output voltage with bipolar switching.


$$t_{on} = t_1 + t_1 + \frac{T_s}{2} = 2t_1 + \frac{T_s}{2}$$
$$\frac{t_1}{(\frac{T_s}{4})} = \frac{U_c}{\hat{U}_E} \Rightarrow t_1 = \frac{T_s}{4} \frac{U_c}{\hat{U}_E}$$

$$\frac{U_c}{V_o} = \frac{\hat{U}_E}{V_s}$$

$$t_{on} = \frac{T_s}{2} \frac{U_c}{\hat{U}_E} + \frac{T_s}{2}$$

$$\delta A = \frac{t_{on}}{T_s} = \frac{1}{2} \left(1 + \frac{U_c}{\hat{U}_E} \right)$$

$$U_c = (2\delta A - 1) \hat{U}_E$$

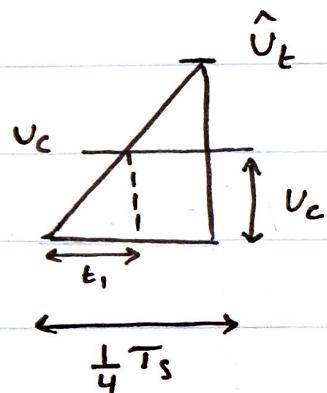

2. Output Voltage with unpolar switching.

switching Function:

when $U_C \geq U_T \Rightarrow T_1$ is ON

$U_A = U_S$ T_4 is OFF

when $U_C \leq U_T \Rightarrow T_1$ is OFF

$U_A = 0$ T_4 is ON

leg A


When $-U_C \geq U_T \Rightarrow T_3$ is ON

$U_B = U_S$ T_2 is OFF

When $-U_C \leq U_T \Rightarrow T_3$ is OFF

$U_B = 0$. T_2 is ON

leg B

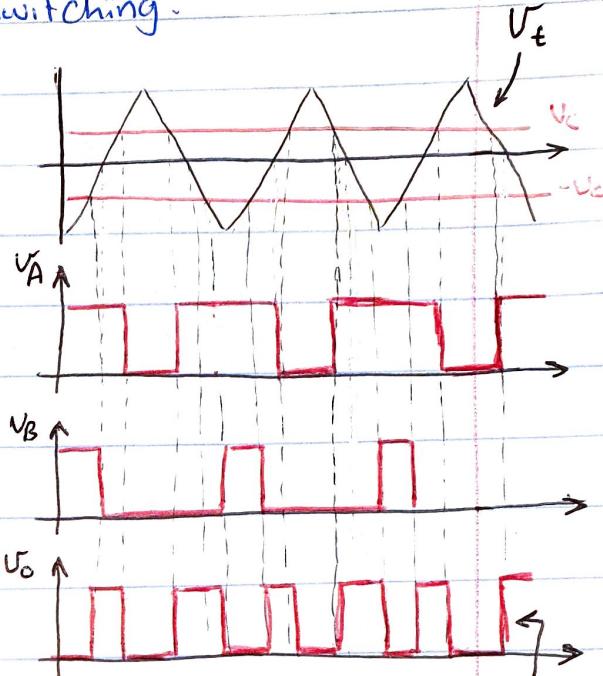

effective switching freq. = $2f_s \Rightarrow$ lower

- Classifications of chopper circuits "Buck converter".

THD

Quadrants of

$i_o \leftarrow$ Torque.



Quadrant operation.

operation
(DC machine)

	T_1 or T_2 ON	T_1, T_2 VS T_1 or T_2 OFF
$i_o < 0$	II (RR)	I (FM)
$i_o > 0$	III (RM)	IV (FR)

- I Forward Motoring (FM).
- IV Forward Regeneration (FR).
- III Revers Motoring (RM).
- II Revers Regeneration (RR).

- Class A.

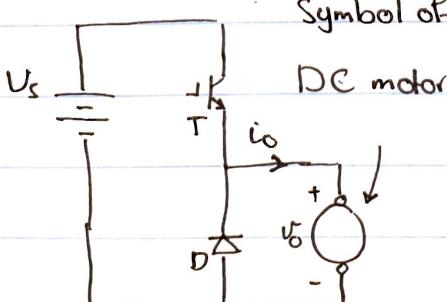
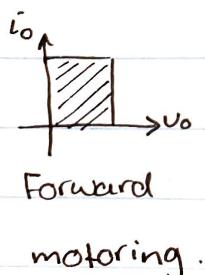


Symbol of

DC motor


Power Flow: Source \rightarrow load.

- Class B

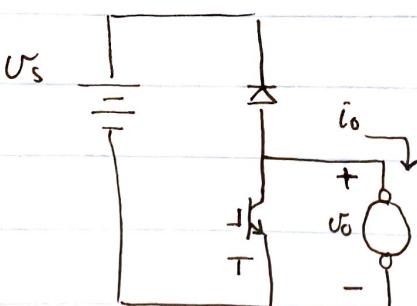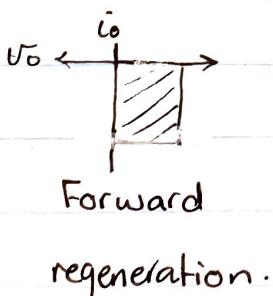


Power Flow: Source \leftarrow load

- Class C:

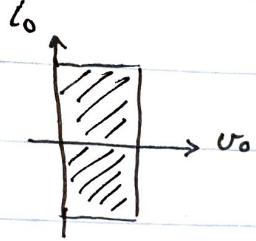

Forward motoring &
Forward regeneration.

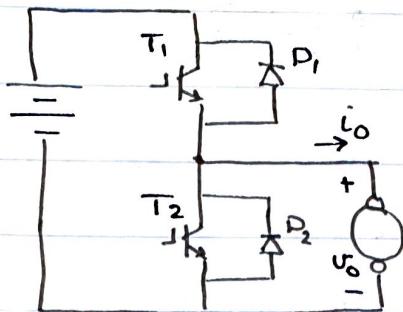


Half-bridge

DC-DC Converter.


Power Flow: Source \rightleftharpoons Load

- Class D:

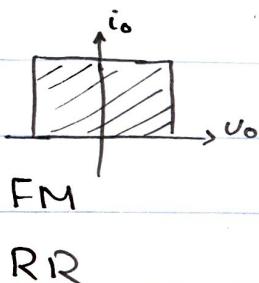

FM

RR

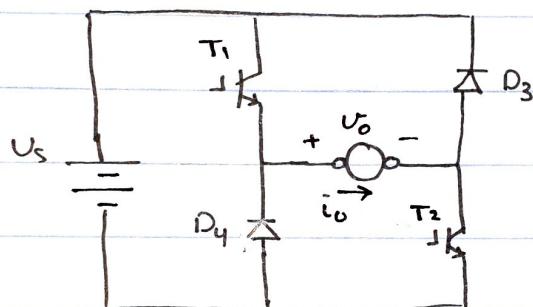


$$\begin{aligned} v_s (-) &\geq 0 \rightarrow T_2 \text{ ON} \\ v_s (+) &\geq 0 \rightarrow T_1 \text{ ON} \end{aligned}$$


$$T_1 \text{ or } T_2 \text{ ON} \leftarrow 0 = V_o \text{ SWL}$$

Power Flow: Source \rightleftharpoons Load.

- Class E:


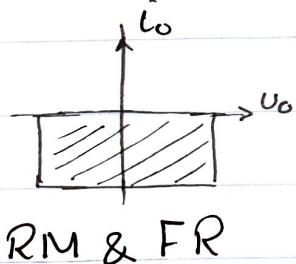


RM & FR

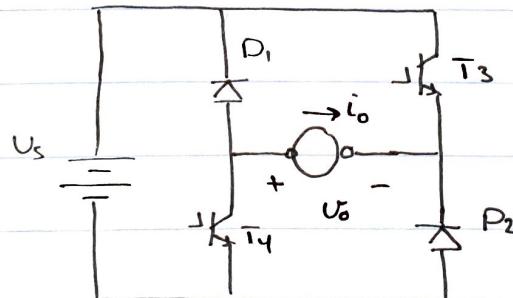


Power Flow: Source \rightleftharpoons Load.

- Class F:

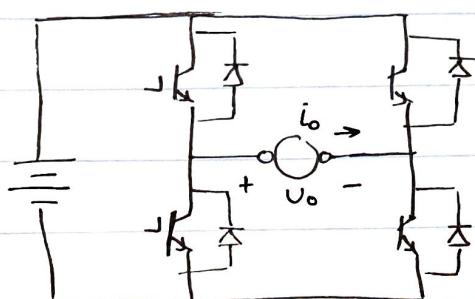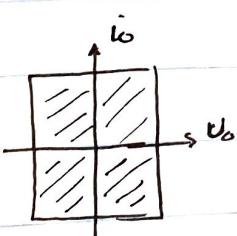

- Example.

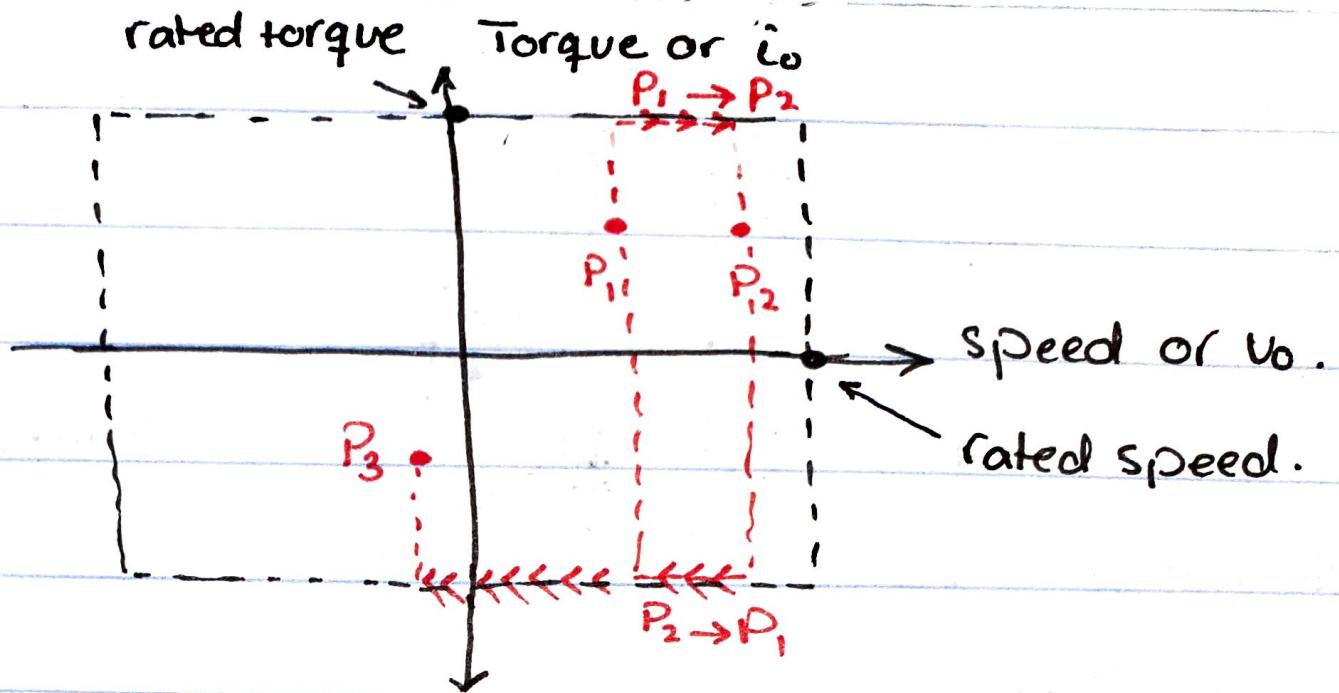


{ Rated نُوكِي مُنْهَج يَتَّبَعُ
 Nominal على هذِهِ القيمة للأداء

Maximum { Rated (أقصى قدرة) قيم تَتَّبَعُ على
 Nominal لعمليات وقفزة

- Chapter 6: DC-AC Converters "Inverters".

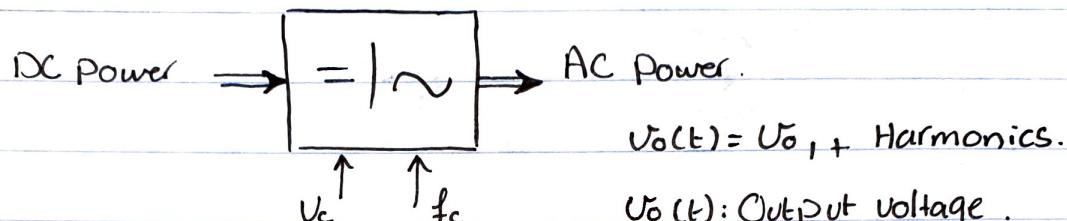The Function of the inverter is to convert the DC Power into AC Power with variable voltage & variable frequency (VVVF).



U_0 : Fundamental Component.

- Types of inverters:

1. Voltage Source Inverter (VSI).

2. Current Source Inverter (CSI).

- Applications:

• AC Machine Drive.

• Renewable Energy PV & wind turbines.

- Modulation Schemes:


a. Square-wave.


b. Sinusoidal Pulse Width Modulation (SPWM).

c. Delta or Hysteresis Modulation.

d. Space Vector Modulation (SVM).

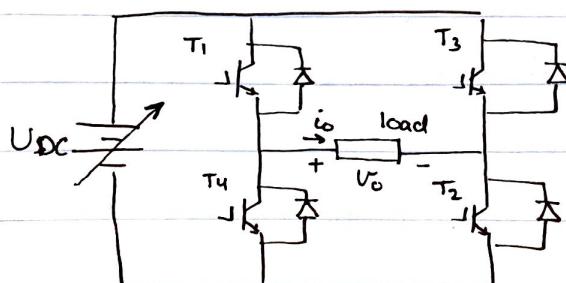1.1 - 1-Φ Voltage Source Inverter Full-bridge "square wave".




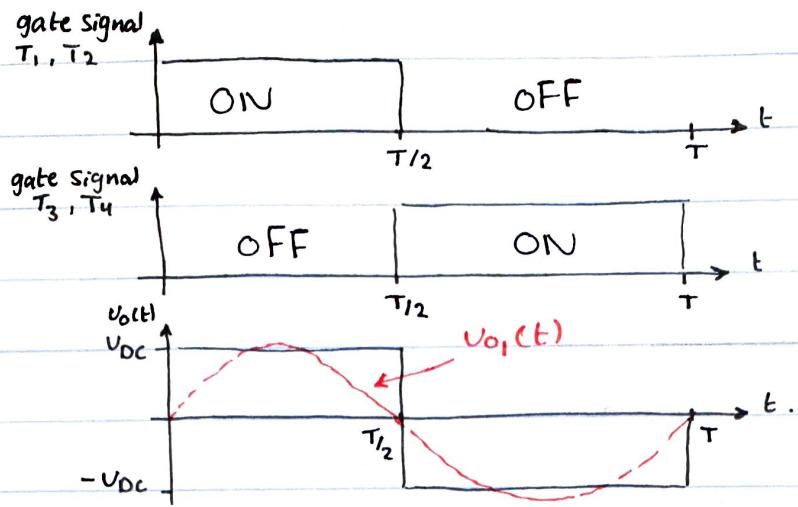


- Using Fourier series, the magnitude of the Fundamental at the Output and its harmonics are:

$$\hat{U}_{0,h} = \frac{4}{\pi h} U_{DC}$$

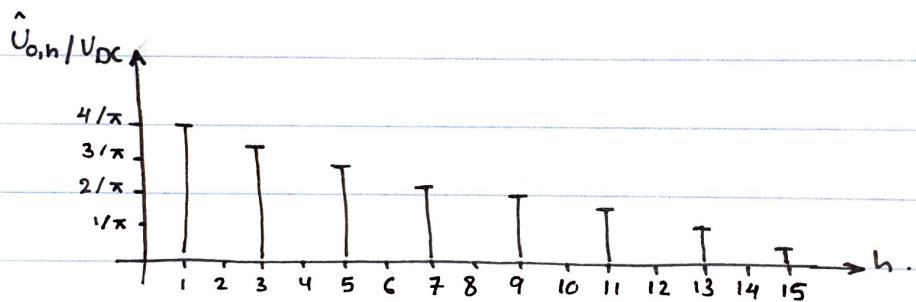Where ; h is the harmonic number. $h = \text{odd integer}$.




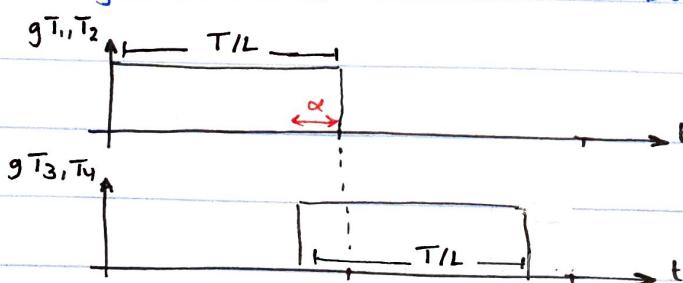- Note: The frequency of $U_{0i}(t)$ is controlled by changing ($T = 1/f$) of the gate signal.
- The voltage is controlled by varying U_{DC} . This can be done by Using uncontrolled rectifiers with buck converters or controlled rectifiers



Single phase VSI Voltage

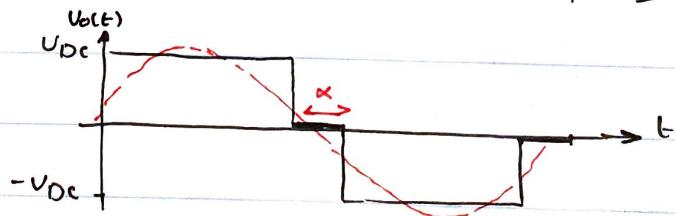Cancellation Method for
Square wave mode.



- Using Fourier Series,

$$\hat{U}_{0,h} = \frac{4}{\pi h} V_{DC} \sin(\beta h)$$


$$\beta = 90^\circ - \frac{\alpha}{2}$$

- Note:

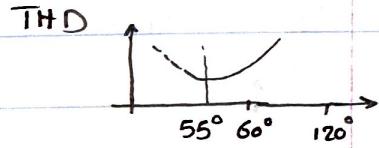1. IF $\alpha = 60^\circ \Rightarrow \beta = 60^\circ \Rightarrow \hat{U}_{0,h} = \frac{4}{\pi h} \sin(60h) \Rightarrow \text{No triplen harmonics}$
 $3, 9, 15, 21, 27, \dots$



$h = 3 \times \text{odd number}$

$$\hat{U}_{0,3} = 0, \hat{U}_{0,9} = 0, \hat{U}_{0,15} = 0, \dots$$



2. THD_{\min} is achieved when $\alpha = 55^\circ$

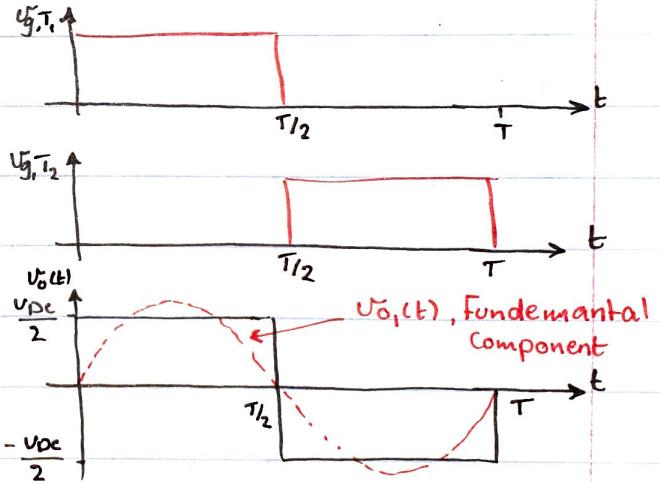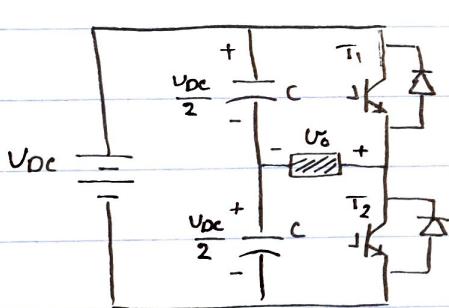
1.2. 1- ϕ VSI "Half-bridge" square wave mode.



- Using Fourier series, the peak value of the fundamental of the output and its harmonics are:

$$\hat{U}_{0,h} = \frac{4}{\pi} \frac{V_{DC}}{2} \cdot \frac{1}{h}, \quad \hat{U}_{0,1} = \frac{4}{\pi} \cdot \frac{V_{DC}}{2} = \frac{2}{\pi} V_{DC}$$


Where h is the harmonic order (odd).

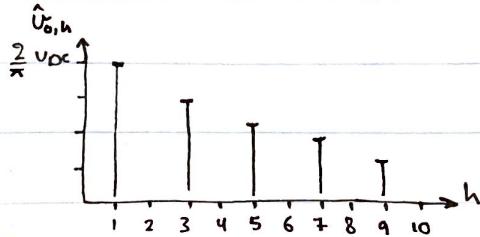


$$\text{THD}_v = \sqrt{\frac{\sum_{h=3,5,\dots} \hat{U}_{0,h}^2}{\hat{U}_{0,1}^2}}$$

Frequency spectrum.


1-3. 3-Φ USI "Square wave Mode".

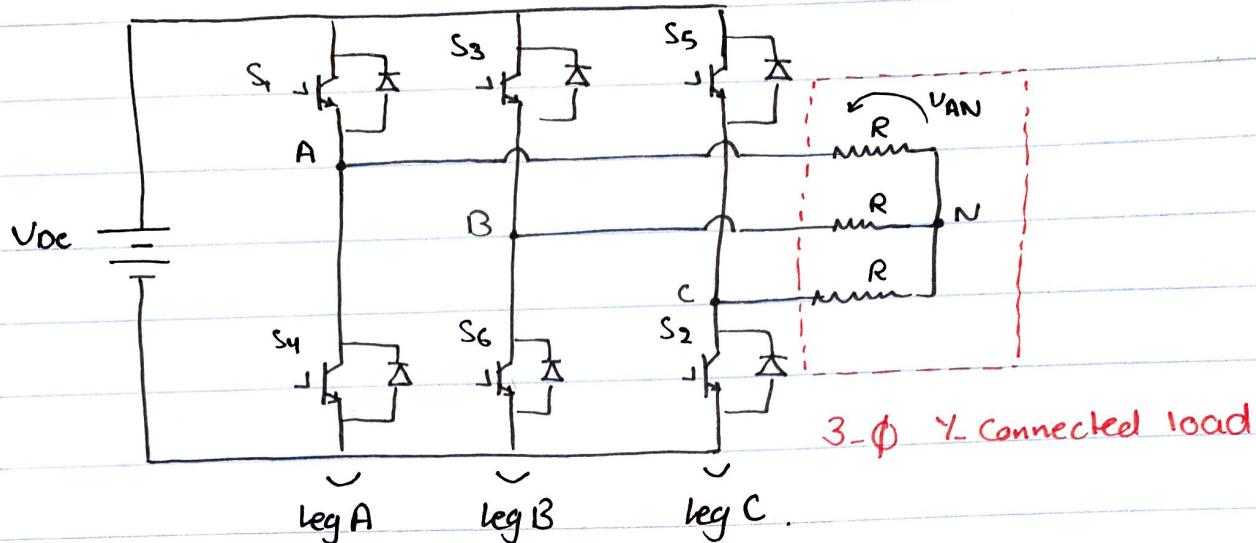

- gate-Signal.

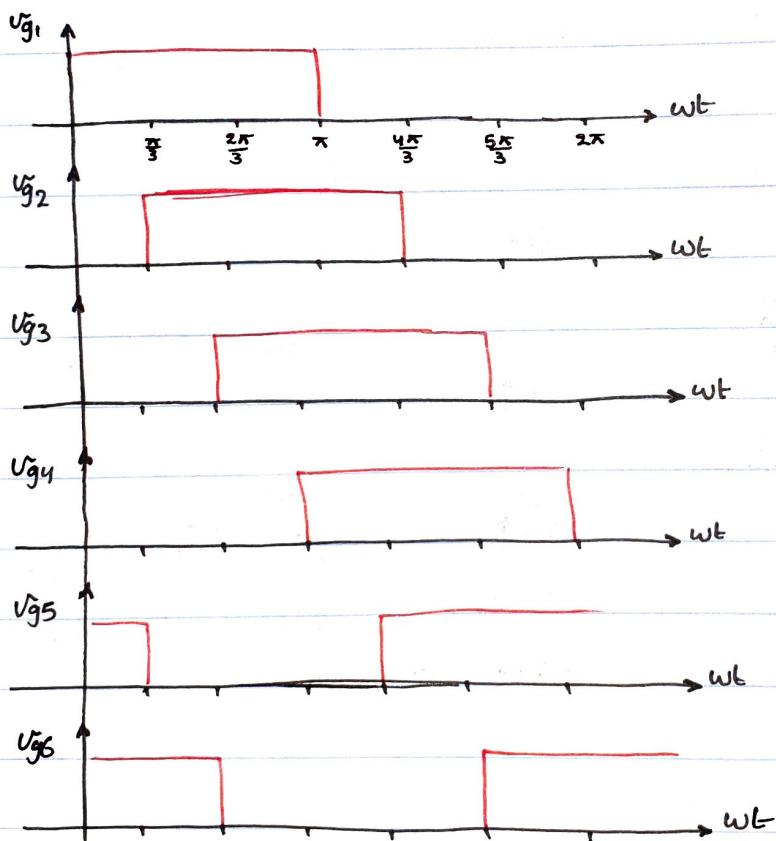


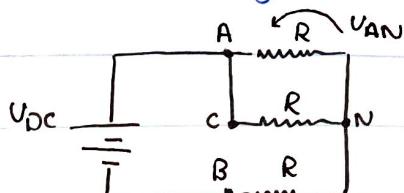$0 \leq wt \leq \frac{\pi}{3}$, S_1, S_5, S_6 are ON




$$U_{AN} = \frac{R_{12}}{R_{12} + R} V_{DC} \Rightarrow U_{AN} = \frac{V_{DC}}{3}$$

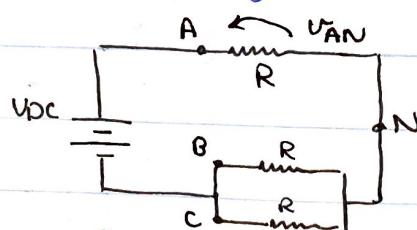$\frac{\pi}{3} \leq wt \leq \frac{2\pi}{3}$, S_1, S_2, S_6 are ON




$$U_{AN} = \frac{R}{R + R_{12}} \cdot V_{DC} \Rightarrow U_{AN} = \frac{2}{3} V_{DC}$$

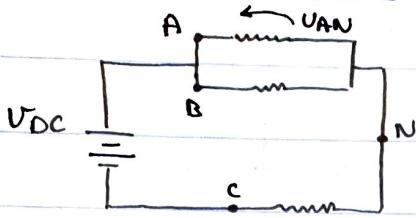$\frac{2\pi}{3} \leq wt \leq \pi$, S_1, S_2 & S_3 are ON




$$U_{AN} = \frac{R/12}{R/12 + R} \cdot V_{DC} \Rightarrow U_{AN} = \frac{V_{DC}}{3}$$

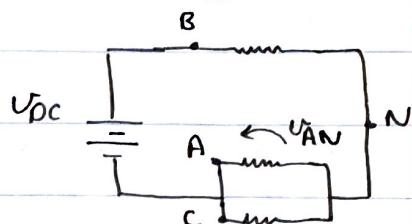$\pi \leq wt \leq \frac{4\pi}{3}$, S_2, S_3 & S_4 are ON




$$U_{AN} = \frac{R/12}{R/12 + R} (-V_{DC}) \Rightarrow U_{AN} = -\frac{V_{DC}}{3}$$

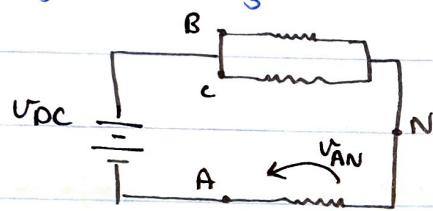$\frac{4\pi}{3} \leq wt \leq \frac{5\pi}{3}$, S_3, S_4 & S_5 are ON



$$U_{AN} = \frac{R}{R/12 + R} (-V_{DC}) \Rightarrow U_{AN} = -\frac{2}{3} V_{DC}$$

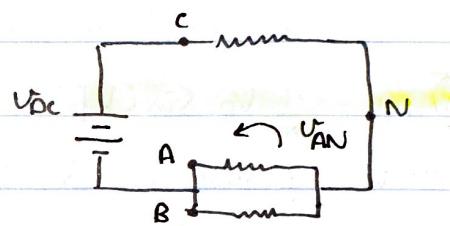$\frac{5\pi}{3} \leq wt \leq 2\pi$, S_4, S_5 & S_6 are ON



$$U_{AN} = \frac{R/12}{R/12 + R} (-V_{DC}) \Rightarrow U_{AN} = -\frac{1}{3} V_{DC}$$

- State Conducting Period Conducting Devices U_{AN}

1 $0 \leq wt \leq \frac{\pi}{3}$ S_1, S_5, S_6 $V_{DC}/3$



2 $\frac{\pi}{3} \leq wt \leq \frac{2\pi}{3}$ S_1, S_2, S_6 $2V_{DC}/3$

3 $\frac{2\pi}{3} \leq wt \leq \pi$ S_1, S_2, S_3 $V_{DC}/3$

4 $\pi \leq wt \leq \frac{4\pi}{3}$ S_2, S_3, S_4 $-V_{DC}/3$

5 $\frac{4\pi}{3} \leq wt \leq \frac{5\pi}{3}$ S_3, S_4, S_5 $-2V_{DC}/3$

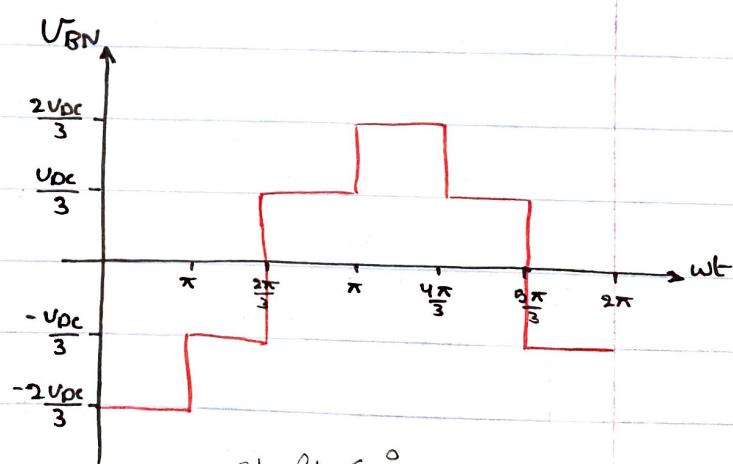
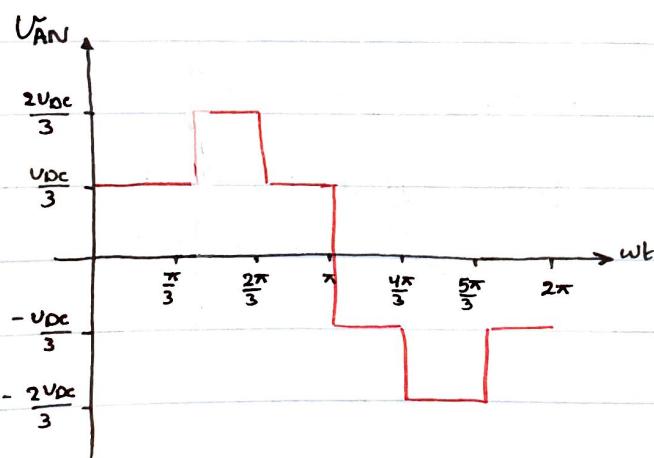
6 $\frac{5\pi}{3} \leq wt \leq 2\pi$ S_4, S_5, S_6 $-V_{DC}/3$



Shift 60°

by 60°

\bar{U}_{AB} : Line-to-Line Voltage.

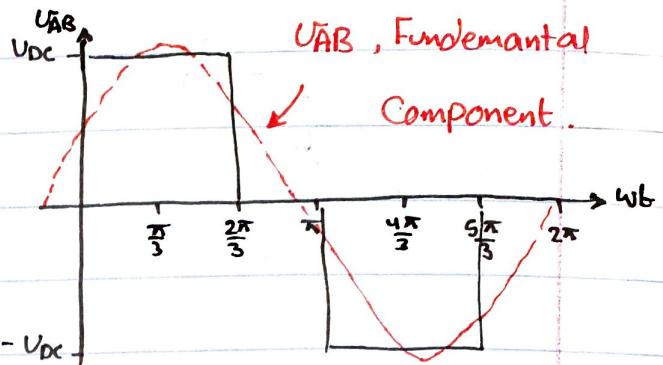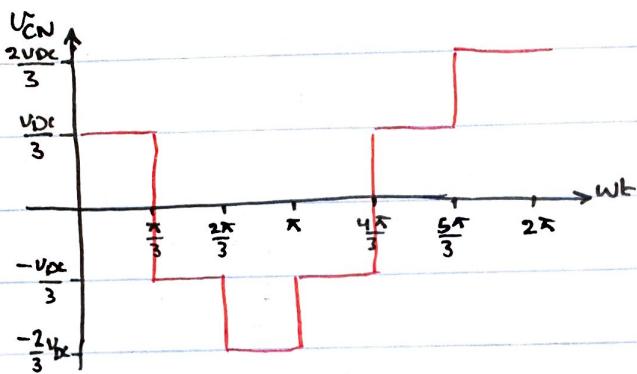

Using Fourier Series, the peak value of the Fundamental at Line-Line output & its harmonics are:

$$\hat{V}_{LL,h} = \frac{4}{\pi} V_{DC} \sin(h\beta) ; \beta = 90 - \frac{\pi}{2}, h \text{ is odd.}$$


$$\hat{V}_{LL,h} = \frac{4}{\pi} V_{DC} \sin(60h), \alpha \text{ is } 60^\circ. \quad \hat{V}_{LL,h} = \frac{\sqrt{3}}{h} \left(\frac{1}{\pi} V_{DC} \right), h = 6m + 1$$

$$\hat{V}_{LL,1} = \frac{2\sqrt{3}}{\pi} V_{DC} \Rightarrow V_{LL,1, RMS} = \frac{\hat{V}_{LL,1}}{\sqrt{2}}$$

$\hat{V}_{LL,1}$: Peak of the main component.

$\Delta 220 \text{ V } 2\sqrt{3} \text{ A } 50 \text{ Hz.}$


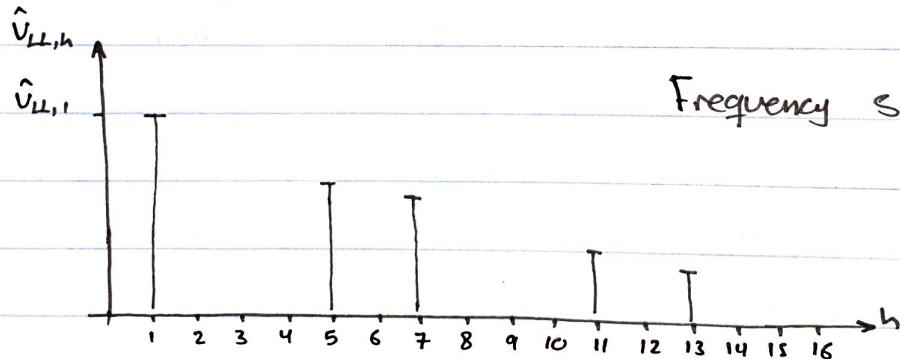
$$\hat{V}_{LL,1, RMS} = \frac{\sqrt{6}}{\pi} V_{DC}.$$



Frequency spectrum.

2. Hysteresis or Delta Modulation.


"Instantaneous Current Controller".

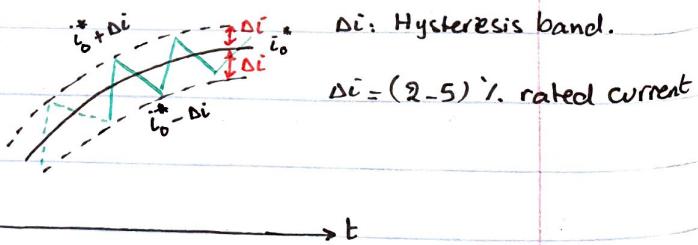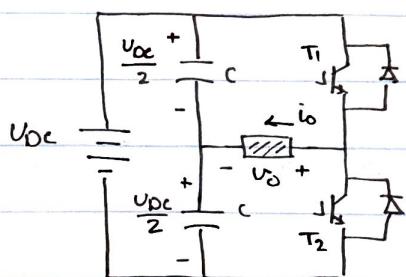


reference current i_o^*

Actual Current i_o
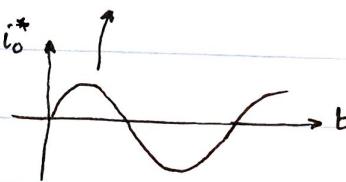
$$i_o^* = I_m \sin(\omega t + \theta_c)$$




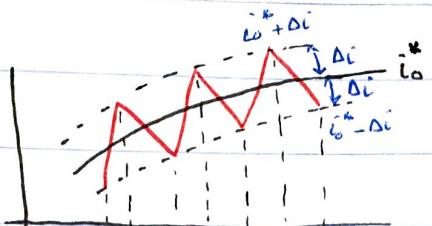

Δi : Hysteresis Band,

$\Delta i = (2-5)\%$ rated current.

- Switching Function.

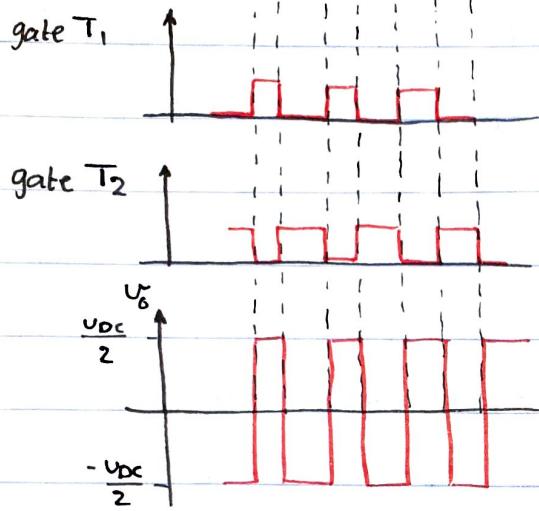


IF $i_o \leq i_o^* - \Delta i$ set $U_o = \frac{U_{DC}}{2}$, T_1 is ON.

IF $i_o \geq i_o^* + \Delta i$ Reset $U_o = -\frac{U_{DC}}{2}$, T_2 is ON.


- Implementation of hysteresis Current Controller

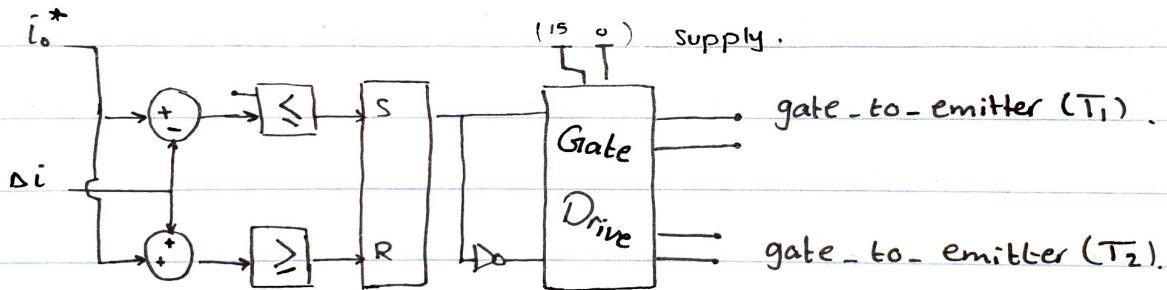- Implementation of hysteresis Current Controller.




3. Sinusoidal pulse width Modulation (SPWM).

3.1. 1-φ Half-bridge VSI (SPWM).

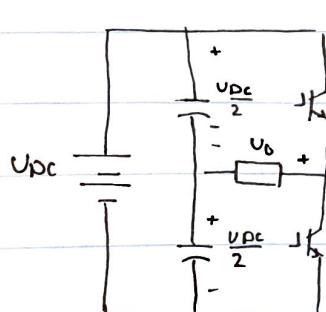

V_C , control signal or modulating wave.

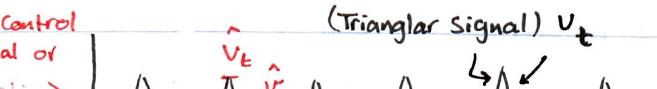

(Triangular signal) V_E


- switching Function:

• IF $V_C > V_E \Rightarrow T_1$ is ON

& $U_o = \frac{U_{DC}}{2}$

else $\Rightarrow T_2$ is ON &

$U_o = -\frac{U_{DC}}{2}$

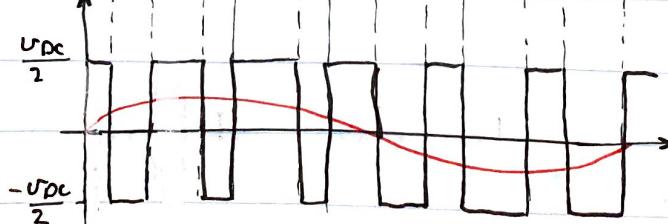

- Fundamental component of $U_O(t)$

- The output voltage is given by (using Fourier Series).

$$U_0(t) = U_{01}(t) + \text{Harmonics}.$$

$$U_{01}(t) = M \frac{U_{DC}}{2}.$$

where; M is called the modulation index and it is defined as the ratio between the peak value of U_t , \hat{U}_t and the peak value of the modulating wave, \hat{U}_c .

$$M = \frac{\hat{U}_c}{\hat{U}_t}$$

T_s : Switching Period. $f_s = \frac{1}{T_s}$: switching frequency or carrier frequency.

T : period of modulating wave.

$\omega_1 = 2\pi f_1 = 2\pi/T$, f_1 : Frequency of modulating wave.

- Frequency modulating; m_f : It is the ratio of switching frequency to the fundamental frequency, $m_f = f_s/f_1$. [Integer].
- The harmonics of $U_0(t)$ appear of sidebands of switching frequency and its multiples.

$$f_h = (n m_f \pm k) f_1$$

n & m are integer; For even values of k , n is odd.


For odd values of k , n is even.

$$m_f, m_f \pm 2, m_f \pm 4, m_f \pm 6, \dots$$

$$2m_f \pm 1, 2m_f \pm 3, 2m_f \pm 5, 2m_f \pm 7, \dots$$


$$3m_f, 3m_f \pm 2, 3m_f \pm 4, 3m_f \pm 6, \dots$$

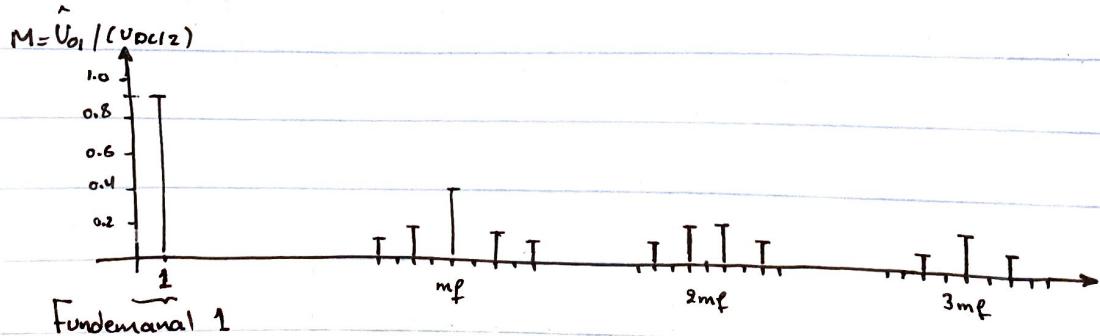- m_f : Integer, & odd number to eliminate the even harmonics.




- Notes:

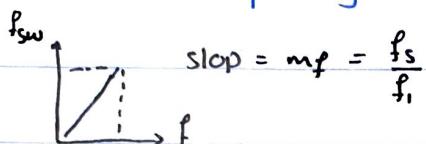1. m_f should be odd integer to eliminate the even harmonics from $V_o(t)$.
2. When m_f is small ($m_f \leq 21$), the switching Frequency must be changed with load Frequency, f_l , to keep m_f constant ($m_f = f_s/f_l = \text{constant}$).



Synchronous SPWM

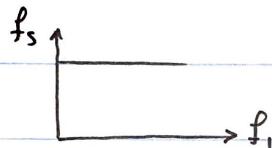3. For large value of m_f ($m_f \geq 21$) the synchronous SPWM is not important.



4. If m_f is high number, the THD is small. However, the switching losses of the Converter will become high (efficiency ↓).


- Over-modulation.

When $M \leq 1$, the relation between \hat{V}_{o1} & V_{DC12} is linear relationship.

$$\hat{V}_{o1} = M \frac{V_{DC}}{2}$$




When $1 \leq M \leq 3.24$, the THD of $V_o(t)$ is high. The region is called Overmodulation region.

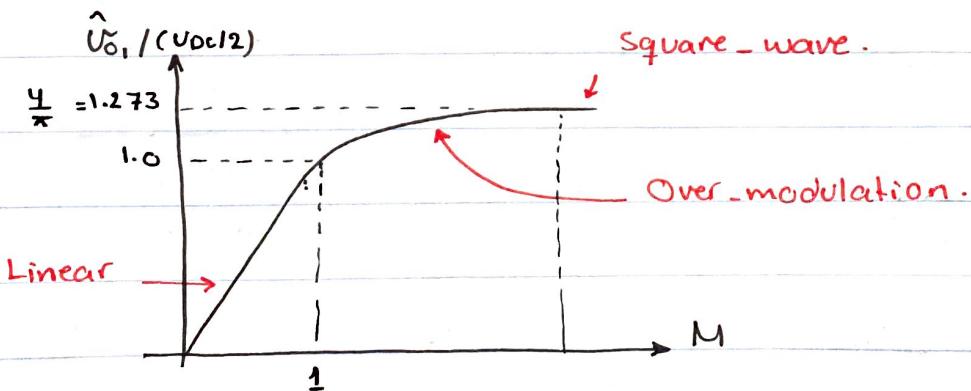When $M \geq 3.24$, we will get square wave output voltage.



- Switching and Conduction in a Controllable switch.
- Real devices do not have ideal characteristic and dissipate power when used.
- Too much power dissipated may lead to the destruction of the device.
- Sources of power dissipation.
 - Switching losses
 - Conduction Losses.

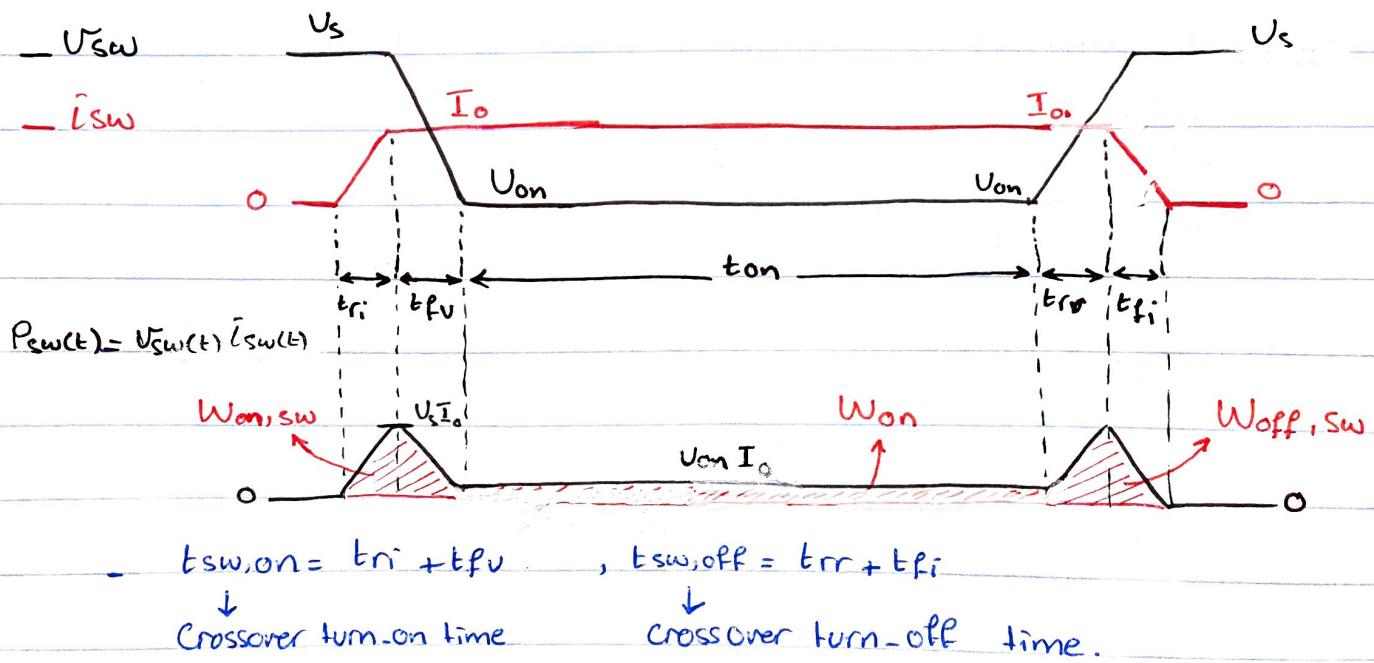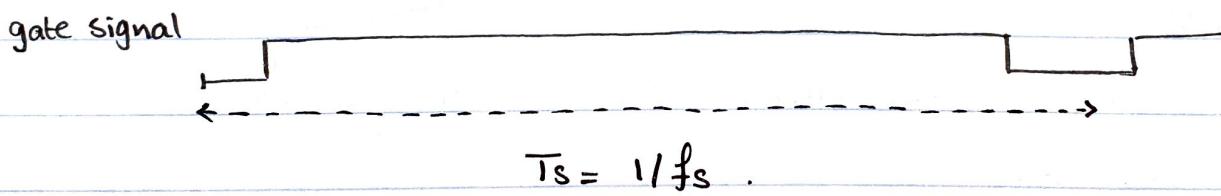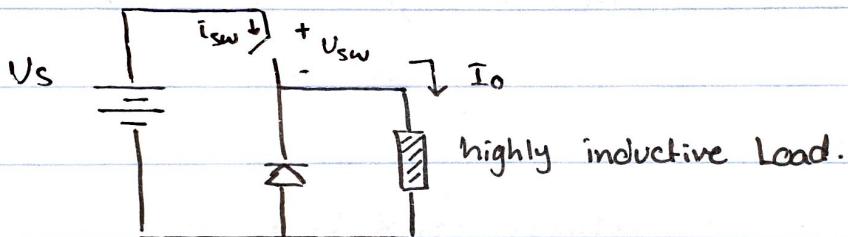Power dissipation in a chopper switch with inductive load.



$$W_{on,sw} = \frac{1}{2} t_{sw,on} U_s I_o$$

$$W_{off,sw} = \frac{1}{2} t_{sw,off} U_s I_o$$


$$W_{sw} (\text{switching energy losses}) = \frac{1}{2} U_s I_o (t_{sw,on} + t_{sw,off})$$

$$W_{on} (\text{conduction energy losses}) = U_{on} I_o t_{on}$$


$$P_{on} (\text{conduction power losses}) = U_{on} I_o t_{on} f_s$$

$$P_{sw} (\text{switching power losses}) = \frac{W_{sw}}{T_s} = \frac{1}{2} U_s I_o f_s (t_{sw,on} + t_{sw,off})$$

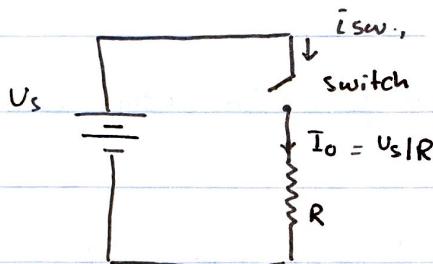- Power dissipation in a chopper switch with resistive load.



gate signal

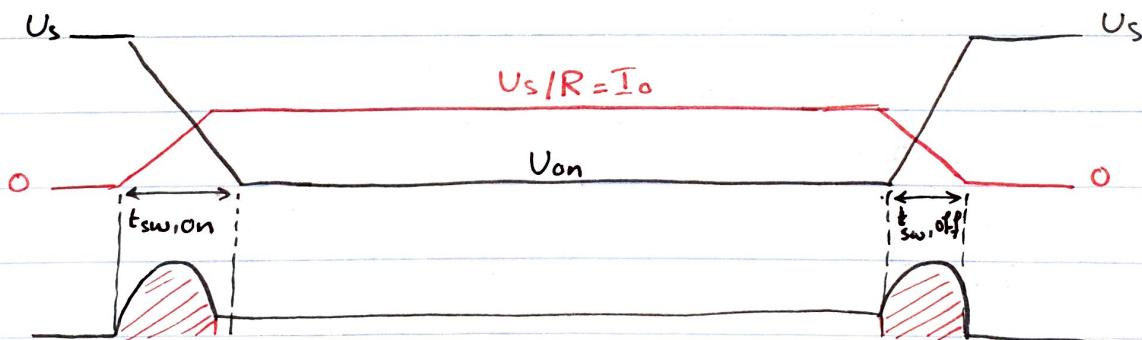

$$0 \leq t \leq t_{sw,on}$$

$$i_{sw} = I_o \frac{t}{t_{sw,on}}, \quad v_{sw} = U_s \left(1 - \frac{t}{t_{sw,on}}\right)$$

$$W_{on,sw} = \int_0^{t_{sw,on}} v_{sw} i_{sw} dt$$

$$W_{on,sw} = \frac{I_o U_s}{t_{sw,on}} \left(\frac{t_{sw,on}^2}{2} - \frac{t_{sw,on}^2}{3} \right) = I_o U_s \left(\frac{t_{sw:on}}{2} - \frac{t_{sw:on}}{3} \right)$$

$$W_{on,sw} = \frac{1}{6} U_s I_o t_{sw,on}$$

$$0 \leq t \leq t_{sw, off}$$

$$I_{sw} = I_o \left(1 - \frac{t}{t_{sw, off}} \right)$$

$$U_{sw} = U_s \frac{t}{t_{sw, off}}$$

$$W_{off, sw} = \int_0^{t_{sw, off}} U_{sw} I_{sw} dt.$$

$$W_{off, sw} = \frac{1}{6} U_s I_o t_{sw, off}.$$



$$W_{sw} = W_{sw, on} + W_{sw, off} = \frac{1}{6} U_s I_o (t_{sw, on} + t_{sw, off})$$

$$P_{sw} = \frac{W_{sw}}{T_s} = \frac{1}{6} U_s I_o f_s (t_{sw, on} + t_{sw, off}) = \frac{1}{3} P_{sw}$$



inductive load.


Note: Switching losses can be reduced using snubber circuit.

- Turn-off snubber circuit.

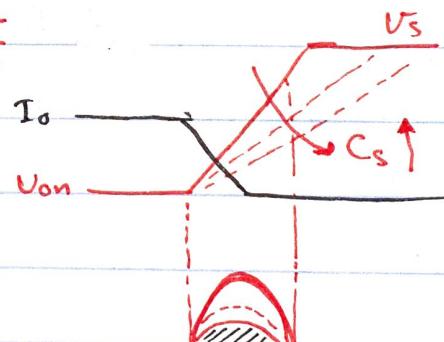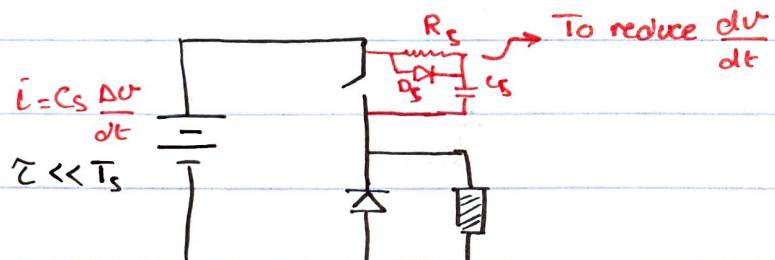

- Turn-on snubber circuit.

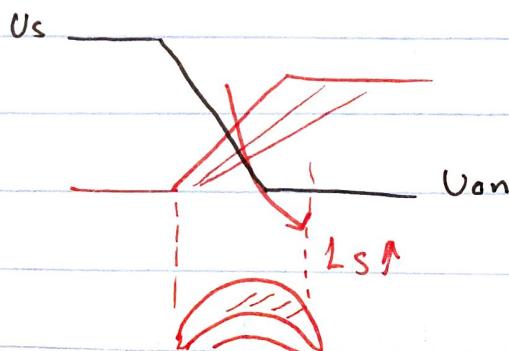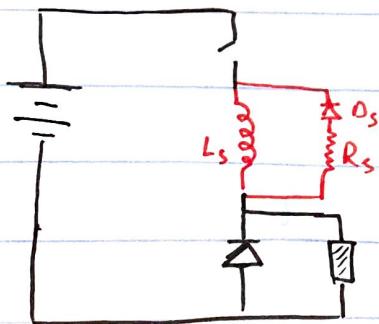

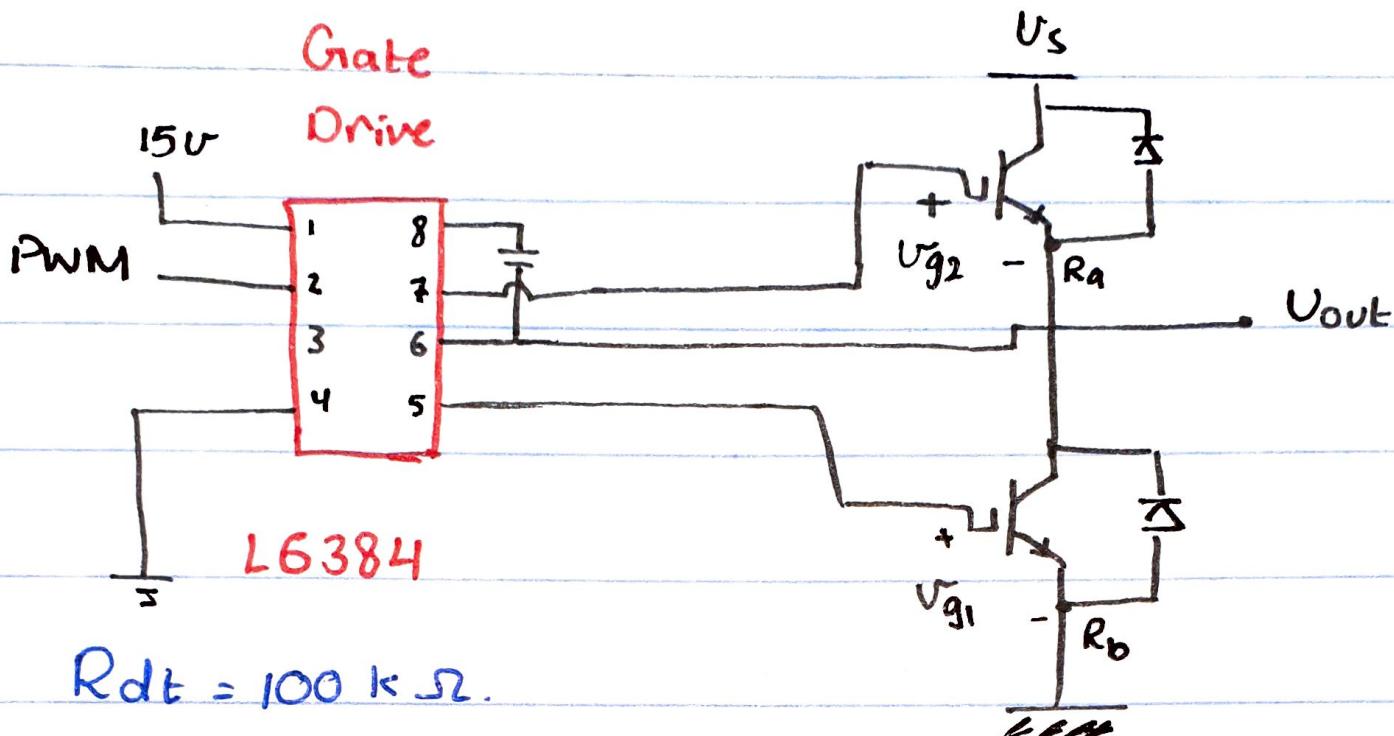

$$Rdt = 100 \text{ k}\Omega$$

Dead time = 1 μ sec.

- Function of gate drive.

Level shifting.

Dead time.

Voltage amplification.