



Faculty of Engineering and Technology  
Electrical and Computer Engineering Department  
Simulation Lab (ENEE4104)

## **Power Electronic Converters in Orcad**

---

Prepared By:

Name: Anas Tomaizeh

Number: 1152325

Instructor: Dr. Jamal seyam

TA: Eng. Ahmed Hamed

Date: 14/3/2019

Sec#: 1

## **1. Abstract:**

The aims of this prelab is to learn concept with Orcad.

## Table of Contents:

1. Series RLC Circuit: .....	3
1.1 The output voltage at the Capacitor: .....	3
2. Series RLC Circuit at Different value of R. ....	4

## List of Figures:

Figure 1: The Series RLC Circuit .....	3
Figure 2: The output voltage at the Capacitor.....	3
Figure 3: Parametric Analysis.....	4
Figure 4: The Output Voltage at Capacitor when the value of resistor variable .....	4

### 1. Series RLC Circuit:

The Circuit:

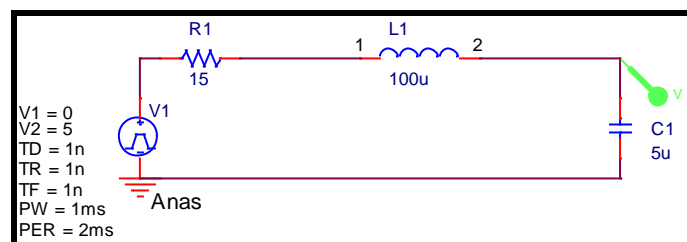


Figure 1: The Series RLC Circuit

#### 1.1 The output voltage at the Capacitor:

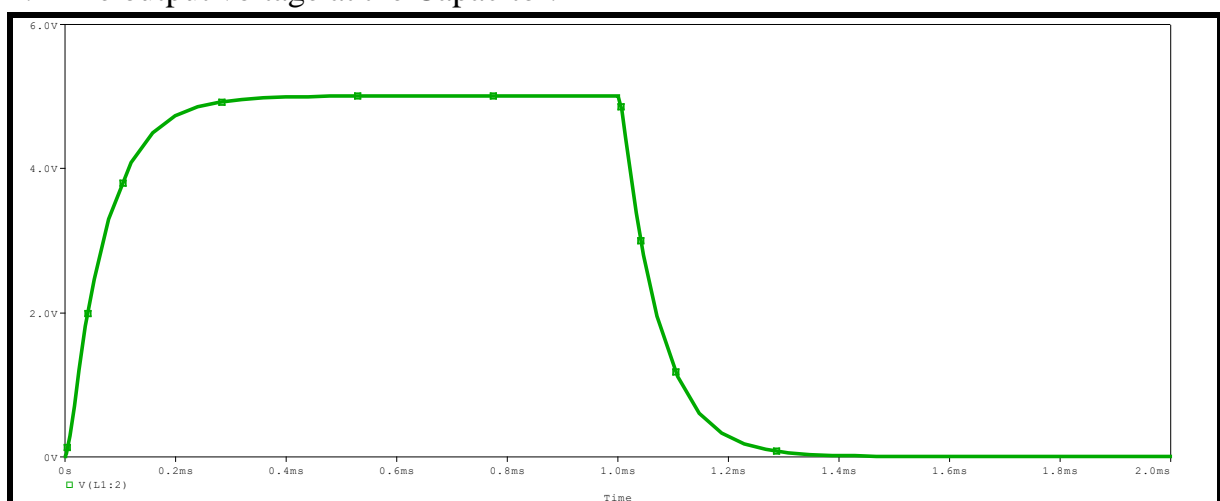


Figure 2: The output voltage at the Capacitor

## 2. Series RLC Circuit at Different value of R.

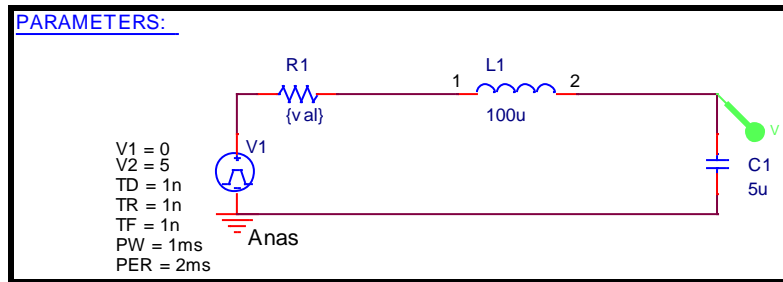


Figure 3: Parametric Analysis

The Value of resistor make the circuit critically damped oscillator:

$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$$

$$R = 8.944 \Omega$$

The simulation result:

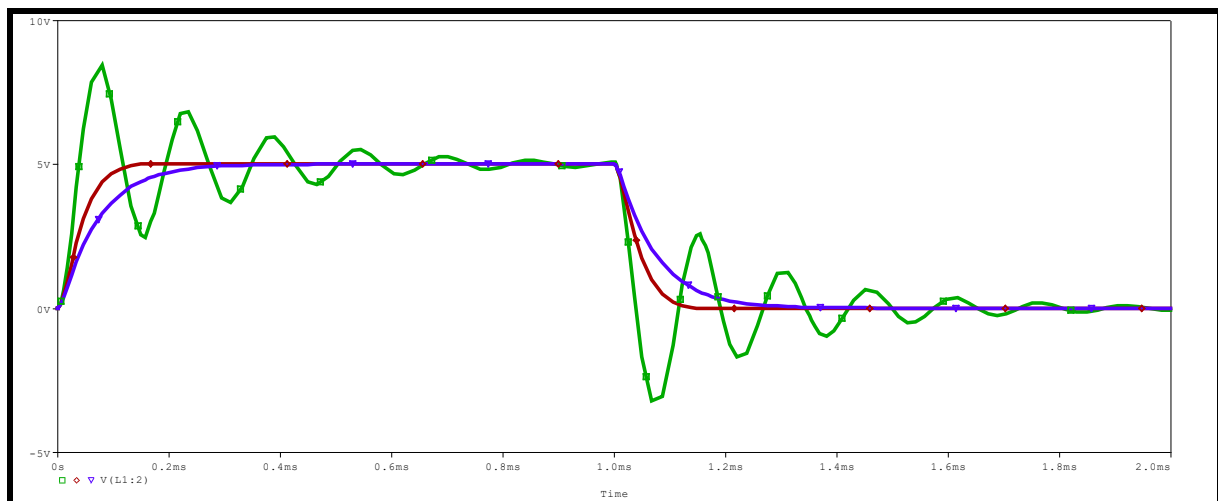


Figure 4: The Output Voltage at Capacitor when the value of resistor variable