



Faculty of Engineering and Technology
Electrical and Computer Engineering Department
Simulation Lab (ENEE4104)

Negative feedback, Modular design and sub-circuits using ORCAD

Prepared By:

Name: Anas Tomaizeh

Number: 1152325

Instructor: Dr. Jamal seyam

TA: Eng. Ahmed Hamed

Date: 27/2/2019

Sec#: 1

1. Abstract:

The aims of this prelab is to learn concept of modular design used ORCAD, to find the gain, input impedance, output impedance and bandwidth of close loop and open loop multistage amplifiers.

Table of Contents:

1. The Open-Loop Multistage amplifier with R=10K:	5
1.1 The gain of open loop multistage Amplifier:	5
1.2 The Input Impedance:	6
1.3 Output impedance:	6
1.4 The bandwidth:	7
2. The Open-Loop multistage amplifier with R=100 Ω	8
2.1 The Gain:	8
2.2 The B.W:	9
2.3The input impedance:	9
2.4 Output impedance:	10
3. The closed loop multistage amplifier at R=10K:	11
3.1 The Gain:	11
3.2The B.W:	12
3.3The input impedance:	12
3.4 The output impedance	13
4. The closed loop multistage amplifier at R=100:.....	13
4.1The gain.....	13
4.2 The B.W:.....	14
4.3 The input impedance	14
4.4 The output impedance:.....	15

List of Figures:

Figure 1: The Open-Loop Multistage Amplifier	5
Figure 2: The Gain of Open loop multistage amplifier at $R=10K\Omega$	5
Figure 3: The Input Impedance of open loop multistage amplifier at $R=10K\Omega$	6
Figure 4: the circuit used to find the Z_{out}	6
Figure 5: The output impedance	7
Figure 6: The B.W of open loop multistage amplifier at $R=10K\Omega$	7
Figure 7: open loop multistage amplifier at $r=100\ \Omega$	8
Figure 8: the gain of open loop multistage amplifier at $R=100\ \Omega$	8
Figure 9: The gain of open loop multistage amplifier at $R=100\Omega$	9
Figure 10: The input impedance of open loop multistage amplifier at $R=100\ \Omega$	9
Figure 11: the circuit used to find Z_{out}	10
Figure 12: The output impedance of multistage amplifier at $R=100\ \Omega$	10
Figure 13: close loop multistage amplifier at $R=10K$	11
Figure 14: The gain of close loop multistage amplifier at $R=10K$	11
Figure 15: The B.W of close loop multistage amplifier at $R=10K$	12
Figure 16: Z_{in} of closed loop multistage Amplifier at $R=10K$	12
Figure 17: Z_{out} of close loop multistage amplifier	13
Figure 18: The gain of close loop multistage amplifier at $R=100\ \Omega$	13
Figure 19: The B.W of close loop multistage amplifier at $R=100$	14
Figure 20: The input impedance of close loop multistage amplifier at $R=100\ \Omega$	14
Figure 21: Z_{out} of multistage amplifier	15

1. The Open-Loop Multistage amplifier with R=10K:

The Circuit:

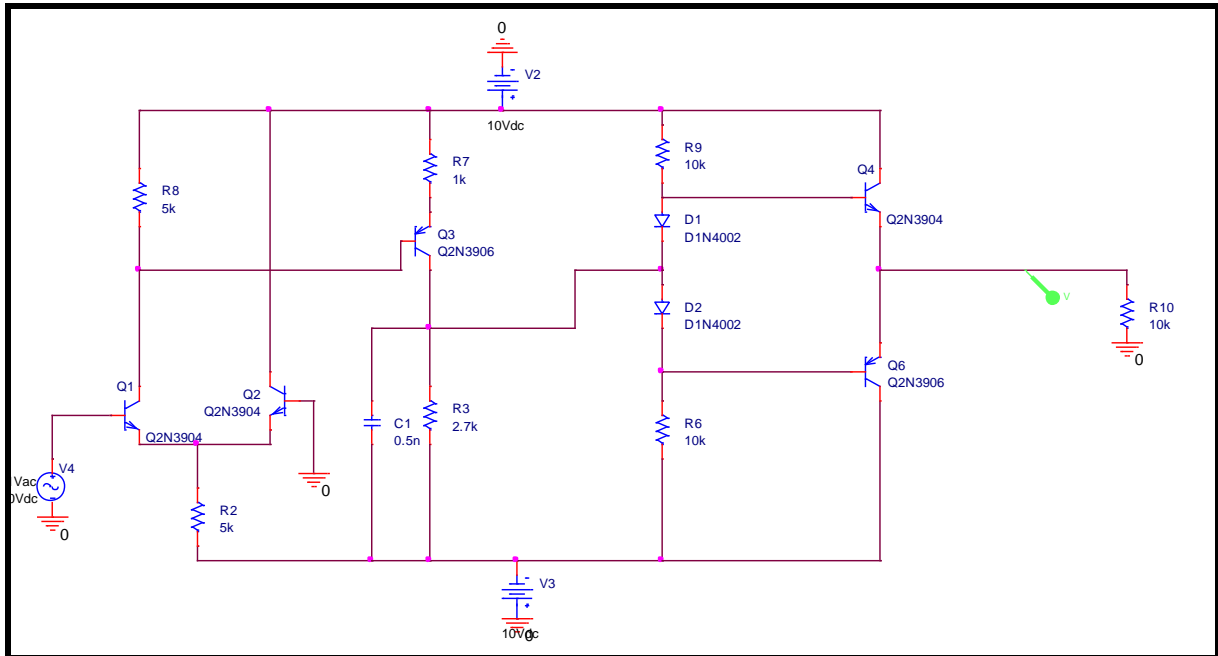


Figure 1: The Open-Loop Multistage Amplifier

1.1 The gain of open loop multistage Amplifier:

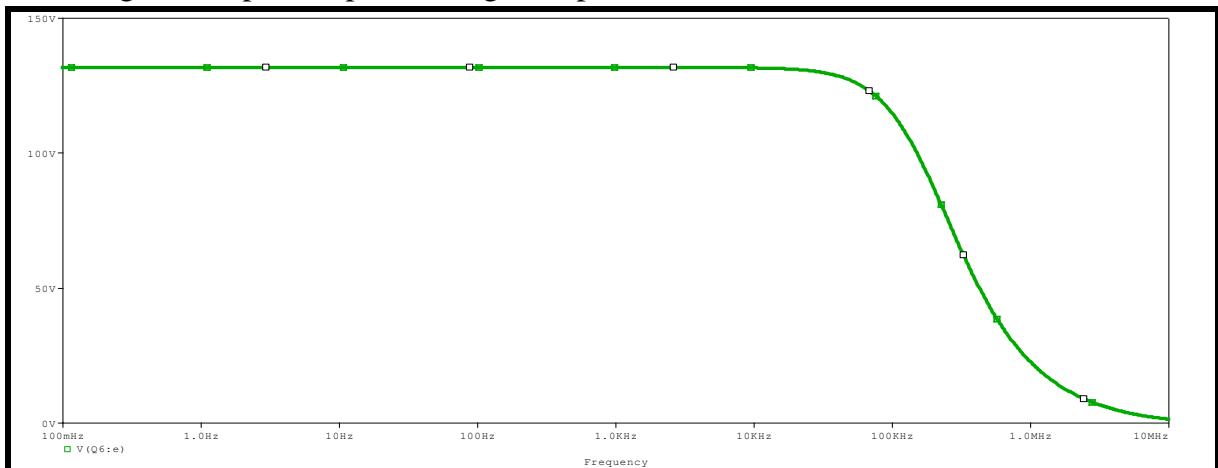


Figure 2: The Gain of Open loop multistage amplifier at R=10K Ω

From the Figure 2: the gain is almost 131.6.

1.2 The Input Impedance:

$$Z_{in} = \frac{V_{in}}{I_{in}}$$

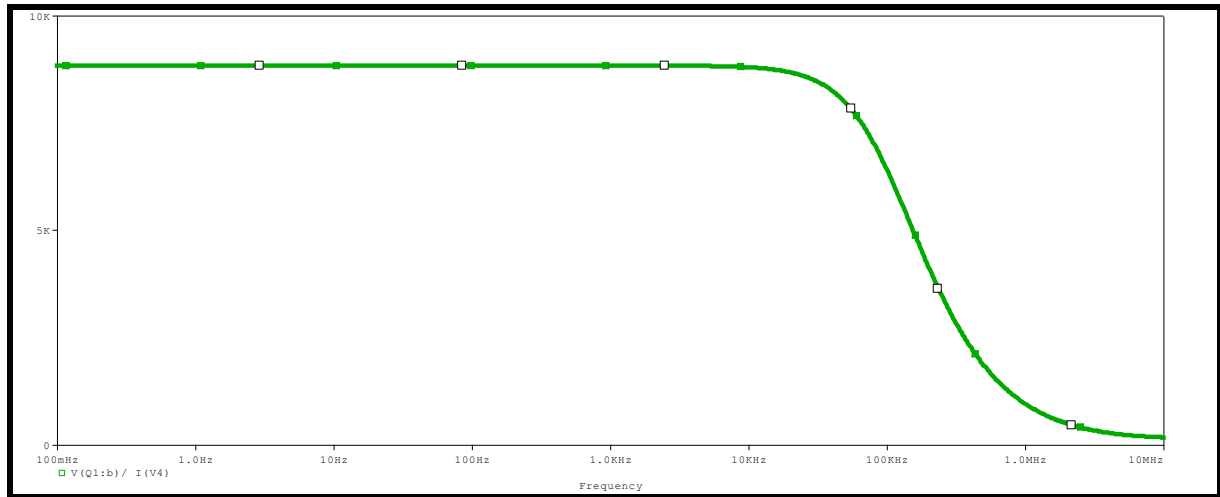


Figure 3: The Input Impedance of open loop multistage amplifier at R=10KΩ

From figure 3 note that the value of input impedance = 8.83KΩ

1.3 Output impedance:

To find the output impedance the Circuit shown in the Figure 4 was plotted:

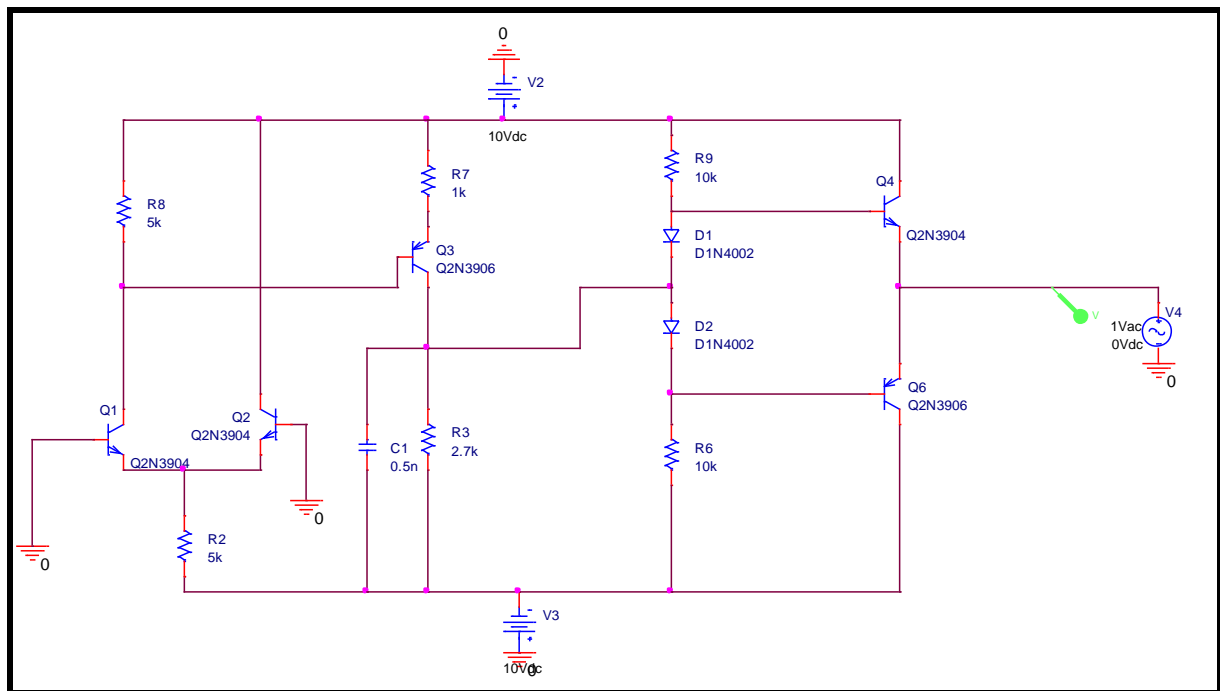


Figure 4: the circuit used to find the Zout

The Zout:

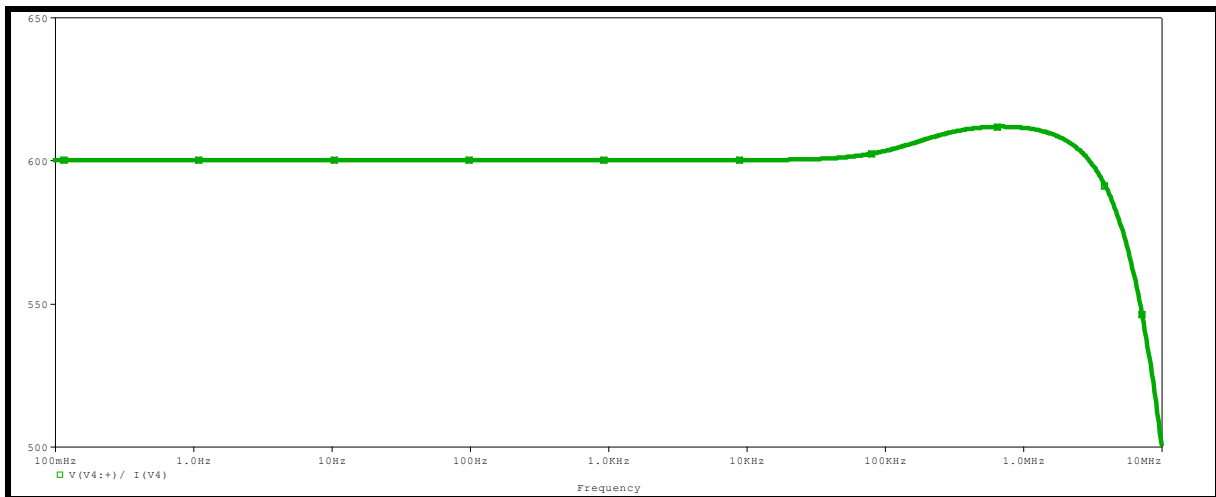


Figure 5: The output impedance

From the Figure 5: the output impedance is 600

1.4 The bandwidth:

$$B.W = \frac{1}{\sqrt{2}} * Gain = 0.707 * 131.7 = 93.1$$

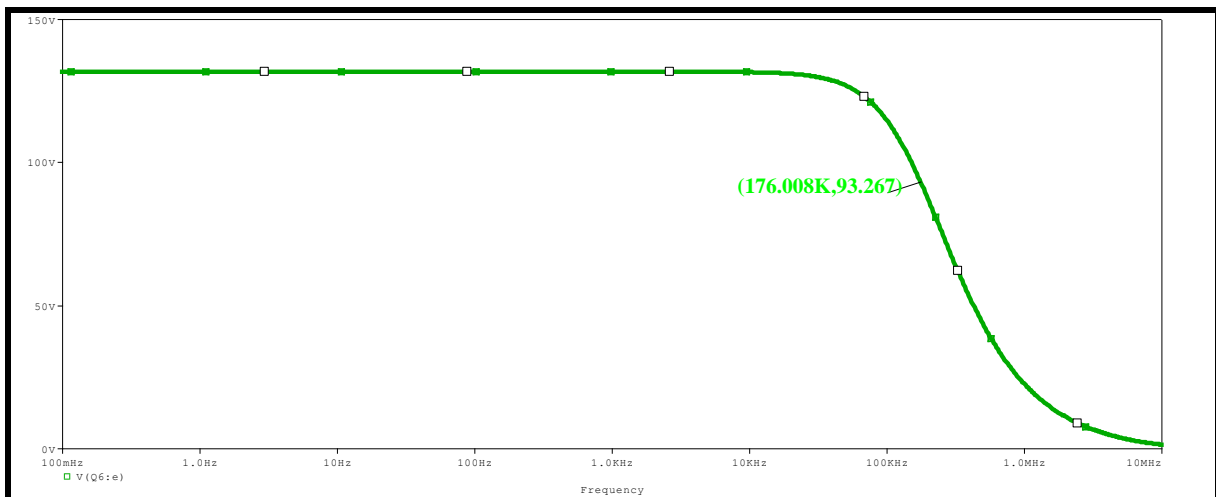


Figure 6: The B.W of open loop multistage amplifier at R=10KΩ

2. The Open-Loop multistage amplifier with $R=100 \Omega$

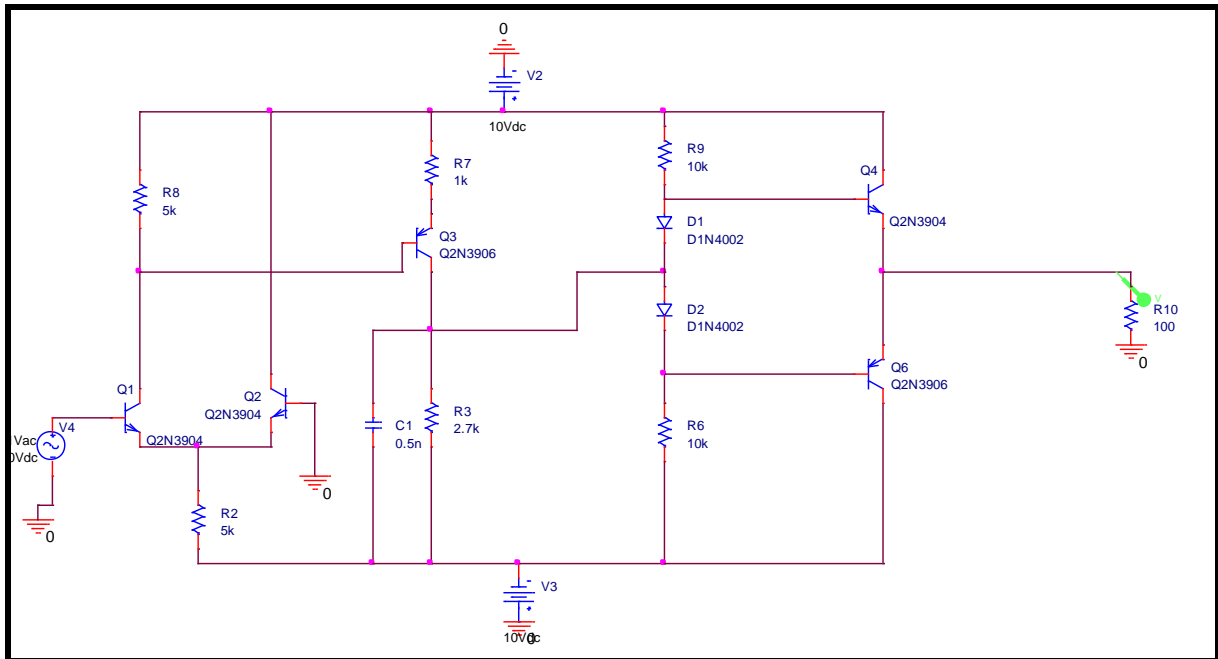


Figure 7: open loop multistage amplifier at $r=100 \Omega$

2.1 The Gain:

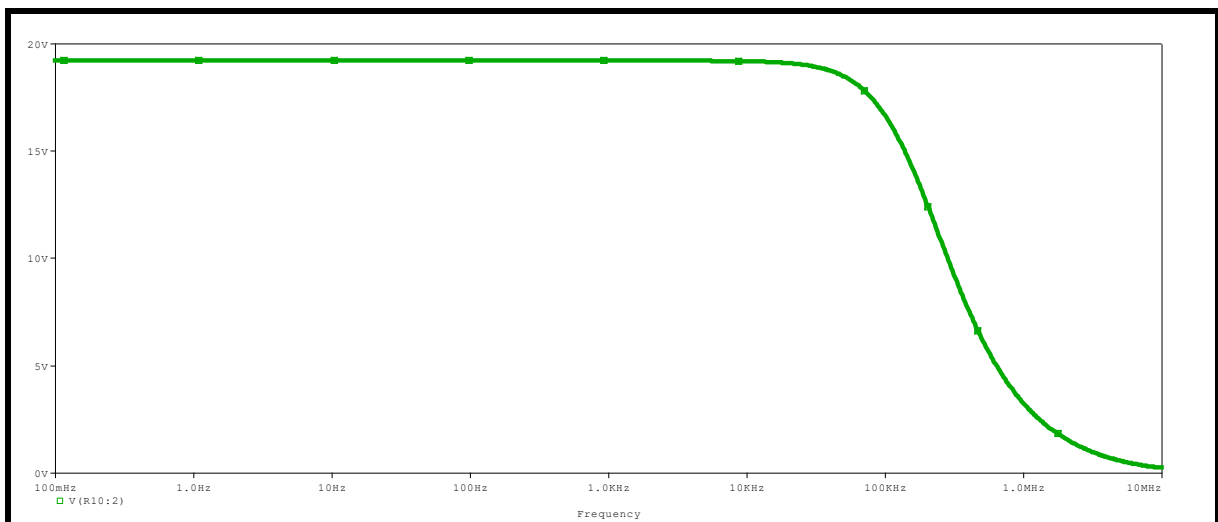


Figure 8: the gain of open loop multistage amplifier at $R=100 \Omega$

2.2 The B.W:

$$\frac{1}{\sqrt{2}} * Gain = 0.707 * 19.198 = 13.572$$

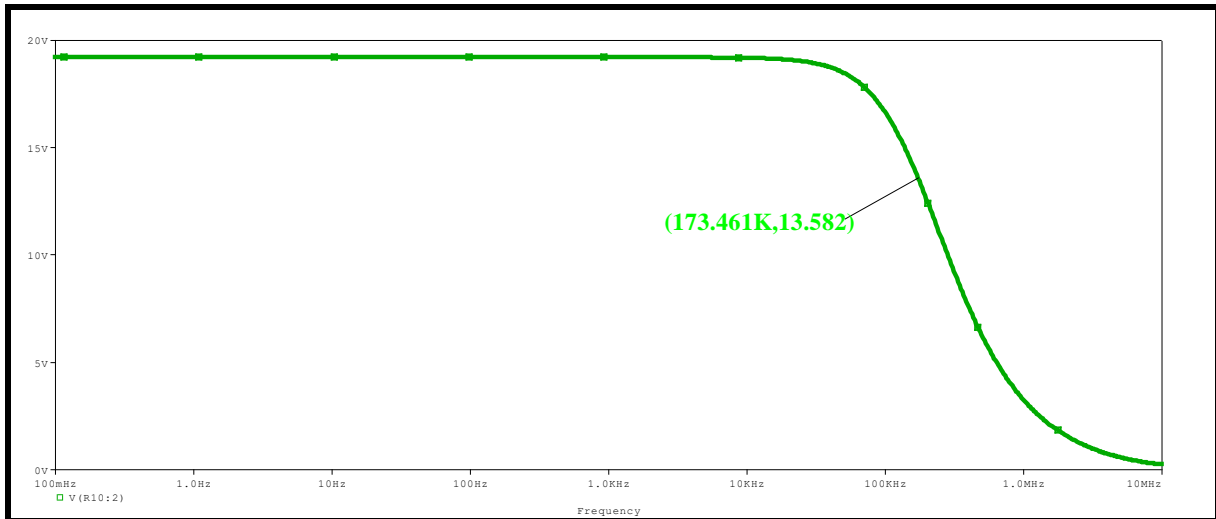


Figure 9: The gain of open loop multistage amplifier at R=100Ω

2.3 The input impedance:

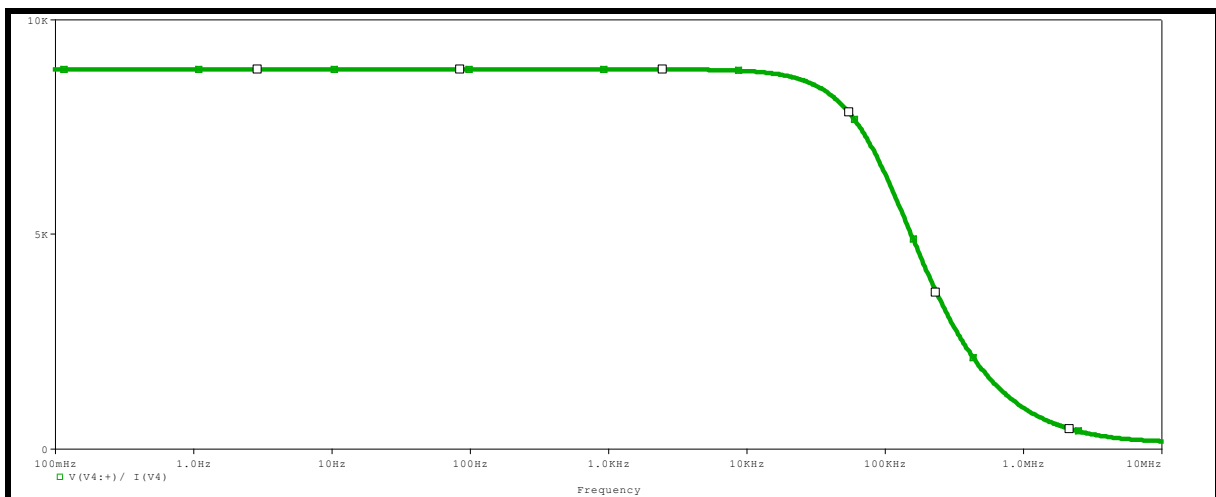


Figure 10: The input impedance of open loop multistage amplifier at R=100 Ω

From figure 10, the input impedance is 8.8K

2.4 Output impedance:

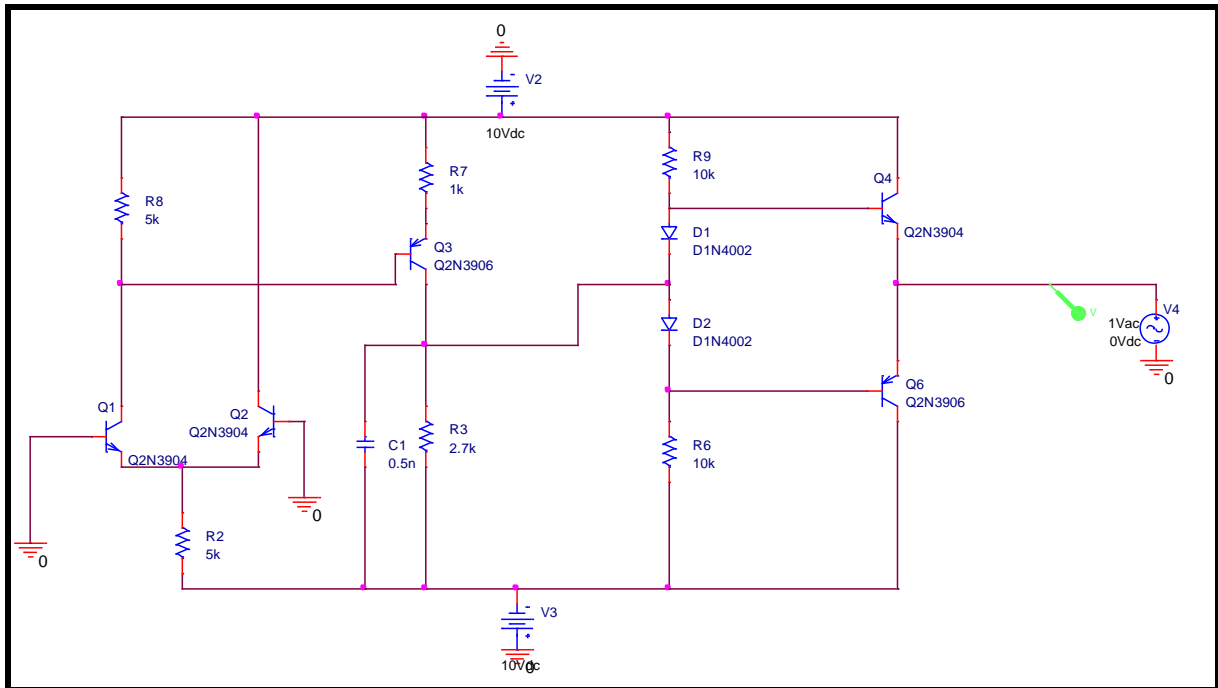


Figure 11: the circuit used to find Zout

The output impedance:

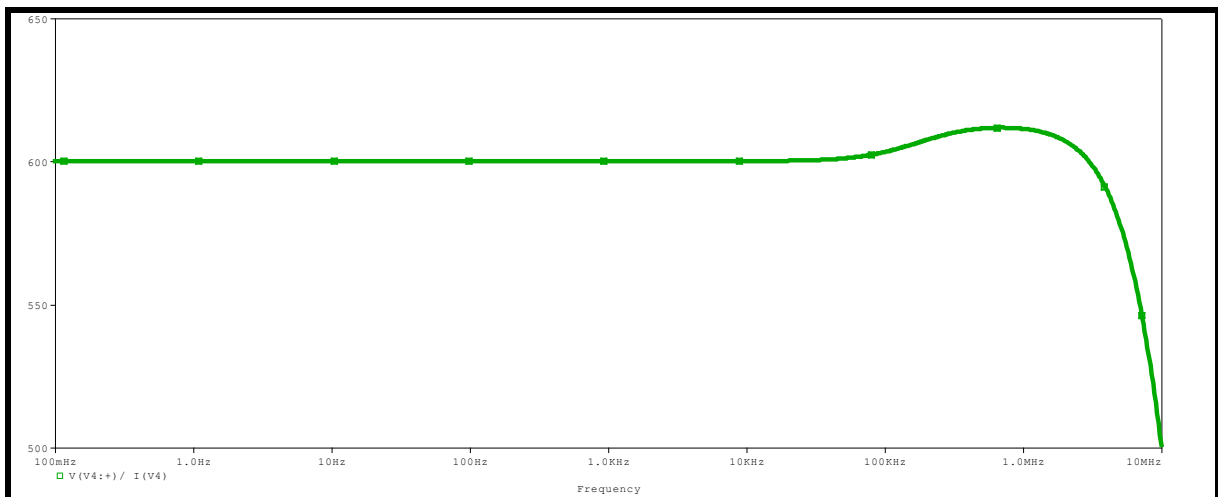


Figure 12: The output impedance of multistage amplifier at R=100 Ω

3. The closed loop multistage amplifier at R=10K:

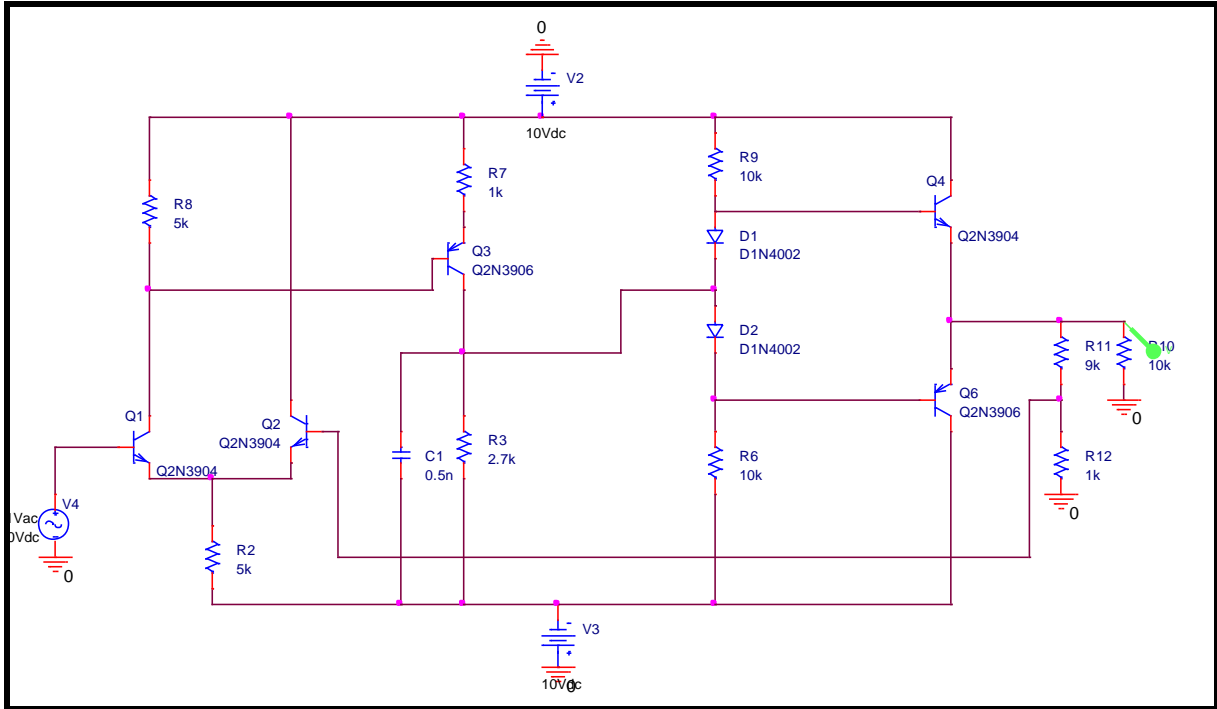


Figure 13: close loop multistage amplifier at R=10K

3.1 The Gain:

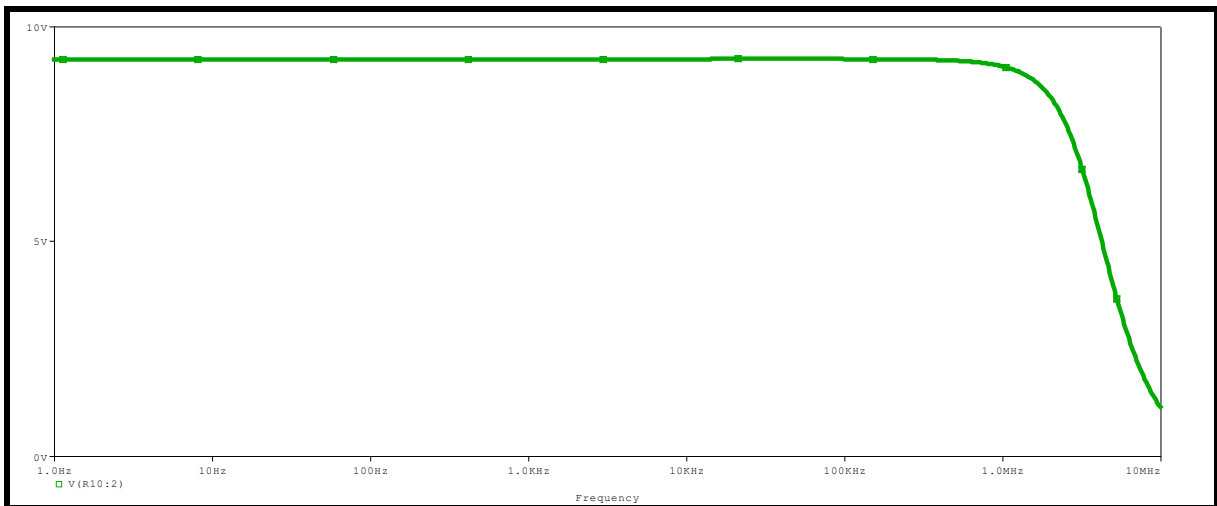


Figure 14: The gain of close loop multistage amplifier at R=10K

From the Figure 14, the gain almost 9.

3.2 The B.W:

$$B.W = \frac{1}{\sqrt{2}} * Gain = 0.707 * 9.2 = 6.5044$$

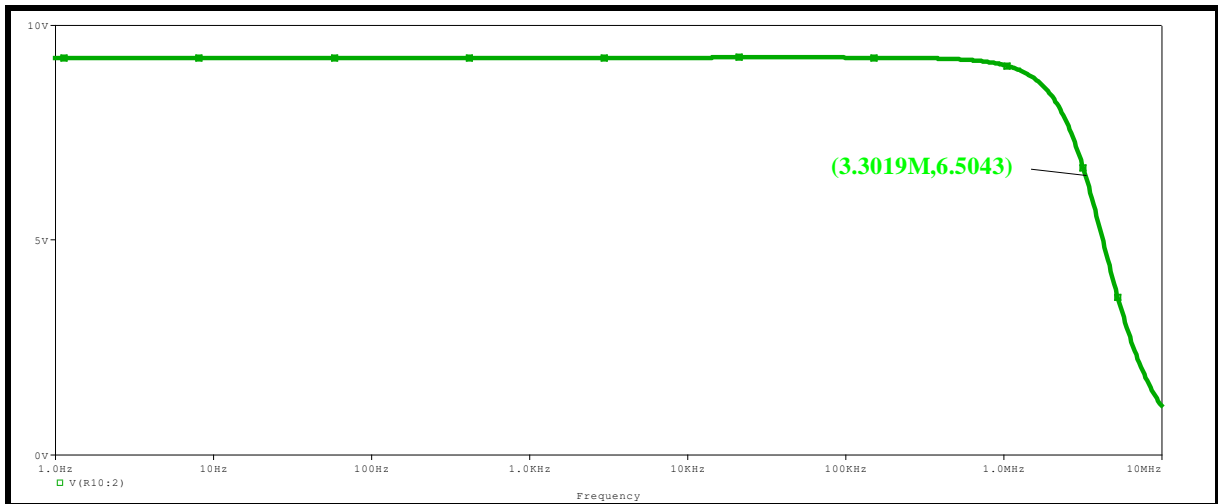


Figure 15: The B.W of close loop multistage amplifier at R=10K

3.3 The input impedance:

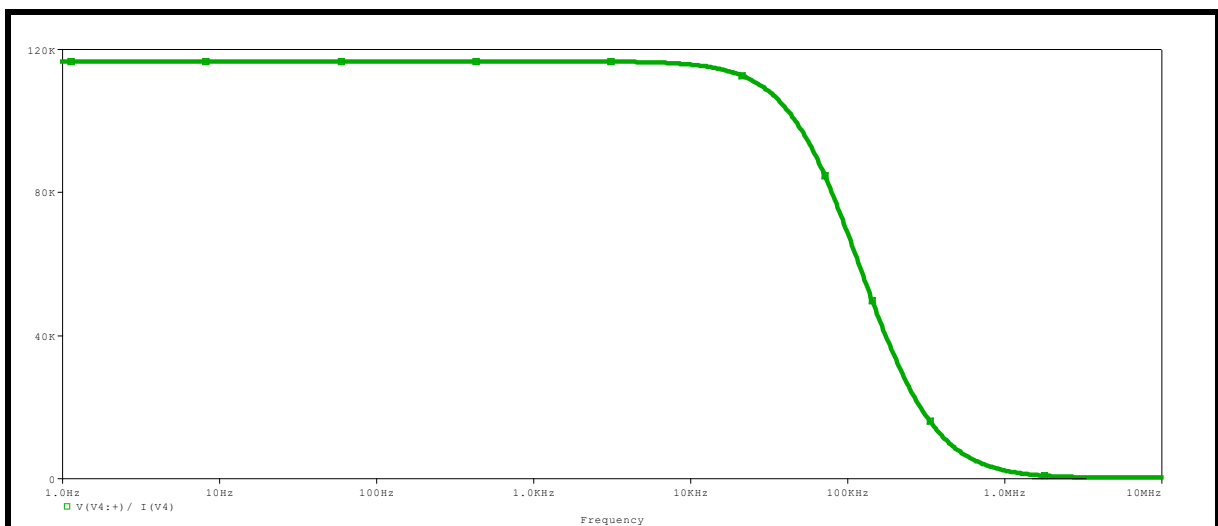


Figure 16: Zin of closed loop multistage Amplifier at R=10K

From the Figure 16, the input impedance 116.5 K

3.4 The output impedance

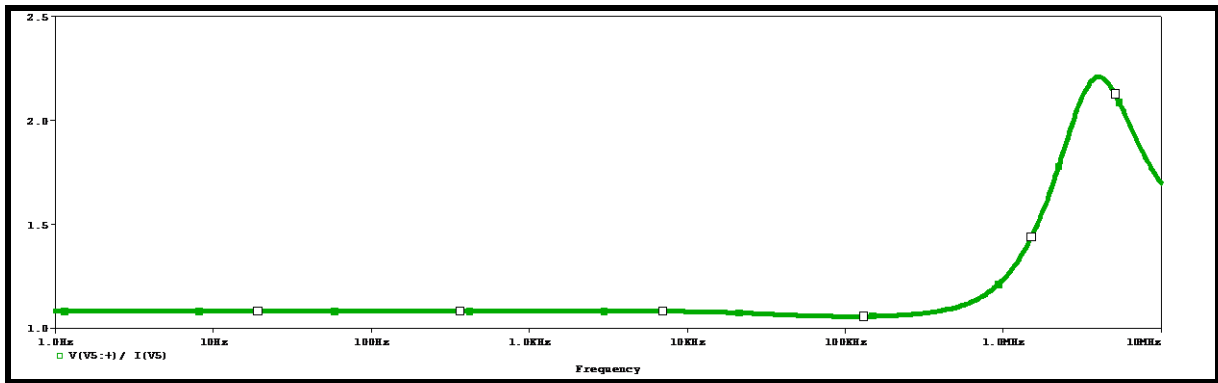


Figure 17: Z_{out} of close loop multistage amplifier

From the Figure 17, the output impedance 2.2K

4. The closed loop multistage amplifier at $R=100$:

4.1 The gain

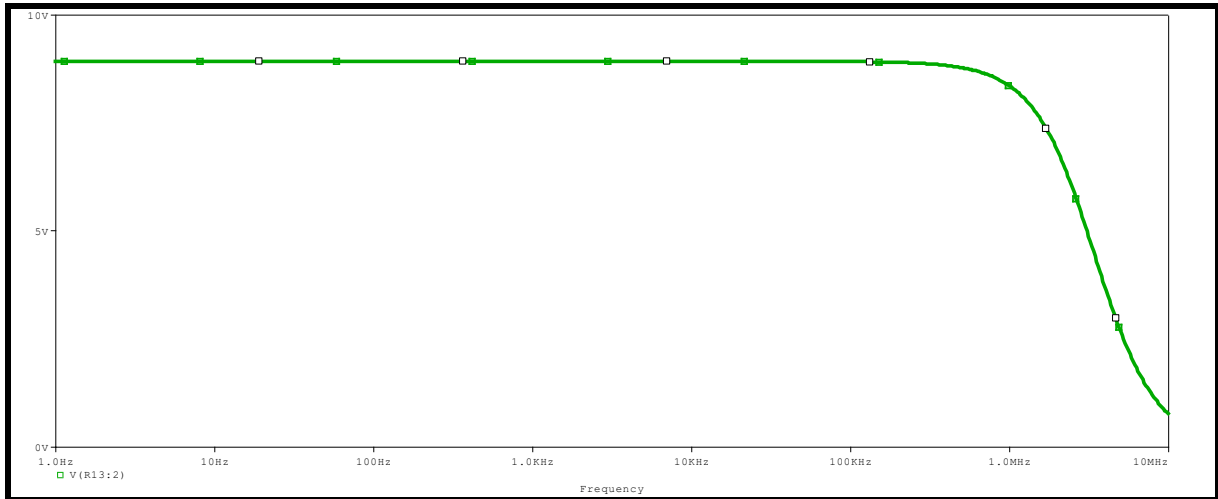


Figure 18: The gain of clos loop multistage amplifier at $R=100\ \Omega$

From the Figure 18, the gain of close loop multistage Amplifier at $R=100$ is 8.9

4.2 The B.W:

$$B.W = \frac{1}{\sqrt{2}} * Gain = 0.707 * 8.9 = 6.2923$$

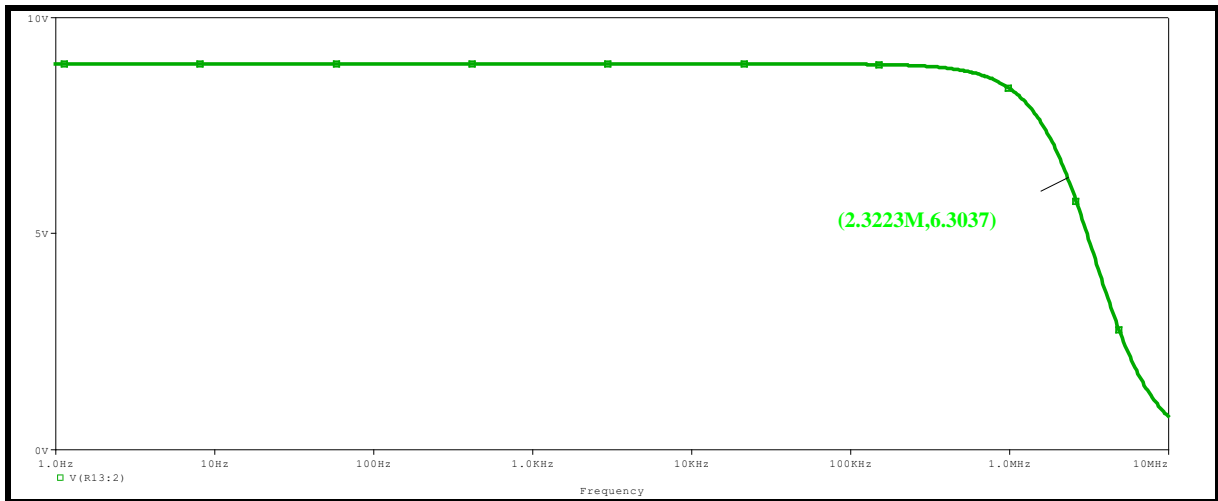


Figure 19: The B.W of close loop multistage amplifier at R=100

4.3 The input impedance

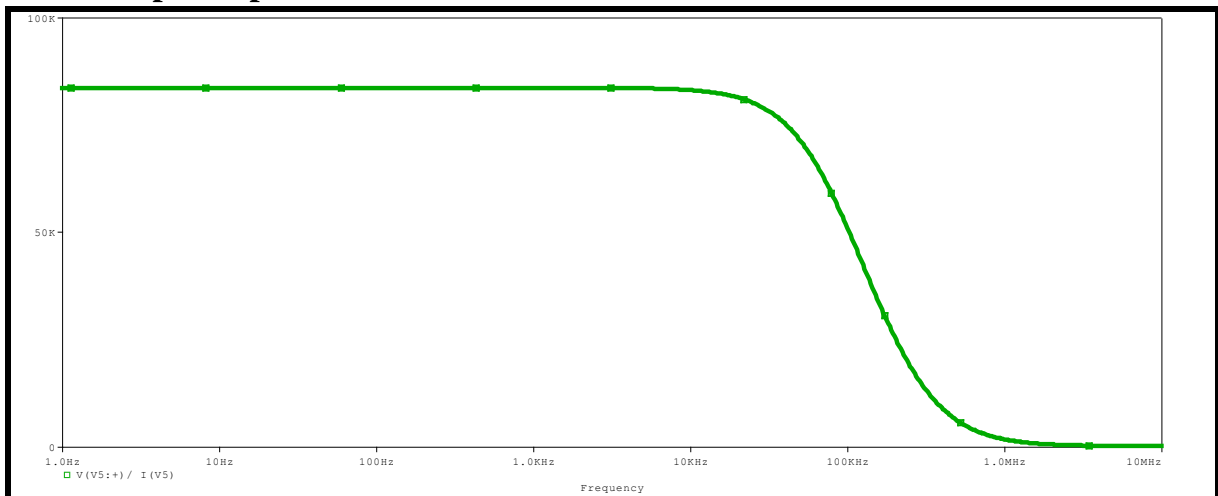


Figure 20: The input impedance of close loop multistage amplifier at R=100 Ω

4.4 The output impedance:

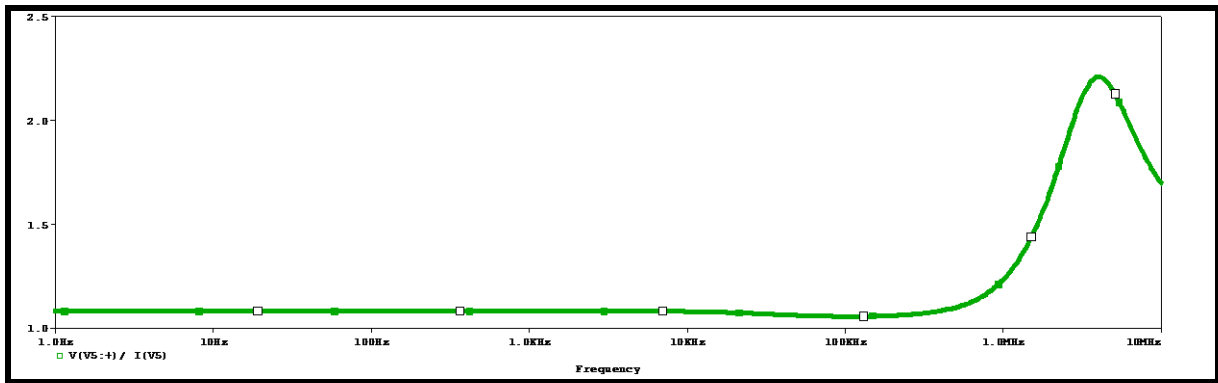


Figure 21: Zout of multistage amplifier