



Electrical and Computer Engineering Department  
Electrical Installations & Drawings Lab (ENEE 4202)

### AutoCAD Final Exam

Student Name:

Date: 20/12/2020

Student Number:

Time: 50 min.

**Use AutoCAD 2018 program to do the following tasks:**

1) Open the AutoCAD file (Final.dwg) located at the desktop.

\*

2) Create three layers, the specifications indicated below, which you will use for the three plans (Lighting/Power/ ELV).

| Layer Name | Color  |
|------------|--------|
| Lighting   | Yellow |
| Power      | Red    |
| ELV        | Green  |

**Save your work.**

3) In the opened AutoCAD file, you have to do the following tasks:

#### **Lighting Plan:**

**[40 Marks]**

- Convert any component you want to use from original layer to Lighting layer.
- You have to add any necessary lamps and switches (one-way switch, two-way switch, cross switch, ...) in the all rooms at necessary places.
- You have to distribute the lighting circuits on the distribution board, so that each room will have its own lighting MCB

## **Save your work.**

### **Power Plan:**

[40 Marks]

- Locate the sub distribution board on the power plan, and then do the following tasks.
- Convert any component you want to use from original layer to Power layer.
- Add power sockets, water proof socket and double pole switch in all rooms at necessary places.
- You have to distribute the power circuits on the distribution board.

## **Save your work.**

### **Extra low voltage Plan:**

[20 Marks]

#### **Tasks:**

- Convert any component you want to use from original layer to ELV layer.
- Locate the low-voltage box
- Locate the electric bell and its push button.
- Add telephone, data, and TV sockets at necessary places.

4) Submit your work by reply on the message through **Ritaj** with the following format

“*StudentID StudentName FinalExam.dwg*”.

**☺ Good Luck ☺**