



Birzeit University
Faculty of Engineering and Technology
Department of Electrical and Computer Engineering
Circuit Analysis – ENEE2304
PSpice Assignment

Deadline for Submission of your report (via Ritaj): Tuesday 14-2-2023 (Max 23:59)

Student Name:


ID Number:

Important notes for questions 1 and 2

- The resistor R_L must be named with the student name and ID. For example, if your name is Ahmad and your ID is 1219999 then, the resistor R_L must be named as Ahmad_1219999. Otherwise, the problem will not be evaluated.
- Also, note that on the simulation window, below the plot, your name and ID (name of the component R_L) must appear as seen in the example at the end of the assignment.

Question # 1: Superposition Technique


For the circuit shown below:

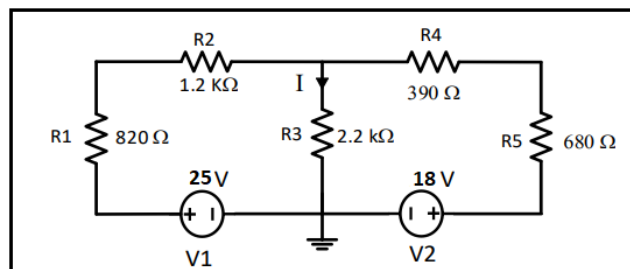

1. Use Pspice software to simulate the circuit and get the voltage across and the current through the resistor R_3 .
2. Apply superposition theorem to get the voltage across and the current through the resistor R_3 . You have to show all the results of simulation.
3. Compare the results obtained from step 1 and step 2.

Question #2: Thevenin's Theorem & Maximum Power Transfer

For the circuit shown below:

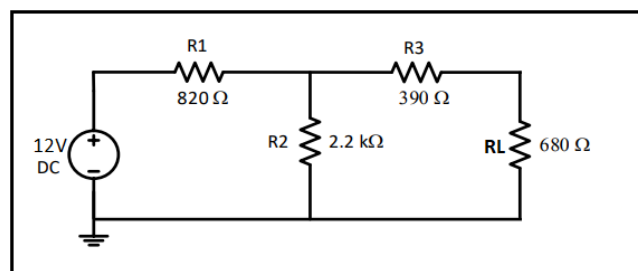


1. Use Pspice software to simulate this circuit and get the voltage across and the current through the resistor R_L (680Ω).
2. Using DC sweep, set R_L as a parameter that varies from 100Ω to $1.5 \text{ k}\Omega$ and **plot** the power dissipated by R_L as it varies (plot the power of R_L versus the value of R_L). With the help of cursors on Pspice simulation window, approximate at which value of R_L the power maximizes)
3. Use Pspice software to calculate R_{thevenin} seen by the resistor R_L . **Use V_{oc} and I_{sc} method only.** You have to show all the simulation results when getting V_{oc} and I_{sc} .
4. Compare the value of R_L at P_{max} obtained from step 2 and the value of R_{thevenin} obtained from step 3.
5. Build and then simulate the Thevenin equivalent circuit with the load resistor R_L and show the voltage across and the current through the resistor R_L .
6. Compare the results obtained from step 1 and step 5.

Important notes for questions 3 and 4

- The capacitor C must be named with the student name and the ID. For example, if your name is Ahmad and your ID is 1219999 then, the capacitor C must be named as Ahmad_1219999. Otherwise, the problem will not be evaluated.
- Also, note that on the simulation window, below the plot, your name and ID (name of the component C) must appear as seen in the example at the end of the assignment.

Question #3: First Order RC Circuit Analysis

For the circuit shown below:

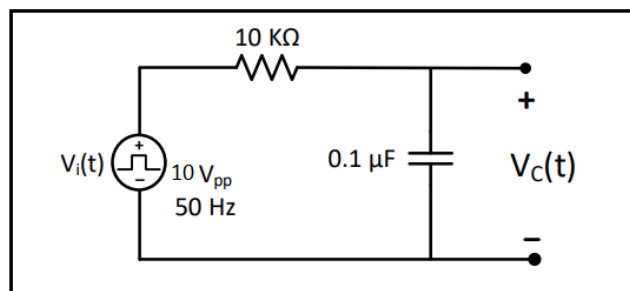


The input voltage is square signal with 10 V peak-peak (0 V to 10 V) and frequency of 50Hz.

1. Use Pspice software to plot both $V_i(t)$ and $V_c(t)$ (on the same graph) for a meaningful period of time.
2. With help of cursors on Pspice simulation window, show the value of the time constant (τ). You have to show both the circuit and the simulation result.

Question #4: Second Order RLC Circuit Analysis



For the circuit shown below:

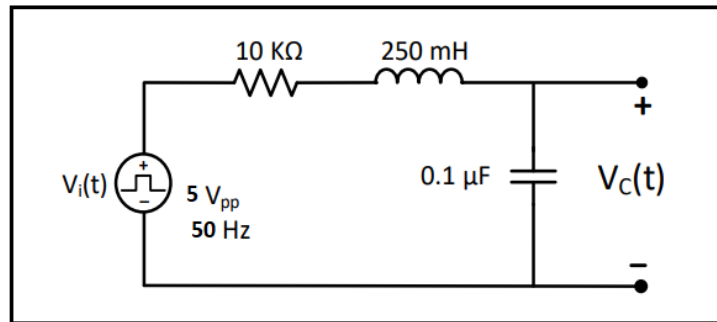

The input voltage is square signal with 5 V peak-peak (0 V to 5 V) and frequency of 50Hz.

1. Use Pspice software to plot both $V_i(t)$ and $V_c(t)$ (on the same graph).
2. Change the Value of R to 3.162 kΩ, repeat step 1.
3. Change the Value of R to 500 Ω, repeat step 1.
4. Comment on each result: is it over-damping, critical-damping, or under-damping response.

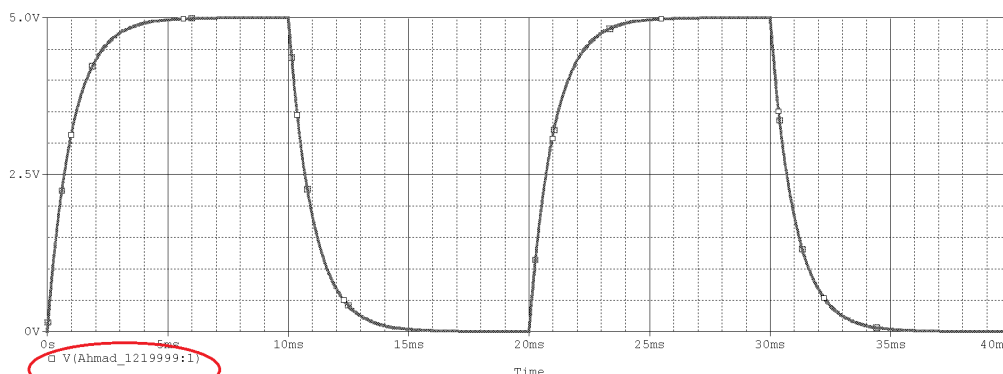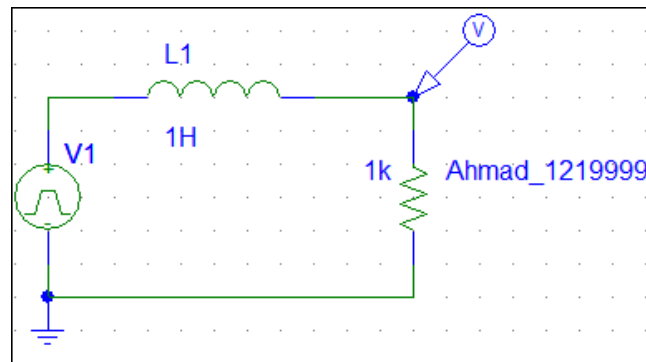Example of a circuit and the simulation result



V (Ahmad_1219999:1)



Your name and ID must appear here

... With Best Wishes ...