

# Chapter 10: Power

- Instantaneous Power  $P(t)$ :

$$P(t) = \frac{V_m I_m}{2} [\cos(\Theta_V - \Phi_i) + \cos(2\omega t + \Theta_V + \Phi_i)] \text{ watt}$$

- Average Power :- (Real Power)

$$P_{av} = \frac{1}{2} V_m I_m \cos(\Theta_V - \Phi_i)$$

Resistor

Inductor

Capacitor

$$\frac{I_m^2 R}{2}$$

$$P_{av} = 0$$

$$P_{av} = 0$$

$$\Theta_V - \Phi_i = 90$$

$$\Theta_V - \Phi_i = -90$$


$$\Theta_V - \Phi_i = 0$$

\* Reactive impedances absorb **No** average Power

- Maximum average Power Transfer

$$Z_{Th} = R_{Th} + j X_{Th}$$

$$Z_L = R_L + j X_L$$

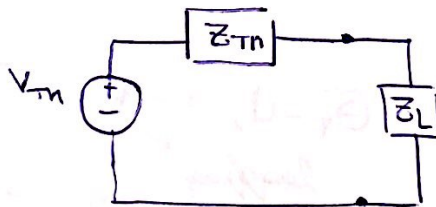

$$\rightarrow Z_L = Z_{Th}^*$$

$$P_{L,max} = \frac{1}{8} \frac{V_{Th}^2}{R_L} \text{ or } R_{Th} \text{ (Real part only)}$$

\* Effective or RMS Value:

$$V_{rms} = V_{eff} = \frac{V_m}{\sqrt{2}} \leftarrow \text{Max amplitude}$$

$$P_{av} = V_{rms} I_{rms} \cos(\Phi_v - \Phi_i)$$

$$V_{rms} = R I_{rms}$$

$$\Theta_v - \Phi_i = 0$$

$$P_{av} = I_{rms}^2 R \leftarrow \text{real part}$$

$$P_{apparent} = V_{rms} I_{rms} \quad \text{measured in VA}$$

PF = Power factor


$$PF = \cos(\Theta_v - \Phi_i) \leftarrow \text{Phase shift}$$

$$S \circlearrowleft P_{av} = P_a \cdot P_F$$

\* PF of Types of loads:-


1) Resistor:  $\Theta_v - \Phi_i = 0$

$$P_F = 1$$

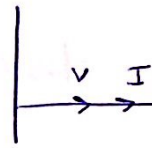


2) Inductor:  $\Theta_v - \Phi_i = 90$  lagging

$$P_F = 0$$

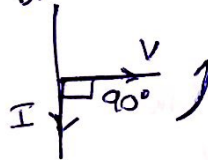

3) Capacitor:  $\Theta_v - \Phi_i = -90$  leading

$$P_F = 0$$

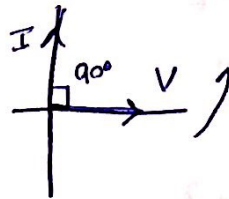

4) Inductive load

$$90^\circ > \Theta_v - \Phi_i > 0$$

$$1 > P_F > 0$$

lagging Power factor

### 5) Capacitive lead

$$-90 < \theta_v - \theta_i < 0$$

$$1 > PF > 0$$

Leading Power factor.

\* عنوان تعرفنا اذا ال  $P_F$  leading or lagging

← اذا كان فرق الزوايا موجب  
 ← اذا كان فرق الزوايا سالب

lagging  
 leading

Note:  $P_{supplied} = P_{av} + P_{ev}$  ← حسابنا

L                  Load

↑  
 average

\* ملاحظة :- اذا كان ال  $P_F$  lagging احسب ال  $\cos^{-1}$  سالب


### Complex Power

$$\vec{S} = V_{rms} \vec{I}_{rms} \angle (\theta_v - \theta_i) = V_{rms} \cdot \vec{I}_{rms}^*$$

$$= \underbrace{V_{rms} I_{rms} \cos(\theta_v - \theta_i)}_{P_{av}} + \underbrace{V_{rms} I_{rms} \sin(\theta_v - \theta_i)}_{Q}$$

$P_{av}$ : average Power in Watt

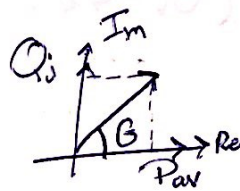$Q$ : Reactive Power in VAR  
 Volt Amperes reactive



\*  $\Phi$  for Types of load:-

1) Resistance  $\Theta_V - \Phi_i = 0$   
 $\Phi_R = 0$

2) Inductance  $\Theta_V - \Phi_i = 90$   
 $\Phi_L = \omega L I_{rms}^2 = \frac{V_{rms}^2}{\omega L}$

3) Capacitance  $\Theta_V - \Phi_i = -90$   
 $\Phi_C = \frac{-I_{rms}^2}{\omega C} = -\omega C (V_{rms})^2$

Remember  $\Theta = \Theta_V - \Phi_i = \tan^{-1} \left( \frac{Q}{P_{av}} \right)$

$Q = P_{av} \tan [\cos^{-1} (PF)]$  lagging

$Q = -P_{av} \tan [\cos^{-1} (PF)]$  leading

• لایبار  $\Phi$  فی  $V_{rms}, I_{rms}$  کلی و  $Q$  کئی  
 آڈ فی  $V, I$  فی سوکس و  $Q$  جی جی  
 تذکرہ  $Q$  جی جی  $Q$  جی جی  $Q$  جی جی

\* Conservation of AC Power

$P_F = \cos(\Theta_V - \Phi_e)$

Note:

$\vec{S}_T = V_{rms} \vec{I}_s^*$

$P_e = |S_T|$

$P_{av loss} = |I_s|^2 \cdot (0.05)$

## Power factor Correction

→ Increasing  $P_F$  without alternating voltage or current

To improve the power factor we decrease  $Q$

In an inductive circuit we add a capacitor parallel to the load

$$Q_c = Q_{\text{final}} - Q_{\text{initial}}$$

$$C = -\frac{Q_c}{\omega V_{\text{rms}}^2}$$

Measuring Power : Wattmeter

- Two coils used
- high impedance voltage coil
- low " current "

ملاحظات عند حل المسئلة :-

إذا جيب ال Powerfactor

أوجد S لكل عنصر load مع أوجد S

ثم حوله إلى ال Power factor عند الزاوية

→  $PF = \cos(\text{الزاوية})$