



Chapter 11: Balanced Three-Phase Circuits

Three Phase Circuit: three sources having the same amplitude and frequency but out of phase by 120°

- 1- • The instantaneous power \rightarrow Constant
- 2- • P_{loss} in 3-phase sys = $\frac{1}{2} P_{\text{loss}}$ in 1-phase sys


* Possible Configurations of 3.p.s :-

1- The Y-connected Source

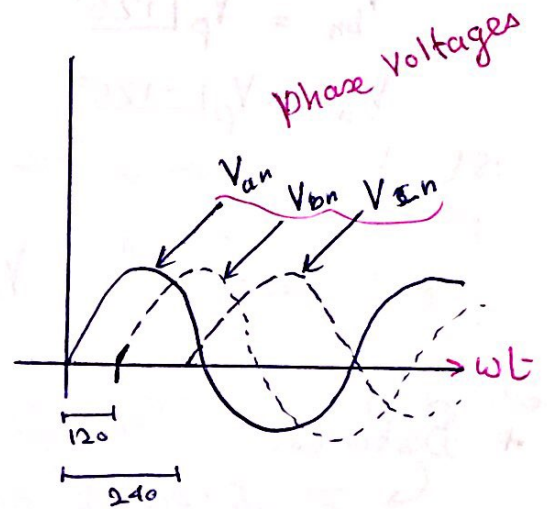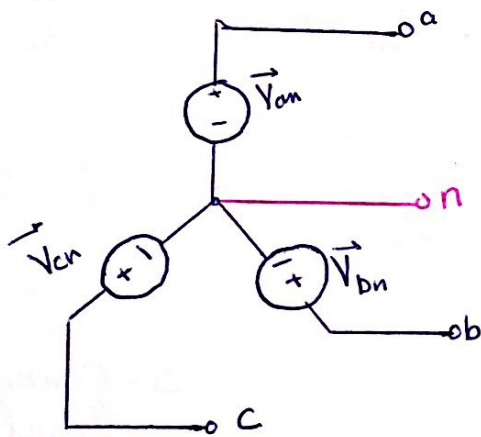

• V_{ab}, V_{bc}, V_{ca} are line-to-line voltages

2- The Δ -Connected Source

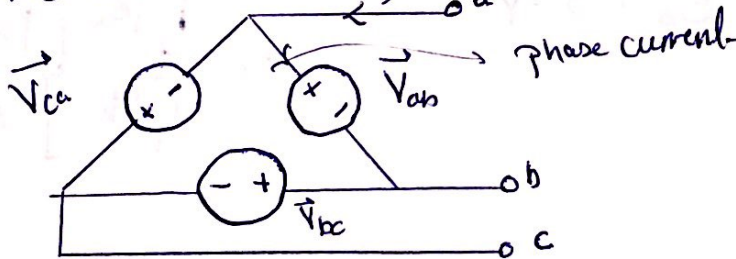

* The phase Sequence

- 1- abc sequence (positive sequence)
- 2- acb sequence (negative sequence)

1- (+) Sequence:-

لقد
التيار
للتيار

$$\begin{cases} V_{an} = V_p \angle 0^\circ \\ V_{bn} = V_p \angle -120^\circ \\ V_{cn} = V_p \angle +120^\circ \end{cases}$$

مع علامات الساعات

line to line voltage → line to line Vol

$$\begin{aligned} \vec{V}_{ab} &= \sqrt{3} \vec{V}_{an} \angle +30^\circ \\ \vec{V}_{bc} &= \sqrt{3} \vec{V}_{bn} \angle +30^\circ \\ \vec{V}_{ca} &= \sqrt{3} \vec{V}_{cn} \angle +30^\circ \end{aligned}$$

I_{ab}, I_{bc}, I_{ca} are phase currents

2- (-) Sequence.

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle +120^\circ$$

$$V_{cn} = V_p \angle -120^\circ$$

عكس علامات الساعة

$$\vec{V}_{ab} = \sqrt{3} \vec{V}_{an} \angle -30^\circ$$

$$\vec{V}_{bc} = \sqrt{3} \vec{V}_{bn} \angle -30^\circ$$


$$\vec{V}_{ca} = \sqrt{3} \vec{V}_{cn} \angle -30^\circ$$

Balanced set: $V_{an} + V_{bn} + V_{cn} = 0$

* Balanced Three phase loads:-


↳ Z is equal on all phases:

Y-Connected load

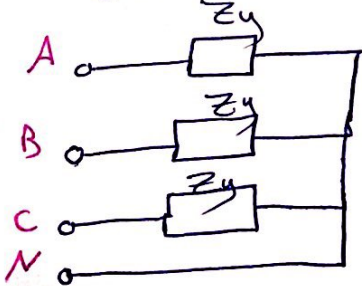

$Z_\Delta = 3Z_Y$


Δ-Connected load

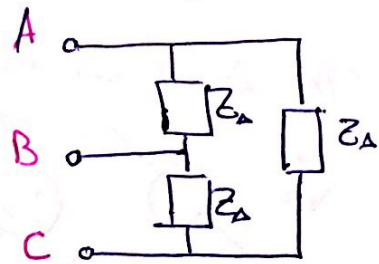

• We connect the three phase source with the phase load by: Y-Y or Y-Δ or Δ-Y or Δ-Δ

Note:

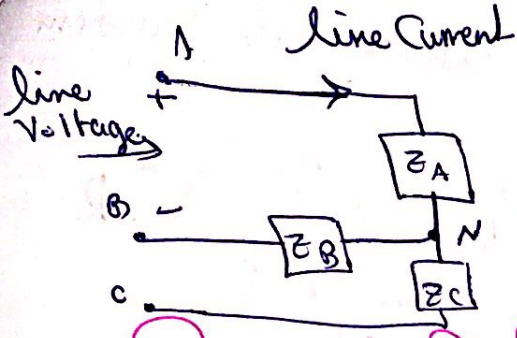فرق بين ال phase current و ال line current



التيار الذي يمر بين A و B و N

التيار الذي يمر باللود

V_{CN} is phase voltage (voltage across a single phase)

V_{AB} is line to line voltage (voltage across any pair of lines)

* Power in Balanced System

- P instantaneous is constant

$$- P_T = 3 V_p I_p \cos \theta$$

loads

Y-load

• P_{av} :-

$$P_A = P_B = P_C = P_T$$

$$P_T = \sqrt{3} V_L I_L \cos \theta$$

• Q

$$Q_T = \sqrt{3} V_L I_L \sin \theta$$

• Complex \vec{S}

$$S_T = \sqrt{3} V_L I_L \angle \theta$$

$$V_{AN} = \frac{V_L}{\sqrt{3}}$$

$$I_{aT} = I_L$$

Δ -load

• P_{av} :-

$$P_T = \sqrt{3} V_L I_L \cos \theta$$

• Q :-

$$Q_T = \sqrt{3} V_L I_L \sin \theta$$

• Complex \vec{S}

$$S_T = \sqrt{3} V_L I_L \angle \theta$$

* Comparing Power loss:



Single phase System

Three-phase System

$$P_{\text{loss}} = \left(\frac{P_L}{V_L \cdot P_F} \right)^2 (2R)$$



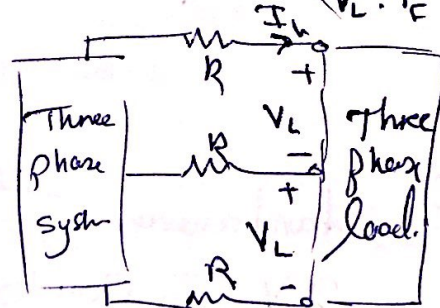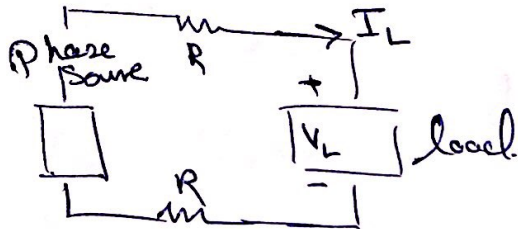
$$P_{\text{loss}} = \left(\frac{P_L}{V_L \cdot P_F} \right)^2 \cdot R$$



* Measuring P_{av} in 3Φ system

$$W_1 = V_L I_L \cos(\Theta_2 + 30^\circ)$$

Impedance angle

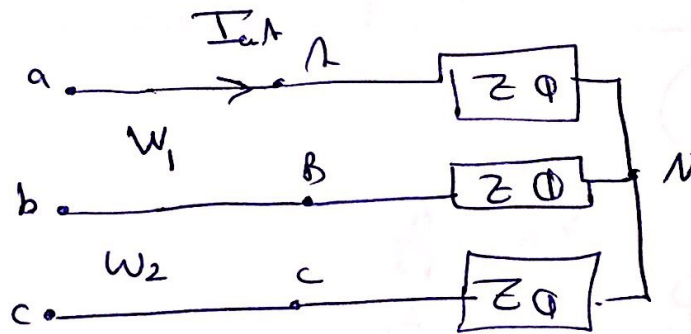

$$W_2 = V_L I_L \cos(\Theta_2 - 30^\circ)$$

$$P_{\text{Total}} = W_1 + W_2 = \sqrt{3} V_L I_L \cos \Theta_2$$