

Chapter 2: Circuit Elements

Elements can be divided to two main Types:-

Active Elements: Destroys power

Passive Elements
Absorbes power

Independent Sources

Dependant sources

فئة تتب من فئة
تخزن الطاقة

Incl. Voltage Sources

Incl Current Sources

فئة الجهد لا تتب
على التيار الذي
غير فيها

فئة التيار لا تتب
على الجهد الذي
غير فيها

There are 4 Types:-

- VCVS
- VCCS
- C CVS
- CCCS

AC

DC



Resistors



Unit: ohm

ohm's law:-

$$V(t) = i(t)R$$

or

$$V(t) = -i(t)R$$

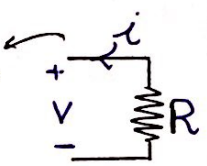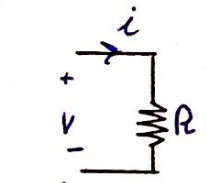

Capacitors

Unit: Farad

$$i_c(t) = C \frac{dV_c(t)}{dt}$$

$$V_c(t) = V_c(0^-) + \int_{0^-}^t \frac{1}{C} i_c(t) dt$$



Inductors

Unit: Henry

$$V_L(t) = L \frac{di_L(t)}{dt}$$

$$i_L(t) = i_L(0^-) + \int_{0^-}^t \frac{1}{L} V_L(t) dt$$



Resistances and Conductance

R


G

$$G = \frac{1}{R} \quad \Omega^{-1}, \text{ S, Simens or mho}$$

Two special Resistor Values:-


Short Circuit

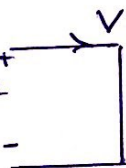- $V = 0$ volts
- $I = \text{has a value}$
- $R = 0$
- $G = \infty$



Open Circuit

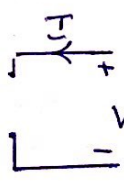- $V = \text{has a value}$
- $R = \infty$
- $G = 0$
- $I = 0$



If you have a capacitor in a circuit for a long time then $i_c(t) = 0$


If you have an inductor for a long time $V_L(t) = 0$

Power :-

The sum of power in any circuit equals zero

$$\sum P_{\text{supplying}} = \sum P_{\text{absorbing}}$$

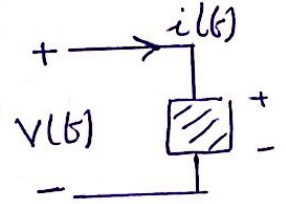If the element polarity is same as i direction
Then it's absorbing Power :- $P(t) = v(t) i(t)$



If the element polarity is in the opposite direction of
 i direction Then it's supplying Power: $P(t) = -i(t) v(t)$

