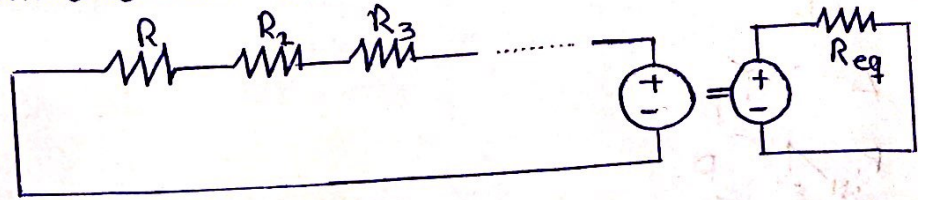


# Chapter 3: Simple Resistor Circuit

- Resistors Can be Connected on Series or on Parallel


Series Connection:

- $R_{eq} = R_1 + R_2 + \dots + R_N$



Parallel Connection:-

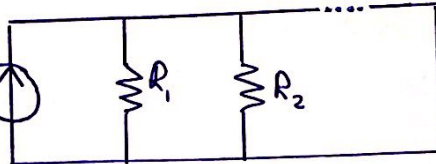- $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$




- $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$  (Special Case)

Dividor Rule

↳ Voltage Dividor Rule
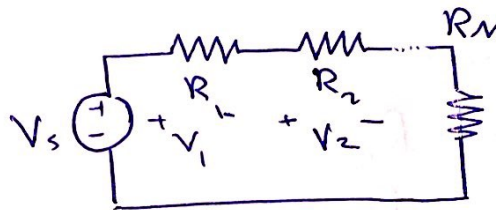
$$V_2 = \frac{V_s R_2}{R_1 + R_2 + \dots + R_N}$$




$$V_1 = \frac{V_s R_1}{R_1 + R_2 + \dots + R_N}$$

- Useel in Series only

↳ Current Dividor Rule


$$I_N = \frac{R_{eq}}{R_N} \cdot I_s$$

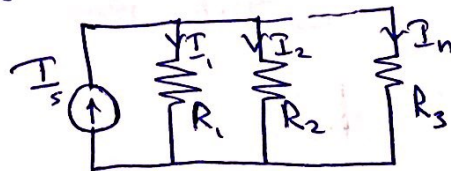

Where  $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$

- Useel in Parallel


# $\Delta \Rightarrow Y$ transformation

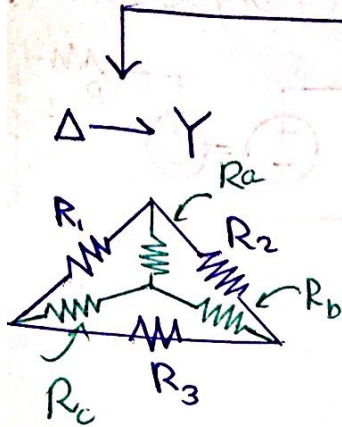

•  $R_a = \frac{R_1 R_2}{R_1 + R_2}$

•  $R_b = \frac{R_2 R_3}{R_2 + R_3}$

•  $R_c = \frac{R_1 R_3}{R_1 + R_3}$

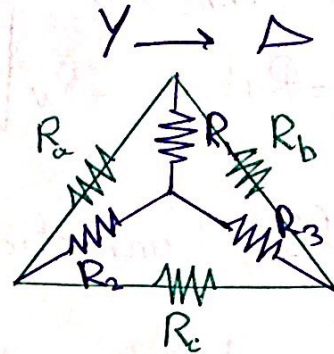

•  $R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$

•  $R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$

•  $R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$

## Special Case:-

If  $R_1 = R_2 = R_3 = R_\Delta$   
 then  $R_Y = \frac{R_\Delta}{3}$

## Steel Store Bridge

لدينا تيار  $I_m = 0$  ربع فوالجيب سادس  
 جيز بالتيه :

$R_1 I_1 = R_2 I_2$

and  $R_3 I_3 = R_4 I_4$

and since  $(R_1$  and  $R_3)$  and  $(R_2$  and  $R_4)$  are each in series  $R_4 = \frac{R_2 R_3}{R_1}$

