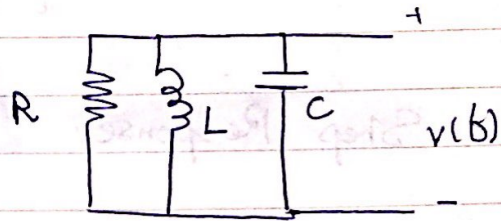


# Chapter 8: RLC - Circuits

• Second order Differential Equations:-

Natural Response:

$$C \frac{d^2 v(t)}{dt^2} + \frac{dv(t)}{R dt} + \frac{1}{L} v(t) = 0$$



Knowing that  $v(t) = Ae^{st}$

$$Cs^2 + \frac{1}{R}s + \frac{1}{L} = 0 \quad \leftarrow \text{characteristic Eq}$$

$$s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\text{or } s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \alpha^2 = \frac{1}{2RC}$$

Depending on Both There are 3 cases:-

$$\alpha > \omega_0$$

$s_1, s_2$  real, unequal

over damped

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\alpha < \omega_0$$

$s_1, s_2$  Complex Conjugate  
under damped

$$v(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\alpha = \omega_0$$

$s_1, s_2$  real equal


critically damped
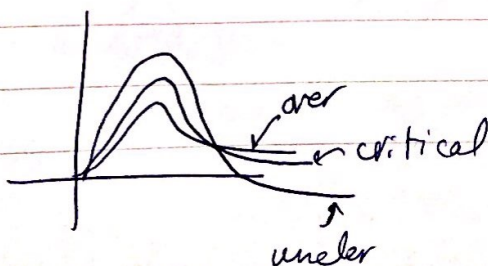
$$v(t) = A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}$$



# Lossless LC - Circuits

$R = \infty$   
 $\alpha = 0$

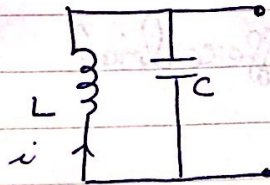

Step Response:

$$\frac{d^2 i_L(t)}{dt^2} + \frac{1}{LC} i_L(t) = \frac{I}{LC}$$


$$i = i_m + i_g$$

$\uparrow$   $K$
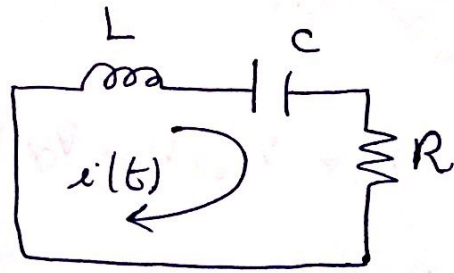
# Series RLC Circuits

The equation used:-

$$L \frac{di(t)}{dt} + R i(t) + V_c(0) + \frac{1}{C} \int_0^t i(t) dt = 0$$



↓

$$L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \alpha = \frac{R}{2L}$$

$$s_{1,2} = -\alpha \pm \sqrt{\omega_0^2 - \alpha^2}$$

- \* Cases:
- Underdamped
  - overdamped
  - critical Damping

• Same Equations as parallel But  $i(t) = i_m$

Responses: Step Response:  $V(t) = V_m + A e^{s_1 t} + B e^{s_2 t}$

$$V(0^+) = V_c(0) = 0, \quad i_L(0) = 0 = i_L(0^+)$$

$$V_c(t) = V_c(0) + \frac{1}{C} \int_0^t i(t) dt$$

↪ from solution

~~or use~~  
To find  $V_c(t)$

$$V_s = RC \frac{dV_c(t)}{dt} + LC \frac{d^2V_c(t)}{dt^2} + V_c(t)$$

B

$$V_c(t) = V_{ch}(t) + V_{cp}(t)$$

$$k = \frac{V_s}{s}$$