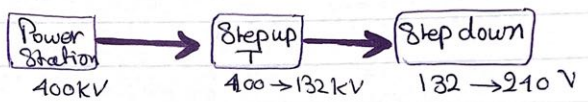


CHAPTER 2

Transformers

▷ Transformer: a device that changes electrical power from a certain frequency and voltage level to same frequency but other voltage level. (AC → AC)

→ Better transmission efficiency for long distance



▷ Types :-

1. Step up transformers (Unit)
2. Step down transformers (Substation)
3. Distribution transformers
4. Special Purpose transformers PT, CT
5. Isolation and impedance matching transformers used for protection $N_1 = N_2$


Power, voltage
current

Forms of Transformers

High reliability

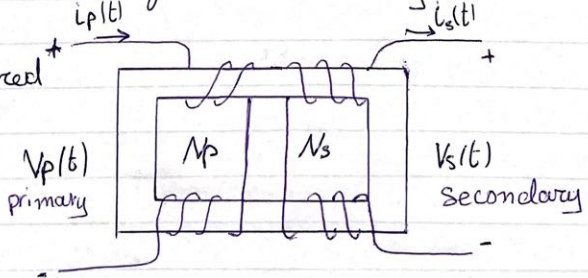1. Core form:
 - Simple rectangular
 - Windings wrapped around two sides of the rectangle

Advantage :- If an error occurred → the damage occurred in one transformer we just replace it



But in shell form it's all damaged → Exists at company

compact form

can be used for 3 phase connection
 → used for long distance
 exists at load

2. Shell Form:-

- Three legged
- Windings wrapped around the center leg: on on top of the other
- low voltage winding inner


why? to simplify problem of insulating the high voltage winding from the core and to reduce leakage flux

▷ Ideal Transformer

→ No losses device
 magnitude is changed

$$\frac{V_p(t)}{V_s(t)} = \frac{N_p}{N_s} = a$$


N : number of Turns
 a : turns ratio

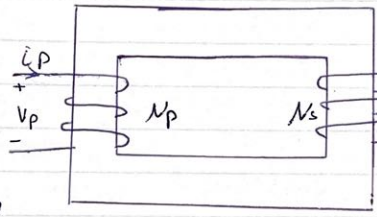

$$\frac{|i_p(t)|}{|i_s(t)|} = \frac{1}{a}$$

→ Phase angle is not affected
 → Frequency not affected

Schematic Symbol of a transformer

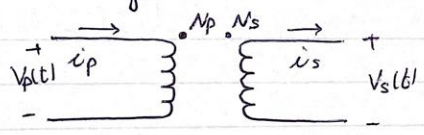

Faraday's law

$$V_p = N_p \frac{d\Phi}{dt}$$

$$V_s = N_s \frac{d\Phi}{dt}$$

▷ Dot connection

for voltage :- V_1, V_2 are both + or - at the dot
 → plus sign otherwise use negative

for Current :- I_1, I_2 are both out or into the dot
 → minus sign otherwise use positive

▷ Power in transformer (Ideal) [Watt]

used by R
 \vec{I} \vec{V}

$P_{in} = P_{out}$ (electrical \rightarrow to any energy)
 $V_p I_p \cos \theta_p = V_s I_s \cos \theta_s$
 equal = θ
P, real Power

used by L, C
 $L \rightarrow j\omega L$
 $C \rightarrow \frac{1}{j\omega C}$

$Q_{in} = Q_{out}$ [VAR] (magnetic field \rightarrow magnetic field)
 $V_p I_p \sin \theta_p = V_s I_s \sin \theta_s$

Q, reactive Power

Revision

Note:


S: Complex Power (apparent)


$$S = \vec{V}_{rms} \vec{I}_{rms}^*$$

$$= V_{rms} \angle \theta_v \cdot I_{rms} \angle -\theta_i$$

$$= V_{rms} I_{rms} \angle \theta_v - \theta_i$$

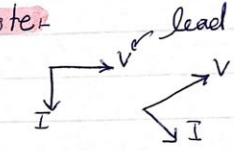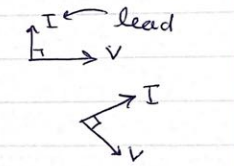
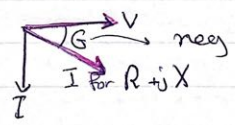
Note:



$+jQ$ L: 

$-jQ$ C: 

$$S = P + jQ = V_{rms} I_{rms} \underbrace{\cos \theta}_{PF} + V_{rms} I_{rms} \sin \theta j$$

Type of loads


RL  

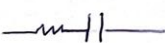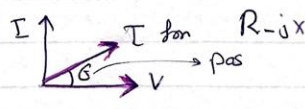RC  

▷ Impedance Transformation

Impedance: ratio of the phasor voltage across it to the phasor current flowing through it

$$Z_L = \frac{V_L}{I_L}$$

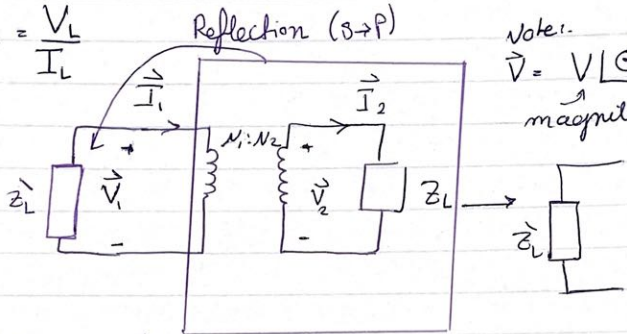

Note: $\vec{V} = V \angle \phi$
 ← phase angle
 ↑ magnitude


$$Z_i = \frac{\vec{V}_1}{\vec{I}_1} = a \frac{\vec{V}_2}{\frac{\vec{I}_2}{a}} = a^2 \frac{\vec{V}_2}{\vec{I}_2} = a^2 Z_L$$

• Reflection (P to S)

$$Z_i = \frac{1}{a^2} Z_L$$

→ Note we can use this to reduce complexity of questions

Example

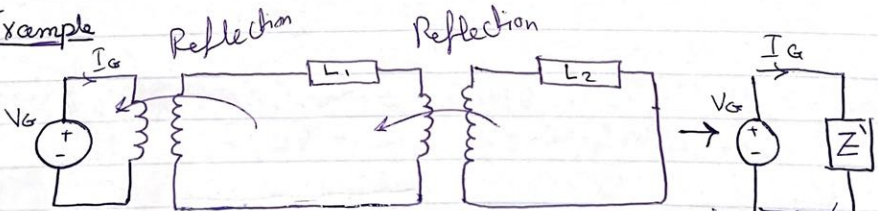


equivalent
 $I_{load}, V_{load} \neq I_g, V_g$

▷ losses for a real transformer there are losses to be considered

- Winding \leftarrow 1. **Copper losses** : Resistive heating losses in windings (R_p and R_s)
- core $\left\{ \right.$ 2. **Eddy Current losses** :- " " " in the core (R_c)
 $\hookrightarrow \propto V^2$ voltage applied to transformer
3. **Hysteresis** : associated with the rearrangement of the magnetic domains in the core during each half cycle.
 Complex, non linear function of the voltage applied to the transformer

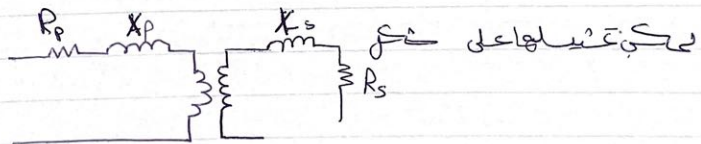Winding \leftarrow 4. **leakage flux** : fluxes and which escape the core and pass through only one of the transformer windings are leakage fluxes. They then produce self inductance in the primary and secondary coils



$R_p, R_s \rightarrow$ copper losses

$X_p, X_s \rightarrow$ leakage flux

$$e_{Lp}(t) = N_p \frac{d\Phi_{Lp}}{dt} = N_p^2 P \frac{di}{dt} \quad / \quad e_{Ls}(t) = N_s \frac{d\Phi_{Ls}}{dt} = N_s^2 P \frac{di}{dt}$$

leakage flux is proportional to current flow in primary and secondary windings \rightarrow

leakage flux

$$\text{So } \Phi_{LP} = (\mu N_p) i_p$$

$$\Phi_{Ls} = (\mu N_s) i_s$$

Where: $\mu = 1/R$ permeance of flux path

Re arranging equations:-

self inductance in primary coil = L_p

$$e_{LP}(t) = N_p \frac{d(\mu N_p) i_p}{dt} = \boxed{N_p^2 \mu} \frac{di_p}{dt}$$

$$e_{LP}(t) = L_p \frac{di_p}{dt} \quad \text{and similarly} \quad e_{Ls}(t) = L_s \frac{di_s}{dt}$$


Core excitation effects :- \rightarrow Primary circuit only

experimental

Magnetization current: $i_m \propto$ Voltage applied to core and lagging X_m by 90° across primary voltage source (in the unsaturated region)


+ hysteresis current

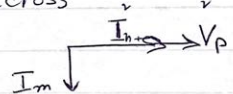Eddy current (core loss current): $i_{h,c} \propto$ voltage applied
 $\sim \sim$ in phase with R_c across




X_m, R_c are applied voltage modeled as loads

▷ Equivalent Circuit

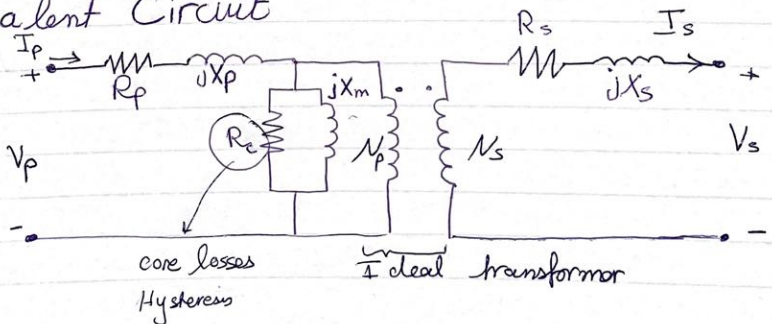


Using Impedance Reflection :-

Referred to primary

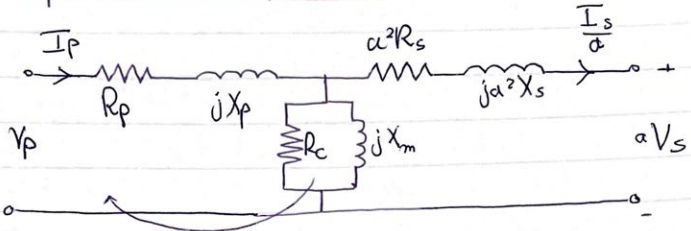


Referred to Secondary

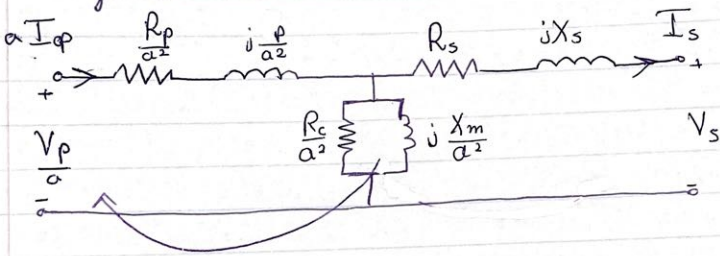

Note:-

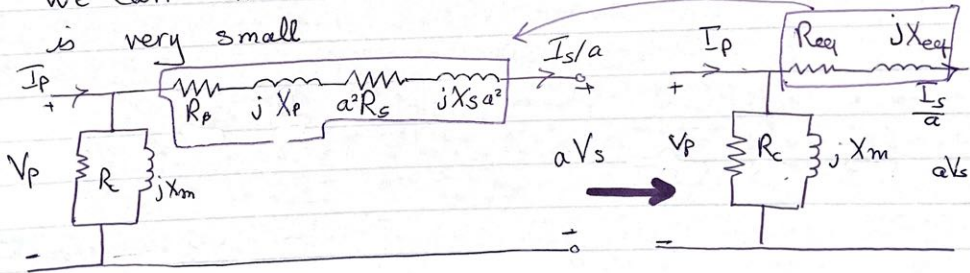We can move the branch since it is very small




$$R_{eq} = R_p + a^2R_s$$

$$jX_{eq} = j(X_p + a^2X_s)$$

for Secondary :-


$$R_{eq} = \frac{R_p}{a^2} + R_s$$

$$X_{eq} = \frac{X_p}{a^2} + X_s$$

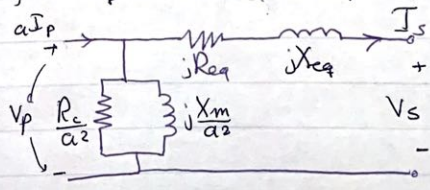

- For more simplicity consider I_m small, impedance is very high so open circuit

(We don't use it)

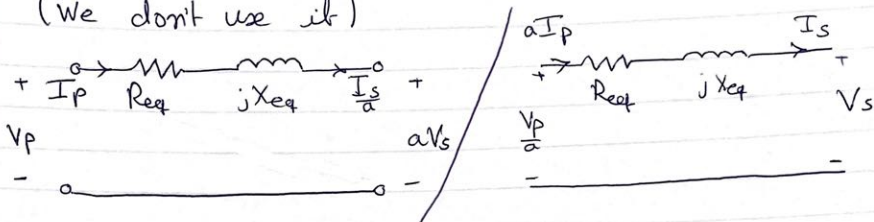

- ▷ To find losses (values of transformer model components)

$R_c =$


$X_m j =$

$R_{eq} =$

$e_{qj} =$


→ We use **open circuit test** and **short circuit test**

- Open circuit test :

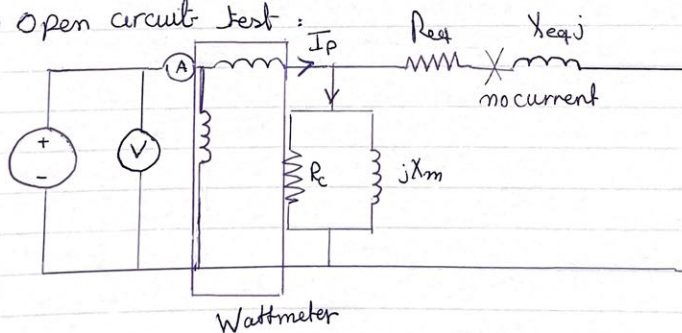

so I_p goes to R_c, jX_m only and we can find them How? page 9

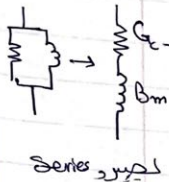• We notice that R_c and jX_m are parallel



Admittance of the branch $Y = Z^{-1}$

$$Y = \frac{1}{R_c} + \frac{1}{jX_m} = G_c - jB_m = Y \angle -\theta$$

angle
How do find it?

How does oper circuit works?

$W \rightarrow$ measures real Power

$A \rightarrow$ " Current

$V \rightarrow$ " Voltage

} From these we find θ

$$P = V_{oc} I_{oc} \cos \theta$$

$$P = V_{oc} I_{oc} PF$$

\rightarrow Magnitude of $Y = \frac{I_{oc}}{V_{oc}}$ (referred to primary)

\rightarrow Angle $\theta = \cos^{-1} \frac{P_{oc}}{V_{oc} I_{oc}}$

• So Y is found, thus G_c, B_m can be calculated

Question: Why is θ negative? Because the transformer is an inductor and so angle is :-


$$0 < \theta_v - \theta_i < 90$$

$$0 < -\theta_i < 90$$

\rightarrow so θ_i need to be negative

$$Y = \frac{I}{V} \angle -\theta_i = \frac{I}{V} \angle -\theta_i$$

Short circuit test

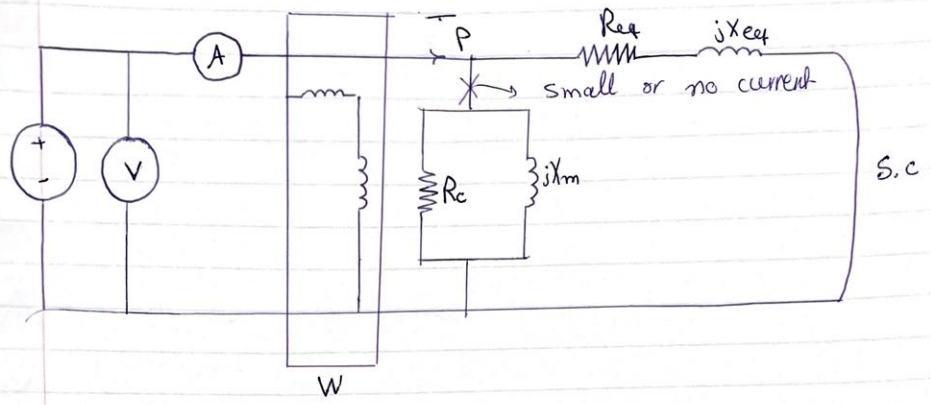

$$Z = R_{eq} + X_{eq}j = \frac{V_{sc}}{I_{sc}} \angle \theta$$

measured from V, A

$$\theta = \cos^{-1} \frac{P_{sc}}{I_{sc} V_{sc}}$$

measured from W

Question: why is θ positive: Because $I_{sc} = |I_{sc}| \angle -\theta$ as explained previously meaning that $Z = \frac{V_{sc} \angle \theta}{I_{sc} \angle -\theta}$ and so $Z = \frac{V_{sc} \angle \theta}{I_{sc}}$

Note:

In open circuit test: it is performed on the low voltage side because devices gives limited values of voltage (to reduce voltage to be measured)

(same for short circuit meaning that we need the current value to be measured by doing it on high voltage side)

▷ Per unit System

Voltage, current, power and impedance are measured in decimal fraction of some base value

$$\text{Quantity per unit} = \frac{\text{Actual value}}{\text{Base value of Quantity}}$$

System 11 12 13 14 15

Advantages

- 1) simplify calculations
- 2) Equivalent circuit can be simplified (like we did in impedance reflection to get rid of winding)

Usually base value of Power and Voltage

← only magnitude so all of them are of unit VA

$$P_{app} = P_{base} \cdot \theta = Q_{base} \cdot \theta = S_{base} \cdot \theta \rightarrow \text{Given}$$

$$I_{base} = \frac{S_{base} \cdot \theta}{V_{base} \cdot LN} \leftarrow \text{line to neutral (single phase)}$$

$$Z_{base} = R_{base} = X_{base} = \frac{V_{base} \cdot LN}{I_{base}}$$

$$Y_{base} = G_{base} = B_{base} = \frac{1}{Z_{base}}$$

} one phase

For three phase:-

$$S_{base} \cdot \theta = \frac{S_{base} \cdot 3\theta}{\sqrt{3}} \leftarrow \text{line to line}$$

$$V_{base} \cdot LN = \frac{V_{base} \cdot LL}{\sqrt{3}}$$

$$I_{base} = \frac{S_{base} \cdot 3\theta}{\sqrt{3} \cdot V_{base} \cdot LL}, \quad Z_{base} = \frac{V_{base} \cdot LL^2}{base \cdot 3\theta} = \frac{V_{base} \cdot LN}{I_{base}}$$

$$R_{base} = X_{base} = Z_{base} = \frac{1}{Y_{base}}$$

▷ Voltage regulation

(12)

Full load voltage regulation: It is used to compare the output voltage at no load with the output voltage at full load

$$VR = \frac{V_{s, nl} - V_{s, fl}}{V_{s, fl}} \times 100\%$$

For Ideal Transformer

$$VR = 0\%$$

$$V_{nl} = V_{fl} = \frac{V_p}{a}$$

- It is used to compare transformers

At the no load, Primary side :- $V_s = \frac{V_p}{a} = V_{nl}$
or Secondary

$V_{s, nl}$: Voltage at no load (output)


$V_{s, fl}$: Voltage at full load ()

الحسن الحظ
دفع أقل سبب
voltage

- To calculate $V_{s, nl}$, $V_{s, fl}$

$$-\frac{V_p}{a} + I_s (R_e + jX_e) + V_s = 0$$

No load : $\boxed{\frac{V_p}{a} = V_s}$

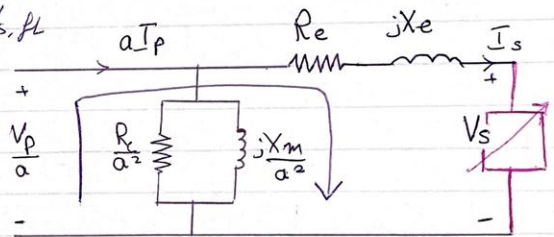


- ▶ With load (As Drawn with this)

$$V_s = \frac{V_p}{a} - \underbrace{I_s (Z_e)}_{\text{voltage drop}}$$

load ↑ → current ↑

▷ Transformer phasor diagram

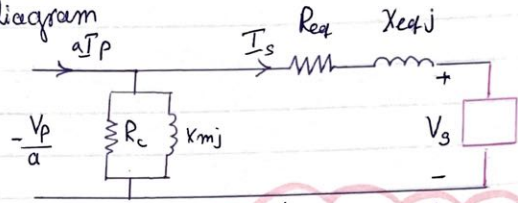

Types of loads:-

1. Resistive load:- (R)


Main Equation

$$V_s = \frac{V_p}{a} - I_s (R_{eq} + X_{eq}j)$$

Taking \vec{V}_s as reference

$$-\frac{\vec{V}_p}{a} + \vec{I}_s (R_{eq} + X_{eq}j) + \vec{V}_s = 0$$

R load means:
 V_s, I_s are in phase

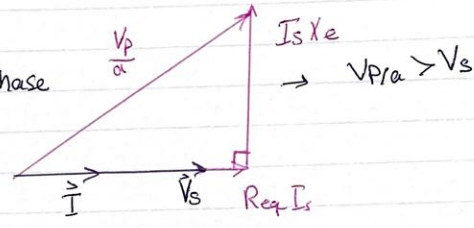


$V_R > 0$ (smaller than V_R lag)

2. Inductive load:- (R + Xj) (lagging PF) → $V_R > 0$

$$-\frac{V_p}{a} + \vec{I}_s (R_{eq} + X_{eq}j) + \vec{V}_s = 0$$


L load means:- I_s is lagging from V_s

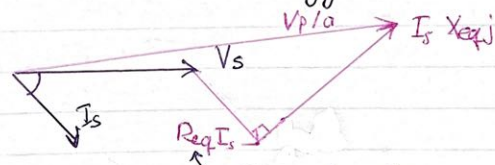

Does not change direction

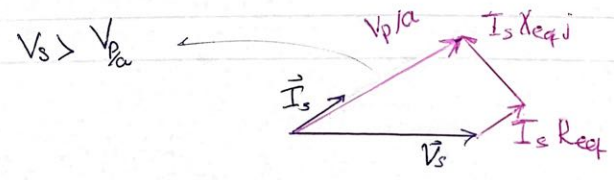3. Capacitive load:- (R - Xj)

load: I_s is leading (leading PF) → $V_R < 0$




→ When we have high capacitive load, V_s is large and so since current moves from high voltage to lower voltage it will reverse its direction.

• This is undesirable and needs to be prevented

▷ Transformer efficiency

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{P_{out}}{P_{loss} + P_{out}} \times 100\%$$

For transformers, generators and motors

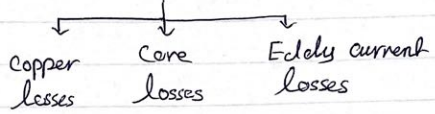


$$\text{for a transformer: } \eta = \frac{V_s I_s \cos \phi}{P_{cu} + P_{core} + V_s I_s \cos \phi} \times 100\%$$


▷ Three-phase transformer calculations wye γ or delta Δ

Important Example

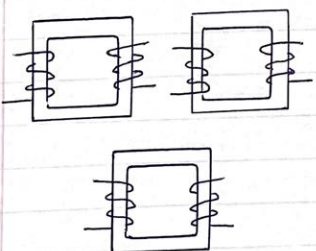To connect a three phase transfer we use:
Core form Shell form




Core form

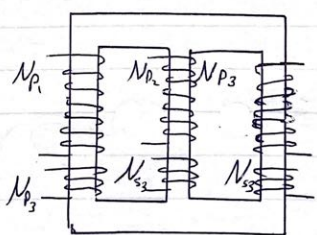


Shell form

Connections:-


Y-Y

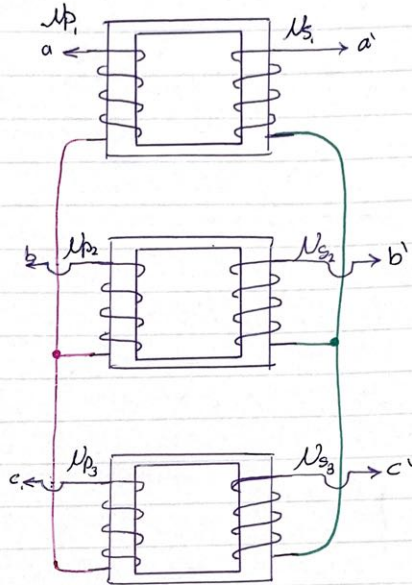


Y- Δ

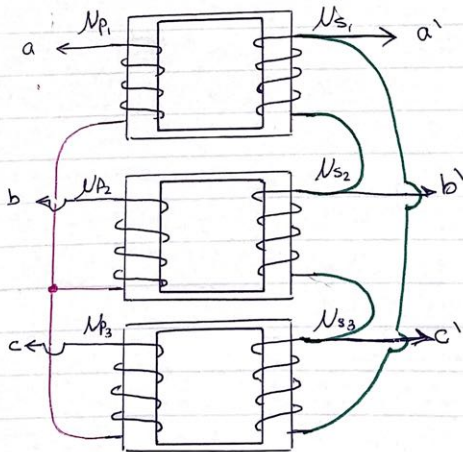

$\Delta - Y$:-

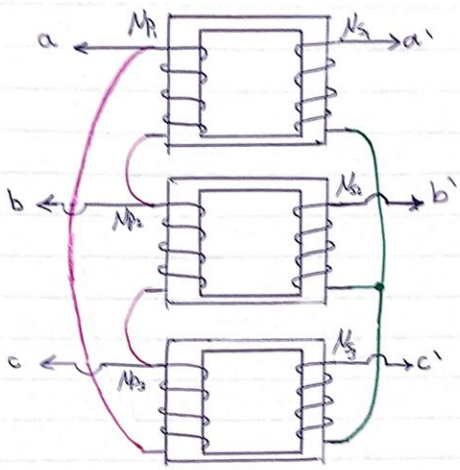

$\Delta - \Delta$:-

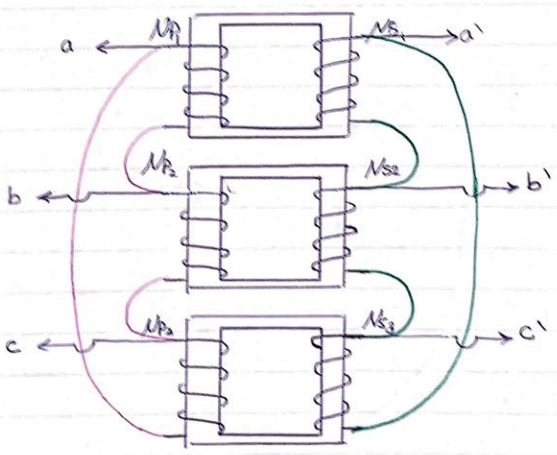

Impedance, voltage regulation, efficiency and similar calculation for 3-Phase are done on a per-Phase basis using same techniques

For Δ $V_{\phi P} = V_L$ $I_{\phi P} = \frac{I_L}{\sqrt{3}}$ $S_{\phi P} = \frac{S}{3}$

\uparrow phase Primary \downarrow line

For Y $V_{\phi P} = \frac{V_L}{\sqrt{3}}$ $I_{\phi P} = I_L$ $S_{\phi P} = \frac{S}{3}$

\uparrow phase second

Turns ratio = $\frac{V_{LP}^{Primary}}{V_{LS, secondary}}$

