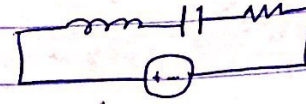


* Exp 11, Series and parallel Resonant Circuits


Series Resonance:-



→ Resonance occurs at min impedance and zero phase and at it: I_m is Max

- Resonance in RLC circuits occurs when inductive & capacitive reactances are equal in Magnitude but -180° in phase. ($X_C = X_L$)
 $\frac{1}{\omega C} = \omega L$

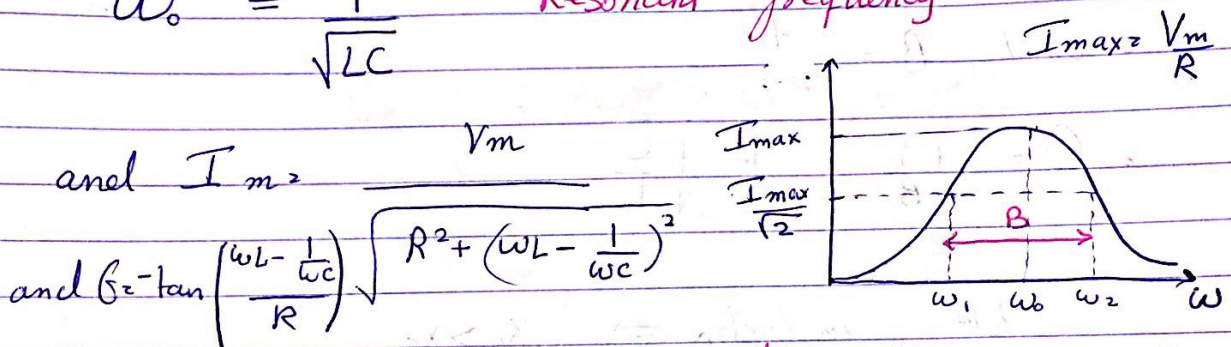$\omega_0 = \frac{1}{\sqrt{LC}}$ Resonant frequency



When $I = \frac{1}{\sqrt{2}} I_m \Rightarrow$ Band width $= B = \omega_2 - \omega_1 = \frac{R}{L}$

Where $\omega_{2,1} = \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \pm \frac{R}{2L}$


$\omega_{2,1} \Rightarrow$ 3 dB frequencies (half power frequencies) occur when $I_m = \frac{I_{max}}{\sqrt{2}}$

* Quality factor: $Q = \frac{\omega_0}{B} = \frac{1}{R} \sqrt{\frac{L}{C}}$

Now: V_R max is when $\omega = \omega_0$
 V_L max at $\omega = \frac{\omega_0}{\sqrt{1 - \frac{R^2 C}{2L}}}$
 V_C max at $\omega = \omega_0 \sqrt{1 - \frac{R^2 C}{2L}}$

Parallel Resonance:-

in this case

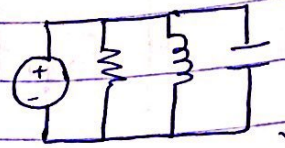

$$N_m = \frac{I_m}{\sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}}$$

$$\text{and } \beta = -\tan\left(R\left(\omega C - \frac{1}{\omega L}\right)\right)$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_{\pm} = \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \pm \frac{1}{2RC}$$

$$\text{and } \beta = \frac{1}{RC}$$

$$Q = \frac{\omega_0}{\beta} = R \sqrt{\frac{C}{L}}$$

Note, inductive $\Rightarrow X_L > X_C$
capacitive $\Rightarrow X_C > X_L$