


Exp 1: Network Theorems

• Proportionality :-

The response in a circuit is proportional to the Source acting in the circuit (linearity)

$$V_{out} = k V_{in}$$


constant \uparrow

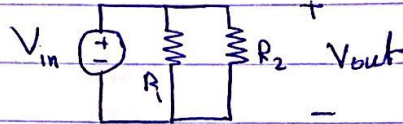



• Superposition :-

Responses are calculated individually by killing Sources.

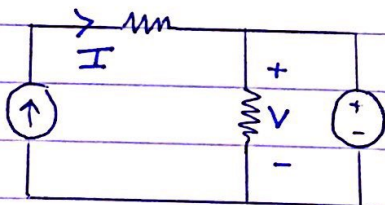Current Sources $\xrightarrow{\text{Turns to}}$ open Circuit
Voltage Sources $\xrightarrow{\text{Turns to}}$ Short Circuits



To find V :-

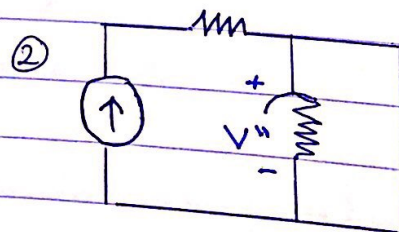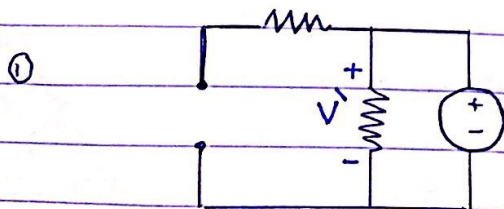

$$V = V' + V''$$

• Thevenin's Theorem

Replacing a circuit with an equivalent Voltage Source (V_{TH}) and an equivalent Resistor (R_{TH})

There are three cases for R_{TH} and V_{TH}

1- Circuit Contains only independent Sources

$$V_{TH} = V_{o.c}$$

Voltage Sources \rightarrow short circuit


Current \rightarrow open circuit

2- ~ ~ independent and dependent Sources.

$$V_{TH} = V_{o.c}$$

R_{TH} : There are two ways:-

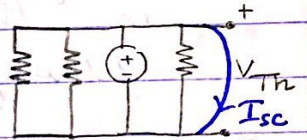find I_{sc} and $R_{TH} = \frac{V_{TH}}{I_{sc}}$




or $R_{TH} = \frac{V_T}{I_T}$
with killing independent Sources as in 1

V_T, I_T are assumed
 \hookrightarrow one of them are assumed and you find the other or

3- ~ ~ only dependent Sources

$$V_{TH} = 0 \quad \text{and} \quad R_{TH} = \frac{V_T}{I_T}$$

• Delta to Wye Equivalent Circuits

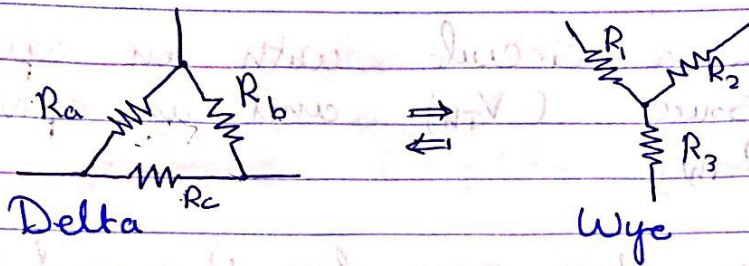

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_1 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

• Reciprocity Theorem

If you replaced two sources (current and voltage) in the circuit, the amount of current and voltage flowing in the circuit stays the same.

