

Exp 6: First Order Circuits :-

RC Circuits :- \rightarrow Natural response :- $V_C = k e^{-t/\tau}$ 88
 \rightarrow step response = $V_C = V_C(\infty) + V_f$
 $\rightarrow = V_S$ (Source)

$$\tau = RC$$

at $t < 0^-$: C: open Circuit
 at $t = 0^+$: C: voltage Source
 at $t > 0$: C: open Circuit

RL Circuits:

$$\tau = L/R$$

at $t < 0^-$: L: Short Circuit
 at $t = 0^+$: L: open Circuit
 at $t > 0$: L: Short Circuit

General form :-

$$r(t) = r(\infty) + [r(0^+) - r(\infty)] e^{-t/\tau}$$

where r is:
 i_L or V_C or any
 voltage or
 current

Note that :-

at $t = \infty$ (5τ) in step Response :-

