

Expt: Second Order Circuits

form $\frac{V}{R} + \frac{1}{L} \int V(t) dt + C \frac{dV}{dt} = \frac{i_c}{C}$
Series

RLC in Parallel

$\omega_0 = \frac{1}{\sqrt{LC}}$, $\alpha = \frac{1}{2RC}$

$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

Natural Response

$C \frac{d^2V(t)}{dt^2} + \frac{1}{R} \frac{dV(t)}{dt} + \frac{1}{L} V(t) = 0$
 $i_C \rightarrow \frac{d^2V(t)}{dt^2}$, $i_R \rightarrow \frac{dV(t)}{dt}$, $i_L \rightarrow V(t)$

- if $\alpha > \omega_0$: overdamped: $V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
 - if $\alpha = \omega_0$: Critical damping: $V(t) = A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$
 - if $\alpha < \omega_0$: underdamped: $V(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$
- where $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$

RLC in Series

$\omega_0 = \frac{1}{\sqrt{LC}}$, $\alpha = \frac{R}{2L}$

$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

$L \frac{d^2i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = 0$
 $i_L \rightarrow \frac{d^2i(t)}{dt^2}$, $i_R \rightarrow \frac{di(t)}{dt}$, $i_C \rightarrow i(t)$

Same Cases

$L \frac{di}{dt} + R i(t) + \frac{1}{C} \int i dt = V_s(t)$ Step Response

$V(t) = \frac{V_s}{V_s} \left(V_n + V_f \right)$

$i(t) = \frac{i_n + i_f}{i_s}$

- if Natural Response
 - Parallel $\rightarrow \frac{dy}{dt} = \frac{i_c(0^+)}{C}$
 - Series $\rightarrow \frac{dy}{dt} = \frac{i_L(0^-)}{C}$
- if Step Response
 - Series $\rightarrow \frac{dy}{dt} = \frac{i_L(0^-)}{C}$
 - Parallel \rightarrow