




Physics Department

Physics 112

*Report 7*

*Done by :Rayan Ghnimat.*

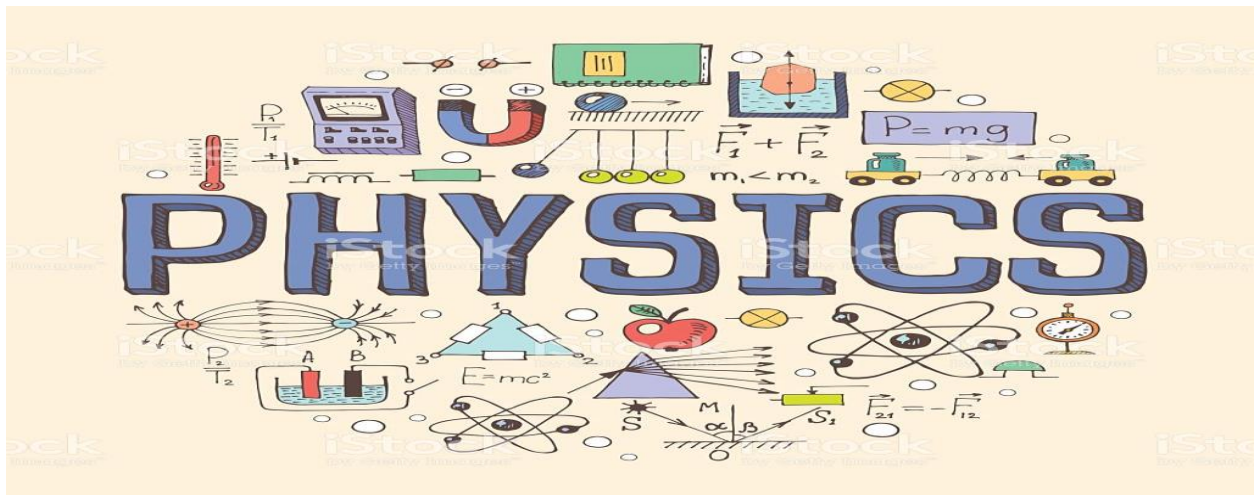*“The world is a book and those who do not travel read only one page.”*



9.5



BIRZEIT UNIVERSITY

Physics Department

Physics 112

Experiment Number 7:

Damped Oscillations

("يزرع الله الذين آمنوا منكم والذين أوتوا العلم درجات والله بما تعملون خبير")

Student's name: Rayan Ghnimat.


Student's no: 1211073.

Partner's name: Layan, Aya.

Partner's no. : 1211439

Section: 6

Instructor: Khalid eid.

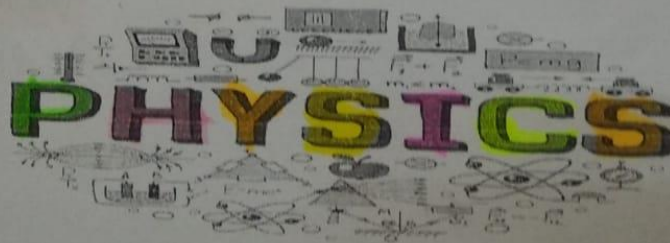

### Abstract:

1. **The Aim:** we did this experiment to study damped Oscillations in their 3 cases, Over damping, critical damping, under damping, it aims to find the ranges of values of the variable resistance where we can find the three types of oscillations, and finds the time constant of under damping situation.

2. **The method we used:** by measuring the voltage difference across the capacitor's plates using the CRO.

### Main results:

#### For Underdamping:

$$R = 0$$

$$\Delta t = 36 \mu s$$

$$F = 762.0$$

$$\omega = 2\pi f = 4785.36$$

$$\omega = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$L = 10 \times 10^{-3} \text{ H}, \delta_{\text{theo}} = \frac{R}{2L} = 9885 \text{ sec}^{-1}$$

$$C = 10 \text{ nF} = 10 \times 10^{-9} \text{ F}$$

$$R = 1997.7 \Omega \Rightarrow \frac{t}{\tau_{\text{theo}}} = \frac{2L \ln 2}{R}$$

$$= \frac{\ln 2}{\delta_{\text{theo}}}$$

$$= 6.93$$

#### For Critical Damping:

$$R = 1410 \Omega$$

$$\Delta t = 32 \mu s$$

$$V_{PP} = 2.92 \text{ V}$$

$$\frac{V_{PP}}{2} = 1.46 \text{ V}$$


#### For Overdamping:

$$R = 2000 \Omega$$

$$\Delta t = 64 \mu s$$
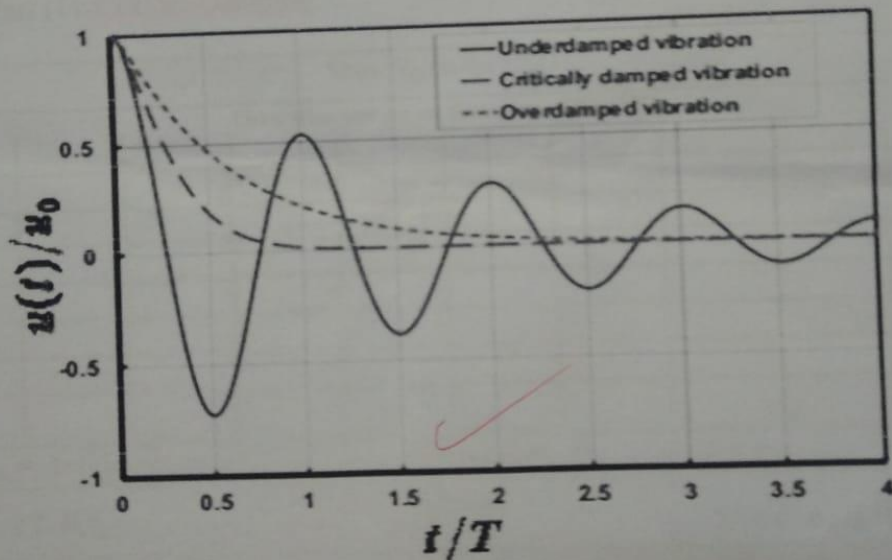
### - Introduction:

In this experiment, we expected to find time-half of the 3 cases: Under damping, Over damping and critical damping. Over damping is where the  $(R/2L)^2$  greater than  $(1/LC)$  it cases an exponential decay, Critical damping is when the  $(R/2L)^2$  equal  $(1/LC)$  which removes the root. Under damping is where the  $(R/2L)^2$  less than  $(1/LC)$  so under the square root becomes negative. Also we can find the frequency.



## Experiment 7

### Damped Oscillations

Student's Name: Rayan Ghnimt Student's No.: 1211073

Partner's Name: Layan, Aya Partner's No.: 1211439

Instructors Name: Khalid eid Section No.: 6

Date: 21 / 12 / 2022


C = find best value!      L = 10 mH      f = (300 - 1000) Hz

### -Data:

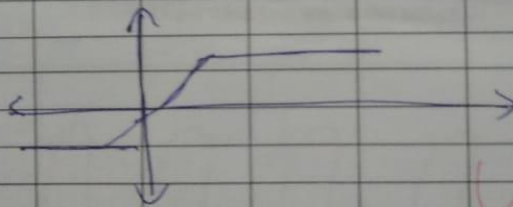Part (1): Critical-Damping

Show  $V_C$  on the DSO

Draw what you see on the screen of the DSO



$$R_{\text{critical}} = 1410 \Omega$$

$$t_{\frac{1}{2}\text{exp}} = 32 \text{ Ms}$$


$$\delta_{\text{C,Theo}} = \frac{R}{2L} = 70500$$

$$\delta_{\text{C,Exp}} = \frac{\ln 2}{T/2} = 21660.84$$

$$V_{PP} = 292 \text{ V}$$


$$\frac{V_{PP}}{2} = 1.46 \text{ V}$$

Part (2): Over-Damping

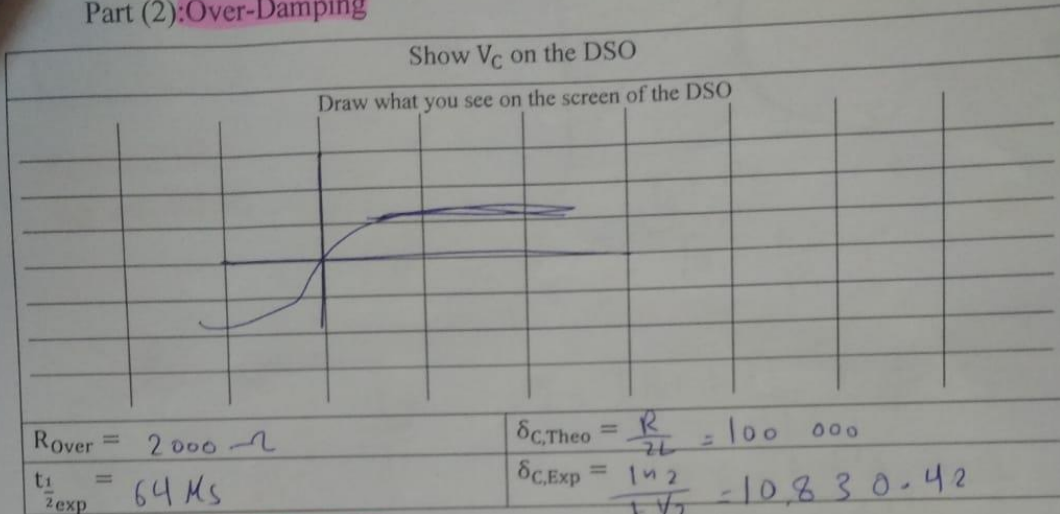


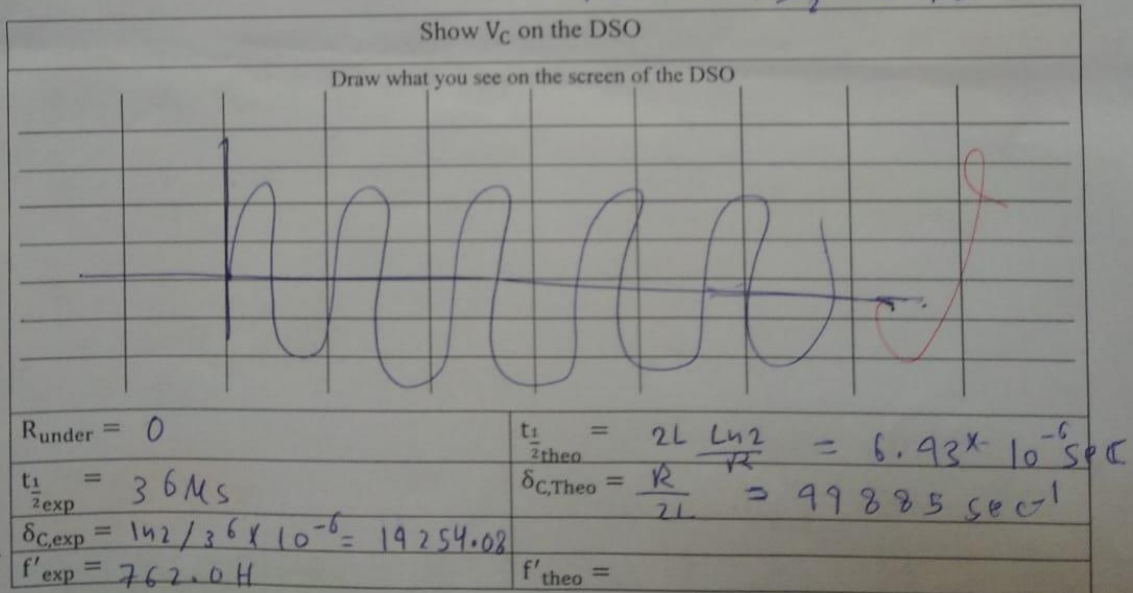Part (3): Under-Damping

$v_{pp} = 2.64, \frac{v_{pp}}{2} = 1.32 \text{ V}$




# Damped Oscillations

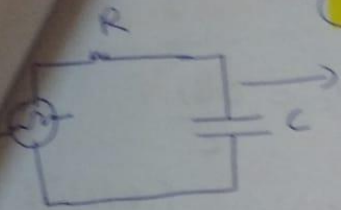


$$V_c = 0.63 V_0$$

$$V_d = 0.37 V_0$$

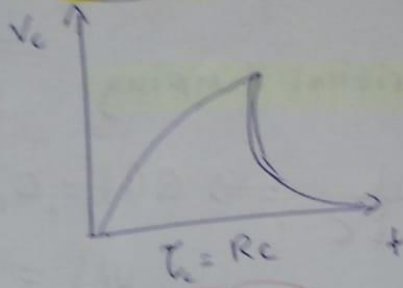

$$\tau_c = \frac{L}{R}$$

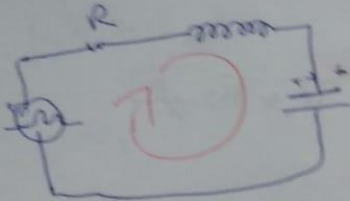

$$\begin{aligned} \Sigma &= IR + L \frac{dI}{dt} + \frac{Q}{C} \\ &= \frac{dQ}{dt} R + L \frac{d^2Q}{dt^2} + \frac{Q}{C} \end{aligned}$$

$$Q(t) = Q_{10} e^{-\lambda_+ t} + Q_{20} e^{-\lambda_- t} \quad \text{--- ①}$$


$$\lambda_+ = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\lambda_- = \frac{-R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

case 1

Overdamping  $\Rightarrow \left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$
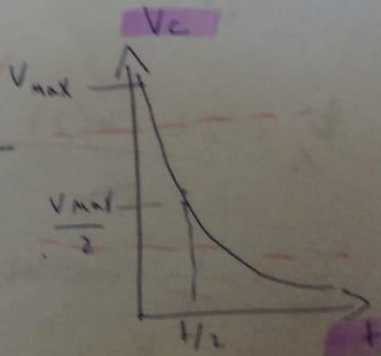
$$\left. \begin{aligned} \lambda &= 0 \\ \lambda &= \frac{-R}{L} \end{aligned} \right\} Q(t) = Q_0 e^{-\frac{R}{L} t}$$




## Case 2

case 2: critical damping

$$\Rightarrow V_c = \frac{Q(t)}{c}$$

$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC} \Rightarrow Q(t) = Q_{10} e^{-(R/2L)t} + Q_{20} e^{-(R/2L)t}$$
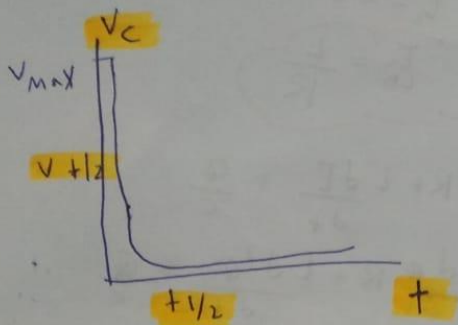
$$V(t) = V_0 e^{-(R/2L)t} + V_0 e^{-(R/2L)t}$$



$$\lambda = \frac{Ln 2}{t/2}$$

$$R_{exp} = R_0 + R$$

## Case 3

$$\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$$

under damping

$$\lambda = \frac{Ln 2}{t/2}$$

$$Q(t) = Q_0 e^{-\delta t} \cos(\omega' t + \theta_0)$$


$$\delta = \frac{R}{2L}$$

$$\omega = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$F_{1/2} = \frac{2L \ln(2)}{R_0}$$

$$F_{exp} = \frac{1}{T} \Rightarrow \omega_{exp} = 2\pi F_{exp}$$

$$R_0 = R$$

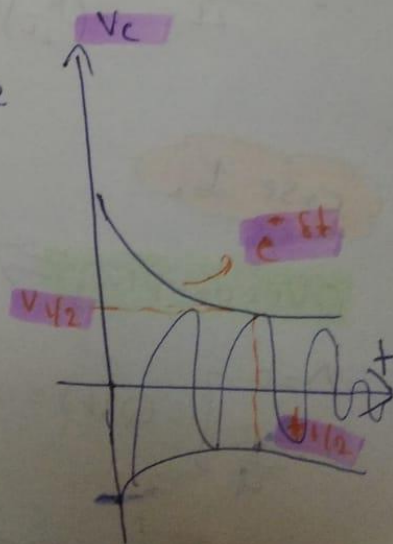



### Conclusion:

We see there are some errors like mistakes in reading the measurements. When we compare theoretical and the experiment values of RC we discover that they are close but there is little difference between them. As well as in the critical damping the voltage reach the min value faster than the over damping one .

✓