

second


BUZETTE UNIVERSITY
Physics 132
 Coordinator: Tawfiq ABOLUB

1st B. EXAM
TIME: 30 MIN

2nd Term 2011
21.4.2011

Student Name: <u> </u>	Student No.: <u> </u>
---	--

درج لكل (X) من التوزيع التالي لعدد من الأسئلة والمرة على رقم المسألة

المسألة	الدرجة	المسألة	الدرجة
3, 8	2	1, 2, 5	2
4, 9, 10	1	7, 9	1

المسألة
الدرجة
المسألة
الدرجة

- | | |
|--|---|
| 1) اشرح برفق الامتحان على وضع له بذلك | 1 |
| 2) اكتب اسمك ورقمك في اولى هذه الصفحة | 2 |
| 3) اذكر كم عدد الاسئلة التي تم التواجد الصحيح والخطا على هذه الصفحة. وذلك بوضع للدرجة (X) الى المسألة المناسبة | 3 |
| 4) اسأل الذي له اكثر من اجابة يظهر بالاحمر | 4 |
| 5) بعد اعادة اولى الاسئلة المتبقية | 5 |
| 6) حد الامتحان 17 سوالاً | 6 |


10

	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17
A							X		X	X							4
B	X			X										X			
C			X								X	X					
D	Y					X										1	
E				X			X						X				3

$Q = V_1 + V_2 + V_3$
 $Q = 9 \mu C \Rightarrow 4 \times 30 = 120 = 9V_1 \Rightarrow \frac{Q}{9} = C_1$
 $Z = 2i\sqrt{2} = 9i$
 $Z = C$

X Determine the energy stored in a capacitor when $C_1 = 10 \mu F$, $C_2 = 12 \mu F$, $C_3 = 15 \mu F$, and $V_0 = 30V$.

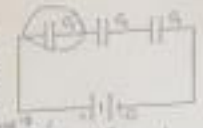$U = \frac{1}{2} CV^2$
 $U = 417mJ + 417 = 834mJ$
 $U = \frac{1}{2} \frac{Q^2}{C}$
 $U = \frac{1}{2} \frac{9^2}{C}$
 $U = 45 \frac{9^2}{C}$



- A) 4.5mJ
- B) 834mJ**
- C) 2.9mJ
- D) 2.1mJ
- E) 9.8mJ

$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$
 $\Rightarrow \frac{1}{10} + \frac{1}{12} + \frac{1}{15}$
 $\frac{6}{60} + \frac{5}{60} + \frac{4}{60} = \frac{15}{60}$
 $C_{eq} = 4 \mu F$

$120 + 150 = R_{eq} = 270$
 $1800 C_2 = 9 \mu F$
 $1800 C_3 = 15 \mu F$

X A 5.0 μF capacitor is connected in series with a 10 μF capacitor. A 220V AC source is connected across the series combination. What is the potential difference across the resistor?

- A) 10V
- B) 47V
- C) 22V
- D) 15V
- E) 41V**

$Q = CV$
 $I = \frac{Q}{t}$
 $I = 800$

$V = IR$
 $I = \frac{Q}{t} = \frac{5 \times 10^{-6}}{10 \times 10^{-6}} = 0.5 A$
 $V = 0.5 \times 80 = 40V$
 $R = \frac{V}{I} = \frac{40}{0.5} = 80 \Omega$
 $I = \frac{V}{R} = \frac{220}{80} = 2.75 A$
 $V = IR = 2.75 \times 80 = 220V$

X A certain substance has a dielectric constant of 2.7 and a dielectric strength of 16 MV/m. If it is used as the dielectric material in a parallel-plate capacitor, the minimum area should the plates of the capacitor have to obtain a capacitance of 15 nF and to ensure (assume the capacitor will be able to withstand a potential difference of 10 kV)

- A) 0.15 m²
- B) 0.27 m²
- C) 0.24 m²
- D) 0.18 m²**
- E) 0.48 m²

$K = 2.7$
 $C = 15 nF = 15 \times 10^{-9} F$
 $V = 10 kV = 10^4 V$
 $d = 0.5 m$
 $C = \frac{K \epsilon_0 A}{d}$
 $A = \frac{Cd}{K \epsilon_0} = \frac{15 \times 10^{-9} \times 0.5}{2.7 \times 8.85 \times 10^{-12}} = 307.8 m^2$
 $\frac{V}{d} = \frac{10^4}{0.5} = 2 \times 10^4 V/m$
 $\frac{V}{d} = \frac{16 \times 10^6}{0.5} = 3.2 \times 10^7 V/m$

$A = \frac{V^2 \epsilon_0}{K} = 310^{-9}$

(A)

$V = \frac{Qd}{K \epsilon_0 A}$
 $V = \frac{Qd}{K \epsilon_0 A}$

Page 2

$K \epsilon_0 A = \frac{CVd}{V}$
 $\frac{K \epsilon_0 A}{V} = \frac{CVd}{V}$
 $\frac{K \epsilon_0 A}{V} = A$

$\frac{8}{d} = 16$
 $d = 0.5 m$

$\frac{V}{d} = 16$

$$\rho_1 = 4 \times 10^{-8} \text{ } \Omega \cdot \text{m} \quad \rho_2 = 1.2 \times 10^{-6} \text{ } \Omega \cdot \text{m}$$

$$\epsilon_1 = 8.85 \times 10^{-12} \text{ } \text{C}^2/\text{N}\cdot\text{m}^2$$

$$\kappa = 1.6 \times 10^{-19} \text{ } \text{C} \quad \rho_0 = 9.1 \times 10^{-31} \text{ } \text{kg}$$



1. How long will it take a charged 80- μF capacitor to lose 20% of its stored energy when it is allowed to discharge through a 20- Ω resistor?

- A) 0.89 ms
- B) 0.27 ms**
- C) 0.40 ms
- D) 0.19 ms
- E) 0.20 ms

$$C = 80 \mu\text{F} = 8 \times 10^{-5} \text{ } \text{F} \quad u = 20\% \text{ } u_0$$

$$u = \frac{1}{2} CV^2 \Rightarrow u = \frac{1}{2} C V_0^2 \cdot 0.8$$

$$\Rightarrow \frac{1}{2} C V^2 = \frac{1}{2} C V_0^2 \cdot 0.8 \Rightarrow V = \sqrt{0.8} V_0$$

$$I = \frac{V}{R} \Rightarrow \frac{CV_0 \cdot 0.8}{R} = \frac{1}{R} \int_0^t \frac{dV}{dt} dt$$

$$\Rightarrow t = \frac{RC}{0.8} \ln \left(\frac{1}{\sqrt{0.8}} \right) = \frac{80 \times 10^{-6} \times 20}{0.8} \ln \left(\frac{1}{\sqrt{0.8}} \right) \approx 0.27 \text{ } \text{ms}$$

2. A light bulb is rated at 100 W when connected to a 120 V source. How much charge enters (and leaves) the light bulb in 1 min?

- A) 35 C
- B) 15 C
- C) 30 C
- D) 20 C**
- E) 60 C


$$P = IV \Rightarrow I = \frac{P}{V} = \frac{100}{120} = \frac{5}{6} \text{ } \text{A}$$

$$Q = I \cdot t = \frac{5}{6} \cdot 60 = 50 \text{ } \text{C}$$

(Note: The handwritten calculation shows a discrepancy with the multiple choice options, possibly due to a typo in the problem or solution.)

3. A 40- μF capacitor charged to 40 V and a capacitor charged to 20 V are connected to each other, with the two positive plates connected and the two negative plates connected. The final potential difference across the 40- μF capacitor is 30 V. What is the value of the capacitance of C?

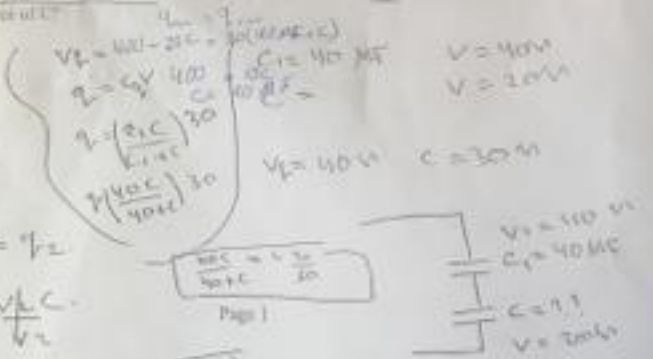- A) 40 μF
- B) 25 μF
- C) 30 μF**
- D) 55 μF
- E) 120 μF



$$Q_1 = Q_2$$

$$\left(\frac{40 \text{ } \mu\text{C}}{40 \text{ } \mu\text{F}} \right) 40 = \left(\frac{30 \text{ } \mu\text{C}}{40 \text{ } \mu\text{F}} \right) 40 + \left(\frac{30 \text{ } \mu\text{C}}{C} \right) C$$

$$\frac{40 \text{ } \mu\text{C}}{40 \text{ } \mu\text{F}} = \frac{30 \text{ } \mu\text{C}}{40 \text{ } \mu\text{F}} + \frac{30 \text{ } \mu\text{C}}{C}$$

$$\frac{1}{40} = \frac{3}{40} + \frac{3}{C} \Rightarrow \frac{1}{C} = \frac{1}{60} \Rightarrow C = 60 \text{ } \mu\text{F}$$

$$\frac{C_1 C_2}{C_1 + C_2} \Rightarrow C = 80 \text{ } \mu\text{F}$$

$$\frac{1}{C_1} + \frac{1}{C_2} \Rightarrow \frac{C_1 + C_2}{C_1 C_2}$$

$$40 \times 10^3 \text{ V} = E$$

A velocity selector with $E = 40 \text{ kV/m}$ and $B = 0.4 \text{ T}$, with $B = 40 \text{ mT}$. If the selector is designed ($m = 1$) to select 5 MeV electrons, then the value of E is

- (A) $210 \times 10^3 \text{ V/m}$
 (B) $126 \times 10^3 \text{ V/m}$
 (C) $33 \times 10^3 \text{ V/m}$
 (D) $168 \times 10^3 \text{ V/m}$
 (E) None of these

$$v = \frac{E}{B} \Rightarrow \frac{E}{B} = v$$

$$v = \frac{5 \times 10^6}{1.7 \times 10^8} = 2.94 \times 10^{-2} \text{ m/s}$$



Copper contains 8.4×10^{28} free electrons/m³. A copper wire of cross-sectional area 0.4 mm^2 carries a current of 6 A . The electron drift speed is approximately ($1 \text{ m} = 10^3 \mu\text{m}$)

- (A) $1.5 \times 10^4 \text{ m/s}$
 (B) $1.5 \times 10^3 \text{ m/s}$
 (C) $1.8 \times 10^4 \text{ m/s}$
 (D) $1.3 \times 10^4 \text{ m/s}$
 (E) $8.2 \times 10^4 \text{ m/s}$

$$n = 8.4 \times 10^{28} \text{ e/m}^3$$

$$A = 0.4 \text{ mm}^2$$


$$I = 6 \text{ A}$$

$$I = n e A v_d$$

$$v_d = \frac{I}{n e A} = \frac{6}{8.4 \times 10^{28} \times 1.6 \times 10^{-19} \times 0.4 \times 10^{-6}} = 1.5 \times 10^3 \text{ m/s}$$

A charged oil drop with a mass of $6.0 \times 10^{-16} \text{ kg}$ is held suspended by an upward electric field of 400 V/cm . The charge on the drop is

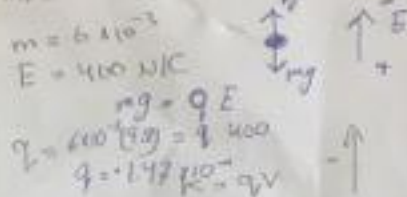- (A) $+1.5 \times 10^{-16} \text{ C}$
 (B) $-1.5 \times 10^{-16} \text{ C}$
 (C) $+1.5 \times 10^{-17} \text{ C}$
 (D) $-2.0 \times 10^{-17} \text{ C}$
 (E) None of these



$$q = m \cdot a$$

$$q = \frac{m \cdot g}{E}$$

$$\Rightarrow E = \frac{m \cdot g}{q}$$

$$\frac{1}{2} m v^2 = q V$$

$$E = \frac{q V}{q}$$

$$\frac{m \cdot g}{E} = \frac{q V}{E}$$


$$q = \frac{m \cdot g}{E} = \frac{6 \times 10^{-16} \times 10}{400} = 3 \times 10^{-17} \text{ C}$$

$$V_1 = I_1 R \Rightarrow 12 =$$

$$V_2 = 5 I_1$$

X The current in the $5.0\text{-}\Omega$ resistor in the circuit is
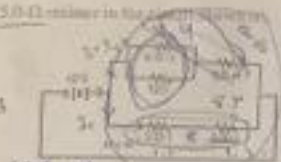
$$I = \frac{V}{R} \Rightarrow \frac{12}{4} = 3$$



$$\frac{12V}{4} I =$$

A) 1.5 A

B) 2.4 A

C) 3.0 A

D) 1.0 A

E) none of these

$$V = V_1 + V_2$$

$$12 = 3$$

$$R = 3\Omega + 5\Omega$$

$$L \quad A = \frac{V}{R} = \frac{12}{4} = 3$$

X A wire is 1.0 m long and 1 mm^2 in cross-sectional area. When connected to a potential difference of 3.2 V , a current of 3 A exists in the wire. The resistivity of this wire is

A) $1 \times 10^{-7}\text{ }\Omega\text{-m}$

B) $2 \times 10^{-7}\text{ }\Omega\text{-m}$

C) $4 \times 10^{-7}\text{ }\Omega\text{-m}$

D) $5 \times 10^{-7}\text{ }\Omega\text{-m}$

E) $3 \times 10^{-7}\text{ }\Omega\text{-m}$

$$R = \frac{V}{I} = \frac{3.2}{3}$$

$$V = IR, \quad I = 3, \quad V = 3.2$$

$$R = \frac{V}{I} = \frac{3.2}{3}$$

$$\rho = \frac{R \cdot A}{L} = \frac{\frac{3.2}{3} \cdot 1 \times 10^{-6}}{1} = 1.07 \times 10^{-6}$$

$$\Rightarrow \frac{3.2}{6} \cdot \frac{1}{3} = \frac{3.2}{18}$$

X A battery of emf 40 V and internal resistance of $2.0\text{ }\Omega$ is connected to an $18\text{-}\Omega$ resistor. The terminal potential difference of the battery is

A) 0

B) 45 V

C) 36 V

D) 18 V

E) 27 V

$$I = \frac{40}{2+18} = 2\text{ A}$$

$$V_{\text{in}} = 2 \times 18 = 36\text{ V}$$

$$R = 18\text{ }\Omega$$

$$40 - 18 \times 2 = 40 - 36 = 4\text{ V}$$

$$I = \frac{V}{R} = \frac{40}{2+18}$$

$$\Rightarrow \frac{2 \times 18}{18} = 2 = I$$

$V =$

$$\textcircled{C} \quad \textcircled{C} + \textcircled{C} = 0 \Rightarrow \frac{0}{0}$$

$$V = 2 \times 18 = 36$$

Page 4

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$V = IR$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$I = \frac{V}{R}$$

$$\Rightarrow I = \frac{VA}{dI}$$

$$\Rightarrow \frac{3.2 \times 1 \times 10^{-6}}{1 \times 10^{-6}}$$

$36 \times (0.01 \text{ J} + 0.02 \text{ k}) \Rightarrow$

* A wire 60 cm long lying along the x axis carries a current of 5 A in the positive x direction, through a magnetic field $\mathbf{B} = (0.10 \text{ T})\mathbf{i} + (0.60 \text{ T})\mathbf{j}$. The force on the wire is

- A) $-0.06\mathbf{i} + 0.12\mathbf{j}$ N
- B) $0.06\mathbf{i} + 0.12\mathbf{j}$ N
- C) $-0.06\mathbf{j} + 0.06\mathbf{k}$ N
- D) $0.06\mathbf{j} + 0.12\mathbf{k}$ N

$d = 60 \text{ cm}$
 $F = I \mathbf{L} \times \mathbf{B}$
 $F = 5 \text{ A} \times (0.60 \text{ T})\mathbf{j} \times (0.10 \text{ T})\mathbf{i} + (0.60 \text{ T})\mathbf{j}$
 $= 5(0.06)\mathbf{k} + 0.012\mathbf{j}$
 $= 0.06\mathbf{j} + 0.12\mathbf{k}$

14. Suppose the electric company charges 21 cents per kWh. How much does it cost to use a 100-watt lamp 8 hours a day for 30 days? ($1 \text{ kWh} = 1000 \text{ watt-h}$)

- A) \$1.20
- B) \$5.40
- C) \$0.50
- D) \$1.20
- E) none of these

Exp: $P = 100 \text{ W}$
 $t = 8 \text{ h/day} \times 30 \text{ days} = 240 \text{ h}$
 $E = P \times t = 100 \text{ W} \times 240 \text{ h} = 24000 \text{ Wh} = 24 \text{ kWh}$
 $\text{Cost} = 24 \text{ kWh} \times 21 \text{ cents/kWh} = 504 \text{ cents} = \5.04

15. In the circuit shown, $V = 6.0 \text{ V}$ and the capacitor is initially uncharged. At time $t = 0$, switch K is closed. If τ is the time constant, the approximate current through the 1Ω resistor when $t = 7\tau$ is

- A) 0.15 A
- B) 0.11 A
- C) 0.09 A
- D) 0.13 A
- E) none of these

$q(t) = C \mathcal{E} (1 - e^{-t/\tau})$
 $I = \frac{dq}{dt} = \frac{C \mathcal{E}}{R} e^{-t/\tau}$
 $I = \frac{1.5 \text{ C} \times 6.0 \text{ V}}{3 \Omega} e^{-7}$
 $I \approx 0.11 \text{ A}$

$Q = C \mathcal{E}$

$I = \left(\frac{C \mathcal{E}}{R} \right) e^{-t/\tau}$

$I = \left(\frac{8.85 \times 10^{-12} \text{ m}^2}{3} \right) e^{-7}$

Page 5

$I \Rightarrow \left(\frac{8.85 \times 10^{-12}}{3} \right) e^{-7/2}$

16. An electron ($m = 9.1 \times 10^{-31} \text{ kg}$) with speed 8000 m/s is prepared into a uniform magnetic field B of 0.7 mT with its velocity vector making an angle of 45° with B . The pitch of the path is:

- A) 0.34 m
 B) 0.80 m
 C) 1.6 m
 D) 0.71 m
 E) none of these

$$F_{\text{net}} = v_{\perp} T$$

$$= 4 \times 10^4 \text{ T}$$



$$T = \frac{2\pi r}{v_{\perp}} = \frac{2\pi m}{qB} = 1.28 \times 10^{-7}$$

17. In a Hall effect experiment, a current of 3 A is sent through a copper wire, 3 cm long, 1 cm wide, and 1 mm thick. The magnetic field B is 0.4 T . Hall potential difference V_H is (The number of charge carriers per unit volume for copper is $8.5 \times 10^{28} \text{ electrons/m}^3$)

- A) $2.8 \times 10^{-4} \text{ V}$
 B) $3.0 \times 10^{-4} \text{ V}$
 C) $1.1 \times 10^{-4} \text{ V}$
 D) $8.3 \times 10^{-4} \text{ V}$
 E) None of these

$$I = qnAv$$

$$qE = qvB$$

$$E = vB$$

$$\frac{V}{L} = \frac{v}{B}$$

$$v = \frac{EL}{B}$$



$$A = L \cdot w \cdot t$$



$$R = \frac{I B}{e n t}$$

$$e n t$$

$$V = \frac{I B}{e n t}$$

$$e n t$$

$$= 3 \text{ A} \cdot 0.4$$

$$1.6 \times 10^{-19} \cdot 8.5 \times 10^{28} \cdot 1 \times 10^{-3}$$

$$= 8.3 \times 10^{-4}$$


BIRZET UNIVERSITY
 -Physics Department-
Physics 132

2nd hour exam
 Time: 80-90 min

2nd Semester 2012/2013
 Date: 28/4/2013

Coordinator: Ghassan Abbas

Student Name: Diana Rowan Student NO.: 1100224

اسم الطالب (X)	Instructor Name	Section No.	
X	Dr. Ghassan Abbas	1,2D	1100224
	Dr. Ghassan Abbas	3,4,5,6D	
	Dr. Ghassan Abbas	7,8,10D	
	Dr. Ghassan Abbas	9D	

Answer Sheet:

Q#	A	B	C	D	E
1					X
2		X			
3			X		
4	X				
5					X
6				X	
7		X			
8			X		
9		X			
10	X				
11			X		
12					X
13	X				
14				X	
15		X			
16					X
17				X	

15

$\mu = 1.6 \times 10^{-19} \text{ C}$

$m_e = 9.1 \times 10^{-31} \text{ kg}$

$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2$

$\mu_0 = 4\pi \times 10^{-7} \text{ Tm/A}$

$1 \text{ eV} = 1.6 \times 10^{-19} \text{ J}$

phys132-22-212

Multiple Choice

Identify the choice that best completes the statement or answers the question.

1. A parallel plate capacitor of capacitance C_0 has plates of area A with separation d between them. When it is connected to a battery of voltage V_0 , it has charge of magnitude Q_0 on its plates. While it is connected to the battery, the space between the plates is filled with a material of dielectric constant ϵ_r . After the dielectric is added, the magnitude of the charge on the plates and the new capacitance are

a. $\frac{2}{3}Q_0$, $\frac{1}{3}C_0$

b. Q_0 , $\frac{1}{3}C_0$

c. Q_0 , C_0

d. $3Q_0$, C_0

e. $3Q_0$, $3C_0$

$$C = \frac{Q}{V} \rightarrow 3 C_0$$

$$V = \frac{Q}{C} = \frac{3Q_0}{3C_0} = \frac{Q_0}{C_0} = V_0$$

2. A certain parallel plate capacitor is filled with a dielectric material with $\epsilon_r = 2.5$ and a dielectric strength of $2.0 \times 10^6 \text{ V/m}$. The area of each plate is 0.01 m^2 . The capacitor will be able to withstand a potential difference of _____ V. The capacitance of this capacitor is _____ F.

a. $7.1 \times 10^7 \text{ V}$

b. $1.3 \times 10^7 \text{ V}$

c. $2.5 \times 10^7 \text{ V}$

d. $2.5 \times 10^8 \text{ V}$

e. $5.1 \times 10^7 \text{ V}$

$$F = \frac{Q}{V}$$

$$2.5 \times 10^6 = \frac{Q}{V} \rightarrow Q = 2.5 \times 10^6 V$$

$$C = \frac{Q}{V} = \frac{2.5 \times 10^6 V}{V} = 2.5 \times 10^6 \text{ F}$$

$$C = \frac{\epsilon_r \epsilon_0 A}{d}$$

$$2.5 \times 10^6 = \frac{2.5 \times 8.85 \times 10^{-12} \times 0.01}{d} \rightarrow d = \frac{2.5 \times 8.85 \times 10^{-12} \times 0.01}{2.5 \times 10^6} = 1.3 \times 10^{-17} \text{ m}$$

3. An air-filled parallel plate capacitor has a capacitance of 2.1 pF . The separation of the plates is doubled, and WAX is inserted between them. The new capacitance is 2 pF . The dielectric constant of the WAX is _____.

a. 1.2

b. 0.8

c. 1.3

d. 5.0

e. 1.6

$$C = \frac{\epsilon_r \epsilon_0 A}{d}$$

$$2.1 = \frac{\epsilon_r \epsilon_0 A}{2d}$$

$$2 = \frac{\epsilon_r \epsilon_0 A}{2d}$$

$$\epsilon_r = 2 \left(\frac{2.1}{2} \right) = 2.1$$

$$2.1 = \frac{\epsilon_r \epsilon_0 A}{d}$$

$$2 = \frac{\epsilon_r \epsilon_0 A}{2d}$$

$$2C = \frac{\epsilon_r \epsilon_0 A}{d}$$

$$2C = \frac{\epsilon_r \epsilon_0 A}{d} = \frac{2.1 \times 2C}{2} = 2.1 C$$

4. Three electrons pass through a $20 \text{ }\Omega$ resistor in 70 ns if there is a potential drop of 70 mV across it.

a. 1.5×10^{18}

b. 8.4×10^{18}

c. 1.1×10^{18}

d. 3.8×10^{18}

$$I = \frac{V}{R}$$

$$= \frac{70}{20}$$

$$= 3.5 \text{ A}$$

$$\frac{dQ}{dt} = 3.5 \text{ A}$$

$$Q = t \times A$$

$$= 70 \times 3.5$$

$$= 245 \text{ C}$$

$$= 245 \times 1.6 \times 10^{-19}$$

$$= 3.92 \times 10^{-17}$$

$$= 3.92 \times 10^{18}$$

$$Q = eN = 900$$

$$N = 5.625 \times 10^{18}$$

$$900 = 1.6 \times 10^{-19} N$$

$$\uparrow R = \frac{\rho L}{A}$$

Name: _____

2. Helen says that you can increase the resistance of a copper wire by making the wire narrower and longer. Alvin says that you can increase its resistance by heating the wire. Which one, if either, is correct, and why?
- Alvin, because the resistivity of the wire increases when it is heated.
 - Alvin, because the resistivity of the wire decreases when it is heated.
 - Helen, because the resistivity of a wire is inversely proportional to its area and directly proportional to its length.
 - Helen, because the resistance of a wire is inversely proportional to its area and directly proportional to its length.

(c) Both are correct because (b) and (d) are both correct.

3. The current density in a cylindrical wire of radius R is varies with radial distance r in $J = ar$. The current in the wire is

- $2aR^2$
- $2aR^3$
- $aR^2/2$
- $2aR^3/3$

$\frac{2}{3} aR^3$

$$I = \int I \cdot dA = \int 0 \text{ to } R 2\pi r \cdot ar \cdot dr = \pi a \int 0 \text{ to } R 2r^2 dr = 2\pi a \frac{1}{3} R^3 = \frac{2}{3} \pi a R^3$$

4. A battery of emf 24 V is connected to a 6- Ω resistor. As a result, current of 3 A exists in the resistor. The internal resistance of the battery is:

- 5- Ω
- 2- Ω
- 3- Ω
- 200

$2-\Omega$

$$3 = \frac{24}{6+r} \quad 3(6+r) = 24 \quad 18+3r = 24 \quad 3r = 6 \quad r = 2\Omega$$

5. A certain capacitor, in series with a 720- Ω resistor, is being charged. At the end of 10 μ s its charge is half the final value. The capacitance is about:

- 9.5 μ F
- 14 μ F
- 30 μ F
- 10F

$30 \mu F$

$$Q = CE \left(1 - e^{-t/RC}\right) \quad \frac{1}{2} CE = CE \left(1 - e^{-t/RC}\right) \quad \frac{1}{2} = 1 - e^{-t/RC} \quad e^{-t/RC} = \frac{1}{2} \quad \ln e^{-t/RC} = \ln \frac{1}{2} \quad -\frac{t}{RC} = -\ln 2 \quad \frac{t}{RC} = \ln 2 \quad RC = \frac{t}{\ln 2} = \frac{10 \mu s}{0.693} \approx 14.4 \mu s$$


6. A charged capacitor with Q_0 is being discharged through a resistor. At the end of two time constants the charge on the capacitor is:

- $0.87 Q_0$
- $0.14 Q_0$
- $0.40 Q_0$
- $0.13 Q_0$

$0.14 Q_0$

$$Q = Q_0 e^{-t/\tau} \quad \tau = 2 \tau \quad Q = Q_0 e^{-2} = 0.135 Q_0$$

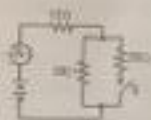16. When switch S is open, the ammeter in the circuit shows a reading of 2.0 A . When S is closed, the ammeter reading:



$$R = \frac{V}{I}$$

$$V = IR$$

$$I = \frac{V}{R}$$


$$E = 70$$

$$\frac{70}{30}$$

$$\frac{60 \times 20}{80} = 15$$

- (a) increases slightly
 b. remains the same
 c. decreases slightly
 d. doubles
 e. halves

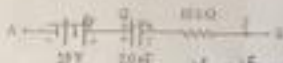17. Determine the potential difference, $V_A - V_B$, in the circuit segment shown below when $I = 2.0\text{ mA}$ and $Q = 30\text{ nC}$.



- a. -41 V
 b. $+40\text{ V}$
 c. $+20\text{ V}$
 d. -20 V
 e. -10 V

$$V_A - V_B = 15 - \frac{Q}{C} + IR + \frac{Q}{C}$$

$$V_A - V_B = 15 - \frac{30 \times 10^{-9}}{20 \times 10^{-9}} + 2 \times 10^{-3} \times 10 + \frac{30 \times 10^{-9}}{20 \times 10^{-9}}$$

$$V_A - V_B = 15 - 1.5 + 20 \times 10^{-3} + 1.5 = 15 + 20 \times 10^{-3} = 15.2\text{ V}$$

18. A proton (charge $+1.6 \times 10^{-19}\text{ C}$) is moving at $3 \times 10^6\text{ m/s}$ in the positive x direction. A magnetic field of 0.8 T is in the positive x direction. The magnetic force on the proton is:

- a. 0
 b. $4 \times 10^{-14}\text{ N}$ in the positive x direction
 c. $4 \times 10^{-14}\text{ N}$ in the negative x direction
 d. $4 \times 10^{-14}\text{ N}$ in the positive y direction
 e. $4 \times 10^{-14}\text{ N}$ in the negative y direction

$q \times v \times B$ Proton

$q \times v \times B$

19. A deflection is measured 20 cm from the 10-kV potential difference and then moves perpendicularly to a uniform magnetic field with $B = 1.6\text{ T}$. What is the radius of the resulting circular path (electron: $m = 9.1 \times 10^{-31}\text{ kg}$, $e = 1.6 \times 10^{-19}\text{ C}$)

- a. 12 mm
 b. 15 mm
 c. 20.1 mm
 d. 10 mm
 e. 15.0 mm

$$\frac{1}{2} (1.6 \times 10^{-19})^2 (1.6 \times 10^6)^2 (1.6 \times 10^{-19})^2$$

$$V = 9.8 \times 10^3$$

$$EV = E_m = \frac{1}{2} mv^2$$

$$V = \frac{1}{2} \frac{mv^2}{e}$$

$$\frac{1}{2} mv^2 = 9.8 \times 10^3$$

$$r = \frac{mv}{qB} = 0.0126 = 12.6 \times 10^{-3}$$

2nd Hour Exam
 Time: 75 Minutes

First Summer 2103
 7/7/2013

Student Name: <i>Abdelhadi Joud</i> Student Number: <i>1191229</i>

اسم المدرس (X) م/م	Instructor Name	Section No.
	م. هادي جود	4D
	م. خالد	3JD
X	م. جود	1D

Answer Sheet

Q#	A	B	C	D	E
1					XX
2					XX
3				X	
4		XX			
5			X		
6					XX
7				X	
8			X		
9	X				
10					XX
11				XX	
12				XX	
13	XX				
14	XX				
15	X				
16					X

$R_1 = \frac{\rho(L_1)^2}{A}$ $R_2 = \frac{\rho(L_2)}{A}$ $\rho = \frac{R_1 A}{L_1} = \frac{R_2 A}{L_2}$
 $R = \frac{\rho(L)}{A}$ $R_2 = \frac{R_1}{4}$ $R_1 = \frac{\rho(L)}{A}$ $R_2 = \frac{\rho(L)}{4A}$

Name: _____ Class: _____ Date: _____

PHYS132-2SD

$R_1 = \frac{\rho(L)}{A}$, $R_2 = \frac{\rho(L)}{4A}$ ρ
 $A_2 = 4A$


Multiple Choice: Identify the choice that best completes the statement or answers the question.

ch 29

1. Two parallel long wires carry the same current and repel each other with a force F per unit length. If both these currents are doubled and the wire separation tripled, the force per unit length becomes:
- 4F
 - 2F
 - 6F
 - 20F
 - 40F

$f = \frac{\mu_0 I_1 I_2}{2\pi r}$ ϵ $\frac{4 \times 10^{-7} T^2 A^2}{2\pi \times 3r}$

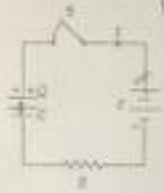2. At $t = 0$ the switch S is closed with the capacitor uncharged. If $\mathcal{E} = 20.0 \text{ V}$, $R = 10.0 \text{ }\Omega$, and $C = 10.0 \text{ }\mu\text{F}$, what is the potential difference across the capacitor when $I = 2.0 \text{ mA}$?



- 25 V
- 20 V
- 15 V
- 10 V
- 5 V

$V_C = \mathcal{E}(1 - e^{-t/\tau})$ $\tau = RC = 10 \times 10^{-6} = 10^{-5} \text{ s}$
 $I = \frac{\mathcal{E}}{R} e^{-t/\tau} = 2.0 \text{ mA}$
 $2.0 \times 10^{-3} = \frac{20}{10} e^{-t/10^{-5}}$
 $0.2 = e^{-t/10^{-5}}$
 $\ln(0.2) = -\frac{t}{10^{-5}}$
 $t = -10^{-5} \ln(0.2) = 1.61 \times 10^{-5} \text{ s}$
 $V_C = 20(1 - e^{-1.61 \times 10^{-5}/10^{-5}}) = 20(1 - e^{-1.61}) = 20(1 - 0.2) = 16 \text{ V}$

3. A resistor of radius r , length L and resistivity ρ is connected to a battery. What is the new resistance if it is stretched to 4 times its original length?



$R = \frac{\rho L}{A}$ $R' = \frac{\rho(4L)}{\pi(r/2)^2} = \frac{4\rho L}{\pi r^2/4} = 16 \frac{\rho L}{\pi r^2} = 16R$

4. Suppose the current density in a wire of length L and diameter D , you can

- increase the potential difference between the two ends of the wire.
- increase the potential difference between the two ends of the wire.
- increase the magnitude of the electric field in the wire.
- heat the wire to a higher temperature.
- combine both (b) and (d).

$J = nqv = \frac{I}{A}$ $V = IR$

$J = \frac{I}{A}$

$F = J \eta$

$\Delta V = I R$

$$22.8 \times 10^{-1}$$

$$V_{out} = 0.38$$

$$0.01$$

$$0.02$$

Name: _____


$$380 \frac{mV}{C \cdot V}$$

$$q_1 = 410^{-9} \cdot 50V = 20.5 \text{ nC}$$

$$C_1 + C_2 = 10^{-9} + 10^{-9} = 2 \times 10^{-9} F$$


2. A $44 \mu F$ capacitor initially charged to $30 V$ and a $5.6 \mu F$ capacitor charged to $50 V$ are connected to each other with the positive plate of each connected to the negative plate of the other. What is the final charge on the $44 \mu F$ capacitor?

- a. 12 nC
 b. 20 nC
 c. 10 nC
 d. 10 mC

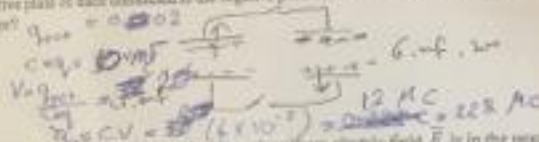

3. An electron is travelling in the positive x direction. A uniform electric field \vec{E} is in the negative y direction. If a uniform magnetic field with the appropriate magnitude and direction also exists in the region, the total force on the electron will be zero. The appropriate direction for the magnetic field is:

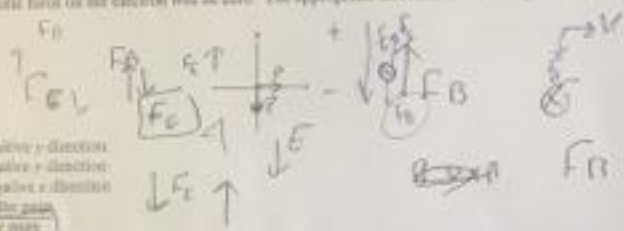- a. the positive x direction
 b. the negative x direction
 c. the negative z direction
 d. out of the page
 e. into the page



4. An electron (charge $-1.6 \times 10^{-19} C$) is moving in the xy plane, the components of its velocity being $v_x = 3 \times 10^6 \text{ m/s}$ and $v_y = 1 \times 10^6 \text{ m/s}$. A magnetic field of $0.8 T$ is in the positive z direction. At that instant the magnitude of the magnetic force on the electron is:

- a. $6.4 \times 10^{-14} N$
 b. $2.4 \times 10^{-14} N$
 c. 0
 d. $3.8 \times 10^{-14} N$
 e. $1.8 \times 10^{-14} N$

$$F_B = qv \times B = (-1.6 \times 10^{-19} C) \sqrt{(3 \times 10^6)^2 + (1 \times 10^6)^2} (0.8 T)$$

5. A parallel plate capacitor of capacitance C , the plates of area A with separation of d between them. When it is connected to a battery of voltage V_0 , it has charge of magnitude Q_0 on its plates. While it is connected to the battery, the space between the plates is filled with a material of dielectric constant κ . After the dielectric is added, the magnitude of the charge on the plates and the potential difference between them are:

- a. κQ_0 , $\frac{V_0}{\kappa}$
 b. $\frac{Q_0}{\kappa}$, V_0
 c. κQ_0 , V_0
 d. $\frac{Q_0}{\kappa}$, $\frac{V_0}{\kappa}$
 e. κQ_0 , V_0

$$Q = \kappa C V_0$$


$$C = \frac{\epsilon_0 \kappa A}{d}$$

$$C_1 \cdot C_2$$

$$V_0 = q_0$$

$$q = C \cdot V$$

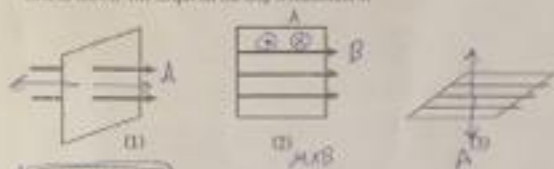9. A square loop is rotated at three different positions relative to a uniform magnetic field. In position 1 the plane of the loop is perpendicular to the field lines. In position 2 and 3 the plane of the loop is parallel to the field as shown. The torque on the loop is maximum in



10. position 2 and 3
 a. position 2
 b. position 1
 c. position 3
 d. all three positions.

$$\mu \times B = \mu B \sin \theta$$

10. What is the current in the 20- Ω inductor when $v = 0.2$ V?



$$I = \frac{V}{R} = \frac{0.2}{30} = 0.0067 \text{ A}$$

$$30 I = 1$$

$$I = 0.1 \text{ A}$$

$$0.2 \times 10 = 2 \text{ V}$$

- a. 0.3A
 b. 0.2A
 c. 0.26A
 d. 0.0067A

E. 0.1A

$$0.3 \times 10 = I_1 \times 30$$


$$16 - V_b + 4 - 12 = 12 - 6 + 30$$

$$V_b - 4 + 4(2.5) - 12 + 12(2.5) = V_b$$

$$16 - 16 = +4 = 10 + 12 = 22 + 30$$

Name: _____

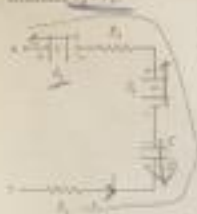11. $\mathcal{E}_1 = 40 \text{ V}$, $\mathcal{E}_2 = 12 \text{ V}$, $R_1 = 4 \Omega$, $R_2 = 12 \Omega$, $C = 1 \mu\text{F}$, $I = 2.5 \text{ A}$. What is the potential difference $V_a - V_b$?



$$V_a - \mathcal{E}_1 + I R_1 - \mathcal{E}_2 + V_b + I R_2 = V_b$$

$$V_a - V_b = \mathcal{E}_1 - I R_1 + \mathcal{E}_2 - V_c - I R_2$$

$$16 - 2.5 \times 4 + 12 - 6 - 2.5 \times 12$$



$$c = \frac{v}{v} = \frac{v}{\frac{v}{\sin \theta}} = \sin \theta$$

12. An electron is launched with velocity v in a uniform magnetic field \vec{B} . The angle θ between v and \vec{B} is chosen to use 90° . As a result, the electron follows a helix, its periodic time is:

- a. $2\pi m / qB$
 b. $2\pi m / q$
 c. $2\pi m / qv$
 d. $2\pi m$

$$T = \frac{2\pi m}{qB}$$

$$T = \frac{2\pi m}{qB} = \frac{2\pi m}{q v \sin \theta}$$

13. The magnitude of the magnetic field at point P, at the center of the semicircle shown, is given by:

- a. $\frac{\mu_0 I}{4R}$
 b. $\frac{\mu_0 I}{2R}$
 c. $\frac{\mu_0 I}{4R^2}$
 d. $\frac{\mu_0 I}{2R^2}$



$$\frac{2\pi m}{qB} = \frac{2\pi m}{q v \sin \theta}$$

$$\Rightarrow B = \frac{\mu_0 I}{2R} = \frac{\mu_0 I}{4R}$$

14. A 10-m wire carries a current of 15 A directed along the positive x-axis in a region where the magnetic field is uniform and given by $\vec{B} = (30\hat{i} - 40\hat{j}) \text{ mT}$. What is the magnetic force on the wire?

- a. $(-1.5 \text{ kN})\hat{j}$
 b. $(+0.8 \text{ kN})\hat{j}$
 c. $(+1.2 \text{ kN})\hat{j}$
 d. $(+1.5 \text{ kN})\hat{j}$

$$F = I \vec{L} \times \vec{B}$$

$$= 15 (20) \times (30\hat{i} - 40\hat{j}) \times 10^{-3}$$

$$= 15 + 80 \hat{k} \sqrt{10^3} \hat{k}$$

$$B = 170\hat{i} - 40\hat{j} \text{ mT}$$

$$\vec{L} \times \vec{B}$$

$$15 [(20) \times (30\hat{i} - 40\hat{j})] \times 10^{-3}$$

$$80$$

$$\vec{L} \times \vec{B}$$

$$\sum \epsilon(1 - e^{-t/\tau}) \cdot 85 \mu\text{s} = \sum (1 - e^{-t/\tau})$$

Answer: 0 → 0.15, 1e

15. A capacitor in a single-loop RC circuit is charged by 100 V of its final potential difference in 2.4 s. What is the time constant for this circuit?

- a. 1.2 s
 b. 1.8 s
 c. 1.5 s
 d. 2.9 s
 e. 1.7 s

$$Q = \epsilon C (1 - e^{-t/\tau})$$

$$V = \frac{Q}{C} = \epsilon (1 - e^{-t/\tau})$$

$$0.85 \epsilon = \epsilon (1 - e^{-2.4/\tau})$$

$$\rightarrow 0.15 = 1 - e^{-2.4/\tau}$$

$$e^{-2.4/\tau} = 0.85$$

$$\ln(0.85) = -\frac{2.4}{\tau}$$


$$\tau = \frac{2.4}{-\ln(0.85)} \approx 1.26 \text{ s}$$

16. Two long straight wires near a room through a window. One carries a current of 3.0 A into the room

while the other carries a current of 3.0 A out. The magnitude in T m of the path integral $\oint \vec{B} \cdot d\vec{s}$ around the window frame is

- a. $3.0 \times 10^{-6} \text{ T} \cdot \text{m}$
 b. none of these
 c. $1.0 \times 10^{-6} \text{ T} \cdot \text{m}$
 d. $6.0 \times 10^{-6} \text{ T} \cdot \text{m}$
e. $2.5 \times 10^{-6} \text{ T} \cdot \text{m}$

chuo

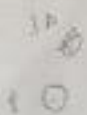


BIRZEIT UNIVERSITY
 Physics 132
 Coordinator: Tayseer AROURI

2nd H. EXAM
Time: 50 min

2nd Sem. 2014
25.5.2014

Student Name: محمد عيسى Student No.: 11309440

ضع إشارة (X) في كل من المربع المقابل لتاريخي شخصك وكتابة على رقم الشعبة

الشعبة	الفصل	التاريخ	المقرن
1, 5, 6	استاذان	2	امير عاروري <input type="checkbox"/>
7, 9	امير عاروري	3, 8, 11	عنان حيا <input type="checkbox"/>
		4, 10	ولاء خلفر <input type="checkbox"/>

تعليمات:

- (1) لا تفتح ورقة الامتحان حتى يسمح لك بذلك
- (2) لكتب اسمك ورقمك في أعلى هذه الصفحة
- (3) اقرأ الجواب الأكثر قرباً للجواب الصحيح وثلاثة على هذه الصفحة. وذلك بوضع إشارة (X) في العادة المتعددة
- (4) السؤال الذي له أكثر من إجابة يعني علامة صفر
- (5) يجب إعادة أوراق الامتحان كاملة
- (6) هذه الأسئلة 14 سؤالا

	1	2	3	4	5	6	7	8	9	10	11	12	13
A		✓	✓										
B				X									
C							X	X	X		X	Y	
D					X								
E	X			Y						X			X

13
8

17

 17

$$E = 24 \text{ V}$$

$$I = \frac{24}{8} = 3 \text{ A}$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2$$

$$e = 1.6 \times 10^{-19} \text{ C}$$

1. A battery of emf 24 V and internal resistance 2 Ω is connected to a 6 Ω resistor. The terminal potential difference of the battery is

- A) 30 V
- B) 24 V
- C) 0
- D) 16 V
- E) 18 V

$$I = \frac{24}{8} = 3 \text{ A}$$

$$V = E - Ir$$

$$= 24 - 3(2)$$

$$= 18$$

2. In a Hall-effect experiment, a current of 0.1 A is sent through a copper strip, 8 cm long, 1 cm wide, and 0.1 mm thick. The magnetic field is 0.51 T. The potential difference V

(The number of charge carriers per unit volume for copper is 8.5×10^{28} electrons m^{-3})

- A) 4.5×10^{-5} V
- B) 1.5×10^{-5} V
- C) 2.5×10^{-5} V
- D) 6.0×10^{-5} V
- E) 1.25×10^{-5} V

$$V = \frac{IB}{nqL}$$

$$V = \frac{0.1 \times 0.51}{8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 0.1}$$

$$= \frac{0.051}{1.36 \times 10^{10}}$$

$$= 3.75 \times 10^{-12} \text{ V}$$

3. An electron ($m_e = 9.1 \times 10^{-31}$ kg) with speed 800 km/s is projected into a uniform magnetic field B of 0.02 T with its velocity vector making an angle of 60° with B . The radius of the path is:

- A) 1.97×10^{-4} m
- B) 4.5×10^{-4} m
- C) 1.94×10^{-4} m
- D) 5.1×10^{-4} m
- E) 2.3×10^{-4} m

$$v = 800 \text{ km/s} = 800000 \text{ m/s}$$

$$r = \frac{mv \sin \theta}{qB}$$

$$= \frac{9.1 \times 10^{-31} \times 800000 \times \sin 60^\circ}{1.6 \times 10^{-19} \times 0.02}$$

$$= 1.97 \times 10^{-4} \text{ m}$$



$$R_1 + R_2 = 48$$

$$\frac{12 + 36}{48}$$

4. By using only two resistors, R_1 and R_2 (one of them or both of them), a student is able to obtain resistances of 9Ω , 12Ω , 16Ω , and 48Ω . The values of R_1 and R_2 (in ohms) are

$$\begin{aligned} 9 &= \frac{R_1 R_2}{R_1 + R_2} \\ 9 &= \frac{R_1 R_2}{48} \end{aligned}$$

- A) 3, 16
B) 16, 32
C) 3, 24
D) 10, 40

2014-15

5. An electron ($m = 9.1 \times 10^{-31} \text{ kg}$) with speed $6.0 \times 10^6 \text{ m/s}$ is projected into a uniform magnetic field B of 6.52 T with its velocity vector making an angle of 60° with the path of the path is

- A) $2.7 \times 10^{-4} \text{ m}$
B) $2.7 \times 10^{-3} \text{ m}$
C) $4.8 \times 10^{-4} \text{ m}$
D) $9.3 \times 10^{-4} \text{ m}$
E) $1.6 \times 10^{-4} \text{ m}$

$$\begin{aligned} \text{pitch} &= v \cdot T \\ &= v \left(\frac{2\pi m}{qB} \right) \sin \theta \\ &= 6.0 \times 10^6 \times \left(\frac{2\pi \times 9.1 \times 10^{-31}}{1.6 \times 10^{-19} \times 6.52} \right) \sin 60^\circ \\ &= 2.7 \times 10^{-3} \end{aligned}$$

6. A parallel-plate capacitor has a plate separation of 0.1 mm . The charge on each plate has a magnitude of $4 \times 10^{-6} \text{ C}$ and the potential difference across the plates is 300 V . The energy density between the plates is

- A) 318 J/m^3
B) 17.7 J/m^3
C) 4.0 J/m^3
D) 19.8 J/m^3
E) 31.8 J/m^3

$$\begin{aligned} U &= \frac{1}{2} qV = \frac{1}{2} (8 \times 10^{-6}) (300) = 1.2 \times 10^{-3} \text{ J} \\ \epsilon_0 &= 8.85 \times 10^{-12} \text{ F/m} \\ \Delta &= 0.1 \times 10^{-3} \text{ m} \\ \sigma &= \frac{q}{A} \\ \epsilon_0 \frac{\sigma^2}{2} &= \frac{U}{Ad} \\ \epsilon_0 \frac{q^2}{2A^2} &= \frac{U}{Ad} \end{aligned}$$

$$\begin{aligned} \frac{1}{2} qV &= U \\ 4 \times 10^{-6} \times 300 &= U \\ C &= \frac{Q}{V} \\ C &= \frac{4 \times 10^{-6}}{300} \\ C &= 1.33 \times 10^{-8} \text{ F} \end{aligned}$$

$$\begin{aligned} \frac{U}{Ad} &= \frac{C \cdot V}{Ad} \\ &= \frac{1.33 \times 10^{-8} \times 300}{0.15 \times 10^{-3}} \\ &= \frac{3.0 \times 10^{-5}}{0.15} \\ &= 2 \times 10^{-4} \text{ J/m}^3 \end{aligned}$$

$$\begin{aligned} \frac{1}{2} \frac{q^2}{\epsilon_0 A} &= \frac{U}{Ad} \\ \frac{1}{2} \frac{q^2}{\epsilon_0 A} &= \frac{U}{Ad} \end{aligned}$$

$$C = \kappa \frac{\epsilon_0 A}{d}$$

$$E = \frac{V}{d}$$

$\frac{d}{\epsilon_0}$

$$\kappa = 3.5$$

$$E = 16 \times 10^6 \text{ V/m}$$

7. A certain substance has a dielectric constant of 3.5 and a dielectric strength of 16 MV/m. If it is used as the dielectric material in a parallel-plate capacitor, the minimum area should the plates of the capacitor have to obtain a capacitance of 2.0 μF and to ensure that the capacitor will be able to withstand a potential difference of 1.0 kV is:

- A) 0.03 m²
 B) 0.11 m²
~~C) 0.041 m²~~
 D) 1.1 m²
 E) 0.145 m²

$$C = \frac{\kappa \epsilon_0 A}{d} \Rightarrow A = \frac{Cd}{\kappa \epsilon_0} = 0.0807 \text{ m}^2$$

$$E = \frac{V}{d} \Rightarrow d = \frac{V}{E} = \frac{1000}{16 \times 10^6} = 6.25 \times 10^{-5} \text{ m}$$

$$E = \frac{V}{d} \Rightarrow V = Ed$$

8. When 240 V is applied across a wire that is 8 m long and has 0.70 mm radius, the current density is $1.5 \times 10^6 \text{ A/m}^2$. The resistivity of the wire is:

- A) $1.5 \times 10^{-7} \Omega \cdot \text{m}$
 B) $4.5 \times 10^{-8} \Omega \cdot \text{m}$
~~C) $3.0 \times 10^{-8} \Omega \cdot \text{m}$~~
 D) $4.0 \times 10^{-8} \Omega \cdot \text{m}$
 E) $8.2 \times 10^{-8} \Omega \cdot \text{m}$

$$J = \frac{I}{A} = \frac{V}{RA} \Rightarrow R = \frac{VA}{I}$$

$$R = \frac{\rho L}{A} \Rightarrow \rho = \frac{R A^2}{L}$$

$$\rho = \frac{(240)^2 (0.0007)^2}{8} = 5.61713 \times 10^{-8} \Omega \cdot \text{m}$$

9. A wire 1.0 m long lying along the x-axis carries a current of 5 A in the positive x-direction, through a magnetic field $B = (0.020 \text{ T})\hat{j} + (0.010 \text{ T})\hat{k}$. The force on the wire is:

- A) -0.11 N
 B) -0.08j - 0.12k N
~~C) -0.1j + 0.15k N~~
 D) 0.08j + 0.12k N
 E) -0.08j + 0.24k N

$$F = I \mathbf{L} \times \mathbf{B}$$

$$= 5(1\hat{i}) \times (0.02\hat{j} + 0.01\hat{k})$$

$$= 5(0.02\hat{k} - 0.01\hat{j}) = 0.1\hat{k} - 0.05\hat{j}$$



$$A = \frac{VC}{\epsilon \epsilon_0 \kappa}$$

$$\omega = 2\pi f = 5.96 \times 10^7 \text{ rad/s}$$

$$k = \frac{2\pi}{\lambda} = \frac{2\pi}{0.1} = 62.8 \text{ rad/m}$$

$$Q = \frac{1}{2} CV^2$$

$$A = 5.1 \times 10^{23}$$

$$A = 4 \text{ mm}^2$$

10. Copper contains 2.4×10^{23} free electrons/m³. A copper wire of cross-sectional area 0.4 mm^2 carries a current of 10 A . The electron drift speed is:

- A) $1.9 \times 10^3 \text{ m/s}$
- B) $3 \times 10^3 \text{ m/s}$
- C) 10^4 m/s
- D) $7.3 \times 10^4 \text{ m/s}$
- E) $3.1 \times 10^3 \text{ m/s}$

$I = n e A v$
 $v = \frac{I}{n e A}$
 $= 3.125 \times 10^3$

11. A certain capacitor, in series with a 120Ω resistor, is being charged. At the end of $\frac{1}{2}$ ms its charge is half the final value. The capacitance is about:

- A) $9.6 \mu\text{F}$
- B) $30 \mu\text{F}$
- C) $30 \mu\text{F}$
- D) $11 \mu\text{F}$
- E) $20 \mu\text{F}$

$Q = CE(1 - e^{-t/\tau})$
 $\frac{1}{2} Q_f = Q_f(1 - e^{-t/\tau})$
 $e^{-t/\tau} = \frac{1}{2}$
 $\frac{t}{\tau} = \ln 2 = 0.693$

12. A velocity selector where $\vec{E} = E\hat{i}$ and $\vec{B} = B\hat{j}$, with $B = 40 \text{ mT}$. If the selector is designed to select 2 keV electrons, then the value of E is:

- A) $4.2 \times 10^5 \text{ V/m}$
- B) $3.5 \times 10^5 \text{ V/m}$
- C) $3.5 \times 10^5 \text{ V/m}$
- D) $2.4 \times 10^5 \text{ V/m}$
- E) $2.4 \times 10^5 \text{ V/m}$

$\frac{1}{2} m v^2 = 2 \text{ keV} = 2 \times 10^3 \text{ eV}$
 $v = \sqrt{\frac{4 \times 10^3 \text{ eV}}{m}}$
 $E = vB = 1.627 \times 10^5 \text{ V/m}$
 $= 1.6 \times 10^5$

13. A 220 potential difference is applied to a lamp whose resistance is 242 ohms . If the price for 1 kWh is 0.25 then the cost to operate the lamp for one week is:

- A) $3.0 \text{ \$}$
- B) $28.8 \text{ \$}$
- C) $38.5 \text{ \$}$
- D) $30.3 \text{ \$}$
- E) $27.5 \text{ \$}$

$P = \frac{V^2}{R} = 200$
 $C = Pt = 2200 \text{ Wh} = 2.2 \text{ kWh}$
 $2.2 \times 0.25 = 0.55 \text{ kWh}$

200

$\frac{P}{A} = \text{Power}$

Power = 200 watt

$\frac{Q}{t} = \frac{1}{R} \frac{dQ}{dt}$

Student Name: Ramad Rafeel Ahmed Alshaykh ID No: 1130592

Please read these instructions carefully before starting the exam.

- Write your name and student number in the above box.
- The exam consists of 17 multiple choice problems, answer all of them.
- Mark the correct answers of the multiple choice problems on the answer sheet.
- Turn in the whole exam sheets.
- Select the section you are registered in by inserting a ✓ mark inside the section.

✓	Sec	Instructor	Time
	1	Ghassan Abbas	MTWTF 09:30-10:50
	2	Wafaa Khair	MTWTF 12:50-01:50
✓	3	Ghassan Abbas	MTWTF 08:00-09:20
	4	Ahmed Shawkat	MTWTF 12:50-01:50

Some useful formulas and constants:

1) $P = qd \cdot E$	5) $f = \frac{1}{\lambda} \cdot c$
2) $f = d \cdot \Delta \theta$	6) $k = 1.4 \times 10^{-23} \text{ J/K}$
3) $x = a(1 - e^{-bt})$	7) $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$
4) $R = \frac{\rho L}{A}$	

Answer Sheet:

Q#	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17
(I)			X										X				
(II)							X	X		X					X	X	
(III)	X	X											X	X			
(IV)				X	X				X								
(V)						X					X						X

$i = 0.1$

$q = C \cdot V = 1 \cdot 10^{-6} \cdot 100 = 10^{-4} \text{ C}$

$i = \frac{dq}{dt} \Rightarrow 0.1 = \frac{10^{-4}}{t} \Rightarrow t = 10^{-3} \text{ s}$


11. A series capacitor, in series with a 720 Ω resistor, is being charged. At the end of 10 ms the charge is half the final value. The capacitance is about:

A	0.2 μF
B	0.4 μF
C	0.8 μF
D	1.2 μF
E	2.0 μF

$Q(t) = C \cdot V (1 - e^{-t/\tau})$
 $\frac{1}{2} C \cdot V = C \cdot V (1 - e^{-t/\tau})$
 $0.5 = 1 - e^{-t/\tau} \Rightarrow e^{-t/\tau} = 0.5$
 $-\frac{t}{\tau} = \ln(0.5) \Rightarrow \tau = \frac{t}{-\ln(0.5)} = \frac{10 \text{ ms}}{0.693} \approx 14.4 \text{ ms}$
 $\tau = RC \Rightarrow C = \frac{\tau}{R} = \frac{14.4 \text{ ms}}{720 \Omega} \approx 20 \mu\text{F}$

12. Determine the potential difference $V_a - V_b$ in the circuit shown when $I = 20 \text{ mA}$ and $C = 50 \mu\text{F}$.

A	-6 V
B	+6 V
C	-20 V
D	-26 V
E	-32 V

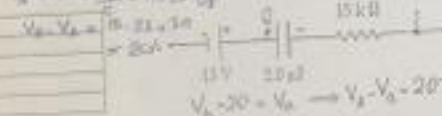

$V_a - V_b = -15 + I \cdot 20k + \frac{Q}{C} - I \cdot 15k$
 $Q = I \cdot C = 20 \text{ mA} \cdot 50 \mu\text{F} = 10^{-3} \text{ C}$
 $V_a - V_b = -15 + 20 \cdot 20 + \frac{10^{-3}}{50 \cdot 10^{-6}} - 20 \cdot 15 = -20 \text{ V}$

13. A proton ($m = 1.67 \cdot 10^{-27} \text{ kg}$, $q = 1.6 \cdot 10^{-19} \text{ C}$) is accelerated to a speed of $22 \cdot 10^6 \text{ m/s}$ and then moves perpendicular to a uniform magnetic field with $B = 2.5 \text{ T}$. What is the radius of the resulting circular path?

A	14.8 mm
B	26.0 mm
C	20.9 mm
D	24.5 mm
E	38.0 mm

$r = \frac{mv}{qB} = \frac{1.67 \cdot 10^{-27} \cdot 22 \cdot 10^6}{1.6 \cdot 10^{-19} \cdot 2.5} = 0.023 \text{ m} = 23 \text{ mm}$

14. A conductor of radius a , length l , and resistivity ρ has resistance R . What is the new resistance if ρ is multiplied by 2 times l original length?

A	$4R$
B	$2R$
C	R
D	$\frac{R}{2}$
E	$\frac{R}{4}$

$R = \rho \frac{l}{A}$
 $R' = \frac{2\rho \cdot 2l}{A} = 4R$

15. A 40 nF capacitor, initially charged to 50 V and a 4.0 mF capacitor charged to 30 V are connected in each other with the positive plate of each connected to the negative plate of the other. What is the final charge on the 4.0 mF capacitor?

A	20 nC
B	4.0 nC
C	10 nC
D	12 nC
E	20 nC

$q_1 = C_1 V_1 = 40 \text{ nF} \cdot 50 \text{ V} = 2000 \text{ nC}$
 $q_2 = C_2 V_2 = 4.0 \text{ mF} \cdot 30 \text{ V} = 120000 \text{ nC}$
 $q_1 + q_2 = 122000 \text{ nC}$
 $V = \frac{q}{C} = \frac{122000 \text{ nC}}{4.0 \text{ mF}} = 30.5 \text{ V}$
 $q = C_1 V = 40 \text{ nF} \cdot 30.5 \text{ V} = 1220 \text{ nC}$

$q_1 + q_2 = q_1' + q_2'$
 $2000 + 120000 = q_1' + q_2'$
 $q_1' = 2000 - q_2'$
 $q_2' = \frac{C_2 V}{C_1 + C_2} = \frac{4.0 \text{ mF} \cdot 30.5 \text{ V}}{4.0 \text{ mF} + 40 \text{ nF}} \approx 30.5 \text{ V}$

$$P \cdot IV = IV^2$$

$$\frac{2}{10} \times \frac{1}{10}$$

$$V \cdot I \cdot R = 21 \cdot 10 = 3$$


$$3 = 15 + 30$$

$$3 = 15(1 + 20(23-1))$$

$$1 = 15(1 + 460) = 15 \cdot 461 = 6915$$

- 4) A resistor with resistance R is connected in a circuit with a battery of emf \mathcal{E} and a resistor of resistance $2R$. The current through the resistor of resistance R is I . The power dissipated in the resistor of resistance R is

A) 0.20 Watt	$I = \frac{\mathcal{E}}{3R}$
B) 0.30 Watt	$P = I^2 R$
C) 0.50 Watt	$= \left(\frac{\mathcal{E}}{3R}\right)^2 R$
D) 0.25 Watt	$= \frac{\mathcal{E}^2}{9R}$
E) 0.40 Watt	$\times 0.6$

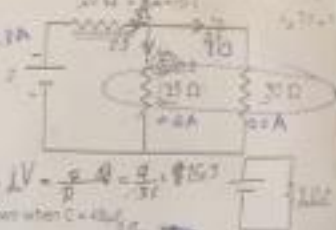

$$P = IV = \frac{\mathcal{E}}{3} \cdot \frac{\mathcal{E}}{3} = \frac{\mathcal{E}^2}{9}$$

- 7) Determine the equivalent capacitance of the combination shown when $C = 4 \mu\text{F}$.

A) 30 μF	$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{C}$
B) 32 μF	$\frac{1}{C_{eq}} = \frac{1}{2C} + \frac{1}{C}$
C) 34 μF	$\frac{1}{C_{eq}} = \frac{1}{3C} + \frac{1}{C}$
D) 36 μF	$\frac{1}{C_{eq}} = \frac{1}{4C} + \frac{1}{C}$
E) 38 μF	$\frac{1}{C_{eq}} = \frac{1}{5C} + \frac{1}{C}$



- 8) A certain parallel plate capacitor is filled with a dielectric constant $\kappa = 2.5$ and a dielectric strength of $3.0 \times 10^6 \text{ V/m}$. The area of each plate is 0.02 m^2 . The capacitor will be able to withstand a potential difference of 4.0 kV. The capacitance of this capacitor is

A) $7.0 \times 10^{-9} \text{ F}$	$C = \frac{\kappa \epsilon_0 A}{d}$
B) $7.0 \times 10^{-8} \text{ F}$	$d = \frac{V}{E}$
C) $2.4 \times 10^{-9} \text{ F}$	$d = 2.22 \times 10^{-3} \text{ m}$
D) $2.4 \times 10^{-8} \text{ F}$	$C = 2.9 \times 10^{-8} \text{ F}$
E) $5.1 \times 10^{-9} \text{ F}$	$d = 2.22 \times 10^{-3} \text{ m}$

- 9) The current density in a cylindrical wire of radius R varies with radial distance r as $J = kr$, where k is a constant. The current in the wire is

A) $2\pi kR^2$	$I = \int J dA = \int_0^R kr \cdot 2\pi r dr$
B) $3\pi kR^2$	$I = \pi k R^2$
C) $4\pi kR^2$	$I = \pi k R^2$
D) $2\pi kR^3$	$I = \pi k R^3$
E) $4\pi kR^3$	$I = \pi k R^3$

- 10) How many electrons pass through a 20Ω resistor in 1 min if there is a potential drop of 20 volts across it?

A) 1.5×10^{18}	$Q = I \cdot t$
B) 1.5×10^{19}	$I = \frac{V}{R}$
C) 1.5×10^{20}	$Q = A \cdot t$
D) 1.5×10^{21}	$n = 5.625 \times 10^{21}$
E) 1.5×10^{22}	$n = 5.625 \times 10^{21}$

$$Q = V R t$$

$$Q = I t$$

$$V = IR \quad Q = \frac{V}{R} t$$

$$n = \frac{Q}{e}$$

$$Q = 90$$

$$n = \frac{90}{1.6}$$

- 12) A straight wire of length 2.4 m runs into the page shown. A magnetic field B is to the right along an x . The net magnetic force on the wire is:

A) 161 mN into the page
B) 161 mN out of the page
C) 3.4 mN out of the page
D) 3.4 mN into the page
E) zero




- 13) At one instant an electron is moving in the xy plane, the components of its velocity being $v_x = 3 \times 10^6$ m/s and $v_y = 3 \times 10^6$ m/s. A magnetic field of 0.8 T is in the positive x direction. At that instant the magnitude of the magnetic force on the electron is:

A) 0
B) 2.4×10^{-14} N
C) 3.8×10^{-14} N
D) 6.8×10^{-14} N
E) 1.8×10^{-14} N

Handwritten calculations for question 13:
 $F = qvB$
 $= 1.6 \times 10^{-19} \times \sqrt{(3 \times 10^6)^2 + (3 \times 10^6)^2} \times 0.8$
 $= 3.8 \times 10^{-14}$ N

- 14) The diagram shows a straight wire carrying a current out of the page. The wire is between the poles of a permanent magnet. The direction of the magnetic force exerted on the wire is:

A) up
B) down
C) left
D) right
E) zero

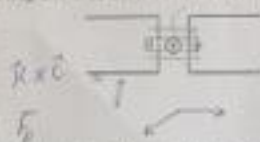

- 15) You are facing a loop of wire which carries a clockwise current of 5.0 A and which encloses an area of radius 0.1 m. The magnetic dipole moment of the loop is:

A) 3.00 A·m ² into the page
B) 3.00 A·m ² out of the page
C) 0.09 A·m ² into the page
D) 0.09 A·m ² out of the page
E) 0.07 A·m ² from left to right

Handwritten calculations for question 15:
 $\mu = NIA$
 $= 5 \times \pi (0.1)^2$
 $= 0.0942$ (A·m²)

- 16) An isolated conducting sphere whose radius R is 5 cm has a charge $q = 1.25 \mu\text{C}$. The potential energy stored in the electric field of the charged conductor is:

A) 0
B) 0.20 J
C) 1.2 J
D) 2.5 J
E) 2.5 μJ

Handwritten calculations for question 16:
 $U = \frac{1}{2} \frac{q^2}{4\pi\epsilon_0 R}$
 $= \frac{1}{2} \frac{(1.25 \times 10^{-6})^2}{4\pi \times 8.85 \times 10^{-12} \times 0.05}$
 $= 0.20$ J

- 14) The electron density in copper is 8.49×10^{28} electrons/m³. When a 2.0 A current is present in a copper wire with a 0.80 cm² cross-section, the electron drift velocity in m/s is

A) 1.84×10^{-4}	$I = nAv_d$
B) 1.84×10^{-6}	$v_d = \frac{I}{nA}$
C) 1.91	
D) 8.49×10^{28}	
E) 8.49×10^{-4}	

- 17) A parallel plate capacitor of capacitance C_0 was fully charged to a potential V_0 and charge Q_0 when connected to a battery. It is then disconnected from the battery and the plates are pulled apart to twice the plate separation without disturbing them. After being pulled, the magnitude of the charge on the plates and the potential difference between the plates are

A) $Q_0/2, V_0$	$q = CV$
B) $Q_0, V_0/2$	$q = \frac{1}{2} CV$
C) $2Q_0, V_0$	$Ck = \frac{1}{2} CV$
D) $Q_0, 2V_0$	
E) $2Q_0, 2V_0$	

$$Q_0 = 2V_0^2$$

$$\frac{1}{2d}$$

$$C = \frac{\epsilon_0 A}{d}$$

$$C = \frac{\epsilon_0 A}{2d} = \frac{1}{2} C$$

$$C_0 = \frac{\epsilon_0 A}{d}$$

$$C = \frac{\epsilon_0 A}{2d} = \frac{C_0}{2}$$

$$Q_0 = C_0 V_0$$

$$Q_0 = C_0 V_0$$

$$Q_0 = \frac{C_0}{2} \cdot 2V_0$$

$$C_0 = \frac{Q_0}{V_0}$$

$$Q = CV$$

$$= \frac{C_0}{2} V_0 \cdot 2$$

$$V = \frac{Q}{C} = \frac{Q_0}{\frac{C_0}{2}} = 2V_0$$

$$V = \frac{Q}{C} = \frac{Q_0}{\frac{C_0}{2}}$$

$$V = 2 \frac{Q_0}{C_0} = 2V_0$$

16



Physics 101

Second Hour Exam

Summer, 2014

Time: 20 minutes

Student Name: Wahid H. H. H. Student No: 4116909

Please read these instructions **thoroughly** before starting the exam!

- Write your name and student number in the above box.
- The exam consists of 17 multiple choice problems, answer all of them.
- Mark the correct answers of the multiple choice problems on the answer sheet.
- Fill in the whole answer sheets.
- Select the section you are registered to by inserting a ✓ mark beside the section

Section	Instruction	Time
1	General Physics	MTWTh 09:30-10:00
2	Water Physics	MTWTh 11:30-12:00
<input checked="" type="checkbox"/> 3	General Physics	MTWTh 08:00-09:30
4	All Students	MTWTh 12:30-01:30

Write useful formulas and constants!

1) $F = mg + F$	8) $F = mg$
2) $F = -1/r^2$	9) $r = 1.0 \times 10^{-10} \text{ m}$
3) $F = mg(1 - \rho/\rho_0)$	7) $A_0 = 8.85 \times 10^{-12} \text{ F/m}$
4) $B = \frac{\mu_0 I}{2r}$	

Answer them!

Q#	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17
01			✓											✓			
02								✓	✓		✓				✓	✓	✓
03	✓	✓											✓		✓		
04				✓	✓					✓							
05							✓					✓					

A-300

$$q(t) = \frac{Q}{\tau} (1 - e^{-t/\tau})$$

$$\frac{1}{2} Q = \frac{Q}{\tau} (1 - e^{-t/\tau})$$

$$e^{-t/\tau} = \frac{1}{2}$$

$$-\frac{t}{\tau} = \ln\left(\frac{1}{2}\right) = -\ln 2$$

$$t = \tau \ln 2 = \frac{Q}{I} \ln 2 = \frac{0.001}{0.001} \ln 2 = \ln 2 \approx 0.693$$

37. A certain capacitor, in series with a 720Ω resistor, is being charged. At the end of 10 ms the charge is half the final value. The capacitance is about:

- A) $9.8 \mu\text{F}$
- B) $1.4 \mu\text{F}$
- C) $10 \mu\text{F}$
- D) $7.2 \mu\text{F}$
- E) $10 \mu\text{F}$


$$\tau = RC = 720 C$$

$$t = \tau \ln 2 = 720 C \ln 2 = 10 \text{ ms}$$

$$C = \frac{10 \text{ ms}}{720 \ln 2} \approx 1.9 \mu\text{F}$$

38. Determine the potential difference, $V_a - V_b$, in the circuit segment shown when $i = 2.0 \text{ mA}$ and $Q = 30 \mu\text{C}$.

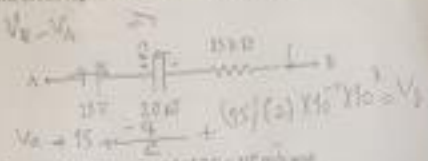- A) -85 V
- B) $+85 \text{ V}$
- C) $+70 \text{ V}$
- D) -26 V
- E) -10 V



$$V_a - V_b = \mathcal{E} - i r - i R + \frac{Q}{C}$$

$$= 25 - (2 \times 10^{-3}) \times 10 - (2 \times 10^{-3}) \times 150 + \frac{30 \times 10^{-6}}{C}$$

39. A proton (mass = $1.67 \times 10^{-27} \text{ kg}$, $q = 1.6 \times 10^{-19} \text{ C}$) is accelerated to a speed of $2.0 \times 10^7 \text{ m/s}$ and then moves perpendicular to a uniform magnetic field with $B = 1.6 \text{ T}$. What is the radius of the resulting circular path?

- A) 12.0 mm
- B) 18.0 mm
- C) 28.3 mm
- D) 24.0 mm
- E) 15.0 mm

$$r = \frac{mv}{qB} = \frac{(1.67 \times 10^{-27})(2.0 \times 10^7)}{(1.6 \times 10^{-19})(1.6)} \approx 13.1 \text{ mm}$$

40. A conductor of radius r , length L , and resistivity ρ has resistance R . What is the new resistance if it is stretched to 2 times its original length?

- A) $R/8$
- B) $R/2$
- C) R
- D) $8R$
- E) $16R$

$$R = \frac{\rho L}{A}$$

$$R' = \frac{\rho (2L)}{A/4} = 8R$$

41. A 4.0 mF capacitor initially charged to 80 V and a 6.0 mF capacitor charged to 30 V are reconnected to each other with the positive plate of each connected to the negative plate of the other. What is the final charge on the 6.0 mF capacitor?

- A) 30 mC
- B) 4.0 mC
- C) 10 mC
- D) 12 mC
- E) 230 mC

$$Q_1 + Q_2 = Q_1' + Q_2'$$

$$320 \mu\text{C} + 180 \mu\text{C} = -Q_1' + Q_2'$$

$$500 \mu\text{C} = -Q_1' + Q_2'$$

$$Q_1' = Q_2' - 500 \mu\text{C}$$

$$Q_2' = 6 \times 10^{-5} \text{ C}$$

$$V = 50 \text{ V}$$

$$200 \times 10^{-6} \text{ C}$$

$$I_{\text{max}} = \frac{V}{R} \quad iR \Rightarrow I = 10$$



13. What rate is electric energy generated in the 10 Ω resistor when $\epsilon = 3 \text{ V}$.


- | |
|--------------|
| A) 1.44 Watt |
| B) 0.30 Watt |
| C) 1.50 Watt |
| D) 0.25 Watt |
| E) 0.40 Watt |



$$I_1 = 10 \text{ A} \Rightarrow I_2 = 10 \text{ A}$$

14. Determine the equivalent capacitance of the combination shown when $\epsilon = 40 \text{ V}$.

- | |
|----------|
| A) 30 μF |
| B) 15 μF |
| C) 14 μF |
| D) 16 μF |
| E) 18 μF |

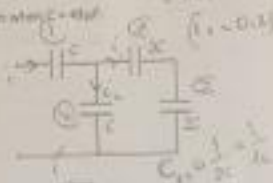

$$C_{\text{eq}} = \frac{1}{\frac{1}{2} + \frac{1}{\frac{1}{4} + \frac{1}{\frac{1}{6} + \frac{1}{3}}}}$$

15. A certain parallel plate capacitor is filled with a dielectric material with $\epsilon = 2.5$ and a dielectric strength of 100 kV/m. The area of each plate is 0.01 m². The capacitor will be able to withstand a maximum difference of 4.0 V. The capacitance of this capacitor is

- | |
|------------|
| A) 1.50 μF |
| B) 7.00 μF |
| C) 14.0 μF |
| D) 2.50 μF |
| E) 3.50 μF |

$$C = \epsilon_0 \epsilon \frac{A}{d}$$

$$C = \epsilon_0 \epsilon \frac{Q}{V}$$

$$Q = \frac{C V}{\epsilon_0 \epsilon}$$

16. The current density in a cylindrical wire of radius R varies with radial distance r as $i = cr$, where c is a constant. The current in the wire is

- | |
|-----------------------|
| A) 2πR ² c |
| B) 2πRc |
| C) πR ² c |
| D) πRc |
| E) 2πR ³ c |

17. How many electrons pass through a 20 Ω resistor in 1 min if there is a potential drop of 30 volts across it?

- | |
|---------------------------|
| A) 1.8 × 10 ¹⁸ |
| B) 1.8 × 10 ¹⁹ |
| C) 1.8 × 10 ²⁰ |
| D) 1.2 × 10 ¹⁹ |
| E) 1.8 × 10 ¹⁷ |

$$V = IR$$

$$I = \frac{V}{R}$$

$P = I^2 R$
 $R = 20 \Rightarrow P = 18 \times 10^3 \text{ W}$
 $56.25 \times 20 = 1125 \text{ W}$
 $Q = I t$
 $Q = 60 \times 60 = 3600 \text{ C}$
 $V = 30, R = 20$
 $t = 60$
 $Q = 90$

$$\begin{aligned}
 \tau_{ac} &= \tau_{ab} + \tau_{bc} \\
 &= L I a \hat{j} - i L a \hat{j} + L I a \hat{i} - L I a \hat{i} \\
 &= 2 L I a \hat{k} \hat{i} \Rightarrow F_a = \vec{\mu} \times \vec{B} \\
 &= \tau L I a \hat{i}
 \end{aligned}$$

- 11) A straight wire of length $2l$ is bent into the shape shown. A magnetic field B is in the right acting on it. The net magnetic force on the wire is:

A) lB into the page
B) lB out of the page
C) $1.414lB$ out of the page
D) $1.707lB$ out of the page
E) zero




- 12) At one instant an electron is moving in the $x-y$ plane, the components of its velocity being $v_x = 5 \times 10^6$ m/s and $v_y = 2 \times 10^6$ m/s. A magnetic field of 0.8 T is in the positive x direction. At this instant the magnitude of the magnetic force on the electron is:

A) 0
B) 2.6×10^{-14} N
C) 3.8×10^{-14} N
D) 6.8×10^{-14} N
E) 1.3×10^{-14} N

- 13) The diagram shows a straight wire carrying a current out of the page. The wire is between the poles of a permanent magnet. The direction of the magnetic force exerted on the wire is:

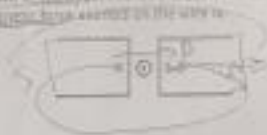A) \uparrow
B) \downarrow
C) \rightarrow
D) \leftarrow
E) \times



- 14) You are facing a loop of wire which carries a clockwise current of 2.0 A and which subtends an area of radius 0.1 m. The magnetic dipole moment of the loop is:

A) 0.50 A.m ² , into the page
B) 0.05 A.m ² , out of the page
C) 0.08 A.m ² , into the page
D) 0.09 A.m ² , out of the page
E) 0.37 A.m ² , from left to right

- 15) An isolated conducting sphere whose radius R is 1 cm has a charge $q = 1.25$ μ C. The potential energy stored in the electric field of the charged conductor is:

A) 0
B) 0.10 J
C) 1.8 mJ
D) 2.8 J
E) 1.8 μ J

$$U_{el} + U_{ch} = \frac{1}{2} \frac{q^2}{4\pi\epsilon_0 R} = \frac{1}{2} \frac{(1.25 \times 10^{-6})^2}{4\pi(8.85 \times 10^{-12}) \times 0.01} = 0.14 \times 10^{-2} \text{ J}$$