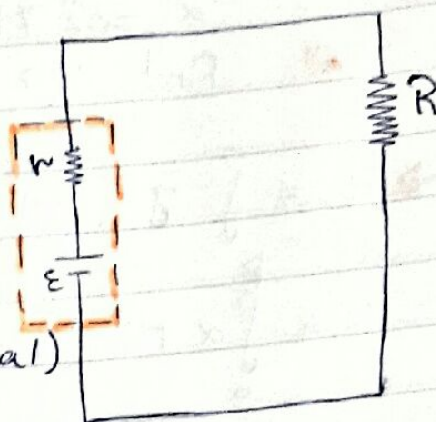


27 - Circuits

→ Electro motive force (\mathcal{E})

Emf = work done by the Power source (Battery) in moving +1C. (-) terminal to (+) terminal in the side the source.



$$\Rightarrow \frac{dw}{dt} = \mathcal{E} \frac{dq}{dt}$$

• Power by $\mathcal{E} = \mathcal{E}i$ watt


→ Energy transfer in the Circuit:

• Electric energy transfer (a → b) = $\Delta q \int_a^b V$ (Joule)

• Energy transfer = $\Delta q \int_a^b V$

• Power transfer = $\frac{\Delta q \int_a^b V}{\Delta t}$ watt

$$P_R = Vi = Ri^2 = r_i$$

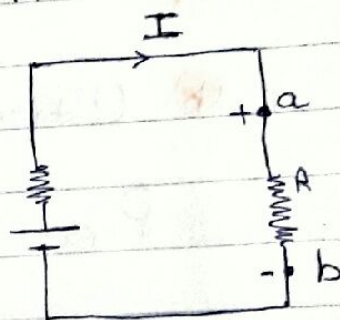


• From Conservation of energy:

$$\mathcal{E}i = i^2 R + i^2 r$$

$$\mathcal{E} = i(R + r) \Rightarrow i = \frac{\mathcal{E}}{R + r}$$

* R in Series:

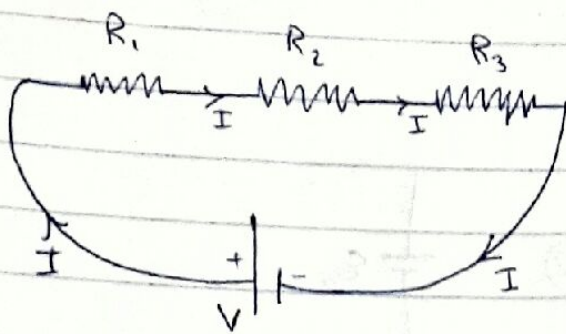

$$\Rightarrow I_1 = I_2 = I_3$$

$$\Rightarrow V = V_1 + V_2 + V_3$$

$$V = R_1 I + R_2 I + R_3 I$$

$$\frac{V}{I} = R_1 + R_2 + R_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

* R in Parallel

$$\Rightarrow V_1 = V_2 = V_3 = V$$


$$I_1 R_1 = I_2 R_2 = I_3 R_3$$

$$\Rightarrow I = I_1 + I_2 + I_3$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$


$$\frac{I}{V} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$
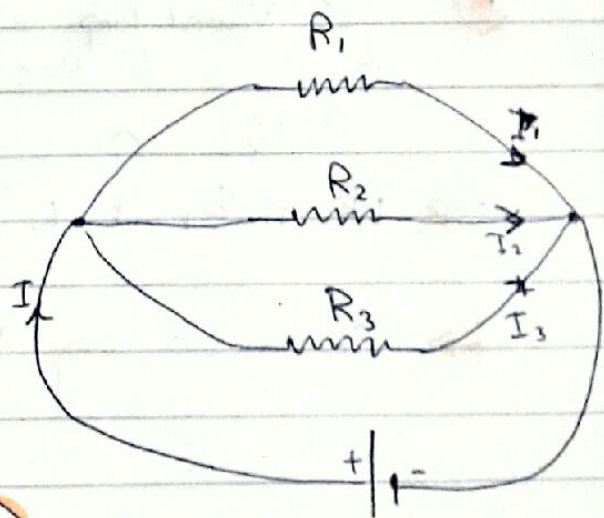
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



* Multi loop circuits :-

Sample Problem (24.04):-

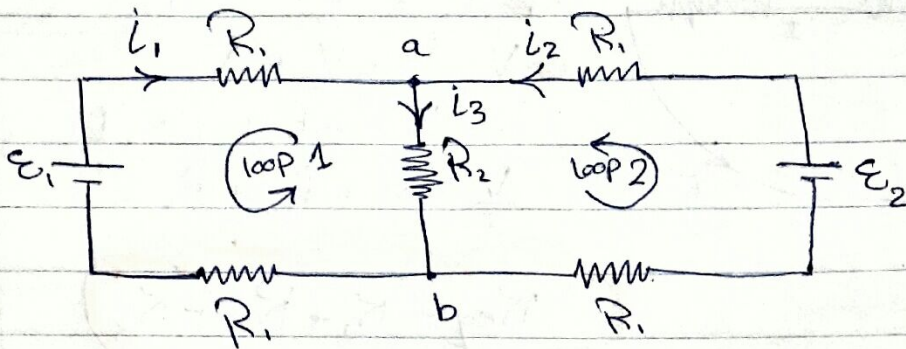

Kirchoff's rules :-

$$\textcircled{1} \quad \sum I_{in} = \sum I_{out}$$

$$I_1 + I_2 = I_3 \quad \textcircled{1}$$

$$\textcircled{2} \quad \sum V_{\text{closed loop}} = 0$$


$$\sum V_{aa} = 0$$

$$\Rightarrow i_1 R_1 - \mathcal{E}_1 + i_1 R_1 + i_3 R_2 = 0 \quad (\text{loop 1})$$

$$\Rightarrow \sum V_{aa} = 0 \Rightarrow -R_2 i_3 - R_1 i_2 + \mathcal{E}_2 - i_2 R_1 = 0 \quad (\text{loop 2})$$

RC - Circuits

① Charging a Capacitor :

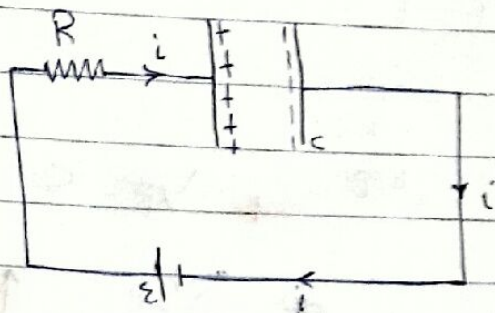

$$\mathcal{E} = V_R + V_C$$

$$\mathcal{E} = Ri + \frac{q}{C}$$

• At $t=0$ $q=0$

$$i = \frac{\mathcal{E}}{R}$$

• After a long time

$$q_{\text{max}} = C\mathcal{E}$$

• Find $q(t)$, $i(t)$, $V_C(t)$, $V_R(t)$? $i=0$

$$\sum V_{ac} = 0$$

$$\mathcal{E} - Ri - \frac{q}{C} = 0$$

$$\mathcal{E} - R \frac{dq}{dt} - \frac{q}{C} = 0$$

$$-R \frac{dq}{dt} = \frac{q}{C} - \mathcal{E}$$

$$\int_0^q \frac{dq}{q - C\mathcal{E}} = \int_0^t \frac{-dt}{RC}$$

$$\ln(q - C\mathcal{E}) \Big|_0^q = \frac{-t}{RC}$$

$$\ln(q - C\mathcal{E}) - \ln(-C\mathcal{E}) = \frac{-t}{RC}$$

$$\Rightarrow \ln \left(\frac{Q - C\varepsilon}{-C\varepsilon} \right) = \frac{-t}{RC} \Rightarrow$$

$$Q(t) = C\varepsilon (1 - e^{-t/RC})$$

$$V_c(t) = \varepsilon (1 - e^{-t/RC})$$

$$\Rightarrow i(t) = \frac{dQ}{dt} = \frac{-C\varepsilon e^{-t/RC}}{-RC}$$

$$i(t) = -\frac{\varepsilon}{R} e^{-t/RC} \Rightarrow V_R = \varepsilon e^{-t/RC}$$

Find q at $t = \tau$??




$$q = C\varepsilon (1 - e^{-\tau/RC})$$

$$= C\varepsilon (1 - e^{-1})$$

$$= C\varepsilon (1 - 0.37)$$

$$q(\tau) = 0.63 C\varepsilon$$

$$V_c(\tau) = 0.63 \varepsilon$$

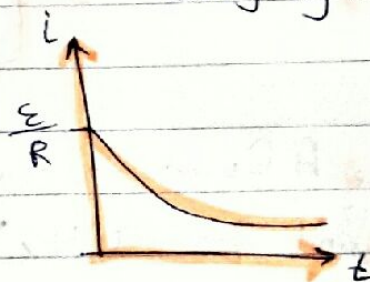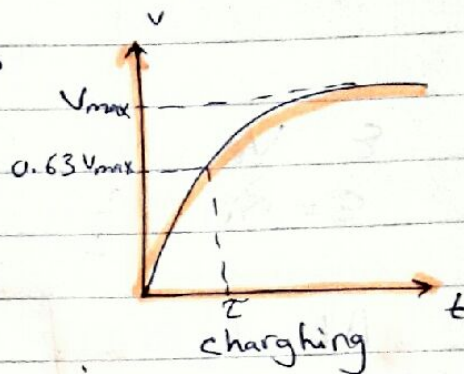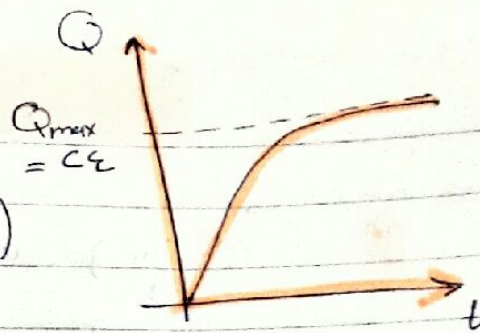

② Discharging a Capacitor:

$$\int_{q_0}^q \frac{dq}{q} = \int_0^t \frac{dt}{RC}$$

$$q(t) = q_0 e^{-t/RC}$$

$$V(t) = V_0 e^{-t/RC}$$

