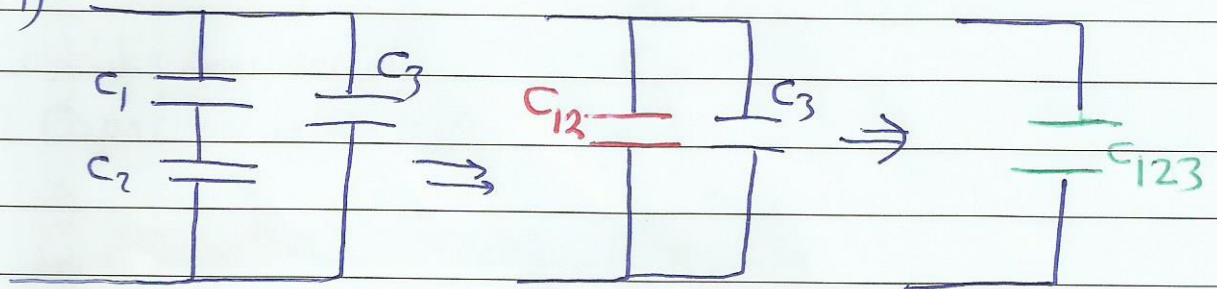


(25) Capacitance Discussion

R5-4)



$$C_1 = 10 \mu\text{F}$$

$$C_2 = 8 \mu\text{F} \text{ Find}$$

$$C_3 = 4 \mu\text{F} \text{ } C_{eq}$$

(1)

(2)

(3)

$C_1 + C_2$ in Series

C_{12} and C_3 in P

$$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2}$$

in Parallel

$$\frac{1}{C_{12}} = \frac{1}{10} + \frac{1}{8}$$

$$C_{123} = C_{12} + C_3$$

$$= 4.44 + 4$$


$$\frac{1}{C_{12}} = \frac{4+5}{40}$$

$$C_{12} = \frac{40}{9} \mu\text{F}$$

$$= 4.44 \mu\text{F}$$

$$C_{123} = 8.44 \mu\text{F}$$

(25-14)

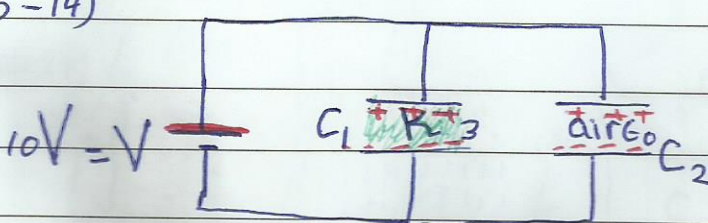

$$A = 5 \times 10^{-3} \text{ m}^2$$

$$d = 2 \text{ mm}$$

$$C_1 = \frac{\kappa \epsilon_0 A}{d} = \frac{3(8.85 \times 10^{-12})(5 \times 10^{-3})}{2 \times 10^{-3}}$$

$$C_2 = \frac{\epsilon_0 A}{d} = \frac{8.85 \times 10^{-12} \times 5 \times 10^{-3}}{2 \times 10^{-3}}$$

$$C_1 = 3(2.2125 \times 10^{-11})$$

$$C_2 = 2.21 \times 10^{-11} \text{ F}$$

$$= 6.64 \times 10^{-11} \text{ F}$$

$$= 22.1 \text{ pF}$$

$$= 66.4 \text{ pF}$$

$$q_2 = C_2 V = (22.1 \text{ pF})(10 \text{ V})$$

$$= 221 \text{ pC}$$

$$q_1 = C_1 V = (66.4 \text{ pF})(10)$$


$$= 664 \text{ pC}$$

$$q_{\text{tot}} = q_1 + q_2 = 664 + 221 = 885 \text{ pC}$$

$$q_{\text{tot}} = C_{eq} V = (C_1 + C_2) V = (22.1 \text{ pF} + 66.4 \text{ pF})(10) = 885 \text{ pC}$$

(1)

(25-18)

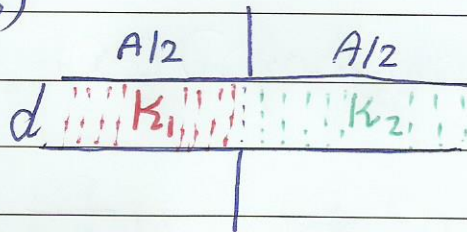

$$A = 5.56 \text{ cm}^2$$

$$d = 5.56 \text{ mm}$$

$$K_1 = 7, K_2 = 10$$

$C_{eq} ?$

Could be considered
2 Capacitors in Parallel

$$C_1 = \frac{K_1 \epsilon_0 A/2}{d}$$

$$C_2 = \frac{K_2 \epsilon_0 A/2}{d}$$

$$C_1 = \frac{K_1 \epsilon_0 A}{2d}$$


$$C_2 = \frac{K_2 \epsilon_0 A}{2d}$$

$$C_{eq} = C_1 + C_2 = \frac{K_1 \epsilon_0 A}{2d} + \frac{K_2 \epsilon_0 A}{2d}$$

$$= \frac{\epsilon_0 A}{d} \left(\frac{K_1 + K_2}{2} \right) = \frac{(8.85 \times 10^{-12}) (5.56 \times 10^{-4})}{5.56 \times 10^{-3}} \left(\frac{7+10}{2} \right)$$

$$= 8.85 \times 10^{-13} \left(\frac{17}{2} \right) = 7.52 \times 10^{-12} \text{ F}$$

$$C = 7.52 \text{ pF}$$

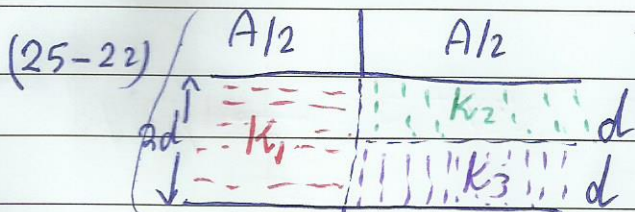

$$C_1 = \frac{K_1 \epsilon_0 A/2}{2d}$$

$$A = 12.5 \text{ cm}^2$$

$$2d = 7.12 \text{ mm}$$

$$K_1 = 21, K_2 = 42, K_3 = 58$$

$$C_1 = \frac{K_1 \epsilon_0 A}{4d} = \frac{K_1}{2} \left(\frac{\epsilon_0 A}{2d} \right)$$

$$= \frac{K_1}{2} \left(\frac{8.85 \times 10^{-12} \times 12.5 \times 10^{-4}}{7.12 \times 10^{-3}} \right)$$

$$= \frac{21}{2} (1.554 \times 10^{-12})$$

$$C_1 = 1.63 \times 10^{-11} \text{ F}$$

$$C_2 = \frac{K_2 \epsilon_0 A/2}{d} = \frac{K_2 \epsilon_0 A}{2d}$$

$$C_3 = \frac{K_3 \epsilon_0 A/2}{d} = \frac{K_3 \epsilon_0 A}{2d}$$

$$C_2 = K_2 \left(\frac{\epsilon_0 A}{2d} \right) = 42 (1.554 \times 10^{-12}) = 6.53 \times 10^{-11} \text{ F}$$

$$C_3 = K_3 \left(\frac{\epsilon_0 A}{2d} \right)$$

$$= 58 (1.554 \times 10^{-12})$$

$$= 9 \times 10^{-11} \text{ F}$$

$$C_1 = 16.3 \text{ pF}$$

$$C_2 = 65.3 \text{ pF}$$

$$C_3 = 90 \text{ pF}$$

(2)


$$C_2 + C_3 \text{ in Series} \Rightarrow \frac{1}{C_{23}} = \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_{23}} = \frac{1}{65.3} + \frac{1}{90} \Rightarrow C_{23} = \frac{(65.3)(90)}{65.3 + 90} = 37.8 \text{ pF}$$


C_{23} is in Parallel with C_1

$$C_{231} = C_{23} + C_1 = 37.8 + 16.3$$

$$C_{231} = 54.14 \text{ pF}$$

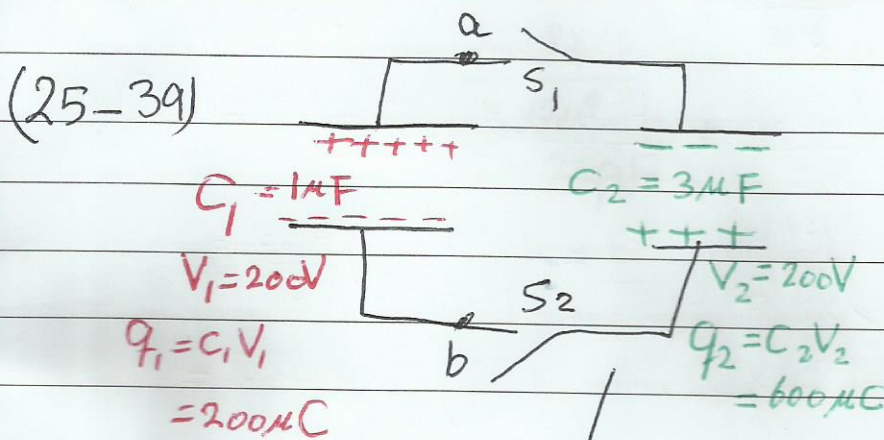

After closing S_1 & S_2

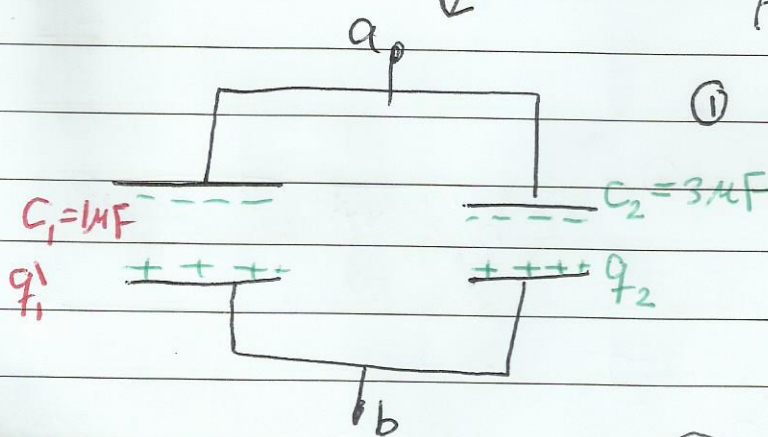

$$\textcircled{1} V_{ab} = V_1' = V_2'$$

$$V_{ab} = \frac{Q_1'}{C_1} = \frac{Q_2'}{C_2}$$

$$\frac{Q_{\text{tot}}}{C_{\text{eq}}} = \frac{Q_1'}{1} = \frac{Q_2'}{3}$$

$$\frac{400}{C_1 + C_2} = \frac{Q_1'}{1} = \frac{Q_2'}{3}$$

$$\frac{400}{4} = 100\text{V} = \frac{Q_1'}{1} + \frac{Q_2'}{3}$$

$$\textcircled{2} Q_{\text{before}} = Q_{\text{after}}$$

$$Q_1 + Q_2 = Q_1' + Q_2'$$

$$600 + 200 = Q_1' + Q_2'$$

$$400 = Q_1' + Q_2'$$

$$Q_1' = 100 \mu\text{C} \Rightarrow Q_2' = 3(100) = 300 \mu\text{C}$$

$$V_{ab} = 100\text{V}$$

(25-45)

$$R = 3 \text{ mm} \quad \left(\overset{\curvearrowright}{R} \right) + \left(\overset{\curvearrowright}{R} \right) = \left(\overset{\curvearrowright}{R'} \right) \quad \leftarrow \text{Mass}_i = \text{Mass}_f$$
$$\frac{4}{3} \pi R^3 + \frac{4}{3} \pi R^3 = \frac{4}{3} \pi R'^3$$

$$2 \left(\frac{4}{3} \pi R^3 \right) = \frac{4}{3} \pi R'^3 \Rightarrow R'^3 = 2 R^3$$

$$R' = \sqrt[3]{2} R = 1.26 R = 1.26 (3 \times 10^{-3})$$

$$R' = 3.78 \text{ mm} = 3.78 \times 10^{-3} \text{ m}$$

$$C' = 4 \pi \epsilon_0 R' = 4 \pi \epsilon_0 (1.26 R)$$

$$= \frac{3.78 \times 10^{-3}}{9 \times 10^9} = 4.2 \times 10^{-13} \text{ F}$$

$$= 0.42 \text{ pF}$$