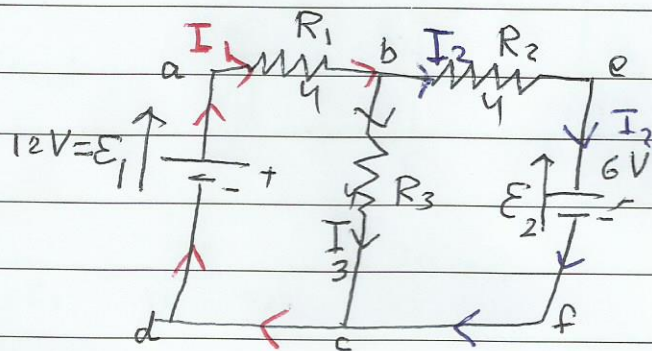


# Chapter 27 - Discussion

Q7-2)  $\mathcal{E}_1 = 12V$ ,  
 $\mathcal{E}_2 = 0.5\mathcal{E}_1 = 6V$   
 $R_1 = R_2 = R_3 = 4\Omega$

find  $I_1, I_2, I_3$ ?



At point  $\odot$   $\sum I_{in} = \sum I_{out}$

$$I_1 = I_2 + I_3 \quad (1)$$

$$\sum V_{abcda} = 0 \Rightarrow -I_1 R_1 + -I_3 R_3 + \mathcal{E}_1 = 0$$

$$\mathcal{E}_1 = I_1 R_1 + I_3 R_3$$

$$12 = 4I_1 + 4I_3$$

$$3 = I_1 + I_3 \quad (2)$$

$$\sum V_{befcb} = 0 \Rightarrow -I_2 R_2 + -\mathcal{E}_2 + I_3 R_3 = 0$$

$$\mathcal{E}_2 = I_3 R_3 - I_2 R_2$$

$$6 = 4I_3 - 4I_2 \quad (3)$$

Put (1) in (2)  $\Rightarrow 3 = (I_2 + I_3) + I_3$

$$3 = I_2 + 2I_3 \quad (2')$$

multiply (2') by 4  $\Rightarrow 12 = 4I_2 + 8I_3 \quad (2'')$

$$6 = -4I_3 + 4I_3 \quad (3) \text{ Add}$$

$$18 = 12I_3$$

$$I_3 = \frac{18}{12} = 1.5A$$

from (2)  $I_1 = 3 - I_3 = 3 - 1.5 = 1.5A$

$$I_1 = 1.5A$$

from (1)  $I_2 = I_1 - I_3 = 1.5 - 1.5 = 0$


$$I_2 = 0$$



(27-a)  $R_1 = 10k\Omega$ ,  $R_2 = 15k\Omega$ ,  $C = 0.4\mu F$

$E = 20V$

First: Closing S (switch) for along time

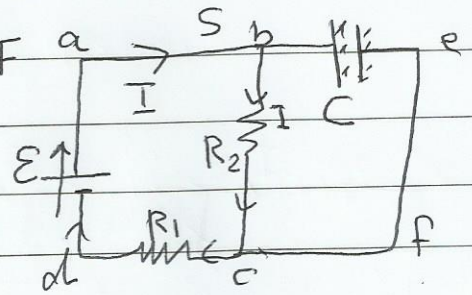

$\sum V_{abcbda} = 0 \Rightarrow$

$-IR_2 + IR_1 + E = 0 \Rightarrow I = \frac{E}{R_1 + R_2} = \frac{20}{10 + 15} = \frac{20}{25} \text{ mA}$

$I = 0.8 \text{ mA}$

$\sum V_{befcb} = 0 \Rightarrow -\frac{Q}{C} + IR_2 = 0 \Rightarrow \frac{Q}{C} = IR_2 = 0.8(15) = 12V$

$Q = C(V) = CV = 0.4(12) = 4.8 \mu C$

at  $t=0$  the switch is opened

at  $t=0$   $\begin{cases} Q_0 = 4.8 \mu C \\ V_{c0} = 12V \end{cases}$

at any time

$V_c = V_{c0} e^{-t/R_2C}$ ,  $\tau = R_2C = 15 \times 10^3 \times 0.4 \times 10^{-6}$

$\tau = 6 \times 10^{-3} = 6 \text{ ms}$

$V_c(t) = 12 e^{-t/R_2C}$

$Q(t) = Q_0 e^{-t/R_2C} = 4.8 \times 10^{-6} e^{-t/\tau}$

$I = \frac{dQ}{dt}$

$I = Q_0 \left(-\frac{1}{R_2C}\right) e^{-t/R_2C}$

$I = \frac{4.8 \times 10^{-6}}{6 \times 10^{-3}} e^{-t/R_2C} = 0.8 \times 10^{-3} e^{-t/R_2C}$

At  $t = 4 \text{ ms} \rightarrow I = 0.8 \times 10^{-3} e^{-4/6} = 0.8 \times 10^{-3} (0.513)$

$I = 0.41 \text{ mA}$

At  $t = 4 \text{ ms}$  find  $\frac{di}{dt} = ?$

$\frac{di}{dt} = \frac{0.8 \times 10^{-3}}{R_2C} e^{-t/R_2C} = \frac{0.8 \times 10^{-3}}{6 \times 10^{-3}} e^{-t/\tau} = 0.133 e^{-t/\tau}$



$$\left. \frac{di}{dt} \right|_{t=4ms} = 0.133 e^{-4/\tau} = 0.13(0.513) = 0.067 \text{ A/s}$$

$$P_{R_2} = I^2 R_2 = [0.8 \times 10^{-3} e^{-t/\tau}]^2 [15 \times 10^3]$$

$$P_{R_2} = 9.6 \times 10^{-3} e^{-2t/\tau}$$

$$\frac{dP_{R_2}}{dt} = 9.6 \times 10^{-3} \left[ \frac{-2}{\tau} e^{-2t/\tau} \right]$$


$$= 9.6 \times 10^{-3} \left( \frac{2}{6 \times 10^{-3}} \right) e^{-2t/\tau}$$

$$\frac{dP_{R_2}}{dt} = 3.2 e^{-2t/\tau}$$

$$\left. \frac{dP_{R_2}}{dt} \right|_{t=4ms} = 3.2 e^{-2(4)/6} = 3.2 e^{-8/6} = 3.2 e^{-1.333} = 3.2(0.26359) = 0.84 \text{ Watt/s}$$

(27-14) circuit (a)

$$R_1 = R_2 = 4 \Omega$$

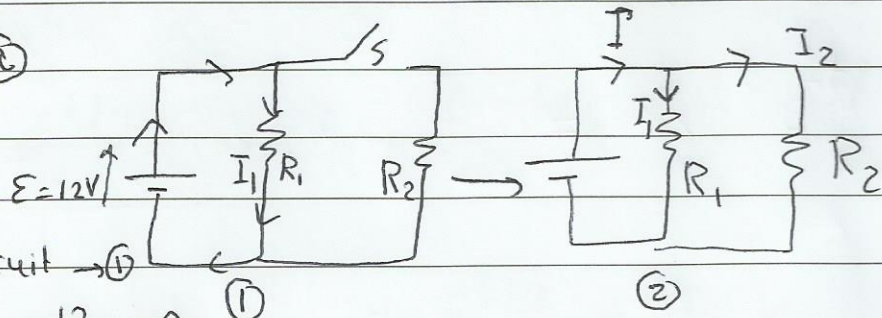

(1) open circuit (1)

$$I_1 = \frac{\mathcal{E}}{R_1} = \frac{12}{4} = 3 \text{ A}$$

$$V_1 = I_1 R_1 = 12 \text{ V}$$

(2) is closed circuit (2)  $\rightarrow$   $R_1 + R_2$  in Parallel

$$R_{12} = \frac{R_1 R_2}{R_1 + R_2} = \frac{4(4)}{4+4} = 2 \Omega$$

$$I = \frac{\mathcal{E}}{R_{12}} = \frac{12}{2} = 6 \text{ A} \rightarrow \begin{cases} I_1 = I_2 = 3 \text{ A} \\ V_1 = I_1 R_1 = 3(4) = 12 \text{ V} \end{cases}$$

$$(\Delta V_1) = V_{1, \text{closed}} - V_{1, \text{open}} = 12 - 12$$

$$= 0$$


(3)



(27-14) Circuit (b)

$$\mathcal{E} = 12V$$

$$R_1 = R_2 = R_3 = 4\Omega$$

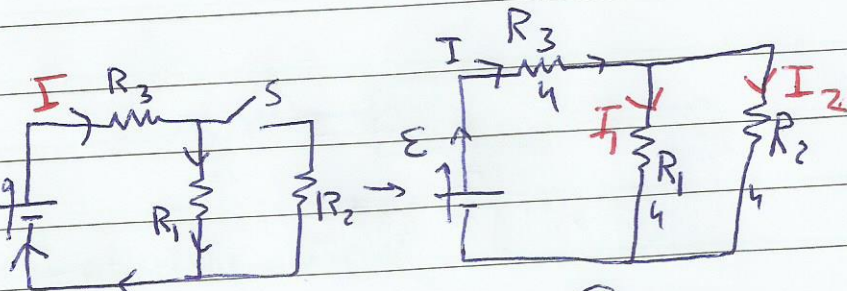

(S) is Opened circuit (1)  $\rightarrow$  (1)

$$I = \frac{\mathcal{E}}{R_1 + R_3} = \frac{12}{8} = 1.5A$$

$$V_1 = I_1 R_1 = (1.5)(4) = 6V$$

(S) is closed circuit (2)  $\rightarrow$  (2)


$$I = \frac{\mathcal{E}}{R_3 + R_{12}} = \frac{12}{4 + 2} = \frac{12}{6} = 2A$$

$$V_1 = I_1 R_1; I_1 = I_2 = 1A$$

$$V_1 = 1(4) = 4V$$

$$\begin{aligned} \Delta V_1 &= V_1(S \text{ closed}) - V_1(S \text{ opened}) \\ &= 4 - 6 \\ &= -2V \end{aligned}$$

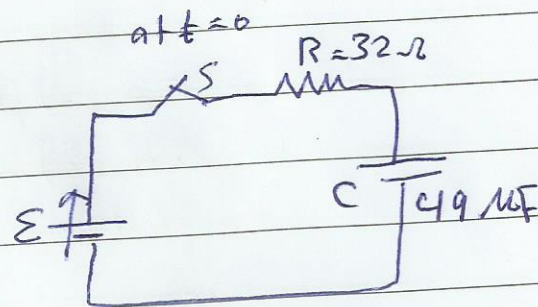(27-21)  $\tau = RC = 32(49 \times 10^{-6})$   
 $= 1.568 \times 10^{-3} s$



Find  $t$ ? When  $V_C = V_R$

$$V_C = \mathcal{E}(1 - e^{-t/\tau}) \Rightarrow V_R = \mathcal{E} e^{-t/\tau}$$

$$V_C = V_R \Rightarrow \mathcal{E}(1 - e^{-t/\tau}) = \mathcal{E} e^{-t/\tau} \Rightarrow 1 - e^{-t/\tau} = e^{-t/\tau}$$

$$1 = 2e^{-t/\tau} \Rightarrow e^{-t/\tau} = 0.5$$

$$-\frac{t}{\tau} = \ln 0.5 \Rightarrow t = -\tau \ln 0.5$$

$$t = 0.69\tau$$

$$t = 1.08 \times 10^{-3} s = 1.1 ms$$

OR

$$V_C = V_R = \frac{\mathcal{E}}{2} \Rightarrow V_R = \frac{\mathcal{E}}{2} \Rightarrow \mathcal{E} e^{-t/\tau} = \frac{\mathcal{E}}{2}$$


$$e^{-t/\tau} = 0.5 \Rightarrow t = 0.69\tau = 1.1 ms$$

(4)



(27-33)

$I = 2A$   
 $R = 2\Omega$

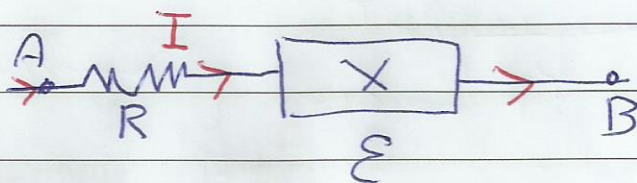

AB absorbs energy at a rate = 50W

a)  $P_{AB} = IV_{AB}$


$V_{AB} = \frac{P_{AB}}{I} = \frac{50}{2} = 25V$

$V_{AB} = 25V$

$P_R = I^2 R = (2)^2 (2) = 8 \text{ Watt}$

$\mathcal{E}$  absorbs = 42Watt this means

$I$  &  $\mathcal{E}$  are opposite

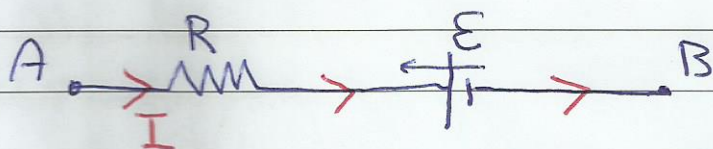

$V_A - RI - \mathcal{E} = V_B$


$(V_A - V_B) - RI = \mathcal{E} \Rightarrow$

$\mathcal{E} = 25 - 2(2) = 21V$

(27-47)  $\mathcal{E} = 1.2 \text{ kV}$ ,  $C = 6.5 \text{ mF}$

$R_1 = R_2 = R_3 = 0.73 \text{ M}\Omega$

Ⓢ closed at  $t=0$

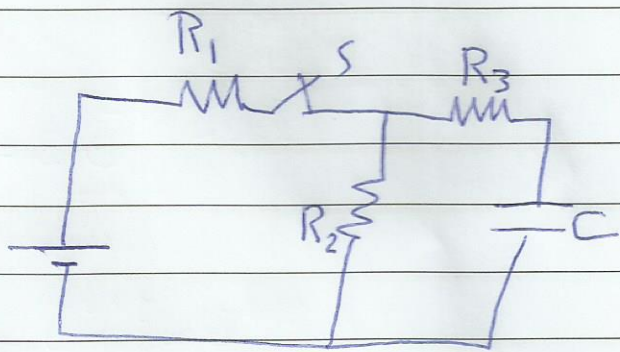

At  $t=0$   $C$  behaves as a wire (short circuit)

$R_2$  &  $R_3$  in Parallel


$R_{23} = \frac{R_2 R_3}{R_2 + R_3} = \frac{0.73 \text{ M}\Omega}{2}$

$R_{23} = 0.365 \text{ k}\Omega$

$I_1 = \frac{\mathcal{E}}{R_1 + R_{23}} = \frac{1.2 \times 10^3}{(0.73 + 0.365) \times 10^6}$

$I_1 = 1.1 \text{ mA}$   $\rightarrow I_2 = I_3 = \frac{1.1}{2} = 0.55 \text{ mA}$

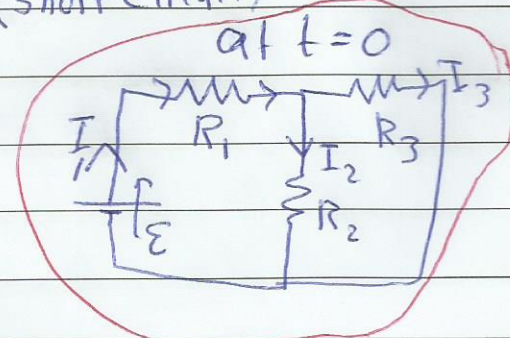$V_2 = I_2 R_2 = (0.55)(0.73) = 0.4 \text{ kV}$  Ⓢ





At  $t = \infty$  C is fully charge  
C will behave as open circuit


$$I_3 = 0$$

$$I = \frac{\mathcal{E}}{R_1 + R_2} = \frac{1.2 \times 10^3}{(0.73 + 0.73) \times 10^6}$$

$$I = 0.82 \text{ mA}$$

$$I_1 = I_2 = 0.82 \text{ mA}$$
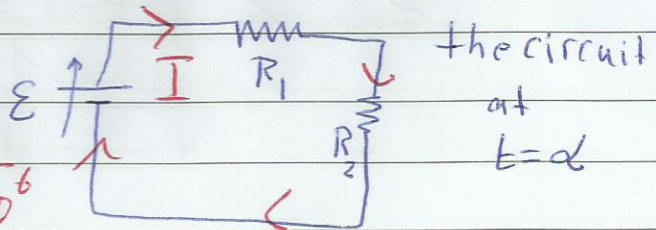
$$V_2 = I_2 R_2 = (0.82)(0.73) \\ = 0.6 \text{ kV}$$




(27-56) From the graph  $V$  vs.  $I$  you can find the slope, the slope =  $R$


$$R_1 = \frac{\Delta V}{\Delta I} = \frac{18}{3 \times 10^{-3}} = 6 \text{ k}\Omega$$

$$R_2 = \frac{\Delta V}{I} = \frac{12}{3 \times 10^{-3}} = 4 \text{ k}\Omega$$
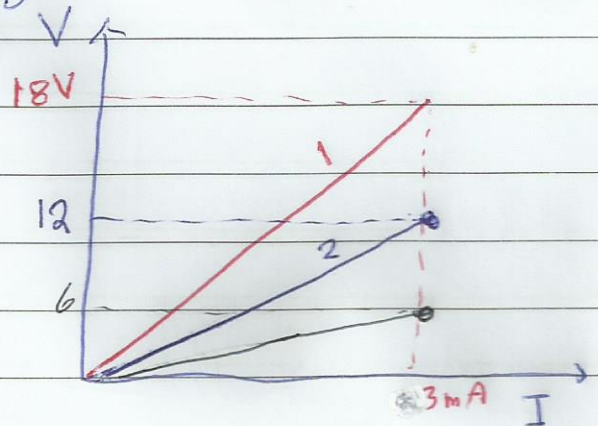
$$R_3 = \frac{\Delta V}{\Delta I} = \frac{6}{3 \times 10^{-3}} = 2 \text{ k}\Omega$$



Find  $I_2$ ?

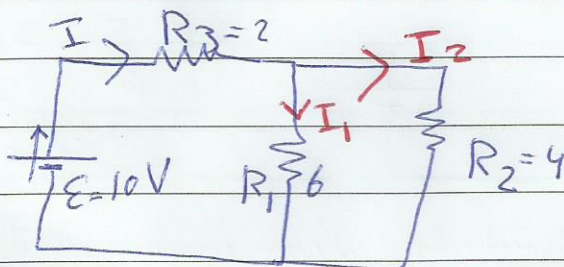

$$\frac{1}{R_{12}} = \frac{1}{6} + \frac{1}{4}$$

$$\frac{1}{R_{12}} = \frac{4 + 6}{24} = \frac{10}{24}$$

$$R_{12} = 2.4 \text{ k}\Omega$$

$$I = \frac{\mathcal{E}}{R_{12} + R_3} = \frac{10}{(2.4 + 2) \times 10^3} = 2.27 \text{ mA}$$

$$I_2 R_2 = I_1 R_1 = I R_{12}$$

$$4 I_2 = 6 I_1 = 2.27 (2.4) = 5.455 \text{ V}$$

$$I_2 = \frac{5.455}{4 \times 10^3} = 1.364 \text{ mA} = 1.4 \text{ mA}$$

(6)